

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DC Biasing Circuits

1. For the given circuit shown in figure 1. Find V_G , I_D , V_{GS} and V_{DS} . Also, determine the region of operation of the given device.

Given data: $V_{GS(th)} = 5V$, $V_{GS(ON)} = 10V$, $I_{D(ON)} = 3mA$

 


Figure 1: Mosfet Circuit

Solution:

Using zero-temperature drift biasing technique

1.) Data:

$$|A_v| = 10, V_o = 2V, f_L = 20Hz$$

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{18M\Omega}{18M\Omega + 22M\Omega} \times 40 = 18V$$

For E-NMOS transistor,

$$k_n = \frac{I_{D(ON)}}{[V_{GS(ON)} - V_{GS(th)}]^2} = \frac{3mA}{[10 - 5]^2}$$

$$k_n = 0.12 \text{ mA/V}^2$$

V_{GS} is given by,

$$V_{GS} = V_G - V_S = V_G - I_D R_S$$

$$V_{GS} = 18 - I_D(820) \quad \text{.....(1)}$$

Assuming that the given E-NMOS transistor is working in the saturation region,

$$I_D = k_n (V_{GS} - V_{GS(th)})^2$$

$$I_D = 0.12 \times 10^{-3} (V_{GS} - 5)^2 \quad \text{.....(2)}$$

Substituting Eq.(2) in Eq.(1), we get

$$V_{GS} = 18 - 820 \times 0.12 \times 10^{-3}(V_{GS} - 5)^2$$

$$V_{GS} = 18 - 0.0984(V_{GS}^2 - 10V_{GS} + 25)$$

$$V_{GS} = 18 - 0.0984V_{GS}^2 + 0.984V_{GS} - 2.46$$

$$\text{i.e. } 0.0984V_{GS}^2 + 0.016V_{GS} - 15.54 = 0$$

Solving the above quadratic equation we get,

$$V_{GS} = 12.48V \text{ or } V_{GS} = -12.64V$$

Since $V_{GS} < V_{GS(th)}$ for $V_{GS} = -12.64V$, it is rejected.

$$\therefore V_{GS} = 12.48V$$

$$\text{i.e. } I_D = k_n(V_{GS} - 5)^2 = 0.12 \times 10^{-3}(12.48 - 5)^2$$

$$\therefore I_D = 6.72mA$$

$$\text{Now, } V_{DS} = V_{DD} - I_D(R_D + R_S) = 40 - 6.72mA(3k + 820)$$

$$\therefore V_{DS} = 14.32V$$

$$\therefore V_{GS} > V_{GS(th)} \text{ \& } V_{DS} > V_{GS} - V_T \text{ i.e. } V_{DS} > (12.48 - 5)$$

\therefore the given E-NMOS device is working in the saturation region

2. Design a E-NMOS DC biasing circuit to give $I_D = 0.25mA$, $V_{DSQ} = 4V$, $V_{R_S} = 1V$. The mosfet parameters are $k'_n = 80\mu A/V^2$, $W/L = 4$, $V_{TN} = 1.2V$. The current in the bias resistors (R_1 & R_2) should be approximately $20\mu A$. $V_{DD} = +5V$ and $V_{SS} = -5V$

 


Figure 2: DC Biasing Circuit

Solution:

From figure 2, we have

$$V_{R_S} = R_S I_{DQ}$$

$$R_S = \frac{V_{R_S}}{I_{DQ}} = \frac{1V}{0.25mA} = 4k\Omega$$

Select $R_S = 3.9k\Omega_{(std)}$, $1/4 W$(L.S.V)

Applying KVL to D-S loop we get,

$$V_{DD} - I_{DQ} R_D - V_{DS} - I_{DQ} R_S + V_{SS} = 0$$

$$\therefore 5 - I_{DQ}(R_D + R_S) - 4 + 5 = 0$$

$$I_{DQ} = 0.25mA.....(given)$$

$$R_S = 3.9k\Omega \text{ \& } R_D = 20.1k\Omega$$

Select $R_D = 22k\Omega_{(std)}$, $1/4 W$(H.S.V)

$$I_D = k_n (V_{GS} - V_T)^2$$

$$I_D = \frac{k'_n}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

$$0.25mA = \frac{80\mu}{2} \times 4^2 \times (V_{GS} - 1.2)^2$$

$$1.5625 = (V_{GS} - 1.2)^2$$

$$\therefore V_{GS} = 2.45V$$

\therefore Current through bias resistor is $20\mu A$

$$R_1 + R_2 = \frac{V_{DD} + V_{SS}}{I_{R_1+R_2}} = \frac{5 + 5}{20\mu A} = 500k\Omega$$

$$V_G = \left[\frac{R_2}{R_1 + R_2} (5 + 5) \right] - 5$$

$$V_G = \frac{R_2 \times 10}{500k} - 5$$

$$V_S = I_D R_S - 5$$

Since, we know that $V_{GS} = V_G - V_S$

$$2.45 = \left[\frac{R_2 \times 10}{500k} - 5 \right] - [3.9k \times 0.25mA - 5]$$

$$2.45 = \frac{R_2}{50k} - 5 - 0.975 + 5$$

$$3.425 = \frac{R_2}{50k}$$

$$\therefore R_2 = 171.25k\Omega$$

Select $R_2 = 150k\Omega_{(std)}$, $1/4W$ (L.S.V)

$$R_1 = 328.75 k\Omega \text{}(\because R_1 + R_2 = 500k)$$

Select $R_1 = 330k\Omega_{(std)}$, $1/4W$ (H.S.V)

The designed MOSFET Biasing Circuit is shown in the figure below

 


Figure 3: Designed MOSFET Biasing Circuit

3. Design a single stage CS JFET amplifier to give output voltage of $2V$ and voltage gain of -10 . The circuit should be suitable for operation upto frequency of $20Hz$

Note: If frequency is not given, then assume it to be $50Hz$

Solution: Using zero-temperature drift biasing technique for designing the circuit.

1) Data:

$$|A_v| = 10, V_o = 2V, f_L = 20Hz$$

2) Selection of JFET:

We select n-JFET BFW11 for the datasheet with the following specifications:

$$g_{mo} = 5600\mu S, V_p = -2.5V, r_d = 50k\Omega \text{ and } I_{DSS} = 7mA$$

3) Selection of Biasing Network:

We select self-bias circuit shown in figure 4 for our design.

 


Figure 4: JFET Self-Biasing Circuit

4) Selection of Q-point:

- i) For zero-temp drift, $|V_p| - |V_{GS}| = 0.63$

$$2.5 - |V_{GS}| = 0.63$$

$$\therefore |V_{GS}| = 1.87$$

$$\text{i.e. } V_{GS} = -1.87V$$

$$\text{ii) } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2 = 7mA \left(1 - \frac{(-1.87)}{(-2.5)}\right)^2$$

$$\therefore I_D = 0.44mA$$

$$\text{iii) } g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p}\right) = 5600 \times 10^{-6} \left(1 - \frac{(-1.87)}{(-2.5)}\right)$$

$$\therefore g_m = 1.4112mA/V$$

5) Selection of R_S :

$$V_{GS} = -R_S I_D \dots \dots \dots (\text{Self-Bias})$$

$$\text{i.e. } R_S = \frac{-V_{GS}}{I_D} = \frac{-(-1.87)}{0.44 \text{mA}} = 4.25 \text{k}\Omega$$

Select L.S.V to maintain Q-point in middle of transfer curve.

$$\therefore \text{Select } R_S = 3.9 \text{k}\Omega_{(\text{std})}, 1/4 \text{W}$$

6) Selection of R_D

$$A_v = -g_m(r_d \parallel R_D)$$

Note: If R_L is given, then $A_v = -g_m(r_d \parallel R_D \parallel R_L)$

$$A_v = -g_m \left(\frac{r_d R_D}{r_d + R_D} \right)$$

$$\therefore -10 = -1.4112 \times 10^{-3} \left(\frac{50 \text{k}\Omega \times R_D}{50 \text{k}\Omega + R_D} \right)$$

Solving the above equation we get,

$$R_D = 8.256 \text{k}\Omega$$

Select H.S.V to increase the gain,

$$\therefore \text{Select } R_D = 9.1 \text{k}\Omega_{(\text{std})}, 1/4 \text{W}$$

7) Selection of R_G :

To prevent loading of preceding stage,

$$\text{Select } R_G = 1 \text{M}\Omega_{(\text{std})}, 1/4 \text{W}$$

8) Selection of V_{DD} :

$$V_{DS} \geq V_{o_{\text{peak}}} + |V_p| \dots \dots (\text{Condition for undistorted output})$$

$$V_{DS} = 1.5(V_{o_{\text{peak}}} + |V_p|)$$

$$V_{DS} = 1.5(V_{o_{\text{peak}}} + 2.5)$$

The value is multiplied by 1.5 to take care of saturation voltages, tolerance in resistance value, variation in supply voltage and device parameter variation.

$$V_{\text{rms}} = 2 \text{V}$$

$$\therefore V_{o_{\text{peak}}} = 2\sqrt{2}$$

$$\text{i.e. } V_{DS} = 1.5(2\sqrt{2} + 2.5) = 7.99 \text{V}$$

$$\therefore V_{DS} = 8 \text{V}$$

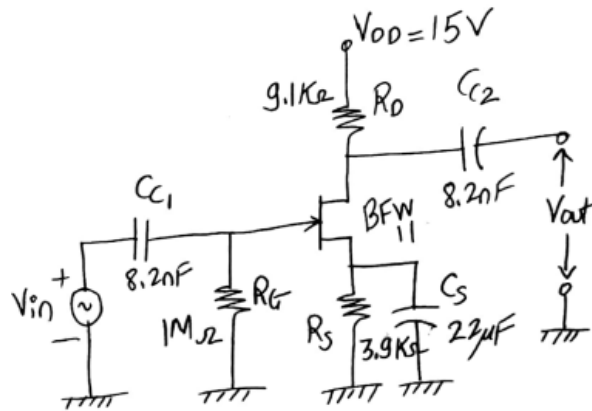


Figure 5: JFET Circuit

Applying KVL to the D-S loop shown in figure 5 we get,

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$V_{DD} = V_{DS} + I_D (R_D + R_S)$$

$$V_{DD} = 8 + 0.44 \times 10^{-3} (3.9k + 9.1k)$$

$$\therefore V_{DD} = 13.72V$$

Select $V_{DD} = 15V$

9) Selection of C_S :

$$f_L = 20Hz$$

$$X_{C_S} \leq 0.1R_S$$

$$\text{i.e. } \frac{1}{2\pi f_L C_S} \leq 0.1R_S$$

$$\text{i.e. } C_S \geq \frac{1}{2\pi f_L \times 0.1R_S} \geq \frac{1}{2\pi \times 20 \times 0.1 \times 3.9k}$$

$$\therefore C_S = 20.4\mu F$$

Select $C_S = 22\mu F / 25V \dots\dots (H.S.V)$

10) Selection of C_{C1} :

 


Figure 6: JFET Small Signal Equivalent Input Circuit

$$C_{C1} = \frac{1}{2\pi f_{L_{C_{C1}}} R_{eq}}$$

$$f_{C_{C1}} = f_L = 20Hz$$

$$R_{eq} = R_G = 1M\Omega$$

$$C_{C1} = \frac{1}{2\pi \times 20 \times 1M\Omega} = 7.957nF$$

Select $C_{C1} = 8.2nF/25V....(H.S.V)$

11) Selection of C_{C2} :

 


Figure 7: JFET Small Signal Equivalent Output Circuit

$$C_{C2} = \frac{1}{2\pi f_{L_{C_{C2}}} R_{eq}}$$

$$R_{eq} = r_d \parallel R_D + R_L$$

If R_L is not given, Select $R_L = R_i(nextstage)$

$$R_L = R_G = 1M\Omega$$

$$R_{eq} = 9.1k \parallel 50k + 1M\Omega$$

$$R_{eq} = 7.698k + 1M\Omega = 1.0077m\Omega$$

$$f_{L_{C_{C2}}} = f_L = 20Hz$$

$$C_{C2} = \frac{1}{2\pi \times 20 \times 1.077M\Omega}$$

$$C_{C2} = 7.89nF$$

Select $C_{C2} = 8.2nF/25V.....(H.S.V)$

12) The designed JFET circuit is:

 


Figure 8: Designed JFET Amplifier Circuit using Zero-temperature Drift Technique

4. For the network shown in figure 9, determine
- I_{DQ} & V_{GS}
 - V_D & V_S
 - V_{DSQ}

 


Figure 9: Circuit 1 for Numerical 4

Solution: The circuit given above is a voltage divider biased circuit.

By applying KVL at the G-S loop we get,

$$V_G - R_2 I_G - V_{GS} - I_S R_S = 0$$

But for JFET, $I_G = 0$

$$\therefore I_D = I_S$$

From equations (1), (2) and (3) we get,

$$V_G - V_{GS} - I_D R_S = 0$$

$$\therefore V_{GS} = V_G - I_D R_S$$

.....(1)

By voltage division rule,

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{110k}{110k + 910k} \times 20$$

$$V_G = 2.15V$$

Substituting the value of V_G and R_S in equation (1) we get,

$$V_{GS} = 2.15 - I_D(1.1k)$$

.....(2)

$$\text{We know that } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$\therefore I_D = 10 \times 10^{-3} \left(1 + \frac{V_{GS}}{3.5} \right)^2$$

.....(3)

Substituting equation (3) in equation (2) we get,

$$V_{GS} = 2.15 - 11 \left(1 + \frac{V_{GS}^2}{12.25} + \frac{2V_{GS}}{3.5} \right)$$

$$\therefore V_{GS} = 2.15 - \left(11 + \frac{11V_{GS}^2}{12.25} + \frac{22V_{GS}}{3.5} \right)$$

$$\therefore V_{GS} = -1.487V \text{ or } V_{GS} = -6.66V$$

Accepting the value of $V_{GS} = -1.48V$ because $V_{GS} > V_p$

$$\therefore V_{GS} = -1.487V$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2 = 10mA \left(1 - \frac{(-1.48)}{(-3.5)} \right)^2$$

$$\therefore I_D = 3.307mA$$

We know that $V_{GS} = V_G - V_S$

$$\therefore V_S = V_G - V_{GS} = 2.15 + 1.487$$

$$\therefore V_S = 3.637V$$

Applying KVL to D-S loop we get,

$$V_{DD} - I_D R_D - V_{DS} - I_S R_S = 0$$

$$\therefore V_{DS} = 20 - 3.307 \times 2.2 - 3.307 \times 1.1$$

$$\therefore V_{DS} = 9.086V$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

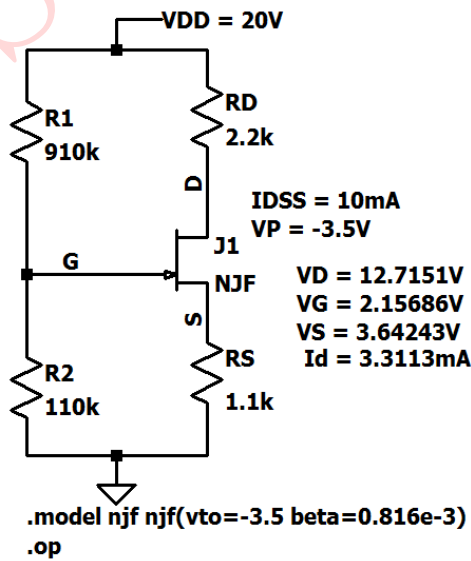


Figure 10: Circuit Schematic: Results

Comparison between observed and theoretical values:

Parameters	Simulated	Theoretical
V_G	2.15V	2.15V
V_S	3.367V	3.64V
I_D	3.31mA	3.307mA

Table 1: Question 4

KJSCE ETRX

5. For the network shown in figure 11, determine
- I_{DQ} & V_{GSQ}
 - V_{DS} & V_D

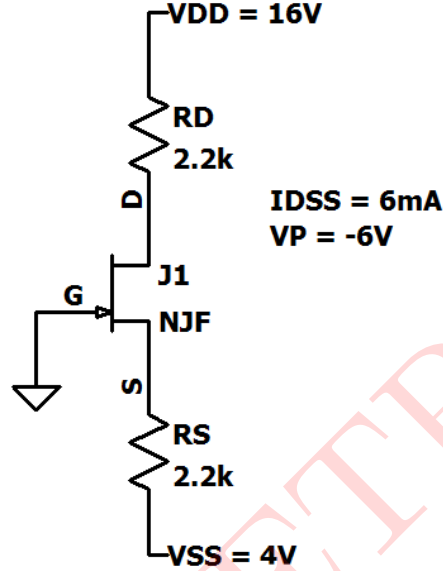


Figure 11: Circuit 1 for Numerical 5

Solution: The circuit given above is common gate configuration.

By applying KVL to the G-S loop we get,

$$0 - V_{GS} - I_S R_S + V_{SS} = 0 \quad \text{.....(1)}$$

But for JFET, $I_G = 0$

$$\therefore I_D = I_S \quad \text{.....(2)}$$

From equations (1) and (2) we get,

$$V_{GS} = V_{SS} - I_D R_S$$

$$\therefore V_{GS} = 4 - I_D(2.2k) \quad \text{.....(3)}$$

$$\text{We know that } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

Substituting the given values in the formula we get,

$$I_D = 6mA \left(1 + \frac{V_{GS}}{6}\right)^2 \quad \text{.....(4)}$$

Substituting equation (4) in equation (3) we get,

$$V_{GS} = 4 - 13.2 \left(1 + \frac{2V_{GS}}{6} + \frac{V_{GS}^2}{36}\right)$$

$$\therefore V_{GS} = 4 - 13.2 - 4.4V_{GS} - 0.3667V_{GS}^2$$

$$\text{i.e. } 0.3667V_{GS}^2 + 5.4V_{GS} + 9.2$$

Solving the above quadratic equation we get,

$$V_{GS} = -1.966V \text{ or } V_{GS} = 12.75V$$

We will select $-1.966V$ because $V_{GS} > V_p$

$$\therefore V_{GS} = -1.966V$$

Assuming the transistor to be in the saturation region,

$$I_D = I_{DSS} \left(1 - \frac{-1.966}{-6} \right)^2$$

$$\therefore I_D = 2.71mA$$

Applying KVL to D-S we get,

$$V_{DD} - I_D R_D - V_{DS} - I_S R_S + V_{SS} = 0$$

$$\therefore V_{DD} + V_{SS} - V_{DS} - I_D (R_D + R_S) = 0$$

$$\therefore V_{DS} = V_{DD} + V_{SS} - I_D (R_D + R_S) = 16 + 4 - 2.71mA(2.2k + 2.2k)$$


$$\therefore V_{DS} = 8.076V$$

$$\text{We know that, } V_D = V_{DD} - I_D R_D = 16 - 2.71mA \times 2.2k\Omega$$

$$\therefore V_D = 10.038V$$

SIMULATED RESULTS:

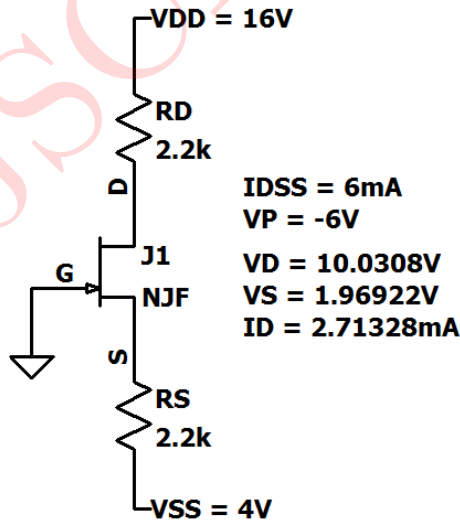Above circuit is simulated in LTspice and results are as follows:



```
.model njf njf(vto = -6V beta = 0.167e-3)
.op
```

Figure 12: Circuit Schematic: Results

Comparison between observed and theoretical values:

Parameters	Simulated	Theoretical
V_D	10.038V	10.038V
V_{DS}	8.07V	8.076V
I_D	0.00271A	2.71mA

Table 2: Question 5

KJSCE ETRX

6. For the network shown in figure 13, determine
- V_{GSQ} & I_{DQ}
 - V_{DS}
 - V_D & V_S

 


Figure 13: Circuit 1 for Numerical 6

Solution: The circuit 1 is a common gate configuration.

We know that, $V_{GS} = V_G - V_S$

Applying KVL to G-S loop we get,

$$V_{GS} = -I_D R_S + V_{SS}$$

$$\therefore V_{GS} = 10 - I_D (1.5k) \quad \text{.....(1)}$$

$$\text{Also, } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$I_D = 9mA \left(1 + \frac{V_{GS}}{3} \right)^2 \quad \text{.....(2)}$$

Substituting (2) in (1) we get

$$V_{GS} = 10 - 13.5 \left(1 + \frac{V_{GS}}{3} \right)^2$$

$$\therefore V_{GS} = \left(-13.5 - \frac{13.5V_{GS}^2}{9} - \frac{2 \times 13.5V_{GS}}{3} \right)$$

$$\therefore 1.5V_{GS}^2 + 10V_{GS} + 3.5 = 0$$

Solving the above quadratic equation we get,

$$V_{GS} = -0.3706V \text{ or } V_{GS} = -6.296V$$

We select $V_{GS} = -0.3706V$ because $V_{GS} > V_p$

$$\therefore I_D = 9mA \left(1 - \frac{0.3706}{3} \right)^2$$

$$\therefore I_D = 6.913mA$$

Applying KVL to D-S loop we get,

$$-V_{SS} + I_S R_S + V_{DS} + I_D R_D - V_{DD} = 0$$

$$V_{DS} = V_{DD} + V_{SS} - I_D(R_D + R_S) \quad (\because I_S = I_D),$$

$$\therefore V_{DS} = 20 + 10 - (6.9\text{mA})(1.8\text{k} + 1.5\text{k}) = 30 - 22.77$$

$$\therefore V_{DS} = 7.23\text{V}$$

$$\text{We know that, } V_D = V_{DD} - I_D R_D = 20 - (6.9\text{mA})(1.8\text{k}) = 20 - 12.42$$

$$\therefore V_D = 7.58\text{V}$$

$$V_{DS} = V_D - V_S$$

$$\therefore V_S = V_D - V_{DS} = 7.58 - 7.23$$

$$\therefore V_S = 0.35\text{V}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

 


Figure 14: Circuit Schematic: Results

Comparison between theoretical and simulated values is given below:

Parameters	Simulated	Theoretical
V_D	7.55V	7.58V
V_S	0.37V	0.35V
I_D	6.913mA	6.913mA

Table 3: Question 6

7. Find V_{DSQ} and I_{DQ} for the enhancement type MOSFET shown in figure 15.

 


Figure 15: Circuit 1 for Numerical 7

Solution:

Given data: $I_{DSS} = 6mA$

$$V_{GS(ON)} = 8V$$

$$V_{GS(Th)} = 3V$$

Solving for k_n we get,

$$k_n = \frac{I_{D(ON)}}{[V_{GS(ON)} - V_{GS(Th)}]^2} = \frac{6mA}{(8V - 3V)^2}$$

$$\therefore k_n = 0.24mA/V^2$$

Applying KVL to D-S loop we get,

$$V_{GS} = V_{DD} - I_D R_D = 12 - I_D(2000) \quad \text{.....(1)}$$

Assuming that the given NMOS-E is in saturation region

$$I_D = k_n(V_{GS} - V_{GS(ON)})^2 = 0.24 \times 10^{-3}(V_{GS} - 3)^2$$

Substituting (2) in (1) we get,

$$V_{GS} = 12 - 0.48(V_{GS} - 3)^2 = 12 - 0.48(V_{GS}^2 - 6V_{GS} + 9)$$

$$\therefore V_{GS} = 12 - 0.48V_{GS}^2 + 2.88V_{GS} - 4.32$$

$$\therefore 0.48V_{GS}^2 - 1.88V_{GS} - 7.68 = 0$$

Solving the above quadratic equation we get,

$$V_{GS} = 6.41V \text{ or } V_{GS} = -2.49V$$

We select $V_{GS} = 6.41V$

$$V_{DS} = V_{GS} = 6.41V$$

$$I_D = k_n(V_{GS} - 3)^2 = 0.24 \times 10^{-3}(6.41 - 3)^2$$

$$I_D = 2.79\text{mA}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

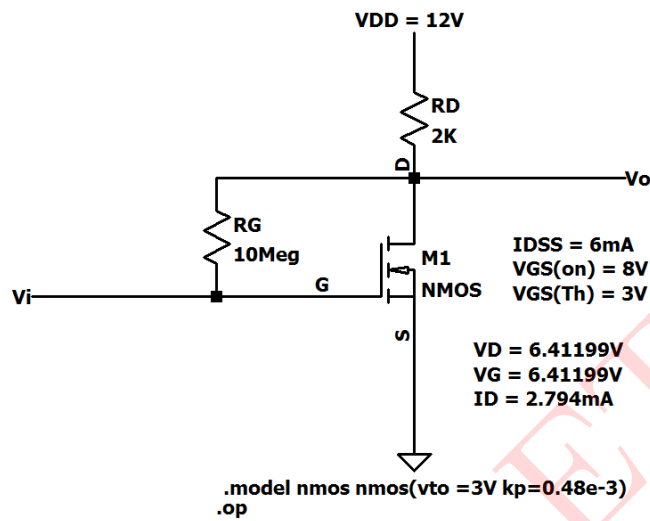


Figure 16: Circuit Schematic: Results

Comparison between observed and theoretical values:

Parameters	Simulated	Theoretical
V_{GS}	6.411V	6.41V
V_{DS}	6.411V	6.41V
I_D	2.794A	2.794mA

Table 4: Question 7

8. The pnp transistor shown in figure 17 has $\beta = 100$ and $V_{EB} = 0.7V$. Find I_B and V_{EC}

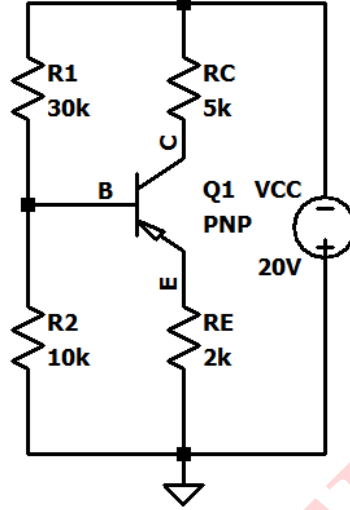


Figure 17: Circuit 1 for Numerical 8

Solution:

Given: $\beta = 100$ and $V_{EB} = 0.7V$

From figure 1 we get,

$$R_{th} = R_1 \parallel R_2$$

$$R_1 = 30k\Omega \text{ and } R_2 = 10k\Omega$$

$$R_{th} = 10k \parallel 30k$$

$$\therefore R_{th} = 7.5k\Omega$$

$$\text{We know that, } V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{10k}{10k + 30k} \times (-20)$$

$$\therefore V_{th} = -5V$$

In DC analysis, the capacitors become open circuit,

Applying KVL to E-B loop we get,

$$-V_{th} - I_B R_{th} - I_E R_E - V_{EB} = 0$$

$$-V_{th} - V_{EB} = I_B R_{th} + (1 + \beta) I_B R_E$$

$$I_B = \frac{-V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E} = \frac{-(-5)V - 0.7V}{7.5 + (101)2}$$

$$\therefore I_B = 20.52\mu A$$

$$I_C = \beta I_B = 100 \times 20.52\mu A$$

$$\therefore I_C = 2.052mA$$

Applying KVL to the E-C loop we get,

$$V_{CC} - I_C R_C - V_{EC} - I_E R_E = 0$$

$$V_{EC} = V_{CC} - I_C R_C - I_E R_E = 20 - (2.052mA)(5k) - (2.072mA)(2k)$$

$$V_{EC} = 5.596V$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

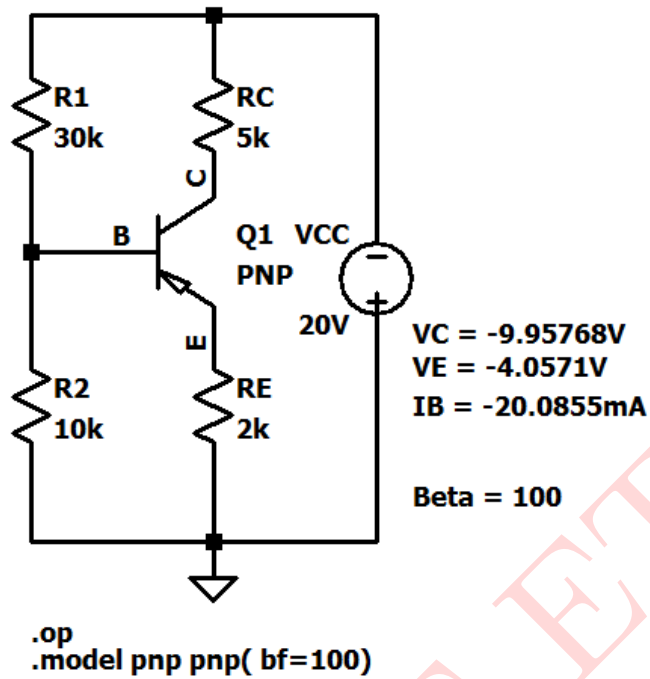


Figure 18: Circuit Schematic: Results

Comparison between theoretical and simulated values is given below:

Parameters	Simulated	Theoretical
I_B	20.0855 μ A	20.52 μ A
V_{EC}	5.9V	5.596V

Table 5: Question 8

9. The parameters of the amplifier circuit shown in figure 19 are $V_{CC} = 5V$, $R_c = 500\Omega$, $R_1 = 6.5k\Omega$, $R_E = 450\Omega$, $R_S = 500\Omega$, $R_L = 5k\Omega$ and C_1 & $C_2 = 1\mu F$, $\beta = 100$

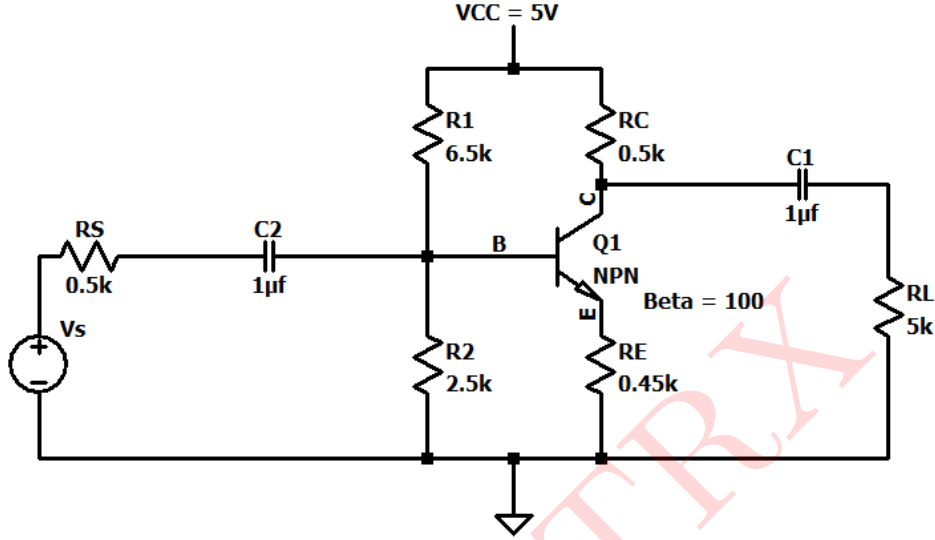


Figure 19: Circuit 1 for Numerical 9

Solution:

From figure 1 we get,

$$R_{th} = R_1 \parallel R_2$$

$$R_{th} = 6.5k \parallel 2.5k$$

$$\therefore R_{th} = 1.80k\Omega$$

$$\text{We know that, } V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{2.5}{6.5 + 2.5} \times 5$$

$$\therefore V_{th} = 1.389V$$

In DC analysis, the capacitors become open circuit,

Applying KVL to B-E loop we get,

$$V_{th} - I_B R_{th} - I_E R_E - V_{BE} = 0$$

$$V_{th} - V_{BE} = I_B R_{th} + (1 + \beta) I_B R_E$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E} = \frac{1.389V - 0.7V}{1.8 + (101)0.45} = \frac{0.689}{47.25}$$

$$\therefore I_B = 14.58\mu A$$

$$I_C = \beta I_B = 100 \times 14.58\mu A$$

$$\therefore I_C = 1.458mA$$

Applying KVL to the C-E loop we get,

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 5 - (1.458mA)(0.5k) - (1.473mA)(0.45k) \quad (\because I_E = I_B + I_C)$$

$$V_{CE} = 3.61V$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

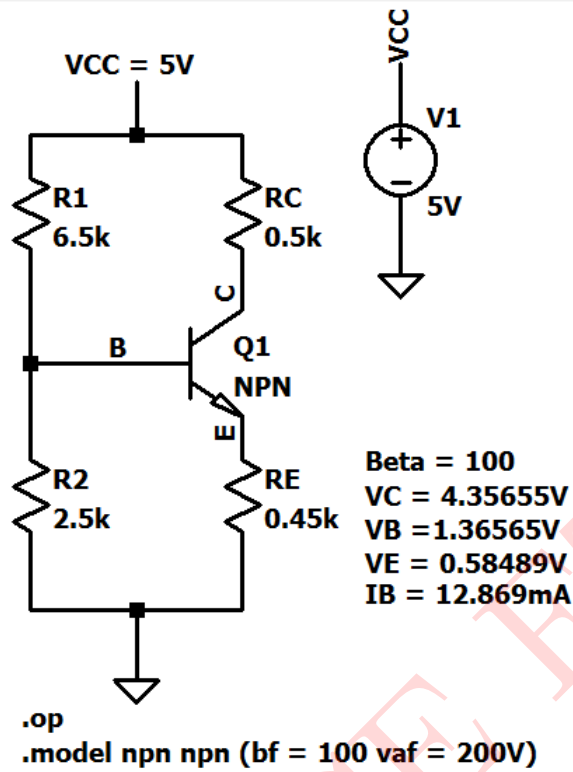


Figure 20: Circuit Schematic: Results

Comparison between theoretical and simulated values is given below:

Parameters	Simulated	Theoretical
I_B	12.869 μ A	14.58 μ A
V_{CE}	3.77V	3.61V

Table 6: Question 9
