

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Differential Amplifier Circuits**

**Numerical 1:**

Determine the following for the circuit shown in figure 1. Assume  $\beta_1 = \beta_2 = 100$

- Name of the Circuit
- Current flowing through resistor  $R_{S1}$ ,  $R_{S2}$ ,  $R_{C1}$ ,  $R_{C2}$  &  $R_E$
- $V_{C1}$ ,  $V_{C2}$ ,  $V_{CE1}$ ,  $V_{CE2}$
- Differential Voltage Gain
- Common Mode Gain
- CMRR in dB

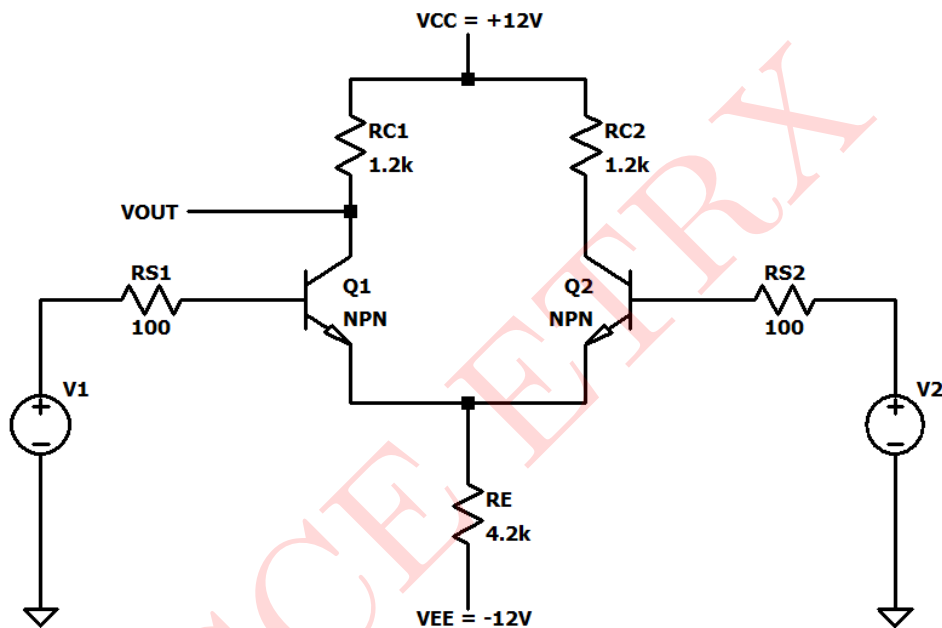


Figure 1: Circuit 1

**Solution:** Above circuit 1 is a Dual input unbalanced output (DIUO) differential amplifier.

**DC Analysis:**

$$\begin{aligned}
 I_{BQ} &= \frac{-V_{EE} - V_{BE}}{R_S + 2(1 + \beta)R_E} \\
 &= \frac{-(-12) - 0.7}{100\Omega + 2(101) \times (4.2k\Omega)} \\
 &= \mathbf{13.317\mu A}
 \end{aligned}$$

Thus the current flowing through  $R_{S1}$  &  $R_{S2}$  is  $I_{BQ} = 13.317\mu A$

$$I_{CQ} = \beta I_{BQ} = 100 \times 13.317\mu A = \mathbf{1.3317mA}$$

Thus the current flowing through  $R_{C1}$  &  $R_{C2}$  is  $I_{CQ} = 1.3317mA$

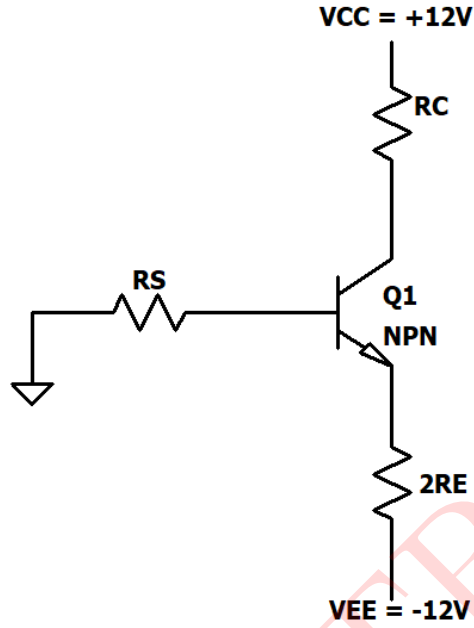


Figure 2: DC Equivalent Circuit

$$\begin{aligned}
 V_{C_1} &= V_{C_2} = V_{CC} - I_{CQ}R_C \\
 &= 12 - (1.3317mA \times 1.2k\Omega) \\
 &= 10.4V
 \end{aligned}$$

$$\therefore V_{C_1} = V_{C_2} = \mathbf{10.4V}$$

$$\begin{aligned}
 V_{CEQ} &= V_{CC} - V_{EE} - I_{CQ}(R_C + 2R_E) \\
 &= 12 - (-12) - (1.3317mA)(1.2k\Omega + 2 \times 4.2k\Omega) \\
 &= 24 - 12.784 \\
 &= \mathbf{11.216V}
 \end{aligned}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 26mV}{1.3317mA} = \mathbf{1.952k\Omega}$$

$$\begin{aligned}
 |A_d| &= \frac{\beta R_C}{2(r_\pi + R_S)} \\
 &= \frac{100 \times 1.2k\Omega}{2(1.952k\Omega + 100\Omega)} \\
 &= \mathbf{29.239}
 \end{aligned}$$

[Differential Voltage Gain]

$$\begin{aligned}
 A_{CM} &= \left| \frac{R_C}{2R_E} \right| \\
 &= \left| \frac{1.2k\Omega}{2 \times 4.2k\Omega} \right| \\
 &= \mathbf{0.1428}
 \end{aligned}$$

[Common mode gain]

$$\text{CMRR} = \left| \frac{A_d}{A_{CM}} \right| = \left| \frac{29.239}{0.1428} \right| = 204.754$$

$$\begin{aligned} \text{CMRR in dB} &= 20 \log_{10} \left( \frac{A_d}{A_{CM}} \right) \\ &= 20 \log_{10}(204.754) \\ &= \mathbf{46.22 \text{ dB}} \end{aligned}$$

### SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

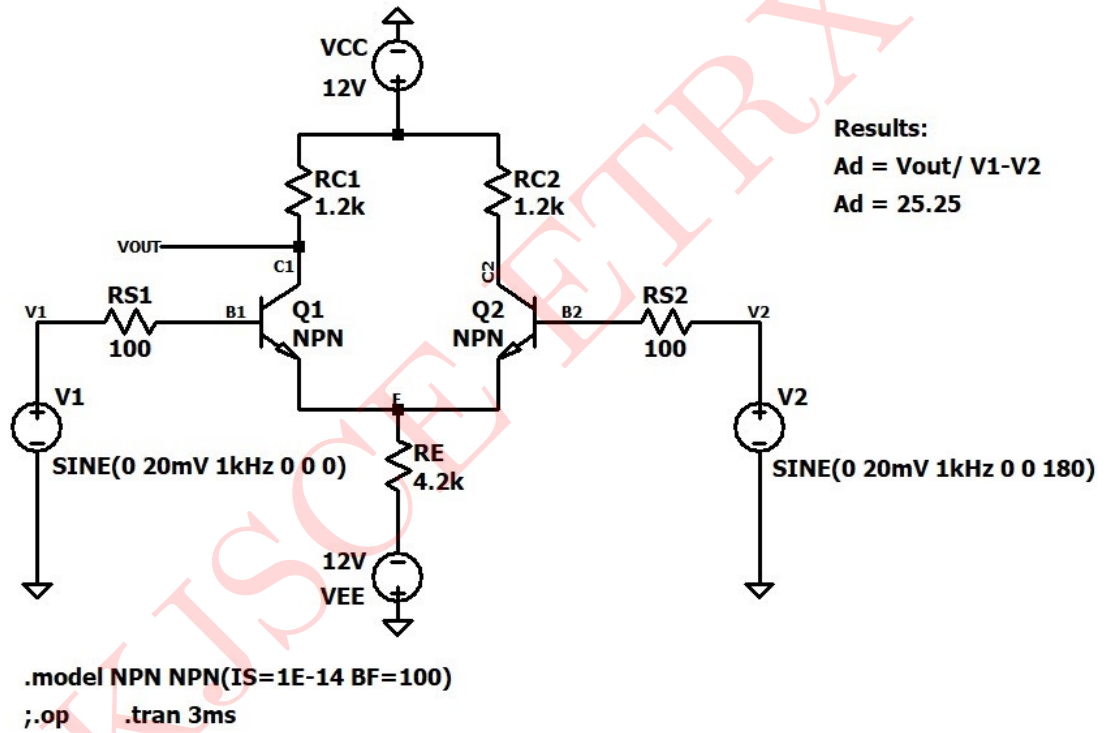


Figure 3: Circuit Schematic

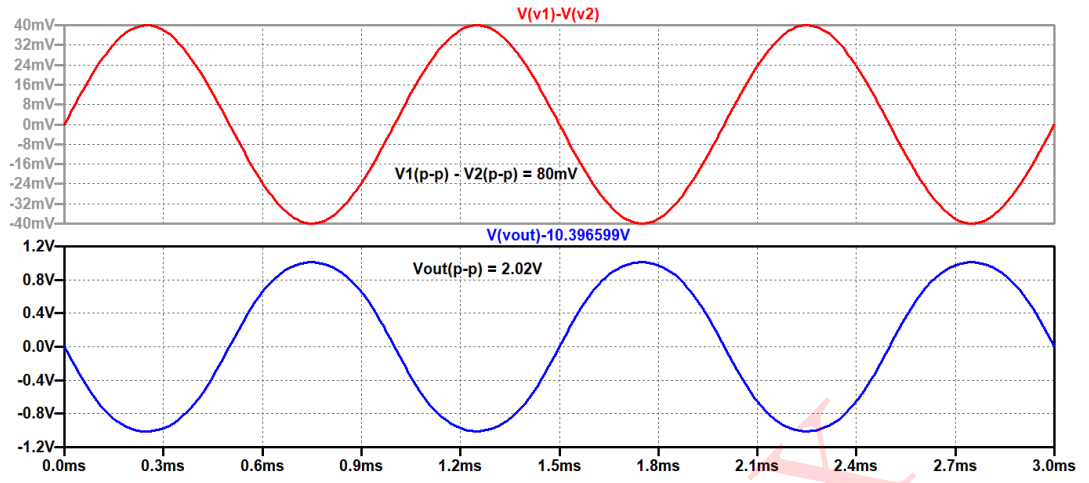


Figure 4: Input and Output waveform

#### Comparison of Theoretical and Simulated results:

Parameters	Theoretical	Simulated
$I_{C1}, I_{C2}$	$1.3317mA, 1.3317mA$	$1.3361mA, 1.3361mA$
$V_{C1}, V_{C2}$	$10.4V, 10.4V$	$10.3966V, 10.3966V$
$V_{CE1}, V_{CE2}$	$11.216V, 11.216V$	$11.06V, 11.06V$
Differential Voltage gain: $ A_d $	29.239	25.25
Commom mode Voltage gain: $A_{CM}$	0.1428	—
CMRR in dB	46.26dB	—

Table 1: Numerical 1

### Numerical 2:

Consider the differential amplifier in the figure 5. The transistor parameters are  $k_{n_1} = k_{n_2} = 50\mu A/V^2$ ,  $\lambda_1 = \lambda_2 = 0.02V^{-1}$  &  $V_{TN_1} = V_{TN_2} = 1V$

- Determine  $I_S$ ,  $I_{D_1}$ ,  $I_{D_2}$ ,  $V_{D_1}$ ,  $V_{D_2}$ ,  $V_{DS_1}$ ,  $V_{DS_2}$
- Determine differential mode voltage gain  $A_d$
- Determine common mode voltage gain  $A_{CM}$
- Determine CMRR in dB

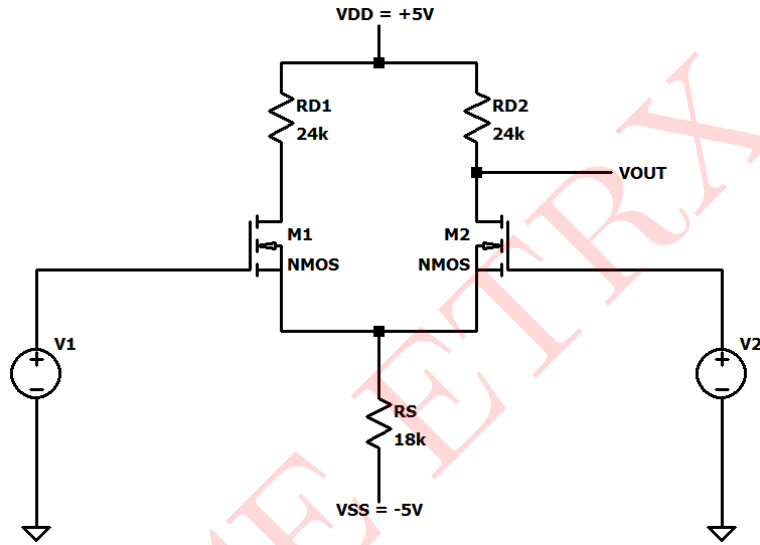


Figure 5: Circuit 2

**Solution:** The above circuit 2 is a Dual input unbalanced output differential amplifier.

**DC Analysis:**

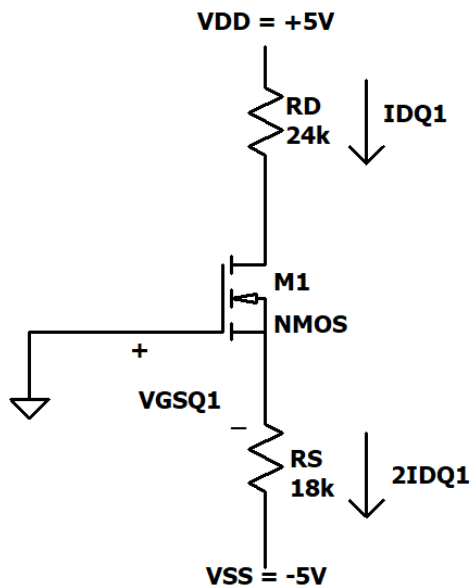


Figure 6: DC Equivalent Circuit

For a symmetrical differential amplifier,

$$V_{GSQ_1} = -V_{SS} - 2I_{DQ_1}R_S$$

$$\text{i.e } V_{GSQ_1} = 5 - 2I_{DQ_1} \times (18k\Omega) \quad \dots(1)$$

$$V_{DSQ_1} = V_{DD} - V_{SS} - I_{DQ_1}(R_D + 2R_S)$$

$$= 10 - I_{DQ_1}(24k\Omega + 2 \times (18k\Omega))$$

$$= 10 - I_{DQ_1} \times (60k\Omega) \quad \dots(2)$$

Now,

$$I_{DQ_1} = k_{n1} (V_{GSQ_1} - V_{TN1})^2 (1 + \lambda V_{DS})$$

$$= (50\mu A/V^2) (V_{GSQ_1} - 1)^2 (1 + 0.02(10 - I_{DQ_1} \times 60k\Omega))$$

$$= (50\mu A/V^2) (V_{GSQ_1} - 1)^2 (1.2 - 1200I_{DQ_1}) \quad \dots[\text{From (2)}]$$

$$= 6 \times 10^{-5} \times (V_{GSQ_1} - 1)^2 - 0.06I_{DQ_1} \times (V_{GSQ_1} - 1)^2$$

$$I_{DQ_1}(1 + 0.06(V_{GSQ_1} - 1)^2) = 6 \times 10^{-5} \times (V_{GSQ_1} - 1)^2$$

$$I_{DQ_1} = \frac{6 \times 10^{-5} \times (V_{GSQ_1} - 1)^2}{1 + 0.06(V_{GSQ_1} - 1)^2} \quad \dots(3)$$

Substituting equation(3) in equation(1),

$$V_{GSQ_1} = 5 - \frac{2 \times 18k\Omega \times 6 \times 10^{-5} \times (V_{GSQ_1} - 1)^2}{1 + 0.06(V_{GSQ_1} - 1)^2}$$

$$= \frac{5 + 0.3(V_{GSQ_1} - 1)^2 - 2.16(V_{GSQ_1} - 1)^2}{1 + 0.06(V_{GSQ_1} - 1)^2}$$

$$V_{GSQ_1} \times (1 + 0.06(V_{GSQ_1} - 1)^2) = 5 + 0.3(V_{GSQ_1} - 1)^2 - 2.16(V_{GSQ_1} - 1)^2$$

$$\text{LHS} = V_{GSQ_1} \times (1 + 0.06(V_{GSQ_1} - 1)^2)$$

$$= 0.06V_{GSQ_1} + 0.06V_{GSQ_1}(V_{GSQ_1}^2 + 1 - 2V_{GSQ_1})$$

$$= 0.06V_{GSQ_1}^3 + 1.06V_{GSQ_1} - 0.12V_{GSQ_1}^2$$

$$\text{RHS} = 5 + 0.3(V_{GSQ_1} - 1)^2 - 2.16(V_{GSQ_1} - 1)^2$$

$$= 5 + 0.3(V_{GSQ_1}^2 + 1 - 2V_{GSQ_1}) - 2.16(V_{GSQ_1}^2 + 1 - 2V_{GSQ_1})$$

$$= -1.86V_{GSQ_1}^2 + 3.14 + 3.72V_{GSQ_1}$$

$$\therefore \text{LHS} = \text{RHS}$$

$$0.06V_{GSQ_1}^3 + 1.06V_{GSQ_1} - 0.12V_{GSQ_1}^2 = -1.86V_{GSQ_1}^2 + 3.14 + 3.72V_{GSQ_1}$$

$$0.06V_{GSQ_1}^3 - 2.66V_{GSQ_1} + 1.74V_{GSQ_1}^2 - 3.14 = 0$$

$$V_{GSQ_1} = -30.4V, 2.188V, -0.786V$$

$$\text{Now, } \therefore V_{GSQ_1} > V_{TN1}$$

$$\therefore V_{GSQ_1} = \mathbf{2.188V}$$

From equation (3),

$$I_{DQ_1} = \frac{6 \times 10^{-5}(V_{GSQ_1} - 1)^2}{1 + 0.06(V_{GSQ_1} - 1)^2}$$

$$\therefore I_{DQ_1} = \mathbf{78.15\mu A}$$

From equation (2),

$$I_{DQ_1} = I_{DQ_2} = I_S = \mathbf{78.15\mu A}$$

$$V_{DSQ_1} = 10 - I_{DQ_1} \times 60k\Omega = 5.311V$$

$$V_{DSQ_1} = V_{DSQ_2} = \mathbf{5.311V}$$

$$\begin{aligned} V_{D_1} &= V_{DD} - I_{DQ_1} R_D \\ &= 5 - (78.15\mu A) \times 24k\Omega \\ &= \mathbf{3.1244} \end{aligned}$$

$$V_{D_1} = V_{D_2} = \mathbf{3.1244V}$$

$$\begin{aligned} g_{m_1} &= 2k_n(V_{GSQ_1} - V_{TN_1}) (1 + \lambda V_{DSQ_1}) \\ &= 2 \times (50\mu A/V^2) (2.188 - 1) (1 + 0.02 \times 5.311) \\ &= \mathbf{0.1314mA/V} \end{aligned}$$

Differential Voltage Gain:

$$A_d = \frac{g_m R_D}{2} = \frac{0.1314mA/V \times 24k\Omega}{2} = \mathbf{1.5768}$$

Common Mode Voltage Gain:

$$\begin{aligned} A_{CM} &= \left| \frac{g_m R_D}{1 + 2g_m R_S} \right| \\ &= \left| \frac{0.1314mA/V \times 24k\Omega}{1 + 2 \times 0.1314mA/V \times 18k\Omega} \right| \\ &= \mathbf{0.55} \end{aligned}$$

$$CMRR = \left| \frac{A_d}{A_{CM}} \right| = \mathbf{2.8669}$$

$$\begin{aligned} CMRR \text{ in dB} &= 20\log_{10}(2.8699) \\ &= \mathbf{9.157dB} \end{aligned}$$

## SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

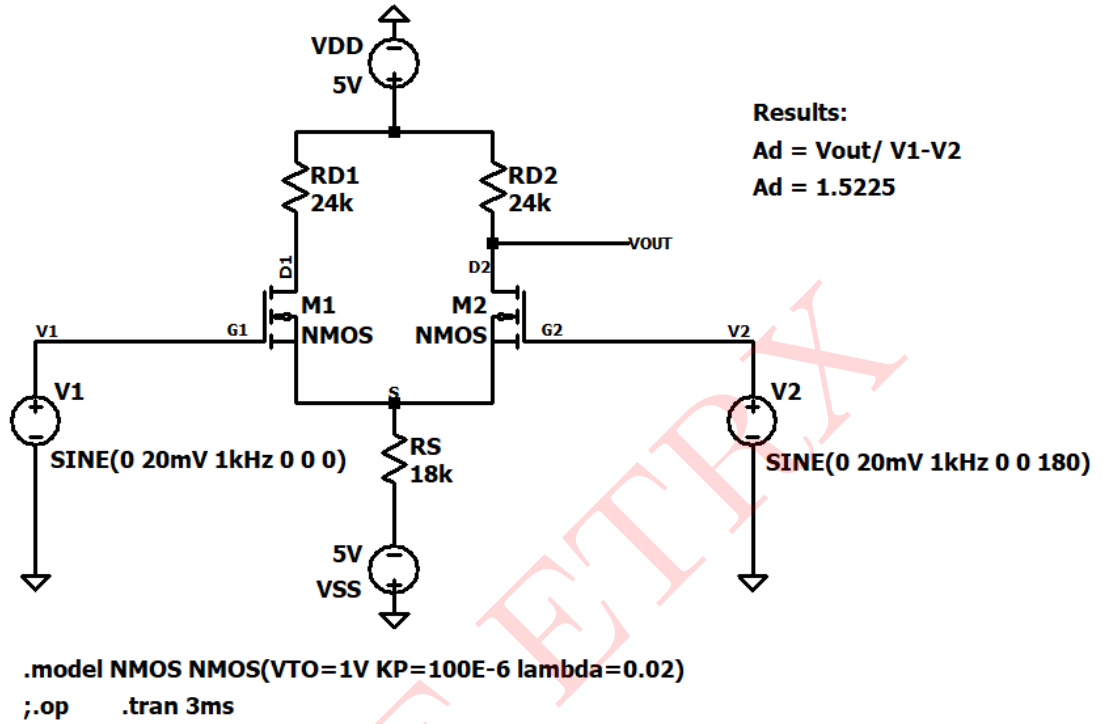


Figure 7: Circuit Schematic

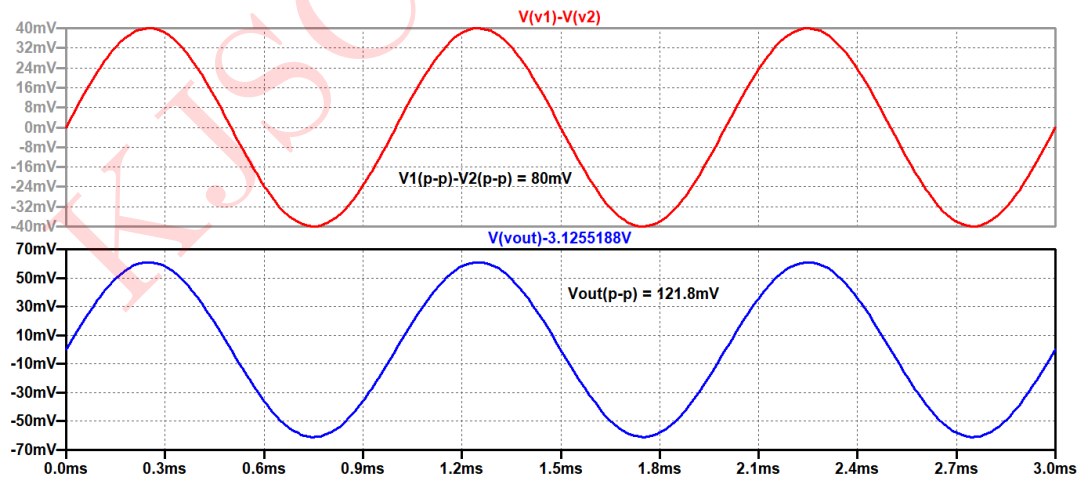


Figure 8: Input and Output waveform



**Comparison of Theoretical and Simulated results:**

Parameters	Theoretical	Simulated
$I_{D_1}, I_{D_2}$	$78.15\mu A, 78.15\mu A$	$78.10\mu A, 78.10\mu A$
$I_S$	$78.15\mu A$	$78.10\mu A$
$V_{D_1}, V_{D_2}$	$3.1244V, 3.1244V$	$3.1255V, 3.1255V$
$V_{DS_1}, V_{DS_2}$	$5.311V, 5.311V$	$5.313V, 5.313V$
Differential Voltage gain: $A_d$	1.5768	1.5225
Commom mode Voltage gain: $A_{CM}$	0.55	—
CMRR in dB	9.157dB	—

Table 2: Numerical 2

### Numerical 3:

For given differential amplifier in figure 9, find:

- DC values of  $V_{o1}$  &  $V_{o2}$
- Double ended output gain:  $\frac{V_{o1} - V_{o2}}{V_1 - V_2}$

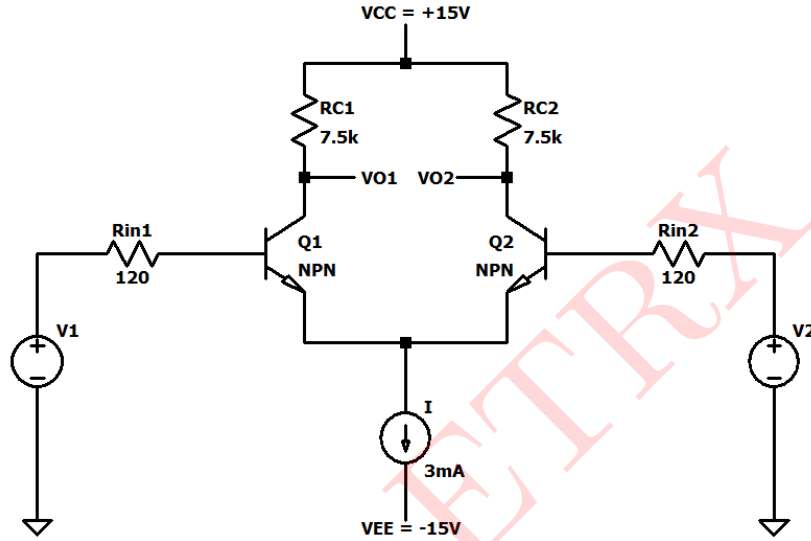


Figure 9: Circuit 3

### Solution:

$$I_{E1} = I_{E2} = \frac{I}{2} = \frac{3mA}{2} = 1.5mA$$

Now, let  $I_{C1} = I_{E1}$  &  $I_{C2} = I_{E2}$

$$\therefore I_{C1} = I_{C2} = \mathbf{1.5mA}$$

DC value of  $V_{o1} = V_{CC} - I_{C1}R_{C1}$

DC value of  $V_{o2} = V_{CC} - I_{C2}R_{C2}$

Since,  $R_{C1} = R_{C2}$  &  $I_{C1} = I_{C2}$

$$\therefore V_{o1} = V_{o2} = 15 - (1.5mA \times 7.5k\Omega)$$

$$\therefore V_{o1} = V_{o2} = \mathbf{3.75V}$$

$$V_{C1} = V_{o1} \text{ \& \; } V_{C2} = V_{o2}$$

$$\therefore V_{C1} = V_{C2} = \mathbf{3.75V}$$

Double ended output gain:  $A_d$

$$A_d = \frac{V_{o1} - V_{o2}}{V_1 - V_2}$$

means output is between two collectors

[Assuming  $V_{o1} > V_{o2}$ ; DIBO]

$$A_d = \frac{V_{o1} - V_{o2}}{V_1 - V_2} = \frac{-\beta R_C}{(r_\pi + R_{in})}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 26mV}{1.5mA} = 1.733k\Omega$$

$$A_d = \frac{-100 \times 7.5k\Omega}{(1.733k\Omega + 120\Omega)} = -404.749$$

### SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

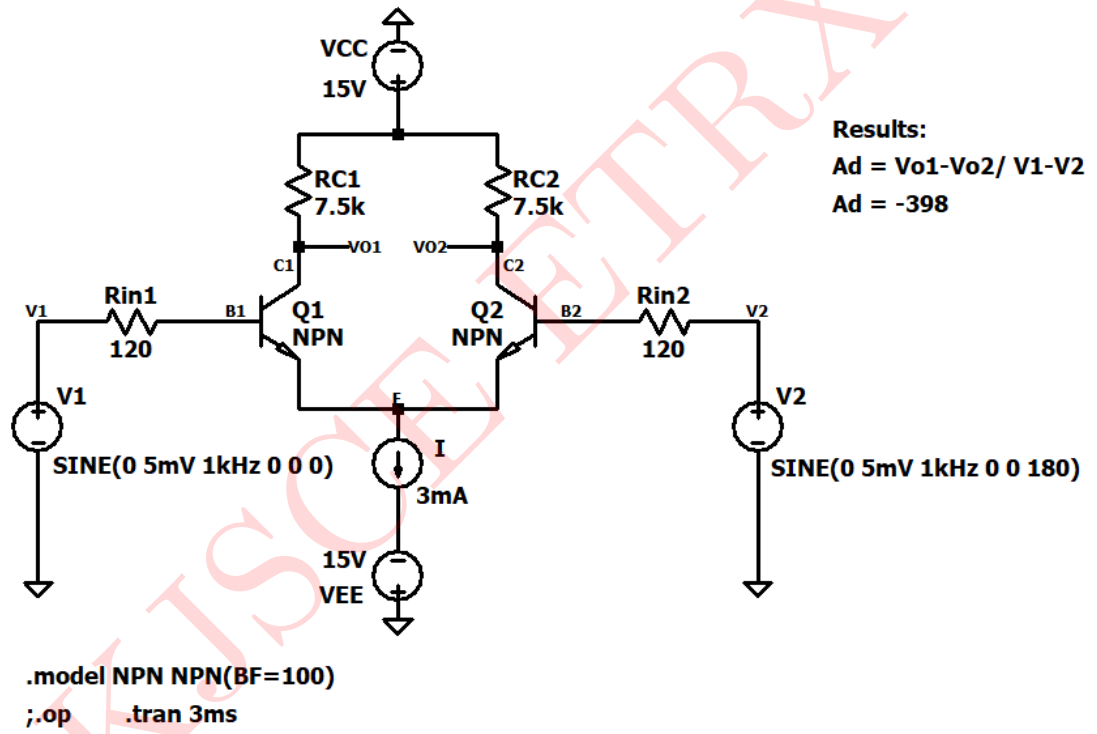


Figure 10: Circuit Schematic

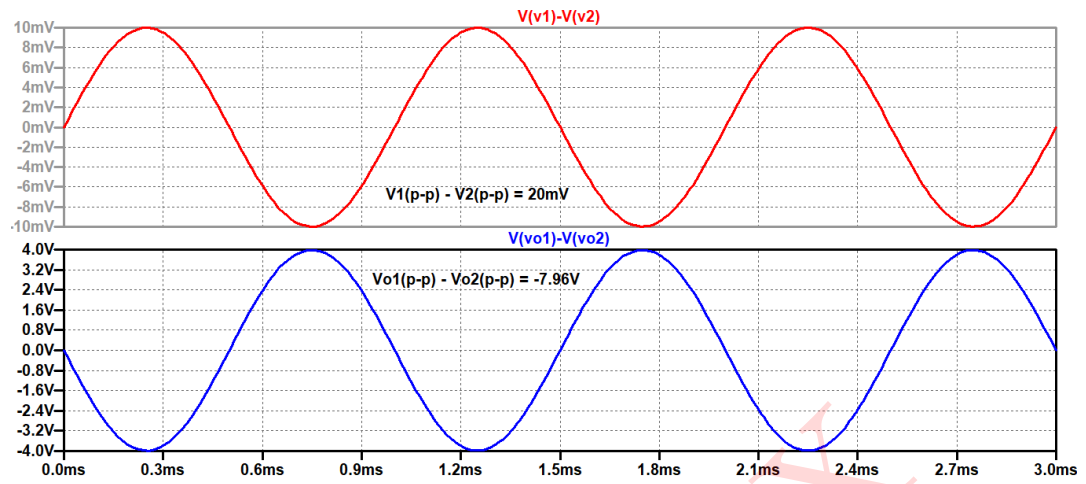


Figure 11: Input and Output waveform

#### Comparison of Theoretical and Simulated results:

Parameters	Theoretical	Simulated
$I_{C1}, I_{C2}$	$1.5mA, 1.5mA$	$1.485A, 1.485\mu A$
$V_{C1}, V_{C2}$	$3.75V, 3.75V$	$3.86V, 3.86V$
Differential Voltage gain: $A_d$	$-404.749$	$-398$

Table 3: Numerical 3

\*\*\*\*\*