

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**DIODE APPLICATIONS**

**Numerical 1:** Simulate a half wave rectifier circuit with input amplitude = 200V peak,  $f = 50$  Hz and  $R_L = 120\Omega$  using LT spice. Select diode as 1N4148. Use 10:1 step down transformer. Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diode
- Current flowing through the circuit

Also, calculate the efficiency of the Half wave rectifier circuit.

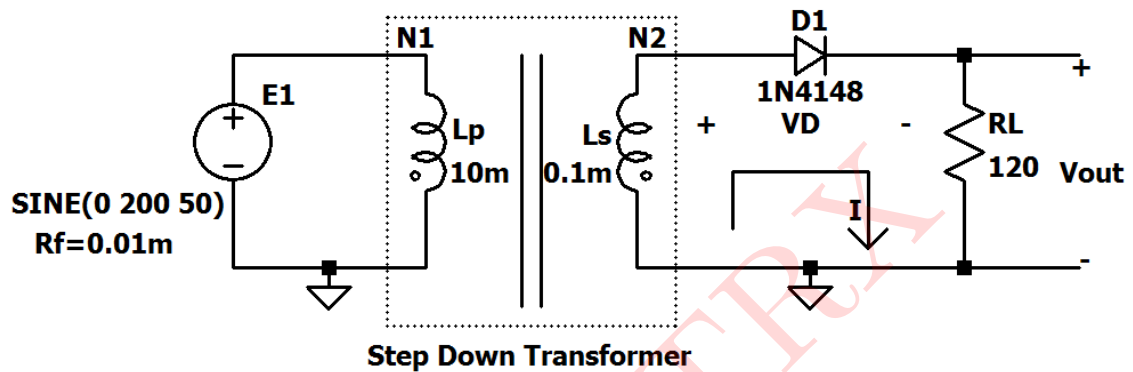


Figure 1: Circuit 1

**Solution:**

Finding primary peak voltage ( $E_1$ ):-

From the figure we can see that,

$$E_1 = 200V$$

Finding secondary peak voltage ( $E_2$ ):-

The turn ratio is given as:

$$\frac{N_1}{N_2} = \frac{10}{1}$$

$$\text{But } \frac{N_1}{N_2} = \frac{E_1}{E_2}$$

$$\therefore \frac{E_1}{E_2} = \frac{10}{1}$$

$$\begin{aligned} \therefore E_2 &= \frac{E_1 \times 1}{10} \\ &= \frac{200 \times 1}{10} \\ &= 20V \end{aligned}$$

Finding output voltage across resistor  $V_m$ :-

$$\begin{aligned} V_m &= E_2 - V_D \\ &= 20 - 0.7 \\ &= 19.3V \end{aligned}$$

Finding output current flowing through the circuit  $I_m$ :-

$$\begin{aligned} I_m &= \frac{V_m}{R_L + R_f} \\ &= \frac{19.3}{120 + 0.01 \times 10^{-3}} \\ &= 160.833\text{mA} \end{aligned}$$

Finding output DC Power ( $P_{dc}$ ) :-

$$\begin{aligned} P_{dc} &= \frac{(V_m)^2}{\pi \times R_L} \\ &= \frac{(19.3)^2}{\pi \times 120} \\ &= 0.314509\text{W} \end{aligned}$$

Finding input AC Power ( $P_{ac}$ ) :-

$$\begin{aligned} P_{ac} &= \frac{(V_m)^2}{4 \times (R_L + R_F)} \\ &= \frac{(19.3)^2}{4 \times (120 + 0.01 \times 10^{-3})} \\ &= 0.776021\text{W} \end{aligned}$$

Finding Efficiency ( $\eta$ ) :-

$$\begin{aligned} \eta &= \frac{P_{dc}}{P_{ac}} \times 100 \\ &= \frac{0.314509}{0.776021} \times 100 \\ &= 40.5284 \% \end{aligned}$$

PIV rating of diode =  $-V_m = -19.3V$

**$\therefore$  Primary peak voltage =  $E_1 = 200\text{ V}$**

**$\therefore$  Secondary peak voltage =  $E_2 = 20\text{ V}$**

**$\therefore$  Output voltage across resistor =  $V_m = 19.3\text{ V}$**

**$\therefore$  Output current through circuit =  $I_m = 160.833\text{ mA}$**

**$\therefore$  DC Power =  $P_{dc} = 0.314509\text{ W}$**

**$\therefore$  AC Power =  $P_{ac} = 0.776021\text{ W}$**

**$\therefore$  Efficiency =  $\eta = 40.4284\%$**

**$\therefore$  PIV rating of diode =  $-19.3\text{ V}$**

## SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

**Output Vm = 19.089891V**  
**Im = 159.08243mA**  
**Pdc =  $V_m \cdot V_m / \pi \cdot \pi \cdot R_1$**   
**= 0.307698W**  
**Pac =  $V_m \cdot V_m / 4(R_s + R_1)$**   
**= 0.759216W**  
**Efficiency =  $P_{dc} \cdot 100 / P_{ac}$**   
**= 40.5284%**  
**PIV rating = -19.993356V**

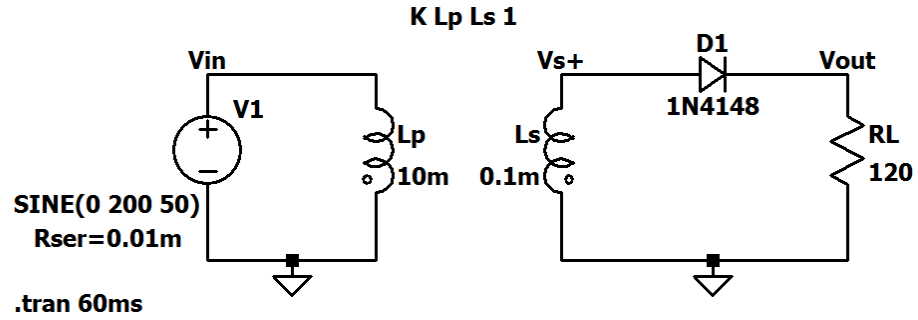


Figure 2: Circuit Schematic for circuit 1

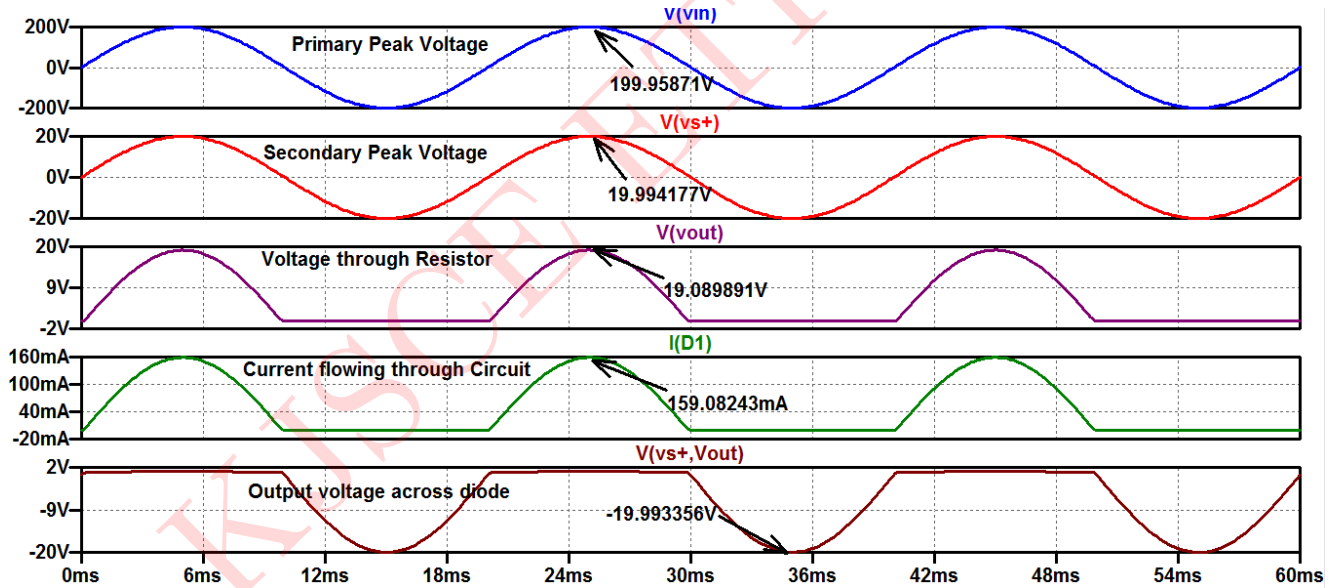


Figure 3: Simulated results for figure 2

**Comparison of Theoretical and Simulated values:-**

Parameters	Theoretical values	Simulated values
Output Peak Voltage ( $V_m$ )	19.3V	19.089531V
Output Peak Current ( $I_m$ )	160.833mA	159.08243mA
AC power	0.776021W	0.759216W
DC Power	0.314509W	0.307698W
Efficiency	40.5284%	40.5284%
PIV rating of diode	-19.3V	-19.993356V

Table 1: Numerical 1

KJSCE ETRX

**Numerical 2:** Simulate a Full wave rectifier circuit with input amplitude = 200V peak,  $f = 50$  Hz and  $R_L = 120\Omega$  using LT spice. Select diode as 1N4148. Use 10:1 step down transformer. Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diodes
- Current flowing through the diodes
- Current flowing through the circuit

Also, calculate the efficiency of the Full wave rectifier circuit.

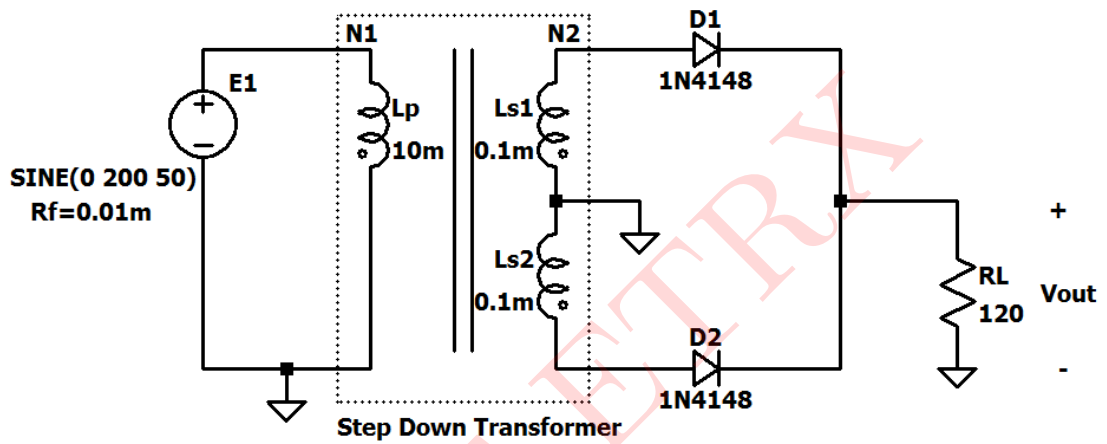


Figure 4: Circuit 2

**Solution:**

Finding primary peak voltage ( $E_1$ ):-

From the figure we can see that,

$$E_1 = 200V$$

Finding secondary peak voltage ( $E_2$ ):-

The turn ratio is given as:

$$\frac{N_1}{N_2} = \frac{10}{1}$$

$$\text{But } \frac{N_1}{N_2} = \frac{E_1}{E_2}$$

$$\therefore \frac{E_1}{E_2} = \frac{10}{1}$$

$$\begin{aligned} \therefore E_2 &= \frac{E_1 \times 1}{10} \\ &= \frac{200 \times 1}{10} \\ &= 20V \end{aligned}$$

Finding output voltage across resistor  $V_m$ :-

$$\begin{aligned} V_m &= E_2 - V_D \\ &= 20 - 0.7 \\ &= 19.3V \end{aligned}$$

Finding output current flowing through the circuit  $I_m$ :-

$$\begin{aligned} I_m &= \frac{V_m}{R_L + R_f} \\ &= \frac{19.3}{120 + 0.01 \times 10^{-3}} \\ &= 160.833mA \end{aligned}$$

Finding current through diodes :-

Current through diode 1 = Current through diode 2 =  $I_m$

Current through diode 1 = 160.833mA

Current through diode 2 = 160.833mA

Finding output DC Power ( $P_{dc}$ ) :-

$$\begin{aligned} P_{dc} &= \frac{4 \times (I_m)^2}{\pi^2} \times R_L \\ &= \frac{4 \times (0.160833)^2}{\pi^2} \times 120 \\ &= 1.258032W \end{aligned}$$

Finding input AC Power ( $P_{ac}$ ) :-

$$\begin{aligned} P_{ac} &= \frac{(I_m)^2}{2} (R_L + R_F) \\ &= \frac{(0.160833)^2}{2} (120 + 0.01 \times 10^{-3}) \\ &= 1.552035W \end{aligned}$$

Finding Efficiency ( $\eta$ ) :-

$$\begin{aligned} \eta &= \frac{P_{dc}}{P_{ac}} \times 100 \\ &= \frac{1.258032}{1.552035} \times 100 \\ &= 81.0569 \% \end{aligned}$$

When the diodes are not conducting, the voltage across the diodes is  $-2V_m$ . This is because the applied reverse voltage ( $V_m$ ) and voltage across  $R_L$  ( $V_m$ ) get developed across the resistor. So net voltage is  $-2V_m$ .

PIV rating of Diode 1 =  $-2V_m = -2 \times 19.3V = -38.6V$

PIV rating of Diode 2 =  $-2V_m = -2 \times 19.3V = -38.6V$

$\therefore$  Primary peak voltage =  $E_1 = 200V$

$\therefore$  Secondary peak voltage =  $E_2 = 20V$

$\therefore$  Output voltage across resistor =  $V_m = 19.3V$

- ∴ Output current through circuit =  $I_m = 160.833 \text{ mA}$
- ∴ Current through diode 1 =  $I_m = 160.833 \text{ mA}$
- ∴ Current through diode 2 =  $I_m = 160.833 \text{ mA}$
- ∴ DC Power =  $P_{dc} = 1.258032 \text{ W}$
- ∴ AC Power =  $P_{ac} = 1.552035 \text{ W}$
- ∴ Efficiency =  $\eta = 81.0569 \%$
- ∴ PIV rating of diode 1 =  $-38.6 \text{ V}$
- ∴ PIV rating of diode 2 =  $-38.6 \text{ V}$

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

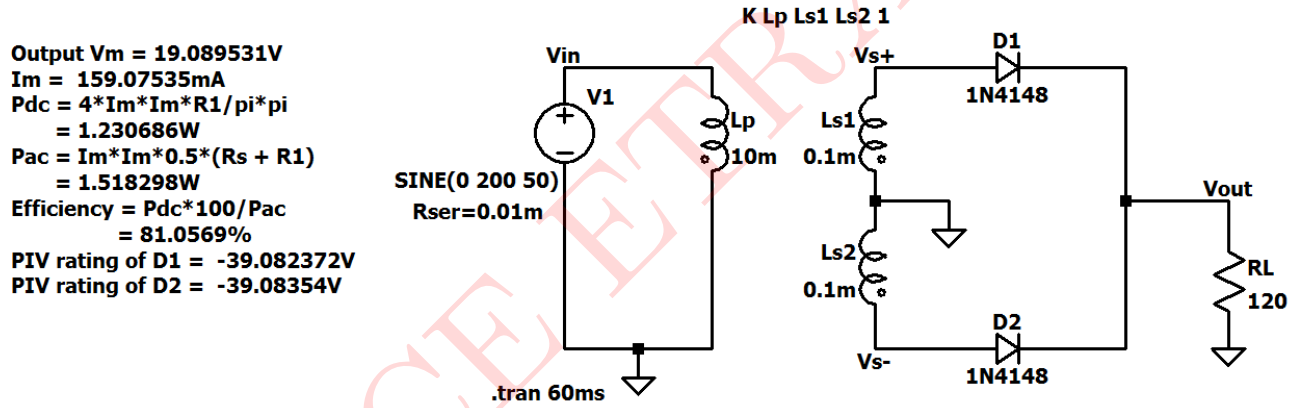


Figure 5: Circuit Schematic for circuit 2

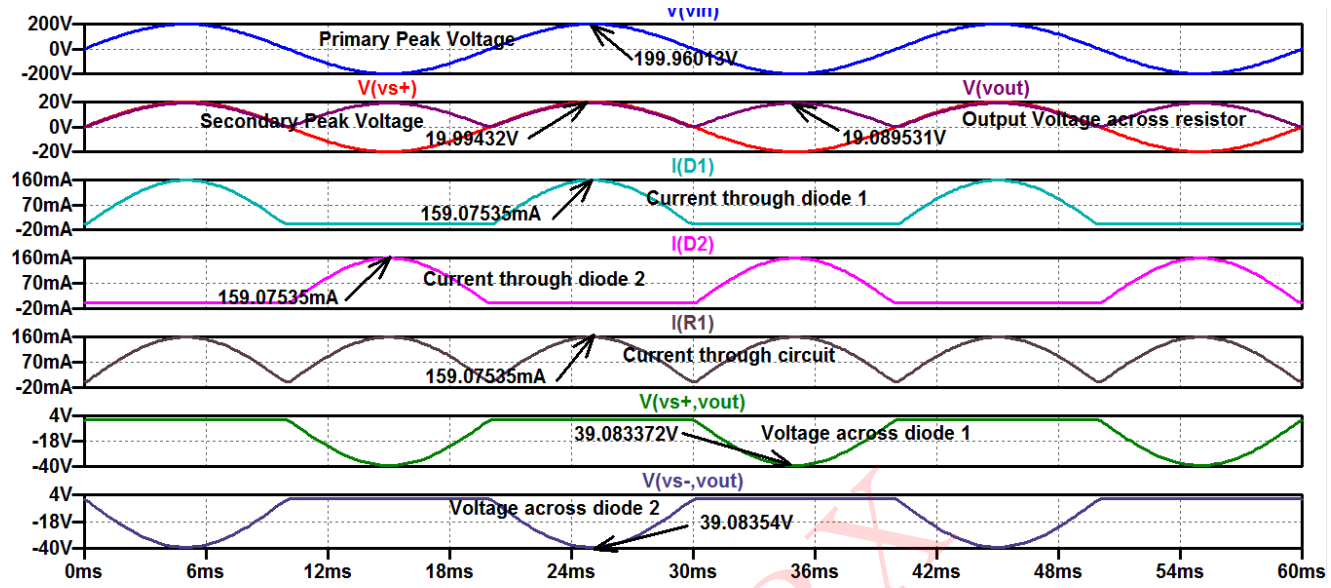


Figure 6: Simulated results for figure 5

#### Comparison of Theoretical and Simulated values:-

Parameters	Theoretical values	Simulated values
Output Peak Voltage ( $V_m$ )	19.3V	19.089531V
Output Peak Current ( $I_m$ )	160.833mA	159.07535mA
AC power	1.552035W	1.518298W
DC Power	1.258032W	1.230686W
Efficiency	81.0569%	81.0569%
PIV rating of diode 1	-38.6V	-39.082372V
PIV rating of diode 2	-38.6V	-39.08354V

Table 2: Numerical 2