

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**

**Design of single stage amplifier**

25<sup>th</sup> June, 2020

Numerical

1. Design a single RC coupled JFET amplifier for the following specifications:  
 $V_o = 2.2V$ ,  $f_l \leq 20 \text{ Hz}$ ,  $|A_v| \geq 9$   
Calculate  $A_v$ ,  $R_i$ ,  $R_o$

**Solution:**

**1) Data:**

$$V_o = 2.2V, f_l \leq 20 \text{ Hz}, |A_v| \geq 9$$

**2) Selection of JFET:**

We select n channel JFET BFW11 from the datasheet with the following specifications:  
 $g_{mo} = 5600\mu S$ ,  $V_p = -2.5V$ ,  $r_d = 50k\Omega$ ,  $I_{DSS} = 7mA$

**3) Selection of biasing circuit:**

Self bias circuit is selected to give mid point biasing

 


Figure 1: Self biased Circuit 1

**4) Selection of Q point:**

a) For mid point biasing :  $I_D = \frac{I_{DSS}}{2} = \frac{7}{2} = 3.5mA$

b)  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$

$$\frac{3.5}{7} = \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$0.5 = \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$V_{GS} = V_p \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$$

$$V_{GS} = -2.5 \left(1 - \sqrt{\frac{1}{2}}\right)$$

$$V_{GS} = -0.732V$$

c) Calculation  $g_m$ :

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p}\right)$$

$$g_m = 5600 \times 10^{-6} \left(1 - \frac{-0.732}{-2.5}\right)$$

$$g_m = 3.96m\Omega$$

**5) Selection of  $R_S$ :**

$$V_{GS} = V_G - V_S \quad (V_G = 0 \because \text{self biased})$$

$$V_{GS} = -V_S$$

$$V_{GS} = -I_D R_S$$

$$R_S = -V_{GS}/I_D = -(-0.732)/3.5mA = 209.142\Omega, 1/4 \text{ W ( H.S.V )}$$

Select  $R_S = 220\Omega, 1/4 \text{ W ( H.S.V )}$

**6) Selection of  $R_D$ :**

$$A_v = -g_m(r_d || R_D)$$

$$-9 = -3.96 \times 10^{-3}(50 \times 10^3 || R_D)$$

$$-9 = -3.96 \times 10^{-3} \left( \frac{50 \times 10^3 \times R_D}{50 \times 10^3 + R_D} \right)$$

$$R_D = 2.380k\Omega$$

Select  $R_D = 2.7k\Omega, 1/4 \text{ W ( H.S.V )}$

**7) Selection of  $R_G$ :**

Select  $R_G = 1M\Omega, 1/4 \text{ W ( H.S.V )}$

**8) Selection of  $V_{DD}$ :**

$$V_{DS} \geq V_{o(peak)} + |V_p|$$

$$V_{DS} = 1.5(V_{o(peak)} + 2.5)$$

$$V_{DS} = 1.5(2\sqrt{2} + 2.5)$$

$$V_{DS} = 8.416V$$

Applying KVL to the DS loop

$$V_{DS} = V_{DD} - I_D R_D - I_D R_S$$

$$V_{DD} = V_{DS} + I_D (R_D + R_S)$$

$$V_{DD} = 3.416 + 3.5 \times 10^{-3} (2.7 \times 10^3 + 220)$$

$$V_{DD} = 18.636V$$

Select  $V_{DD} = 20V$

### 9) Selection of $C_S$ :

$$X_{CS} \leq 0.1 R_S$$

$$\frac{1}{2\pi \times f_{LCS} C_S} \leq 0.1 R_S \quad (f_{LCS} = f_L \leq 20Hz)$$

$$C_S \geq \frac{1}{2\pi \times 0.1 R_S} \geq \frac{1}{2\pi \times 0.1 \times 220}$$

$$C_S \geq 361.715\mu F$$

Select  $C_S = 390\mu F, 25V$  ( H.S.V )

### 10) Selection of $C_{C1}$ :

$$C_{C1} = \frac{1}{2\pi \times f_{LCC1} R_{eq}} \quad (f_{LCC1} = f_L \leq 20Hz)$$

$$R_{eq} = R_G = 1M\Omega$$

$$C_{C1} = \frac{1}{2\pi \times 20 \times 1 \times 10^6}$$

$$C_{C1} = 7.9 \text{ nF}$$

Small signal equivalent circuit:

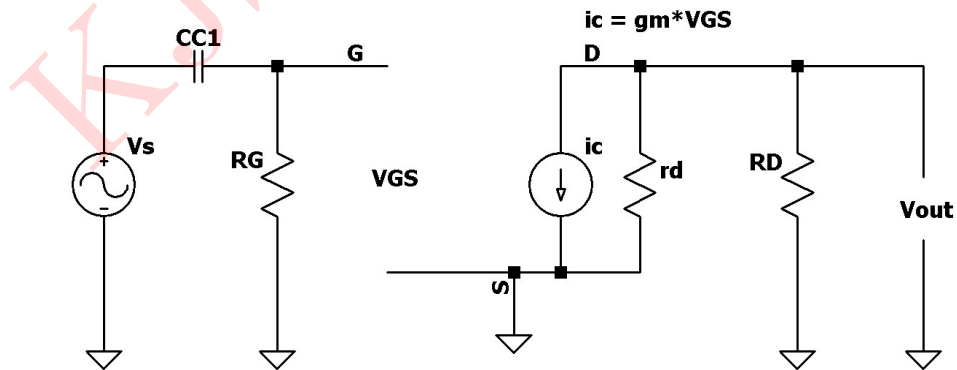


Figure 2: Small signal equivalent circuit for CC1

Select  $C_{C1} = 8.2 \text{ nF}, 25V$  ( H.S.V )

11) Selection of  $C_{C2}$ :

$$C_{C2} = \frac{1}{2\pi \times f_{LCC2} R_{eq}} \quad (f_{LCC2} = f_L \leq 20Hz)$$

$$R_{eq} = r_d || R_D = 2.7 \times 10^3 || 20 \times 10^3 = 2.56k\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 2.56 \times 10^3 \times 20}$$

$$C_{C2} = 3.107nF$$

Small signal equivalent circuit:

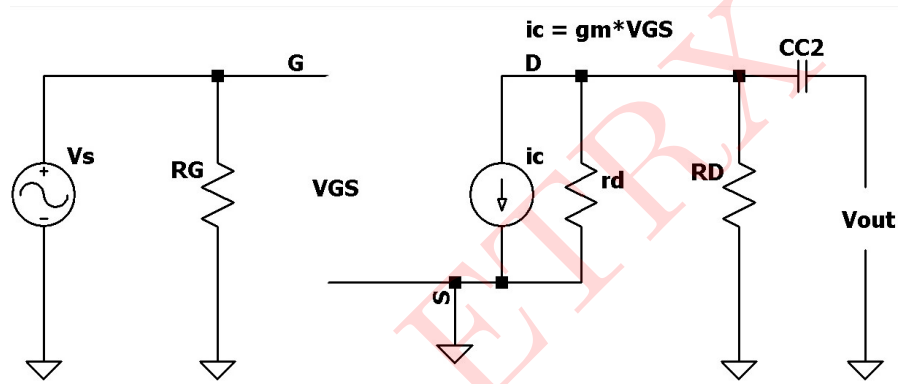


Figure 3: Small signal equivalent circuit for CC2

Select  $C_{C2} = 3.3nF$ , 25V ( H.S.V )

12) Designed Circuit is:

 


Figure 4: Designed circuit 1

## SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

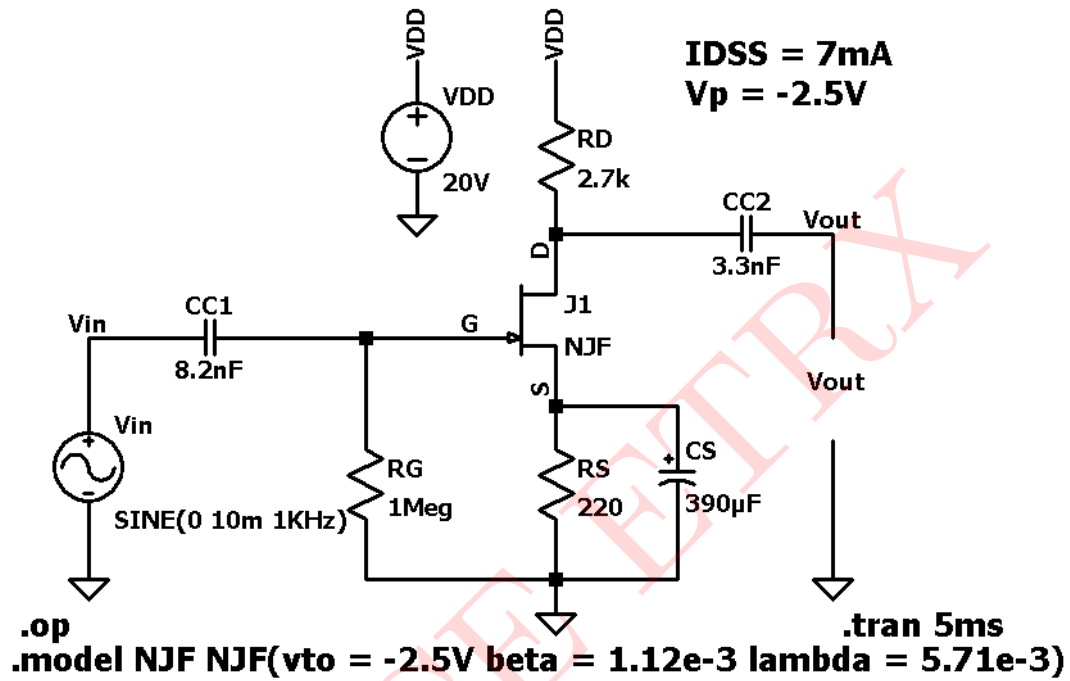


Figure 5: Circuit schematic 1

 


Figure 6: Circuit Schematic: Input Output Waveform

**Comparsion between simulated and theoretical values :**

Parameters	Simulated	Theoretical
$I_{DQ}$	3.420mA	3.5mA
$A_v$	10.418	$\geq 9$

KJSCE ETRX