

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**DC CIRCUITS**

**Numerical 1:** For the circuit shown in figure 1, find:

- a) Current  $I$
- b) Voltage between A and B ( $V_{ab}$ )

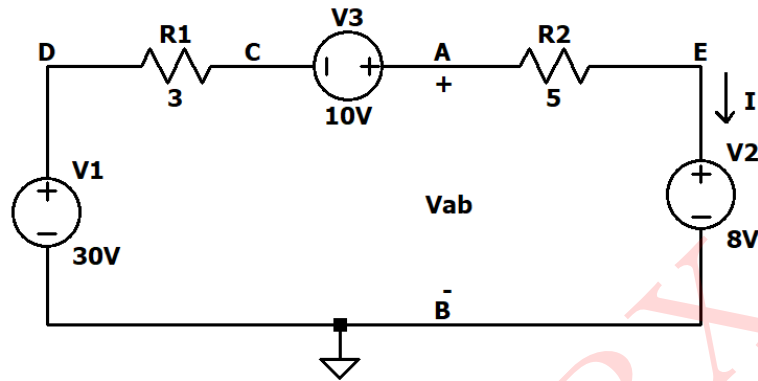


Figure 1: Circuit 1

**Solution:**

**Case 1:** To determine Current  $I$

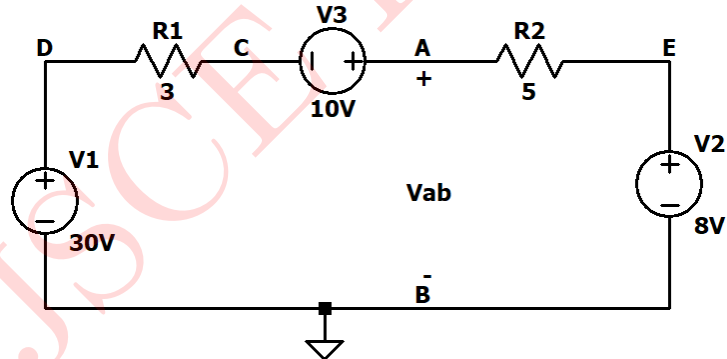


Figure 2: To determine Current  $I$

Applying KVL to the loop,

$$30 + 3I - 5I + 10 - 8 = 0$$

$$\therefore 32 - 8I = 0$$

$$\therefore 8I = 32$$

$$\therefore I = \frac{32}{8}$$

$$\therefore \text{Current } I = 4\text{A}$$

**Case 2:** To determine Voltage  $V_{ab}$

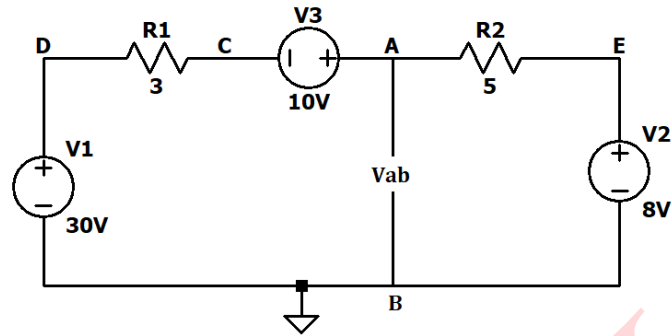


Figure 3: To determine Voltage  $V_{ab}$

Applying KVL to the second loop,

$$V_{ab} - 5I - 8 = 0 \quad \dots(1)$$

Since, we know that  $I = 4A$

Substituting the value of  $I$  in the equation (1)

$$\therefore V_{ab} - 5 \times 4 - 8 = 0$$

$$\therefore V_{ab} - 20 - 8 = 0$$

$$\therefore V_{ab} = 20 + 8$$

$$\therefore V_{ab} = 28V$$

### **SIMULATED RESULTS:**

The given circuit is simulated in LTspice and the results obtained are as follows:

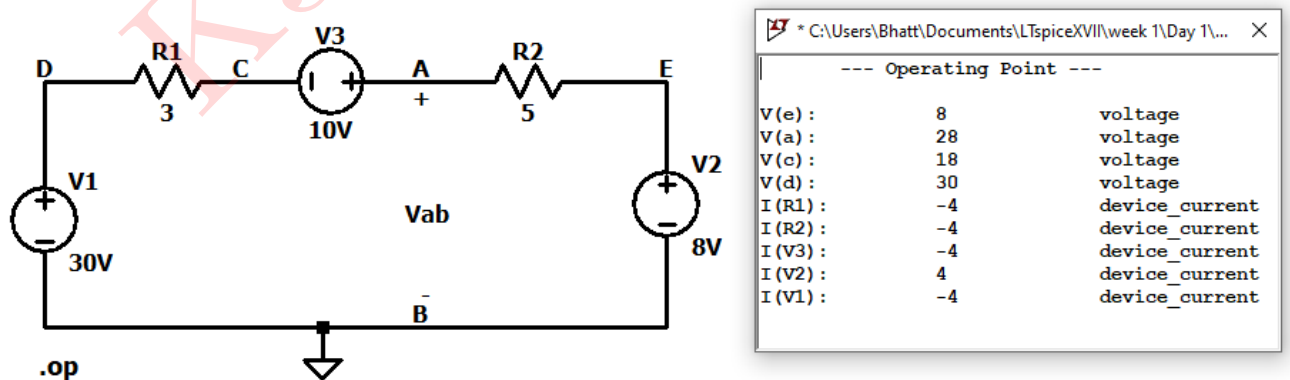


Figure 4: Circuit Schematic and Simulated Results

**Comparison of theoretical and simulated values:**

<b>Parameters</b>	<b>Theoretical Values</b>	<b>Simulated Values</b>
Current (I)	4A	4A
Voltage $V_{ab}$	28V	28V

Table 1: Numerical 1

KJSCE ETRX

**Numerical 2:** For the circuits shown in figure 5, find the equivalent resistance  $R_{eq}$

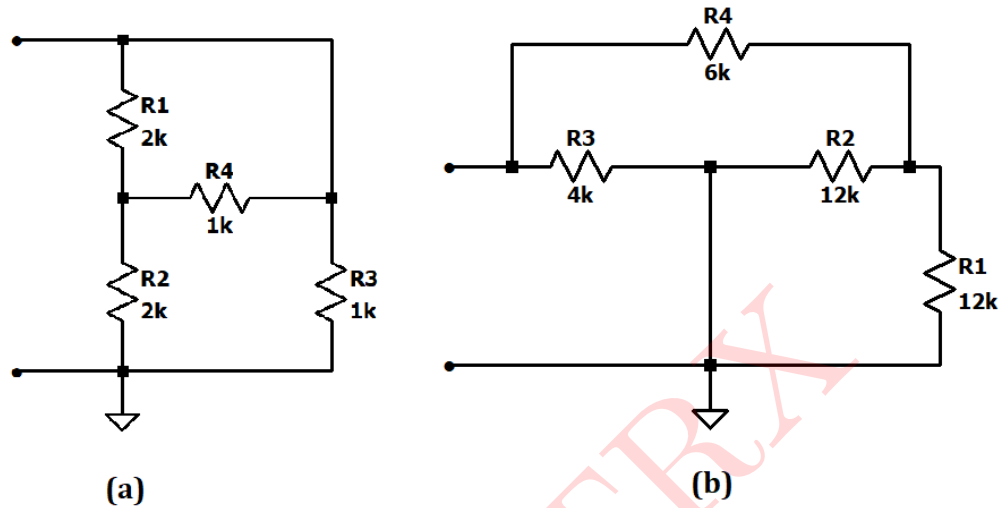


Figure 5: Circuit 2a and Circuit 2b

**Solution:**

**Case 1 : Circuit 2a**

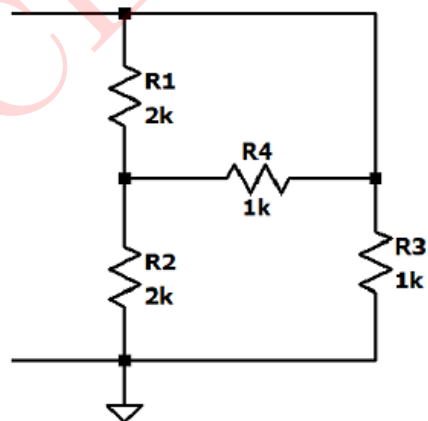


Figure 6: Circuit 2a

To get  $R_{eq}$ , we combine resistor in series and in parallel.

The resistor  $R_1 = 2\text{k}\Omega$  and  $R_2 = 2\text{k}\Omega$  are parallel.

$$\therefore 2\text{k}\Omega \parallel 2\text{k}\Omega = \frac{2}{2+1}$$

$$\therefore 2\text{k}\Omega \parallel 2\text{k}\Omega = \frac{2}{3}\text{k}\Omega = 0.666\text{k}\Omega$$

Thus, the circuit is reduced to figure 7

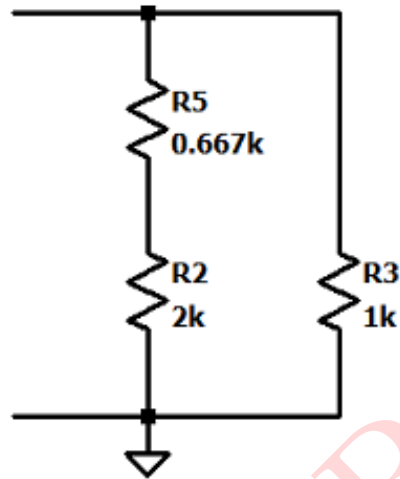


Figure 7: Modified circuit for figure 6

Now, resistors  $R_5 = 0.666 \text{ k}\Omega$  and  $R_2 = 2 \text{ k}\Omega$  are in series.

Hence, the equivalent resistance is

$$0.6667 \text{ k}\Omega + 2 \text{ k}\Omega = 2.6667 \text{ k}\Omega$$

Now, the circuit is reduced to figure 8

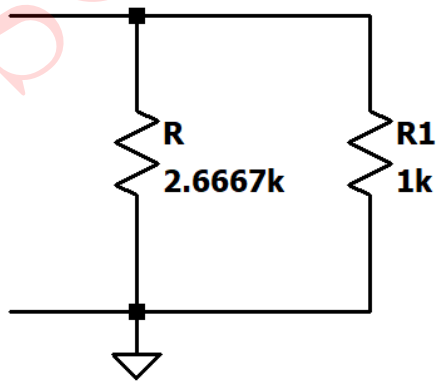


Figure 8: Modified Circuit for figure 7

Here, the resistor  $R = 2.6667 \text{ k}\Omega$  and  $R_1 = 1 \text{ k}\Omega$  are parallel.

$$\therefore 2.6667 \text{ k}\Omega \parallel 1 \text{ k}\Omega = \frac{2.6667}{2.6667 + 1}$$

$$\therefore 2 \text{ k}\Omega \parallel 1 \text{ k}\Omega = \frac{2}{3.6667} \text{ k}\Omega$$

$$\therefore 2 \text{ k}\Omega \parallel 1 \text{ k}\Omega = 0.72727 \text{ k}\Omega$$

$$\therefore R_{eq} = \mathbf{727.27 \text{ k}\Omega}$$

**Case 2 : Circuit 2b**

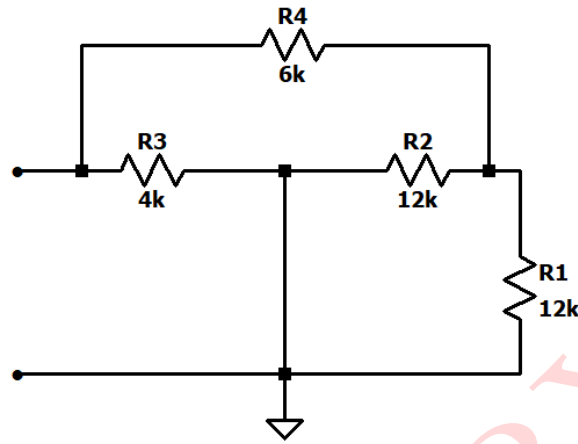


Figure 9: Circuit 2b

**Solution:**

Here the resistors  $R_1 = 12\text{ k}\Omega$ ,  $R_2 = 12\text{ k}\Omega$  and  $R_3 = 4\text{ k}\Omega$  form a delta network.

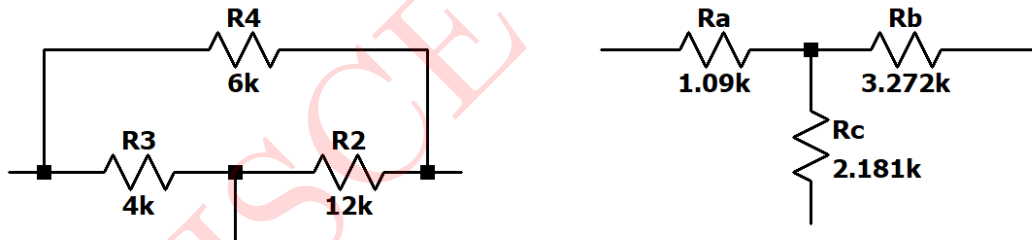


Figure 10: Star - Delta Transformation modified circuit

Therefore, using Star - Delta Transformation

The formulas are :

$$R_a = \frac{R_3 \times R_4}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 \times R_4}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_2 \times R_3}{R_1 + R_2 + R_3}$$

Substituting the values of resistors in the formula, we get

$$R_a = \frac{4 \times 6}{4 + 6 + 12}$$

$$\therefore R_a = \frac{24}{22}$$

$$\therefore R_a = \mathbf{1.0909 \text{ k}\Omega}$$

$$R_a = \frac{12 \times 6}{4 + 6 + 12}$$

$$\therefore R_a = \frac{72}{22}$$

$$\therefore R_a = \mathbf{3.2728 \text{ k}\Omega}$$

$$R_a = \frac{12 \times 4}{4 + 6 + 12}$$

$$\therefore R_a = \frac{48}{22}$$

$$\therefore R_a = \mathbf{2.1818 \text{ k}\Omega}$$

Now, the circuit is reduced to figure 11

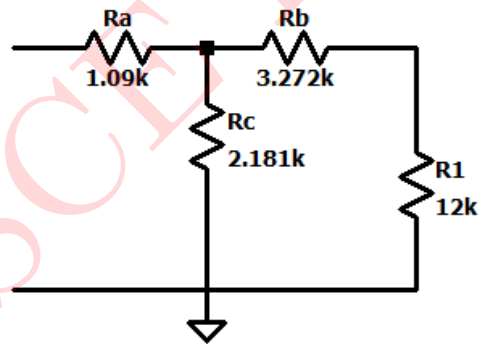


Figure 11: Modified circuit for figure 9

Now Resistor  $3.2728 \text{ k}\Omega$  is in series with  $12 \text{ k}\Omega$

$$\therefore 3.2728 \text{ k}\Omega + 12 \text{ k}\Omega = 15.2728 \text{ k}\Omega$$

The circuit is reduced to to figure 12

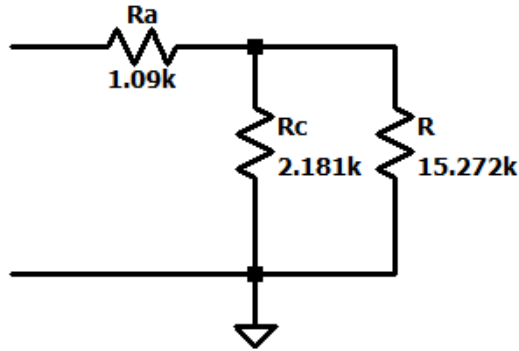


Figure 12: Modified circuit for figure 11

Now Resistor  $15.2728\text{ k}\Omega$  is in parallel with  $2.181\text{ k}\Omega$

$$\therefore 15.2728\text{ k}\Omega \parallel 2.181\text{ k}\Omega = \frac{152728 \times 2.181}{2.181 + 15.2728}\text{ k}\Omega$$

$$\therefore 15.2728\text{ k}\Omega \parallel 2.181\text{ k}\Omega = 1.909\text{ k}\Omega$$

Thus, finally circuit is reduced to figure 13

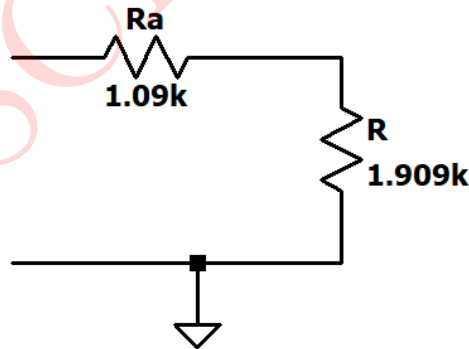


Figure 13: Modified circuit for figure 12

Now Resistor  $1.09\text{ k}\Omega$  is in series with  $1.909\text{ k}\Omega$

$$\therefore 1.09\text{ k}\Omega + 1.909\text{ k}\Omega = 2.999\text{ k}\Omega$$

$$\therefore R_{eq} = \mathbf{2.999\text{ k}\Omega}$$



### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

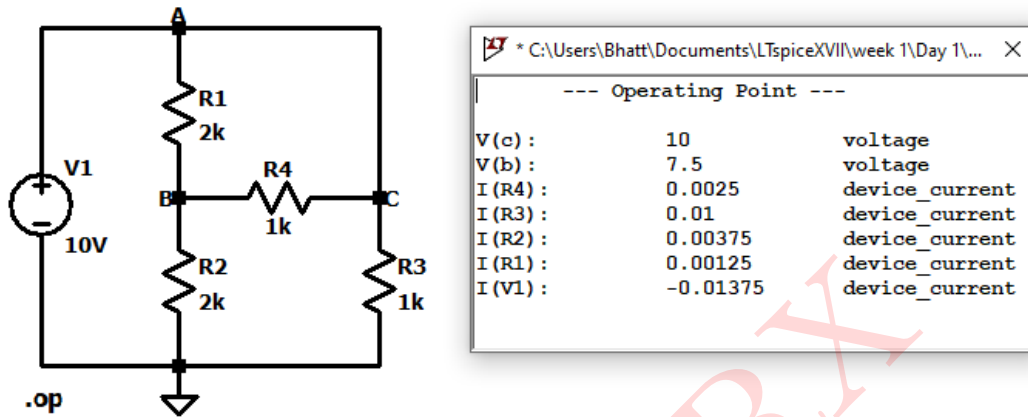


Figure 14: Circuit 2a Schematic and Simulated Results

**Calculation:**

$$R_{eq} = \frac{V_1}{I_{V1}}$$

$$R_{eq} = \frac{10}{0.01375}$$

$$R_{eq} = 727.27 \, \Omega$$

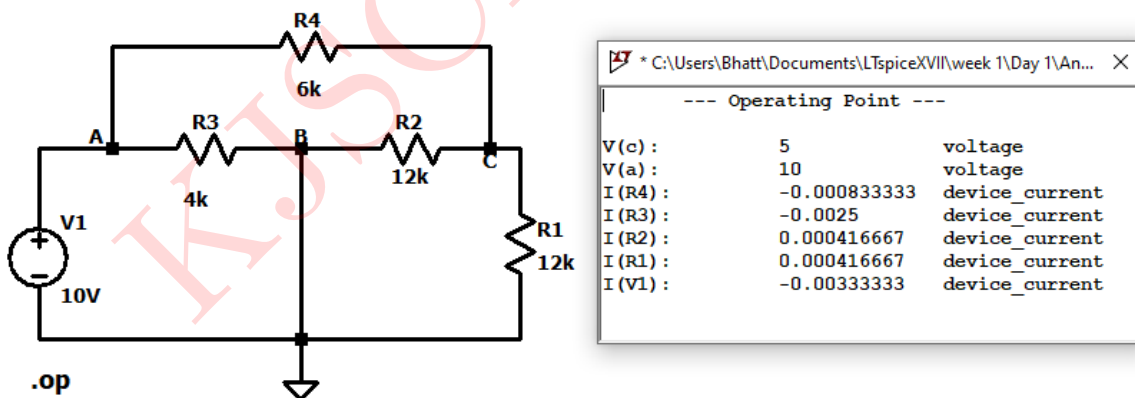


Figure 15: Circuit 2b Schematic and Simulated Results

**Calculation:**

$$R_{eq} = \frac{V_1}{I_{V1}}$$

$$R_{eq} = \frac{10}{0.00333}$$

$$R_{eq} = 3000 \, \Omega$$

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$R_{eq}(2a)$	727.3 $\Omega$	727.3 $\Omega$
$R_{eq}(2b)$	2999 $\Omega$	3000 $\Omega$

Table 2: Numerical 2

KJSCE ETRX

**Numerical 3:** Using Superposition theorem, calculate the magnitude and direction of the current through each resistor in the circuit of Figure 16

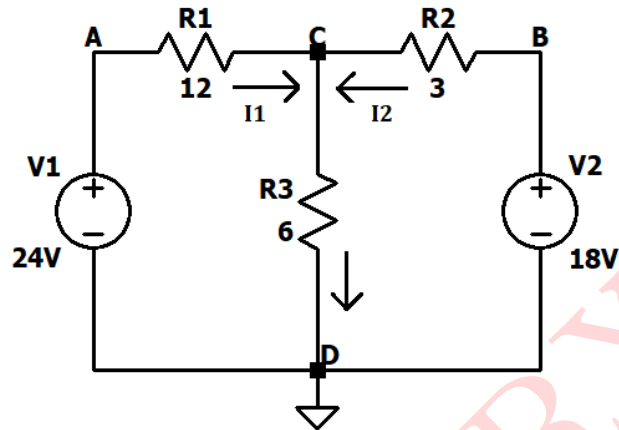


Figure 16: Circuit 3

**Solution:**

**Case 1:** 24V voltage source is active and 18V voltage source is inactive

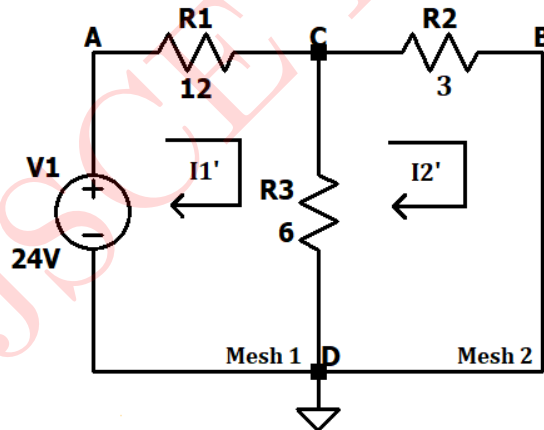


Figure 17: When only 24V voltage source is active

Let  $I_1'$  and  $I_2'$  be the current flowing through Mesh 1 and Mesh 2 in clockwise direction

Applying KVL to the Mesh 1,

$$-12I_1' - 6(I_1' - I_2') + 24 = 0$$

$$\therefore -12I_1' - 6I_1' + 6I_2' + 24 = 0$$

$$\therefore -18I_1' + 6I_2' + 24 = 0$$

$$\therefore 18I_1' - 6I_2' = 24 \quad \dots(1)$$

Applying KVL to Mesh 2,

$$-3I'_2 - 6(I'_2 - I'_1) = 0$$

$$\therefore -3I'_2 - 6I'_2 + 6I'_1 = 0$$

$$\therefore -9I'_2 + 6I'_1 = 0$$

$$\therefore 9I'_2 - 6I'_1 = 0 \quad \dots(2)$$

Solving equation (1) and (2) simultaneously, we get

$$I'_1 = 1.71429\text{A}$$

$$I'_2 = 1.14286\text{A}$$

Now let  $I'_3$  be the current flowing through branch CD in the downward direction

$$\therefore I'_3 = I'_1 - I'_2$$

$$\therefore I'_3 = 1.71429 - 1.14286$$

$$\therefore I'_3 = 0.57143\text{A}$$

Therefore, current flowing through the resistor  $R_1$ ,  $R_2$  and  $R_3$  when only 24V voltage source is active is

$$I'_1 = \mathbf{1.71429\text{ A}}$$

$$I'_2 = \mathbf{-1.14286\text{A}}$$

$$I'_3 = \mathbf{0.57143\text{A}}$$

**Case 2 :** 18V voltage source is active and 24V voltage source is inactive

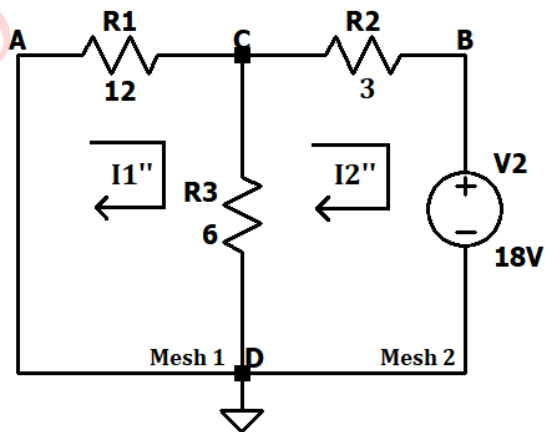


Figure 18: When only 18V voltage source is active

Let  $I_1''$  and  $I_2''$  be the current flowing through Mesh 1 and Mesh 2 in clockwise direction

Applying KVL to the Mesh 1,

$$-12I_1'' - 6(I_1'' - I_2'') = 0$$

$$\therefore -12I_1'' - 6I_1'' + 6I_2'' = 0$$

$$\therefore -18I_1'' + 6I_2'' = 0$$

$$\therefore 18I_1'' - 6I_2'' = 0 \quad \dots(1)$$

Applying KVL to Mesh 2,

$$-3I_2'' - 18 - 6(I_2'' - I_1'') = 0$$

$$\therefore -3I_2'' - 18 - 6I_2'' + 6I_1'' = 0$$

$$\therefore 6I_1'' - 9I_2'' - 18 = 0$$

$$\therefore 6I_1'' - 9I_2'' = 18 \quad \dots(2)$$

Solving equation (1) and (2) simultaneously, we get

$$I_1' = -0.85714\text{A}$$

$$I_2' = -2.57143\text{A}$$

Now let  $I_3''$  be the current flowing through branch CD in the downward direction

$$\therefore I_3'' = I_1'' - I_2''$$

$$\therefore I_3'' = (-0.85714) - (-2.57143)$$

$$\therefore I_3'' = 2.57143 - 0.857143$$

$$\therefore I_3'' = 1.71429\text{A}$$

Therefore, currents flowing through the resistor  $R_1$ ,  $R_2$  and  $R_3$  when only 18V voltage source is active is

$$I_1'' = -0.85714\text{A}$$

$$I_2'' = -2.57143\text{A}$$

$$I_3'' = 1.71429\text{A}$$

Using Superposition theorem,

Currents  $I_1'$  and  $I_1''$  are flowing through resistor  $R_1 = 12 \Omega$

$$\therefore I_1 = I_1' + I_1''$$

$$\therefore I_1 = 1.71429 + (-0.85714)$$

$$\therefore I_1 = 1.71429 - 0.85714$$

$$\therefore I_1 = 0.85714\text{A}$$

Here, the positive sign denotes that the assumed direction is correct.

Hence, a current of 0.85714A is flowing through the  $12 \Omega$  resistor in clockwise direction.

Currents  $I'_2$  and  $I''_2$  are flowing through resistor  $R_2 = 3 \Omega$

$$\therefore I_2 = I'_2 + I''_2$$

$$\therefore I_2 = 1.14286 + (-2.57143)$$

$$\therefore I_2 = 1.14286 - 2.57143$$

$$\therefore I_2 = -1.42857 \text{ A}$$

Here, the negative sign denotes that the assumed direction is wrong.

Hence, a current of 1.42857A is flowing through the  $3 \Omega$  resistor in anti-clockwise direction.

Also,  $I'_3$  and  $I''_3$  are the currents flowing through resistor  $R_3 = 6 \Omega$

$$\therefore I_3 = I'_3 + I''_3$$

$$\therefore I_3 = 0.571429 + 1.71429$$

$$\therefore I_3 = 2.28571 \text{ A}$$

Here, the positive sign denotes that the assumed direction is correct.

Hence, a current of 2.28571A is flowing through the  $6 \Omega$  resistor in clockwise direction.

Therefore, the current flowing through resistors  $12 \Omega$ ,  $3 \Omega$  and  $6 \Omega$  are **0.85714A**, **1.42857A** and **2.28571A** respectively.

#### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

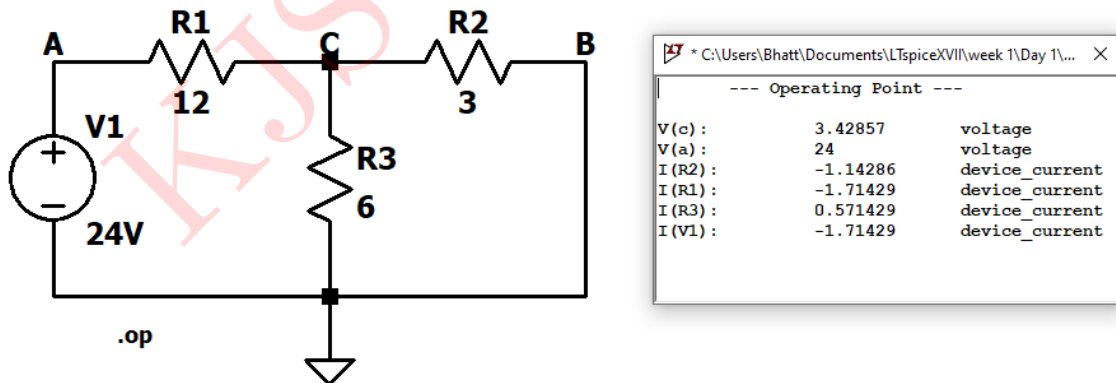


Figure 19: Circuit Schematic and Simulated Results: when only 24V voltage source is active

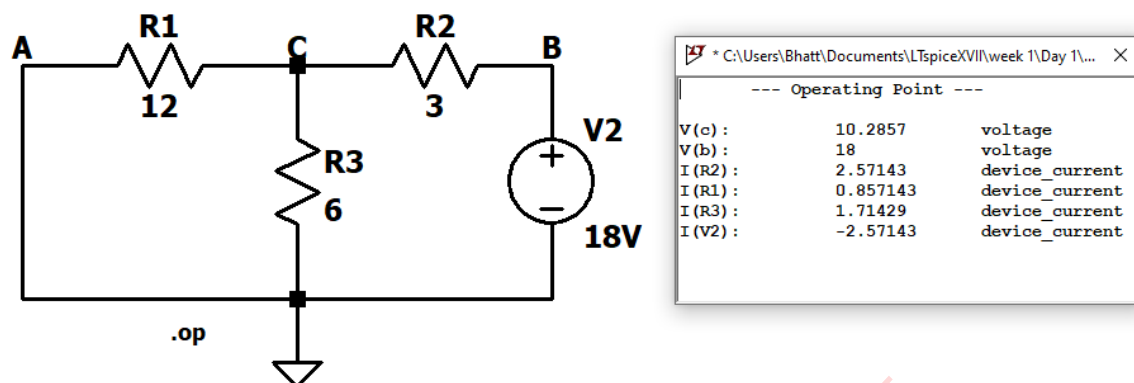


Figure 20: Circuit Schematic and Simulated Results: when only 18V voltage source is active

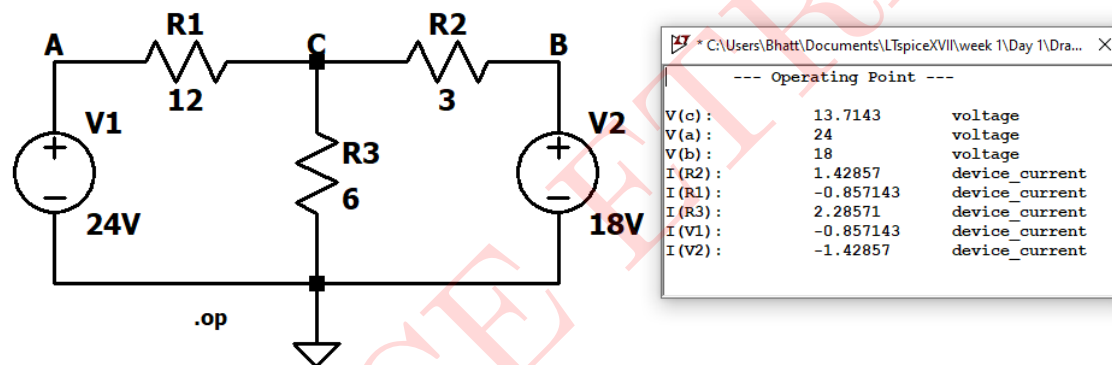


Figure 21: Circuit Schematic and Simulated Results: when both the sources are active

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{12\Omega}$	0.85714A	0.85714A
$I_{3\Omega}$	1.42857A	1.42857A
$I_{6\Omega}$	2.28571A	2.28571A

Table 3: Numerical 3

**Numerical 4:** For the circuit shown in Figure 22 find the current in  $R = 8 \Omega$  resistance in the branch AB using superposition theorem.

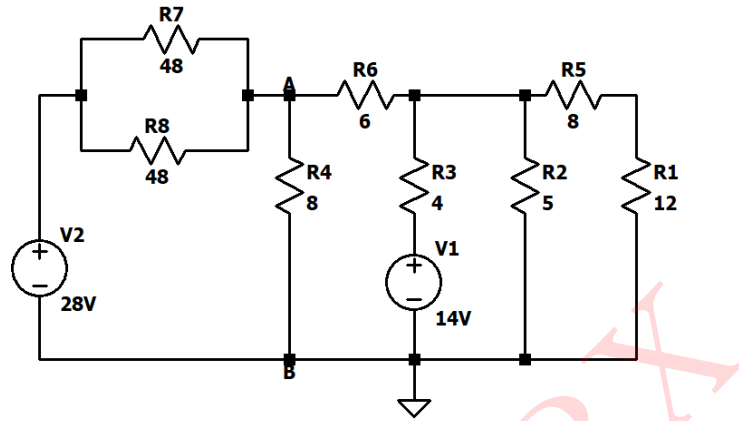


Figure 22: Circuit 4

**Solution:**

**Case 1 :** 28V voltage source is active and 14V voltage source is inactive

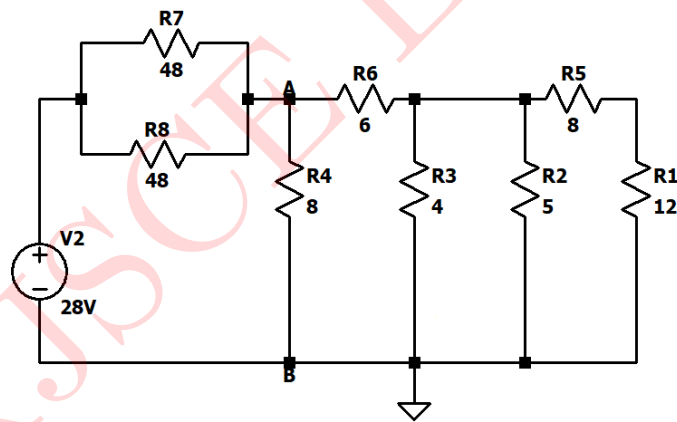


Figure 23: When only 28V voltage source is active

Resistors  $R_1$  and  $R_5$  i.e.  $8 \Omega$  and  $12 \Omega$  are in series

$$\therefore 8 \Omega + 12 \Omega = 20 \Omega$$

The resistors  $R_7 = 48 \Omega$  and  $R_8 = 48 \Omega$  are parallel.

$$\therefore 48\Omega \parallel 48\Omega = \frac{48 \times 48}{48 + 48}$$

$$\therefore 48\Omega \parallel 48\Omega = 24 \Omega$$



Now the circuit is reduced to figure 24

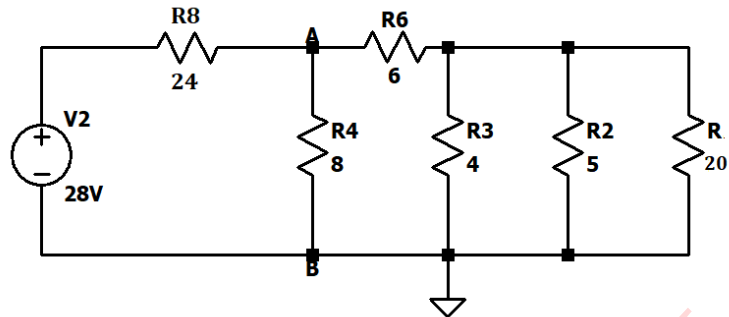


Figure 24: Modified circuit for figure 23

The resistors  $R = 20 \Omega$  and  $R_2 = 5 \Omega$  are parallel.

$$\therefore 20\Omega \parallel 5\Omega = \frac{20 \times 5}{20 + 5}$$

$$\therefore 20\Omega \parallel 5\Omega = \frac{100}{24} \Omega$$

$$\therefore 20\Omega \parallel 5\Omega = 4 \Omega$$

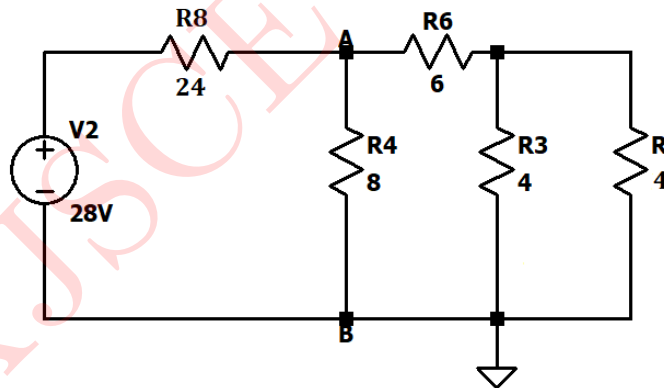


Figure 25: Modified circuit for figure 24

The resistors  $R = 4 \Omega$  and  $R_3 = 4 \Omega$  are parallel.

$$\therefore 4\Omega \parallel 4\Omega = \frac{4 \times 4}{4 + 4}$$

$$\therefore 4\Omega \parallel 4\Omega = \frac{16}{8} \Omega$$

$$\therefore 4\Omega \parallel 4\Omega = 2 \Omega$$

Now the circuit is reduced to figure 26

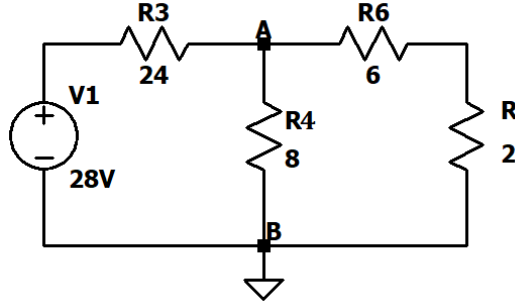


Figure 26: Modified circuit for figure 25

Resistors  $R$  and  $R_6$  i.e.  $2\ \Omega$  and  $6\ \Omega$  are in series

$$\therefore 2\ \Omega + 6\ \Omega = 8\ \Omega$$

Using source transformation,

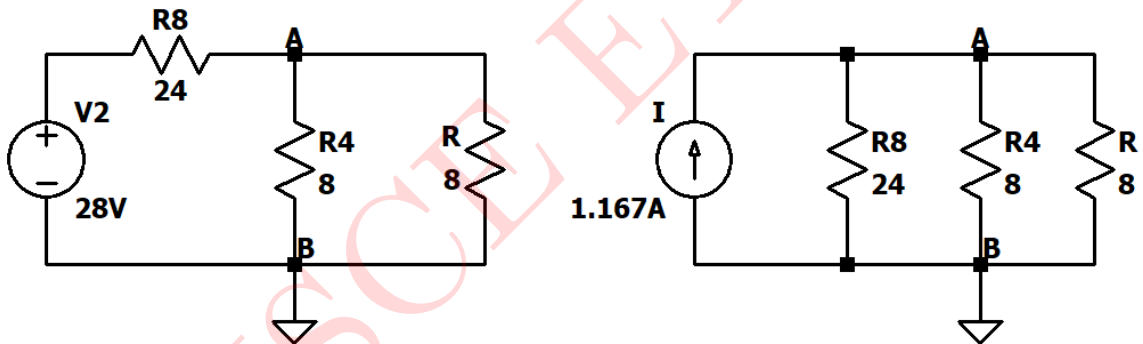


Figure 27: Source Transformation modified circuit for figure 26

$$\therefore I = \frac{V_2}{R_8}$$

$$\therefore I = \frac{28}{24}$$

$$\therefore I = 1.167\text{A}$$

The resistors  $R = 8\ \Omega$  and  $R_8 = 24\ \Omega$  are parallel.

$$\therefore 8\ \Omega \parallel 24\ \Omega = \frac{8 \times 24}{8 + 24}$$

$$\therefore 8\ \Omega \parallel 24\ \Omega = \frac{192}{32}\ \Omega$$

$$\therefore 8\ \Omega \parallel 24\ \Omega = 6\ \Omega$$

Now the circuit is reduced to figure 28

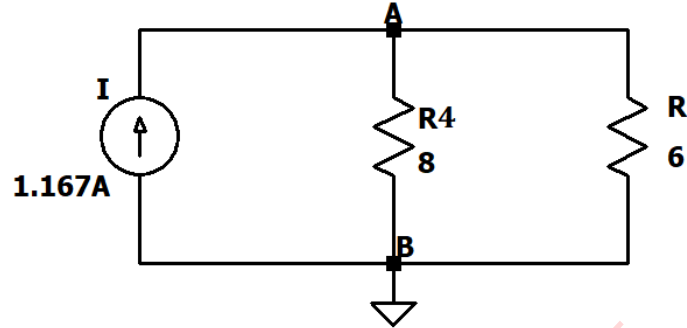


Figure 28: Modified circuit for figure 27

Let  $I'$  be the current flowing through  $8\ \Omega$  resistor when only  $24\text{V}$  voltage source is active

Using Current Division Rule,

$$I' = I \times \frac{R}{R + R_4}$$

$$I' = 1.167 \times \frac{6}{6 + 8}$$

$$I' = 1.167 \times \frac{6}{14}$$

$$I' = 0.5\text{A}$$

**Case 2 :**  $14\text{V}$  voltage source is active and  $28\text{V}$  voltage source is inactive

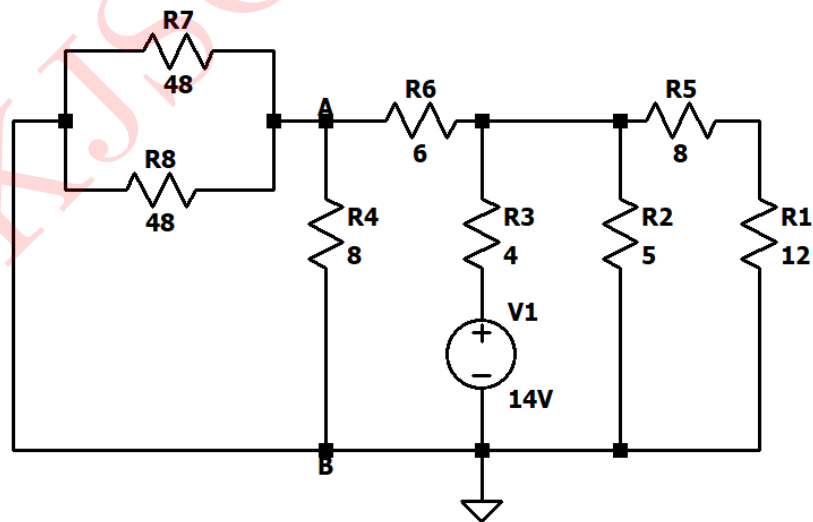


Figure 29: When only  $14\text{V}$  voltage source is active

Resistors  $R_1$  and  $R_5$  i.e.  $8\ \Omega$  and  $12\ \Omega$  are in series

$$\therefore 8\ \Omega + 12\ \Omega = 20\ \Omega$$

The resistors  $R_7 = 48\ \Omega$  and  $R_8 = 48\ \Omega$  are parallel.

$$\therefore 48\ \Omega \parallel 48\ \Omega = \frac{48 \times 48}{48 + 48}$$

$$\therefore 48\ \Omega \parallel 48\ \Omega = 24\ \Omega$$

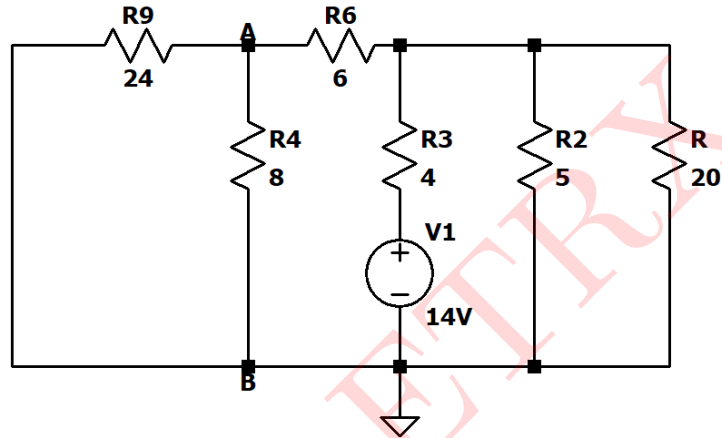


Figure 30: Modified circuit for figure 29

The resistors  $R = 20\ \Omega$  and  $R_2 = 5\ \Omega$  are parallel.

$$\therefore 20\ \Omega \parallel 5\ \Omega = \frac{20 \times 5}{20 + 5}$$

$$\therefore 20\ \Omega \parallel 5\ \Omega = 4\ \Omega$$

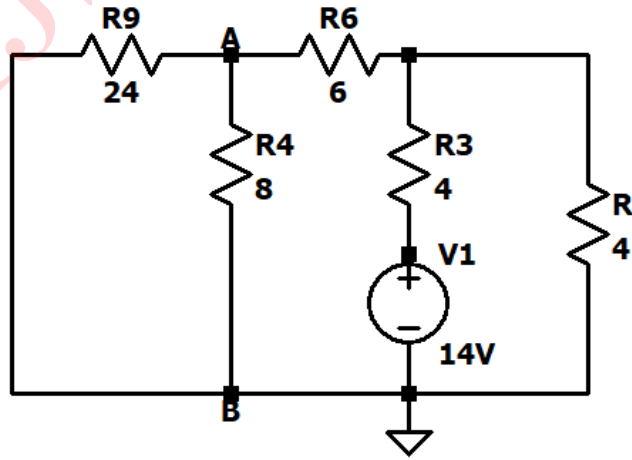


Figure 31: Modified circuit for figure 30

Using Source Transformation,

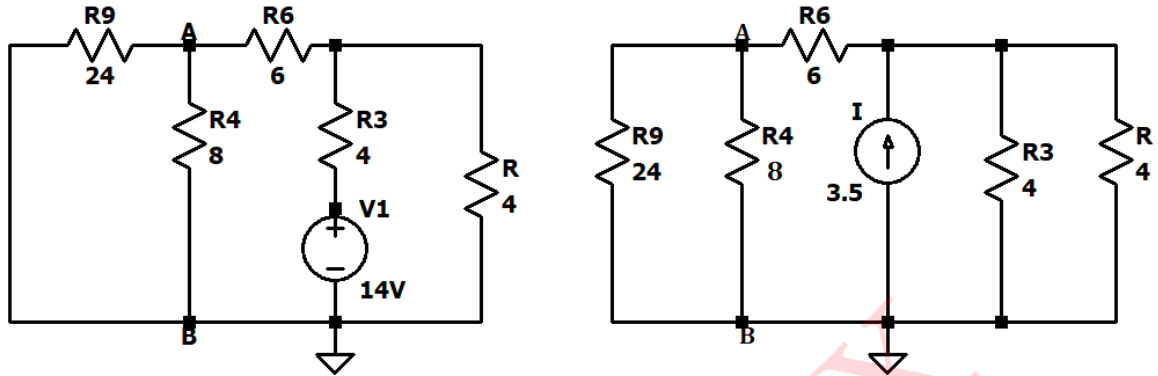


Figure 32: Source Transformation modified circuit for figure 31

$$\begin{aligned} \therefore I &= \frac{V_1}{R_3} \\ \therefore I &= \frac{14}{4} \\ \therefore I &= 3.5\text{A} \end{aligned}$$

The resistors  $R = 4\ \Omega$  and  $R_3 = 4\ \Omega$  are parallel.

$$\begin{aligned} \therefore 4\ \Omega \parallel 4\ \Omega &= \frac{4 \times 4}{4 + 4} \\ \therefore 4\ \Omega \parallel 4\ \Omega &= 2\ \Omega \end{aligned}$$

Using Source Transformation,

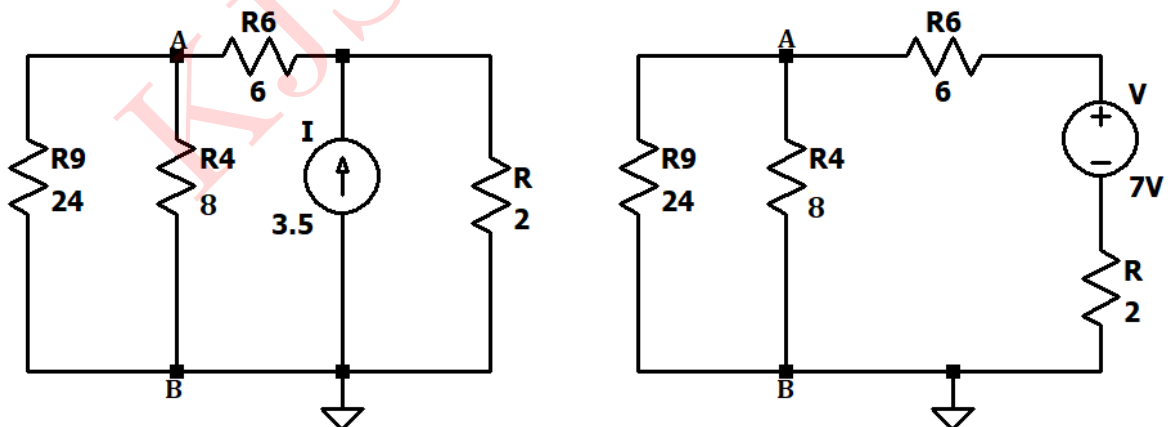


Figure 33: Source Transformation modified circuit for figure 32

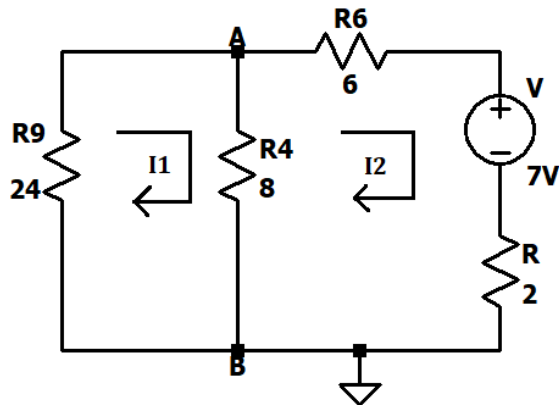


Figure 34: Modified circuit for figure 33

Applying KVL to Mesh 1,

$$-24I_2 - 8(I_1 - I_2) = 0$$

$$\therefore -24I_1 - 8I_1 + 8I_2 = 0$$

$$\therefore -32I_1 + 8I_2 = 0 \quad \dots(1)$$

Applying KVL to Mesh 2,

$$-6I_2 - 2I_2 - 8(I_2 - I_1) - 7 = 0$$

$$\therefore -8I_2 - 8I_2 + 8I_1 - 7 = 0$$

$$\therefore -16I_2 + 8I_1 - 7 = 0$$

$$\therefore 8I_1 - 16I_2 = 7 \quad \dots(2)$$

Solving equation(1) and (2) simultaneously, we get

$$I_1 = -0.125A$$

$$I_2 = -0.5A$$

Current through branch AB when 14V is acting alone

$$I'' = I_1 - I_2$$

$$I'' = (-0.125) - (-0.5)$$

$$I'' = 0.5 - 0.125$$

$$I'' = 0.375A$$

Using Superposition theorem,

Current flowing through branch AB is

$$I = I' + I''$$

$$I = 0.5 + 0.375$$

$$I = \mathbf{0.875A}$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

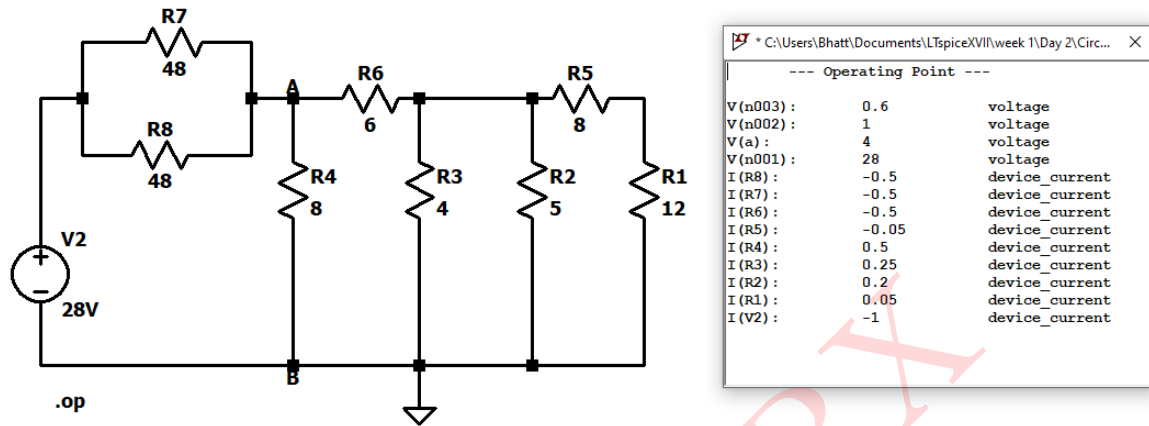


Figure 35: Circuit Schematic: when only 28V source is active

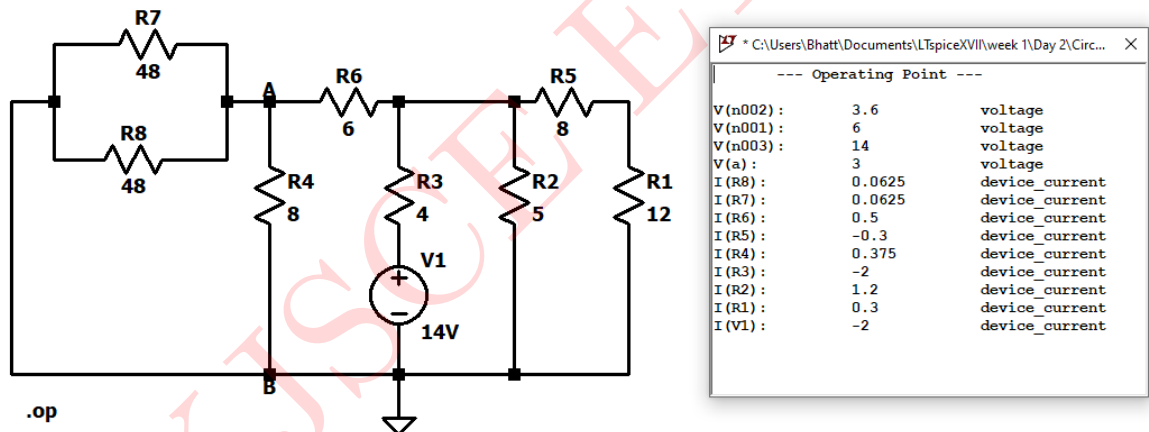


Figure 36: Circuit Schematic: when only 14V source is active

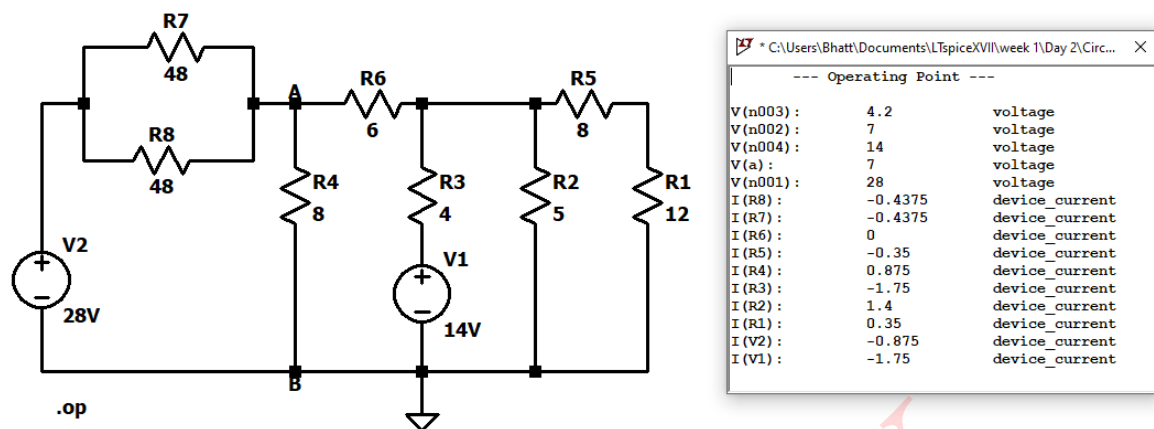


Figure 37: Circuit Schematic: when both the sources are active

#### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{AB}$	0.875A	0.875A

Table 4: Numerical 4



**Numerical 5:** In the circuit shown in figure 38, obtain the condition from maximum power transfer to the load  $R_L$ . Hence, determine the maximum power transferred.

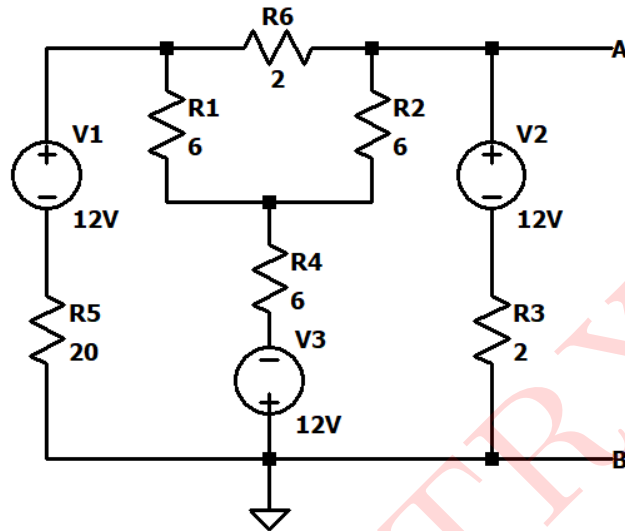


Figure 38: Circuit 5

**Solution:**

**Case 1:** To determine Thevenin's resistance ( $R_{th}$ )

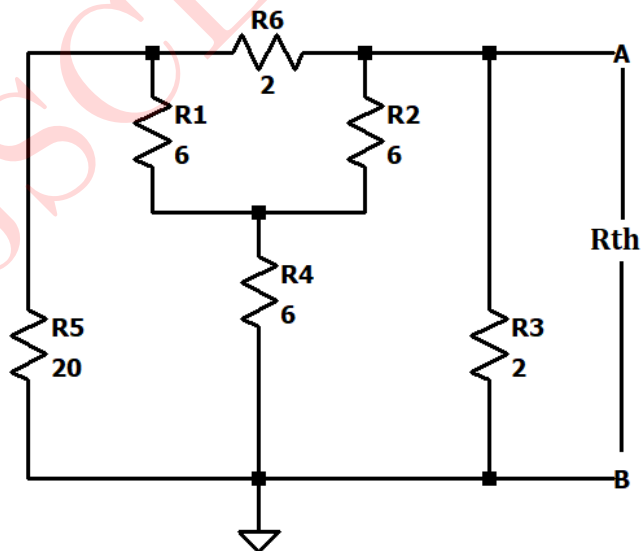


Figure 39: To determine  $R_{th}$

Here the resistors  $R_1 = 6 \Omega$ ,  $R_6 = 2 \Omega$  and  $R_2 = 6 \Omega$  form a delta network.

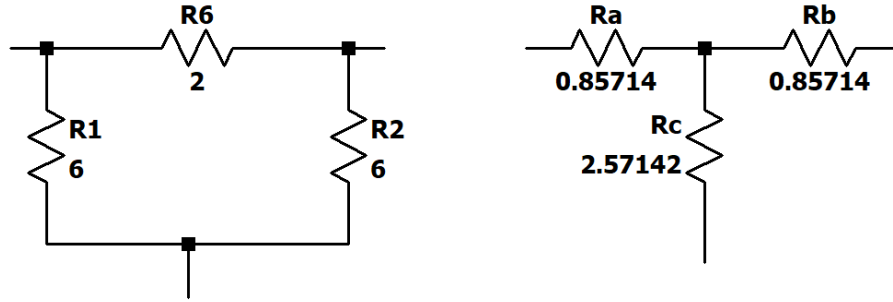


Figure 40: Star - Delta Transformation modified circuit for figure 39

Therefore, using Star - Delta Transformation

The formulas are :

$$R_a = \frac{R_1 \times R_6}{R_1 + R_2 + R_6}$$

$$R_b = \frac{R_2 \times R_6}{R_1 + R_2 + R_6}$$

$$R_c = \frac{R_1 \times R_2}{R_1 + R_2 + R_6}$$

Substituting the values of resistors in the formula, we get

$$R_a = \frac{6 \times 2}{6 + 2 + 6}$$

$$\therefore R_a = \frac{12}{14}$$

$$\therefore R_a = 0.85714 \, \Omega$$

$$R_b = \frac{6 \times 2}{6 + 2 + 6}$$

$$\therefore R_b = \frac{12}{14}$$

$$\therefore R_b = 0.85714 \, \Omega$$

$$R_c = \frac{6 \times 6}{6 + 2 + 6}$$

$$\therefore R_c = \frac{36}{14}$$

$$\therefore R_c = 2.57142 \, \Omega$$

Now the circuit is reduced to figure 41

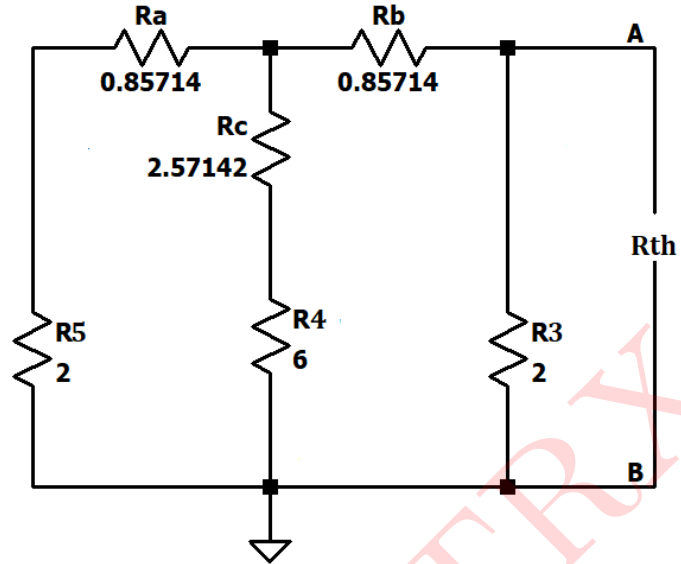


Figure 41: Modified circuit for figure 39

Now, resistor  $2\ \Omega$  is in series with  $0.85714\ \Omega$

$$\therefore 2\ \Omega + 0.85714\ \Omega = 2.85714\ \Omega$$

Also, resistor  $6\ \Omega$  is in series with  $2.5714\ \Omega$

$$\therefore 6\ \Omega + 2.5714\ \Omega = 8.5714\ \Omega$$

Now the circuit is reduced to figure 42

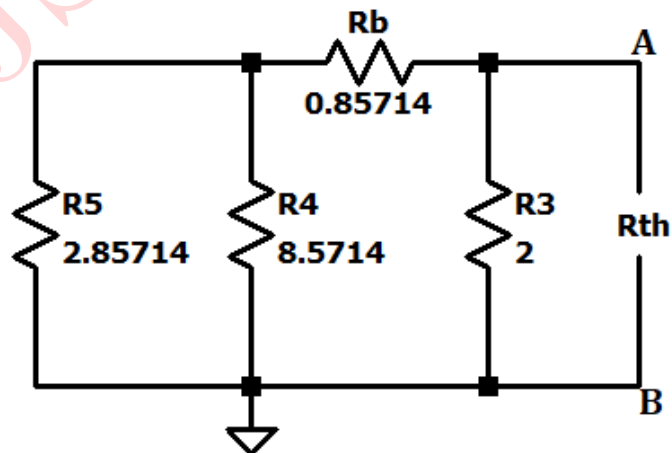


Figure 42: Modified circuit for figure 41

Now, resistor  $2.85714 \Omega$  is in parallel with  $8.5714 \Omega$

$$\therefore 2.85714 \Omega \parallel 8.5714 \Omega = \frac{2.85714 \times 8.5714}{2.85714 + 8.5714} \Omega$$

$$\therefore 2.85714 \Omega \parallel 8.5714 \Omega = 2.14277 \Omega$$

Also, resistor  $0.85714 \Omega$  is in series with  $2.14277 \Omega$

$$\therefore 0.85714 \Omega + 2.14277 \Omega = 2.99991 \Omega$$

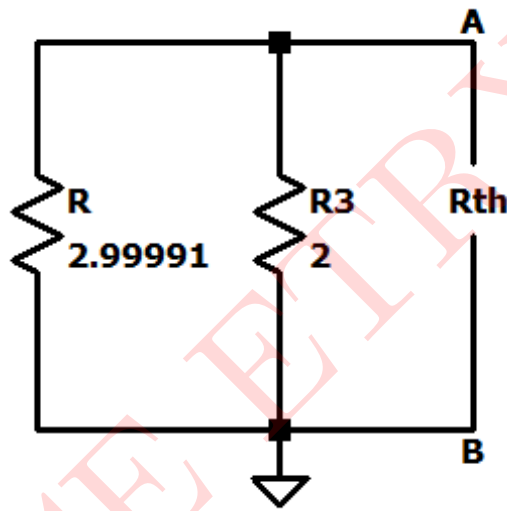


Figure 43: Modified circuit for figure 42

Now, resistor  $2.99991 \Omega$  is in parallel with  $2 \Omega$

$$\therefore 2.99991 \Omega \parallel 2 \Omega = \frac{2.9999 \times 2}{2.99991 + 2} \Omega$$

$$\therefore 2.99991 \Omega \parallel 2 \Omega = 1.2 \Omega$$

$$R_{th} = 1.2 \Omega$$

**Case 2 :** To determine Thevenin's voltage ( $V_{th}$ )

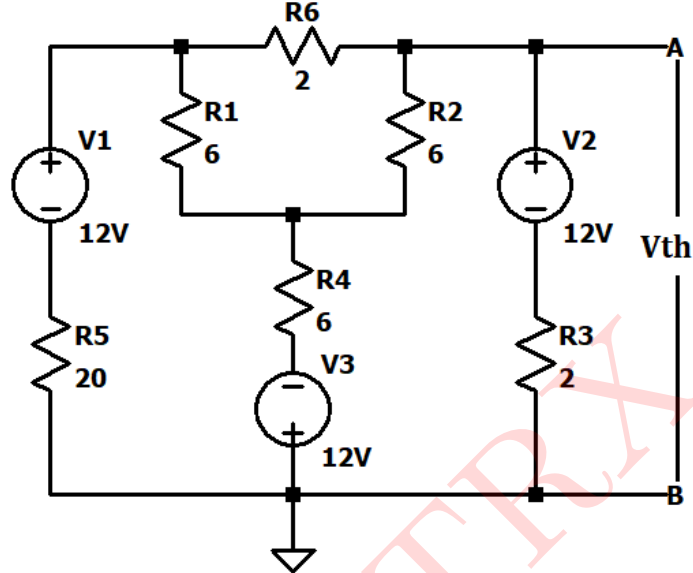


Figure 44: To determine  $V_{th}$

Here the resistors  $R_1 = 6\ \Omega$ ,  $R_6 = 2\ \Omega$  and  $R_2 = 6\ \Omega$  form a delta network.

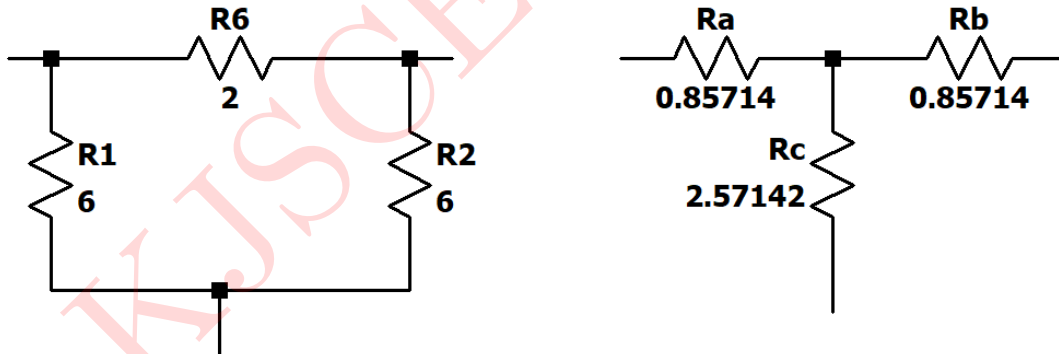


Figure 45: Star - Delta Transformation modified circuit for figure 44

Therefore, using Star - Delta Transformation

The formulas are :

$$R_a = \frac{R_1 \times R_6}{R_1 + R_2 + R_6}$$

$$R_b = \frac{R_2 \times R_6}{R_1 + R_2 + R_6}$$

$$R_c = \frac{R_1 \times R_2}{R_1 + R_2 + R_6}$$

Substituting the values of resistors in the formula, we get

$$R_a = \frac{6 \times 2}{6 + 2 + 6}$$

$$\therefore R_a = \frac{12}{14}$$

$$\therefore R_a = \mathbf{0.85714 \, \Omega}$$

$$R_b = \frac{6 \times 2}{6 + 2 + 6}$$

$$\therefore R_b = \frac{12}{14}$$

$$\therefore R_b = \mathbf{0.85714 \, \Omega}$$

$$R_c = \frac{6 \times 6}{6 + 2 + 6}$$

$$\therefore R_c = \frac{36}{14}$$

$$\therefore R_c = \mathbf{2.57142 \, \Omega}$$

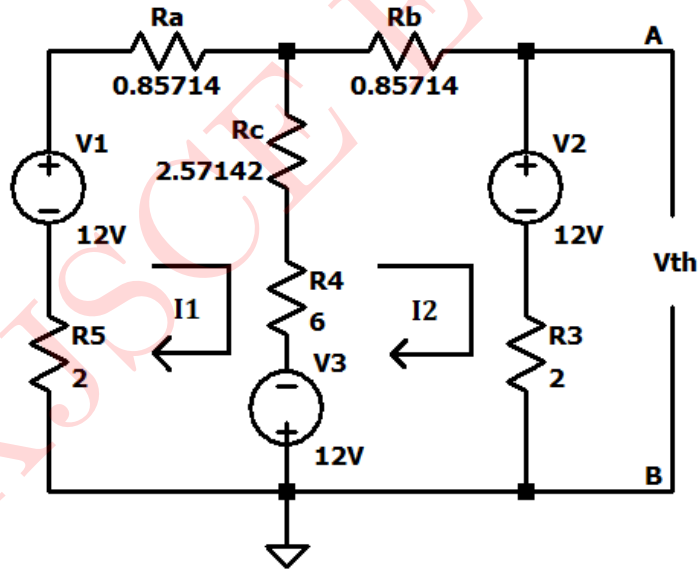


Figure 46: Modified circuit for figure 44

Let  $I_1$  and  $I_2$  be the current flowing through Mesh 1 and Mesh 2 in clockwise direction

Applying KVL to the Mesh 1,

$$-0.857I_1 - 6I_1 - 2.571(I_1 - I_2) + 6I_2 + 12 + 12 - 2I_1 = 0$$

$$-0.857I_1 - 6I_1 - 2.571I_1 + 2.571I_2 + 6I_2 + 12 - 12 - 2I_1 = 0$$

$$\therefore -11.4284I_1 + 8.5714I_2 + 24 = 0$$

$$\therefore 11.4284I_1 - 8.5714I_2 = 24 \quad \dots(1)$$

Applying KVL to Mesh 2,

$$-0.857I_2 - 2I_2 - 12 - 12 - 6(I_2 - I_1) - 2.5714(I_2 - I_1) = 0$$

$$-0.857I_2 - 2I_2 - 24 - 6I_2 + 6I_1 - 2.5714I_2 + 2.5714I_1 = 0$$

$$\therefore -8.5714I_1 + 11.4284I_2 + 24 = 0$$

$$\therefore 8.5714I_1 - 11.4284I_2 = 24 \quad \dots(2)$$

Solving equation(1) and (2) simultaneously, we get

$$I_1 = 1.2\text{A}$$

$$I_2 = -1.2\text{A}$$

Applying KVL to Mesh 3,

$$V_{th} - 12 - 2I_2 = 0$$

$$\therefore V_{th} = 12 + 2I_2$$

$$\therefore V_{th} = 12 + 2 \times -1.2$$

$$\therefore V_{th} = 12 - 2.4$$

$$V_{th} = \mathbf{9.6V}$$

**Thevenin's Equivalent circuit**

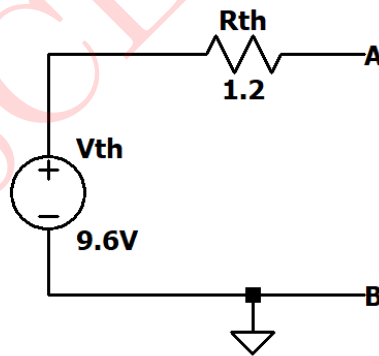


Figure 47: Thevenin's equivalent circuit

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

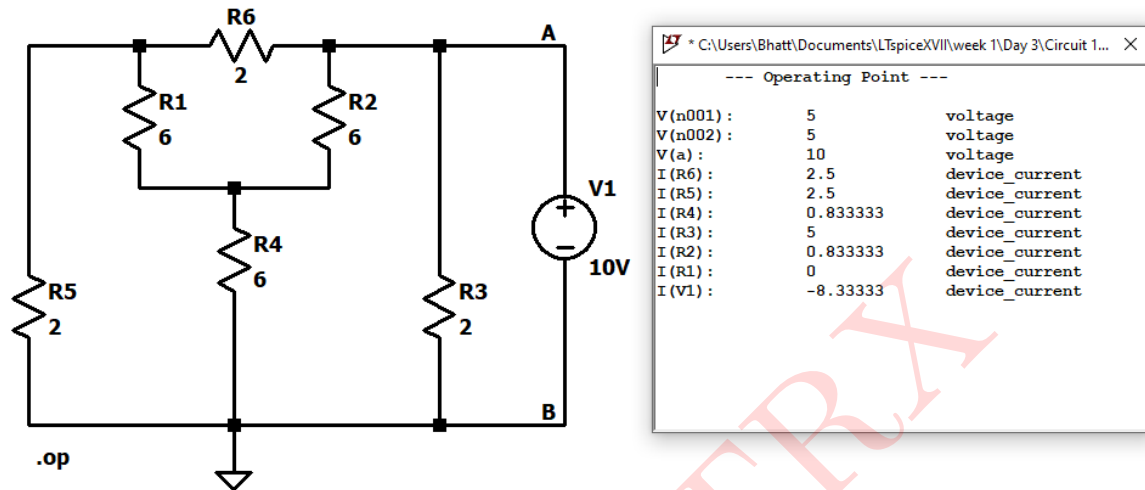


Figure 48: Circuit Schematic and Simulated Results: To determine Rth

### Calculation:

$$R_{th} = \frac{V_1}{I_{V1}}$$

$$R_{th} = \frac{10}{8.3333}$$

$$R_{th} = 1.2 \Omega$$

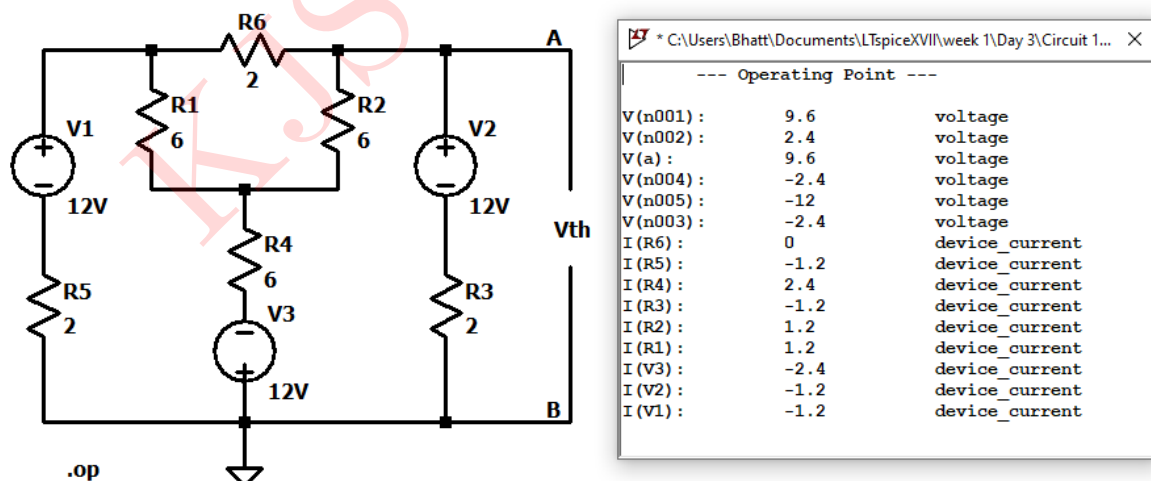


Figure 49: Circuit Schematic and Simulated Results: To determine Vth



Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$V_{th}$	9.6V	9.6V
$R_{th}$	1.2 $\Omega$	1.2 $\Omega$

Table 5: Numerical 5

KJSCE ETRX

**Numerical 6:** Find Thevenin's Equivalent Circuit for circuit 6 shown in figure 50

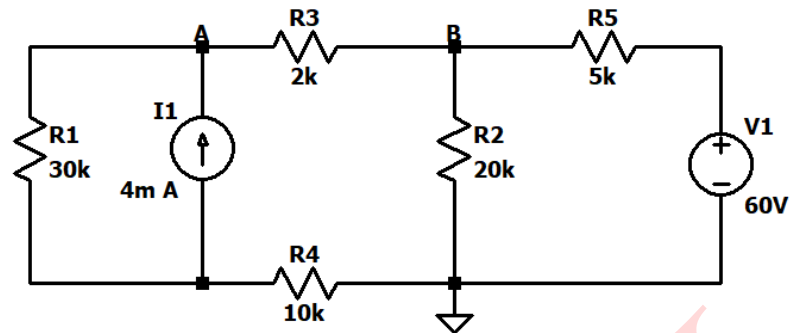


Figure 50: Circuit 6

**Solution:**

**Case 1:** To determine Thevenin's Resistance ( $R_{th}$ )

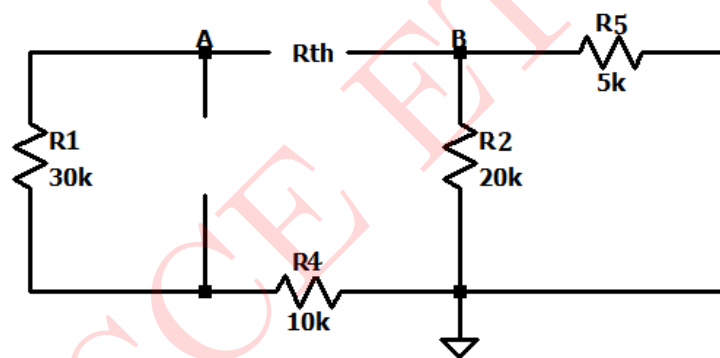


Figure 51: To determine  $R_{th}$

The resistors  $R_5 = 5 \text{ k}\Omega$  and  $R_2 = 20 \text{ k}\Omega$  are parallel.

$$\therefore 5 \text{ k}\Omega \parallel 20 \text{ k}\Omega = \frac{5 \times 20}{5 + 20}$$

$$\therefore 5 \text{ k}\Omega \parallel 20 \text{ k}\Omega = 4 \text{ k}\Omega$$

Now, the circuit is reduced to figure 52

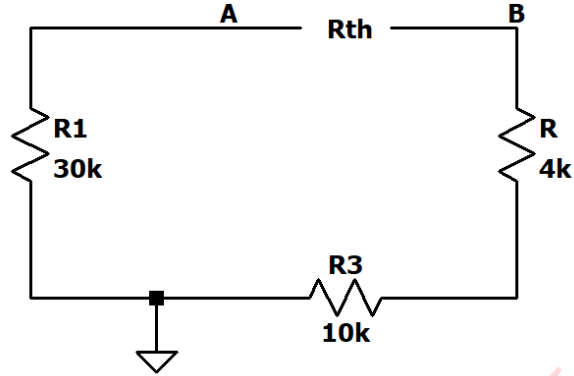


Figure 52: Modified circuit for figure 51

Resistors  $R_1$ ,  $R$  and  $R_4$  i.e.  $30\text{ k}\Omega$ ,  $4\text{ k}\Omega$  and  $10\text{ k}\Omega$  are in series  
 $\therefore 30\text{ k}\Omega + 4\text{ k}\Omega + 10\text{ k}\Omega = 44\text{ k}\Omega$

$$R_{th} = 44\text{ k}\Omega$$

**Case 2:** To determine Thevenin's voltage

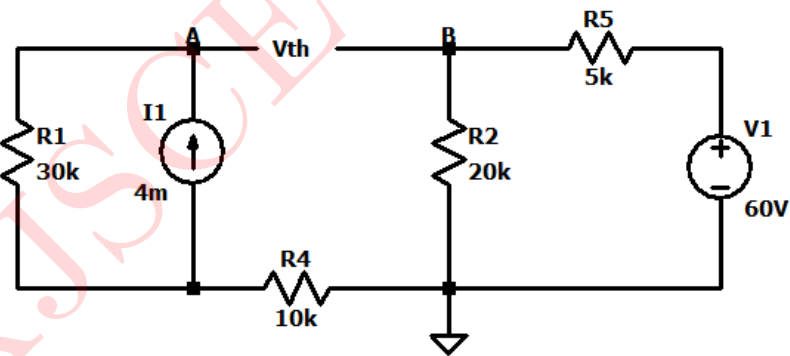


Figure 53: To determine  $V_{th}$

Using source transformation,

$$\therefore I = \frac{V_1}{R_5}$$

$$\therefore I = \frac{60}{5000}$$

$$\therefore I = 0.012\text{A}$$

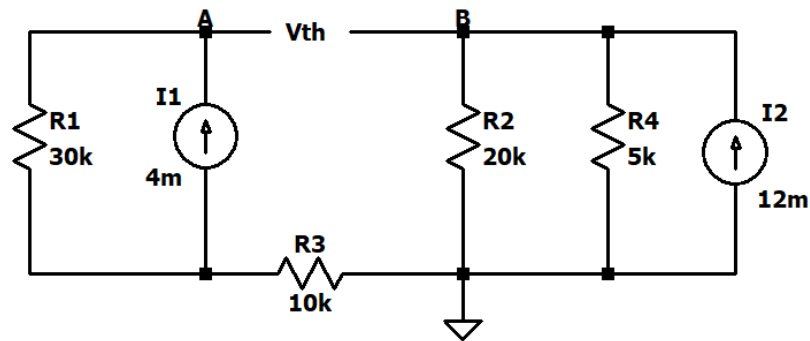


Figure 54: Source Transformation modified circuit for figure 53

The resistors  $R_5 = 5 \text{ k}\Omega$  and  $R_2 = 20 \text{ k}\Omega$  are parallel.

$$\therefore 20 \text{ k}\Omega \parallel 5 \text{ k}\Omega = \frac{20 \times 5}{20 + 5}$$

$$\therefore 20 \text{ k}\Omega \parallel 5 \text{ k}\Omega = \frac{100}{24} \text{ k}\Omega$$

$$\therefore 20 \text{ k}\Omega \parallel 5 \text{ k}\Omega = 4 \text{ k}\Omega$$

Now the circuit is reduced to figure 55

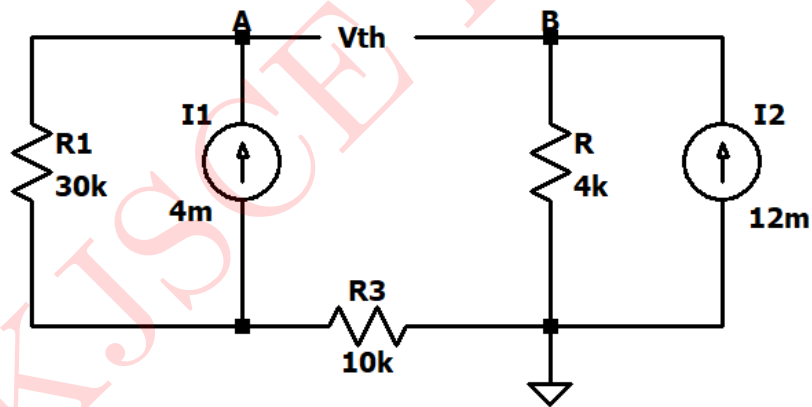


Figure 55: Modified circuit for figure 54

Using source transformation,

$$\therefore V = I \times R_1$$

$$\therefore V = 4\text{m} \times 30 \text{ k}$$

$$\therefore V = 120\text{V}$$

Similarly

$$\therefore V = I \times R$$

$$\therefore V = 12\text{m} \times 4 \text{ k}$$

$$\therefore V = 48\text{V}$$

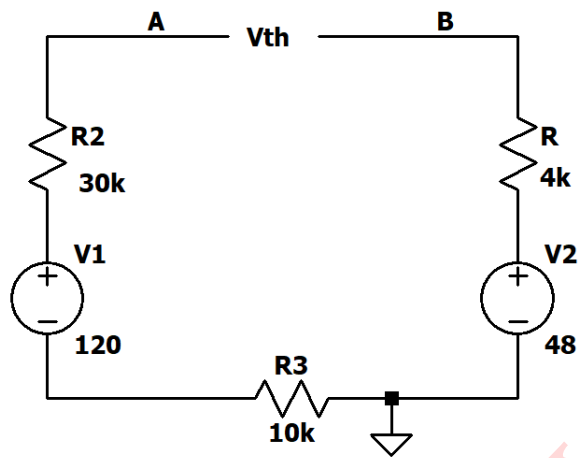


Figure 56: Source Transformation modified circuit for figure 55

$$\begin{aligned}\therefore V_{th} &= V_1 - V_2 \\ \therefore V_{th} &= 120 - 48 \\ \therefore V_{th} &= 72V\end{aligned}$$

Thevenin's Equivalent circuit

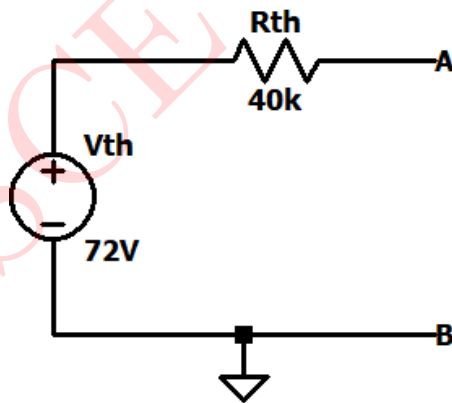


Figure 57: Thevenin's equivalent circuit

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

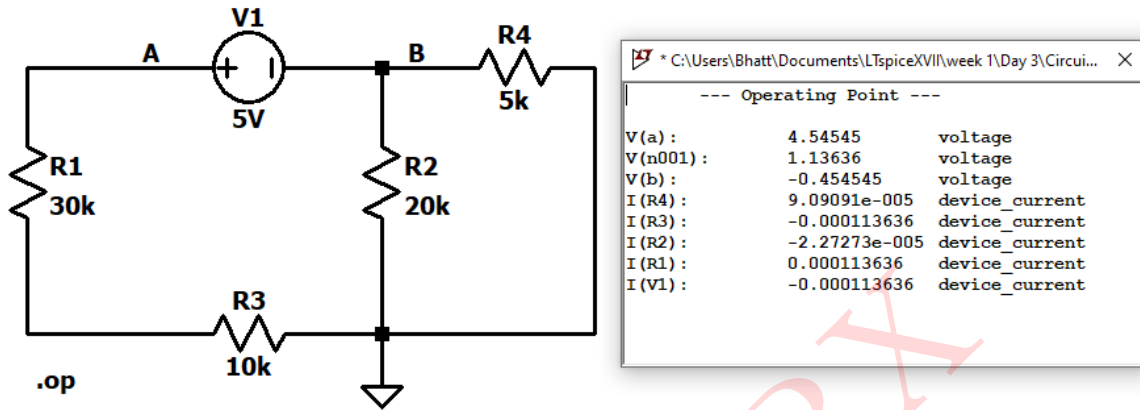


Figure 58: Circuit Schematic and Simulated Results: To determine  $R_{th}$

### Calculation:

$$\therefore R_{th} = \frac{V_1}{I_{V1}}$$

$$\therefore R_{th} = \frac{5}{0.0001136}$$

$$\therefore R_{th} = 44 \text{ k}\Omega$$

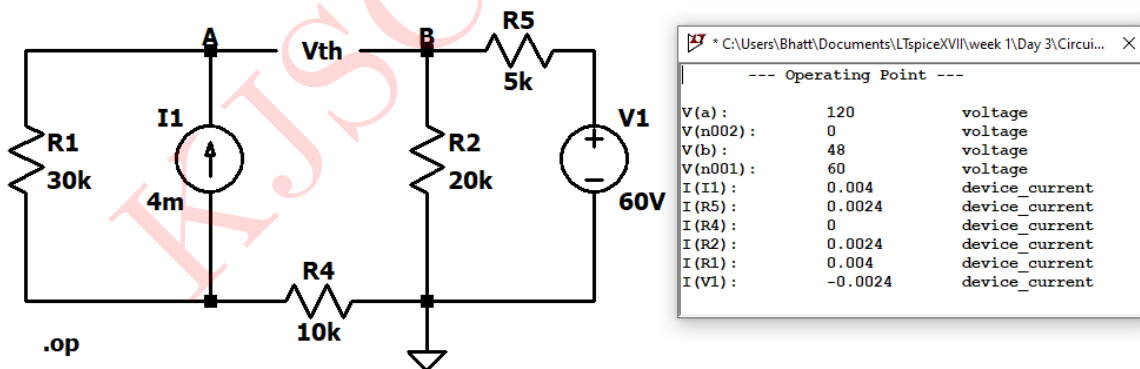


Figure 59: Circuit Schematic and Simulated Results: To determine  $V_{th}$

### Calculation:

$$\therefore V_{th} = V_a - V_b$$

$$\therefore V_{th} = 120 - 48$$

$$\therefore V_{th} = 72V$$

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$V_{th}$	72V	72V
$R_{th}$	44 k $\Omega$	44 k $\Omega$

Table 6: Numerical 6

KJSCE ETRX

**Numerical 7:** Find the voltage across points A and B in the network shown in figure 60 using Norton's Theorem.

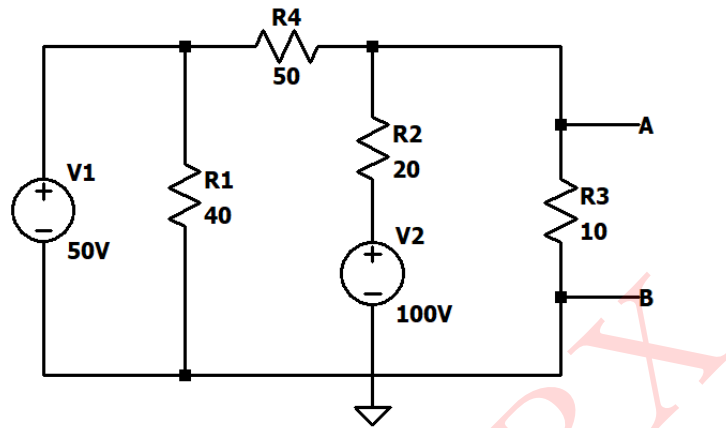


Figure 60: Circuit 7

**Solution:**

**Case 1:** To determine  $R_{th}$

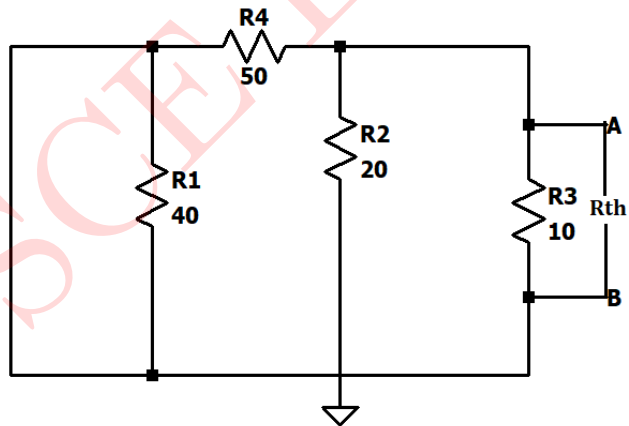


Figure 61: To determine  $R_{th}$

Here, the resistor  $R_1 = 40\ \Omega$  becomes redundant when the voltage source is replaced by a short circuit.



Now, the circuit is reduced to figure 62

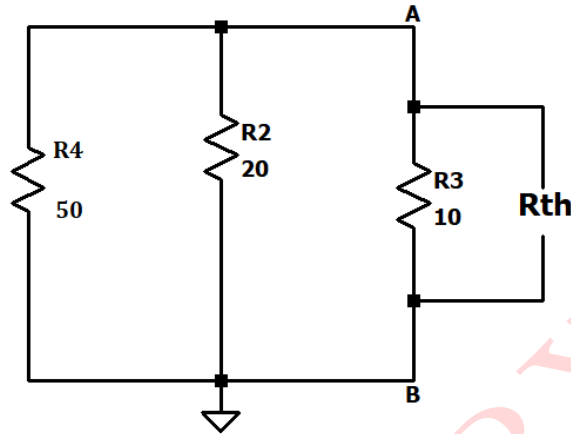


Figure 62: Modified circuit for figure 61

Now, resistors  $R_4 = 50 \, \Omega$  is in parallel with  $R_2 = 20 \, \Omega$

$$\therefore 50 \, \Omega \parallel 20 \, \Omega = \frac{50 \times 20}{50 + 20} \, \Omega$$

$$\therefore 50 \, \Omega \parallel 20 \, \Omega = 14.2857 \, \Omega$$

Now,  $14.2857 \, \Omega$  is in parallel with  $R_3 = 10 \, \Omega$

$$\therefore 14.2857 \, \Omega \parallel 10 \, \Omega = \frac{14.2857 \times 10}{14.2857 + 10} \, \Omega$$

$$\therefore 14.2857 \, \Omega \parallel 10 \, \Omega = 5.8824 \, \Omega$$

$$R_{th} = 5.8824 \, \Omega$$

**Case 2 :** To determine  $I_{SC}$

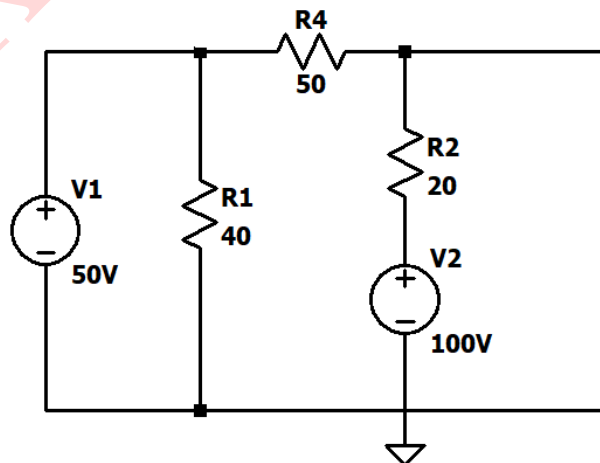


Figure 63: To determine  $I_{SC}$

Here,  $R_2$  becomes redundant due to the branch AB being replaced by a short circuit.

When only 50V voltage source is active

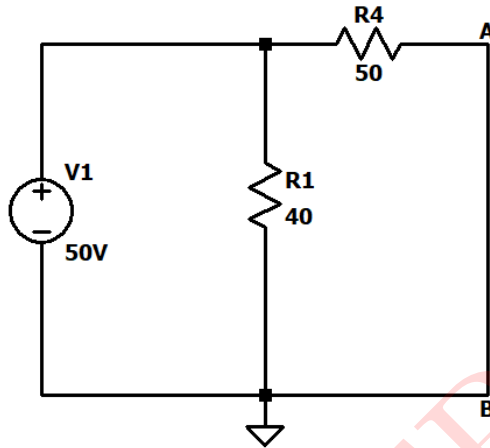


Figure 64: When only 50V voltage source is active

Current  $I_1$  flowing through AB in clockwise direction is

$$I_1 = \frac{V_1}{R_4}$$

$$\therefore I_1 = \frac{50}{50}$$

$$\therefore I_1 = 1\text{A} \quad \dots(1)$$

When only 100V voltage source is active

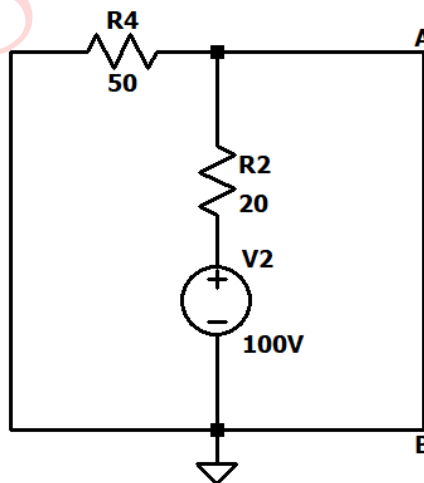


Figure 65: When only 100V voltage source is active

The current  $I_2$  flowing through AB in clockwise direction is

$$I_2 = \frac{V_2}{R_2}$$

$$\therefore I_2 = \frac{-100}{20}$$

$$\therefore I_2 = -5\text{A} \quad \dots(2)$$

Now, using Superposition Theorem

The current flowing through branch AB is

$$I_{AB} = I_1 + I_2$$

$$\therefore I_{AB} = 1 - 5$$

$$\therefore I_{AB} = -4\text{A}$$

Here the negative sign denotes that the current is flowing in anti-clockwise direction.

$$\therefore I_{SC} = 4\text{A}$$

**Norton's Equivalent circuit**

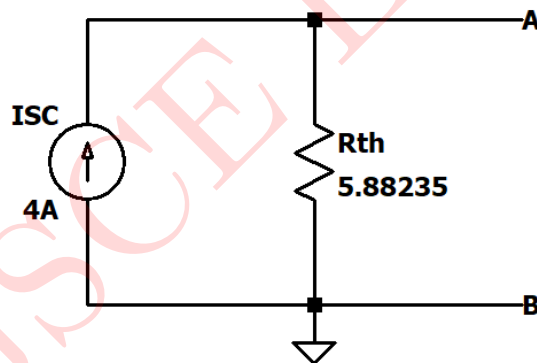


Figure 66: Norton's equivalent circuit

Now, voltage across branch AB is

$$V_{AB} = I_{SC} \times R_{th}$$

$$\therefore V_{AB} = 4 \times 5.8824$$

$$\therefore V_{AB} = \mathbf{23.5V}$$

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

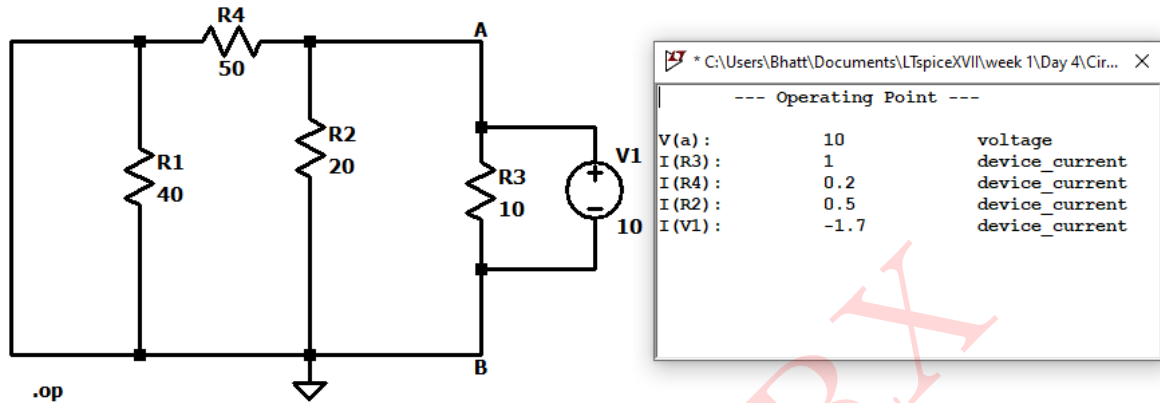


Figure 67: Circuit Schematic and Simulated Results: To determine  $R_{th}$

#### Calculation:

$$R_{th} = \frac{V_1}{I_{V1}}$$

$$\therefore R_{th} = \frac{10}{1.7}$$

$$\therefore R_{th} = 5.8824 \Omega$$

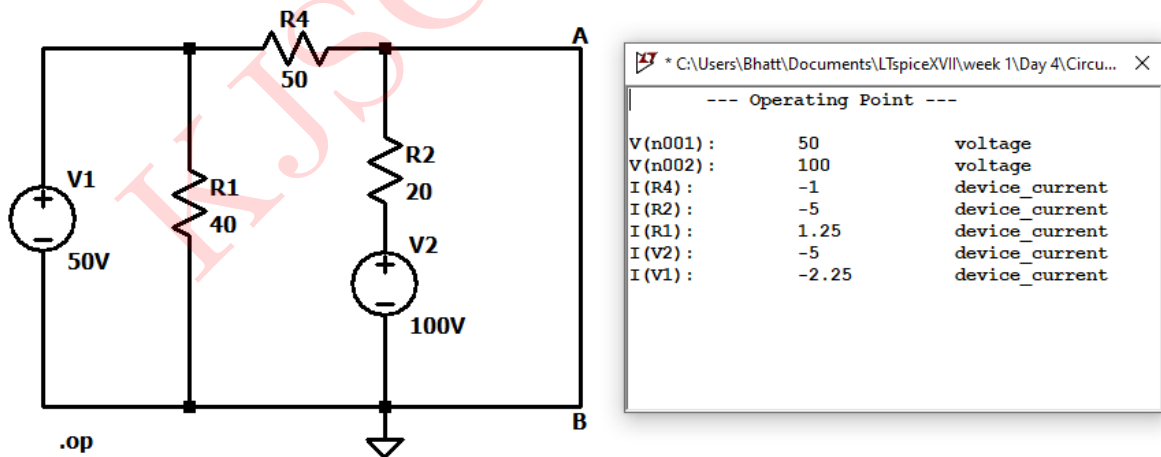


Figure 68: Circuit Schematic and Simulated Results: To determine  $I_{SC}$

#### Calculation:

$$I_{SC} = I_{R4} - I_{R2}$$

$$\therefore I_{SC} = 5 - 1$$

$$\therefore I_{SC} = 4A$$

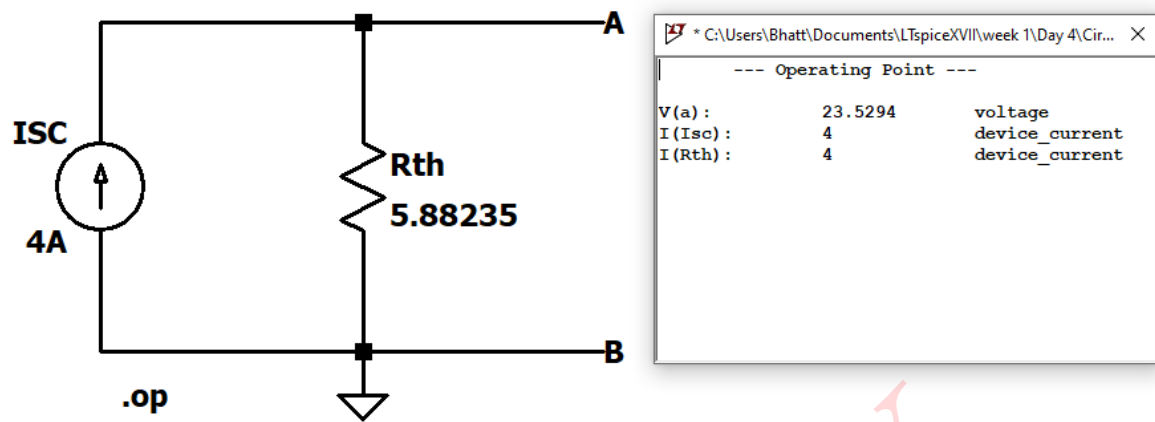


Figure 69: Circuit Schematic and Simulated Results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$V_{th}$	23.5V	23.5V

Table 7: Numerical 7

**Numerical 8:** Obtain Norton's Equivalent of terminal a-b and c-d of circuit 8 shown in figure 70

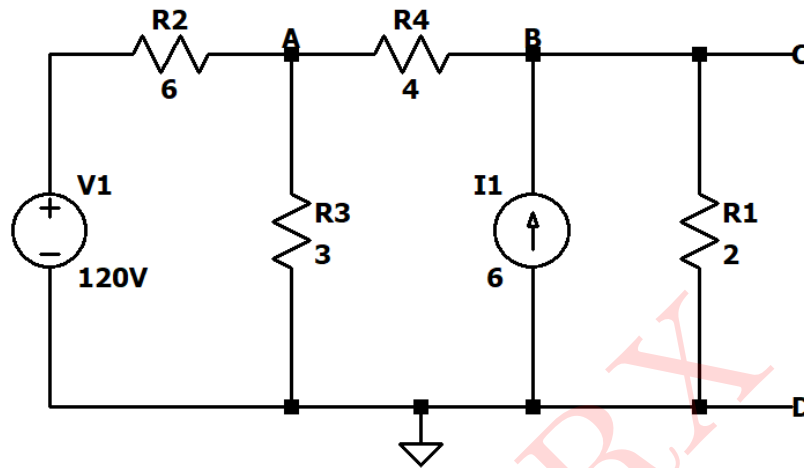


Figure 70: Circuit 8

i) Terminal A-B

**Solution:**

**Case 1:** To determine  $R_{th}$

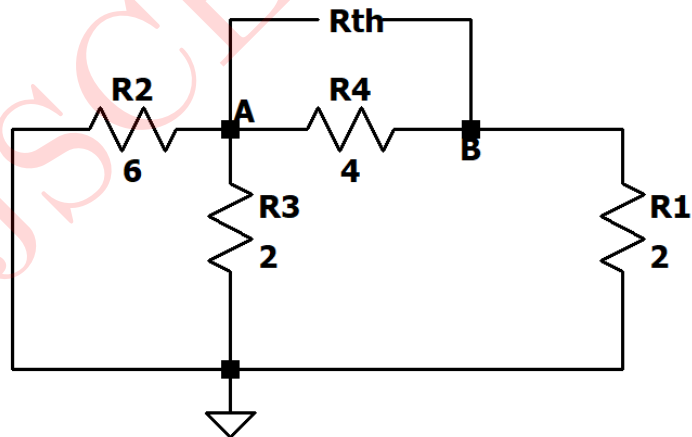


Figure 71: To determine  $R_{th}$

Now, resistors  $R_2 = 6 \Omega$  is in parallel with  $R_3 = 3 \Omega$

$$\therefore 6 \Omega \parallel 3 \Omega = \frac{6 \times 3}{6 + 3} \Omega$$

$$\therefore 6 \Omega \parallel 3 \Omega = 2 \Omega$$

The circuit is reduced to figure 72

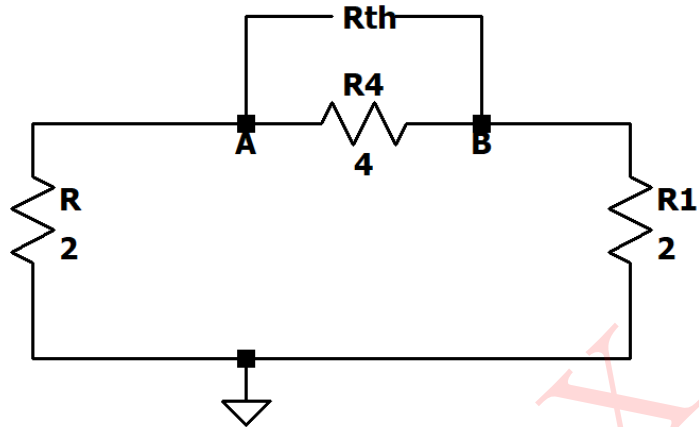


Figure 72: Modified circuit for figure 71

Now, resistors  $2\ \Omega$  and  $2\ \Omega$  are in series.

$$2\ \Omega + 2\ \Omega = 4\ \Omega$$

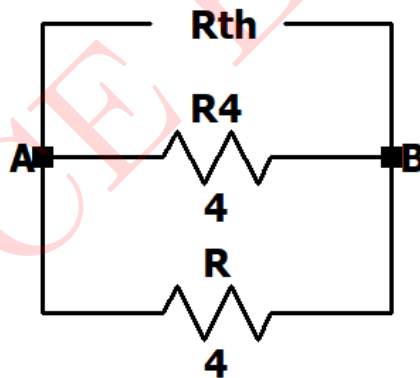


Figure 73: Modified circuit for figure 72

Here, resistors  $R = 4\ \Omega$  and  $R_4 = 4\ \Omega$  are in parallel.

$$\therefore 4\ \Omega \parallel 4\ \Omega = \frac{4 \times 4}{4 + 4}\ \Omega$$

$$\therefore 4\ \Omega \parallel 4\ \Omega = 2\ \Omega$$

$$\therefore R_{th} = 2\ \Omega$$

**Case 2:** To determine  $I_{SC}$

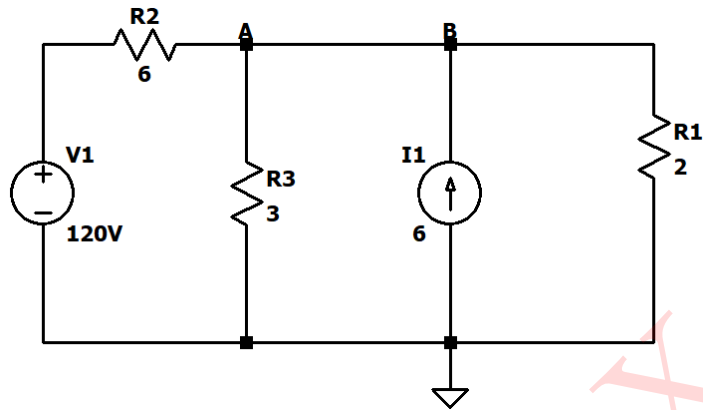


Figure 74: To determine  $I_{SC}$

Using Source transformation,

$$V_2 = I_1 \times R_1$$

$$\therefore V_2 = 6 \times 2$$

$$\therefore V_2 = 12\text{A}$$

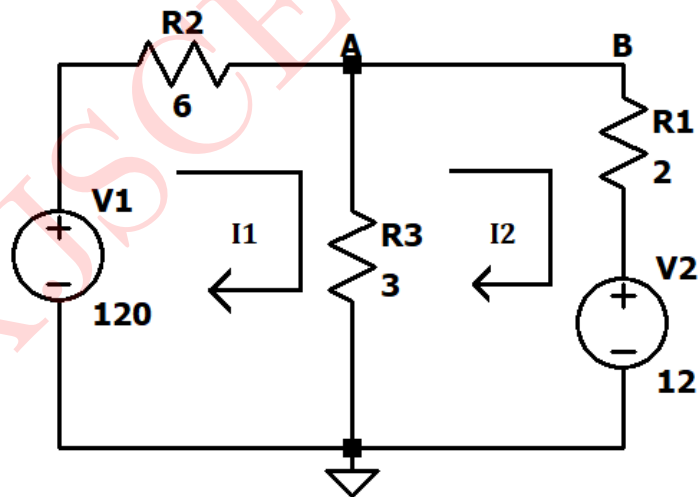


Figure 75: Source transformation modified circuit for figure 74



Let  $I_1$  and  $I_2$  be the current flowing through Mesh 1 and Mesh 2 in clockwise direction

Applying KVL to the Mesh 1,

$$-6I_1 - 3(I_1 - I_2) + 120 = 0$$

$$\therefore -6I_1 - 3I_1 + 3I_2 + 120 = 0$$

$$\therefore -9I_1 + 3I_2 + 120 = 0$$

$$\therefore 9I_1 - 3I_2 = 120 \quad \dots(1)$$

Applying KVL to the Mesh 2,

$$-2I_2 - 3(I_2 - I_1) + 12 = 0$$

$$\therefore -2I_2 - 3I_2 + 3I_1 - 12 = 0$$

$$\therefore -5I_2 + 3I_1 - 12 = 0$$

$$\therefore 3I_1 - 5I_2 = 12 \quad \dots(2)$$

Solving equation (1) and (2) simultaneously, we get

$$I_1 = 15.6667A$$

$$I_2 = 7A$$

Here, current flowing through Mesh 2 is  $I_{SC}$

$$\therefore I_{SC} = I_2 = 7A$$

**Norton's Equivalent circuit**

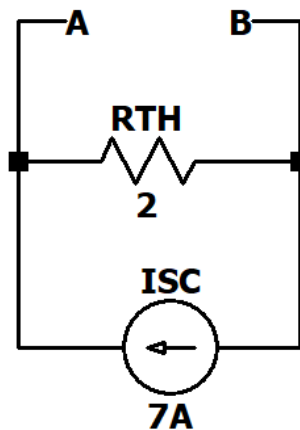


Figure 76: Norton's equivalent circuit

ii) Terminal C-D

**Solution:**

**Case 1:** To determine  $R_{th}$

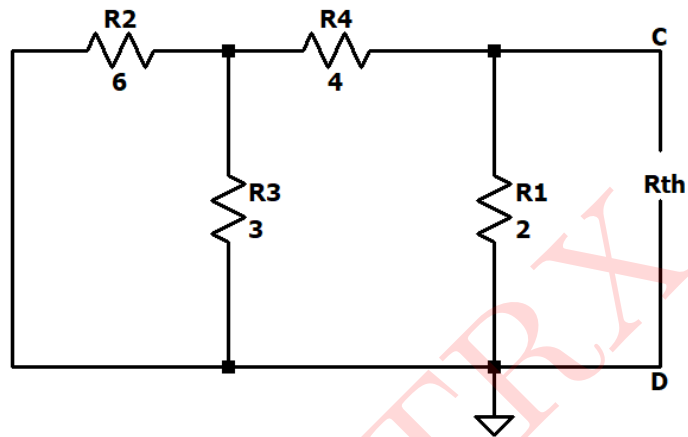


Figure 77: To determine  $R_{th}$

Resistors  $R_2 = 6 \Omega$  is in parallel with  $R_3 = 3 \Omega$

$$\therefore 6 \Omega \parallel 3 \Omega = \frac{6 \times 3}{6 + 3} \Omega$$

$$\therefore 6 \Omega \parallel 3 \Omega = 2 \Omega$$

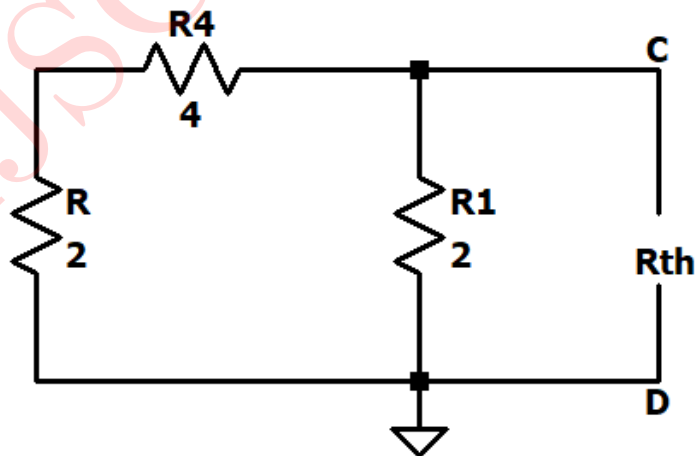


Figure 78: Modified circuit for figure 77

Now, resistor  $2 \Omega$  and  $4 \Omega$  are in series.

$$2 \Omega + 4 \Omega = 6 \Omega$$

Also, resistors  $R_1 = 2 \Omega$  is in parallel with  $R = 6 \Omega$

$$\therefore 2 \Omega \parallel 6 \Omega = \frac{2 \times 6}{2 + 6} \Omega$$

$$\therefore 2 \Omega \parallel 6 \Omega = 1.5 \Omega$$

$$R_{th} = 1.5 \Omega$$

**Case 2:** To determine  $I_{SC}$

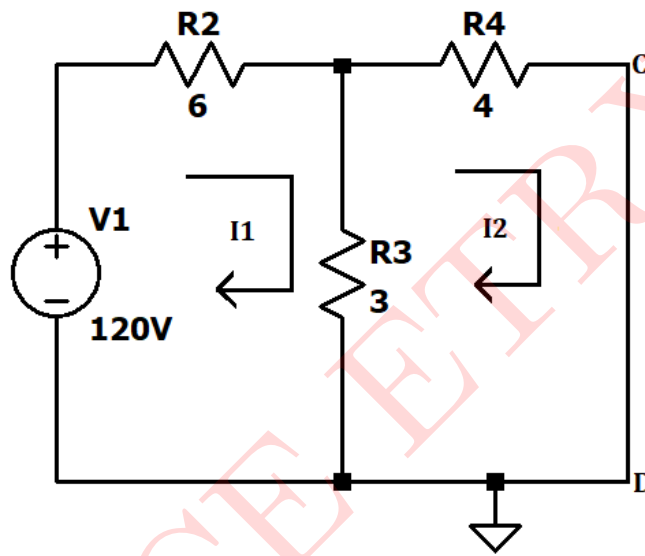


Figure 79: To determine  $I_{SC}$

Let  $I_1$  and  $I_2$  be the current flowing through Mesh 1 and Mesh 2 in clockwise direction

Applying KVL to the Mesh 1,

$$-6I_1 - 3(I_1 - I_2) + 120 = 0$$

$$\therefore -6I_1 - 3I_1 + 3I_2 + 120 = 0$$

$$\therefore -9I_1 + 3I_2 + 120 = 0$$

$$\therefore 9I_1 - 3I_2 = 120 \quad \dots(1)$$

Applying KVL to the Mesh 2,

$$-4I_2 - 3(I_2 - I_1) = 0$$

$$\therefore -4I_2 - 3I_2 + 3I_1 = 0$$

$$\therefore -7I_2 + 3I_1 = 0$$

$$\therefore 3I_1 - 7I_2 = 0 \quad \dots(2)$$

Solving equation (1) and (2) simultaneously, we get

$$I_1 = 15.5556A$$

$$I_2 = 6.6667A$$

Here,  $I_{SC}$  is the current flowing through Mesh 2

$$\therefore I_{SC} = I_2 = 6.6667 \text{ A}$$

**Norton's Equivalent circuit**

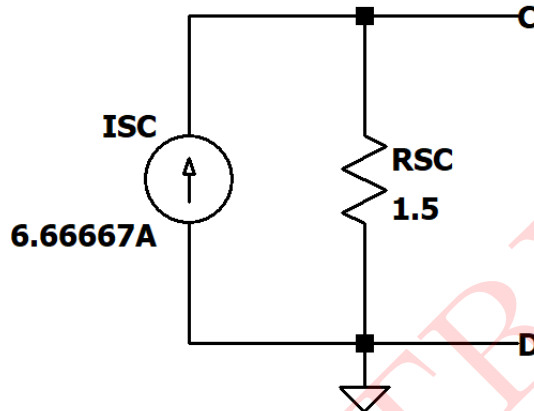


Figure 80: Norton's equivalent circuit

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

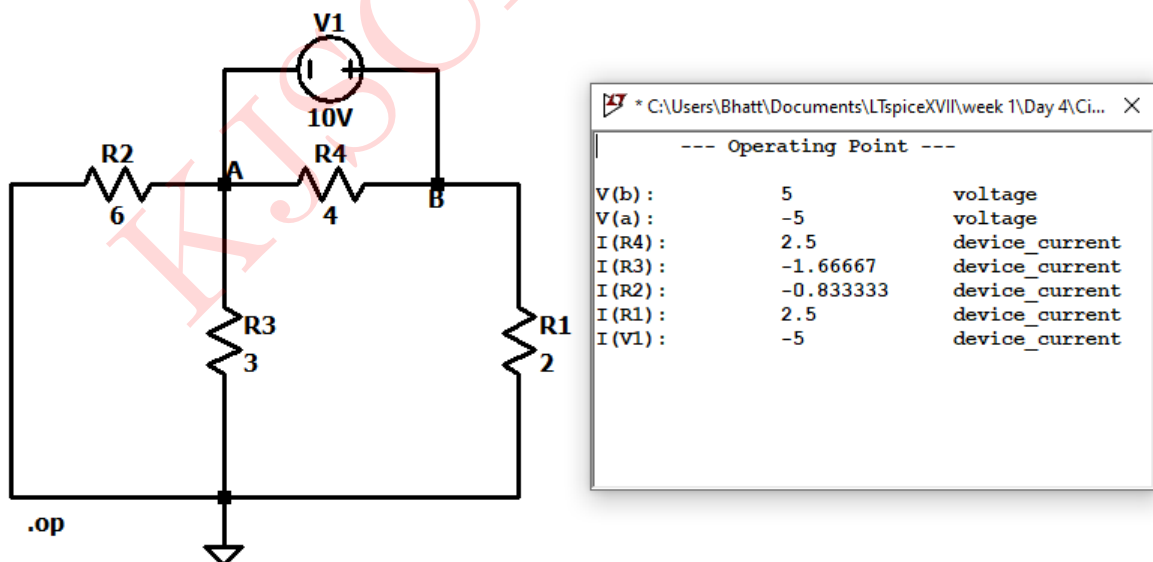


Figure 81: Circuit Schematic and Simulated Results: To determine  $R_{th}$  at terminal A-B

**Calculation:**

$$R_{th} = \frac{V_1}{I_{V1}}$$

$$R_{th} = \frac{10}{5}$$

$$R_{th} = 2 \Omega$$

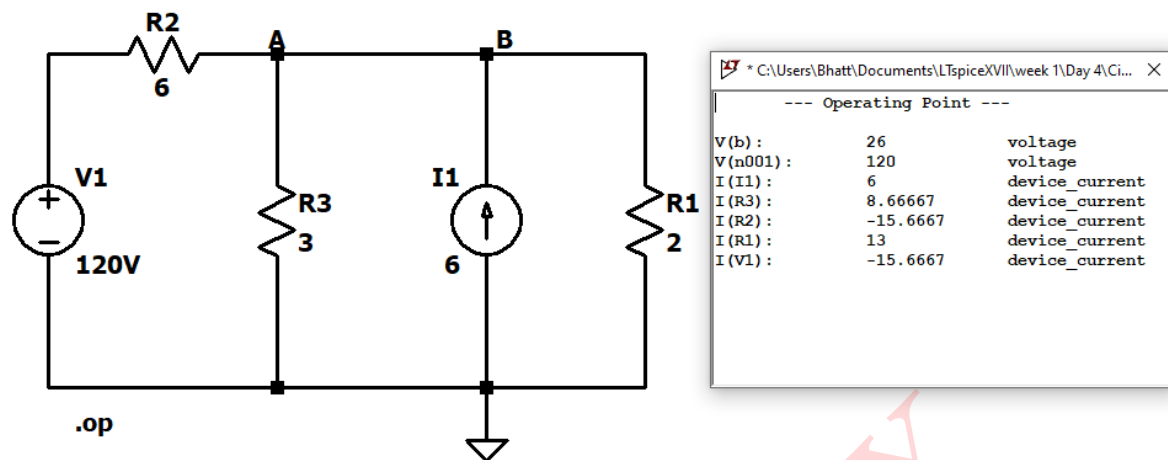


Figure 82: Circuit Schematic and Simulated Results: To determine  $I_{SC}$  at terminal A-B

**Calculation:**

$$I_{SC} = I_{R2} + I_{R3}$$

$$I_{SC} = 15.6667 - 8.6667$$

$$I_{SC} = 7A$$

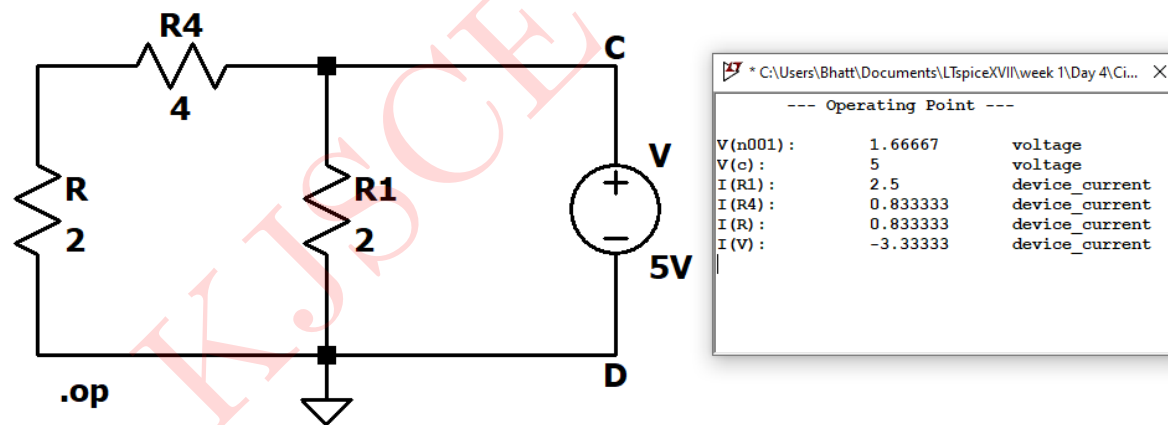


Figure 83: Circuit Schematic and Simulated Results: To determine  $R_{th}$  at terminal C-D

**Calculation:**

$$R_{th} = \frac{V_1}{I_{V1}}$$

$$R_{th} = \frac{5}{3.33}$$

$$R_{th} = 1.5 \Omega$$

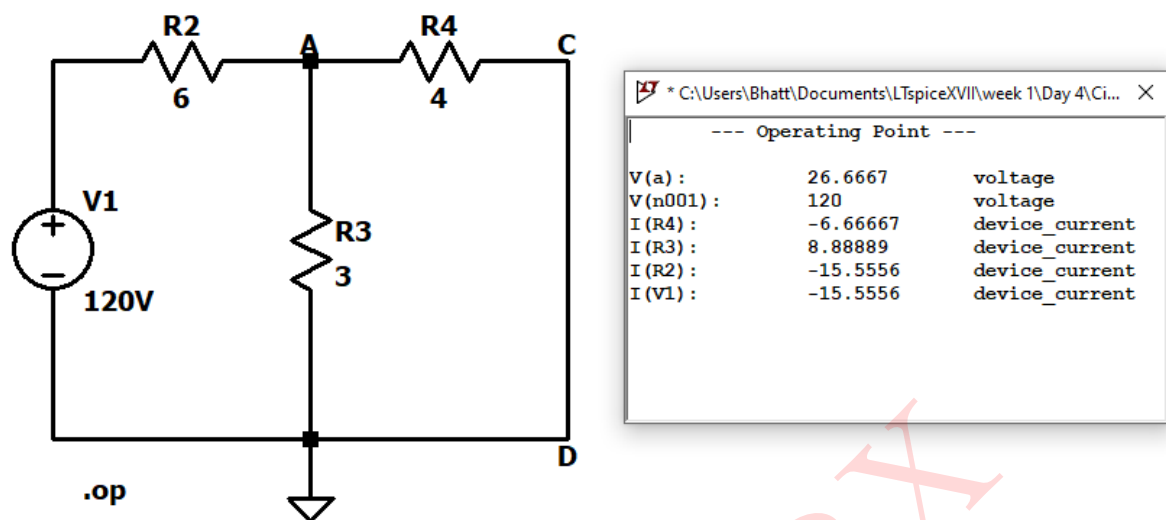


Figure 84: Circuit Schematic and Simulated Results: To determine  $I_{SC}$  at terminal C-D

#### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$R_{th}$	4 $\Omega$	4 $\Omega$
$I_{SC}$	7A	7A

Table 8: Numerical 8 : Terminal A-B

Parameters	Theoretical Values	Simulated Values
$R_{th}$	1.5 $\Omega$	1.5 $\Omega$
$I_{SC}$	6.6667A	6.6667A

Table 9: Numerical 8 : Terminal C-D

**Numerical 9:** Use Norton's theorem to find  $V_0$  in circuit 9 shown in figure 85

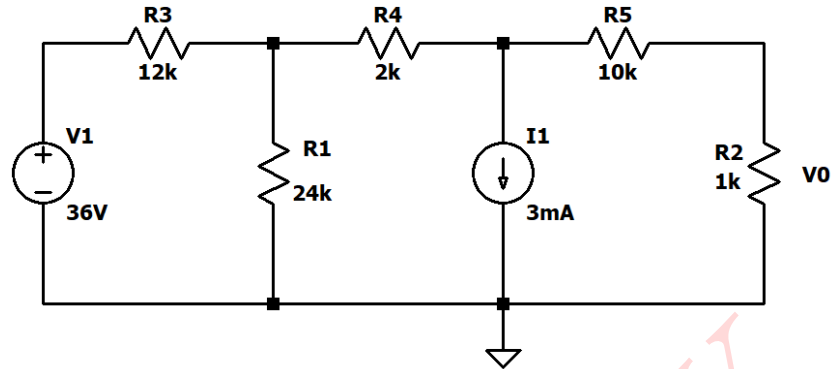


Figure 85: Circuit 9

**Solution:**

**Case 1:** To determine  $R_{th}$

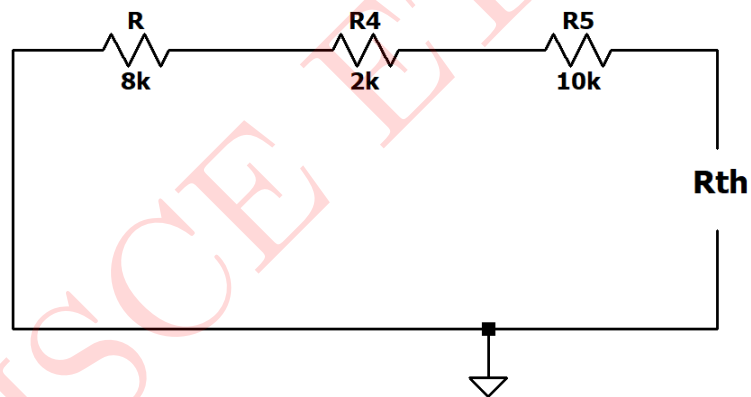


Figure 86: To determine Norton's resistance ( $R_{th}$ )

Resistors  $R_1 = 24 \text{ k}\Omega$  and  $R_3 = 12 \text{ k}\Omega$  are in parallel.

$$\therefore 24 \text{ k}\Omega \parallel 12 \text{ k}\Omega = \frac{24 \times 12}{24 + 12} \Omega$$

$$\therefore 24 \text{ k}\Omega \parallel 12 \text{ k}\Omega = 8 \text{ k}\Omega$$

Thus, the circuit is reduced to figure 87

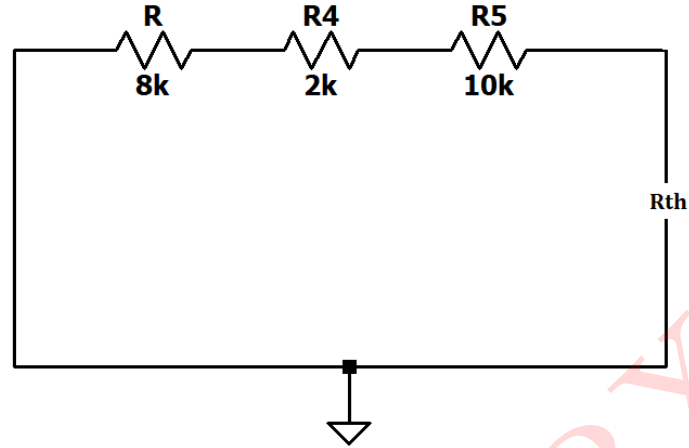


Figure 87: Modified circuit for figure 86

Now, resistor 2 k $\Omega$ , 8 k $\Omega$  and 10 k $\Omega$  are in series.

$$\therefore 2 \text{ k}\Omega + 8 \text{ k}\Omega + 10 \text{ k}\Omega = 20 \text{ k}\Omega$$

$$\therefore R_{th} = 20 \text{ k}\Omega$$

**Case 2:** To determine  $I_{SC}$

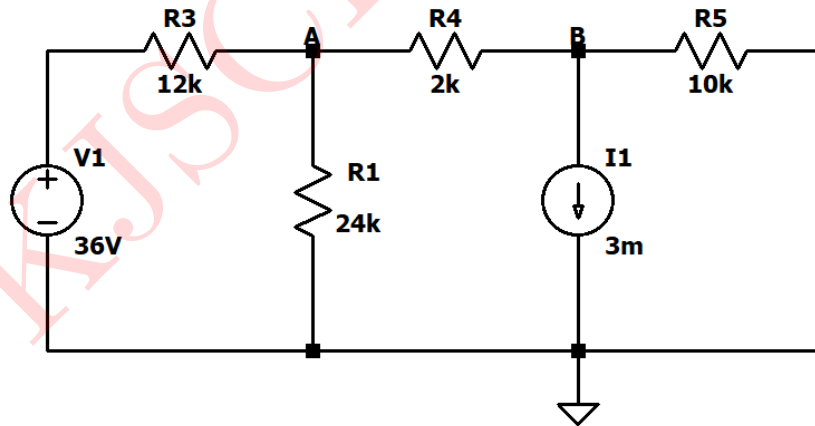


Figure 88: To determine  $I_{SC}$

Applying KCL at Node A,

$$\frac{V_A - 36}{12} + \frac{V_A}{24} + \frac{V_A - V_B}{2} = 0$$

$$\therefore 0.625V_A - 0.5V_B - 3 = 0$$

$$\therefore 0.625V_A - 0.5V_B = 3 \quad \dots(1)$$



Applying KCL at Node B,

$$\frac{V_B - V_A}{2} + 3 + \frac{V_B}{10} = 0$$

$$\therefore -0.5V_A + 0.6V_B - 3 = 0$$

$$\therefore 0.5V_A - 0.6V_B = 3 \quad \dots(2)$$

Solving equation (1) and (2) simultaneously, we get

$$V_A = 2.4\text{V}$$

$$V_B = 3\text{V}$$

Now, current flowing through  $R_4 = 10\text{ k}\Omega$  is

$$I_{10\text{k}\Omega} = \frac{V_B}{10\text{k}}$$

$$I_{10\text{k}\Omega} = \frac{3}{10\text{k}}$$

$$I_{10\text{k}\Omega} = 0.3\text{ mA}$$

$$\text{Also, } I_{SC} = I_{10\text{k}\Omega}$$

$$\therefore I_{SC} = \mathbf{0.3\text{ mA}}$$

**Norton's Equivalent circuit**

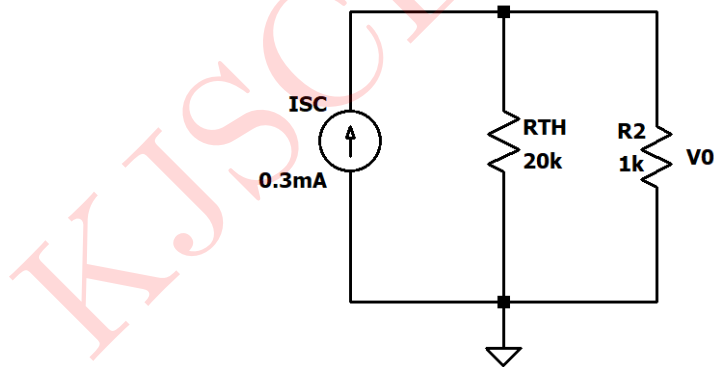


Figure 89: Norton's equivalent circuit

Resistor  $20\text{ k}\Omega$  and  $1\text{ k}\Omega$  are in parallel.

$$\therefore 10\text{ k}\Omega \parallel 1\text{ k}\Omega = \frac{10 \times 1}{10 + 1}\text{ k}\Omega$$

$$\therefore 10\text{ k}\Omega \parallel 1\text{ k}\Omega = 0.9523\text{ k}\Omega$$

Now,

$$V_0 = I_{SC} \times 0.9523 \text{ k}\Omega$$

$$V_0 = 0.3 \text{ mA} \times 0.9523 \text{ k}\Omega$$

$$V_0 = \mathbf{0.28571V}$$

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

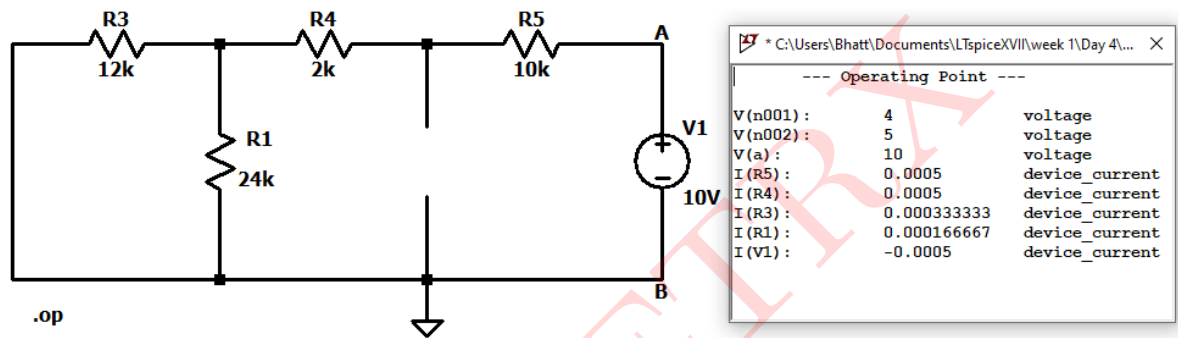


Figure 90: Circuit Schematic and Simulated Results: To determine  $R_{th}$

### Calculation:

$$R_{th} = \frac{V_1}{I_{V1}}$$

$$R_{th} = \frac{10}{0.0005}$$

$$R_{th} = 20 \text{ k}\Omega$$

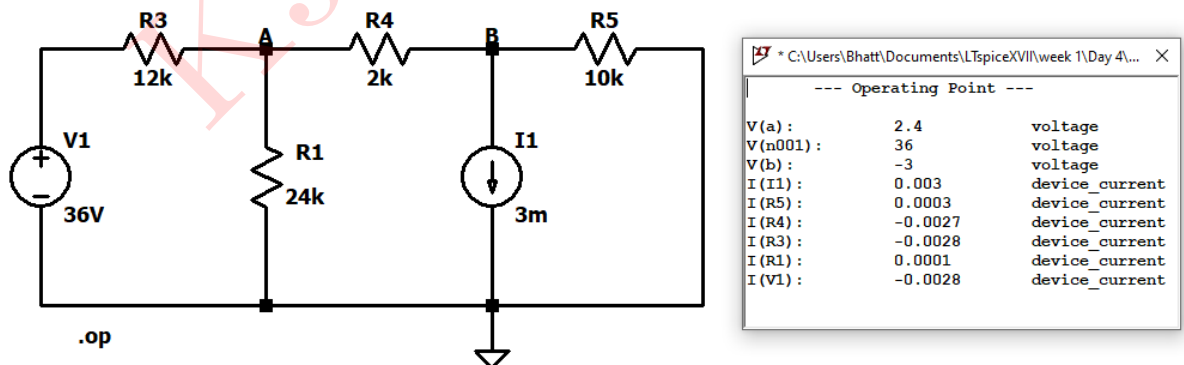


Figure 91: Circuit Schematic and Simulated Results: To determine  $I_{SC}$

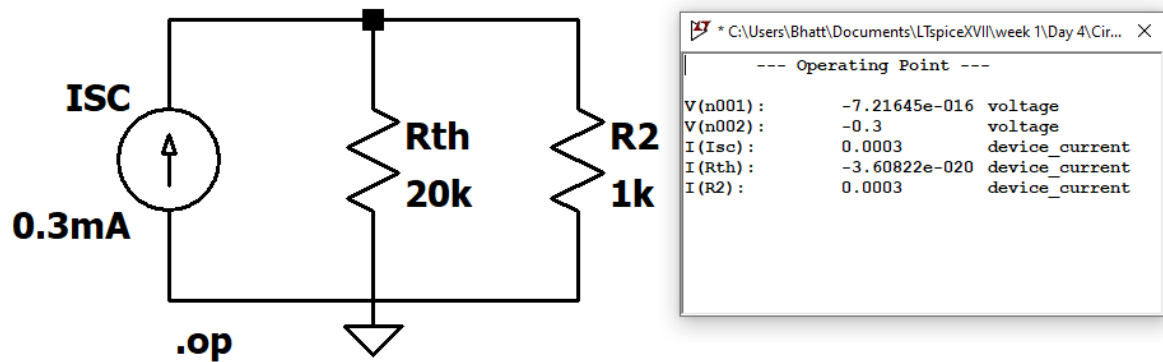


Figure 92: Circuit Schematic and Simulated Results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$V_0$	0.28571V	0.28571V

Table 10: Numerical 9

**Numerical 10:** In the circuit shown in figure 93, obtain the condition from maximum power transfer to the load  $R_L$ . Hence, determine the maximum power transferred.

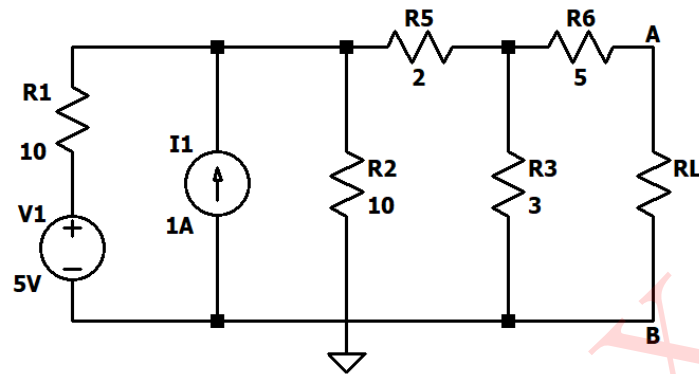


Figure 93: Circuit 10

**Solution:**

**Case 1:** To determine  $R_{th}$

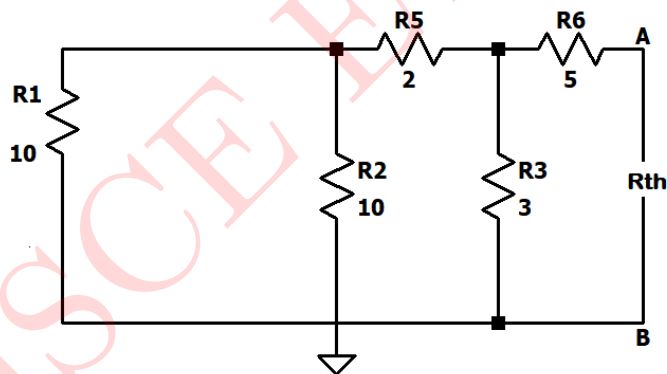


Figure 94: To determine  $R_{th}$

Here, resistor  $10\ \Omega$  is in parallel with  $10\ \Omega$

$$\therefore 10\ \Omega \parallel 10\ \Omega = \frac{10 \times 10}{10 + 10}\ \Omega$$

$$\therefore 10\ \Omega \parallel 10\ \Omega = \frac{100}{20}\ \Omega$$

$$\therefore 10\ \Omega \parallel 10\ \Omega = 5\ \Omega$$

Now, the circuit is reduced to figure 95

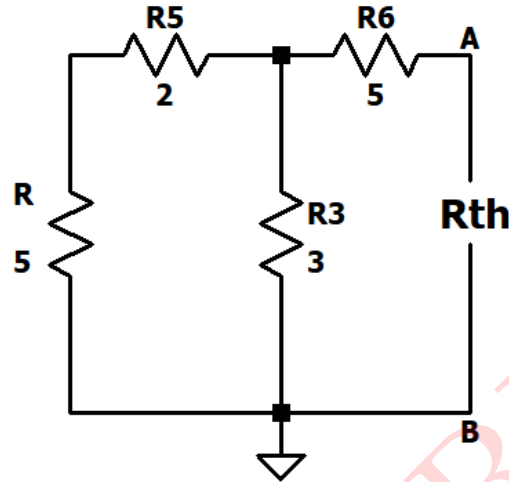


Figure 95: Modified circuit for figure 94

Resistor  $2\ \Omega$  is in series with  $5\ \Omega$

$$\therefore 2\ \Omega + 5\ \Omega = 7\ \Omega$$

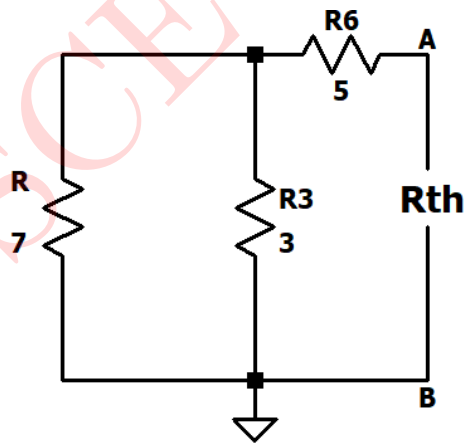


Figure 96: Modified circuit for figure 95

Now, resistor  $7\ \Omega$  is in parallel with  $3\ \Omega$

$$\therefore 7\ \Omega \parallel 3\ \Omega = \frac{7 \times 3}{7 + 3}\ \Omega$$

$$\therefore 7\ \Omega \parallel 3\ \Omega = 2.1\ \Omega$$

Also, resistor  $2.1\ \Omega$  is in series with  $5\ \Omega$

$$\therefore 2.1\ \Omega + 5\ \Omega = 7.1\ \Omega$$

$$\therefore R_{th} = 7.1\ \Omega$$

**Case 2 :** To determine  $V_{th}$

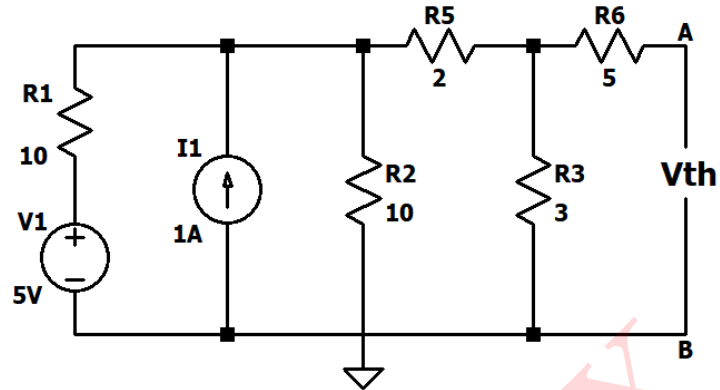


Figure 97: To determine  $V_{th}$

Using source transformation,

$$\begin{aligned}\therefore I_2 &= \frac{V_1}{R_1} \\ \therefore I_2 &= \frac{5}{10} \\ \therefore I_2 &= 0.5A\end{aligned}$$

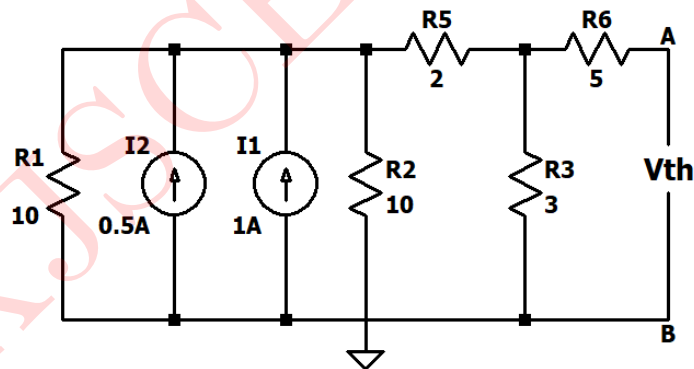


Figure 98: Source Transformation modified circuit for figure 97

Also, Current sources  $I_1$  and  $I_2$  are in parallel

$$\begin{aligned}\therefore I &= I_1 + I_2 \\ \therefore I &= 1 + 0.5 \\ \therefore I &= 1.5A\end{aligned}$$

Now, the circuit is reduced to figure 99

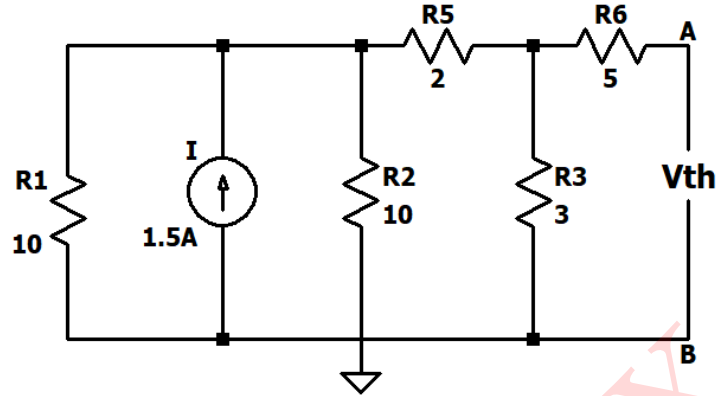


Figure 99: Modified circuit for figure 98

Here, resistor  $10\ \Omega$  is in parallel with  $10\ \Omega$

$$\therefore 10\ \Omega \parallel 10\ \Omega = \frac{10 \times 10}{10 + 10}\ \Omega$$

$$\therefore 10\ \Omega \parallel 10\ \Omega = 5\ \Omega$$

Using source transformation,

$$\therefore V = I \times R_1$$

$$\therefore V = 5 \times 1.5$$

$$\therefore V = 7.5V$$

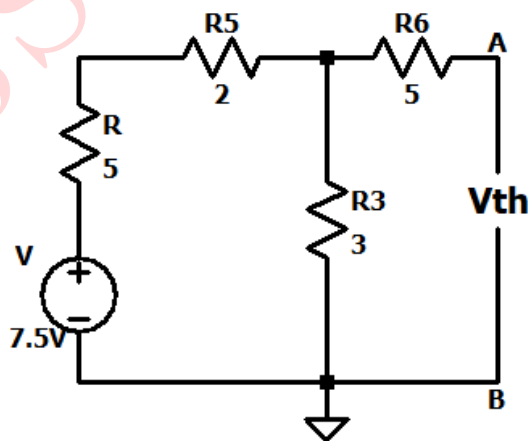


Figure 100: Source Transformation modified circuit for figure 99

Now, resistor  $2\ \Omega$  is in series with  $5\ \Omega$

$$\therefore 2\ \Omega + 5\ \Omega = 7\ \Omega$$

Using source transformation,

$$\therefore I = \frac{V_1}{R_1}$$

$$\therefore I = \frac{7.5}{7}$$

$$\therefore I = 1.0714\text{A}$$

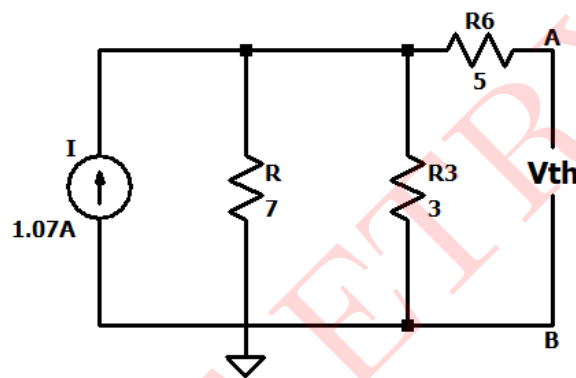


Figure 101: Source Transformation modified circuit for figure 100

Now, resistor  $7\ \Omega$  is in parallel with  $3\ \Omega$

$$\therefore 7\ \Omega \parallel 3\ \Omega = \frac{7 \times 3}{7 + 3}\ \Omega$$

$$\therefore 7\ \Omega \parallel 3\ \Omega = 2.1\ \Omega$$

Now, the circuit is reduced to figure 102

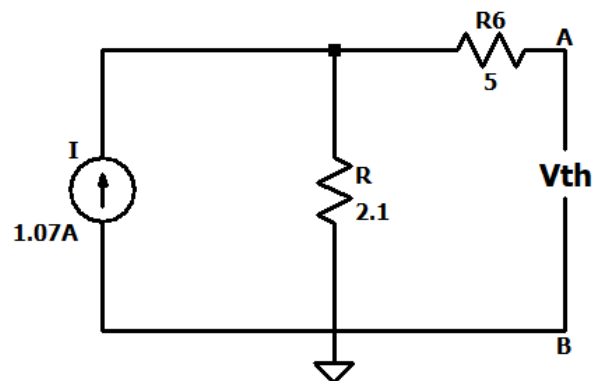


Figure 102: Modified circuit for figure 101



Now,

$$V_{th} = I \times R$$

$$\therefore V = 1.0714 \times 2.1$$

$$\therefore V = 2.25\text{V}$$

$$\therefore V_{th} = \mathbf{2.25V}$$

Also, according to Maximum Power Transfer Theorem, maximum power will be transferred to  $R_L$  when the load resistance is equal to the resistance of the network.

$$\therefore R_L = 7.1 \, \Omega$$

**Thevenin's Equivalent circuit**

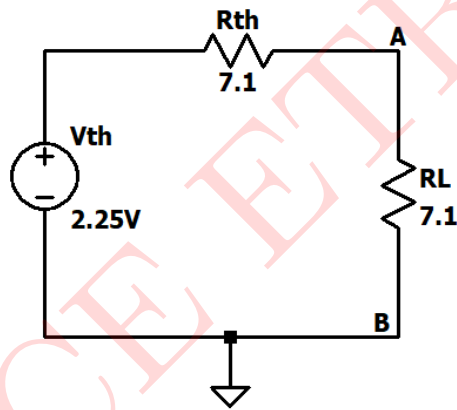


Figure 103: Thevenin's equivalent circuit

Maximum Power transferred is

$$P_{max} = \frac{V_{th} \times V_{th}}{4R_L}$$

$$P_{max} = \frac{2.25 \times 2.25}{4 \times 7.1}$$

$$P_{max} = 178.257\text{mW}$$

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

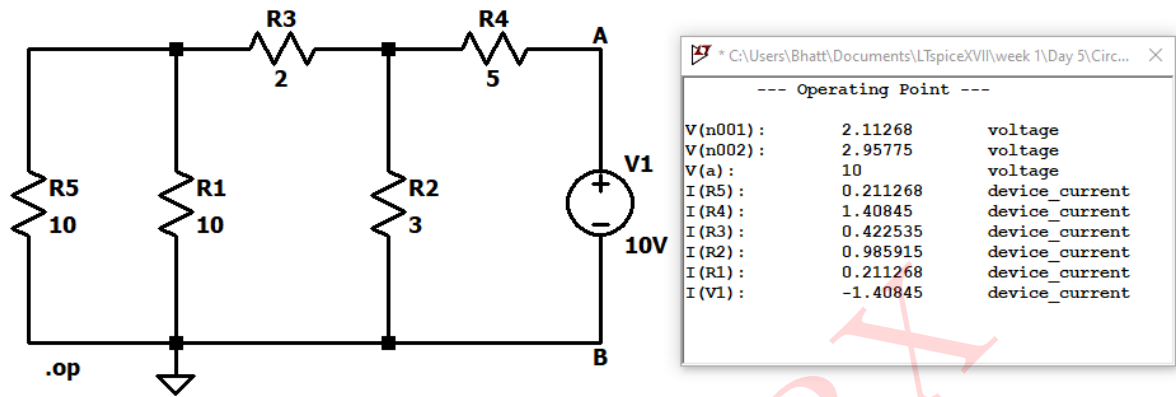


Figure 104: Circuit Schematic and Simulated Results: To determine  $R_{th}$

### Calculation:

$$R_{th} = \frac{V_1}{I_{V1}}$$

$$R_{th} = \frac{10}{1.40845}$$

$$R_{th} = 7.1 \Omega$$

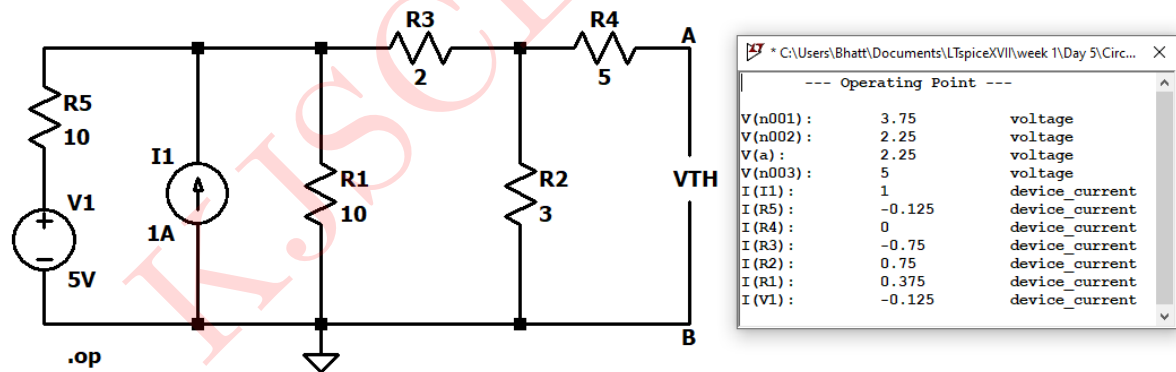


Figure 105: Circuit Schematic and Simulated Results: To determine  $V_{th}$

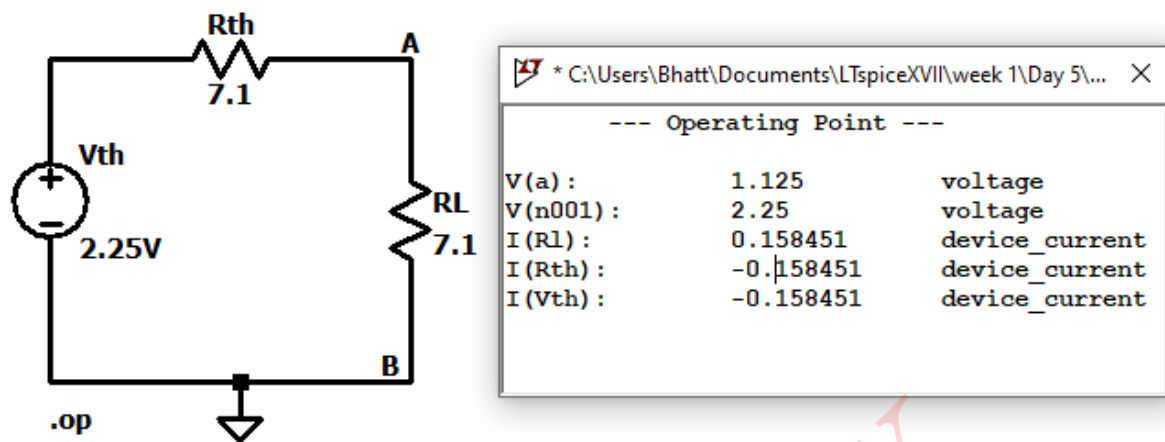


Figure 106: Circuit Schematic and Simulated Results

#### Calculation:

$$P_{max} = I \times I \times R_L$$

$$P_{max} = 0.1584 \times 0.1584 \times 7.1$$

$$P_{max} = 178.257\text{mW}$$

#### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$R_L$	7.1 $\Omega$	7.1 $\Omega$
$P_{max}$	178.257mW	178.257mW

Table 11: Numerical 10

**Numerical 11:** The variable resistor  $R$  is adjusted until it absorbs the maximum power from the circuit shown in figure 107

- Calculate the value of  $R$  for maximum power
- Determine the maximum power absorbed by  $R$

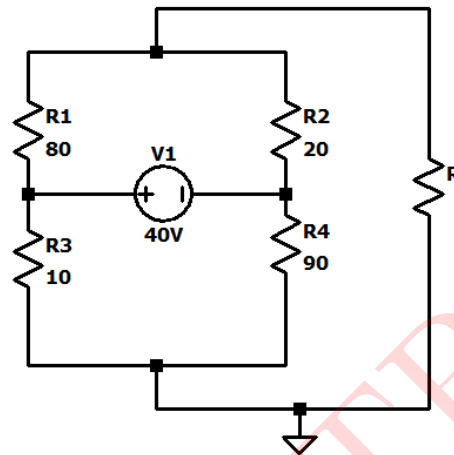


Figure 107: Circuit 11

**Solution:**

**Case 1:** To determine  $R_{th}$

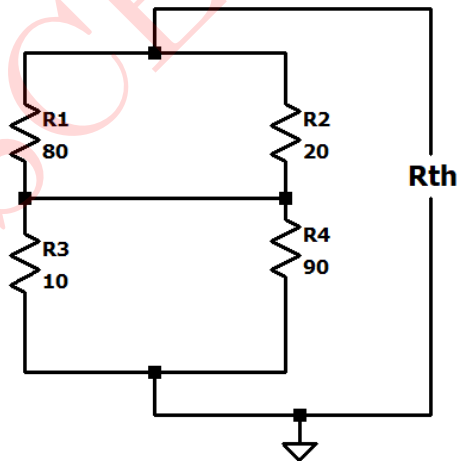


Figure 108: To determine  $R_{th}$

Here, resistor  $80\ \Omega$  is in parallel with  $20\ \Omega$

$$\therefore 80\ \Omega \parallel 20\ \Omega = \frac{80 \times 20}{80 + 20}\ \Omega$$

$$\therefore 80\ \Omega \parallel 20\ \Omega = 16\ \Omega$$

Also, resistor  $90\ \Omega$  is in parallel with  $10\ \Omega$

$$\therefore 90\ \Omega \parallel 10\ \Omega = \frac{90 \times 10}{90 + 10}\ \Omega$$

$$\therefore 90\ \Omega \parallel 10\ \Omega = 9\ \Omega$$

The circuit is reduced to figure 109

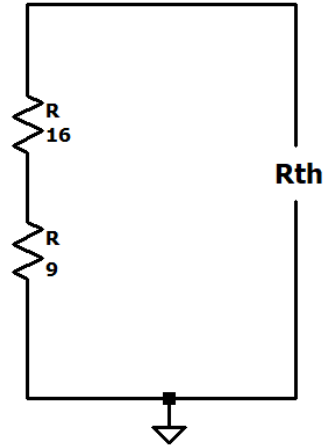


Figure 109: Modified circuit for figure 108

Also, resistor  $16\ \Omega$  is in series with  $9\ \Omega$

$$\therefore 16\ \Omega + 9\ \Omega = 25\ \Omega$$

$$\therefore R_{th} = 25\ \Omega$$

**Case 2:** To determine  $V_{th}$

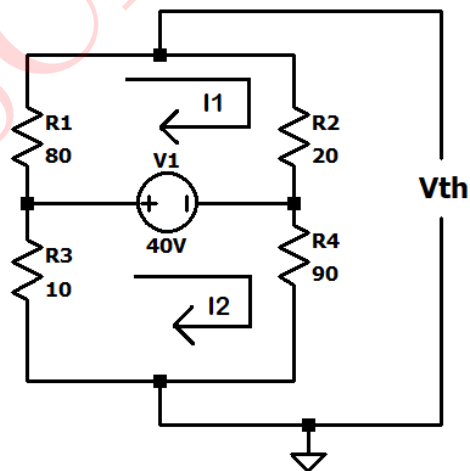


Figure 110: To determine  $V_{th}$

Let  $I_1$  and  $I_2$  be the current flowing through Mesh 1 and Mesh 2 in clockwise direction

Applying KVL to the Mesh 1,

$$-80I_1 - 20I_1 = -40$$

$$\therefore -100I_1 = -40$$

$$\therefore I_1 = \frac{40}{100}$$

$$\therefore I_1 = 0.4\text{A}$$

Applying KVL to Mesh 2,

$$-40 - 90I_2 - 10I_2 = 0$$

$$\therefore -100I_2 = 40$$

$$\therefore I_2 = \frac{40}{-100}$$

$$\therefore I_2 = -0.4\text{A}$$

The negative sign denotes that the current  $I_2$  flows in anti-clockwise direction.

Applying KVL to Mesh 3,

$$V_{th} - 90I_2 - 20I_1 = 0$$

$$\therefore V_{th} = 90I_2 + 20I_1$$

$$\therefore V_{th} = 90 \times 0.4 + 20 \times -0.4$$

$$\therefore V_{th} = 36 - 8$$

$$\therefore V_{th} = 28\text{V}$$

Now, according to Maximum Power Transfer Theorem, maximum power will be transferred to  $R$  when the load resistance is equal to the resistance of the network.

$$\therefore R = 25\Omega$$

**Thevenin's Equivalent circuit**

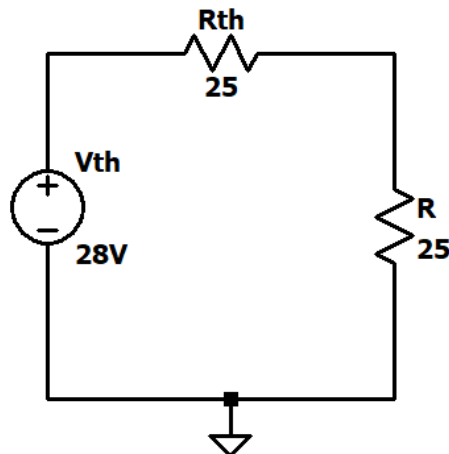


Figure 111: Thevenin's equivalent circuit

Maximum Power transferred is

$$P_{max} = \frac{V_{th} \times V_{th}}{4R_L}$$

$$P_{max} = \frac{28 \times 28}{4 \times 25}$$

$$P_{max} = 7.84 \text{ W}$$

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

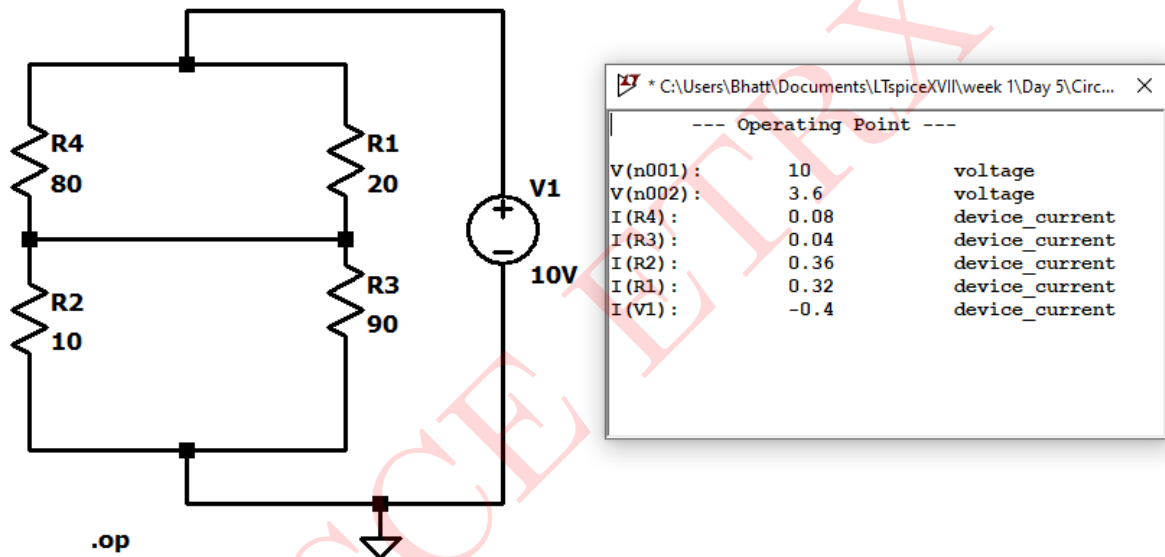


Figure 112: Circuit Schematic and Simulated Results: To determine  $R_{th}$

### Calculation:

$$R_{th} = \frac{V_1}{I_{V1}}$$

$$\therefore R_{th} = \frac{10}{0.4}$$

$$\therefore R_{th} = 25 \Omega$$

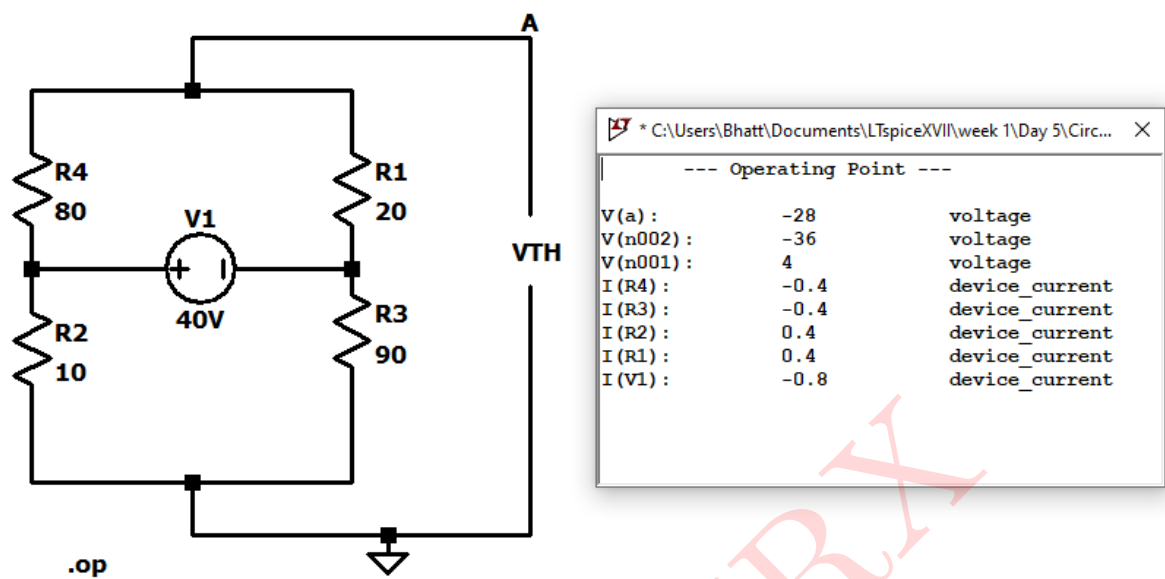


Figure 113: Circuit Schematic and Simulated Results: To determine Vth

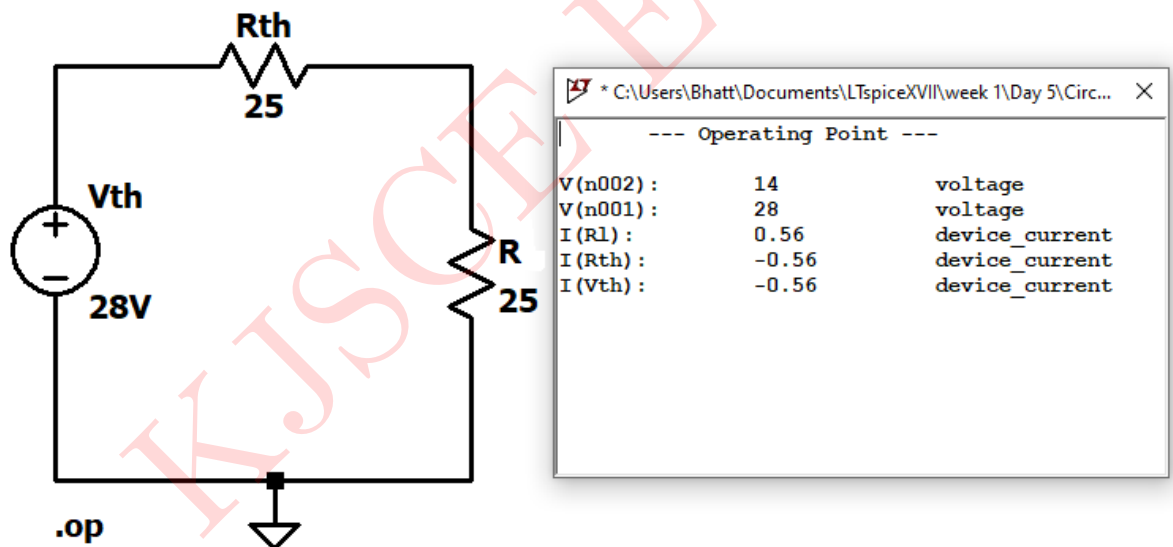


Figure 114: Circuit Schematic and Simulated Results

**Calculation:**

$$P_{max} = I \times I \times R$$

$$P_{max} = 0.56 \times 0.56 \times 25$$

$$P_{max} = 7.84W$$



Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$R$	$25\ \Omega$	$25\ \Omega$
$P_{max}$	7.84W	7.84W

Table 12: Numerical 11

KJSCE ETRX