

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Darlington Amplifier**

**Numerical 1:** A two stage circuit is shown in figure 1. Its BJT parameters are  $\beta_1 = \beta_2 = 100$ ,  $V_{BE1} = V_{BE2} = 0.7$  V. Calculate 1<sup>st</sup> and 2<sup>nd</sup> stage DC parameters, current gain, voltage gain, overall current gain and voltage gain, input impedance, output impedance and output voltage. Given:  $\beta_1 = \beta_2 = 100$

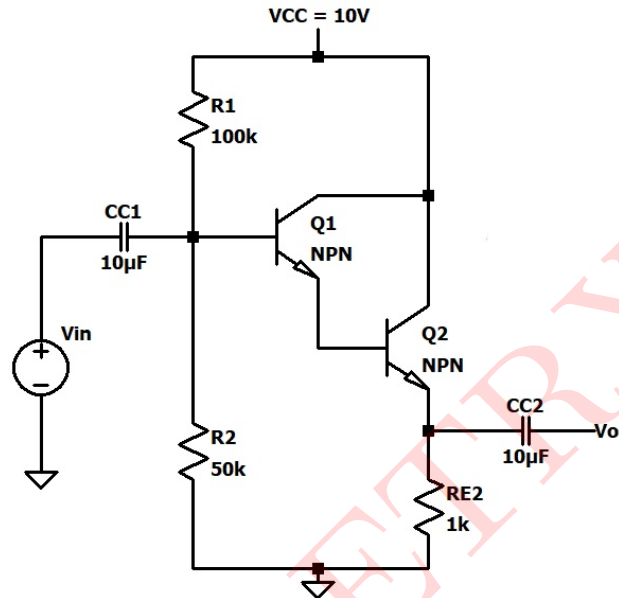


Figure 1: Circuit 1

**Solution:**

The given circuit 1 is a Darlington pair amplifier employing npn-BJT. For DC biasing, the capacitors acts as an open source.

**DC Analysis:**

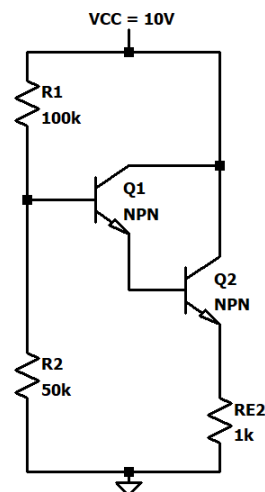


Figure 2: DC Equivalent circuit

$$V_{th} = \frac{V_{CC} \times R_2}{R_1 + R_2}$$

$$V_{th} = \frac{10 \times 50 \times 10^3}{100 \times 10^3 + 50 \times 10^3} = \mathbf{3.33 \text{ V}}$$

$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2}$$

$$R_{th} = \frac{100 \times 10^3 \times 50 \times 10^3}{100 \times 10^3 + 50 \times 10^3} = \mathbf{33.33 \text{ k}\Omega}$$

Thevenin's Equivalent Circuit:

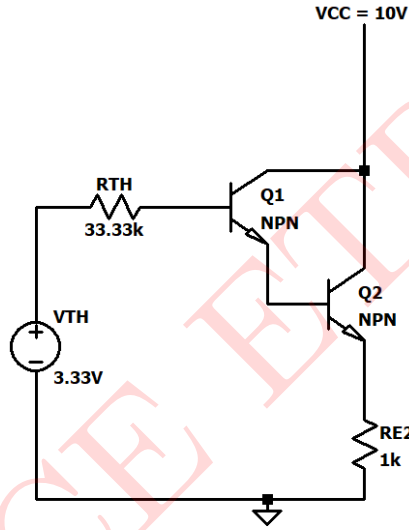


Figure 3: Thevenin's Equivalent circuit

Applying KVL to the base emitter loop,

$$V_{th} - R_{th}I_{B_1} - V_{BE_1} - V_{BE_2} - I_{E_2}R_{E_2} = 0$$

$$R_{th}I_{B_1} + (1 + \beta_1)(1 + \beta_2)I_{B_1}R_{E_2} = V_{th} - V_{BE_1} - V_{BE_2}$$

$$\dots (\because I_{E_2} = (1 + \beta_2)I_{B_2}, I_{B_2} = I_{E_1} \text{ \& } I_{E_1} = (1 + \beta_1)I_{B_1})$$

$$I_{B_1} = \frac{V_{th} - V_{BE_1} - V_{BE_2}}{R_{th} + (1 + \beta_1)(1 + \beta_2)R_{E_2}}$$

$$I_{B_1} = \frac{3.33 - 0.7 - 0.7}{33.33 \times 10^3 + (1 + 00)(1 + 100) \times 1 \times 10^3} = \mathbf{0.1889 \text{ }\mu\text{A}}$$

$$I_{C_1} = \beta_1 I_{B_1}$$

$$I_{C_1} = 100 \times 0.1889 \times 10^{-6} = \mathbf{0.01889 \text{ mA}}$$

$$I_{E_1} = (1 + \beta_1)I_{B_1}$$

$$I_{E_1} = (1 + 100) \times 0.1889 \times 10^{-6} = \mathbf{0.01907 \text{ mA}}$$

Terminal  $B_2$  is connected to terminal  $E_1$ ,

$$I_{B_2} = I_{E_1} = \mathbf{0.01907 \text{ mA}}$$

$$I_{C_2} = \beta_2 I_{B_2}$$

$$I_{C_2} = 100 \times 0.01907 \times 10^{-3} = \mathbf{1.9079 \text{ mA}}$$

$$I_{E_2} = (1 + \beta_2) I_{B_2}$$

$$I_{E_2} = (1 + 100) \times 0.01907 \times 10^{-3} = \mathbf{1.9269 \text{ mA}}$$

Voltage across terminal  $C_2$  is given as,

$$V_{C_2} = V_{CC} = \mathbf{10 \text{ V}}$$

Voltage across terminal  $E_2$  can be given as,

$$V_{E_2} = I_{E_2} R_{E_2}$$

$$V_{E_2} = 1.9269 \times 10^{-3} \times 1 \times 10^3 = \mathbf{1.9269 \text{ V}}$$

#### AC Analysis:

Small signal parameters:

$$r_{\pi_1} = \frac{\beta_1 V_T}{I_{E_1}}$$

$$r_{\pi_1} = \frac{100 \times 26 \times 10^{-3}}{0.01907 \times 10^{-3}} = \mathbf{136.339 \text{ k}\Omega}$$

$$r_{\pi_2} = \frac{\beta_2 V_T}{I_{E_2}}$$

$$r_{\pi_2} = \frac{100 \times 26 \times 10^{-3}}{1.9269 \times 10^{-3}} = \mathbf{1.349 \text{ k}\Omega}$$

$$g_{m_1} = \frac{I_{C_1}}{V_T}$$

$$g_{m_1} = \frac{0.01889 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{0.726 \text{ mA/V}}$$

$$g_{m_2} = \frac{I_{C_2}}{V_T}$$

$$g_{m_2} = \frac{1.9079 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{73.38 \text{ mA/V}}$$

Small Signal Equivalent Circuit is shown in figure 4:

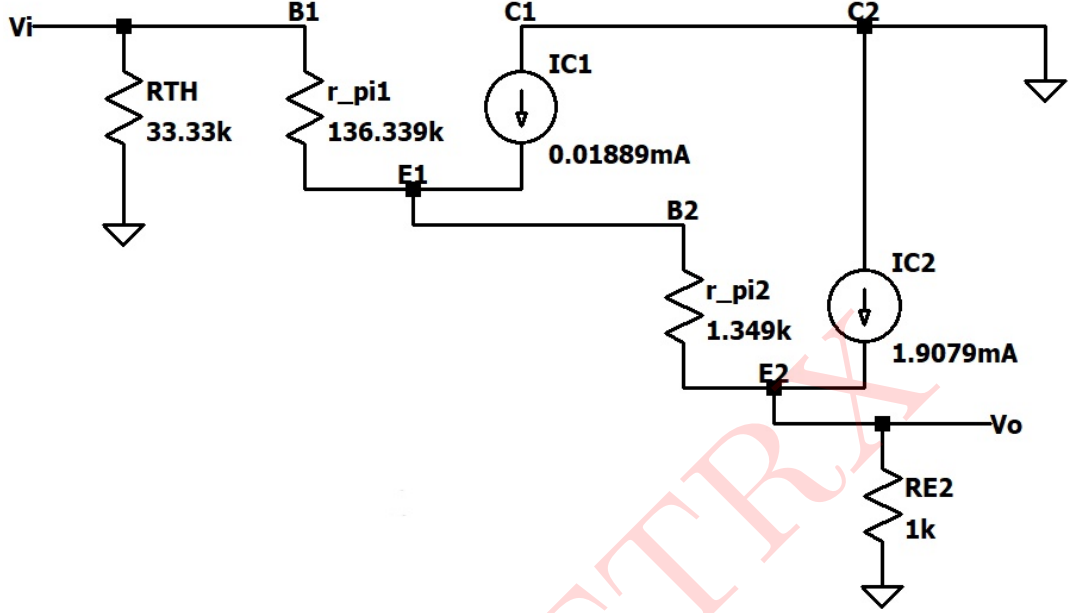


Figure 4: Small Signal Equivalent Circuit

Input impedance of stage 1:

$$Z_{i_2} = r_{\pi_2} + (1 + \beta_2)R_{E_2}$$

$$Z_{i_2} = 1.349 \times 10^3 + (1 + 100) \times 1 \times 10^3 = \mathbf{102.349 \text{ k}\Omega}$$

$$Z_{i_1} = (1 + \beta_1)Z_{i_2} + r_{\pi_1}$$

$$Z_{i_1} = (1 + 100) \times 102.349 \times 10^3 + 136.339 \times 10^3 = \mathbf{10.4735 \text{ M}\Omega}$$

$$Z_i = (R_{th} \parallel Z_{i_1})$$

$$Z_i = (33.33 \times 10^3 \parallel 10.4735 \times 10^6) = \mathbf{33.224 \text{ k}\Omega}$$

Output impedance of stage 2:

$$Z_{o_1} = \frac{R_{th} + r_{\pi_1}}{1 + \beta_1}$$

$$Z_{o_1} = \frac{33.33 \times 10^3 + 136.339 \times 10^3}{1 + 100} = \mathbf{1.679 \text{ k}\Omega}$$

$$Z_{o_2} = \frac{Z_{o_1} + r_{\pi_2}}{1 + \beta_2}$$

$$Z_{o_2} = \frac{1.679 \times 10^3 + 1.349 \times 10^3}{1 + 100} = \mathbf{29.98 \text{ }\Omega}$$

$$Z_o = Z_{o_2} \parallel R_{E_2}$$

$$Z_o = 29.98 \parallel 1 \times 10^3 = \mathbf{29.1073 \text{ }\Omega}$$

Current gain of stage 1:

$$A_{i_1} = \frac{I_{E_1}}{I_{B_1}}$$

$$A_{i_1} = \frac{(1 + \beta_1)I_{B_1}}{I_{B_1}}$$

$$A_{i_1} = (1 + \beta_1) = \mathbf{101}$$

Current gain of stage 2:

$$A_{i_2} = \frac{I_{E_2}}{I_{B_2}}$$

$$A_{i_2} = \frac{(1 + \beta_2)I_{B_2}}{I_{B_2}}$$

$$A_{i_2} = (1 + \beta_2) = \mathbf{101}$$

Overall voltage gain:

$$A_{i_T} = A_{i_1} \times A_{i_2}$$

$$A_{i_T} = 101 \times 101 = \mathbf{10201}$$

Stage 1 Voltage gain:

$$A_{V_1} = \frac{V_{o1}}{V_i}$$

$$A_{V_1} = \frac{I_{E_1} \times Z_{i_2}}{I_{B_1} \times Z_{i_1}}$$

$$A_{V_1} = A_{i_1} \times \frac{Z_{i_2}}{Z_{i_1}}$$

$$A_{V_1} = 101 \times \frac{102.349 \times 10^3}{10.4735 \times 10^6} = \mathbf{0.9869}$$

Stage 2 Voltage gain:

$$A_{V_2} = \frac{V_o}{V_{o1}}$$

$$A_{V_2} = \frac{I_o \times R_E}{I_{B_2} \times Z_{i_2}}$$

$$A_{V_2} = A_{i_2} \times \frac{R_E}{Z_{i_2}}$$

$$A_{V_2} = 101 \times \frac{1 \times 10^3}{102.349 \times 10^3} = \mathbf{0.9868}$$

Overall voltage gain:

$$A_{V_T} = A_{V_1} \times A_{V_2}$$

$$A_{V_T} = 0.9869 \times 0.9868 = \mathbf{0.9738}$$

$$A_{V_T} \text{ in dB} = 20\log_{10}(|A_{V_T}|)$$

$$A_{V_T} \text{ in dB} = 20\log_{10}(0.9738) = \mathbf{-0.2306 \text{ dB}}$$

Output Voltage:

$$V_o = A_{V_T} V_i$$

$$V_o = 0.9738 \times 100 \times 10^{-3} = 97.38 \text{ mV}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

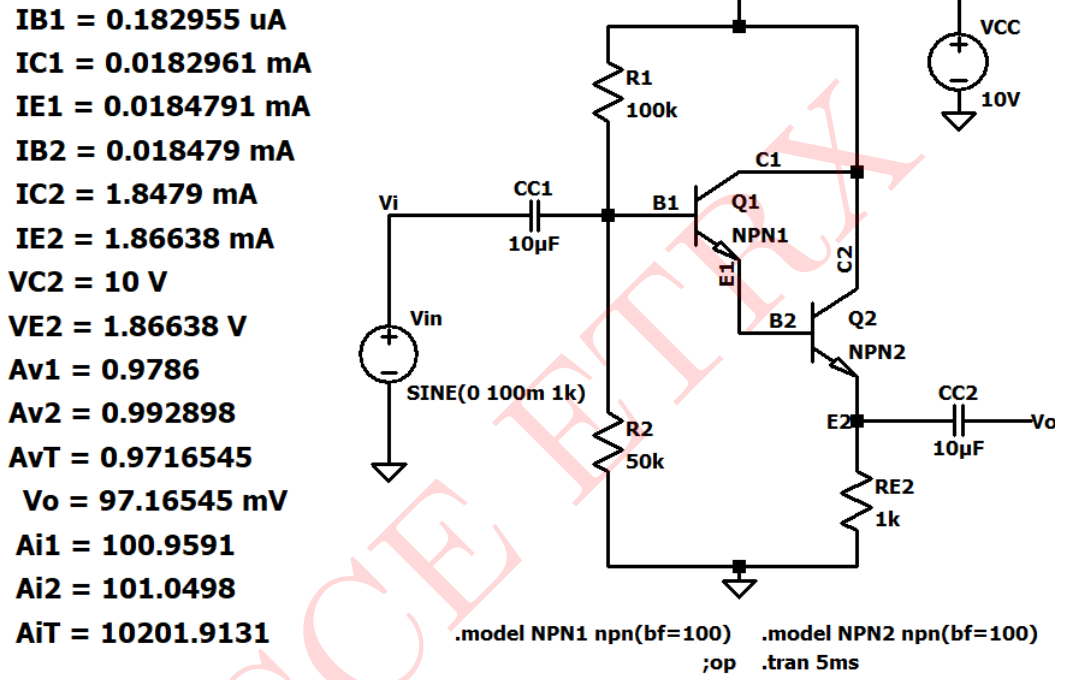


Figure 5: Circuit Schematic 1: Results

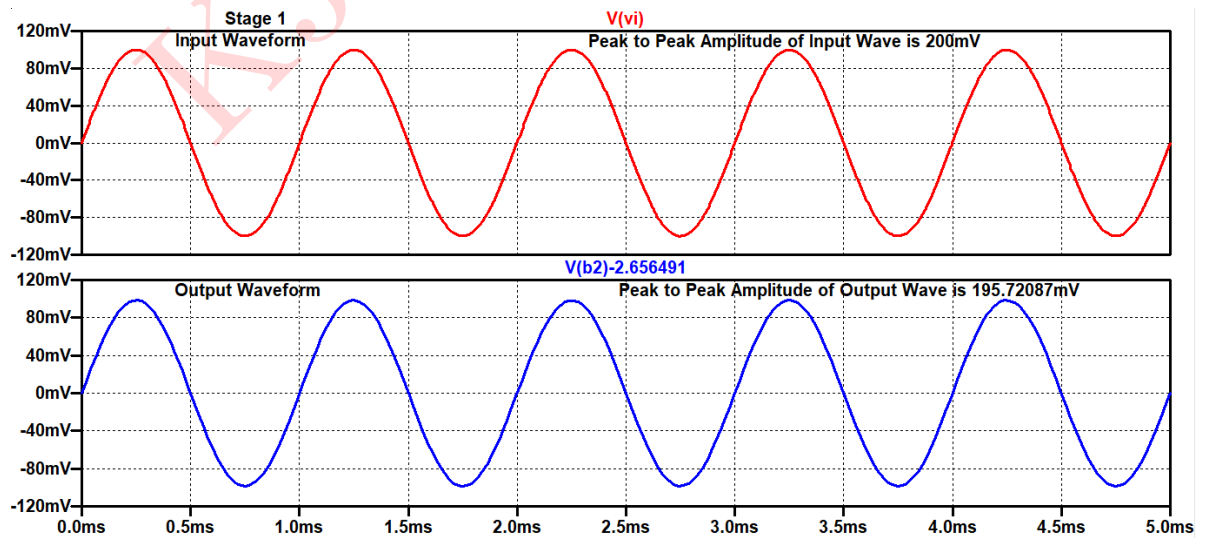


Figure 6: Input & Output waveforms for stage 1 voltage gain

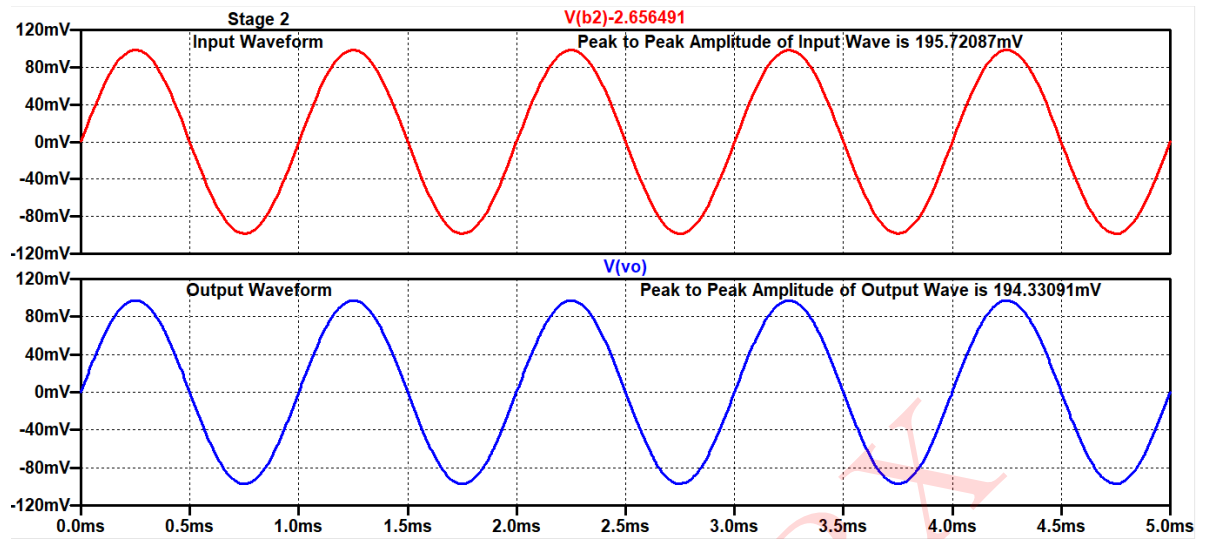


Figure 7: Input & Output waveforms for stage 2 voltage gain

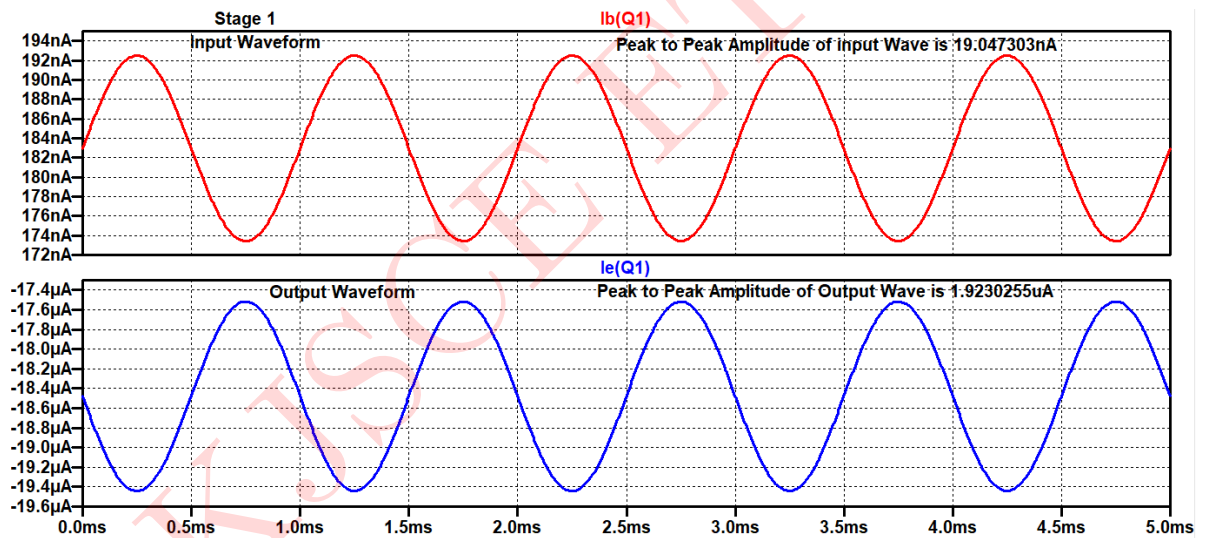


Figure 8: Input & Output waveforms for stage 1 current gain

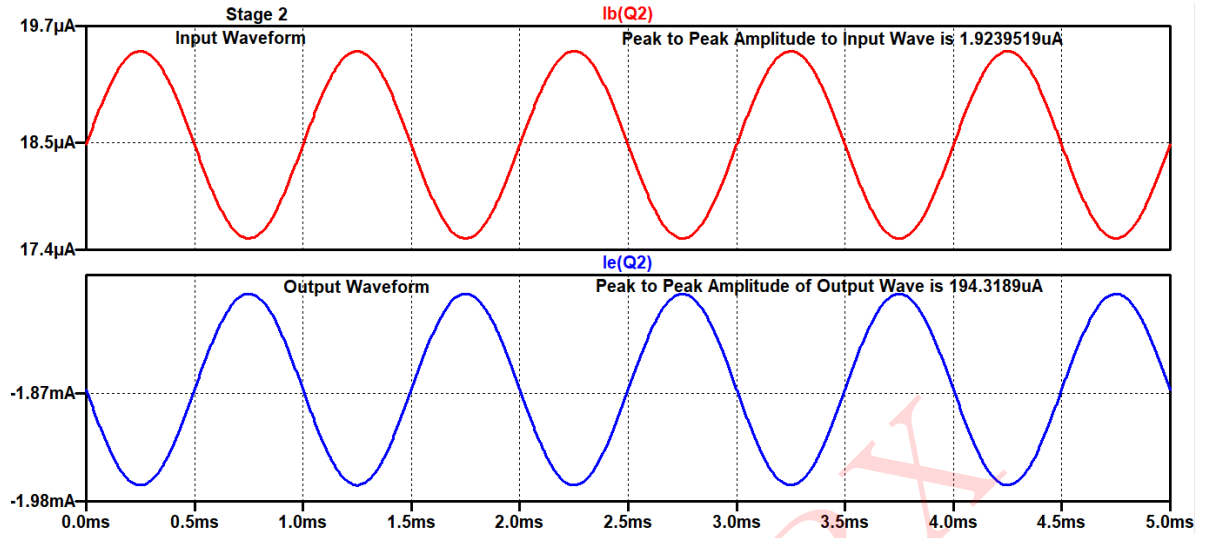


Figure 9: Input & Output waveforms for stage 2 current gain

#### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{B1}$	0.1889 $\mu$ A	0.1829 $\mu$ A
$I_{C1}$	0.01889 mA	0.01829 mA
$I_{E1}$	0.01907 mA	0.01847 mA
$I_{B2}$	0.01907 mA	0.01847 mA
$I_{C2}$	1.9079 mA	1.8479 mA
$I_{E2}$	1.9269 mA	1.8663 mA
$V_{C2}$	10 V	10 V
$V_{E2}$	1.9269 V	1.8663 V
Voltage gain of stage 1: $A_{V1}$	0.9869	0.9786
Voltage gain of stage 2: $A_{V2}$	0.9868	0.9928
Overall voltage gain: $A_{VT}$ in dB	0.9738 dB	0.9716 dB
Current gain of stage 1: $A_{i1}$	101	100.9591
Current gain of stage 2: $A_{i2}$	101	101.0498
Overall Current gain: $A_{iT}$	10201	10201.9131
Input impedance of stage 1	33.224 k $\Omega$	—
Output impedance of stage 2	29.1073 $\Omega$	—
Output Voltage	97.38 mV	97.1654 mV

Table 1: Numerical 1

\*\*\*\*\*