

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Power Amplifier Circuits

Numerical 1

In a class AB push-pull amplifier load $R_L = 12\Omega$. Supply voltage $V_{CC} = 18V$ and $V_{EE} = -18V$, AC input voltage is $16V$ peak, frequency is $1000Hz$. Calculate efficiency of circuit.

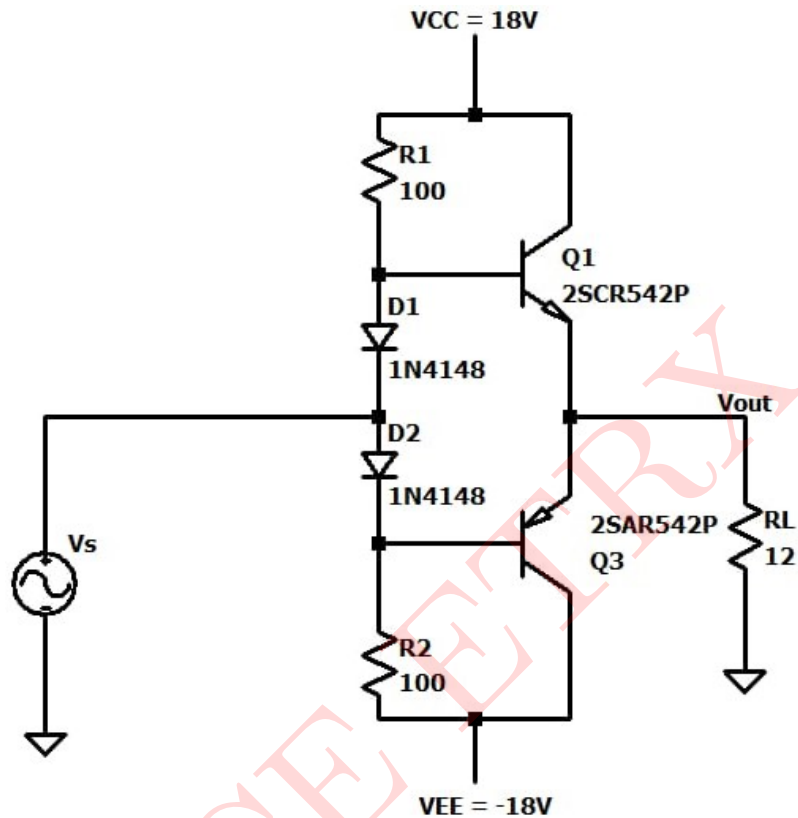


Figure 1: Circuit for Numerical 1

Solution:

$$V_s = V_m \sin(\omega t)$$

$$V_s = V_m \sin(2\pi ft)$$

$$V_s = 16 \sin(2\pi \times 1000t)$$

$$V_m = 16V$$

$$P_{ac} = \frac{V_m^2}{2R_L} = \frac{16^2}{2 \times 12}$$

$$P_{ac} = 10.66W$$

$$I_m = \frac{V_m}{R_L} = \frac{16V}{12\Omega}$$

$$I_m = 1.33A$$

$$P_{dc} = \frac{2V_{CC}I_m}{\pi} = \frac{2 \times 18V \times 1.33A}{\pi}$$

$$P_{dc} = 15.24W$$

Efficiency:

$$\eta = \frac{P_{ac}}{P_{dc}} = \frac{10.66W}{15.24W} \times 100$$

$$\eta = 69.9\%$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

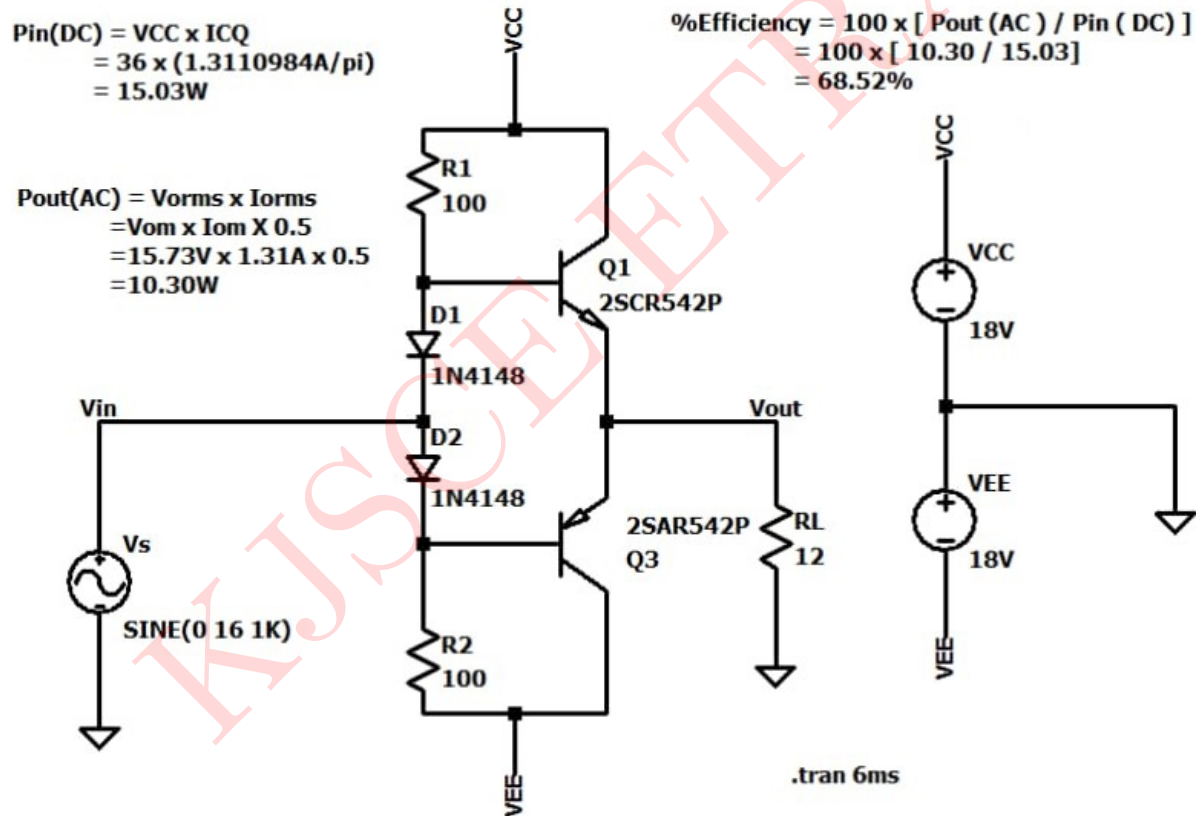


Figure 2: Circuit Schematic: Results

Output Waveforms:

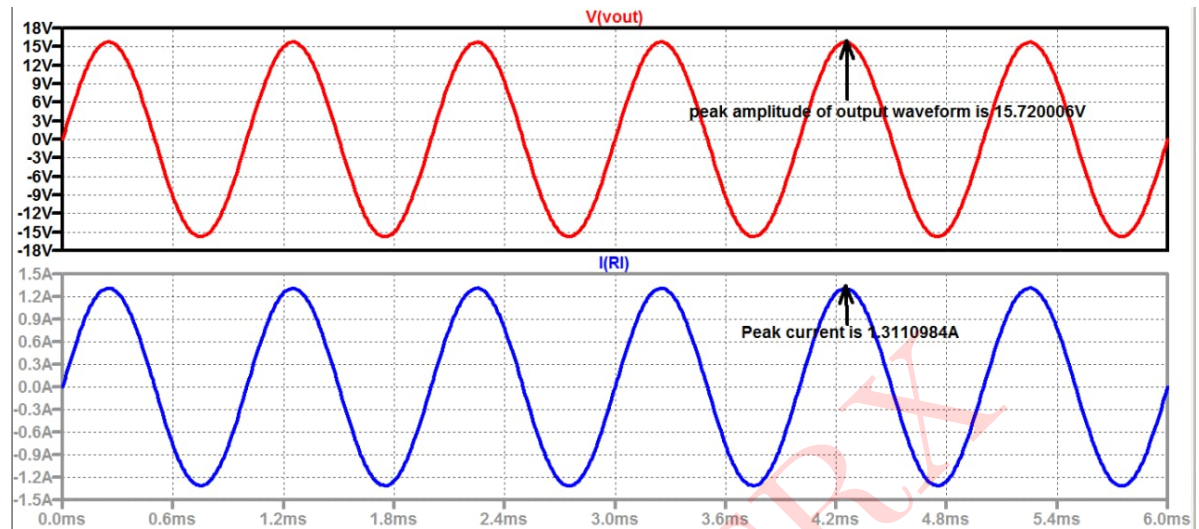


Figure 3: Output load voltage and load current waveforms

Comparison between theoretical and simulated values is given below:

Parameters	Simulated Values	Theoretical Values
Input DC Power	15.03W	15.24W
Output DC Power	10.30W	10.66W
Efficiency	68.52%	69.9%

Table 1: Numerical 1
