

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**DC CIRCUITS**

**Numerical 1:** (a) Consider the wheatstone shown in the figure calculate  $V_a$ ,  $V_b$ ,  $V_{ab}$   
(b) Rework Part (a) if the ground is placed at A instead of O  
(Solve analytically using any technique and verify theoretical results with simulated values)

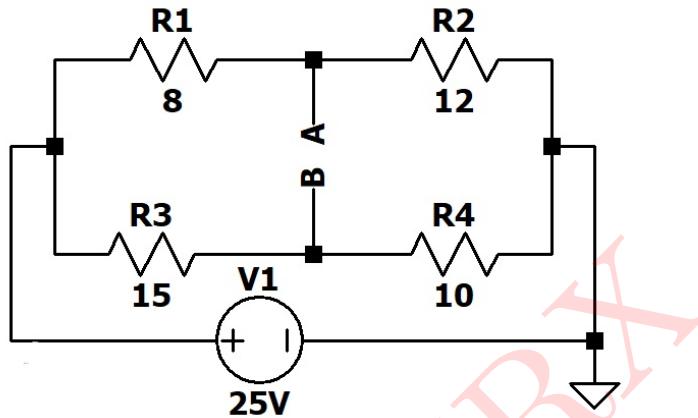


Figure 1: Circuit 1

**Solution:**

**Part a:**

We can observe that the source voltage in a circuit is divided among the resistors  $8\text{ k}\Omega$ ,  $12\text{ k}\Omega$ ,  $15\text{ k}\Omega$  and  $10\text{ k}\Omega$

$\therefore$  voltage at terminals can be find out by voltage divider rule

Using voltage divider rule,

$$V_a = \frac{12}{12 + 8} \times 25 = 15\text{ V}$$

$$V_b = \frac{10}{10 + 15} \times 25 = 10\text{ V}$$

$$V_{ab} = V_a - V_b = 15 - 10 = 5\text{ V}$$

Part b:

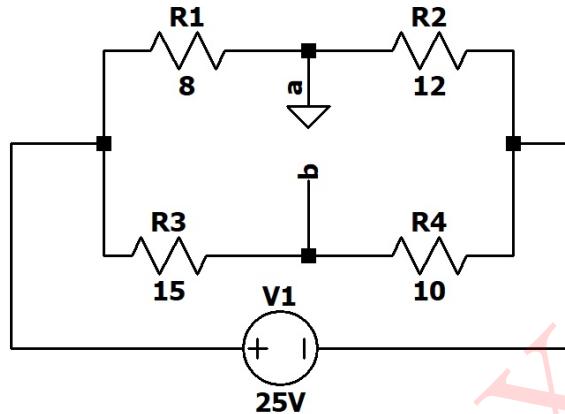


Figure 2: Circuit 1b

Since the terminal A is grounded

$$V_a = 0V$$

Now,  $V_{ab} = V_{cb} + V_{ac}$  ... (from circuit 1b)

Again by voltage divider rule,

$$V_{cb} = \frac{15}{15+10} \times 25 = 15V \text{ and}$$

$$V_{ac} = \frac{-8}{8+12} \times 25$$

$$V_{ac} = -10V$$

Since  $V_{ab} = V_{cb} + V_{ac}$

$$\therefore V_{ab} = 15 - 10 = 5V$$

$$V_b = -V_{ab} = -5V$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

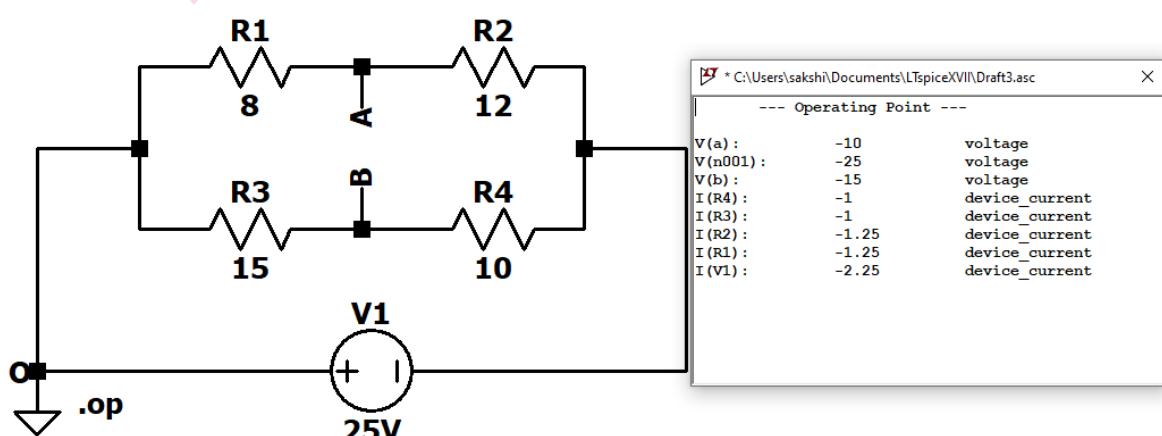


Figure 3: Circuit schematic and simulated results

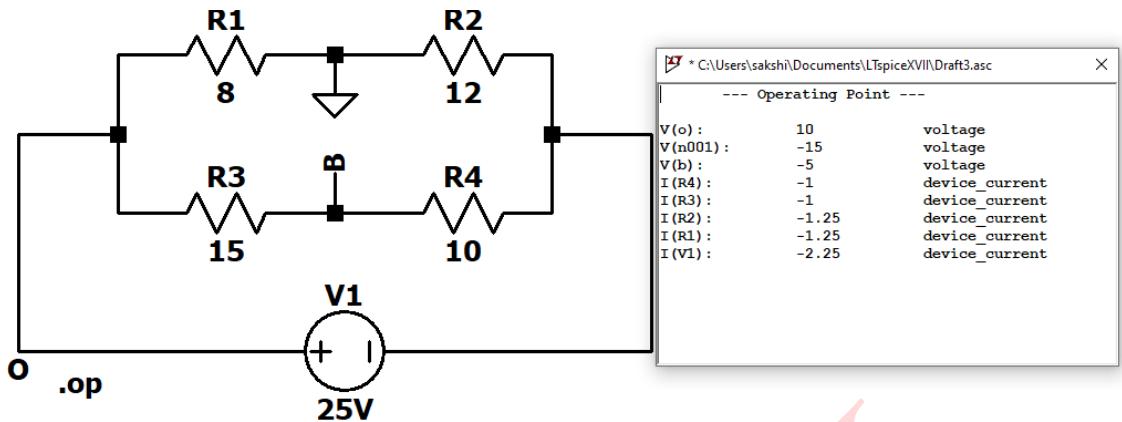


Figure 4: Circuit schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $V_a$      | 15V                | 15V              |
| $V_b$      | 10V                | 10V              |
| $V_{ab}$   | 5V                 | 5V               |

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $V_a$      | 0V                 | 0V               |
| $V_b$      | -5V                | -5V              |
| $V_{ab}$   | 5V                 | 5V               |

**Numerical 2:** Find  $R_{TH}$  in eight way divider shown in figure 5

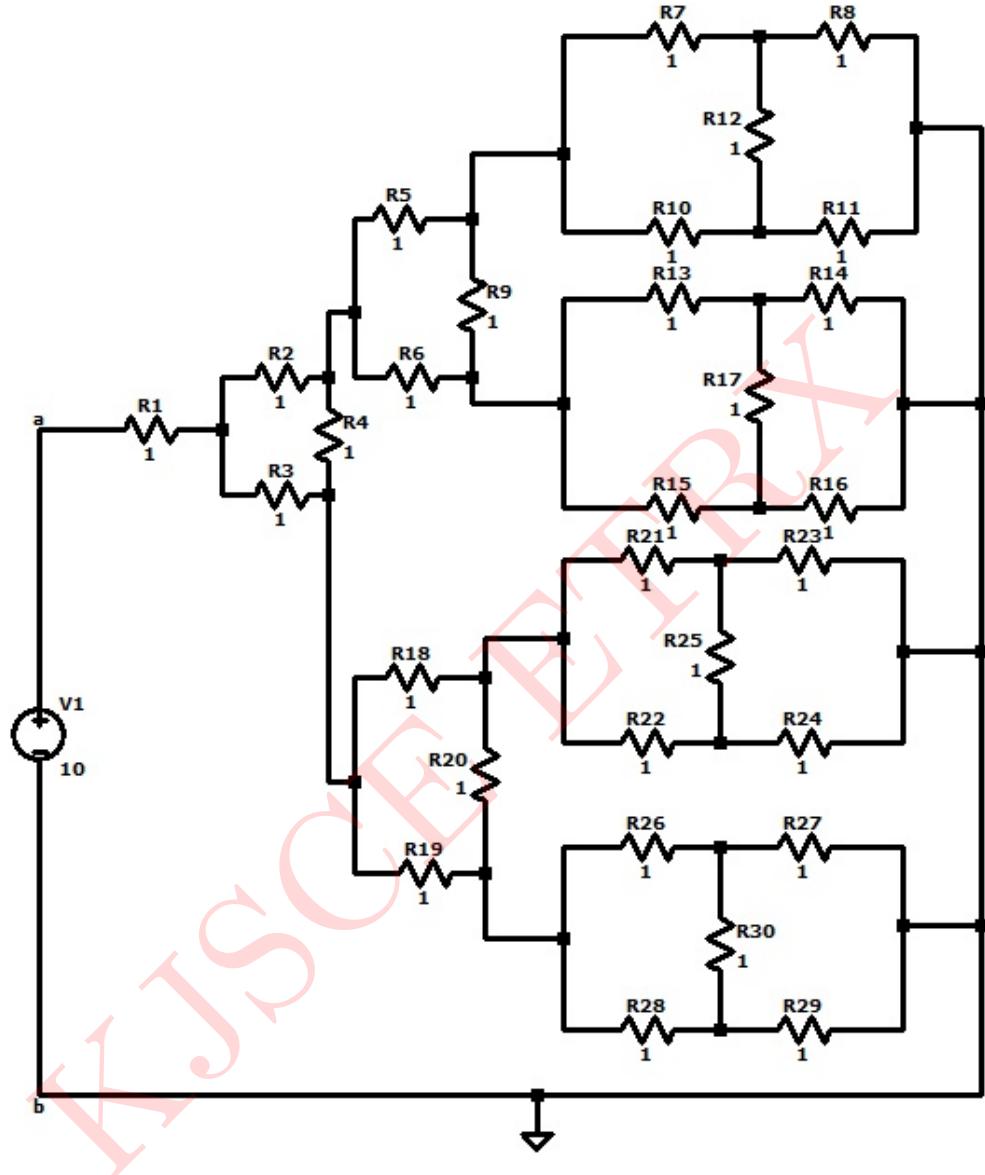


Figure 5: Circuit 2

**Solution:**

Since all the resistances are  $1\Omega$  and wheatstone networks are balanced  
Circuit in figure 5 can be simplified as follows:

The Wheatstone network in circuit of figure 5 is-

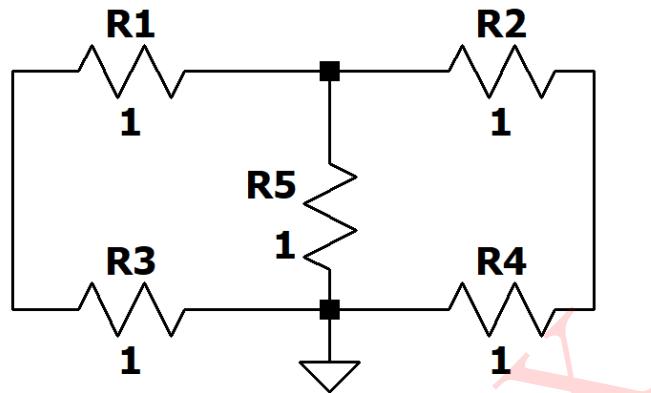


Figure 6: Modified circuit for figure 5

As bridge is balanced we can neglect the middle  $1\Omega$  resistor

$\therefore$  Circuit in figure 6 will reduce to:

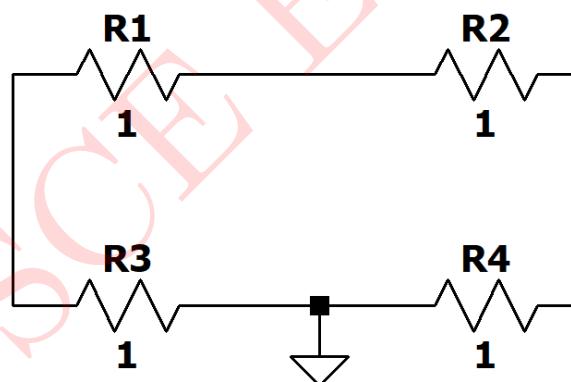


Figure 7: Modified circuit for figure 6

Here two  $1\Omega$  resistances are in series and their resultant is in parallel with each other .

$$V_a = \frac{2 \times 2}{2 + 2}$$

$\therefore$  Circuit in figure 7 will reduce to:

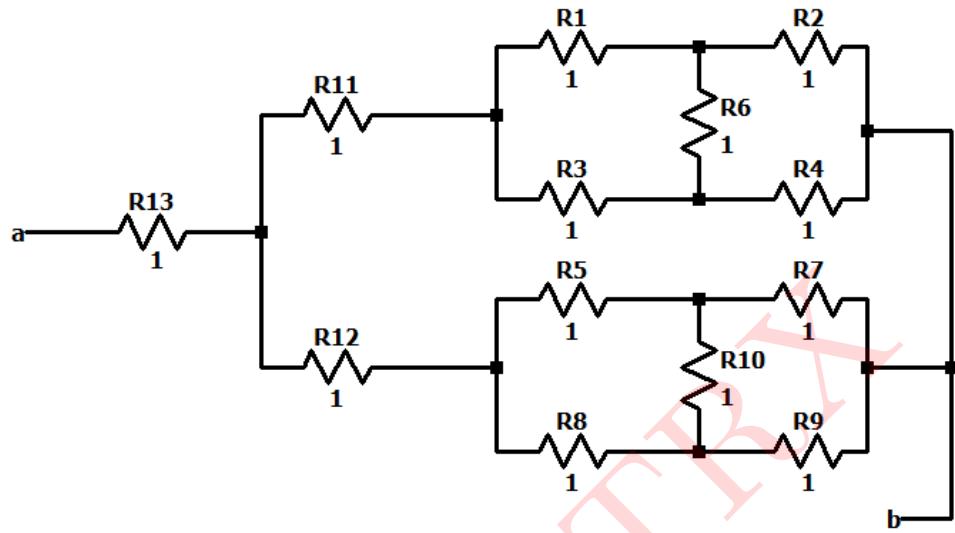


Figure 8: Modified circuit for figure 7

Again by the same method of wheatstone network, circuit in figure 8 will reduce to:

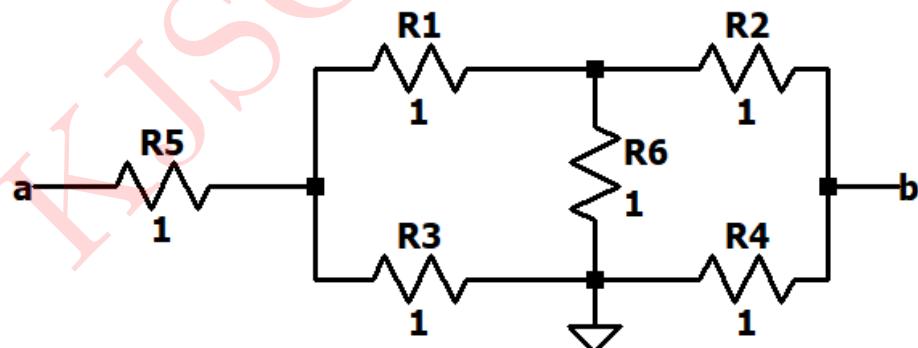


Figure 9: Modified circuit of figure 8

Here if we simply the wheatstone network, we will get two  $1\Omega$  resistors in series

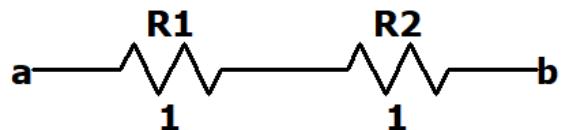


Figure 10: Modified circuit of figure 9

Hence, both resistances are in series

$$R_{eq} = (1 + 1) = 2\Omega$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below

$$\text{Req.} = V_1/I(V_1) = 10/5 = 2\Omega$$

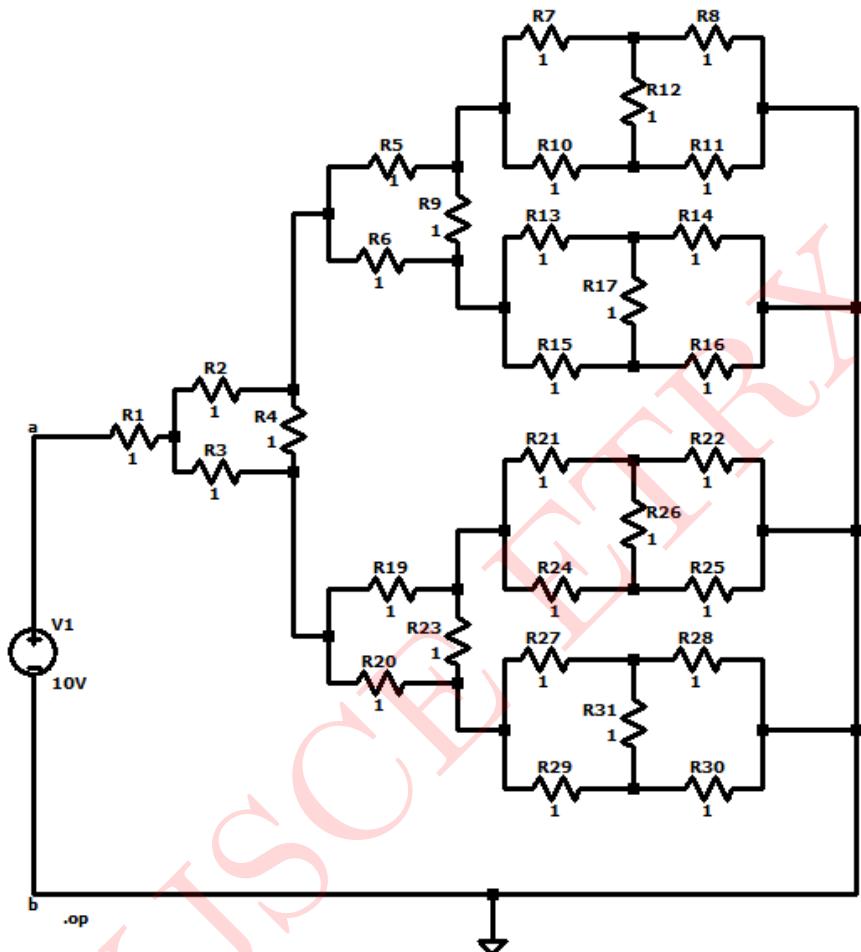


Figure 11: Circuit schematic and simulated results

**Comparison of theoretical and simulated values:**

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $R_{eq}$   | $2\Omega$          | $2\Omega$        |

### Numerical 3:

Use Superposition Theorem to find  $V_O$  in the circuit shown in figure 12

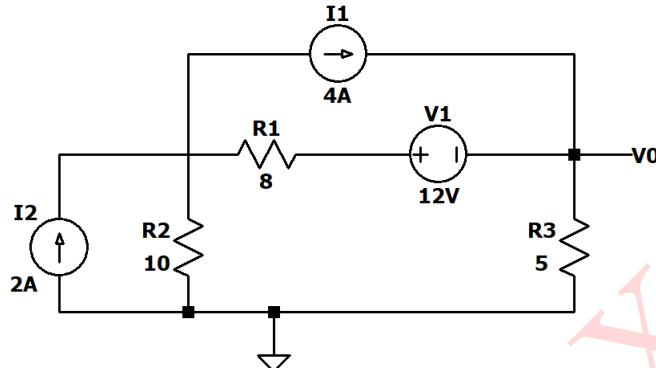


Figure 12: Circuit 3

#### Solution:

$$\text{Let, } V_O = V_1 + V_2 + V_3$$

where  $V_1$ ,  $V_2$  and  $V_3$  are voltages due to independent sources

(i) To find  $V_1$ , consider  $I_2$  and  $V_1$  inactive and  $I_1$  active

$\therefore$  Circuit in figure 12 will be-

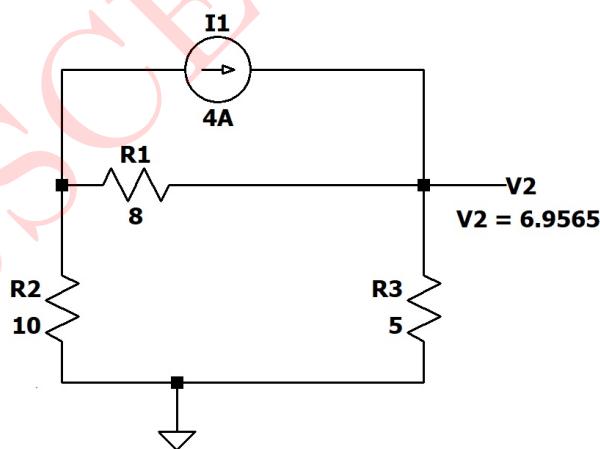


Figure 13: Modified circuit for figure 12(i)

From the circuit,  $I_1 = 4A$

To find  $I_2$ , applying kirchhoff's voltage law for circuit:

$$-10I_2 - 5I_2 - 8(I_2 - I_1) = 0$$

$$8I_1 - 23I_2 = 0 \dots \text{(i)}$$

Since,  $I_1 = 4A$

$$\therefore I_2 = \frac{32}{23} = 1.3913A$$

$$V_1 = I_2 \times 5 = 1.3913 \times 5 = 6.9565V$$

(ii) To find  $V_2$ , consider  $I_2$  and  $V_1$  inactive and  $I_1$  active.

$\therefore$  Circuit in figure 12 will be-

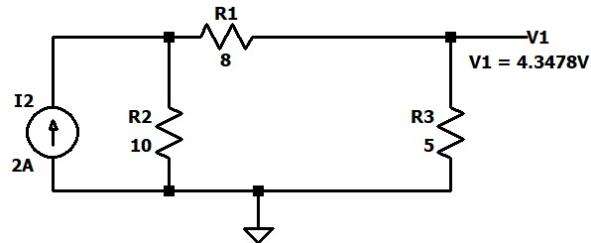


Figure 14: Modified circuit for figure 12(ii)

There are two meshes in the following circuit, consider the current through mesh 1 and 2 is  $I_x$  and  $I_y$  respectively

From the circuit,  $I_x = 2A$

To find  $I_y$ , applying kirchhoff's voltage law for circuit:

$$-10(I_y - I_x) - 8I_y - 5I_x = 0$$

$$10I_x - 23I_y = 0 \dots \text{(ii)}$$

Since,  $I_x = 2A$

$$\therefore I_y = \frac{20}{23} = 0.8695A$$

$$V_2 = I_y \times R_3 = 0.8695 \times 5 = 4.3478V$$

(iii) To find  $V_3$ , consider  $I_1$  and  $I_2$  inactive and  $V_1$  active

$\therefore$  Circuit in figure 12 will be-

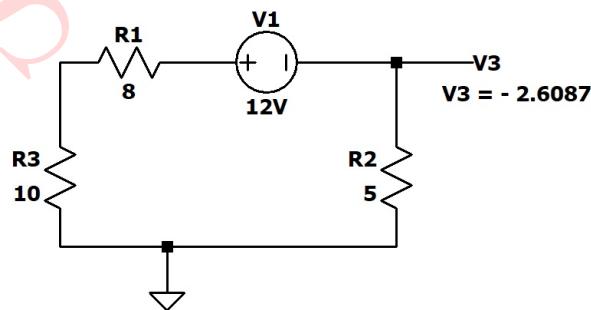


Figure 15: Modified circuit for figure 12(iii)

By voltage divider rule,

$$V_3 = \frac{5}{5 + 10 + 8} \times (-12)$$

$$V_3 = \frac{-60}{23} = -2.6087V$$

$$V_3 = -2.6087V$$

$$\text{since, } V_O = V_1 + V_2 + V_3$$

$$V_O = 4.3478 + 6.9565 - 2.6087$$

$$\therefore V_O = 8.696V$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

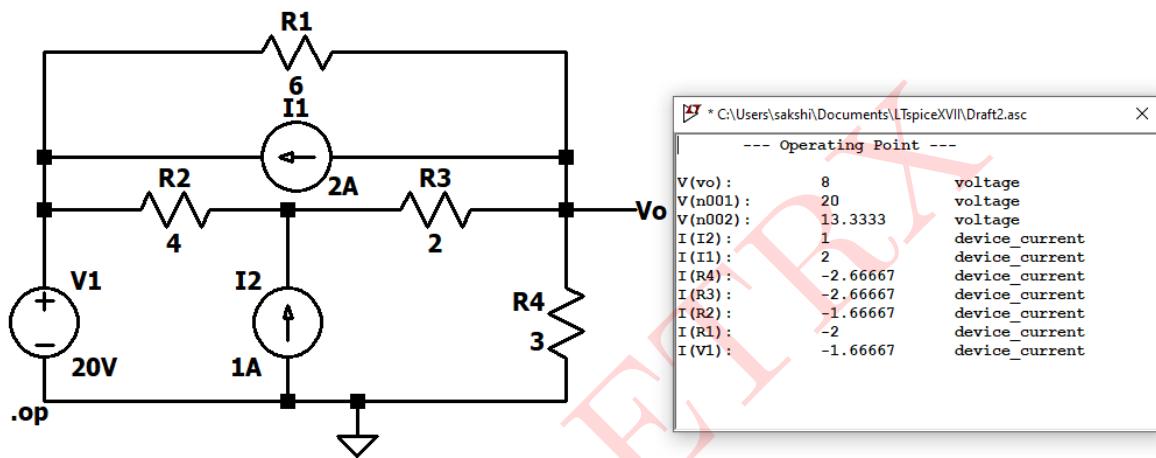


Figure 16: Circuit schematic and simulated results

### Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $V_1$      | $6.9565V$          | $6.9565V$        |
| $V_2$      | $4.3478V$          | $4.3478V$        |
| $V_3$      | $-2.6087V$         | $-2.6087V$       |
| $V_O$      | $8.696V$           | $8.696VV$        |

**Numerical 4:** Use Superposition Theorem to find  $V_O$  in the circuit shown in figure 17

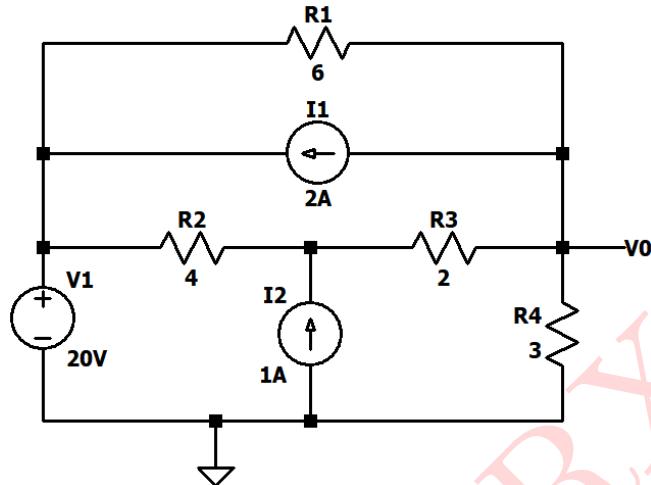


Figure 17: Circuit 4

**Solution:**

$$\text{Let, } V_O = V_1 + V_2 + V_3$$

where  $V_1$ ,  $V_2$  and  $V_3$  are voltages due to independent sources

(i) To find  $V_1$ , consider  $I_2$  and  $V_1$  inactive and  $I_1$  active

$\therefore$  Circuit in figure 17 will be:

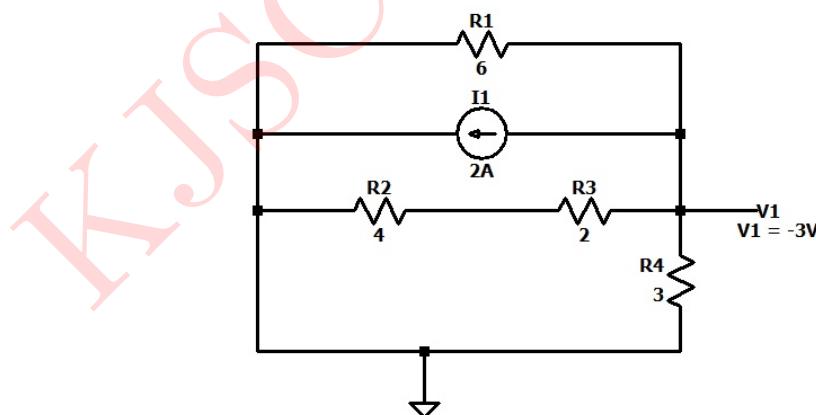


Figure 18: Modified circuit for figure 17(i)

The  $6\Omega$  resistor is in parallel with  $4\Omega$  and  $2\Omega$  resistors which are connected in series

$$R_{eq} = \frac{6 \times 6}{6 + 6} = 3\Omega$$

$\therefore$  By current divider rule,

$$V_1 = 3 \times (-1) = -3V$$

(ii) To find  $V_2$ , consider  $I_1$  and  $V_1$  inactive and  $I_2$  active

$\therefore$  Circuit in figure 17 will be:

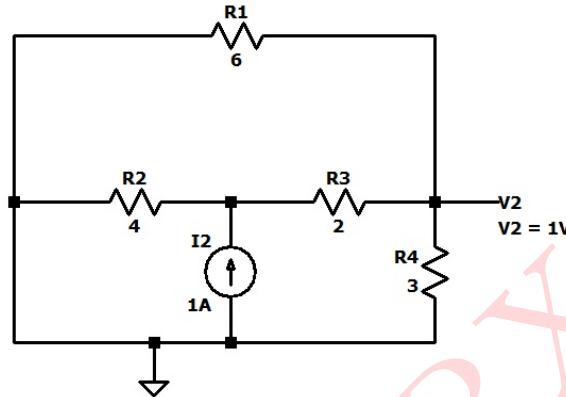


Figure 19: Modified circuit for figure 17(ii)

The  $4\Omega$  and  $2\Omega$  resistors are in series and their resultant is in parallel with  $3\Omega$  resistor

$$R_{eq} = \frac{3 \times 6}{3 + 6} = 2\Omega$$

By current divider rule,

$$V_2 = \frac{2}{4 + 2 + 2} \times 4 = 1V$$

$$V_2 = 1V$$

(iii) To find  $V_3$ , consider  $I_1$  and  $I_2$  inactive and  $V_1$  active

$\therefore$  Circuit in figure 17 will be:

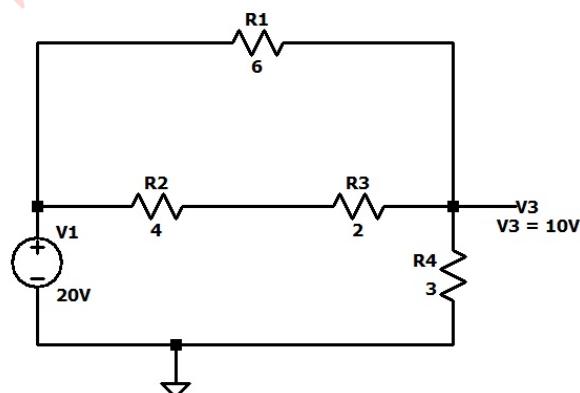


Figure 20: Modified circuit for figure 17(iii)

The  $4\Omega$  and  $2\Omega$  resistors are in series and their resultant is in parallel with  $6\Omega$  resistor

$$R_{eq} = \frac{6 \times 6}{6 + 6} = 3\Omega$$

By current divider rule,

$$V_3 = \frac{20}{2} = 10V$$

$$V_3 = 10V$$

$$\text{since, } V_O = V_1 + V_2 + V_3$$

$$V_O = -3 + 1 + 10 = 8V$$

$$\therefore V_O = 8V$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

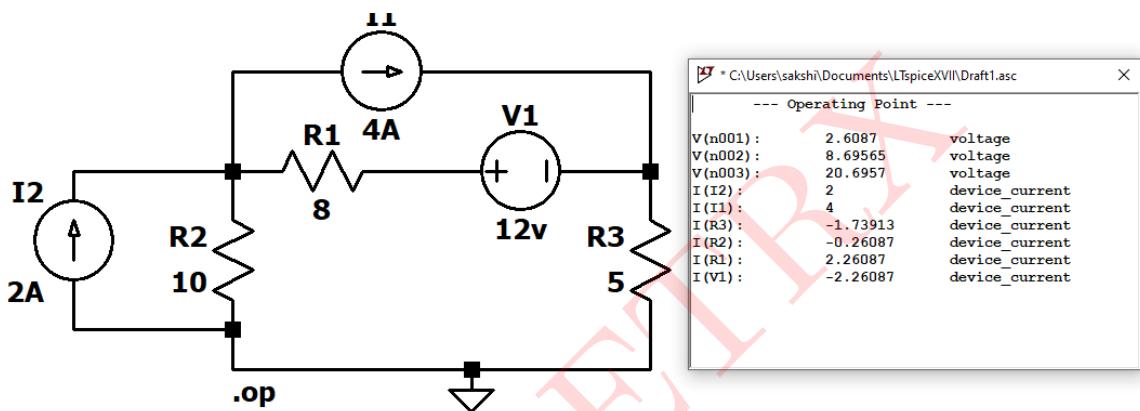


Figure 21: Circuit schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $V_1$      | $-3V$              | $-3V$            |
| $V_2$      | $1V$               | $1V$             |
| $V_3$      | $10V$              | $10V$            |
| $V_O$      | $8V$               | $8V$             |

**Numerical 5:** Use Thevenin's theorem to calculate the potential difference across terminal  $V_a$  and  $V_b$  shown in the figure 22

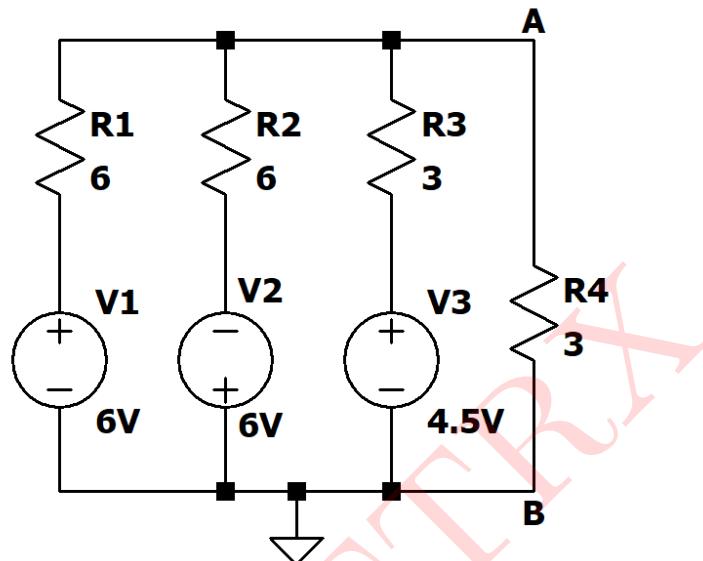


Figure 22: Circuit 5

**Solution:**

(i) To find Thevenin's voltage  $V_{TH}$ , replace load resistance( $3\Omega$ ) with open circuit voltage  $V_{TH}$

The resultant circuit will be:

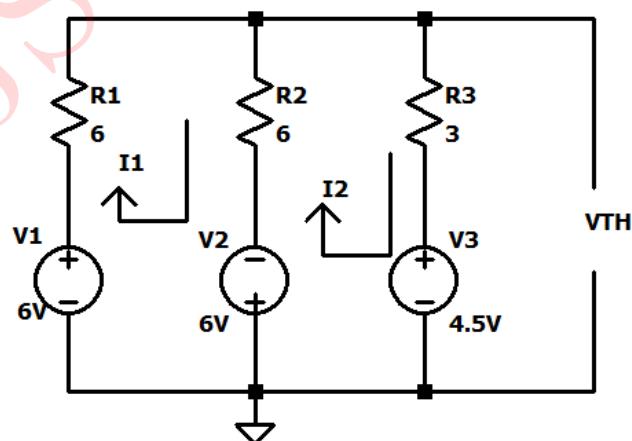


Figure 23: Modified circuit for figure 22(i)

Applying Kirchhoff's voltage law (KVL) for mesh 1:

$$6 - 6I_1 - 6(I_1 - I_2) + 6 = 0$$

$$\text{i.e. } 12I_1 - 6I_2 = 12 \dots\text{(i)}$$

Applying Kirchhoff's voltage law (KVL) for mesh 2:

$$-6 - 6(I_2 - I_1) - 3I_2 - 4.5 = 0$$

$$\text{i.e. } 6I_1 - 9I_2 = 10.5 \dots\text{(ii)}$$

∴ Solving equations (i) and (ii)

$$I_1 = 0.625\text{A}$$

$$I_2 = -0.75\text{A}$$

$$V_{TH} = V_{AB} = 4.5 + 3I_2$$

$$= 4.5 + 3(-0.75) = 4.5 - 2.25 = 2.25V$$

(ii) To find Thevenin's resistance  $R_{TH}$ , replace all active sources by their internal resistances

The resultant circuit will be:

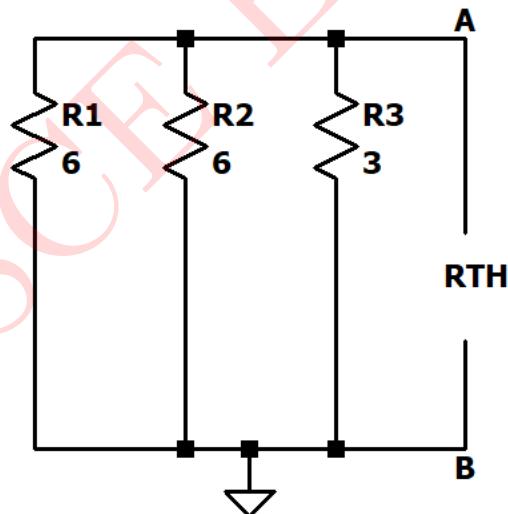


Figure 24: Modified circuit for figure 22(ii)

Here two  $6\Omega$  resistors are in parallel and their resultant is in parallel with  $3\Omega$

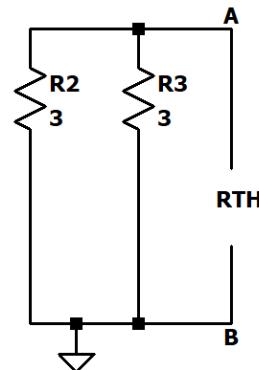


Figure 25: Modified circuit for figure 24

Now again two  $3\Omega$  resistances are in parallel

$$\therefore R_{TH} = 1.5\Omega$$

$\therefore$  Thevenin's equivalent circuit will be:

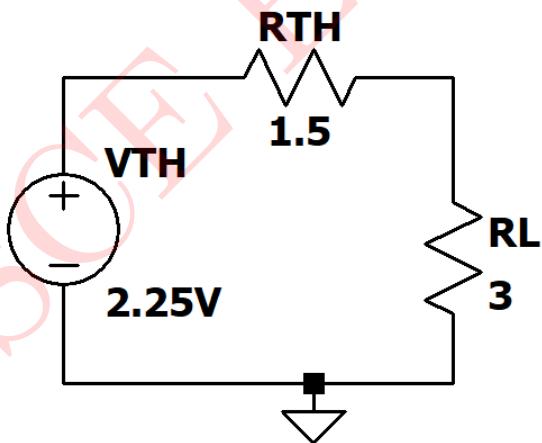


Figure 26: Thevenin's equivalent circuit

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$I_L = \frac{2.25}{3 + 1.5}$$

$$I_L = 0.5A$$

$$V_{AB} = I_L R_L = 0.5 \times 3 = 1.5V$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

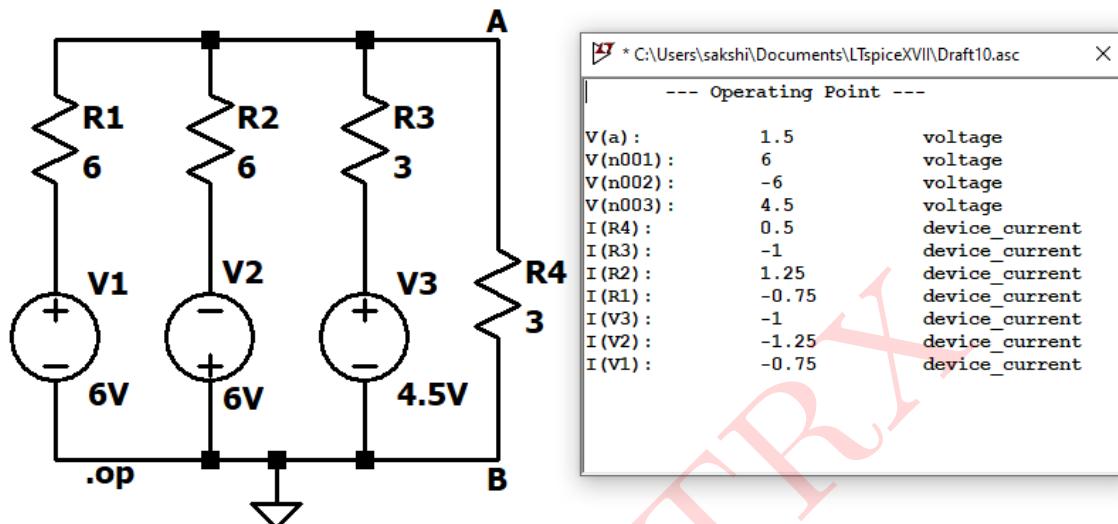


Figure 27: Circuit schematic and simulated results

**Comparison of theoretical and simulated values:**

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $V_{TH}$   | $2.25V$            | $2.25V$          |
| $R_{TH}$   | $1.5\Omega$        | $1.5\Omega$      |
| $V_{AB}$   | $1.5V$             | $1.5V$           |
| $I_L$      | $0.5A$             | $0.5A$           |

**Numerical 6:** Find the current flowing through the load resistance of  $10\Omega$  connected Across terminals  $V_a$  and  $V_b$  using the Thevenin's theorem for circuit shown in figure 28

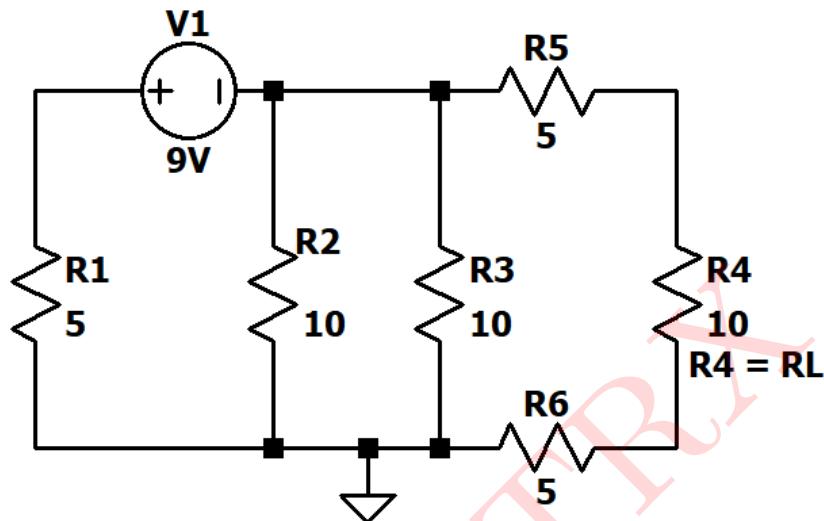


Figure 28: Circuit 6

**Solution:**

- (i) To find Thevenin's voltage  $V_{TH}$ , replace load resistance( $10\Omega$ ) with open circuit voltage  $V_{TH}$

The resultant circuit will be:

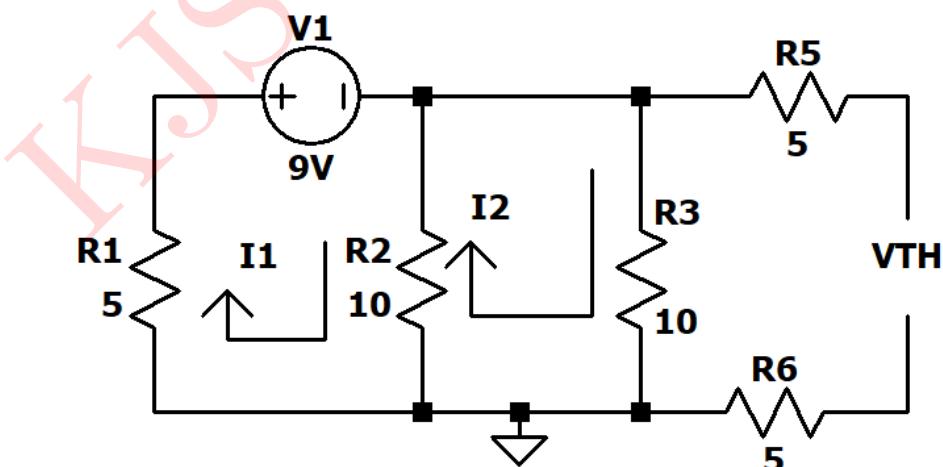


Figure 29: Modified circuit for figure 28(i)

Applying Kirchhoff's voltage law (KVL) for mesh 1:

$$-5I_1 - 10(I_1 - I_2) + 9 = 0$$

$$\text{i.e. } 15I_1 - 10I_2 = 9 \dots\text{(i)}$$

Applying Kirchhoff's voltage law (KVL) for mesh 2:

$$-10(I_2 - I_1) - 10I_2 = 0$$

$$\text{i.e. } 10I_1 - 20I_2 = 0 \dots\text{(ii)}$$

$\therefore$  Solving equations (i) and (ii)

$$I_1 = 0.9\text{A}$$

$$I_2 = 4.5\text{A}$$

$$V_{TH} = V_{AB} = 5I_2 - 10I_2 + 5I_2$$

$$V_{TH} = -10 \times 4.5$$

$$V_{TH} = -45\text{V}$$

(ii) To find Thevenin's resistance  $R_{TH}$ , replace all active sources by their internal resistances

The resultant circuit will be:

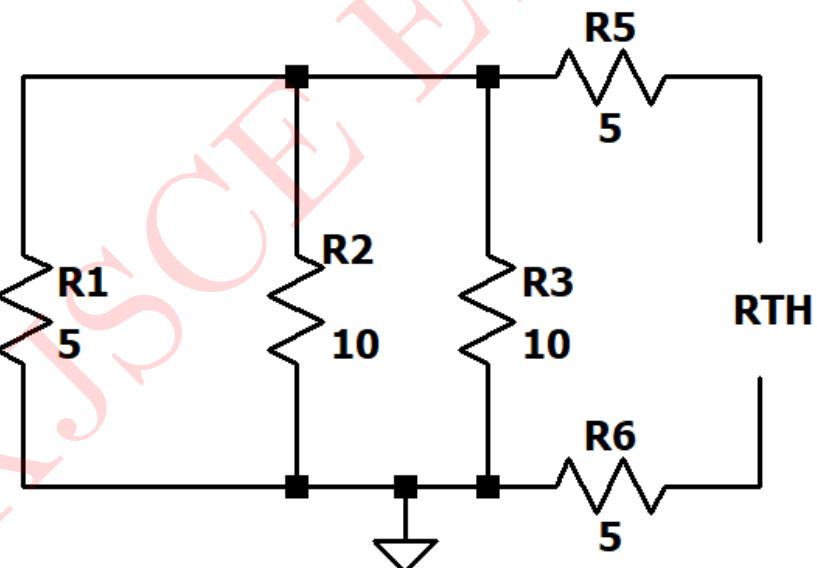


Figure 30: Modified circuit for figure 28(ii)

Here,  $5\Omega$  and  $10\Omega$  resistances are in parallel

Therefore circuit will be:

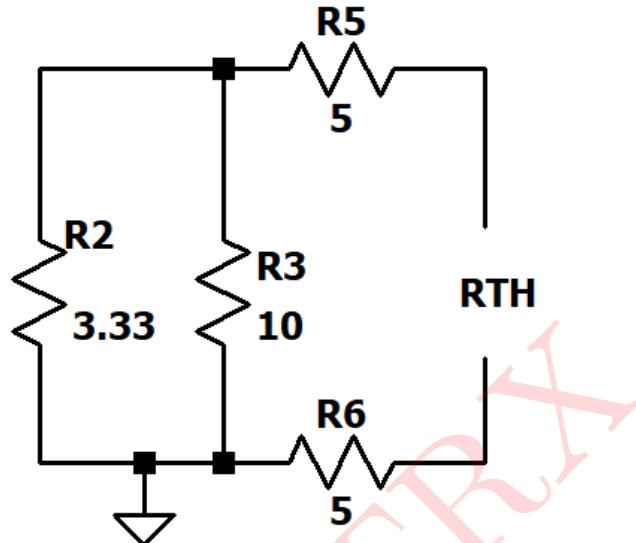


Figure 31: Modified circuit for figure 30

$$\therefore R_{TH} = 12.5\Omega$$

Thevenin's equivalent circuit will be:

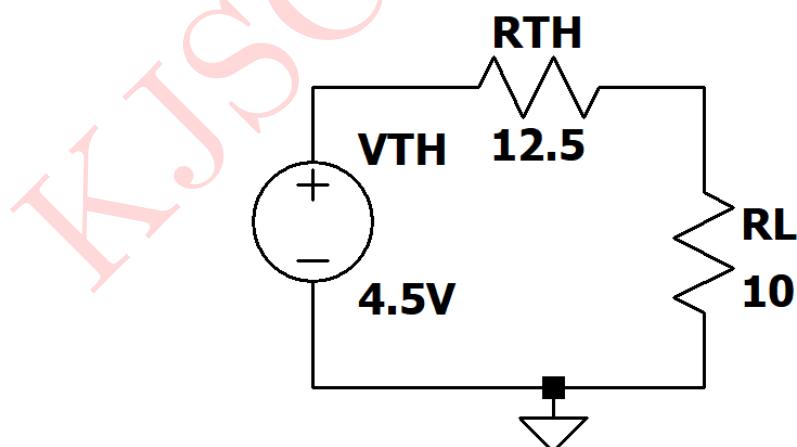


Figure 32: Thevenin's equivalent circuit

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$I_L = \frac{-4.5}{12.5 + 10}$$

$$I_L = -0.2A$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

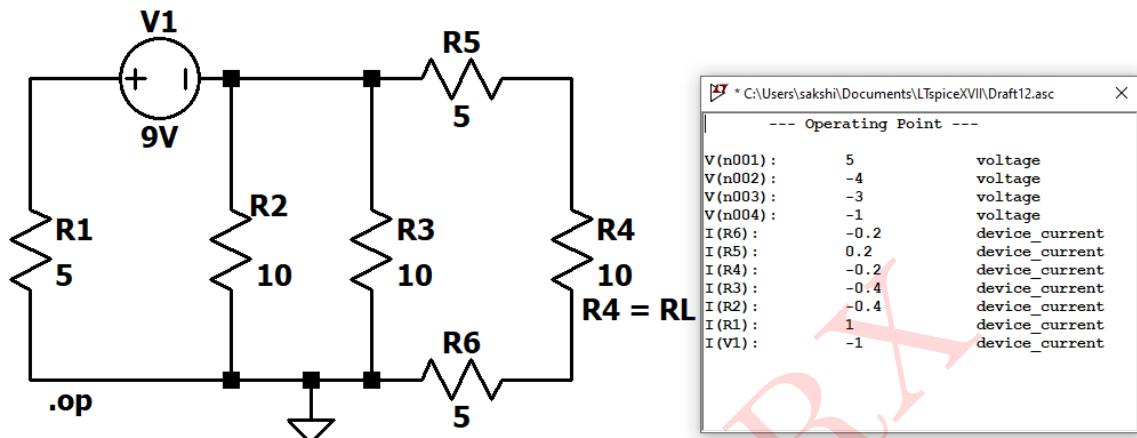


Figure 33: Circuit schematic and simulated results

**Comparison of theoretical and simulated values:**

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $V_{TH}$   | -4.5V              | -4.5V            |
| $R_{TH}$   | 12.5Ω              | 12.5Ω            |
| $I_L$      | -0.2A              | -0.2A            |

**Numerical 7:** Obtain the Thevenin and Norton equivalent circuit for the circuit in figure 34 given that all resistances are in  $\Omega$

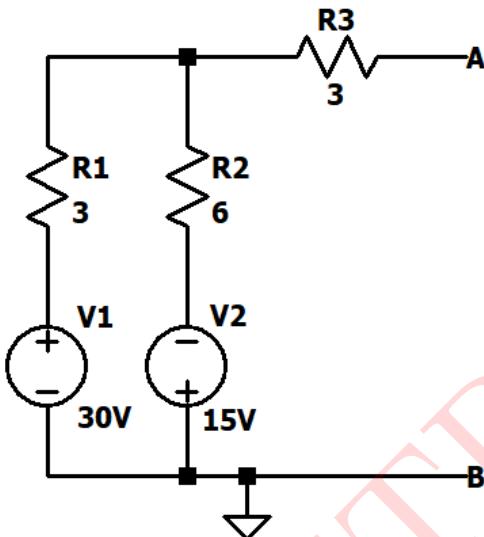


Figure 34: Circuit 7

**Solution:**

i) To find short circuit current  $I_{SC}$

The resultant circuit will be:

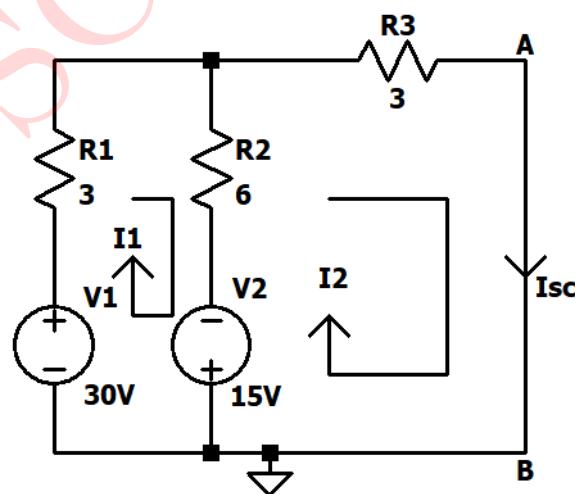


Figure 35: Modified circuit for figure 34(i)

Applying Kirchhoff's voltage law (KVL) for mesh 1:

$$30 - 3I_1 - 6(I_1 - I_2) + 15 = 0$$

$$\text{i.e. } 3I_1 - 2I_2 = 15 \dots \text{(i)}$$

Applying Kirchhoff's voltage law (KVL) for mesh 2:

$$-15 - 6(I_2 - I_1) - 3I_2 = 0$$

$$\text{i.e. } 2I_1 - 3I_2 = 5 \dots \text{(ii)}$$

$\therefore$  Solving equations (i) and (ii)

$$I_1 = 7\text{A} \text{ and}$$

$$I_2 = I_{SC} = 3\text{A}$$

ii) To find Thevenin's resistance  $R_{TH}$ , replace all active sources by their internal resistances

The resultant circuit will be:

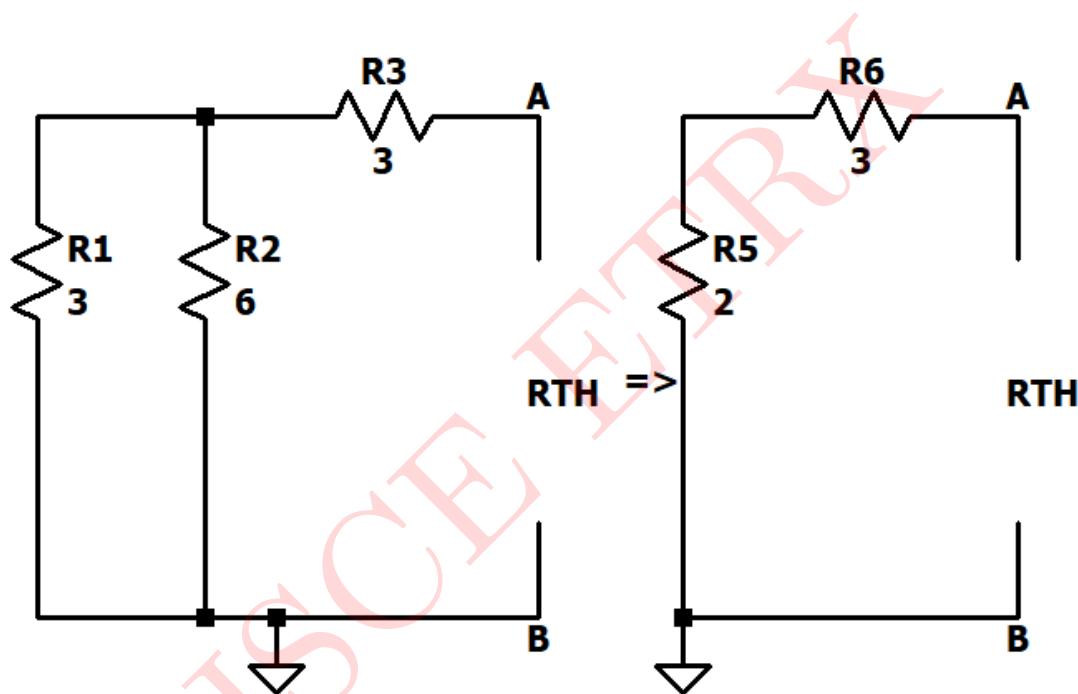


Figure 36: Modified circuit for figure 34(ii)

$$\therefore R_{TH} = 5\Omega$$

iii) To find Thevenin's voltage  $V_{TH}$

The circuit will be:

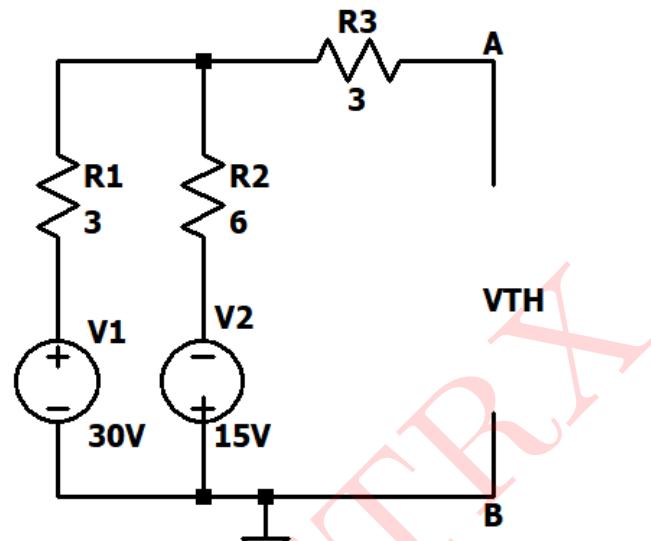


Figure 37: Modified circuit for figure 34(iii)

With the terminal A and B open, two voltage sources are connected in subtractive series

$$\therefore V_{TH} = V_{AB} = (30 - 15)V = 15V$$

Norton's equivalent circuit will be:

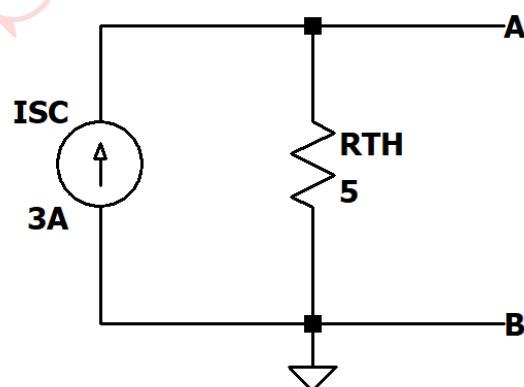


Figure 38: Norton's equivalent circuit

Thevenin's equivalent circuit will be:

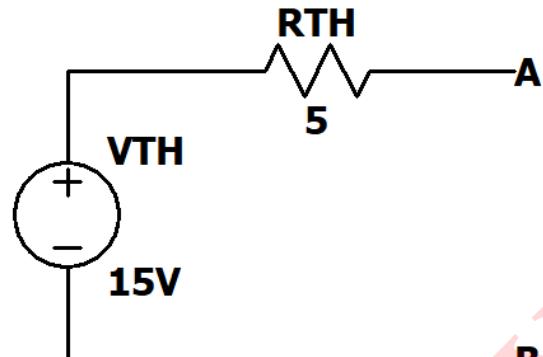


Figure 39: Thevenin's equivalent circuit

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

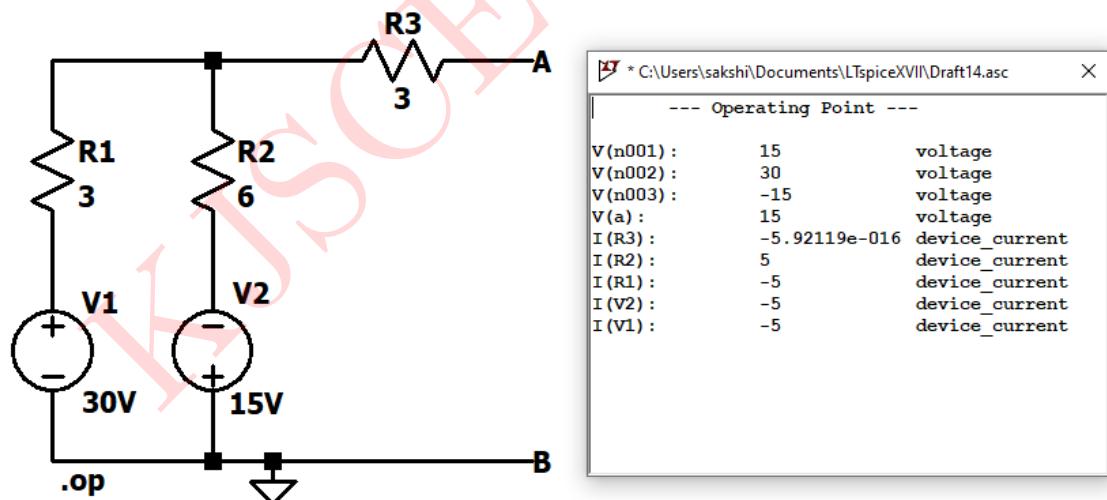


Figure 40: Circuit schematic and simulated results

**Comparison of theoretical and simulated values:**

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $V_{TH}$   | $15V$              | $15V$            |
| $R_{TH}$   | $5\Omega$          | $5\Omega$        |
| $I_{SC}$   | $3A$               | $3A$             |

**Numerical 8:** Solve the circuit shown in figure 41 determine unknown current by method of Thevenin's and Norton's equivalent circuit

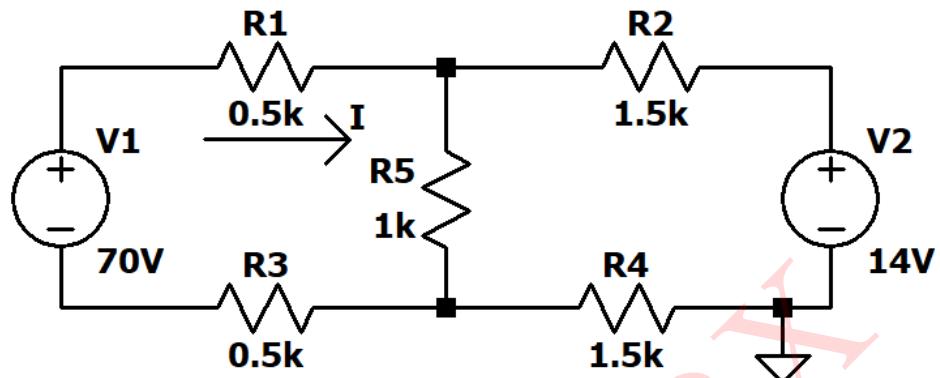


Figure 41: Circuit 8

**Solution:**

Load resistance  $R_L = 0.5\text{K}\Omega$

i) To find Thevenin's voltage  $V_{TH}$

The resultant circuit will be:

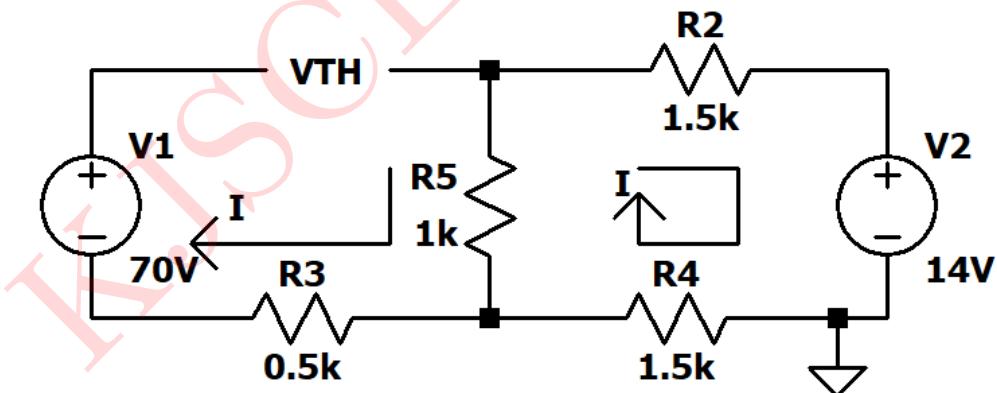


Figure 42: Modified circuit for figure 41(i)

Applying Kirchhoff's voltage law (KVL),

$$-1.5I - 1I - 1.5I = 14$$

$$\therefore I = 3.5\text{mA}$$

$$\text{For } V_{AB} = V_A - 70 + 1000 \times 3.5 = V_B$$

$$V_B = V_{TH} = 66.5V$$

ii) To find Thevenin's resistance  $R_{TH}$

The resultant circuit will be:

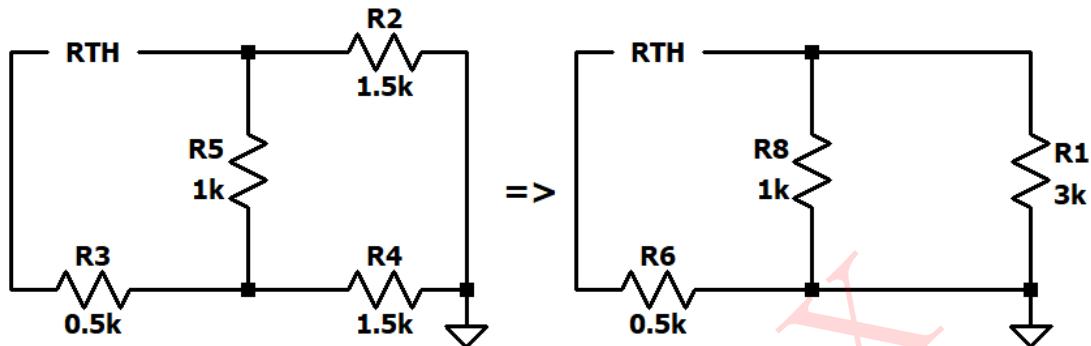


Figure 43: Modified circuit for figure 41(ii)

$$R_{TH} = 1.25\text{K}\Omega$$

Thevenin's equivalent circuit will be:

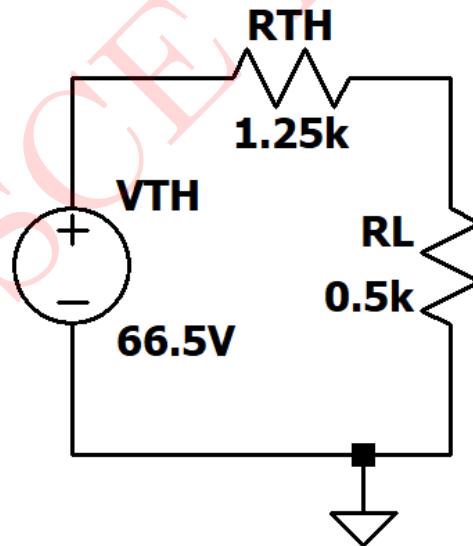


Figure 44: Thevenin's equivalent circuit

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$I_L = \frac{66.5}{1.25 + 0.5}$$

$$I_L = -38\text{mA}$$

iii) To find short circuit current  $I_{SC}$

The circuit will be:

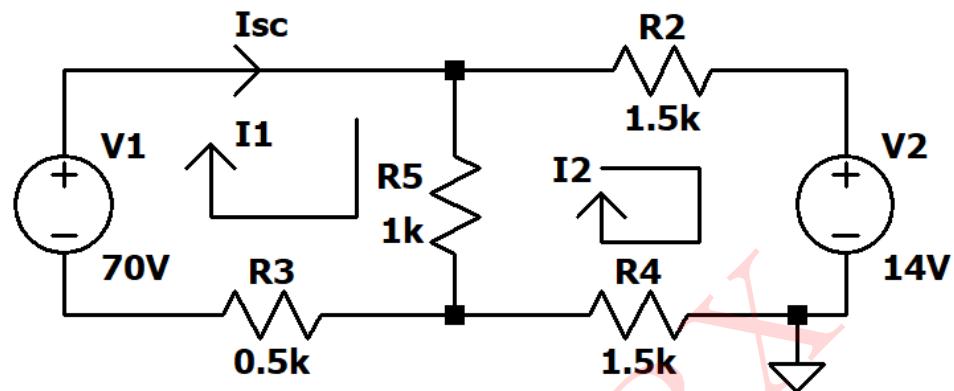


Figure 45: Modified circuit for figure 41(iii)

Applying Kirchhoff's voltage law (KVL) for mesh 1:

$$70 - 0.5I_1 - 1(I_1 - I_2) = 0$$

$$\text{i.e. } I_1 - I_2 = 70 \dots \text{(i)}$$

Applying Kirchhoff's voltage law (KVL) for mesh 2:

$$-1.5I_2 - 1.5I_2 - (I_2 - I_1) - 14 = 0$$

$$\text{i.e. } I_1 - 4I_2 = 14 \dots \text{(ii)}$$

$\therefore$  Solving equations (i) and (ii)

$$I_1 = I_{SC} = 53.2A$$

$$\text{Also, } R_{TH} = 1.25\Omega$$

Nortons's equivalent circuit will be:

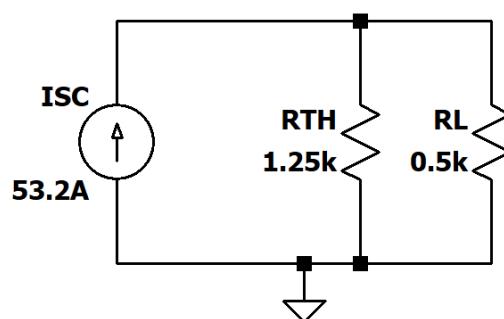


Figure 46: Norton's equivalent circuit

$$I_L = I = \frac{V_{TH}R_N}{R_{TH} + R_L} \dots (R_{TH} = R_N)$$

$$I_L = \frac{66.5}{1.25 + 0.5}$$

$$I_L = I = 38mA$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

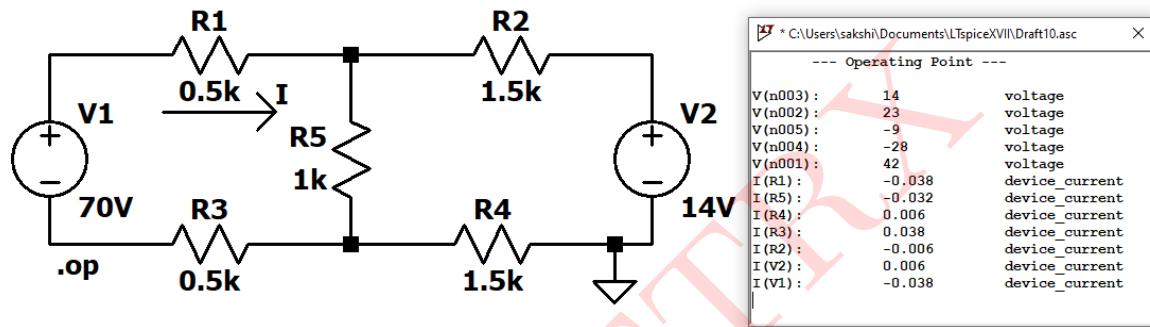


Figure 47: Circuit schematic and simulated results

### Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $V_{TH}$   | 66.5V              | 66.5V            |
| $R_{TH}$   | 1.25KΩ             | 1.25KΩ           |
| $I_{SC}$   | 53.2mA             | 53.2mA           |
| $I$        | 38mA               | 38mA             |

**Numerical 9:** Solve the circuit shown in figure 48 determine unknown voltage or current By method of Norton's theorem

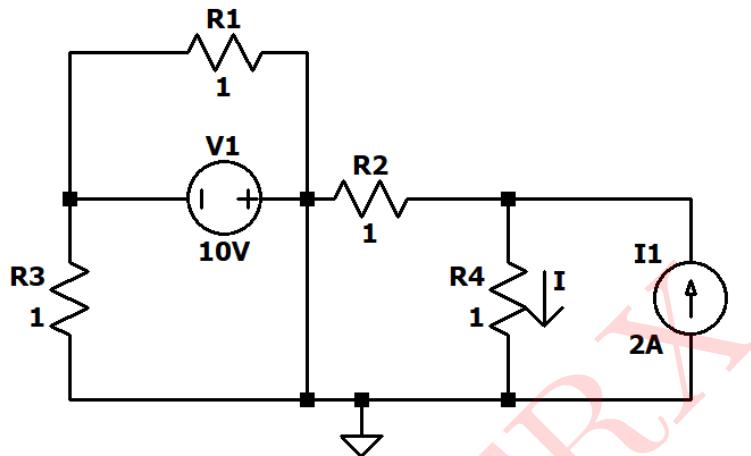


Figure 48: Circuit 9

**Solution:**

Load resistance  $R_L = 1\Omega$

i) To find short circuit current  $I_{SC}$

The circuit will be:

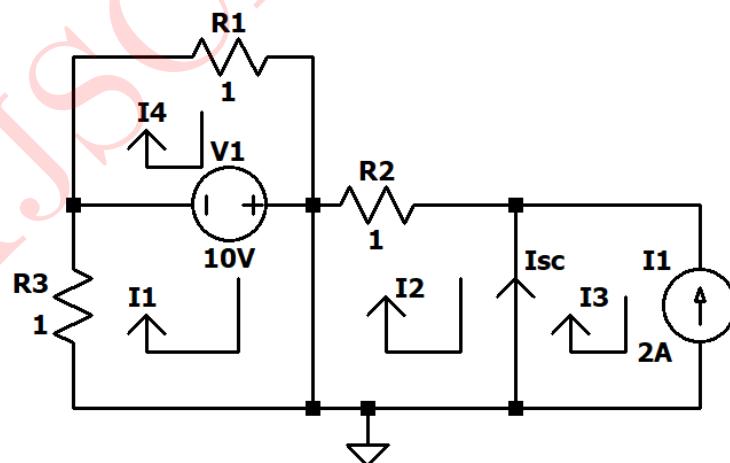


Figure 49: Modified circuit for figure 48(i)

By observations, current through short circuit branch,  $I_{SC} = 2A$

ii) To find Thevenin's resistance  $R_{TH}$

The resultant circuit will be:

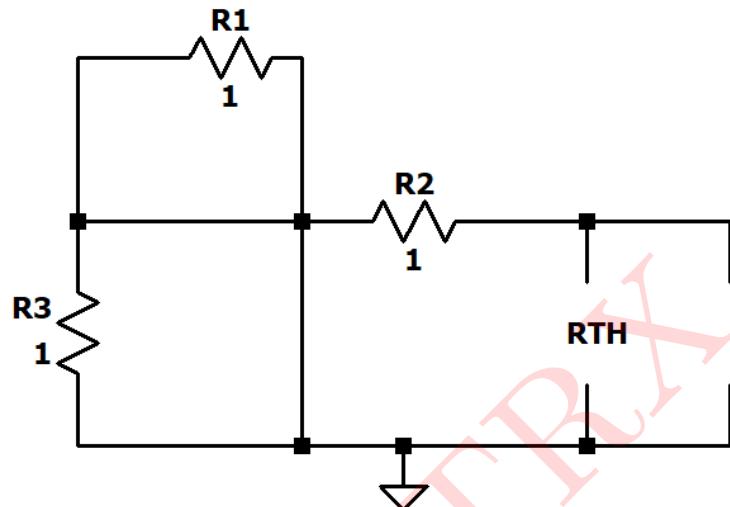


Figure 50: Modified circuit for figure 48(ii)

By calculation,  $R_{TH} = 1\Omega$

Norton's equivalent circuit will be:

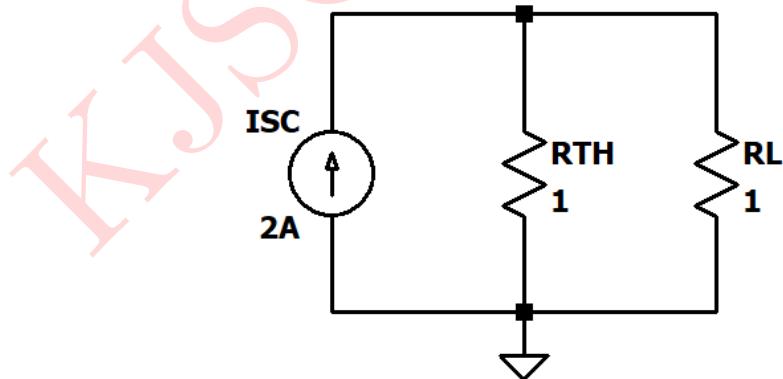


Figure 51: Norton's equivalent circuit

$$I_L = \frac{V_{TH} \times R_N}{R_N + R_L}$$

$$I_L = \frac{200}{1+1}$$

$$I_L = I = 1A$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

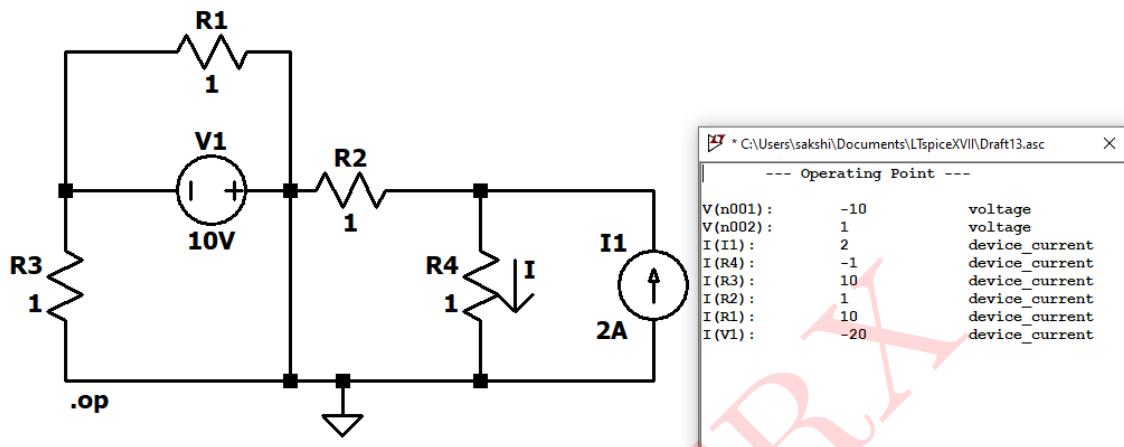


Figure 52: Circuit schematic and simulated results

## Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $R_{TH}$   | $1.25\Omega$       | $1.25\Omega$     |
| $I_{SC}$   | $2A$               | $2A$             |
| $I$        | $1A$               | $1A$             |

**Numerical 10:** In given figure 53 what value of  $R$  will allow maximum power transfer to the load? Also calculate the maximum total load power.

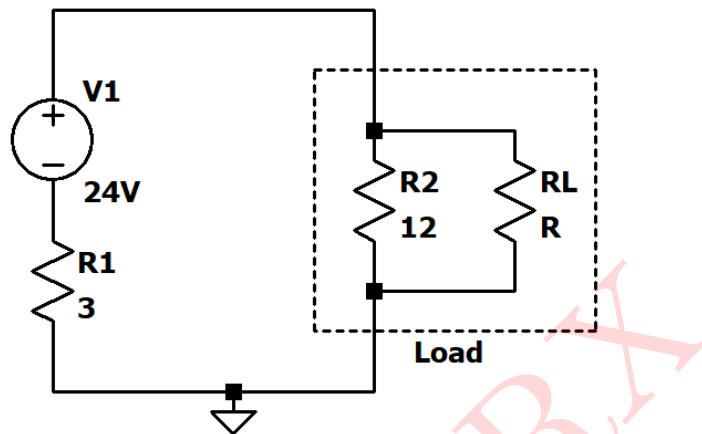


Figure 53: Circuit 10

**Solution:** Both resistances  $R$  and  $12\Omega$  are in parallel

$\therefore$  Their resultant will be load resistance  $R_L$

To find  $R_{TH}$ , remove all active sources by their internal resistances

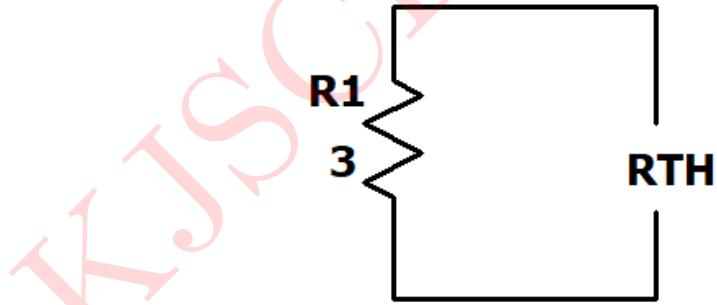


Figure 54: Modified circuit for figure 53

$$\therefore R_{TH} = 3\Omega$$

By maximum power transfer theorem, to allow maximum power transferred through the load  $R_{TH} = R_L$

Since  $R_{TH} = 3\Omega$

$$3\Omega = \frac{12R}{12 + R}$$

$$12R = 36 + 3R$$

$$R = 4 \Omega$$

Hence value of  $R$  should be  $4\Omega$  to allow maximum power to be transferred

$$\therefore \text{Load resistance } R_L = \frac{48}{16} = 3\Omega$$

For maximum power to be transferred  $R_L = R_{TH} = 3\Omega$

$$\therefore P_{MAX.} = \frac{V^2}{4R_L}$$

$$P_{MAX.} = \frac{24^2}{4 \times 3}$$

$$P_{MAX.} = \frac{576}{12} = 48W$$

The maximum power through  $R_L = 3\Omega$  is  $48W$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

$$P_{max} = 576/4(3) = 48W$$

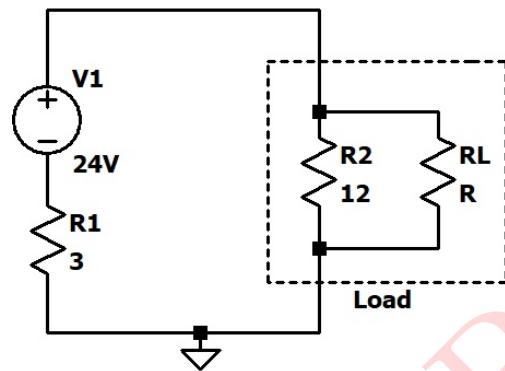


Figure 55: Circuit schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $R_{TH}$   | $3\Omega$          | $3\Omega$        |
| $P_{MAX}$  | $48W$              | $48W$            |

**Numerical 11:** Find the value of adjustable resistance  $R$  which result in maximum power transfer across the terminal  $AB$  in the circuit of figure 56

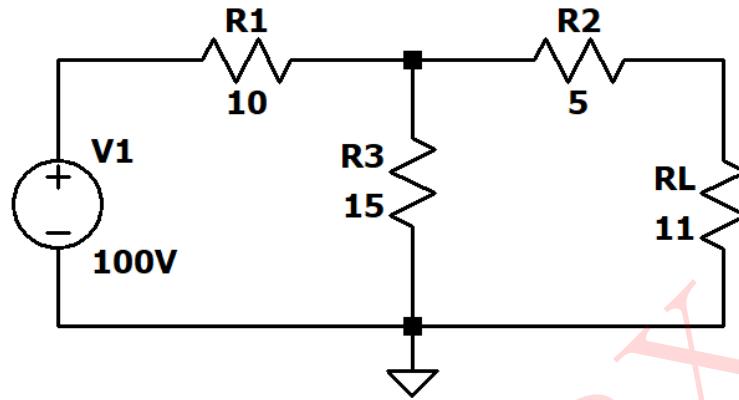


Figure 56: Circuit 11

**Solution:**

By Thenenin's Theorem

To find Thevenin's voltage  $V_{TH}$ :

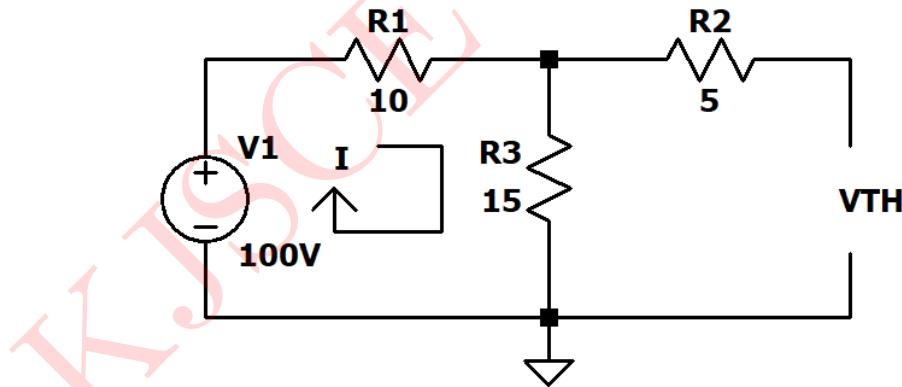


Figure 57: Modified circuit for figure 56(i)

Apply Kirchhoff's Voltage Law(KVL):

$$100 - 10I - 15I = 0$$

$$I = 4A$$

$$V_{AB} = V_{TH} = 15I$$

$$V_{TH} = 15 \times 4 = 60V$$

$$\therefore V_{TH} = 60V$$

To find Thevenin's resistance  $R_{TH}$ :

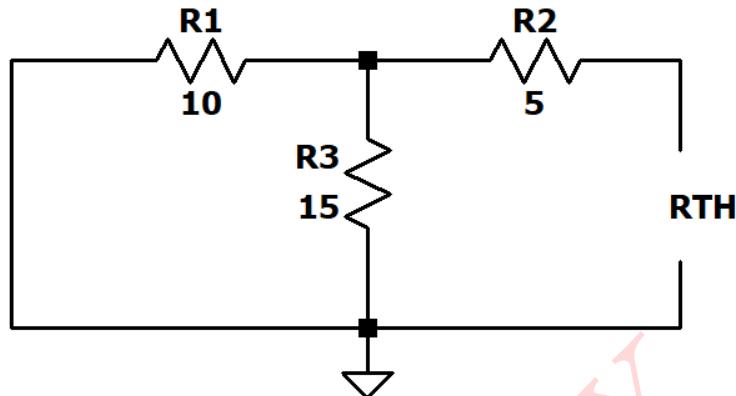


Figure 58: Modified circuit for figure 56(ii)

Here  $10\Omega$  and  $15\Omega$  resistances are in parallel and their resultant is in series with  $5\Omega$

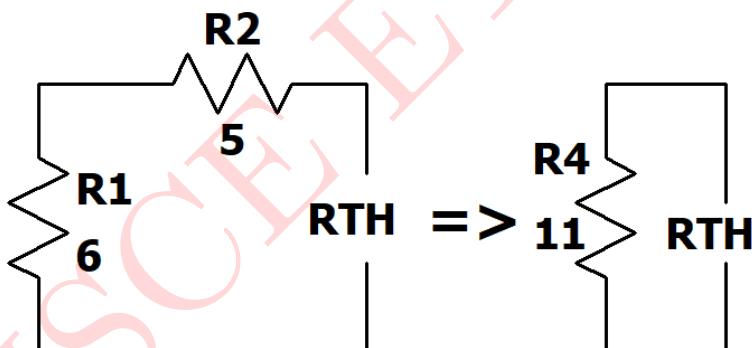


Figure 59: Modified circuit for figure 58

$$R_{TH} = \frac{10 \times 15}{10 + 15} + 5$$

$$R_{TH} = 11\Omega$$

By maximum power transfer theorem, for maximum power to be transferred across terminal  $AB$ ,  $R_{TH} = R_L$

$$R_{TH} = R_L = 11\Omega$$

$$\therefore P_{MAX.} = \frac{V^2}{4R_L}$$

$$P_{MAX.} = \frac{60^2}{4 \times 11}$$

$$P_{MAX.} = \frac{3600}{44} = 81.818W$$

The maximum power through  $R_L$  is  $81.818W$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below

$$P_{max} = 3600/44 = 81.818W$$

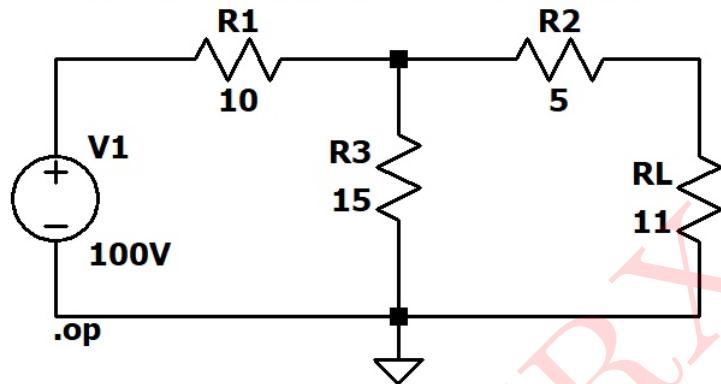


Figure 60: Circuit schematic and simulated results

### Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $R_{th}$   | $11\Omega$         | $11\Omega$       |
| $V_{TH}$   | $60V$              | $60V$            |
| $P_{MAX}$  | $81.818W$          | $81.818W$        |