

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Darlington Amplifier

Numerical 1:

For the circuit shown in figure 1, the parameters for each transistor are $\beta = 100$, $V_A = \infty$

a) Determine Q-point value for Q1 and Q2

b) Determine overall small-signal voltage-gain $A_V = \frac{V_{out}}{V_S}$

c) Determine input and output resistances R_{iS} & R_o

Given:- $V_S = 20mV$

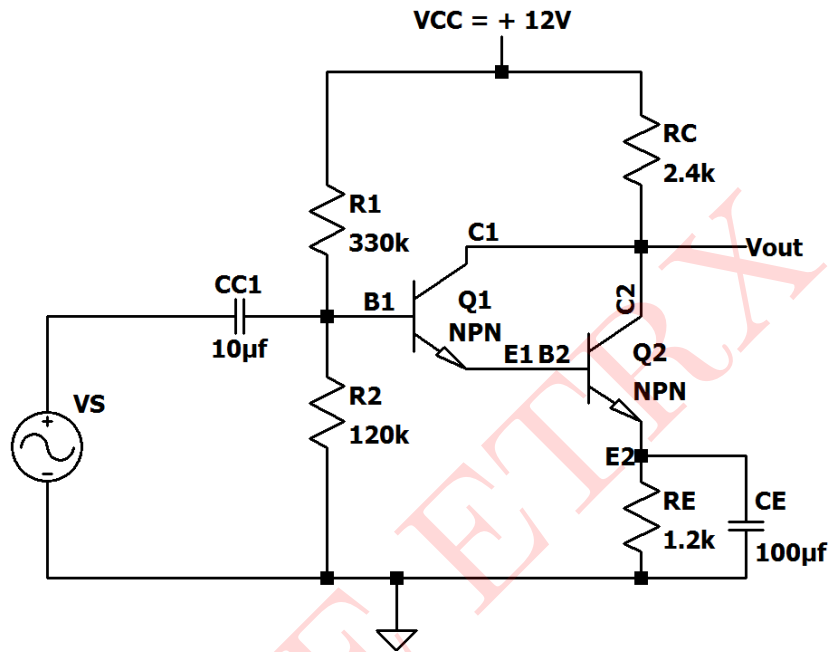


Figure 1: Circuit 1

Solution:

Above circuit 1 is a CE Darlington pair

DC Analysis:-

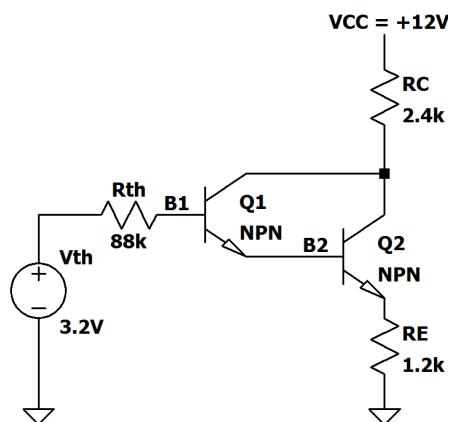


Figure 2: DC Equivalent circuit

$$R_{th} = R_1 \parallel R_2 = 330k \parallel 120k = 88k\Omega$$

$$V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{120k}{450k} \times 12 = 3.2V$$

$$V_{BE} = 2 \times V_{BE} = 1.4V \quad [\text{Since, } V_{BE_1} = V_{BE_2}]$$

Applying KVL to the base emitter loop:-

$$V_{th} - I_{B_1}R_{th} - V_{BE_1} - V_{BE_2} - I_{E_2}R_E = 0$$

$$I_{E_1} = I_{B_2} = (1 + \beta_1)I_{B_1}$$

$$I_{E_2} = (1 + \beta_2)I_{B_2} = (1 + \beta_2)(1 + \beta_1)I_{B_1} \approx \beta_1\beta_2I_{B_1}$$

$$I_{E_2} = \beta_D I_{B_1} \quad [\beta_D = \beta_1 \times \beta_2]$$

$$\beta_D = 100 \times 100 = 10^4$$

$$V_{th} - V_{BE} = I_B(R_{th} + \beta_D R_E)$$

$$I_{B_1} = \frac{V_{th} - V_{BE}}{R_{th} + \beta_D R_E} = \frac{3.2 - 1.4}{88k + 10^4 \times 1.2k} = 0.148\mu A$$

$$\mathbf{I_{B_1} = 0.148\mu A}$$

$$I_{B_2} = (1 + \beta_1)I_{B_1} = I_{E_1}$$

$$I_{B_2} = 101 \times 0.148\mu A = 14.95\mu A$$

$$\mathbf{I_{B_2} = 14.95\mu A}$$

$$\mathbf{I_{E_1} = 14.95\mu A}$$

$$I_{C_1} = \beta_1 I_{B_1} = 14.8\mu A$$

$$\mathbf{I_{C_1} = 14.8\mu A}$$

$$I_{C_2} = \beta_1 I_{B_2} = 1.49mA$$

$$\mathbf{I_{C_2} = 1.49mA}$$

$$I_{E_2} = \beta_D I_{B_1} = 10^4 \times 0.148\mu A = 1.51mA$$

$$\mathbf{I_{E_2} = 1.51mA}$$

$$V_{E_2} = I_{E_2}R_E = 1.51mA \times 1.2k = 1.812V$$

$$\mathbf{V_{E_2} = 1.812V}$$

$$V_{C_2} = V_{CC} - I_{C_2}R_C = 12 - (1.49 \times 2.4) = 8.24V$$

$$\mathbf{V_{C_2} = 8.24V}$$

Small-Signal parameters:-

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{14.9\mu A}{26mV} = 0.569 \text{ mA/V}$$

$$g_{m1} = \mathbf{0.569 \text{ mA/V}}$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{1.49mA}{26mV} = 57.3 \text{ mA/V}$$

$$g_{m2} = \mathbf{57.3 \text{ mA/V}}$$

$$r_{\pi1} = \frac{V_T}{I_{B1}} = \frac{26mV}{0.148\mu A} = 175.67k\Omega$$

$$r_{\pi1} = \mathbf{175.67k\Omega}$$

$$r_{\pi2} = \frac{V_T}{I_{B2}} = \frac{26mV}{14.95\mu A} = 1.74k\Omega$$

$$r_{\pi2} = \mathbf{1.74k\Omega}$$

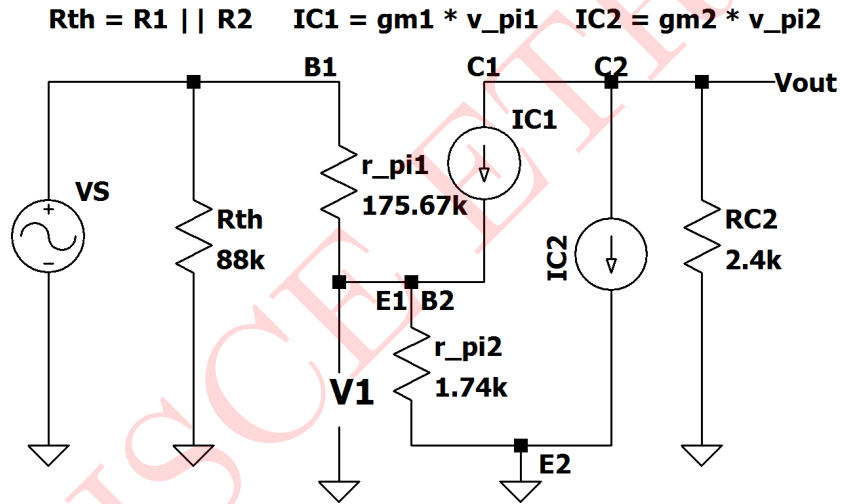


Figure 3: Mid-frequency AC Equivalent Circuit

Input Impedance

$$Z_{i1} = r_{\pi1} + (1 + \beta_1)r_{\pi2} = 175.67k\Omega + (101 \times 1.74k) = 351.41k\Omega$$

$$Z_i = R_{th} \parallel Z_{i1} = 88k \parallel 351.41k = 70.376k\Omega$$

$$\mathbf{Z_i = 70.376k\Omega}$$

Output Impedance:-

$$Z_{o1} = \frac{R_{th} + r_{\pi1}}{1 + \beta_1} = \frac{88k + 175.67k}{101} = 2.91k\Omega$$

$$Z_{o2} = \frac{Z_{o1} + r_{\pi2}}{1 + \beta_2} = \frac{2.61k + 1.74k}{101} = 43.07\Omega$$

$$Z_o = Z_{o2} \parallel R_C = 43.07 \parallel 2400 = 42.31\Omega$$

$$\mathbf{Z_o = 42.31\Omega}$$

Current gain:-

Stage 1:-

$$A_{i_1} = \frac{I_{C_1}}{I_{B_1}} = \frac{\beta_1 I_{B_1}}{I_{B_1}} = \beta_1 = 100$$

Stage 2:-

$$A_{i_2} = \frac{I_{C_2}}{I_{B_2}} = \frac{\beta_2 I_{B_2}}{I_{B_2}} = \beta_2 = 100$$

$$A_{i_T} = A_{i_1} \times A_{i_2} = 100 \times 100 = 10^4$$

Overall Voltage gain:-

$$A_{i_S} = \frac{I_o}{I_i} = \frac{I_o}{I_{B_2}} \times \frac{I_{B_2}}{I_{B_1}} \times \frac{I_{B_1}}{I_i}$$

$$\therefore A_{i_S} = A_{i_2} \times A_{i_1} \times \frac{I_{B_1}}{I_i} \quad [I_{B_2} = I_{E_1}, I_{E_1} = I_{C_1}]$$

$$\therefore A_{i_S} = A_{i_2} \times A_{i_1} \times \frac{R_B}{R_B + Z_{i_1}} \quad A_{i_S} = 100 \times 100 \times \frac{88k}{88k + 551.41k} = 2002.685$$

$$\mathbf{A_{i_S} = 2002.685}$$

$$A_{V_1} = \frac{V_1}{V_S} = \frac{I_{E_1}}{I_{B_1}} \times \frac{r_{\pi_2}}{Z_{i_1}}$$

$$A_{V_1} = \frac{I_{C_1}}{I_{B_1}} \times \frac{r_{\pi_2}}{Z_{i_1}} = A_{i_1} \times \frac{r_{\pi_2}}{Z_{i_1}} = 100 \times \frac{1.74k}{351.41k} = 0.495$$

$$\mathbf{A_{V_1} = 0.495}$$

$$A_{V_2} = \frac{V_o}{V_1} = \frac{I_o}{I_{B_2}} \times \frac{R_C}{r_{\pi_2}}$$

$$A_{V_2} = \frac{I_{C_2}}{I_{B_2}} \times \frac{R_C}{r_{\pi_2}} = A_{i_2} \times \frac{R_C}{r_{\pi_2}} = 100 \times \frac{2.4k}{1.74k} = 137.93$$

$$\mathbf{A_{V_2} = 137.93}$$

$$A_{V_t} = A_{V_1} \times A_{V_2} = 0.495 \times 137.93 = 68.275$$

$$\mathbf{A_{V_t} = 68.275}$$

$$\mathbf{A_{V_t} \text{ in dB} = 20 \log_{10}(68.275) = 36.68 \text{ dB}}$$

$$\text{Also, } A_{V_t} = \frac{V_{out}}{V_S}$$

$$V_{out} = A_{V_t} \times V_S = 68.275 \times 20 \text{ mV} = 2.731 \text{ V}$$

$$\mathbf{V_{out} = 2.731 \text{ V}}$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

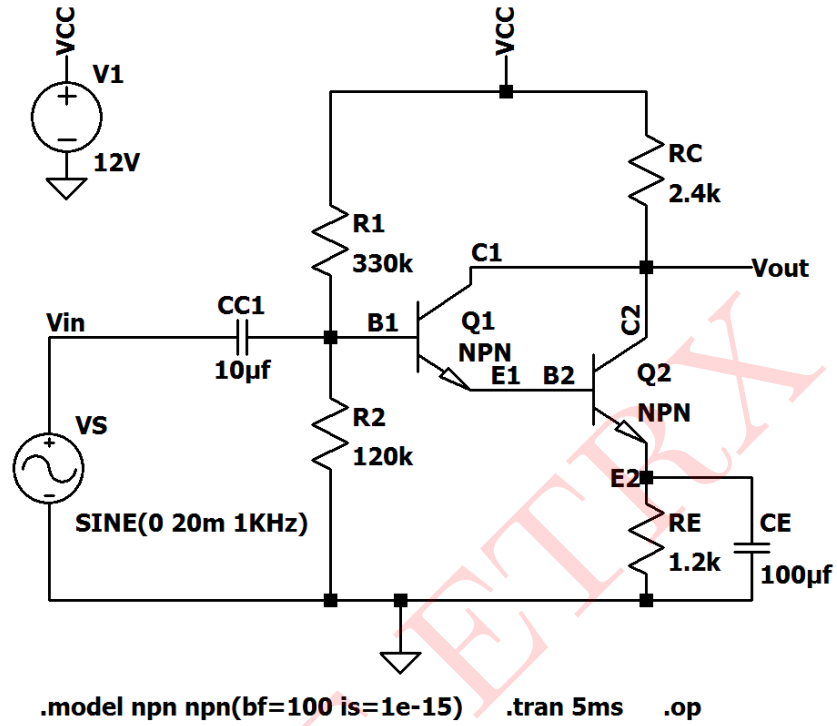


Figure 4: Circuit Schematic 1

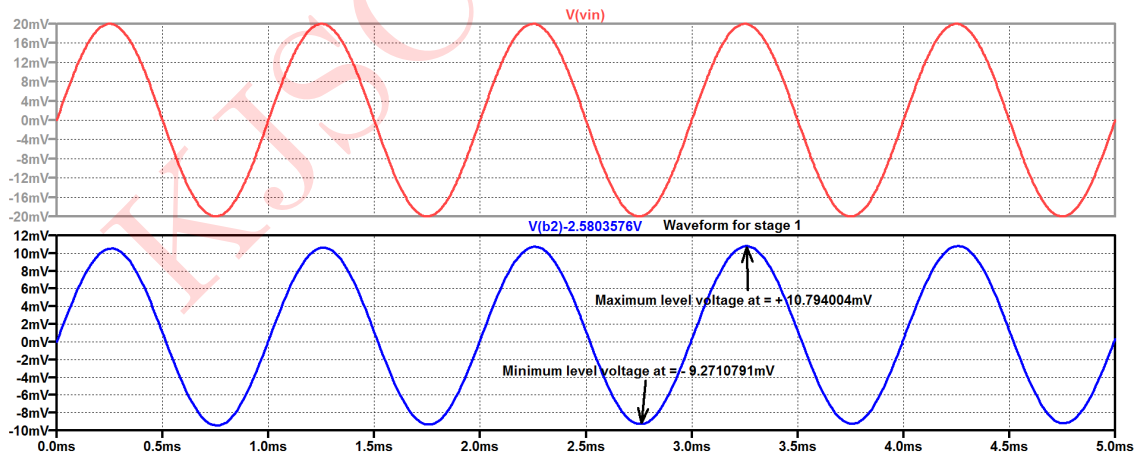


Figure 5: Input and Output waveform for stage 1

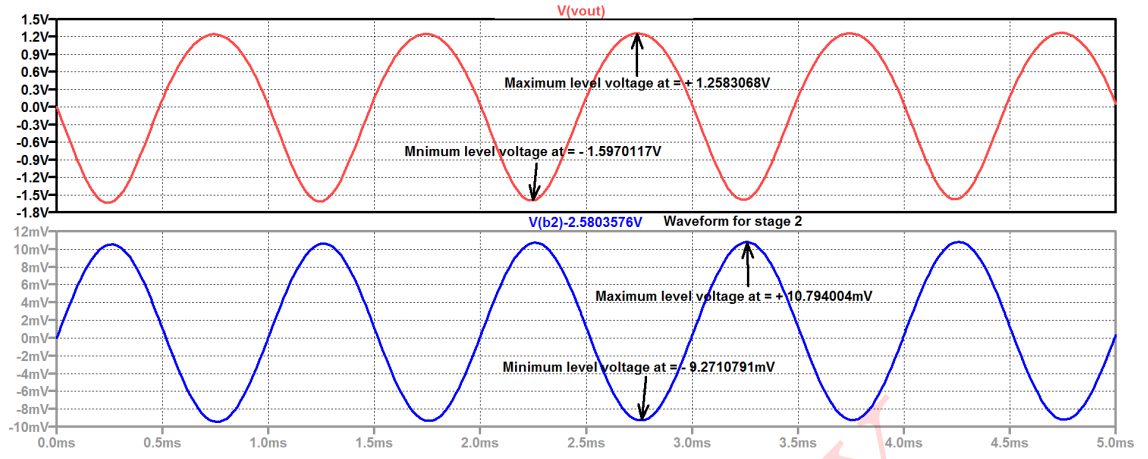


Figure 6: Input and Output waveform for stage 2

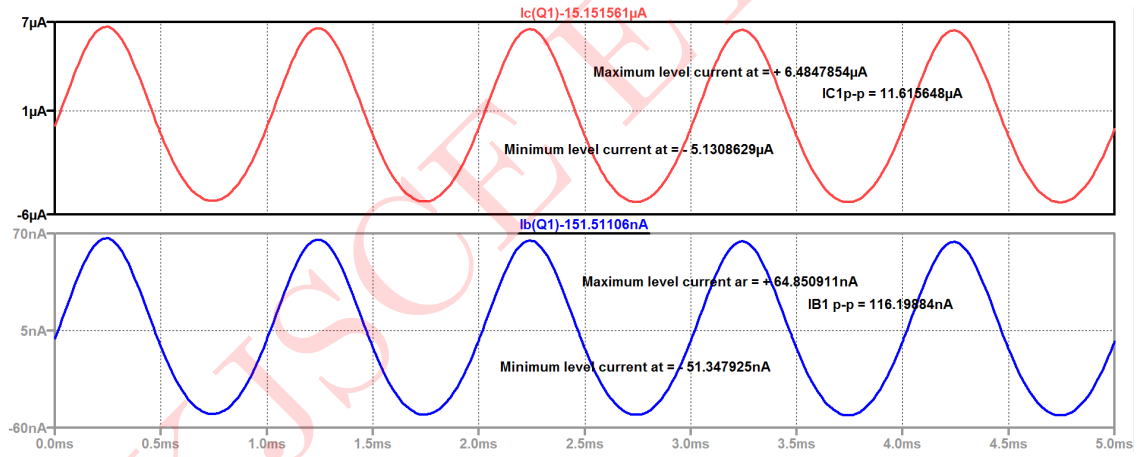


Figure 7: Input and Output Waveforms for A_{i1}

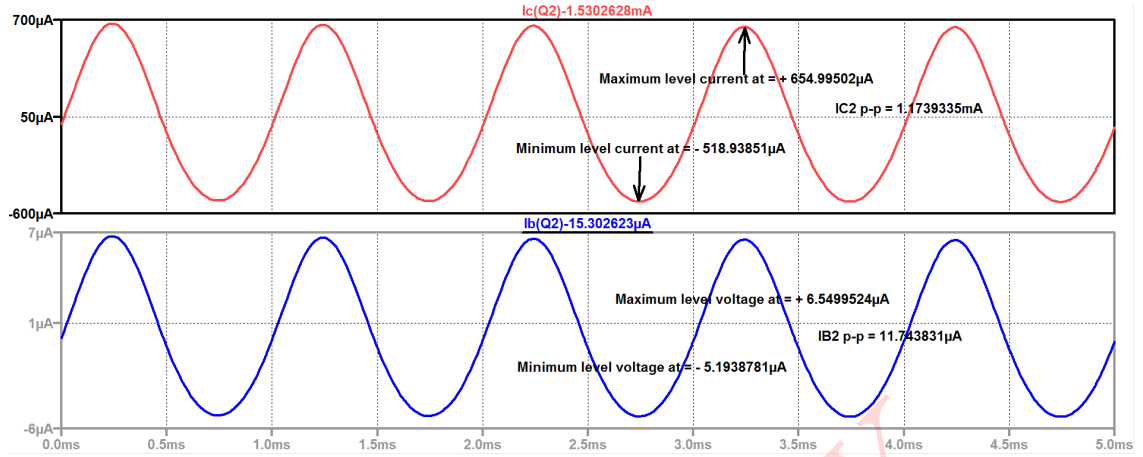


Figure 8: Input and Output Waveforms for A_{i_2}

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
$I_{B_1}, I_{C_1}, I_{E_1}$	$0.148\mu A, 14.8\mu A, 14.95\mu A$	$0.151\mu A, 15.1\mu A, 15.3\mu A$
$I_{B_2}, I_{C_2}, I_{E_2}$	$14.95\mu A, 1.49mA, 1.51mA$	$15.3\mu A, 1.53mA, 1.54mA$
V_{E_2}, V_{C_2}	$1.812V, 8.24V$	$1.84V, 8.27V$
A_{V_1}, A_{V_2}	$0.495, 137.83$	$0.501, 141.64$
$A_{V_t}(dB)$	36.68	37.02
A_{i_1}, A_{i_2}	$100, 100$	$99.96, 99.96$
A_{i_T}	10000	9992.0016
V_{out}	$2.731V$	$2.855V$
Z_i, Z_o	$70.38k\Omega, 42.31\Omega$	—

Table 1: Numerical 1
