

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
AC CIRCUITS

Numerical 1: A series RLC circuit containing a resistance of 15Ω , an inductance of 0.1H and a capacitor of $150\mu\text{F}$ are connected in series across a 220V , 60Hz supply. Calculate:

- Current drawn by the circuit
- V_R , V_L and V_C
- Power factor
- Draw the voltage phasor diagram

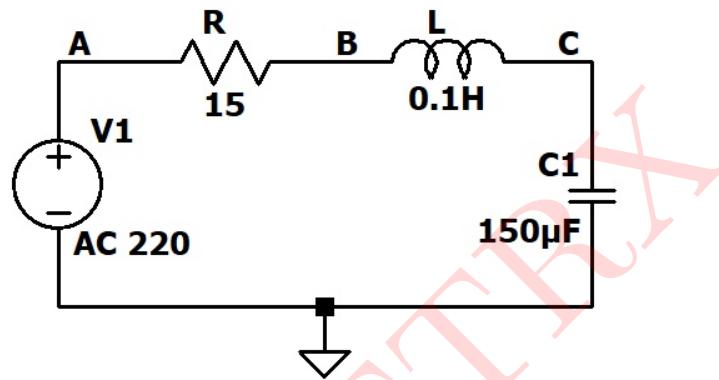


Figure 1: Circuit 1

Solution:

$$X_L = 2\pi f L = 37.6991\Omega$$

$$V_C = \frac{1}{2\pi f C} = 17.6839\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 25.0122\Omega$$

$$\text{a) } I = \frac{V_S}{Z}$$

$$I = \frac{220}{25.0122} = 8.7957A$$

$$\text{b) } V_R = I \times R = 131.9355V$$

$$V_L = I \times X_L = 331.589V$$

$$V_C = I \times X_C = 155.542V$$

$$\text{c) } \cos \phi = \frac{R}{Z} = 0.5997$$

$$\therefore \phi = 53.1515^\circ$$

d) Voltage phasor diagram:

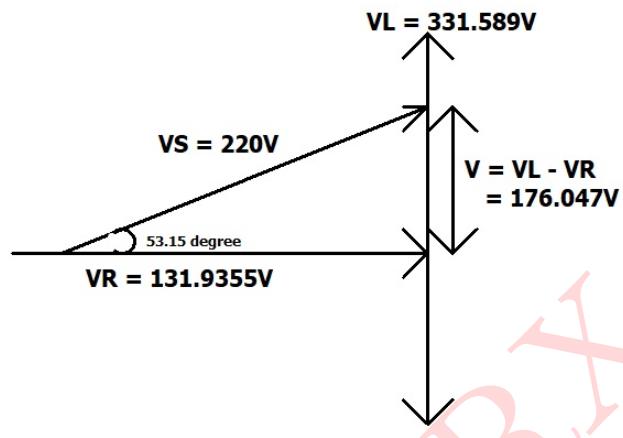


Figure 2: Circuit 1

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

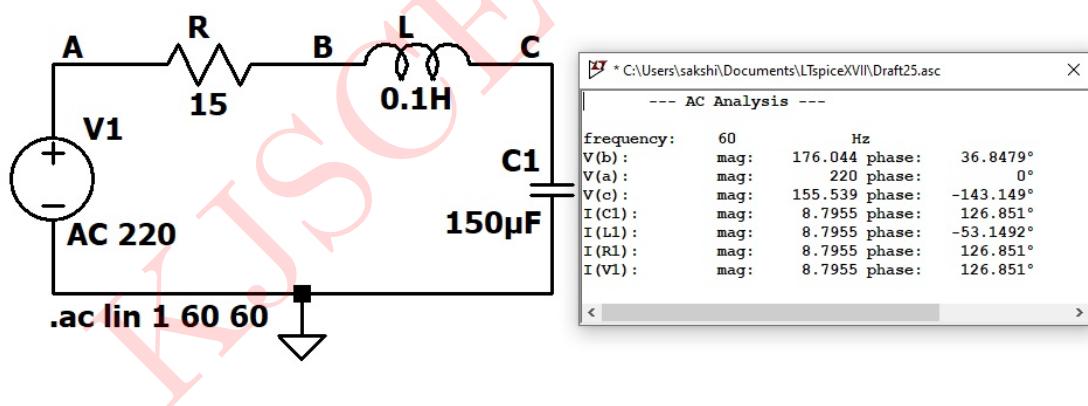


Figure 3: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I	8.7957A	8.7655A
V_R	131.9355V	131.933V
V_L	331.589V	331.583V
V_C	155.542V	155.539V
<i>powerfactor</i>	0.5997	0.5997

Numerical 2: In the given RL circuit $R = 3\Omega$ and $L = 0.15H$
Find:

- Current through the circuit
- Power factor

If a 50Hz AC voltage $V = 230\angle 60^\circ$ is applied across the circuit 2

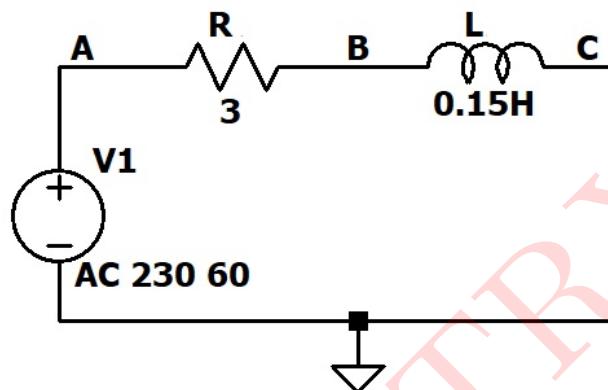


Figure 4: Circuit 2

Solution:

$$X_L = 2\pi fL = 47.12388\Omega$$

$$Z = 3 + j47.12388 = 47.21927\angle 86.357^\circ$$

$$\text{a) } I = \frac{V_S}{Z}$$

$$I = \frac{230\angle 60^\circ}{47.21927\angle 86.357^\circ} = 4.87089\angle -26.35^\circ A$$

$$\text{b) power factor} = \cos \phi = \cos(26.35) = 0.8961$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

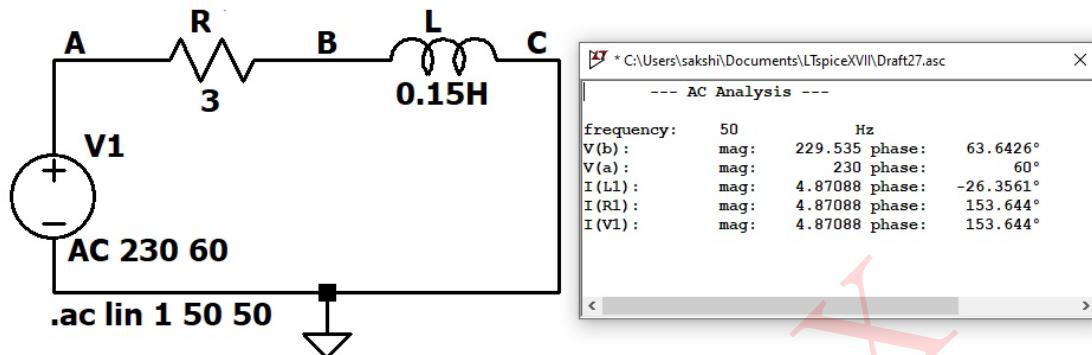


Figure 5: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I	$4.870892 \angle -26.35A$	$4.870892 \angle -26.35A$
$power\ factor$	0.891	0.8961

Numerical 3: A voltage $V = 120\sin(314)t$ is applied to a circuit consisting of a 40Ω resistor and a $95\mu F$ capacitor in series.

Determine:

- An expression for the value of current flowing at any instant
- V_R and V_C
- Power factor

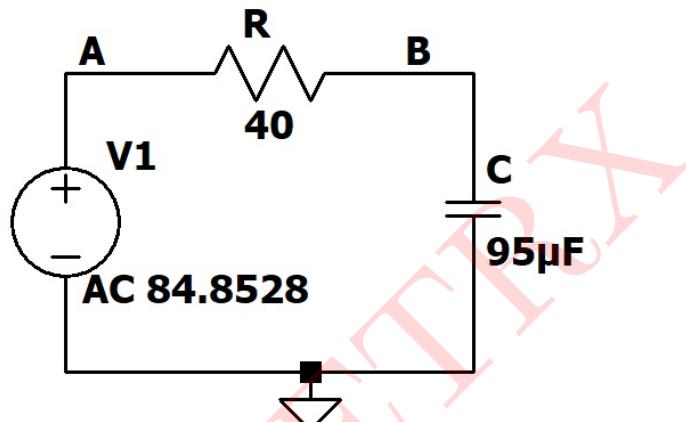


Figure 6: Circuit 3

Solution:

$$V = 120 \sin(314)t$$

$$\therefore V_{rms} = \frac{120}{\sqrt{2}} = 84.8528V$$

$$V_C = \frac{1}{2\pi f C}$$

$$V_C = \frac{1}{0.02982} = 33.5233\Omega$$

$$Z = \sqrt{R^2 + (X_C)^2} = 52.1901\Omega$$

$$\text{a) } I = \frac{V_S}{Z}$$

$$I = \frac{84.8528}{52.1901} = 1.6258A$$

$$\text{b) } V_R = I \times R = 65.0336V$$

$$V_C = I \times X_C = 54.5035V$$

$$\text{c) } \cos \phi = \frac{R}{Z} = 0.766428$$

$$\therefore \phi = 39.9658^\circ$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

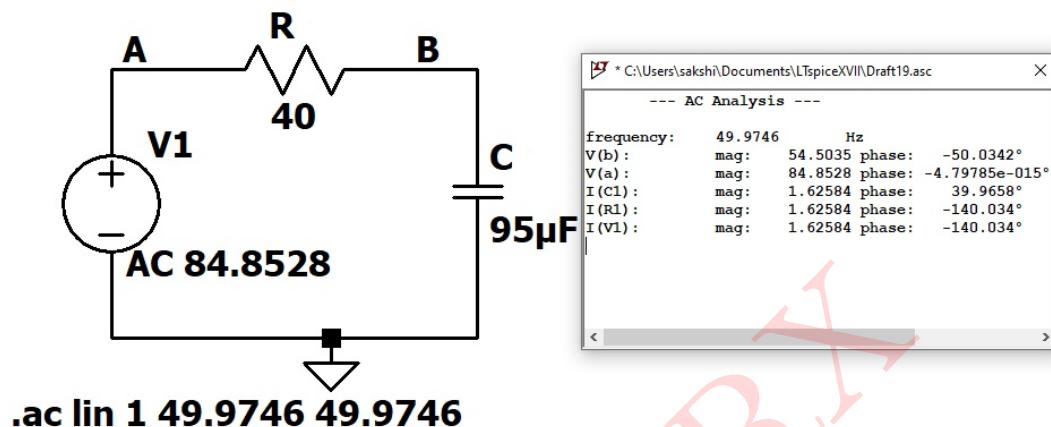


Figure 7: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I	1.6258A	1.6258A
V_R	65.0336V	65.0336V
V_C	54.5035V	54.5035V
powerfactor	0.766428	0.766428

Numerical 4: A circuit consists of resistance of 20Ω , an inductance of 54mH and a Capacitor of $30\mu\text{F}$ are connected in parallel across a 110V 50Hz supply, calculate:

- Individual current drawn by each supply
- Total current drawn from the supply
- Overall Power factor of the circuit
- Draw the phasor diagram

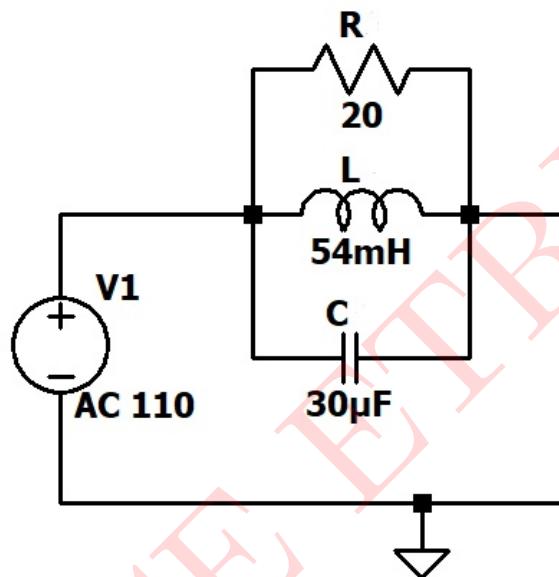


Figure 8: Circuit 4

Solution:

$$X_L = 2\pi fL = 16.9646\Omega$$

$$V_C = \frac{1}{2\pi fC} = 106.1033\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = 91.35484\angle - 77.3536\Omega$$

$$\text{a)} I = \frac{V_S}{Z}$$

$$I = \frac{110}{91.35484\angle - 77.3536} = 1.204096\angle 77.3536A$$

$$\text{b)} I_R = \frac{V}{R} = 5.5\angle 0A \text{(In phase)}$$

$$I_L = \frac{V}{X_L} = 6.4840\angle 90A$$

$$I_C = \frac{V}{X_C} = 1.03673\angle - 90A$$

$$\text{c)} \text{Power factor} = \cos \phi = \frac{R}{Z} = 0.218926 \text{ (lagging)}$$

$$\therefore \phi = -77.3536^\circ$$

d) Phasor diagram:

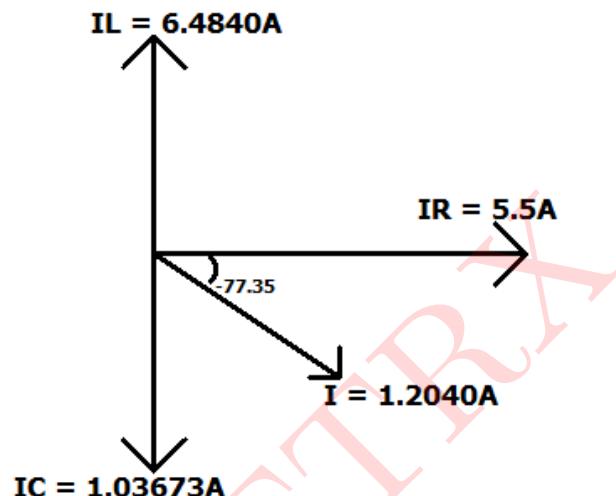


Figure 9: Phasor diagram

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

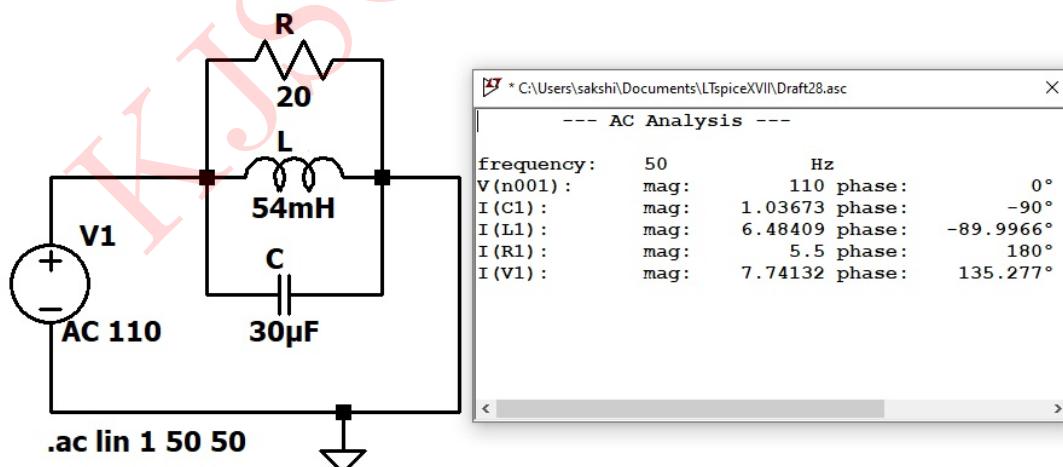


Figure 10: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I	$1.2040\angle -77.35A$	$1.2040\angle -77.35A$
I_R	$5.5\angle 0A$	$5.5\angle 0A$
I_L	$6.4840\angle 90A$	$6.4840\angle 89.99A$
I_C	$1.03673\angle -90A$	$1.03673\angle -90A$

Numerical 5: A coil having a resistor of $R_1 = 5\Omega$ and an inductance of $L_1 = 0.02H$ is Arranged in parallel with another coil having a resistor of $R_2 = 1\Omega$ and an Inductance of $L_2 = 0.08H$, Find:

- Current through I , I_1 and I_2 when a voltage of $V_1 = 110V$ at 60Hz is applied
- Also the Power factor of the circuit

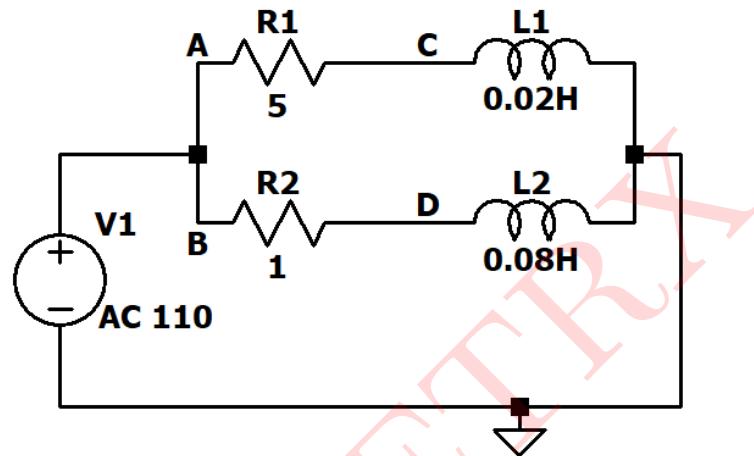


Figure 11: Circuit 5

Solution:

$$X_{L_1} = 2\pi f L_1 = 7.5398\Omega$$

$$X_{L_2} = 2\pi f L_2 = 30.1593\Omega$$

$$Z_1 = 5 + j7.5398 = 9.04702\angle56.449\Omega$$

$$Z_2 = 1 + j30.1593 = 30.17587\angle88.10\Omega$$

$$\text{a) } I_1 = \frac{X_{L_1}}{Z_1}$$

$$I_1 = \frac{7.5398}{9.04702\angle56.449} = 12.1587\angle-56.449A$$

$$I_2 = \frac{X_{L_2}}{Z_2}$$

$$I_2 = \frac{30.1593}{30.17587\angle88.10} = 3.645296\angle-88.10A$$

$$I = I_1 + I_2 = 15.8039\angle -63.20$$

$$\text{b) power factor} = \frac{I_1}{I} = 0.769343$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

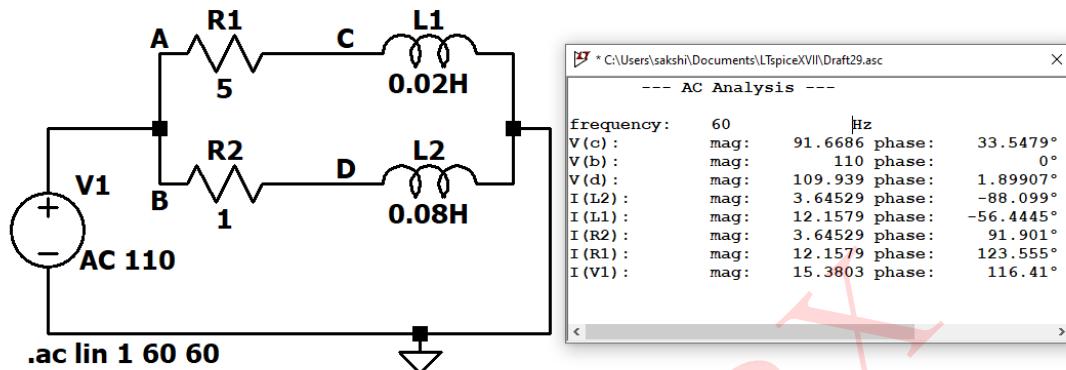


Figure 12: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I	$15.8039 \angle -63.20\text{A}$	$15.3803 \angle -63.20\text{A}$
I_1	$12.1587 \angle -56.449\text{A}$	$12.1579 \angle -56.445\text{A}$
I_2	$3.645296 \angle -88.1\text{A}$	$3.64529 \angle -88.009\text{A}$
Powerfactor	0.76934	0.76934

Numerical 6: Find I , I_1 and I_2 and voltage drop in each branch in the following figure 13 if $R_1 = 8\Omega$, $L_1 = j4\Omega$, $R_2 = 15\Omega$, $L_2 = j8\Omega$, $R_3 = 9\Omega$, $C_1 = -j6\Omega$, $V_1 = 100V$, Frequency = 50Hz

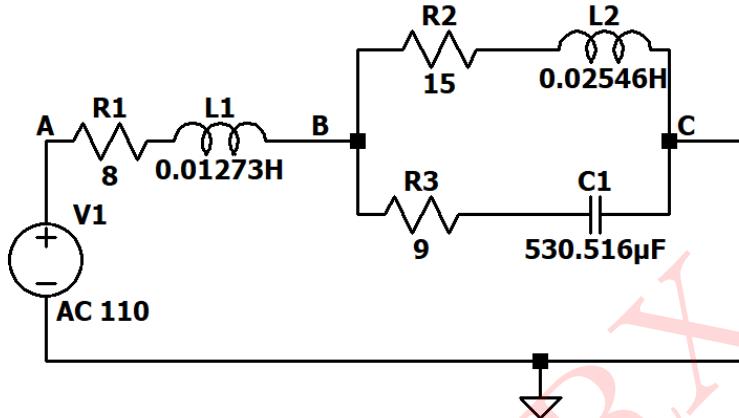


Figure 13: Circuit 6

Solution:

$$Z_1 = 8+j4 = 8.9443 \angle 26.5650^\circ \Omega$$

$$Z_2 = 15+j8 = 17 \angle 28.0725^\circ \Omega$$

$$Z_3 = 9 - j6 = 10.8167 \angle -33.69^\circ \Omega$$

$$Z = 15.15 + j2.624 = 15.7307 \angle 9.602^\circ \Omega$$

a) $I = 6.3569 \angle -9.607^\circ A$

$$I_1 = I \times \frac{Z_3}{Z_2 + Z_3}$$

$$I_1 = 6.3569 \angle -9.607 \times \frac{9 - j6}{j8 + 15 + 9 - j6}$$

$$I_1 = 2.8551 \angle -48.0563^\circ A$$

$$I_2 = I - I_1 = (6.3569 \angle -9.607) - (2.8551 \angle -48.0563)$$

$$I_2 = 4.4873 \angle 13.7059^\circ A$$

b) $V_1 = I \times Z_1 = (6.3569 \angle -9.6027) \times (8 + j4)$

$$V_1 = 56.8578 \angle 16.9623^\circ V$$

$$V_2 = I \times Z_2 = (2.8551 \angle -48.0563) \times (15 + j8)$$

$$V_2 = 48.5367 \angle -19.9838^\circ V$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

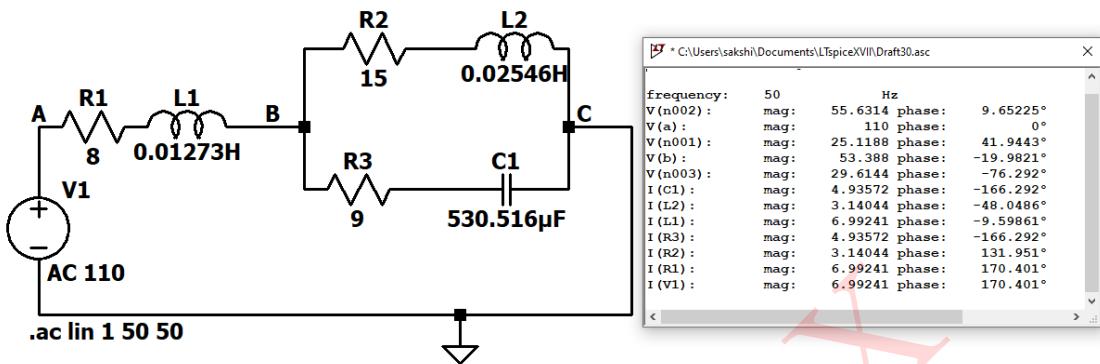


Figure 14: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I	$6.3569 \angle -9.607A$	$6.3567 \angle -9.5986A$
I_1	$2.8551 \angle -48.0563A$	$2.8549 \angle -48.0486A$
I_2	$4.4873 \angle 13.7059A$	$4.48702 \angle 13.708A$
V_1	$56.8578 \angle 16.9623V$	$56.8591 \angle 16.9618V$
V_2	$48.5367 \angle -19.9838V$	$48.5346 \angle -19.9821V$

Numerical 7: A 50Hz sinusoidal voltage $V = 141\sin \omega t$ is applied to a series R-L circuit. The value of resistance and inductance are 3Ω and $0.012H$ respectively. Determine:

- Calculate the peak voltage across resistor and inductor and find the peak voltage of Source current in LTspice
- Plot the input source voltage $V_S(t)$ vs input source current $I_S(t)$ in LTspice
- Measure the phase difference between $V_S(t)$ vs $I_S(t)$ in time and degree
- Plot the input source voltage $V_S(t)$ vs voltage across resistor $V_R(t)$ in LTspice
- Measure the phase difference between $V_S(t)$ vs $V_R(t)$ in time and degree

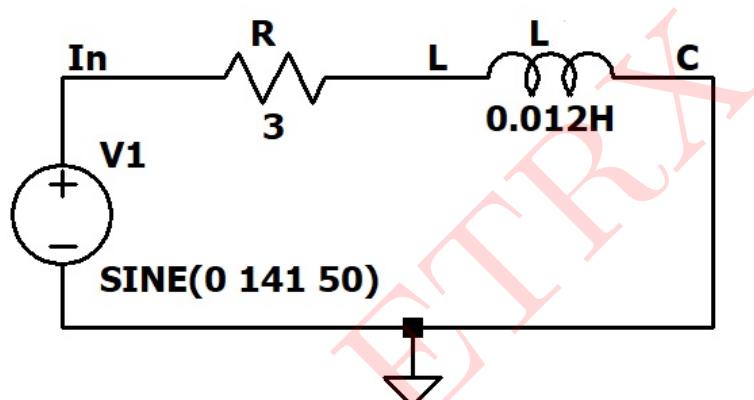


Figure 15: Circuit 7

Solution:

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{rms} = \frac{141}{\sqrt{2}} = 99.7020V$$

$$X_L = 2\pi fL$$

$$X_L = 2 \times \pi \times 50 \times 0.012 = 3.76991\Omega \dots (\pi = 3.14)$$

$$Z = R + jX_L = 3 + j3.76991 = 4.8179\angle 51.4881$$

$$I = \frac{V}{Z}$$

$$I = \frac{99.7020\angle 0}{4.8179\angle 51.488} = 20.6940\angle -51.488A$$

$$V_R = I \times R = 3 \times 20.6941\angle -51.488$$

$$V_R = 62.083\angle -51.488V$$

$$V_L = I \times L$$

$$V_L = (20.6941\angle -51.488) \times (3.76991\angle 90)$$

$$V_L = 78.01489\angle 38.512V$$

$$\text{Peak value of current} = I_{rms} \times \sqrt{2} = 29.26587A$$

$$V_R(\text{peak}) = V_R(\text{rms}) \times \sqrt{2}$$

$$V_R(\text{peak}) = 87.79862V$$

$$V_L(\text{peak}) = V_L(\text{rms}) \times \sqrt{2}$$

$$V_L(\text{peak}) = 110.3297V$$

c) Power factor = $\cos \phi = \cos(51.488) = 0.622678$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

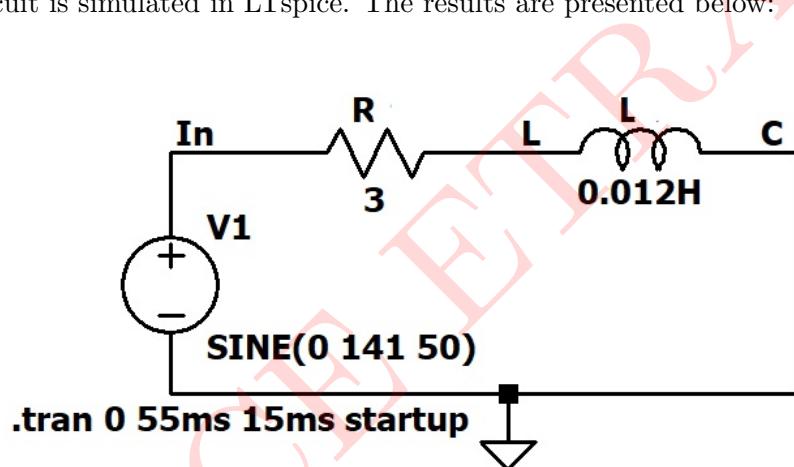


Figure 16: Circuit Schematic

The $V_S(t)$ vs $I_S(t)$ curve is shown in figure 17:

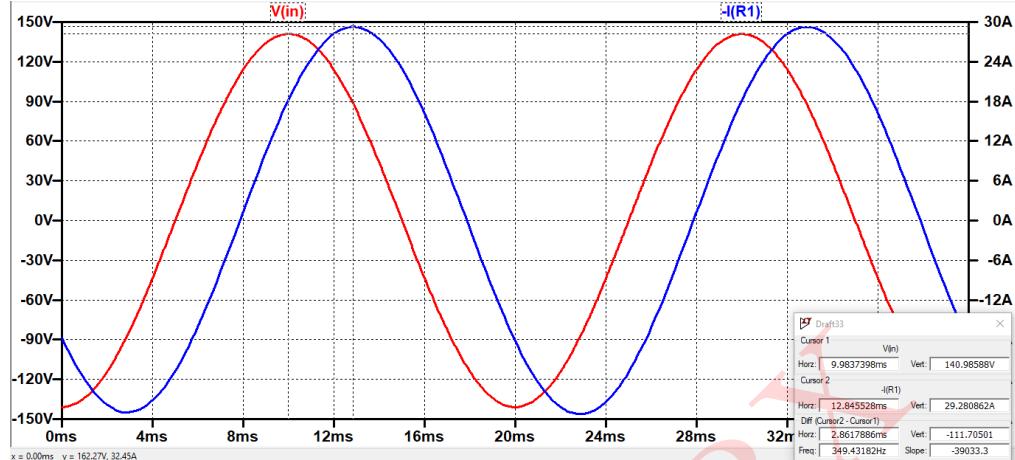


Figure 17: Plot of input source voltage vs input source current

The input vs output source voltage is shown in figure 18:

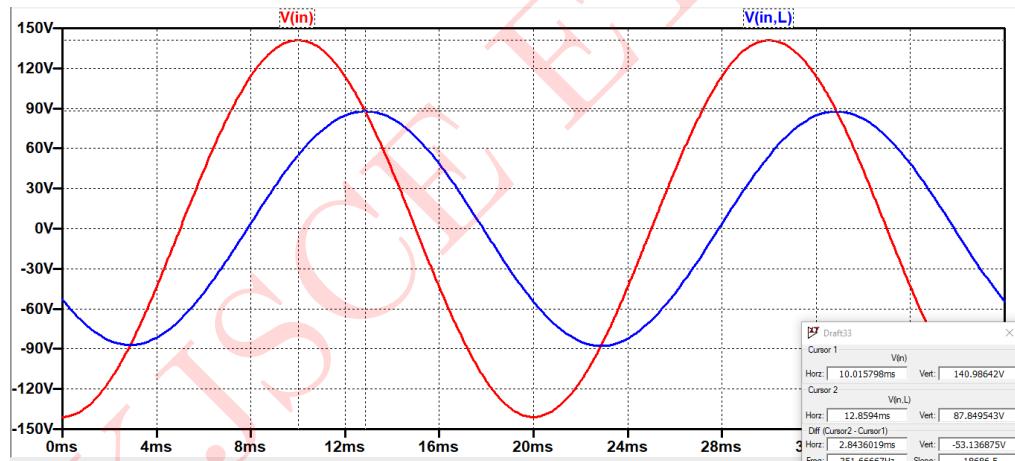


Figure 18: Plot of input source voltage vs voltage across resistere

Input source voltage vs voltage across Inductor is shown in figure 19:

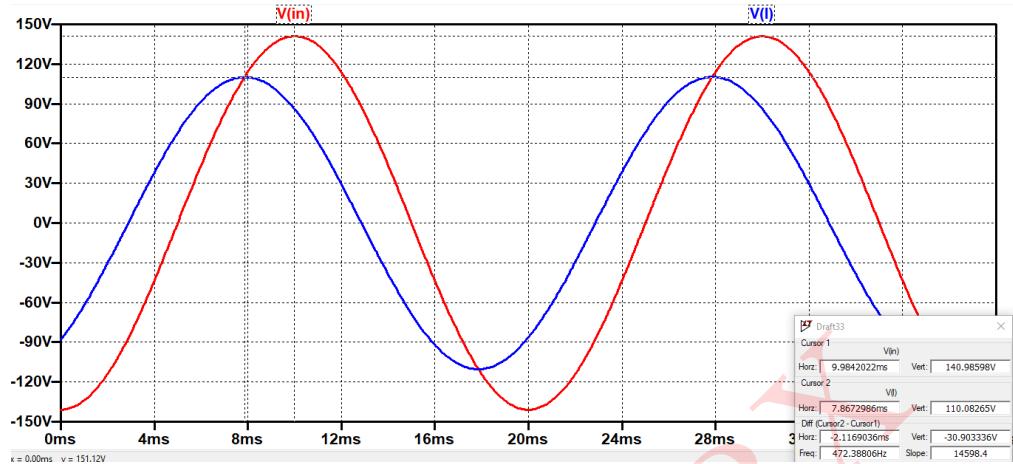


Figure 19: Plot of input source voltage vs voltage across Inductor

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I_{peak}	29.26587A	29.281052A
$V_R(peak)$	87.7862V	87.84V
$V_L(peak)$	110.3297V	110.08134V
$\phi(V_S, I_S)$	51.488°	51.5121948°
$\phi(V_S, V_R)$	51.488°	51.1848342°
$\phi(V_S, V_L)$	38.512°	38.1042648°

Numerical 8: A pure resistance of 33Ω is in series with a pure capacitor of $90\mu F$. The series combination is connected across $110V, 60Hz$ supply. Determine:

- Calculate Peak voltage across resistor and capacitor and also find the peak value of Source current in LTspice
- Plot $V_S(t)$ vs $I_S(t)$ in LTspice
- Measure the phase difference between $V_S(t)$ vs $I_S(t)$ in time and phase
- Plot $V_S(t)$ vs $V_R(t)$ in LTspice
- Measure phase difference between $V_S(t)$ vs $V_R(t)$
- Plot $V_S(t)$ vs $V_C(t)$ in LTspice
- Measure the phase difference between $V_S(t)$ vs $V_C(t)$
- Calculate the power factor of the circuit

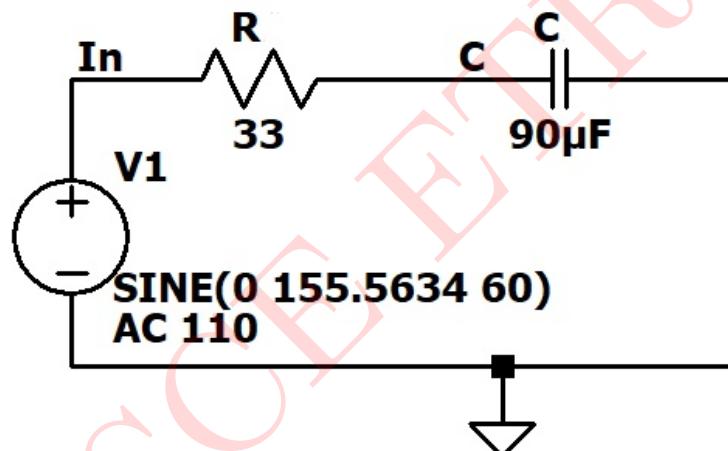


Figure 20: Circuit 8

Solution:

$$V_{rms} = 110V$$

$$X_c = \frac{1}{2\pi f C}$$

$$X_c = \frac{1}{2 \times \pi \times 60 \times 90\mu F} = 29.4733\Omega \dots (\pi = 3.14)$$

$$Z = R + jX_C = 33 + j29.4733 = 44.2456\angle 41.7690$$

$$I = \frac{V}{Z}$$

$$I = \frac{110\angle 0}{44.2456\angle 41.7690} = 2.48612\angle -41.7690A$$

$$V_R = I \times R = 33 \times 2.48612\angle -41.7690$$

$$V_R = 82.04196\angle -41.77690V$$

$$V_C = I \times C$$

$$V_C = (2.48612\angle - 41.7690) \times (29.4733\angle - 90)$$

$$V_C = 73.27416\angle - 131.769V$$

$$\text{Peak value of current} = I_{rms} \times \sqrt{2} = 3.515905A$$

$$V_R(\text{peak}) = V_R(\text{rms}) \times \sqrt{2}$$

$$V_R(\text{peak}) = 116.02485V$$

$$V_C(\text{peak}) = V_C(\text{rms}) \times \sqrt{2}$$

$$V_C(\text{peak}) = 103.6253V$$

c) Power factor = $\cos \phi = \cos(41.7690) = 0.745865$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

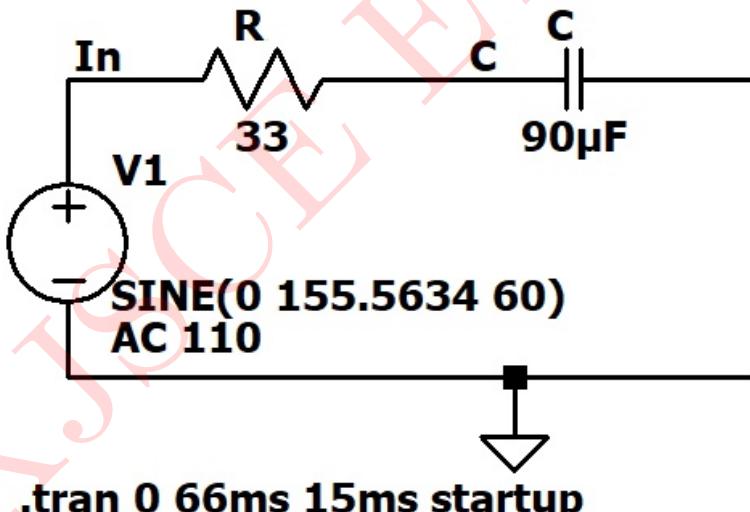


Figure 21: Circuit Schematic

Graph of $V_S(t)$ vs $I_S(t)$ graph is shown below in 22:

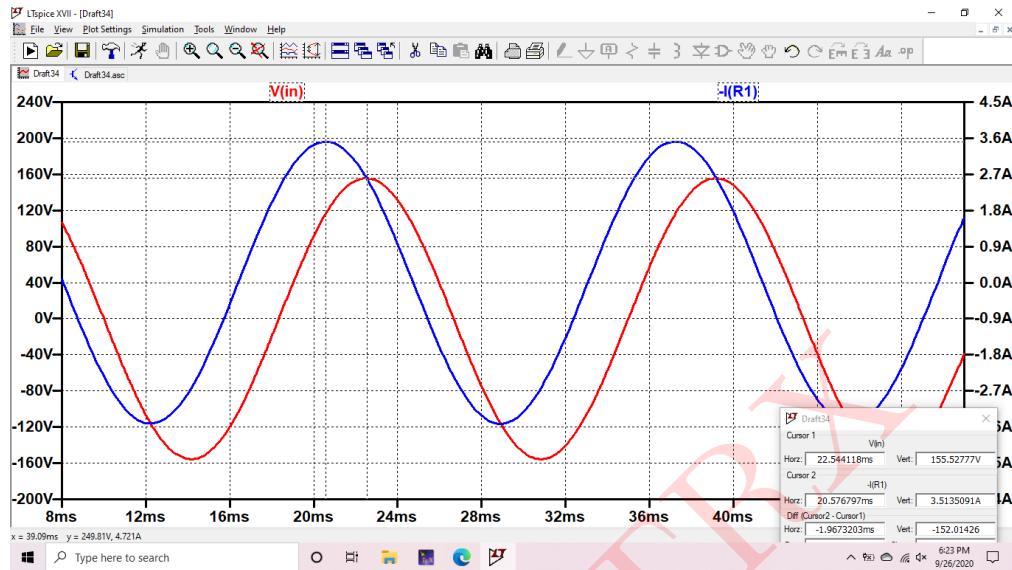


Figure 22: Plot of input source voltage vs input source current

Graph of $V_S(t)$ vs $V_R(t)$ is shown below in figure 23:

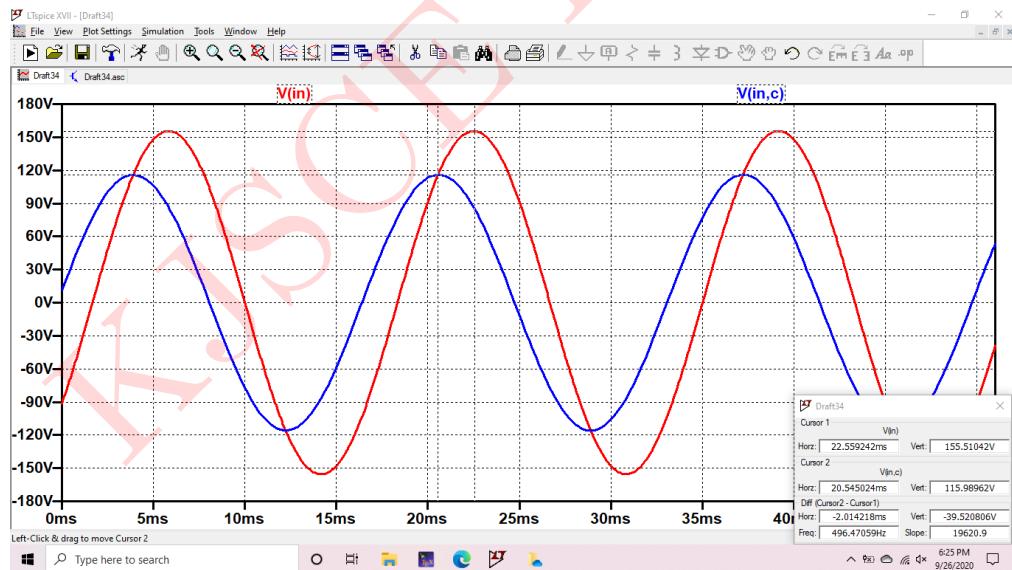


Figure 23: Plot of input source voltage vs voltage across resistor

graph of $V_S(t)$ vs $V_C(t)$ is shown below in figure 24:

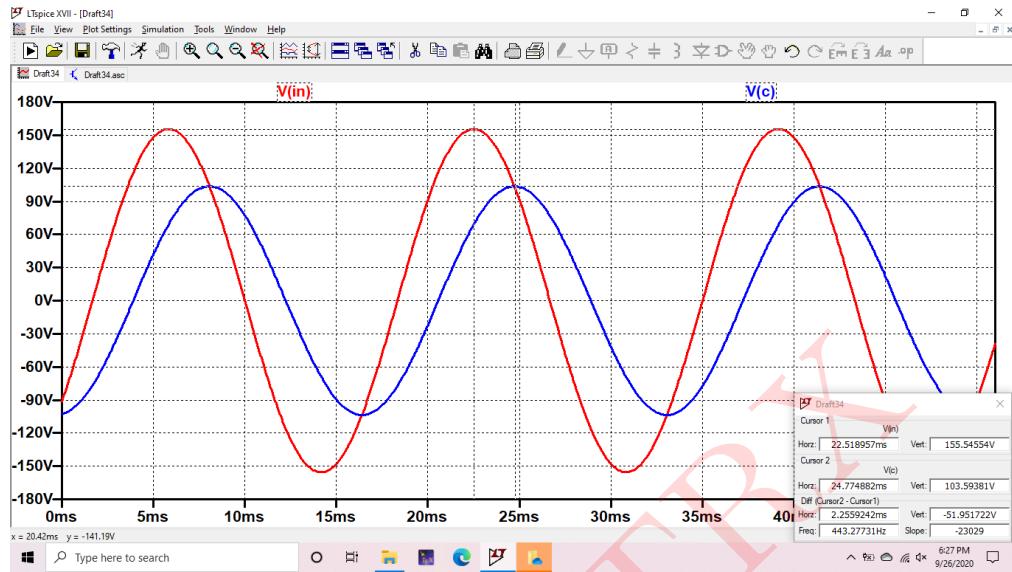


Figure 24: Plot of input source voltage vs voltage across capacitor

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
I_{peak}	$3.515905A$	$3.515905A$
$V_R(peak)$	$116.02485V$	$115.98962V$
$V_C(peak)$	$103.6253V$	$103.59381V$
$\phi(V_S, I_S)$	41.769°	42.662°
$\phi(V_S, V_R)$	41.769°	42.456°
$\phi(V_S, V_C)$	48.213°	48.7182°

Numerical 9: A series resonance network consisting of a resistor of 20Ω , a capacitor of $5\mu F$ and an inductor of $30mH$ is connected across a sinusoidal supply voltage which has a constant output of AC 9 volts at all frequencies. Calculate, the resonant frequency, the current at resonance, the voltage across the inductor and capacitor at Resonance, the quality factor and the bandwidth of the circuit. Plot the resonance curve, the current at resonance, the voltage across the inductor and Capacitor at resonance in LTspice

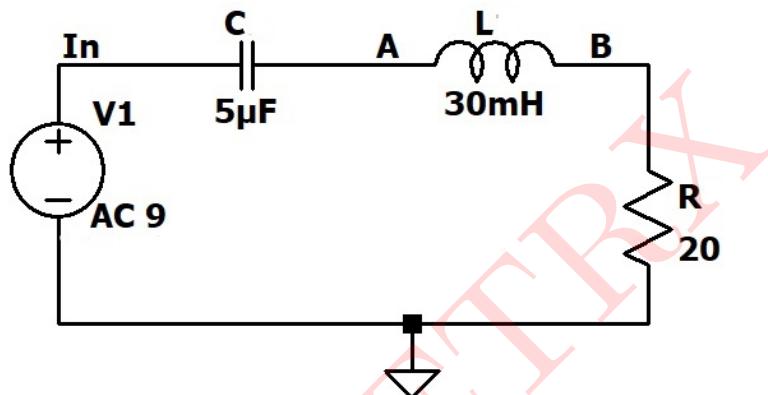


Figure 25: Circuit 9

Solution:

a) Resonant frequency $f_o = \frac{1}{2\pi\sqrt{LC}}$

$$f_o = \frac{1}{2 \times \pi \times \sqrt{30mH \times 5\mu F}} = 410.936Hz$$

b) Circuit current at resonance $I_m = \frac{V}{R}$

$$I_m = \frac{9}{20} = 636.396mA$$

c) Inductive Reactance, $X_L = 2\pi f L = 77.45\Omega$

$$V_L/V_C = I \times X_L = 49.288V$$

d) Quality factor (Q) = $\frac{X_L}{R} = 3.8725$

e) Band width = $\frac{f_o}{Q}$

$$\text{Band width} = \frac{410.936}{3.8725} = 106.116$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

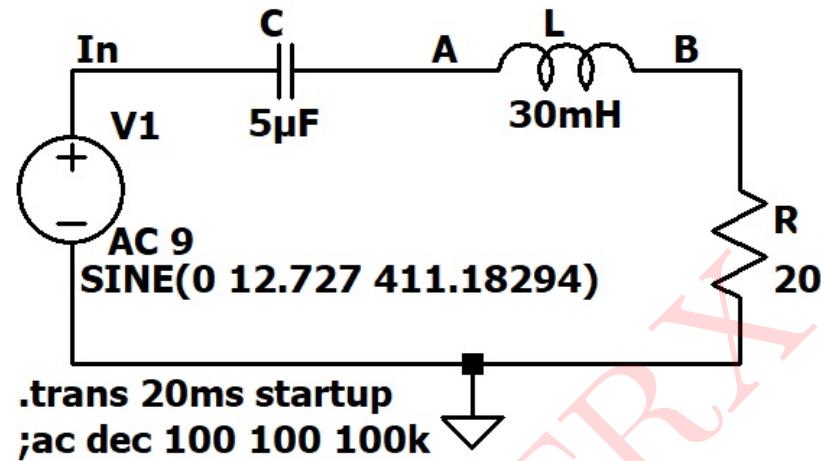


Figure 26: Circuit Schematic

Graph of resonance Curve is shown below in figure 27:

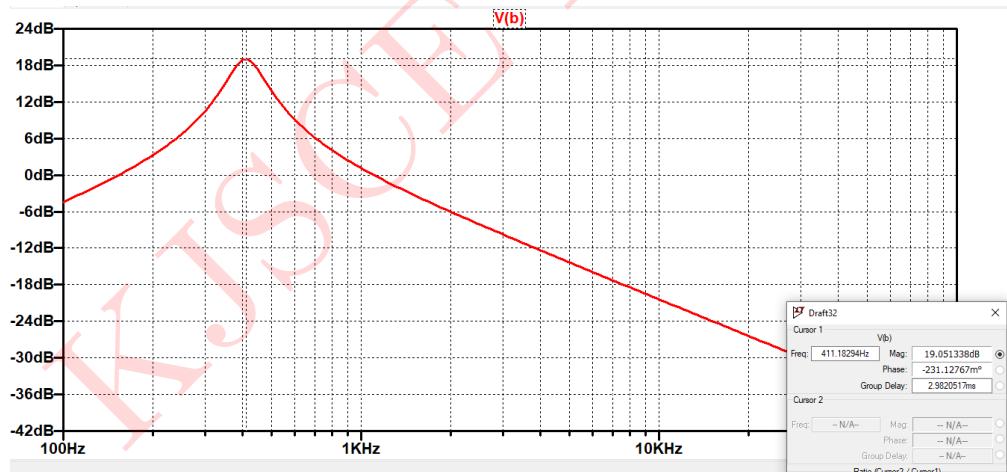


Figure 27: Plot of resonance curve

Graph for current at resonance is shown in figure 28:

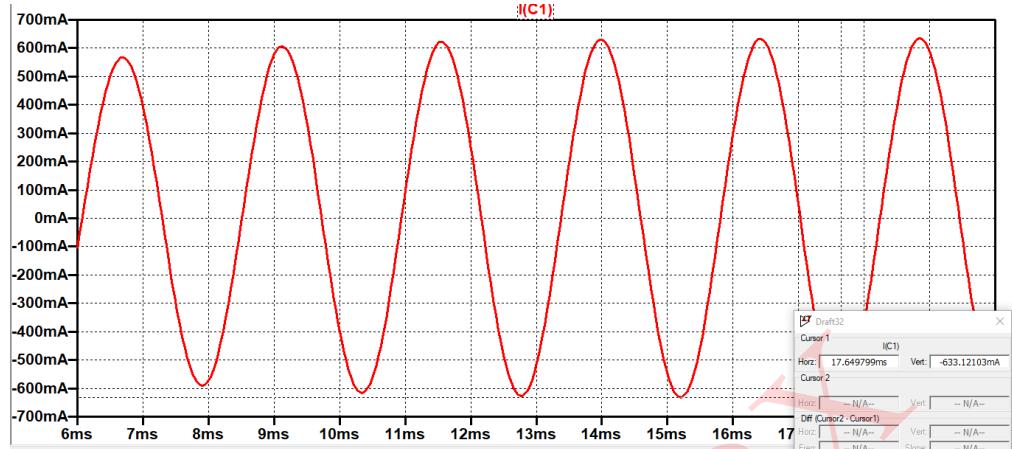


Figure 28: Plot of current at resonance

Graph for Voltage across inductor and capacitor at resonance is shown in figure 29:

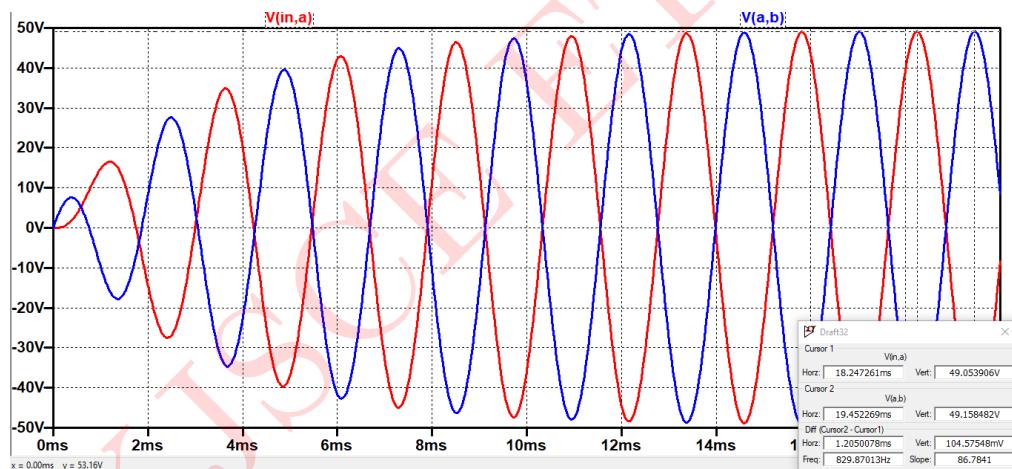


Figure 29: Plot of voltage cross inductor and capacitor at resonance

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
f_o	410.936Hz	411.1829Hz
I_m	636.396mA	634.0582mA
V_L/V_C	49.288V	49.158482V
