

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Differential Amplifier Circuits

Q1. For the differential amplifier :

- a) Name of the circuit
- b) Q point
- c) Differential gain A_d
- d) Common mode Gain

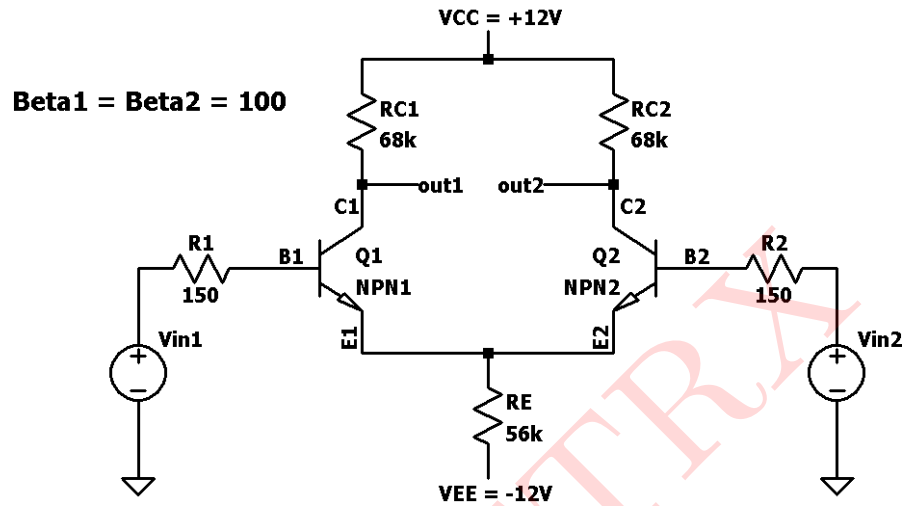


Figure 1: Circuit 1

Given:

$$h_{fe} = 100, h_{ie} = 2k\Omega$$

Solution:

The above circuit is a DIBO (Dual input balanced outout differential amplifier)

DC Analysis:

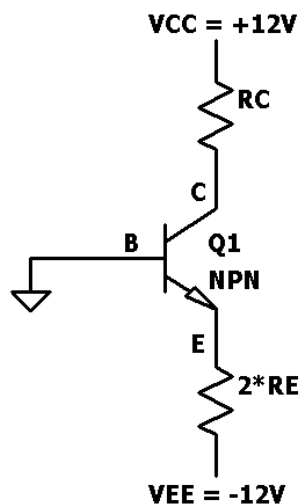


Figure 2: DC equivalent circuit

$$I_{CQ} = \beta \left(\frac{V_{EE} - V_{BE}}{R_1 + \beta(2R_E)} \right)$$

$$I_{CQ} = 100 \left(\frac{12 - 0.7}{150 + 100(2 \times 56k)} \right)$$

$$I_{CQ} = 0.10\text{mA}$$

$$V_{CEQ} = V_{CC} + V_{EE} - I_{CQ}(R_C + 2R_E) = 12 + 12 - 0.1m(180k) = 6\text{V}$$

$$I_{BQ} = I_{CQ}/\beta = 0.1m/100 = 1\mu\text{A}$$

$$V_{C1} = V_{C2} = V_{CC} - I_C R_C = 12 - (0.1m)(68k) = 5.2\text{V}$$

$$V_E = V_C - V_{CE} = 5.2 - 6 = -0.8\text{V}$$

$$r_\pi = \frac{\beta V_T}{I_C} = 100 \times 26/0.1m = 26k\Omega$$

$$|A_d| = \frac{\beta R_C}{R_s + r_\pi} = \frac{100 \times 68k}{150 + 26k} = 260.038$$

$$A_{cm} = \left| \frac{R_C}{2R_E} \right| = \left| \frac{68k}{116k} \right| = 0.6071$$

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| = 260.038/0.6071 = 428.328$$

$$\text{CMRR in dB} = 20 \log_{10}(428.328) = 52.6355\text{dB}$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

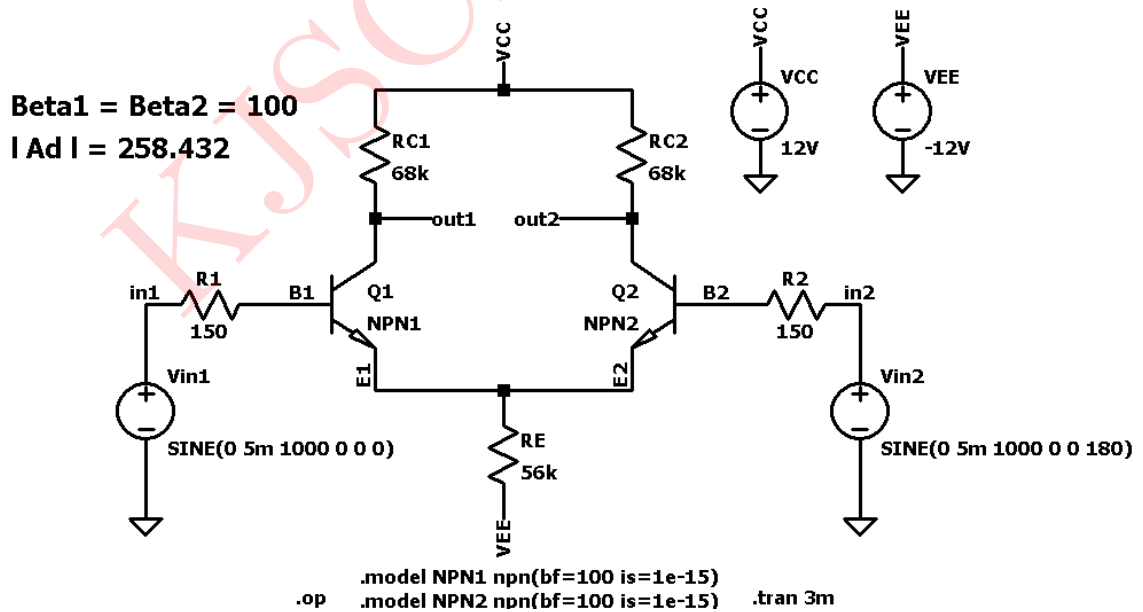


Figure 3: Circuit Schematic

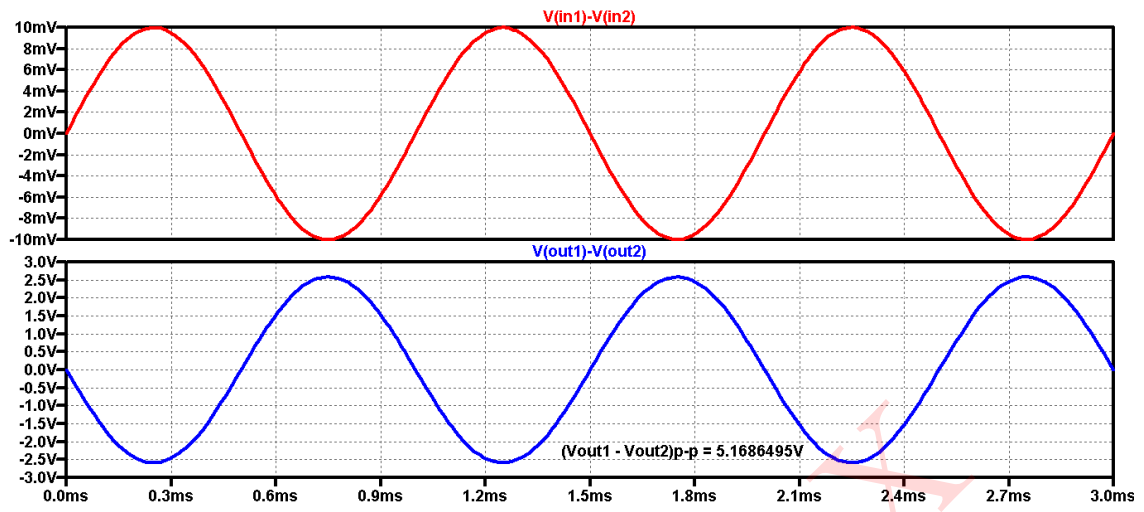


Figure 4: Input output waveform

Comparison of Theoretical and Simulated Values:

Parameters	Simulated	Theoretical
I_C	0.101mA	0.1mA
V_C	5.18V	5.2V
V_{CE}	6V	5.835V
A_d	258.432	260.038
A_{cm}	—	0.6071
CMRR in dB	—	52.6355dB

Table 1: Numerical 1

- Q2. For the differential amplifier :
- Name of the circuit
 - Current through R_{D1} , R_{D2} , R_{D3}
 - A_d
 - Common mode Gain

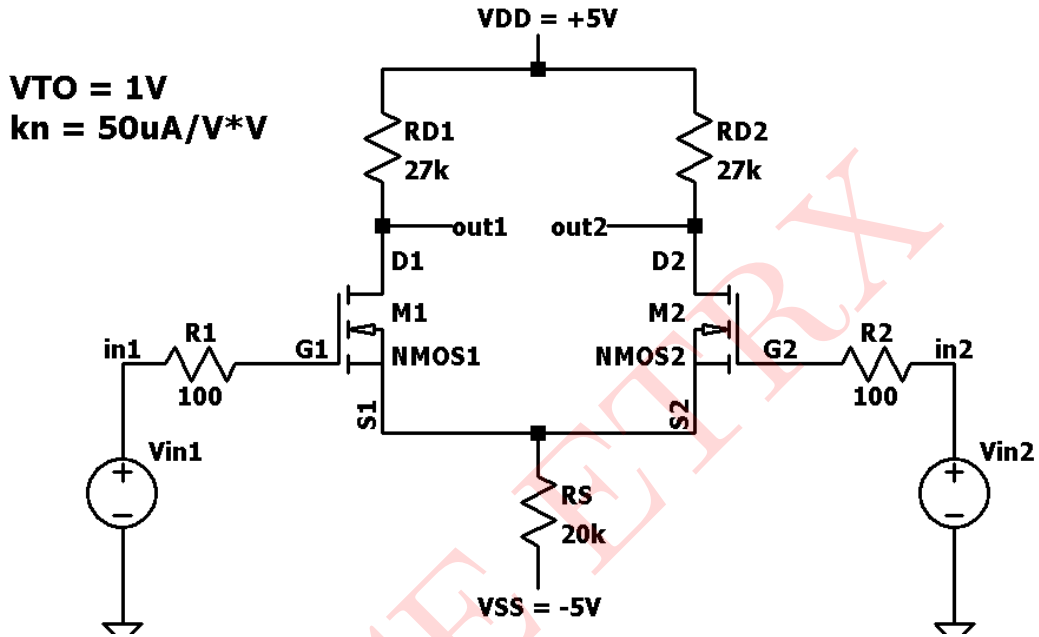


Figure 5: Circuit 2

Given:

$$R_{D1} = R_{D2} = 27k\Omega, R_S = 20k, V_{DD} = 5V$$

Solution:

The above circuit is a DIBO (Dual input balanced outout differential amplifier)

DC Analysis:

$$V_{GSQ} = V_{SS} - 2I_{DQ}R_S$$

$$V_{GSQ} = 5 - 2I_{DQ}20k \text{ ——— (1)}$$

$$I_{DQ} = k_n(V_{GSQ} - V_{TN})^2$$

$$I_{DQ} = 50 \times 10^{-6}(V_{GSQ} - 1)^2 \text{ ——— (2)}$$

Put (2) in (1)

$$V_{GSQ} = 5 - 2 \times 50 \times 10^{-6} \times 20k(V_{GSQ}^2 - 2V_{GSQ} + 1)$$

$$2V_{GSQ}^2 - 3V_{GSQ} - 3 = 0$$

$$V_{GSQ} = 2.186V \text{ or } -0.6861V$$

$$V_{GSQ} = \mathbf{2.186V} (\because V_{GSQ} < V_T)$$

$$I_{DQ} = 50 \times 10^{-6}(2.186 - 1)^2$$

$$I_{DQ} = \mathbf{70.33\mu A}$$

$$V_{DSQ} = (V_{DD} + V_{SS}) - I_{DQ}(R_D + 2R_S) = 10 - (70.33\mu)(67k) = 5.2878V$$

$$V_{D1} = V_{DD} - I_D R_S = 5 - (70.33\mu)(27k) = 3.101V$$

Current through R_{D1} , R_{D2} , $R_S = \mathbf{70.33\mu A}$

$$|A_d| = g_m R_D = 0.118 \times 27k = \mathbf{3.186}$$

$$A_{cm} = \left| \frac{g_m R_D}{1 + 2g_m R_S} \right| = \left| \frac{27k}{2 \times 20k} \right| = \mathbf{0.675}$$

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| = 3.186/0.675 = \mathbf{4.72}$$

$$CMRR \text{ in dB} = 20 \log_{10}(4.72) = \mathbf{13.478dB}$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

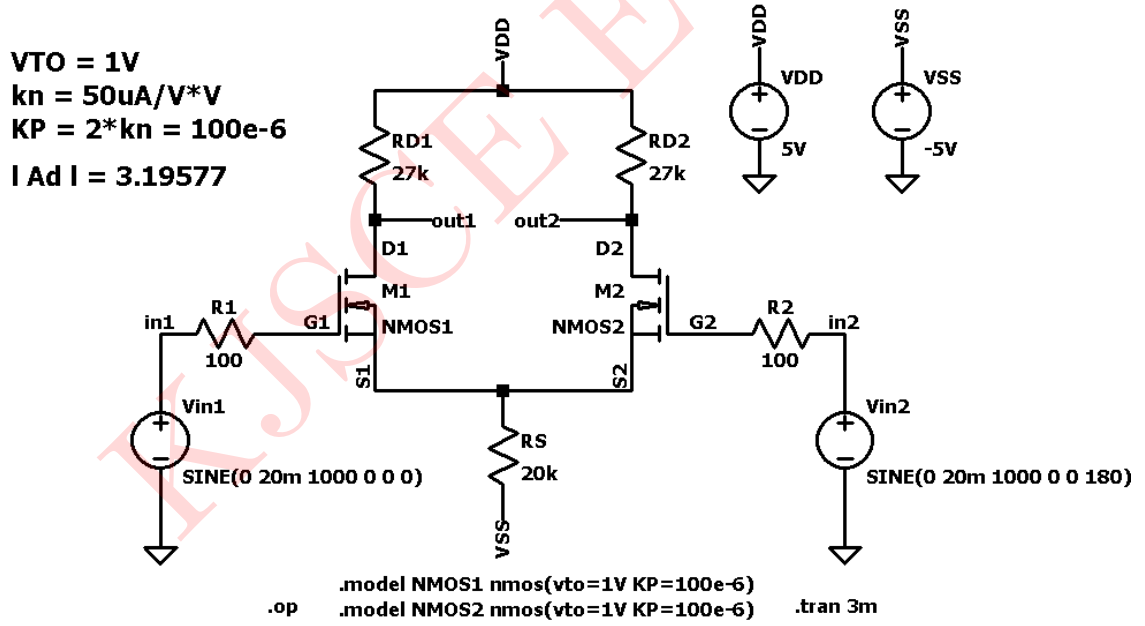


Figure 6: Circuit Schematic

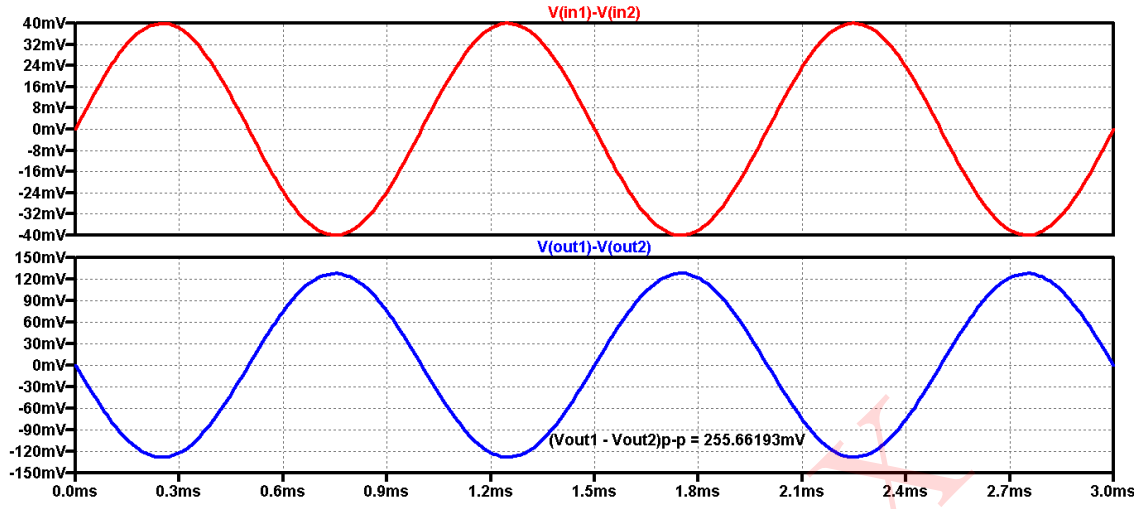


Figure 7: Input output waveform

Comparison of Theoretical and Simulated Values:

Parameters	Simulated	Theoretical
I_D	$70.346\mu\text{A}$	$70.33\mu\text{A}$
V_D	3.100V	3.101V
V_{DS}	5.286V	5.2878V
V_{GS}	2.1861V	2.186V
$ A_d $	3.1957	3.186
A_{cm}	—	0.675
CMRR in dB	—	13.4788dB

Table 2: Numerical 2

Q3. For the differential amplifier :

- Name of the circuit
- I_{D1} , I_{D2} , V_{D1} , V_{D2}
- A_d

$V_{TO} = 0.7V$
 $k_n = 30\mu A/V^2$

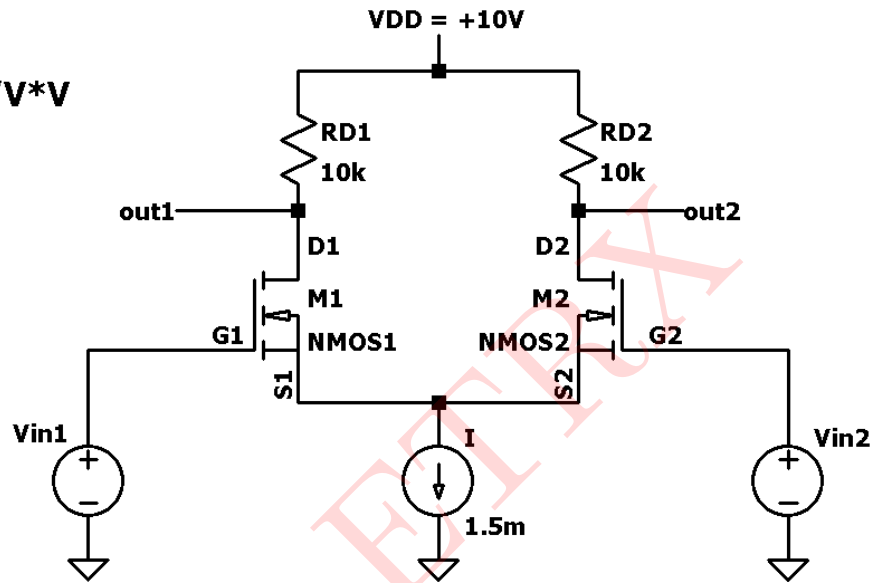


Figure 8: Circuit 3

Given:

$$k_{n1} = k_{n2} = 30\mu A/V^2, I = 1.5mA, V_{DD} = 10V$$

Solution:

The above circuit is a DIBO (Dual input balanced outout differential amplifier)

DC Analysis:

$$I_{D1} = I_{D2} = I/2 = 1.5m/2 = 0.75mA$$

$$V_{D1} = V_{D2} = V_{DD} - I_D R_D = 10 - (0.75m \times 10k) = 2.5V$$

$$A_d = -g_m R_D$$

$$g_m = 2k_n(V_{GS} - V_{TN})$$

Now,

$$I_D = k_n(V_{GS} - V_{TN})^2$$

$$0.75m = 30 \times 10^{-6}(V_{GS} - 0.7)^2$$

$$25 = (V_{GS} - 0.7)^2$$

$$5 = (V_{GS} - 0.7)$$

$$V_{GS} = 5.7V$$

$$g_m = 2 \times 30 \times 10^{-6}(5.7 - 0.7) = 0.3mA/V$$

$$|A_d| = 0.3v \times 10^{-3}(10^4) = 3$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

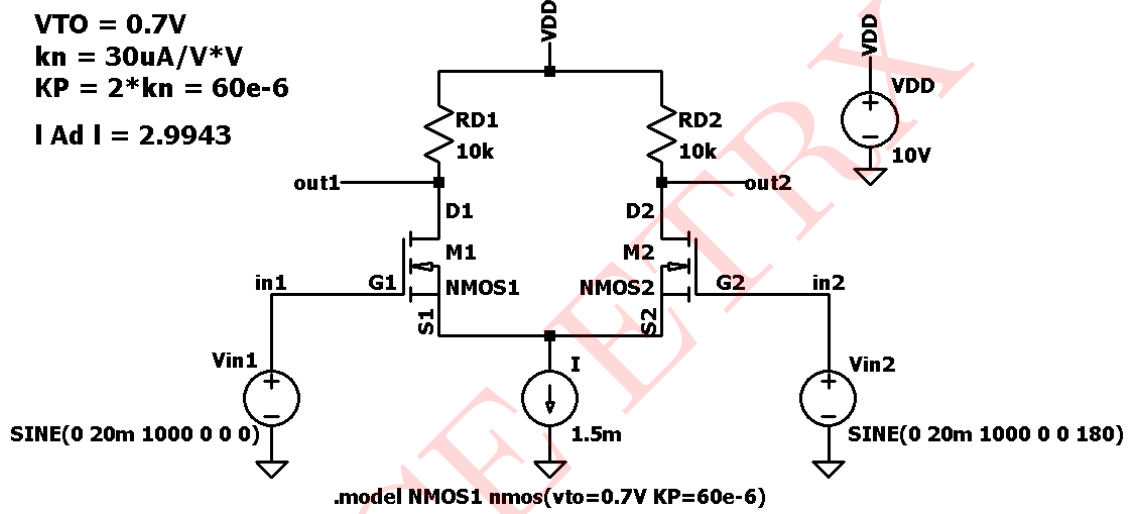


Figure 9: Circuit Schematic

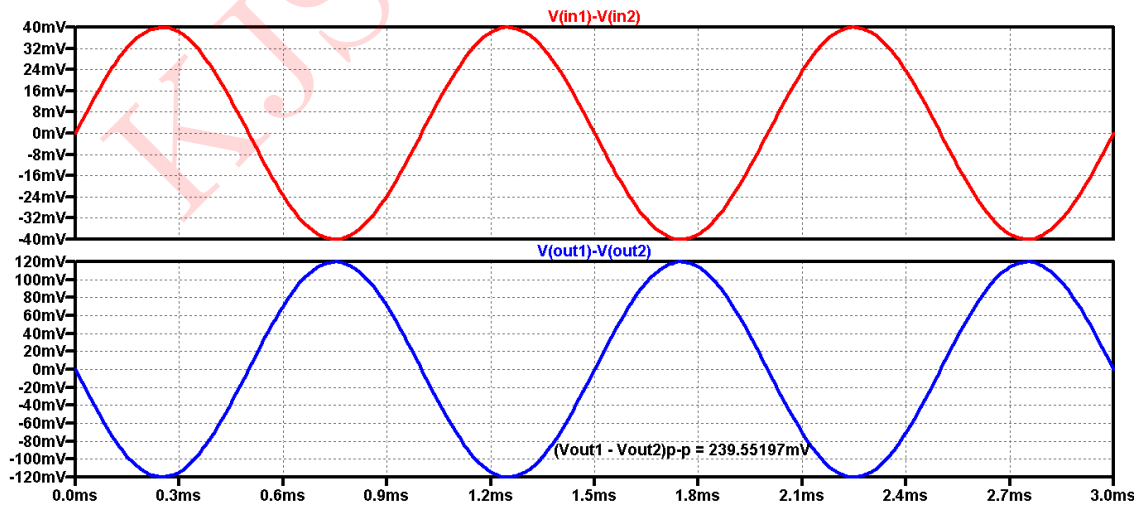


Figure 10: Input and output waveform

Comparison of Theoretical and Simulated Values:

Parameters	Simulated	Theoretical
I_D	0.75 mA	0.75mA
V_D	2.5V	2.5V
$ A_d $	2.9943	3

Table 3: Numerical 3

KJSCE ETRX