

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Multi Transistor Circuits

Numerical 1:

For the circuit shown in figure 1, Determine I_{C1} , I_{C2} , V_{CE1} , V_{CE2} , A_{V1} , A_{V2} , A_{VT} , Input impedance of 1st stage, Output impedance of 2nd stage

Given: $\beta_1 = \beta_2 = 200$

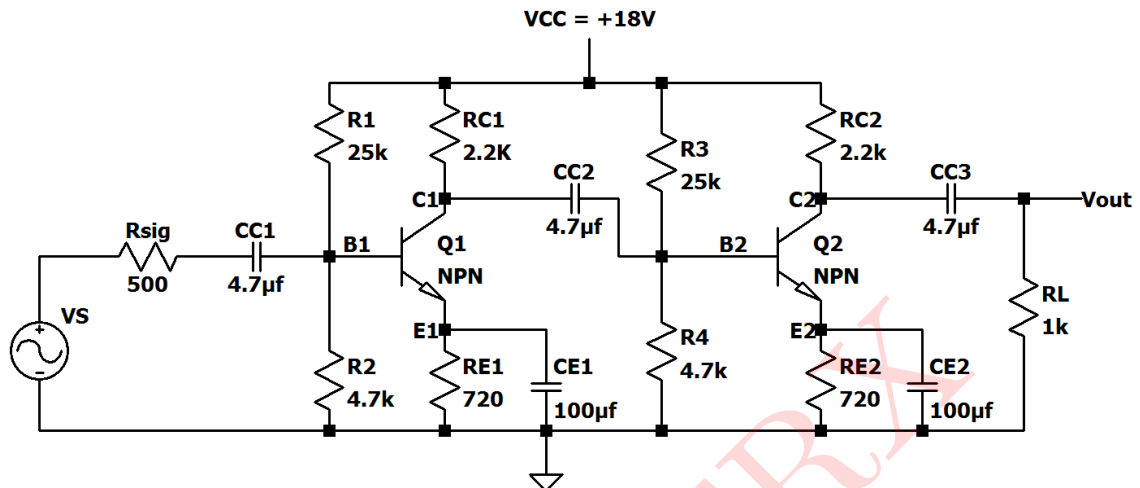


Figure 1: Circuit 1

Solution:

Above given circuit 1 is 2-stage RC coupled CE-CE amplifier

$V_{BE1} = V_{BE2} = 0.7V$ (Assumption)

→ Due to R-C coupling, both the stages Q-point are isolated

→ Since, both the stage are symmetric in parameter and resistor values, DC analysis of one stage is sufficient

DC Analysis:-

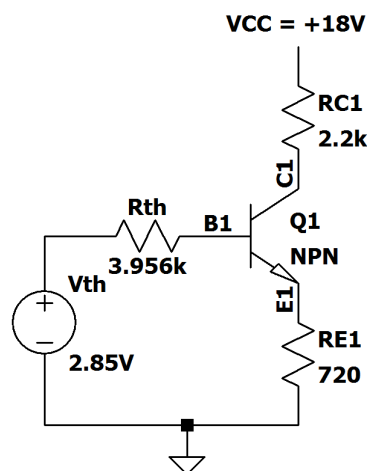


Figure 2: DC Equivalent circuit

$$V_B = V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{4.7k\Omega}{25k\Omega + 4.7k\Omega} \times 18 = 2.85V$$

$$\mathbf{V_{th} = 2.85V}$$

$$R_{th} = R_1 \parallel R_2 = 25k \parallel 4.7k = 3.956k\Omega$$

$$\mathbf{R_{th} = 3.956k\Omega}$$

Applying KVL to the base-emitter loop:-

$$V_{th} - I_B R_{th} - V_{BE(ON)} - I_E R_E = 0$$

$$I_E = I_C + I_B = (\beta + 1)I_B$$

$$\text{Assume } V_{BE(ON)} = 0.7V$$

$$V_{th} - I_B R_{th} - 0.7V - (\beta + 1)I_B R_E = 0$$

$$I_B = \frac{V_{th} - 0.7V}{R_{th} + ((\beta + 1)R_E)} = \frac{2.85 - 0.7}{2.956k\Omega + (201 \times 0.72k\Omega)} = 14.46\mu A$$

$$\therefore \mathbf{I_{B1} = I_{B2} = 14.46\mu A}$$

$$I_C = \beta I_B = 200 \times 14.46\mu A = 2.89mA$$

$$\therefore \mathbf{I_{C1} = I_{C2} = 2.89mA}$$

Applying KVL to the collector-emitter loop:-

$$V_{CE} = V_{CC} - I_C R_C - (\beta + 1)I_B R_E$$

$$V_{CE} = 19 - (2.89mA \times 2.2k\Omega) - (201 \times 720\Omega \times 14.46\mu A) = 9.549$$

$$\mathbf{V_{CE1} = V_{CE2} = 9.549V}$$

Small-Signal parameters:-

$$g_{m1} = \frac{I_C}{V_T} = \frac{2.89mA}{26mV} = 111.15 \text{ mA/V}$$

$$\mathbf{g_{m1} = g_{m2} = 111.15 \text{ mA/V}}$$

$$r_{\pi1} = \frac{V_T}{I_B} = \frac{26mV}{14.46\mu A} = 1.8k\Omega$$

$$\mathbf{r_{\pi1} = r_{\pi2} = 1.8k\Omega}$$

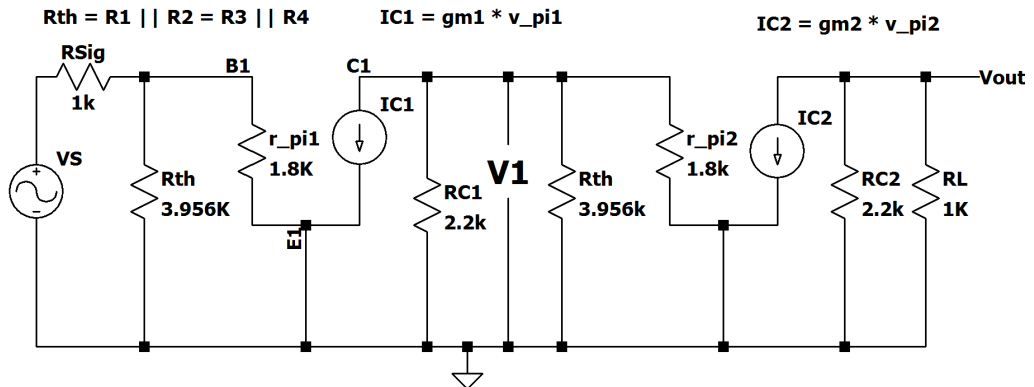


Figure 3: Small Signal Equivalent Circuit

Input Impedance:-

$$Z_i = R_1 \parallel R_2 \parallel r_{\pi_1} = R_{th} \parallel r_{\pi_1} = 3.956k \parallel 1.8k = 1.237k\Omega$$

$$Z_{in} = Z_i + R_{sig} = 1.237k + 0.5k = 1.737k\Omega$$

$$\mathbf{Z_{in} = 1.737k\Omega}$$

Output Impedance:-

$$Z_o = R_{C_2} \parallel R_L$$

$$Z_o = 2.2k \parallel 1k = 687.5\Omega$$

$$\mathbf{Z_o = 687.5\Omega}$$

Voltage Gain of Stage 1(A_{V_1})

$$A_{V_1} = \frac{V_1}{V_{in}}$$

$$V_1 = -g_{m_1} V_{\pi_1} (R_{C_1} \parallel R_3 \parallel R_4 \parallel r_{\pi_2})$$

$$V_1 = -g_{m_1} V_{\pi_1} (R_{C_1} \parallel R_{th} \parallel r_{\pi_2})$$

$$V_{in} = V_{\pi_1}$$

$$A_{V_1} = \frac{V_1}{V_{in}} = -g_m (R_{C_1} \parallel R_{th} \parallel r_{\pi_2})$$

$$A_{V_1} = \frac{V_1}{V_{in}} = -111.15mA/V (2.2k \parallel 3.956k \parallel 1.8k)$$

$$A_{V_1} = \frac{V_1}{V_{in}} = -111.15mA/V (721.82)$$

$$A_{V_1} = \frac{V_1}{V_{in}} = -88.01$$

$$\mathbf{A_{V_1} = -88.01}$$

$$A_{V_{1S}} = \frac{V_1}{V_S} = \frac{V_1}{V_{in}} \times \frac{V_{in}}{V_S}$$

$$\frac{V_{in}}{V_S} = \frac{Z_i}{Z_i + R_{sig}} = \frac{1.237k}{1.237k + 0.5k} = 0.71215$$

$$A_{V_{1S}} = -88.01 \times 0.71215 = -62.676$$

$$\mathbf{A_{V_{1S}} = -62.676}$$

Voltage gain for Stage 2:-

$$A_{V_2} = \frac{V_{out}}{V_1}$$

$$V_o = -g_{m_2} V_{\pi_2} (R_{C_2} \parallel R_2)$$

$$V_1 = V_{\pi_2}$$

$$A_{V_2} = \frac{V_{out}}{V_1} = -111.15mA/V (2.2k \parallel 1k) = -26.415$$

$$\mathbf{A_{V_2} = -26.415}$$

Overall mid-band voltage gain = $A_{V1s} \times A_{V2} = -62.676 \times -76.415$

$A_V = 4789.43$

A_V in dB = $20 \log_{10}(4789.43) = 73.605 \text{ dB}$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

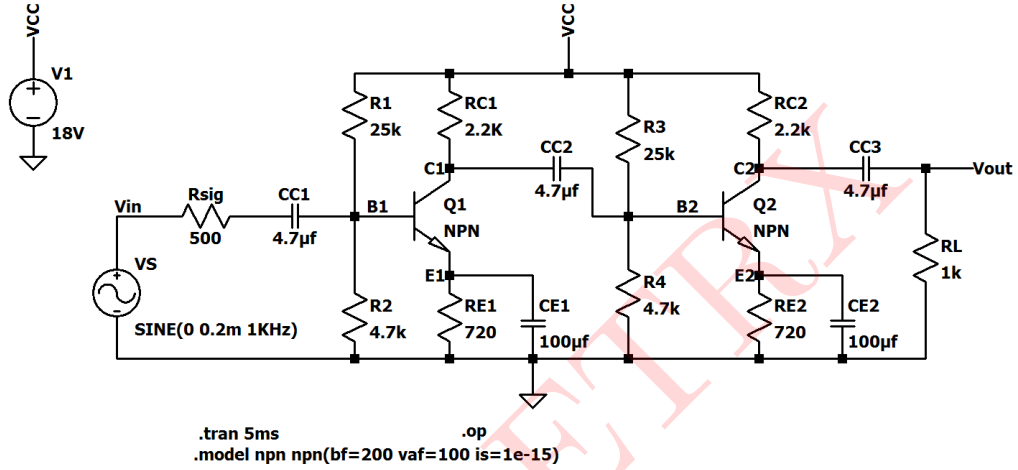


Figure 4: Circuit Schematic 1

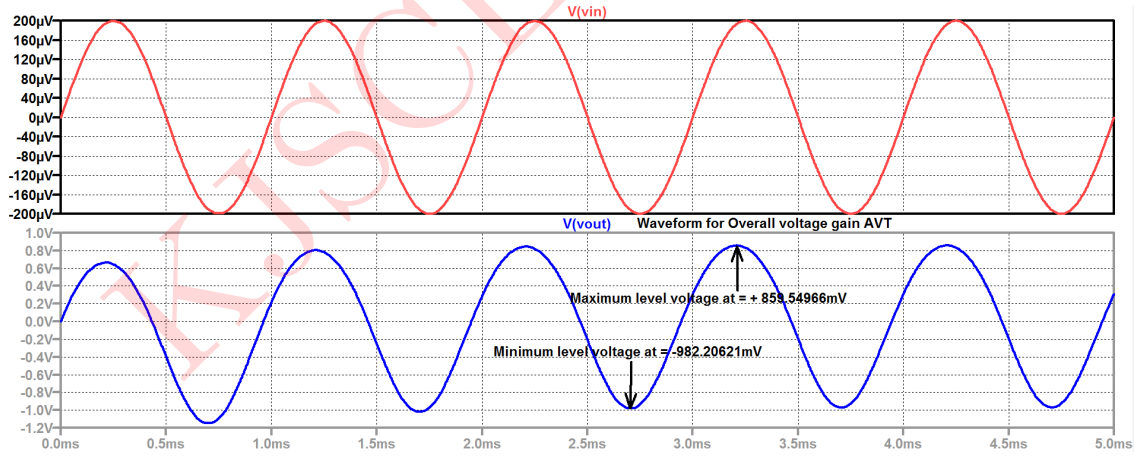


Figure 5: Input and Output waveform for overall voltage gain A_{VT}

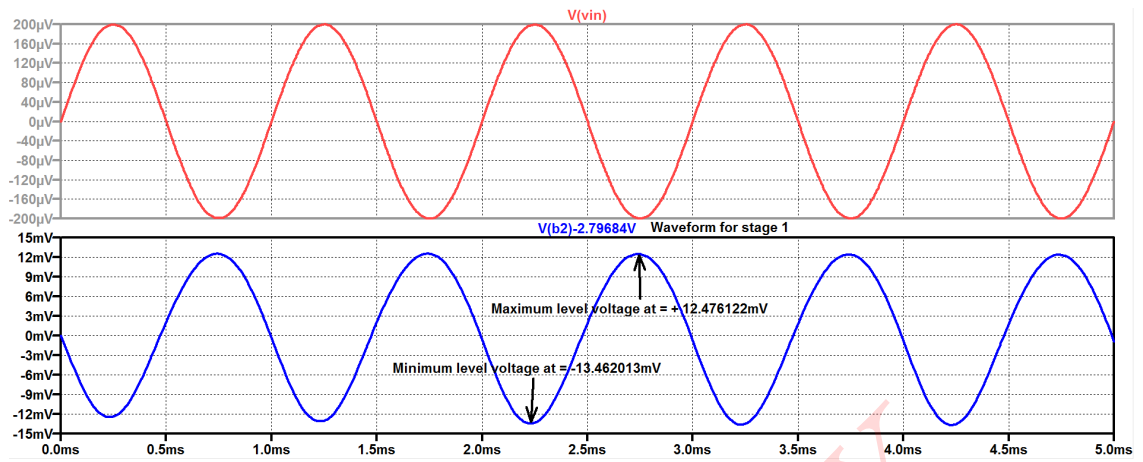


Figure 6: Input and Output waveform for stage 1

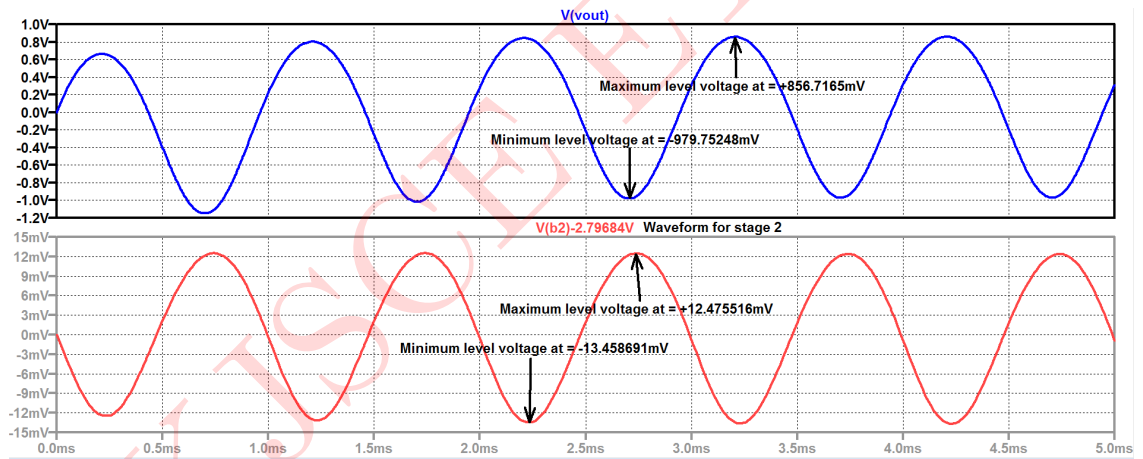


Figure 7: Input and Output waveform for stage 2

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
I_{C_1}, V_{CE_1}	$2.89mA, 9.549V$	$2.85mA, 9.685V$
I_{C_2}, V_{CE_2}	$2.89mA, 9.549V$	$2.85mA, 9.685V$
$A_{V_{1S}}$	-62.676	-63.84
A_{V_2}	-76.415	-73.435
A_{V_T}	$73.605dB$	$73.43dB$
Input Impedance Z_i	$1.237k\Omega$	—
Output Impedance Z_o	687.5Ω	—

Table 1: Numerical 1

Numerical 2:

For the circuit shown in figure 8, Determine I_D , I_C , V_{GS} , V_{CC} , A_{V_1} , A_{V_2} , A_{V_T} , Input impedance of 1st stage, Output impedance of 2nd stage

Given: $V_S = 2mV$, $I_{DSS} = 6mA$, $V_P = -3V$ and $\beta = 150$

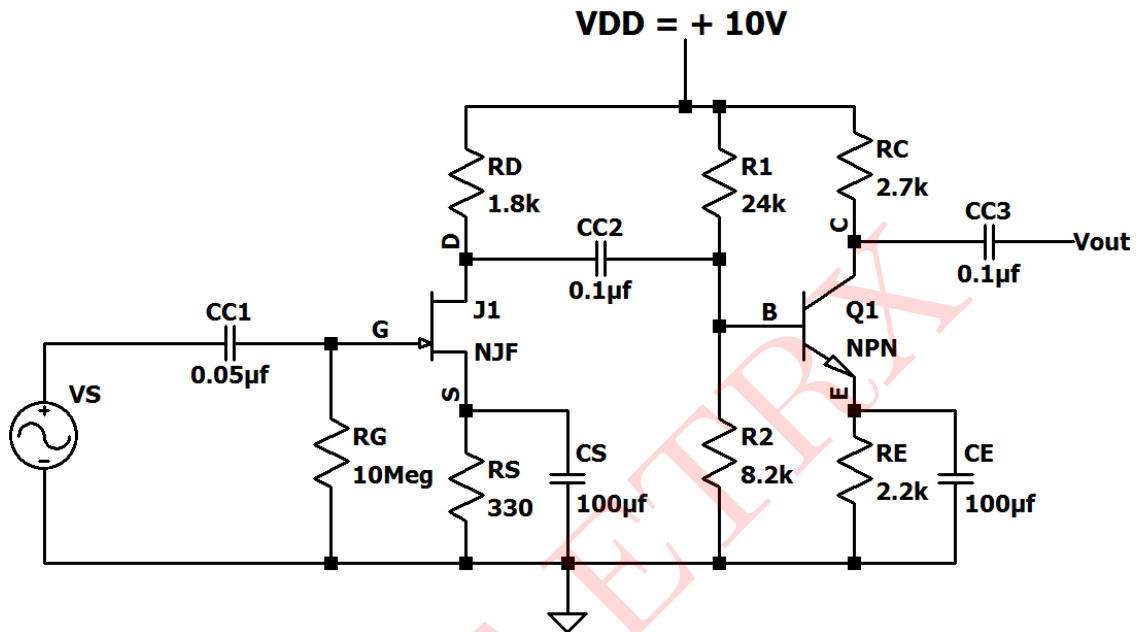


Figure 8: Circuit 1

Solution:

Above given circuit 2 is 2-stage RC coupled circuit, DC Analysis of both stages can be performed individually.

DC Analysis for 1st:-

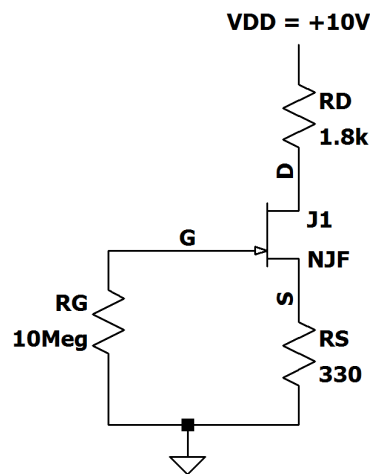


Figure 9: DC Equivalent circuit

Applying KVL to the Gate-Source loop:-

$$V_{GS} = -I_D R_S$$

$$V_{GS} = -I_D(330) \quad \text{.....(1)}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 6mA \left(1 + \frac{V_{GS}}{3}\right)^2 \quad \text{.....(2)}$$

Put (2) in (1)

$$V_{GS} = -330 \left(\frac{6}{1000} \left(1 + \frac{V_{GS}}{3}\right)^2 \right)$$

$$V_{GS} = -1.98 \left(1 + \frac{V_{GS}^2}{9} + \frac{2 \times V_{GS}}{3}\right)$$

$$V_{GS} = -1.98 - 0.22V_{GS}^2 - 1.32V_{GS}$$

$$0.22V_{GS}^2 + 2.32V_{GS} + 1.98 = 0$$

Solving above quadratic equation we get

$$V_{GS} = -0.936639V$$

or

$$V_{GS} = -9.608V, \text{ We reject this value, as } (V_{GS} > V_P)$$

$$\therefore V_{GS} = -0.936V$$

$$I_D = -\frac{V_{GS}}{R_S} = \frac{0.936V}{330\Omega} = 2.84mA$$

$$I_D = 2.84mA$$

Small-Signal parameters:-

$$g_{m1} = \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2 \times 6 \times 10^{-3}}{3} \left(1 - \frac{0.936}{3}\right) = 2.752 \text{ mA/V}$$

$$g_{m1} = 2.752 \text{ mA/V}$$

DC Analysis for 2nd stage:-

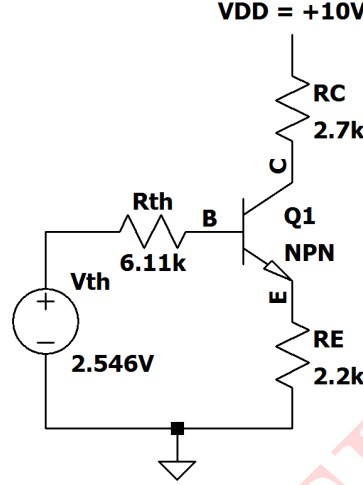


Figure 10: DC Equivalent circuit

$$V_B = V_{th} = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{8.2k\Omega}{2.4k\Omega + 8.2k\Omega} \times 10 = 2.546V$$

$$\mathbf{V_{th} = 2.546V}$$

$$R_{th} = R_1 \parallel R_2 = 2.4k \parallel 8.2k = 6.11k\Omega$$

$$\mathbf{R_{th} = 6.11k\Omega}$$

Applying KVL to the base-emitter loop:-

$$V_{th} - I_B R_{th} - V_{BE(ON)} - I_E R_E = 0$$

$$I_E = I_C + I_B = (\beta + 1)I_B$$

Assume $V_{BE(ON)} = 0.7V$

$$V_{th} - I_B R_{th} - 0.7V - (\beta + 1)I_B R_E = 0$$

$$I_B = \frac{V_{th} - 0.7V}{R_{th} + ((\beta + 1)R_E)} = \frac{2.546 - 0.7}{6.11k\Omega + (151 \times 2.2k\Omega)} = 5.456\mu A$$

$$\therefore \mathbf{I_B = 5.456\mu A}$$

$$I_C = \beta I_B = 150 \times 5.456\mu A = 0.818mA$$

$$\therefore \mathbf{I_C = 0.818mA}$$

Applying KVL to the collector-emitter loop:-

$$V_{CE} = V_{DD} - I_C R_C - (\beta + 1)I_B R_E$$

$$V_{CE} = 10 - (0.818mA \times 2.7k\Omega) - (151 \times 2.2k\Omega \times 5.456\mu A) = 5.9776V$$

$$\mathbf{V_{CE} = 5.9776V}$$

Small-Signal parameters:-

$$g_{m_2} = \frac{I_C}{V_T} = \frac{0.818mA}{26mV} = 31.47 \text{ mA/V}$$

$$g_{m_2} = 31.47 \text{ mA/V}$$

$$r_\pi = \frac{V_T}{I_B} = \frac{26mV}{5.456\mu A} = 4.765k\Omega$$

$$r_\pi = 4.765k\Omega$$

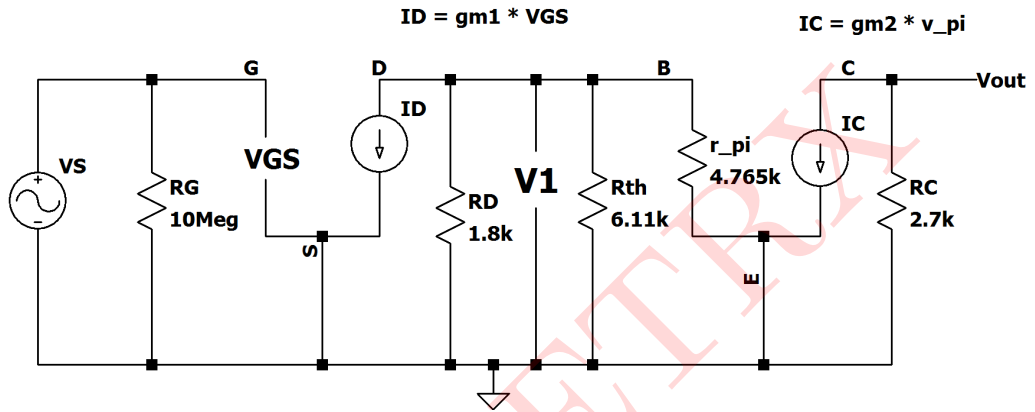


Figure 11: Small Signal Mid-Frequency Equivalent Circuit

Input Impedance:-

$$Z_i = R_G = 10M\Omega$$

$$Z_i = 10M\Omega$$

Output Impedance:-

$$Z_o = R_C = 2.7k\Omega$$

$$Z_o = 2.7k\Omega$$

Voltage Gain of Stage 1 (A_{V_1})

$$A_{V_1} = \frac{V_1}{V_{in}}$$

$$V_1 = -g_{m_1} V_{gs} (R_D \parallel R_{th} \parallel r_\pi)$$

$$V_{in} = V_{GS}$$

$$A_{V_1} = \frac{V_1}{V_{in}} = -g_m (R_D \parallel R_{th} \parallel r_\pi)$$

$$A_{V_1} = \frac{V_1}{V_{in}} = -2.752mA/V (1.8k \parallel 6.11k \parallel 4.765k)$$

$$A_{V_1} = \frac{V_1}{V_{in}} = -2.752mA/V (1.076k)$$

$$A_{V_1} = \frac{V_1}{V_{in}} = -2.96$$

$$A_{V_1} = -2.96$$

Voltage gain for Stage 2:-

$$A_{V_2} = \frac{V_{out}}{V_1}$$

$$V_o = -g_{m_2} V_\pi (R_C)$$

$$V_1 = V_\pi$$

$$A_{V_2} = \frac{V_{out}}{V_1} = -31.47 \times 10^{-3} \times 2.7 \times 10^3 = -84.969$$

$$A_{V_2} = -84.969$$

$$\text{Overall mid-band voltage gain} = A_{V_1} \times A_{V_2} = -2.96 \times -84.969 = 251.508$$

$$A_{V_T} = 251.508$$

$$A_{V_T} \text{ in dB} = 20 \log_{10}(251.508) = 48.01 \text{ dB}$$

$$A_{V_T} = \frac{V_{out}}{V_{in}}$$

$$\therefore V_{out} = A_{V_T} \times V_{in} = 251.508 \times 4 \times 10^{-3} = 1.006 \text{ V}$$

$$V_{out} = 1.006 \text{ V}$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

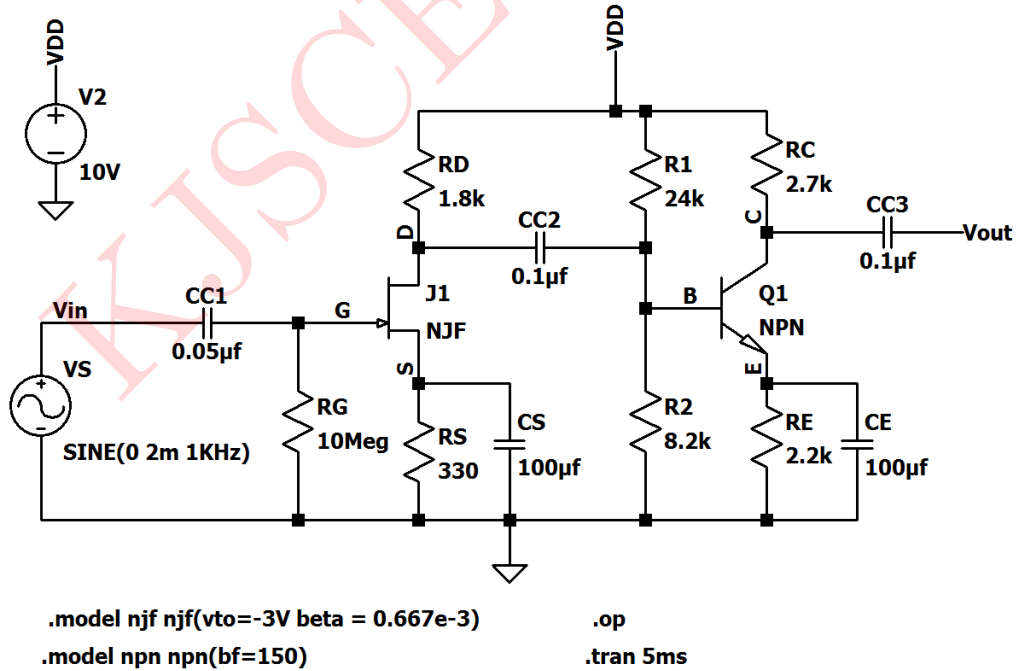


Figure 12: Circuit Schematic 2

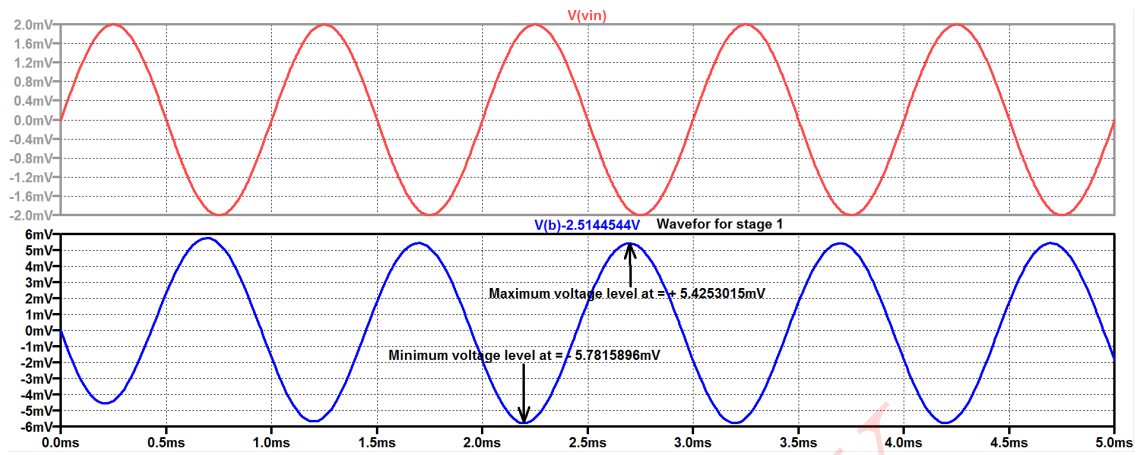


Figure 13: Input and Output waveform for stage 1

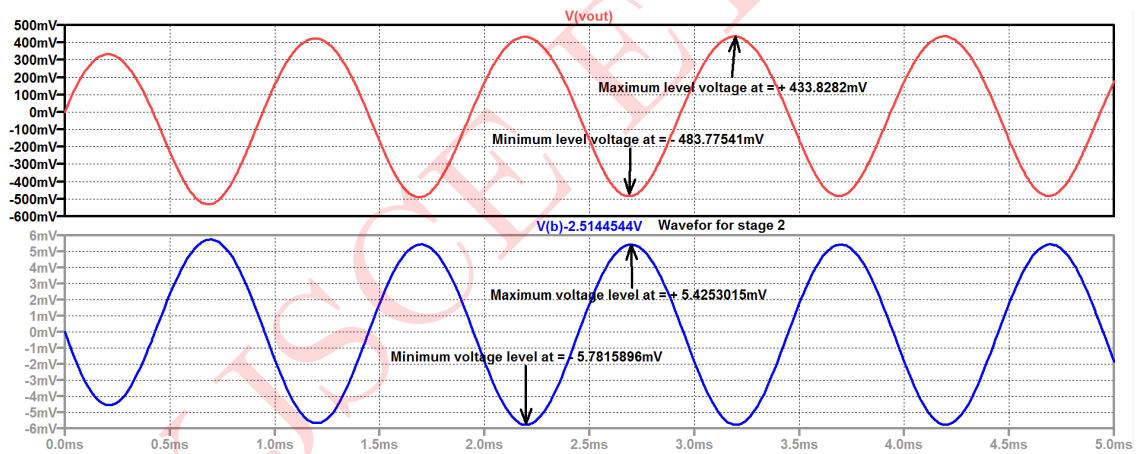


Figure 14: Input and Output waveform for stage 2

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
I_D, V_{GS}	$2.84mA, -0.936V$	$2.84mA, -0.936V$
I_C, V_{CE}	$0.818mA, 5.9778V$	$0.79mA, 6.12V$
A_{V_1}	-2.96	-2.801
A_{V_2}	-84.969	-81.88
A_{V_T}	$48.01dB$	$47.21dB$
Input Impedance Z_i	$10M\Omega$	—
Output Impedance Z_o	$2.7k\Omega$	—
V_{out}	$1.006V$	$0.92V$

Table 2: Numerical 2

Numerical 3:

For the circuit shown in figure 15, the BJT parameters are $\beta_1 = \beta_2 = 100$, $V_{BE_1} = V_{BE_2} = 0.7V$

- Determine all node voltage and terminal currents under DC analysis
- Determine overall voltage gain of the circuit

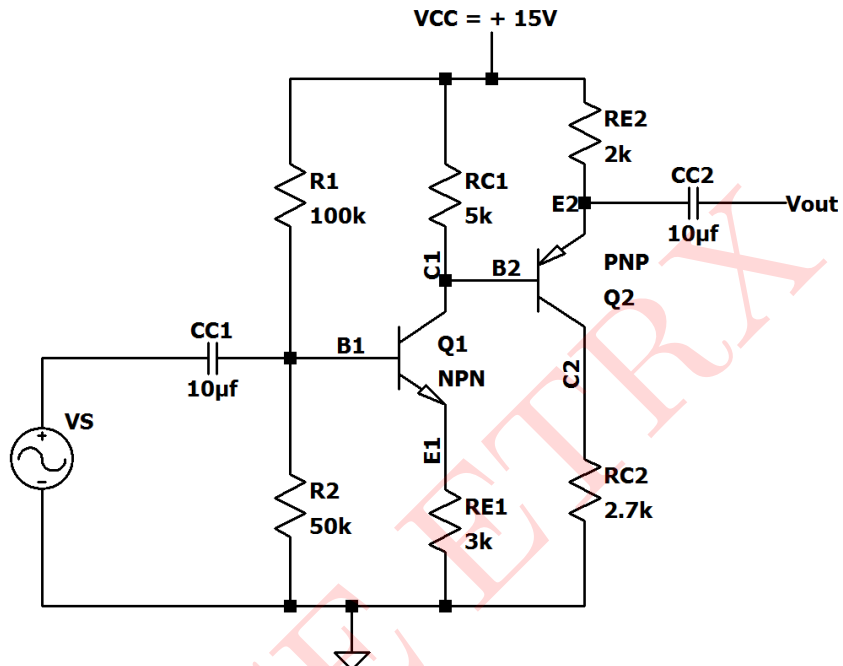


Figure 15: Circuit 3

Solution:

Above given circuit 3 is 2-stage RC coupled amplifier

∴ DC Analysis will be done for both the stages

DC Analysis:-

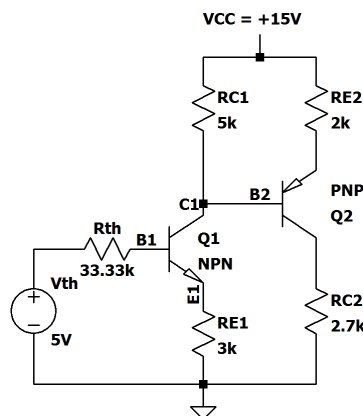


Figure 16: DC Equivalent circuit

$$V_B = V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{50k\Omega}{100k\Omega + 50k\Omega} \times 15 = 5V$$

$$\mathbf{V_{th} = 5V}$$

$$R_{th} = R_1 \parallel R_2 = 100k \parallel 50k = 33.33k\Omega$$

$$\mathbf{R_{th} = 33.33k\Omega}$$

Applying KVL to the base-emitter loop:-

$$V_{th} - I_{B_1} R_{th} - V_{BE(ON)} - I_{E_1} R_{E_1} = 0$$

$$I_{E_1} = I_{C_1} + I_{B_1} = (\beta_1 + 1)I_{B_1}$$

$$\text{Assume } V_{BE(ON)} = 0.7V$$

$$V_{th} - I_{B_1} R_{th} - 0.7V - (\beta + 1)I_{B_1} R_{E_1} = 0$$

$$I_{B_1} = \frac{V_{th} - 0.7V}{R_{th} + ((\beta + 1)R_{E_1})} = \frac{5 - 0.7}{33.33k\Omega + (101 \times 3k\Omega)} = 12.785\mu A$$

$$\therefore \mathbf{I_{B_1} = 12.785\mu A}$$

$$I_{C_1} = \beta_1 I_{B_1} = 100 \times 12.785\mu A = 1.2785mA$$

$$\therefore \mathbf{I_{C_1} = 1.2785mA}$$

$$I_{E_1} = I_{C_1} + I_{B_1} = 1.2785mA + 12.785\mu A = 1.291mA$$

$$\therefore \mathbf{I_{E_1} = 1.291mA}$$

$$V_{C_1} = V_{CC} - I_{C_1} R_{C_1} \quad [\text{Ignoring } I_{B_2} \text{ and } I_{R_{C_1}} \approx I_{C_1}]$$

.....(1)

$$V_{C_1} = 15 - 1.2785mA \times 5k\Omega = 8.607V$$

$$\mathbf{V_{C_1} = 8.607V}$$

$$V_{E_2} = V_{B_2} + V_{EB_2(on)} = V_{C_1} + V_{EB_2(on)}$$

$$V_{E_2} = 8.607 + 0.7 = 9.307V$$

$$\mathbf{V_{E_2} = 9.307V}$$

From the circuit:-

$$V_{CC} - I_{E_2} R_{E_2} - V_{E_2} = 0$$

$$I_{E_2} = \frac{V_{CC} - V_{E_2}}{R_{E_2}} = \frac{15 - 9.037}{2k\Omega} = 2.8465mA$$

$$\mathbf{I_{E_2} = 2.8465mA}$$

$$I_{C_2} = \frac{\beta_2}{1 + \beta_2} \times I_{E_2} = \frac{100}{101} \times 2.8465mA = 2.818mA$$

$$\mathbf{I_{C_2} = 2.818mA}$$

$$I_{B_2} = \frac{I_{E_2}}{1 + \beta_2} = \frac{2.8465mA}{101} = 281.8\mu A$$

$$\mathbf{I_{B_2} = 28.18\mu A}$$

Rewriting expression for equation (1):-

$$V_{C_1} = V_{CC} - I_{RC_1} R_{C_1}$$

$$I_{RC_1} = I_{C_1} - I_{B_2} = 1.2785mA - 28.18\mu A = 1.25mA$$

$$V_{C1_{new}} = 15.1.25mA \times 5k\Omega = 8.75V$$

$$V_{E2_{new}} = V_{C1_{new}} + V_{EB_2} = 8.75 + 0.7 = 9.45V$$

$$I_{E2_{new}} = \frac{V_{CC} - V_{E2_{new}}}{R_{E_2}} = \frac{15 - 9.45}{2k\Omega} = 2.775mA$$

$$I_{C2_{new}} = \frac{\beta_2}{1 + \beta_2} \times I_{E2_{new}} = \frac{100}{101} \times 2.775mA = 2.743mA$$

$$I_{B2_{new}} = \frac{I_{E2_{new}}}{1 + \beta_2} = \frac{2.775mA}{101} = 27.47\mu A$$

$$V_{E_1} = I_{E_1} R_{E_1} = 1291mA \times 3k = 3.873V$$

$$V_{C_2} = I_{C_2} R_{C_2} = 2.743 \times 2.7k\Omega = 7.406V$$

$$V_{B_1} = V_{BE_1}(on) + V_{E_1} = 4.573V$$

Node Voltages:-

$$V_{B_1} = 4.573V, V_{C_1} = 8.75V, V_{E_1} = 3.873V$$

$$V_{C_2} = 7.406V, V_{E_2} = 9.45V, V_{B_2} = V_{C_1} = 8.75V$$

Terminal Currents:-

$$I_{B_1} = 12.785\mu A, I_{C_1} = 1.2785mA, I_{E_1} = 1.291mA$$

$$I_{B_2} = 27.47\mu A, I_{C_2} = 2.743mA, I_{E_2} = 2.775mA$$

Small-Signal parameters:-

$$g_{m_1} = \frac{I_{C_1}}{V_T} = \frac{1.2785mA}{26mV} = 491.73 \text{ mA/V}$$

$$\mathbf{g_{m_1} = 491.73 \text{ mA/V}}$$

$$r_{\pi_1} = \frac{V_T}{I_{B_1}} = \frac{26mV}{12.785\mu A} = 2.033k\Omega$$

$$\mathbf{r_{\pi_1} = 2.033k\Omega}$$

$$g_{m_2} = \frac{I_{C_2}}{V_T} = \frac{2.743mA}{26mV} = 105.5 \text{ mA/V}$$

$$\mathbf{g_{m_2} = 105.5 \text{ mA/V}}$$

$$r_{\pi_2} = \frac{V_T}{I_{B_2}} = \frac{26mV}{27.43\mu A} = 947.867\Omega$$

$$\mathbf{r_{\pi_2} = 947.687\Omega}$$

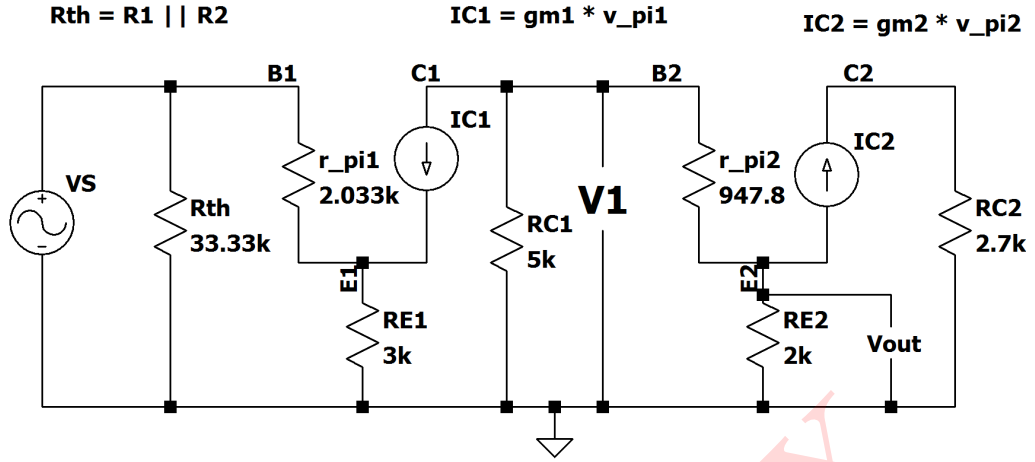


Figure 17: Small Signal Equivalent Circuit

Voltage Gain of Stage 1 (A_{V_1})

$$A_{V_1} = \frac{V_1}{V_S}$$

$$V_1 = -g_{m1} V_{\pi_1} (R_{C1}) = -(\beta_1 i_{b1}) R_{C1}$$

$$V_S = i_{b1} [r_{\pi_1} + (1 + \beta_1) R_{E1}]$$

$$A_{V_1} = \frac{V_1}{V_S} = \frac{-(\beta_1 i_{b1}) R_{C1}}{i_{b1} [r_{\pi_1} + (1 + \beta_1) R_{E1}]} = \frac{-100 \times 5k}{[2.033k\Omega + (101 \times 3k\Omega)]} = -1.639$$

$$\mathbf{A_{V_1} = -1.639}$$

Voltage Gain of Stage 2 (A_{V_2})

$$A_{V_2} = \frac{V_{out}}{V_1}$$

$$V_{out} = -g_{m2} V_{\pi_2} (R_{E2}) = -(\beta_2 i_{b2}) R_{E2}$$

$$V_1 = i_{b2} [r_{\pi_2} + (1 + \beta_2) R_{E2}]$$

$$A_{V_2} = \frac{V_{out}}{V_1} = \frac{(\beta_2 i_{b2}) R_{C2}}{i_{b2} [r_{\pi_2} + (1 + \beta_2) R_{E2}]} = \frac{100 \times 2k}{[947.867\Omega + (101 \times 2k\Omega)]} = 0.985$$

$$\mathbf{A_{V_2} = 0.985}$$

Overall mid-band voltage gain = $A_{V_1} \times A_{V_2} = -1.639 \times 0.985$

$$\mathbf{A_{V_T} = -1.614}$$

Output voltage:-

$$A_{V_T} = \frac{V_{out}}{V_S}$$

$$V_{out} = A_{V_T} \times V_S = -1.614 \times 40mV = -64.56mV$$

$$\mathbf{V_{out} = -64.56mV}$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

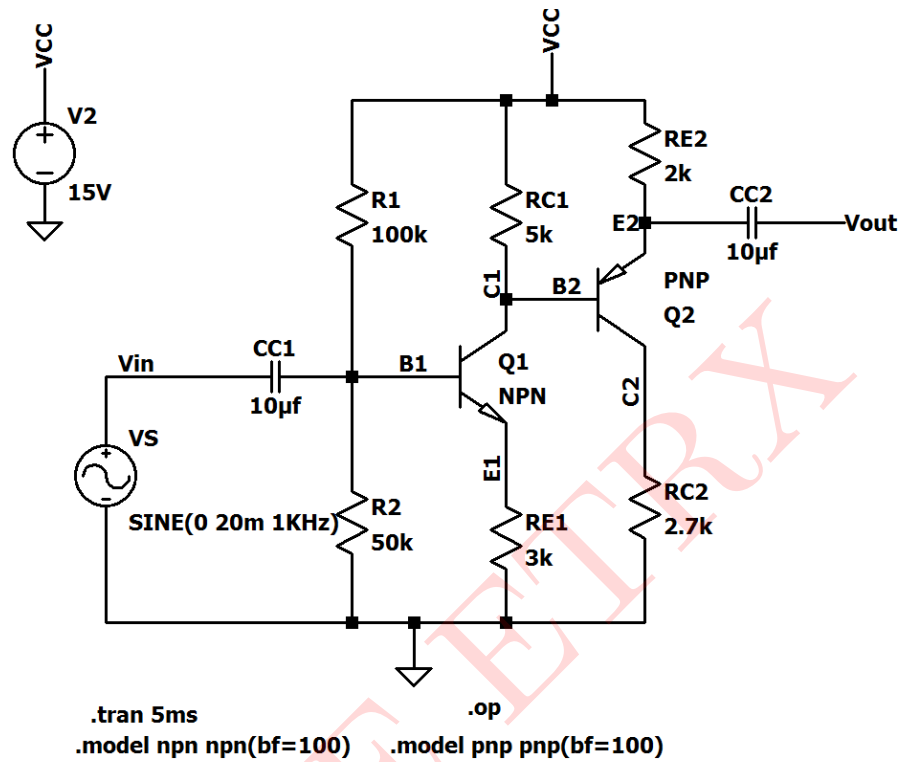


Figure 18: Circuit Schematic 3

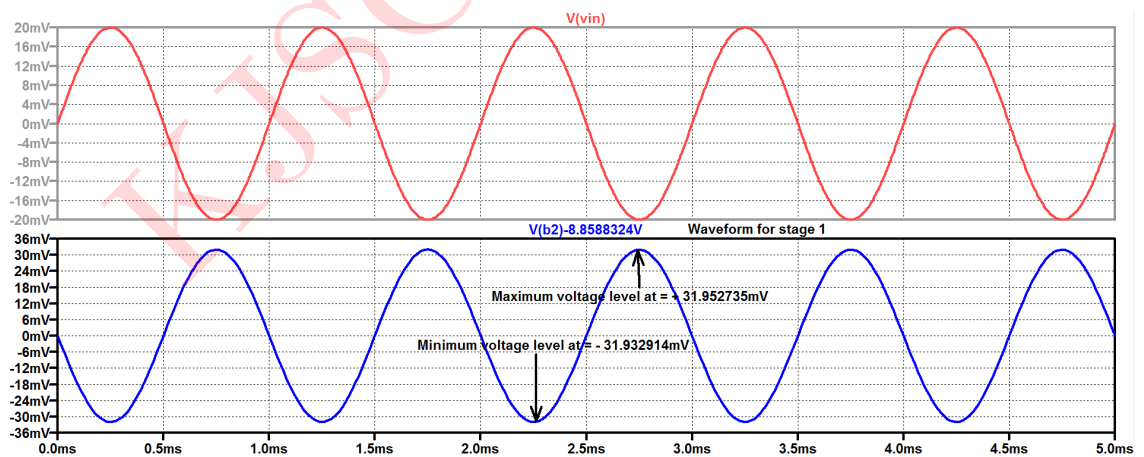


Figure 19: Input and Output waveform for stage 1

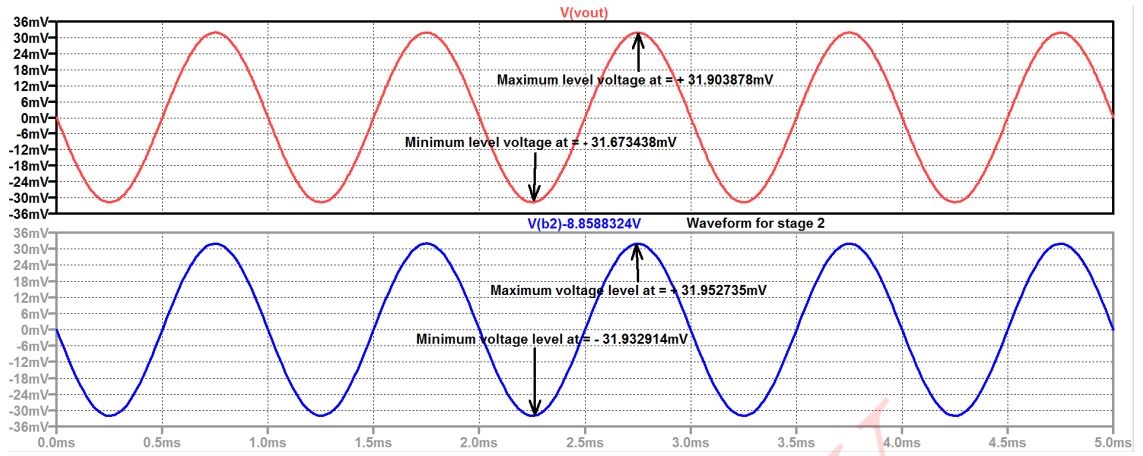


Figure 20: Input and Output waveform for stage 2

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
I_{C1}, I_{B1}, I_{E1}	$12.78\mu A, 1.2785mA, 1.29mA$	$12.55\mu A, 1.25mA, 1.273mA$
I_{C2}, I_{B2}, I_{E2}	$27.74\mu A, 2.47mA, 2.77mA$	$26.45\mu A, 2.65mA, 2.67mA$
V_{C1}, V_{C2}	$8.75V, 7.406V$	$8.85V, 7.21V$
V_{E1}, V_{E2}	$3.873V, 9.45V$	$3.82V, 9.65V$
V_{B1}, V_{B2}	$4.573V, 8.75V$	$4.581V, 8.85V$
A_{VT}	-1.614	-1.59
V_{out}	$-64.56mV$	$-63.57mV$

Table 3: Numerical 3
