

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Cascode Amplifier

Numerical 1:

For the circuit shown in figure 1, the BJT parameters are $\beta_1 = \beta_2 = 120$, $V_{BE_1} = V_{BE_2} = 0.7V$

- Calculate DC parameters of the circuit.
- Calculate input and output impedance of the circuit.
- Calculate overall voltage gain for the circuit.

Given:- $V_S = 20mV$

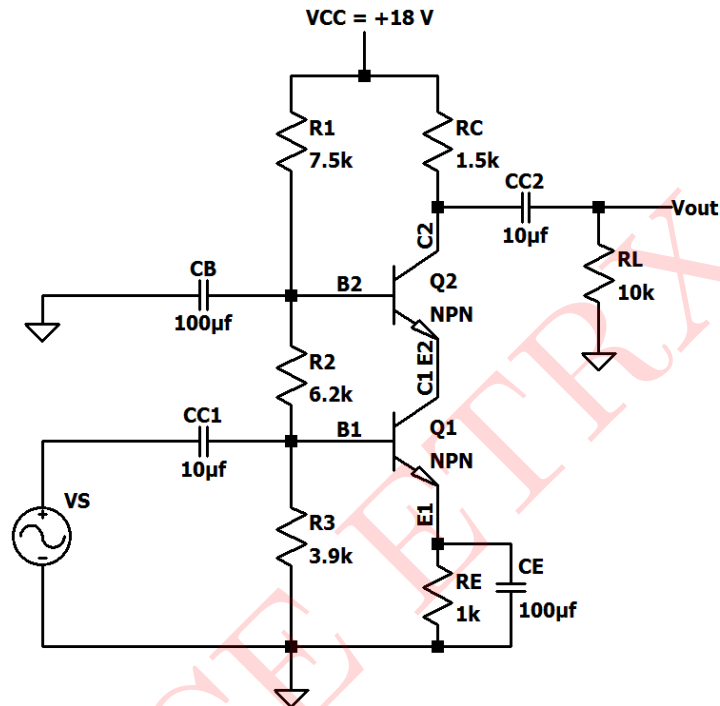


Figure 1: Circuit 1

Solution:

DC Analysis:-

$$I_{C_1} = I_{C_2} = I_{E_1} = I_{E_2}$$

$$V_{B_1} = \frac{R_3}{R_1 + R_2 + R_3} \times V_{CC} = \frac{3.9k\Omega}{3.9k\Omega + 6.2k\Omega + 7.5k\Omega} \times 18 = 3.988V$$

$$V_{B_1} = 3.988V$$

$$V_{B_2} = \frac{R_3 + R_2}{R_1 + R_2 + R_3} \times V_{CC} = \frac{3.9k\Omega + 6.2k\Omega}{3.9k\Omega + 6.2k\Omega + 7.5k\Omega} \times 18 = 10.33V$$

$$V_{B_2} = 10.33V$$

$$V_{BE_1} = V_{B_1} - V_{E_1}$$

$$V_{E_1} = V_{B_1} - V_{BE_1} = 3.99V - 0.7V = 3.29V$$

$$V_{E_1} = 3.29V$$

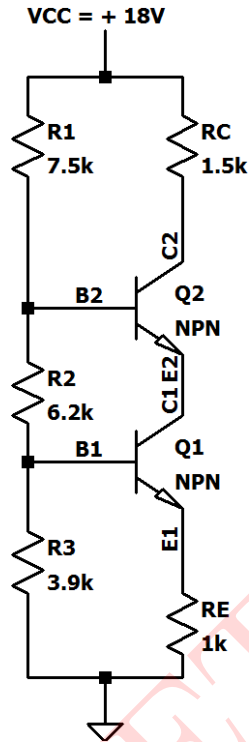


Figure 2: DC Equivalent circuit

$$V_{E1} = I_{E1} R_E$$

$$I_{E1} = \frac{V_{E1}}{R_E} = \frac{3.29}{1k\Omega} = 3.29mA$$

$$I_{E1} = 3.29mA$$

$$I_{C1} = I_{C2} = I_{E1} = I_{E2} = 3.29mA$$

$$V_{C2} = V_{CC} - I_{C2} R_C = 18 - (3.29 \times 1.5) = 13.07V$$

$$V_{C2} = 13.07V$$

$$V_{E2} = V_{B2} - V_{BE2} = 10.33 - 0.7V = 9.63V$$

$$V_{E2} = V_{C1} = 9.63V$$

$$I_{B1} = \frac{I_{C1}}{\beta_1} = \frac{3.29mA}{120} = 27.42\mu A$$

$$I_{B2} = \frac{I_{C2}}{\beta_2} = \frac{3.29mA}{120} = 27.42\mu A$$

$$I_{B1} = I_{B2} = 27.42\mu A$$

Small-Signal parameters:-

$$g_m = \frac{I_C}{V_T} = \frac{3.29mA}{26mV} = 126.54 \text{ mA/V}$$

$$g_{m1} = g_{m2} = 126.54 \text{ mA/V}$$

$$r_\pi = \frac{V_T}{I_B} = \frac{26mV}{27.42\mu A} = 948.33\Omega$$

$$r_{\pi1} = r_{\pi2} = 948.33\Omega$$

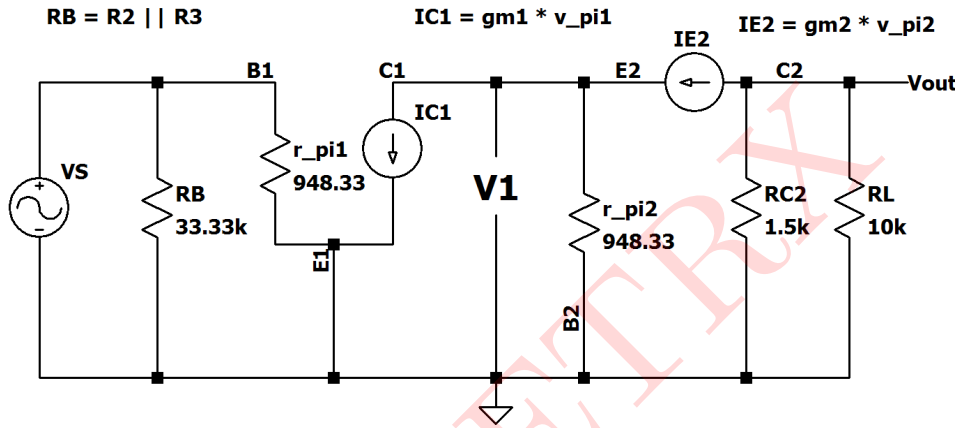


Figure 3: Small Signal Equivalent Circuit

Input Impedance

$$Z_i = R_2 \parallel R_3 \parallel r_{\pi1} = 3.9k \parallel 6.2k \parallel 948.33 = 910.915\Omega$$

$$Z_i = 910.915\Omega$$

$$Z_i = R_C \parallel R_L = 1.5k \parallel 10k = 1.3k\Omega$$

$$Z_o = 1.3k\Omega$$

Voltage Gain of Stage 1(A_{V1}):-

$$A_{V1} = \frac{V_1}{V_{in}}$$

$$V_1 = -g_{m1} V_{\pi1} \left(\frac{r_{\pi2}}{1 + \beta_2} \right)$$

$$V_{in} = V_{\pi1}$$

$$A_{V1} = \frac{V_1}{V_{in}} = -g_{m1} \left(\frac{r_{\pi2}}{1 + \beta_2} \right) = -126.54 \left(\frac{948.33}{121} \right) = -0.99175$$

$$A_{V1} = -0.99175$$

Voltage Gain of Stage 2(A_{V_2}):-

$$A_{V_2} = \frac{V_{out}}{V_1} = \frac{-g_{m_2} V_{\pi_2} (R_C \parallel R_L)}{-V_{\pi_2}} = g_{\pi_2} (R_C \parallel R_L)$$

$$A_{V_2} = 126.54(1.5k\Omega \parallel 10k\Omega) = 126.54mA/V \times 1300 = 164.5$$

$$\mathbf{A_{V_2} = 164.5}$$

$$\text{Overall mid-band voltage gain} = A_{V_1} \times A_{V_2} = 164.5 \times -0.99175 = -163.14$$

$$\mathbf{A_{V_T} = -163.14}$$

$$\mathbf{A_{V_T} \text{ in dB} = 20\log_{10}(163.14) = 44.25dB}$$

Output voltage:-

$$V_{out} = A_{V_T} \times V_S = -163.14 \times 40mV = -6.52V$$

$$\mathbf{V_{out} = -6.52V}$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

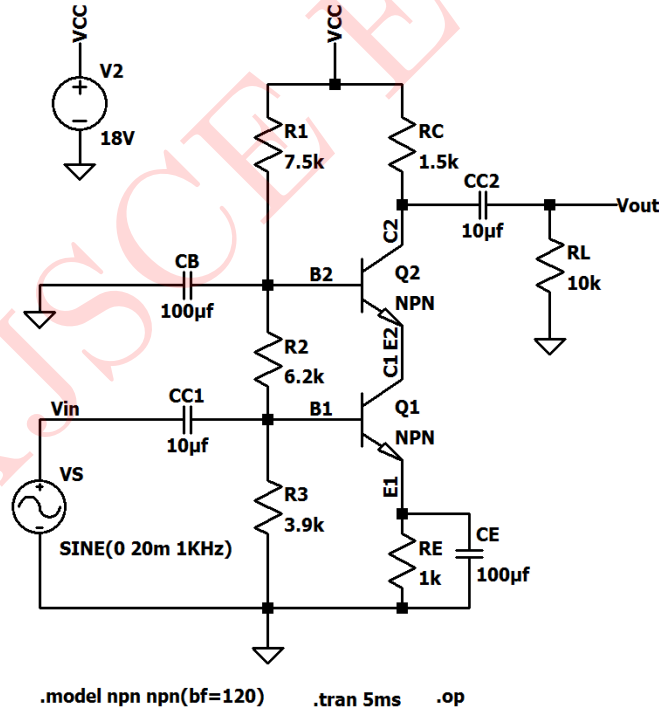


Figure 4: Circuit Schematic 1

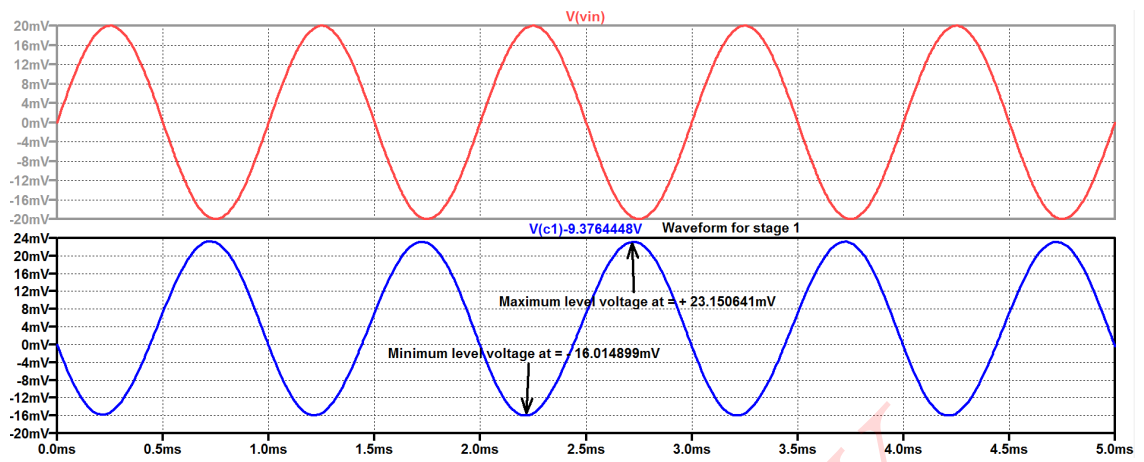


Figure 5: Input and Output waveform for stage 1

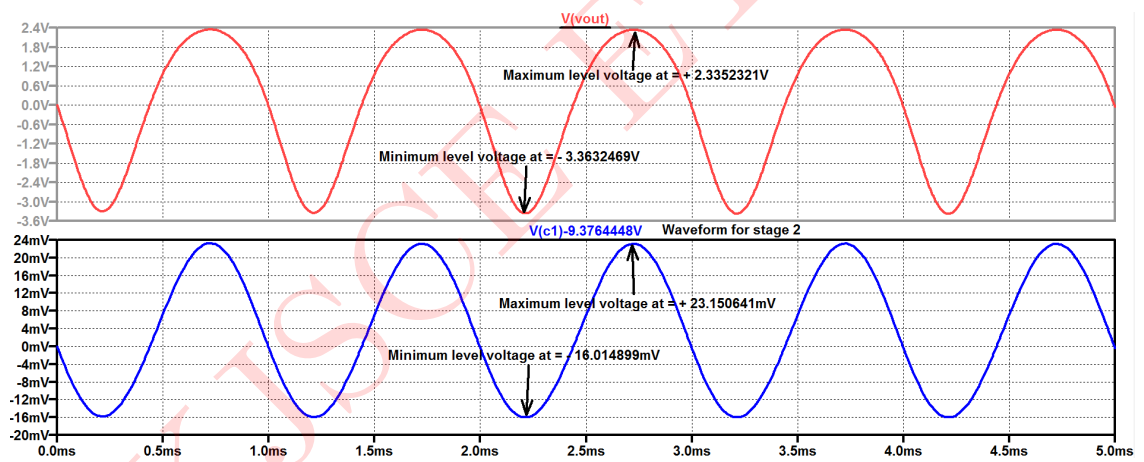


Figure 6: Input and Output waveform for stage 2

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
I_{B_1}, I_{B_2}	$27.42\mu A, 27.42\mu A$	$27.34\mu A, 27.14\mu A$
I_{C_1}, I_{C_2}	$3.29mA, 3.29mA$	$3.04mA, 3.02mA$
I_{E_1}, I_{E_2}	$3.29mA, 7.406V$	$3.07mA, 3.04mA$
V_{C_1}, V_{C_2}	$9.63V, 13.07V$	$9.38V, 13.47V$
V_{B_1}, V_{B_2}	$3.99V, 10.33V$	$3.87V, 10.18V$
V_{E_1}, V_{E_2}	$3.29V, 9.63V$	$3.07V, 9.38V$
A_{V_1}	-0.99175	-0.979
A_{V_2}	164.5	148.63
$A_{V_T}(dB)$	$44.25dB$	$43.26dB$
V_{out}	$-6.52V$	$-5.72V$
Z_i, Z_o	$910\Omega, 1.3k\Omega$	$-$

Table 1: Numerical 1

Numerical 2:

For the circuit shown in figure 7, the E-MOSFET parameters are $k_{n1} = k_{n2} = 0.8mA/V^2$, $V_{TN1} = V_{TN2} = 0.8V$

- Calculate DC parameters of the circuit.
- Calculate input and output impedance of the circuit.
- Calculate overall voltage gain for the circuit.

Given:- $V_S = 20mV$

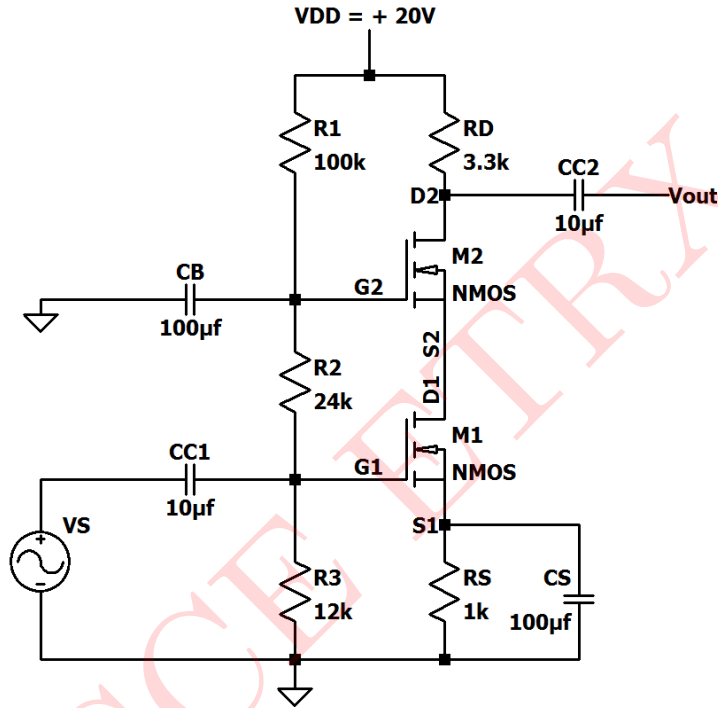


Figure 7: Circuit 2

Solution:

DC Analysis:-

$$R_T = R_1 + R_2 + R_3 = 136K\Omega$$

$$V_{G1} = \left(\frac{R_3}{R_1 + R_2 + R_3} \right) \times V_{DD} = \left(\frac{12k}{136k} \right) 20 = 1.765V$$

$$V_{G1} = 1.765V$$

$$V_{G2} = \left(\frac{R_3 + R_2}{R_1 + R_2 + R_3} \right) \times V_{DD} = \left(\frac{12k + 24k}{136k} \right) 20 = 5.294V$$

$$V_{G2} = 5.294V$$

$$V_{GS1} = V_{G1} - V_{S1}$$

$$V_{GS1} = 1.765 - I_{D1}R_S = 1.765 - 1000I_{D1} \quad \text{.....(1)}$$

For E-MOSFET, drain current is given by:-

$$I_{D1} = k_{n1}(V_{GS1} - V_{TN1})^2$$

$$I_{D1} = 0.8 \times 10^{-3}(V_{GS1} - 0.8)^2 \quad \text{.....(2)}$$

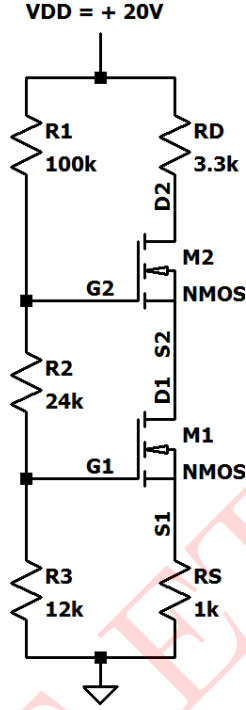


Figure 8: DC Equivalent circuit

Put (2) in (1), we get

$$V_{GS_1} = 1.765 - 0.8 \times 10^{-3} \times 10^3 (V_{GS_1} - 0.8)^2$$

$$V_{GS_1} = 1.765 - 0.8(V_{GS_1}^2 + 0.64 - 1.6V_{GS_1})$$

$$V_{GS_1} = 1.765 - 0.8V_{GS_1}^2 - 0.512 + 1.28V_{GS_1}$$

$$0.8V_{GS_1}^2 - 0.28V_{GS_1} - 1.2527 = 0$$

Solving above quadratic equation we get

$$V_{GS_1} = 1.4385V$$

or

$$V_{GS_1} = -1.0885V, \text{ We reject this value, as } (V_{GS_1} > V_{TN_1})$$

$$\therefore V_{GS_1} = 1.4385V$$

$$I_{D1} = k_{n1}(V_{GS1} - V_{TN1})^2$$

$$I_{D1} = 0.8 \times 10^{-3}(1.4385 - 0.8)^2 = 0.326mA$$

$$I_{D1} = I_{D2} = \mathbf{0.326mA}$$

$$V_{D2} = V_{DD} - I_{D2}R_D = 20 - (0.326 \times 3.3) = 18.923V$$

$$V_{D2} = \mathbf{18.923V}$$

$$V_{S1} = I_{D1}R_S = 0.326 \times 1 = 0.326V$$

$$V_{S1} = \mathbf{0.326V}$$

$$V_{GS1} = V_{GS2} = V_{G2} - V_{S2} = 1.4385V$$

$$V_{GS1} = V_{GS2} = \mathbf{1.4385V}$$

$$V_{S2} = V_{G2} - 1.4385 = 5.294 - 1.4385 = 3.855V$$

$$V_{S2} = V_{D1} = \mathbf{3.855V}$$

$$V_{DS2} = V_{D2} - V_{S2} = 18.923 - 3.855 = 15.068V$$

$$V_{DS2} = \mathbf{15.068V}$$

$$V_{DS1} = V_{D1} - V_{S1} = 3.855 - 0.326 = 3.529V$$

$$V_{DS1} = \mathbf{3.529V}$$

Small-Signal parameters:-

$$g_{m1} = g_{m2} = 2k_n(V_{GS} - V_{TN})$$

$$g_{m1} = g_{m2} = 2 \times 0.8 \times 10^{-3}(1.4385 - 0.8) = 1.022mA/V$$

$$g_{m1} = g_{m2} = \mathbf{1.022 mA/V}$$

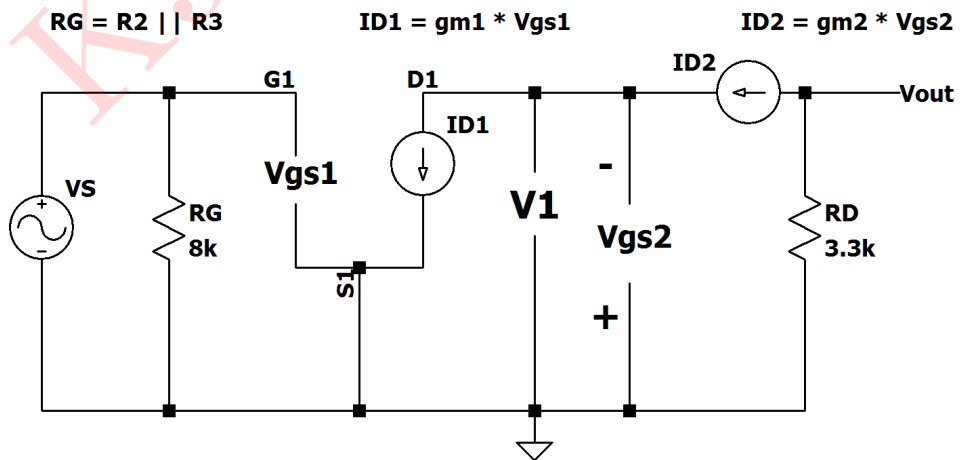


Figure 9: Small Signal Equivalent Circuit

Input and Output Impedance

$$Z_i = R_G = R_3 \parallel R_2 = 8k\Omega$$

$$\mathbf{Z_i = 8k\Omega}$$

$$Z_o = R_D = 3.3k\Omega$$

$$\mathbf{Z_o = 3.3k\Omega}$$

Voltage Gain of Stage 1(A_{V_1}):-

$$A_{V_1} = \frac{V_1}{V_S} = \frac{-V_{gs_2}}{V_{gs_1}} = -1$$

$$\mathbf{A_{V_1} = -1}$$

Voltage Gain of Stage 2(A_{V_2}):-

$$A_{V_2} = \frac{V_{out}}{V_1} = \frac{-g_{m_2} V_{gs_2} (R_D)}{-V_{gs_2}} = g_{m_2} (R_D)$$

$$A_{V_2} = 1.022 \times 10^{-3} \times 3.3 \times 10^3 = 3.373$$

$$\mathbf{A_{V_2} = 3.373}$$

$$\text{Overall mid-band voltage gain} = A_{V_1} \times A_{V_2} = -1 \times 3.373 = -3.373$$

$$\mathbf{A_{V_T} = -3.373}$$

$$\mathbf{A_{V_T} \text{ in dB} = 20 \log_{10}(3.373) = 10.56 \text{ dB}}$$

Output voltage:-

$$V_{out} = A_{V_T} \times V_S = -3.373 \times 40 \text{ mV} = -134.92 \text{ mV}$$

$$\mathbf{V_{out} = -134.92 \text{ mV}}$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

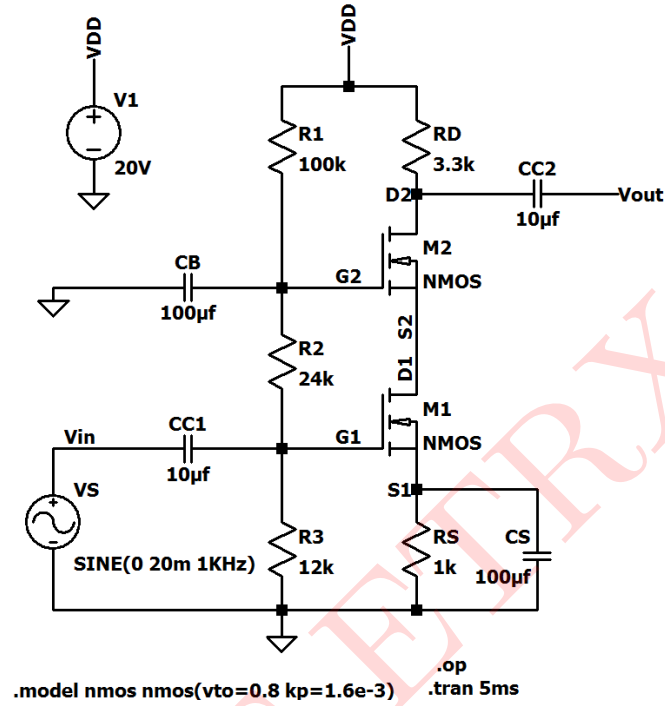


Figure 10: Circuit Schematic 2

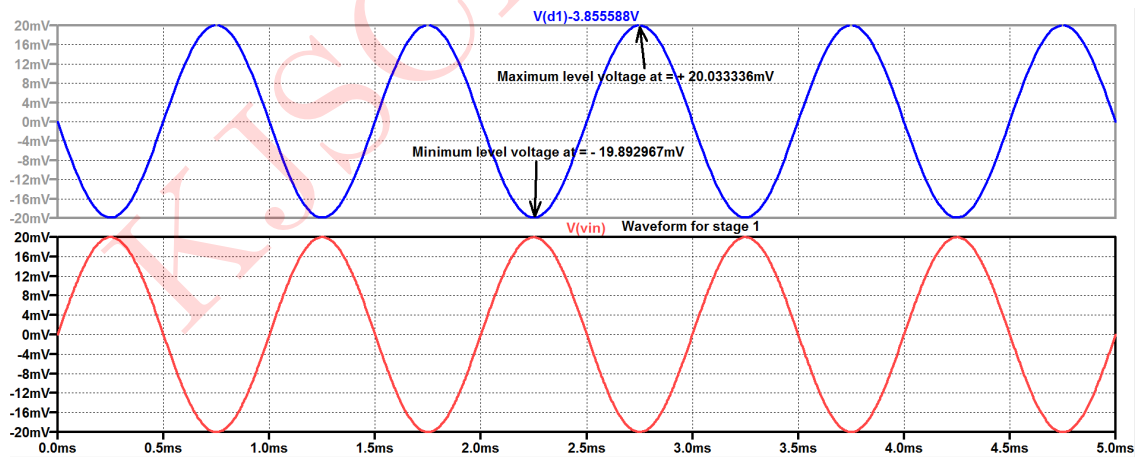


Figure 11: Input and Output waveform for stage 1

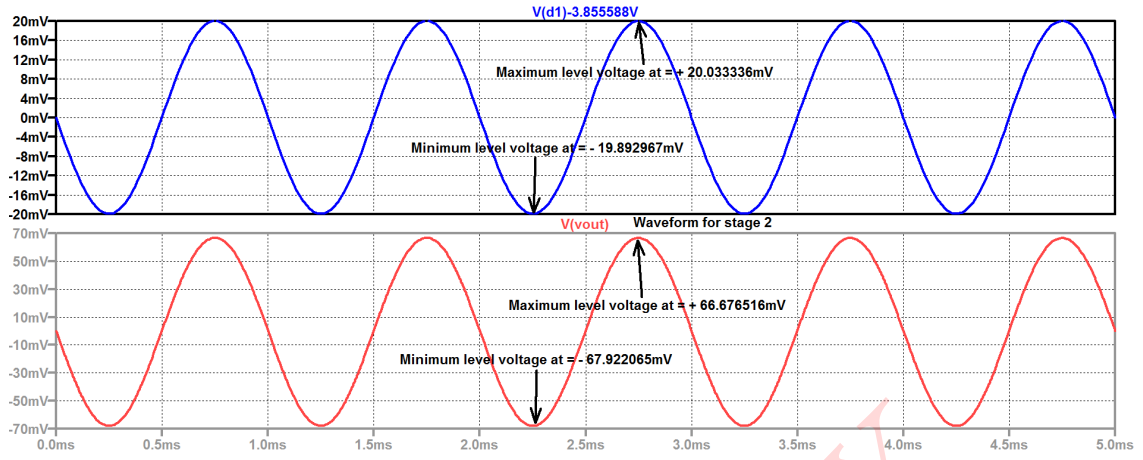


Figure 12: Input and Output waveform for stage 2

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
I_{D1}, I_{D2}	$0.326\text{mA}, 0.326\text{mA}$	$0.326\text{mA}, 0.326\text{mA}$
V_{G1}, V_{G2}	$1.765\text{V}, 5.294\text{V}$	$1.765\text{V}, 5.294\text{V}$
V_{S1}, V_{S2}	$0.326\text{V}, 3.855\text{V}$	$0.326\text{V}, 3.855\text{V}$
V_{D1}, V_{D2}	$3.855\text{V}, 18.923\text{V}$	$3.855\text{V}, 18.923\text{V}$
A_{V1}	-1	-0.998
A_{V2}	3.373	3.371
$A_{VT}(\text{dB})$	10.56	10.54
V_{out}	-134.92mV	-134.59mV
Z_i, Z_o	$8\text{k}\Omega, 3.3\text{k}\Omega$	—

Table 2: Numerical 2
