

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Darlington Amplifier

Numerical 1:

A two stage circuit is shown in figure 1. Calculate the Q point, input impedance, output impedance, overall voltage gain and overall current gain. Given $\beta_D = 8000$, $V_{BE} = 1.6V$

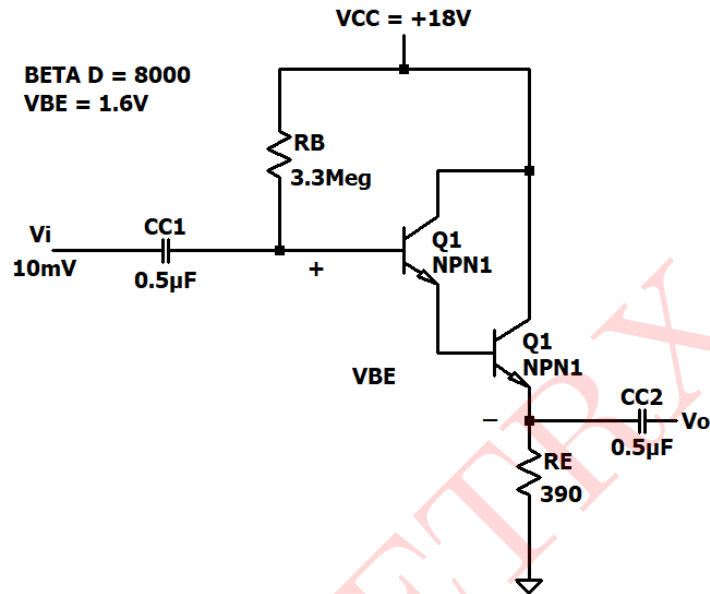


Figure 1: Circuit 1

Solution:

DC Analysis:

For DC Analysis, we open circuit all the capacitors as the frequency is $0Hz$,

 


Figure 2: DC Equivalent Circuit

$$B_D = \beta_1 \beta_2$$

Considering $\beta_1 = \beta_2$

$$\therefore \beta_D = \beta^2$$

[where $\beta = \beta_1 = \beta_2$]

$$\beta = 89.44 = \beta_1 = \beta_2$$

Applying KVL to Base Emitter loop,

$$V_{CC} - I_{B_1 Q} R_B - V_{BE} - I_{E_2 Q} R_E = 0$$

$$V_{CC} - I_{B_1 Q} R_B - V_{BE} - \beta_D I_{B_1 Q} R_E = 0 \quad [\text{For Darlington pair, } I_{E_2} = \beta_D I_{B_1}]$$

$$\begin{aligned} I_{B_1 Q} &= \frac{V_{CC} - V_{BE}}{R_B + \beta_D R_E} \\ &= \frac{18V - 1.6V}{3.3M\Omega + (8000 \times 390\Omega)} \\ &= \mathbf{2.55\mu A} \end{aligned}$$

$$\begin{aligned} I_{C_1} &= \beta_1 I_{B_1} \\ &= (89.44) \times (2.55\mu A) \\ &= \mathbf{0.228mA} \end{aligned}$$

$$\begin{aligned} I_{E_1} &= I_{C_1} + I_{B_1} \\ &= 0.228mA + 2.55\mu A \\ &= \mathbf{0.23mA} \end{aligned}$$

$$I_{E_1} = I_{B_1} = \mathbf{0.23mA}$$

$$\begin{aligned} I_{C_2} &= \beta_2 I_{B_2} \\ &= (89.44) \times (0.23\mu A) \\ &= \mathbf{20.57mA} \end{aligned}$$

$$\begin{aligned} I_{E_2} &= I_{C_2} + I_{B_2} \\ &= 20.57mA + 0.23mA \\ &= \mathbf{20.8mA} \end{aligned}$$

$$\begin{aligned} V_{E_2} &= I_{E_2} R_E \\ &= (20.8mA) \times (390) \\ &= \mathbf{8.112V} \end{aligned}$$

$$V_{C_2} = V_{C_1} = \mathbf{18V}$$

$$\begin{aligned} V_{CE_2} &= I_{C_2} - V_{E_2} \\ &= 18 - 8.112 \\ &= \mathbf{9.888V} \end{aligned}$$

Small Signal Parameters:

$$r_{\pi_1} = \frac{\beta_1 V_T}{I_{C_1}} = \frac{89.44 \times 0.026V}{0.228mA} = 10.199k\Omega$$

$$r_{\pi_2} = \frac{\beta_2 V_T}{I_{C_2}} = \frac{89.44 \times 0.026V}{20.578mA} = 113.05\Omega$$

AC (Mid Frequency) Equivalent Circuit:

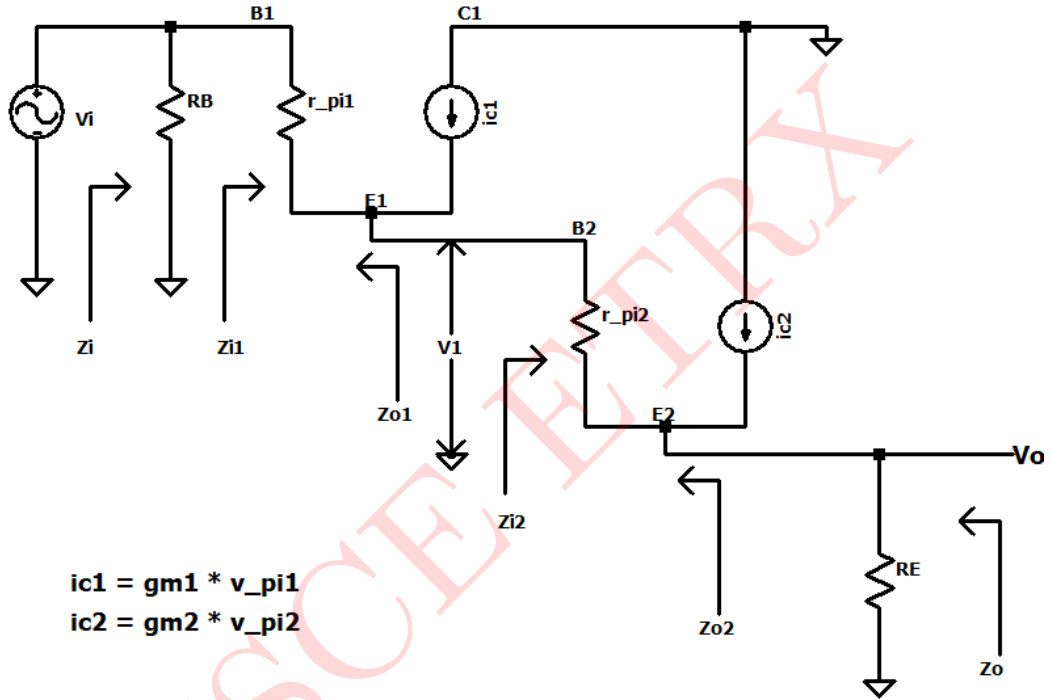


Figure 3: Small Signal Equivalent Circuit

$$\begin{aligned} Z_{i_2} &= r_{\pi_2} + (1 + \beta_2)R_E \\ &= 113.05\Omega + (1 + 89.44)390\Omega \\ &= 35.384k\Omega \end{aligned}$$

$$\begin{aligned} Z_{i_1} &= Z_{i_2}(1 + \beta_1) + r_{\pi_1} \\ &= (35.384k\Omega)(1 + 89.44) + 10.199k\Omega \\ &= 3.21M\Omega \end{aligned} \quad [\text{Input Impedance of Darlington pair is very high}]$$

Input Impedance of 1st stage: Z_i

$$\begin{aligned} Z_i &= R_B \parallel Z_{i_1} \\ &= 3.3M\Omega \parallel 3.21M\Omega \\ &= 1.627M\Omega \end{aligned} \quad [R_B \text{ decreases the input impedance of amplifier}]$$

$$\begin{aligned} Z_{o1} &= \frac{R_B + r_{\pi_1}}{1 + \beta_2} \\ &= \frac{3.3M\Omega + 10.199k\Omega}{1 + 89.44} = 36.6k\Omega \end{aligned}$$

$$\begin{aligned}
Z_{o2} &= \frac{Z_{o1} + r_{\pi 2}}{1 + \beta_2} \\
&= \frac{36.6k\Omega + 113.05\Omega}{1 + 89.44} \\
&= \mathbf{405.938\Omega}
\end{aligned}$$

Output Impedance of 2nd stage: Z_o

$$\begin{aligned}
Z_o &= Z_{o2} \parallel R_E \\
&= 405.938 \parallel 390 \\
&= \mathbf{198.9\Omega}
\end{aligned}$$

Current gain of 1st stage: A_{i1}

$$A_{i1} = \frac{I_{E1}}{I_{B1}} = 1 + \beta_1 = 1 + 89.44 = \mathbf{90.44}$$

Current gain of 2nd stage: A_{i2}

$$A_{i2} = \frac{I_{E2}}{I_{B2}} = 1 + \beta_2 = 1 + 89.44 = \mathbf{90.44}$$

Overall current gain: A_{iT}

$$\begin{aligned}
A_{iT} &= A_{i1} \times A_{i2} \\
&= \mathbf{8179.3936}
\end{aligned}$$

[Current gain of Darlington pair is very high]

$$A_{iT} \text{ in dB} = 20 \log_{10}(A_{iT}) = \mathbf{78.254dB}$$

Voltage Gain of 1st stage : Av_1

$$\begin{aligned}
Av_1 &= \frac{V_1}{V_i} = \frac{I_{E1}}{I_{B1}} \times \frac{Z_{i2}}{Z_{i1}} = A_{i1} \times \frac{Z_{i2}}{Z_{i1}} \\
&= 90.44 \times \frac{35.384k\Omega}{3.21M\Omega} \\
&= \mathbf{0.996}
\end{aligned}$$

Voltage Gain of 2nd stage : Av_2

$$\begin{aligned}
Av_2 &= \frac{V_o}{V_1} = \frac{I_{E2}}{I_{B2}} \times \frac{R_E}{Z_{i2}} = A_{i2} \times \frac{R_E}{Z_{i2}} \\
&= 90.44 \times \frac{390\Omega}{35.384k\Omega} \\
&= \mathbf{0.996}
\end{aligned}$$

Overall Voltage Gain (A_{V_T}):

$$\begin{aligned}
A_{V_T} &= Av_1 \times Av_2 \\
&= 0.996 \times 0.996 \\
&= \mathbf{0.992}
\end{aligned}$$

Output Voltage (V_o):

$$A_{V_T} = \frac{V_o}{V_i} \implies V_o = A_{V_T} \times V_i$$

$$\therefore V_o = 0.992 \times 10mV$$

$$= 9.92V$$

SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

Results:

$$Av1 = V1/Vi = 9.945mV/10mV = 0.9945$$

$$Av2 = Vo/V1 = 9.9139V/9.945mV = 0.996$$

$$Avt = Av1 * Av2 = 0.9905$$

$$Ai1 = Ie1/Ib1 = 280.892nA/3.108nA = 90.377$$

$$Ai2 = Ie2/Ib2 = 25.4uA/280.984nA = 90.396$$

$$Ait = Ai1 * Ai2 = 8169.719$$

$$Ait(dB) = 78.244dB$$

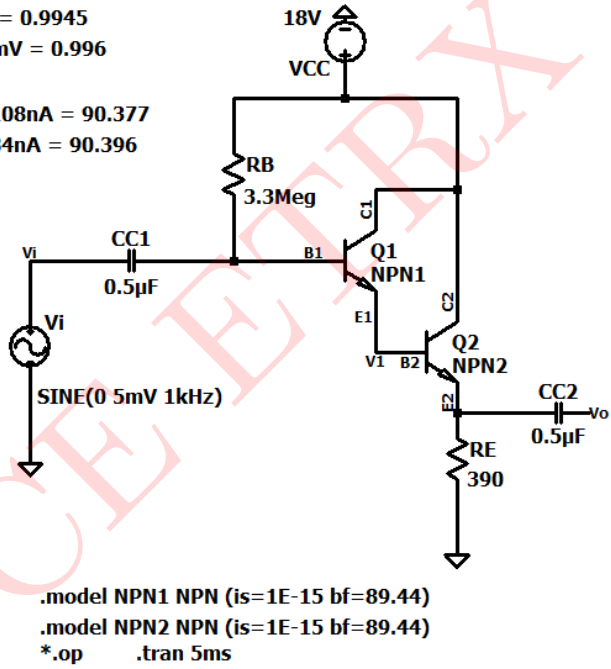


Figure 4: Circuit Schematic

 


Figure 5: Voltage gain of 1st stage

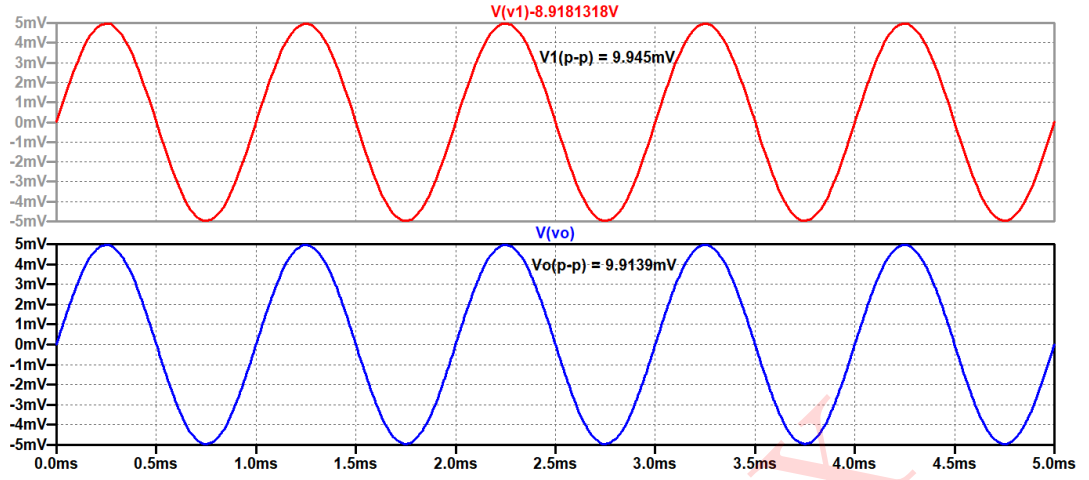


Figure 6: Voltage gain of 2nd stage

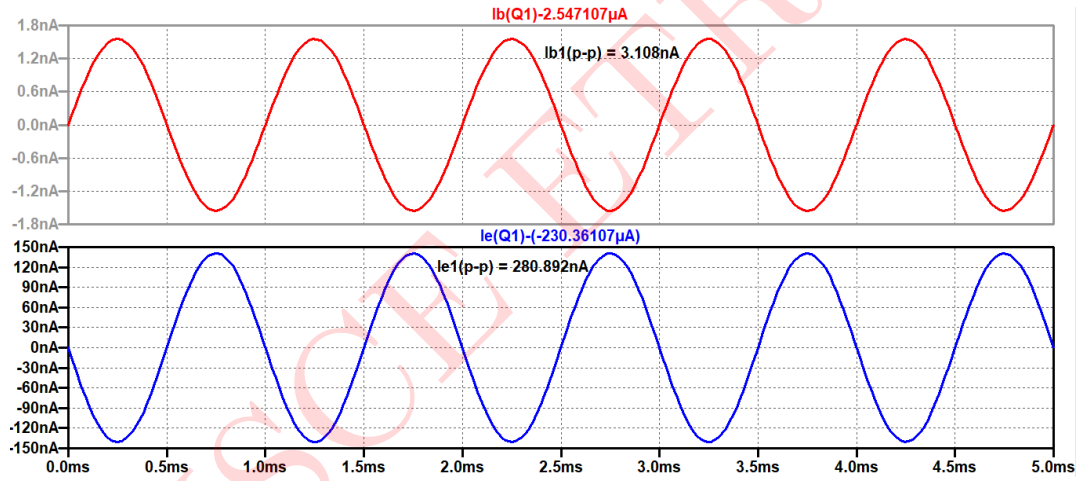


Figure 7: Current gain of 1st stage

 


Figure 8: Current gain of 2nd stage

Comparison of Theoretical and Simulated results:

Parameters	Theoretical	Simulated
I_{B_1}, I_{B_2}	$2.55\mu A, 0.23mA$	$2.547\mu A, 0.23mA$
I_{C_1}, I_{C_2}	$0.228mA, 20.57mA$	$0.2278mA, 20.6mA$
I_{E_1}, I_{E_2}	$0.23mA, 20.8mA$	$0.23mA, 20.83mA$
V_{E_2}	$8.112V$	$8.1252V$
V_{C_2}	$18V$	$18V$
Voltage gain of 1 st stage: Av_1	0.996	0.9945
Voltage gain of 2 nd stage: Av_2	0.996	0.996
Overall Voltage gain: Av_T	0.992	0.9905
Current gain of 1 st stage: Ai_1	90.44	90.377
Current gain of 2 nd stage: Ai_2	90.44	90.396
Overall Current gain: Ai_T in dB	78.254dB	78.244dB
Input Impedance of 1 st stage: Z_i	$1.627M\Omega$	—
Output Impedance of 2 nd stage: Z_o	198.9Ω	—
Output Voltage: V_o	$9.92mV$	$9.9139mV$

Table 1: Numerical 1
