

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Single Stage BJT Amplifier**

11<sup>th</sup> July, 2020

**Numerical 1:**

For the network shown in figure 1, determine  $A_V$ ,  $Z_i$  and  $Z_O$

Given:  $\beta = 210$ ,  $V_A = 100V$

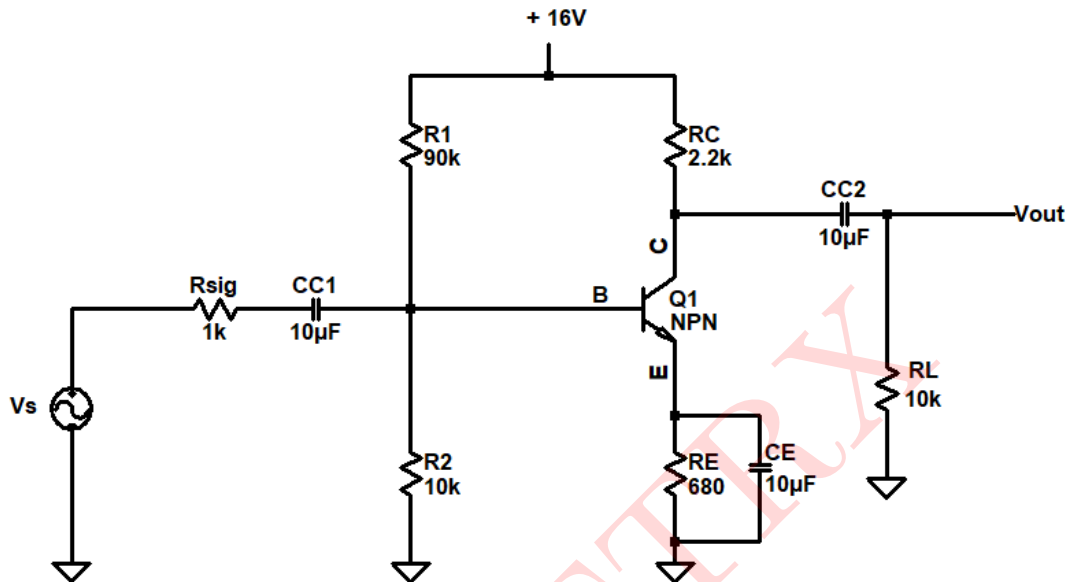


Figure 1: Circuit Diagram

**Solution:** Circuit shown in figure 1 is a common emitter BJT amplifier.

DC equivalent circuit is shown in figure 2:

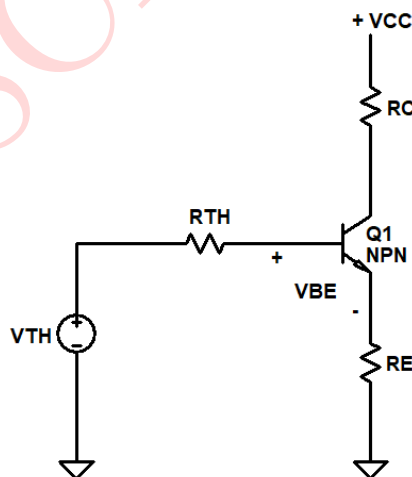


Figure 2: DC equivalent circuit

$$\text{Thevenin's voltage, } V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{10k\Omega}{10k\Omega + 90k\Omega} \times 16V = 1.6V$$

$$\text{Thevenin's equivalent resistance, } R_{TH} = R_1 \parallel R_2 = 10k\Omega \parallel 90k\Omega = 9k\Omega$$

Applying KVL to the B-E loop:

$$V_{TH} - I_B R_{TH} - V_{BE(ON)} - I_E R_E = 0$$

$$\therefore V_{TH} - I_B R_{TH} - V_{BE(ON)} - (1 + \beta) I_B R_E = 0 \quad \dots (\because I_E = (1 + \beta) I_B)$$

$$\therefore I_{BQ} = \frac{V_{TH} - V_{BE(ON)}}{R_{TH} + (1 + \beta) R_E} = \frac{1.6 - 0.7}{9k\Omega + 211 \times 680} = \mathbf{5.9024\mu A}$$

$$\therefore I_{CQ} = \beta I_{BQ} = 210 \times 5.9024\mu A = \mathbf{1.2395\text{ mA}}$$

$$I_{EQ} = I_{CQ} + I_{BQ} = \mathbf{1.2454\text{ mA}}$$

Applying KVL to C-E loop:

$$V_{CEQ} = V_{CC} - I_C R_C - I_E R_E = 16 - (1.2395\text{ mA})(2.2k\Omega) - (1.2454\text{ mA})(680)$$

$$\therefore V_{CEQ} = \mathbf{12.462V}$$

Small signal equivalent parameters:

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.2395\text{ mA}}{26\text{ mV}} = 47.673\text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{1.2395\text{ mA}} = 80.677\text{ k}\Omega$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{210 \times 26\text{ mV}}{1.2395\text{ mA}} = 4.405\text{ k}\Omega$$

Figure 3 shows Small signal equivalent circuit:

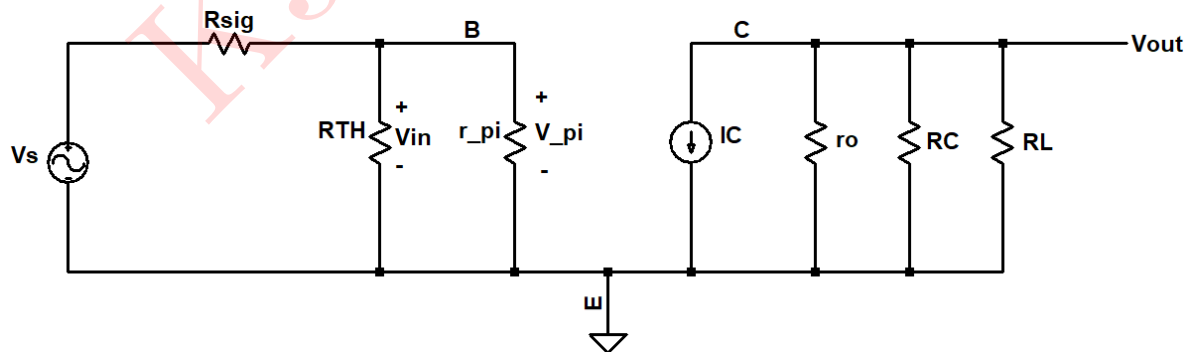


Figure 3: Small signal equivalent circuit

For mid-band analysis, all the capacitors are short-circuited.

Collector current is represented using small signal parameters as:  $I_C = g_m V_\pi$

The impedance seen by looking from the input side gives input impedance, which is:

$$Z_i = R_1 \parallel R_2 = 90k\Omega \parallel 10k\Omega = \mathbf{9k\Omega}$$

The output impedance is given as:

$$Z_o = r_o \parallel R_C \parallel R_L = 80.677k\Omega \parallel 2.2k\Omega \parallel 10k\Omega = \mathbf{1.7639k\Omega}$$

$$\text{Voltage gain: } A_V = \frac{V_{out}}{V_S} \quad \dots(1)$$

$$\text{We know, } V_{in} = \frac{R_1 \parallel R_2}{R_{sig} + (R_1 \parallel R_2)} \times V_S$$

$$\therefore \frac{1}{V_S} = \frac{R_1 \parallel R_2}{R_{sig} + (R_1 \parallel R_2)} \times \frac{1}{V_{in}} \quad \dots(2)$$

$$\text{Also, } V_{out} = -g_m V_\pi (r_o \parallel R_C \parallel R_L) \quad \dots(3)$$

From (1), (2) & (3),

$$A_V = \frac{V_{out}}{V_S} = \frac{-g_m (R_1 \parallel R_2) (r_o \parallel R_C \parallel R_L)}{R_{sig} + (R_1 \parallel R_2)} \quad \dots(\because V_{in} = V_\pi)$$

$$\therefore A_V = \frac{-47.673 \times 10^{-3} \times 9 \times 10^3 \times 1.7639 \times 10^3}{1 \times 10^3 + 9 \times 10^3}$$

$$\mathbf{A_V = -75.6814}$$

### SIMULATED RESULTS:

Above circuit was simulated in LTspice and results obtained are as follows:

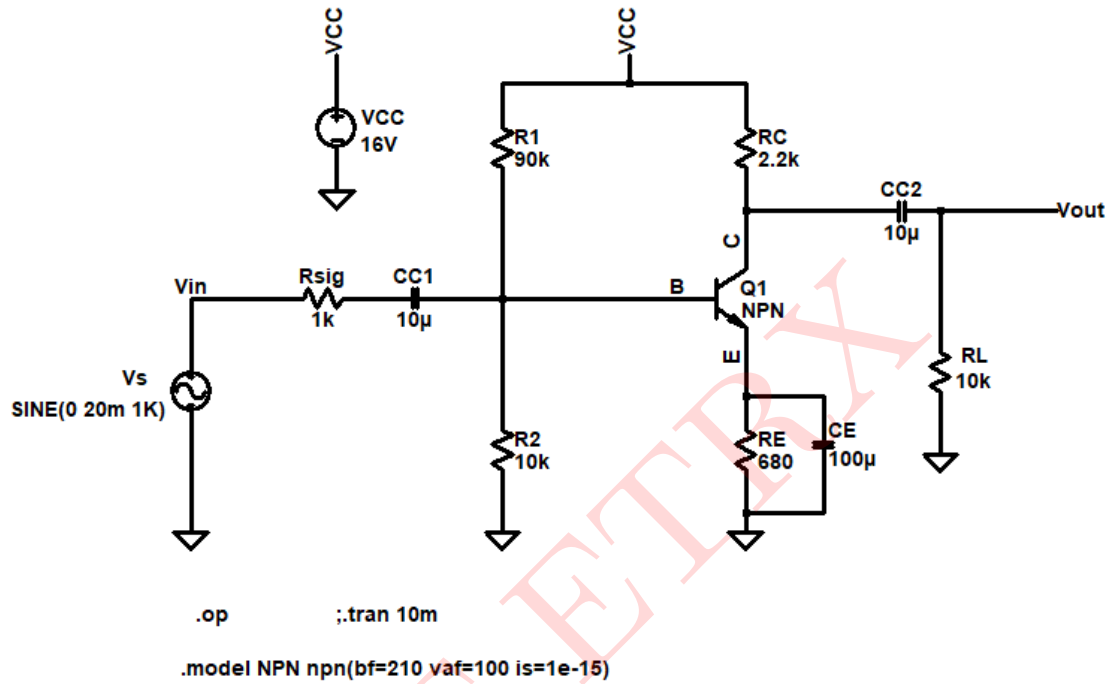


Figure 4: Circuit Schematic: Results

Input and Output waveforms are shown in figure 5:

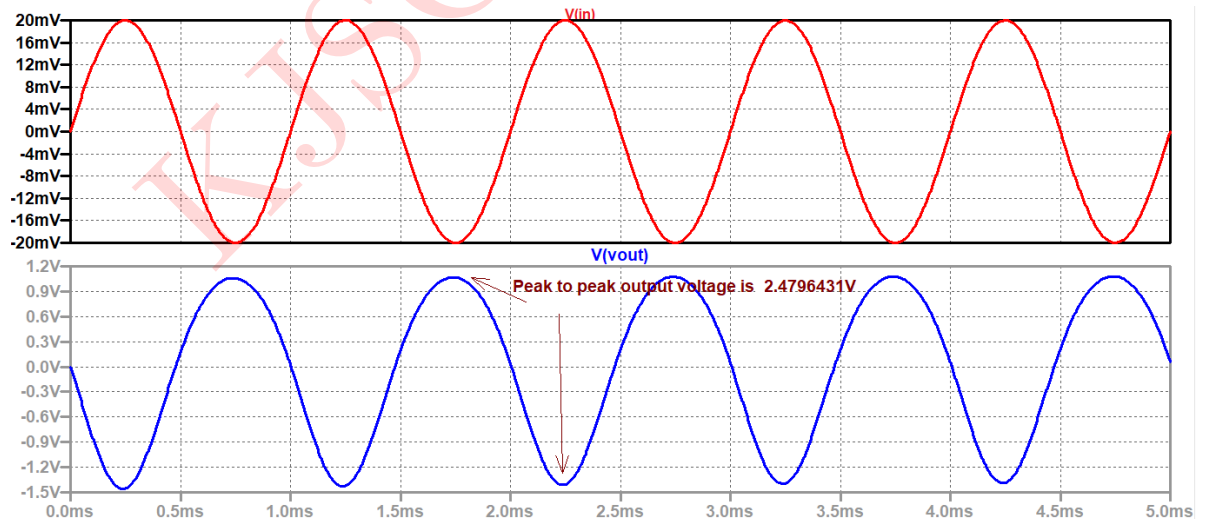


Figure 5: Input and output waveforms

**Comparison between theoretical and simulated values:**

Parameter	Theoretical value	Simulated value
$I_{CQ}$	1.2395mA	1.2242mA
$V_{CEQ}$	12.4262V	12.4707V
$I_{BQ}$	5.9024uA	5.2164uA
$V_{TH}$	1.6V	1.5531V
$A_V$	-75.6814	-61.6075

Table 1: Numerical 1

KJSCE ETRX

**Numerical 2:**

For the network shown in figure 6,  $\beta = 90$ , determine:

- $r_\pi$
- $Z_i$
- $Z_o(r_o = \infty)$
- $A_V(r_o = \infty)$
- The parameters of parts (b) to (d) if  $r_o = 50k\Omega$  and compare results.

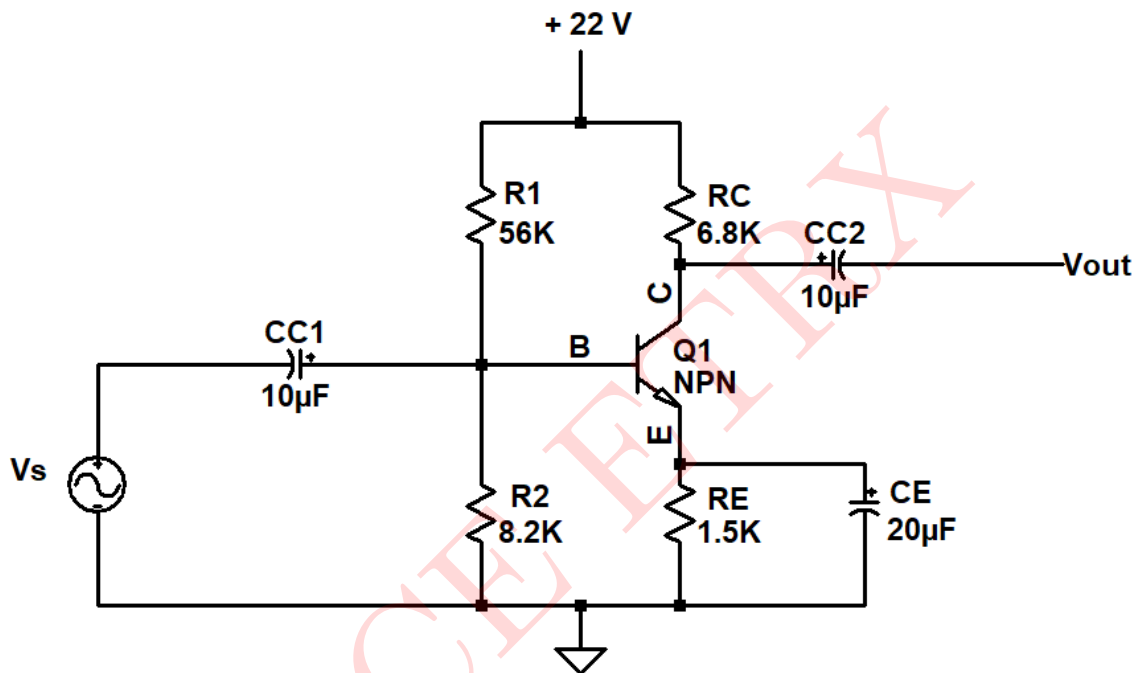


Figure 6: Circuit Diagram

**Solution:** The circuit shown in figure 6 is common emitter BJT amplifier.

Using Thevenin's theorem:

$$V_{TH} = \frac{R_2 \times 22}{R_1 + R_2} = \frac{8.2 \times 22}{56 + 8.2} = 2.81V$$

$$R_{TH} = R_1 \parallel R_2 = 56k\Omega \parallel 8.2k\Omega = 7.1526k\Omega$$

Thevenin's equivalent circuit is shown in figure 7:

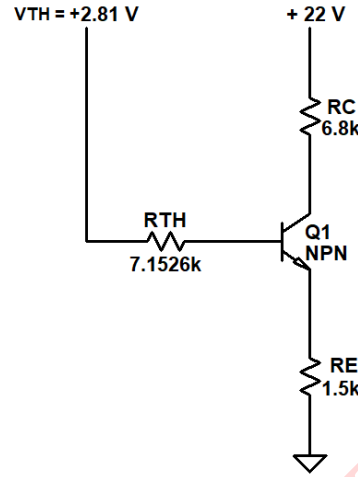


Figure 7: Thevenin's equivalent circuit

Applying KVL to B-E loop:

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$\therefore V_{TH} - I_B R_{TH} - V_{BE} - I_B(\beta + 1)R_E = 0 \quad \dots(\because I_E = (\beta + 1)I_B)$$

$$I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1)R_E} = \frac{2.81 - 0.7}{7.1526k\Omega + 91 \times 1.5k\Omega}$$

$$\therefore I_{BQ} = 14.690\mu A$$

$$I_{CQ} = \beta I_{BQ} = (90)(14.690\mu A)$$

$$\therefore I_{CQ} = 1.3221mA$$

$$I_{EQ} = (\beta + 1)I_{BQ} = (91)(14.69\mu A)$$

$$\therefore I_{EQ} = 1.3368mA$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{90 \times 26mV}{1.3221mA} = \mathbf{1.770k\Omega} \quad \dots V_T \text{ is thermal voltage which is } 26mV \text{ at } 27^\circ C$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.3221mA}{26mV} = \mathbf{50.85mA/V}$$

Applying KVL to C-E loop:

$$V_{CEQ} = 22 - I_C R_C - I_E R_E$$

$$\therefore V_{CEQ} = 22 - (1.3221mA)(6.8k\Omega) - (1.3368mA)(1.5k\Omega)$$

$$\therefore V_{CEQ} = 11V$$

Figure 8 shows Small signal equivalent circuit:

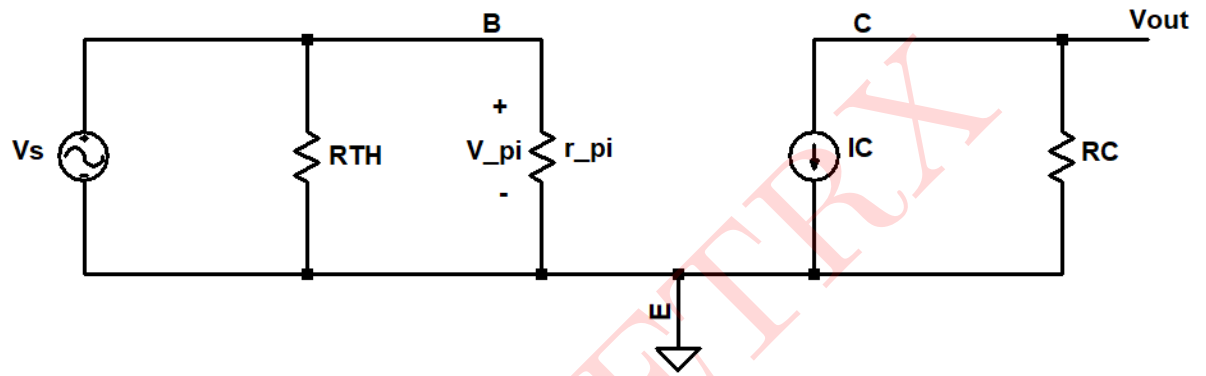


Figure 8: Small signal equivalent circuit

Here  $r_o = \infty$  hence open-circuited

For mid-band analysis, all the capacitors are short-circuited.

Collector current is represented using small signal parameters as:  $I_C = g_m V_\pi$

The impedance seen by looking from the input side gives input impedance, which is:

$$Z_i = R_1 \parallel R_2 \parallel r_\pi = 56k\Omega \parallel 8.2k\Omega \parallel 1.77k\Omega$$

$$\therefore \mathbf{Z_i = 1.4189k\Omega}$$

Output impedance is given as:

$$Z_o = R_C$$

$$\therefore \mathbf{Z_o = 6.8k\Omega}$$

$$\text{Voltage gain, } A_V = \frac{V_{out}}{V_{in}} \quad \dots(1)$$

$$V_{out} = -g_m V_\pi R_C \quad \dots(2)$$

As seen from small signal equivalent circuit:

$$V_{in} = V_\pi \quad \dots(3)$$



From (1), (2) & (3), we get:

$$A_V = \frac{-g_m \times V_\pi \times R_C}{V_\pi}$$

$$\therefore A_V = -g_m R_C$$

$$\therefore A_V = -50.85mA \times 6.8k\Omega$$

$$\mathbf{A_V = -345.75}$$

Small signal equivalent circuit with  $r_o$  is shown in figure 9:

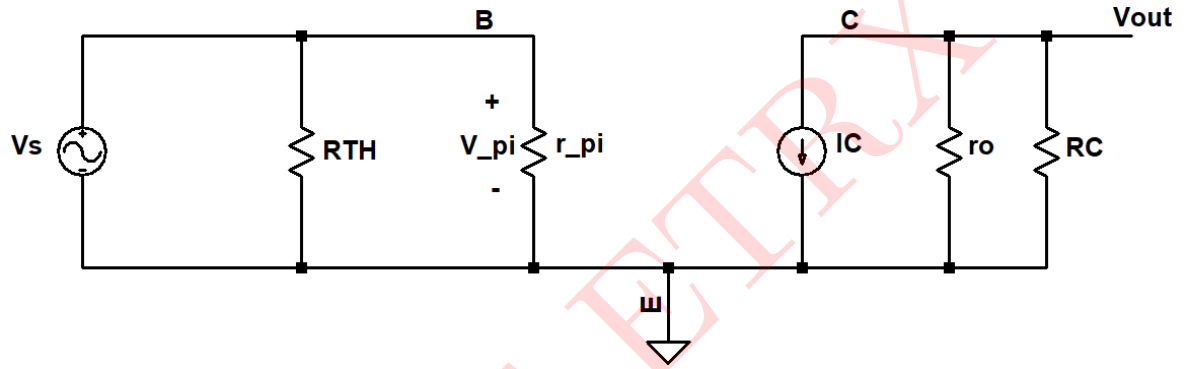


Figure 9: Small signal equivalent circuit with  $r_o$

Input impedance remains unchanged,

$$Z_i = R_1 \parallel R_2 \parallel r_\pi$$

$$\mathbf{Z_i = 1.4189k\Omega}$$

Output impedance is given as:

$$Z_o = R_C \parallel r_o = 6.8k\Omega \parallel 50k\Omega$$

$$\mathbf{Z_o = 5.9859k\Omega}$$

$$\text{Also voltage gain, } A_V = \frac{V_{out}}{V_{in}}$$

$$V_{out} = -g_m V_\pi (R_C \parallel r_o) \quad \dots (V_{in} = V_\pi)$$

$$\therefore A_V = -g_m (R_C \parallel r_o)$$

$$A_V = -(50.85mA)(6.8k\Omega \parallel 50k\Omega)$$

$$\mathbf{A_V = -304.38}$$

Comparing results with and without  $r_o$  :

Parameter	$r_o = 50k\Omega$	$r_o = \infty$
$Z_i$	1.4189k $\Omega$	1.4189k $\Omega$
$Z_o$	5.9859k $\Omega$	6.8k $\Omega$
$A_V$	-304.38	-345.75

Table 2: Numerical 2

Output impedance decreases and  $r_o$  changes from  $\infty$  to 50k $\Omega$

Also, the voltage gain of the amplifier decreases from  $\infty$  to 50k $\Omega$  which means that early voltage  $V_A$  is no more  $\infty$  ( $\because r_o \propto V_A$ ). Hence, BJT deviates from its ideal characteristics.

### SIMULATED RESULTS:

Above circuit was simulated in LTspice and results obtained are as follows:

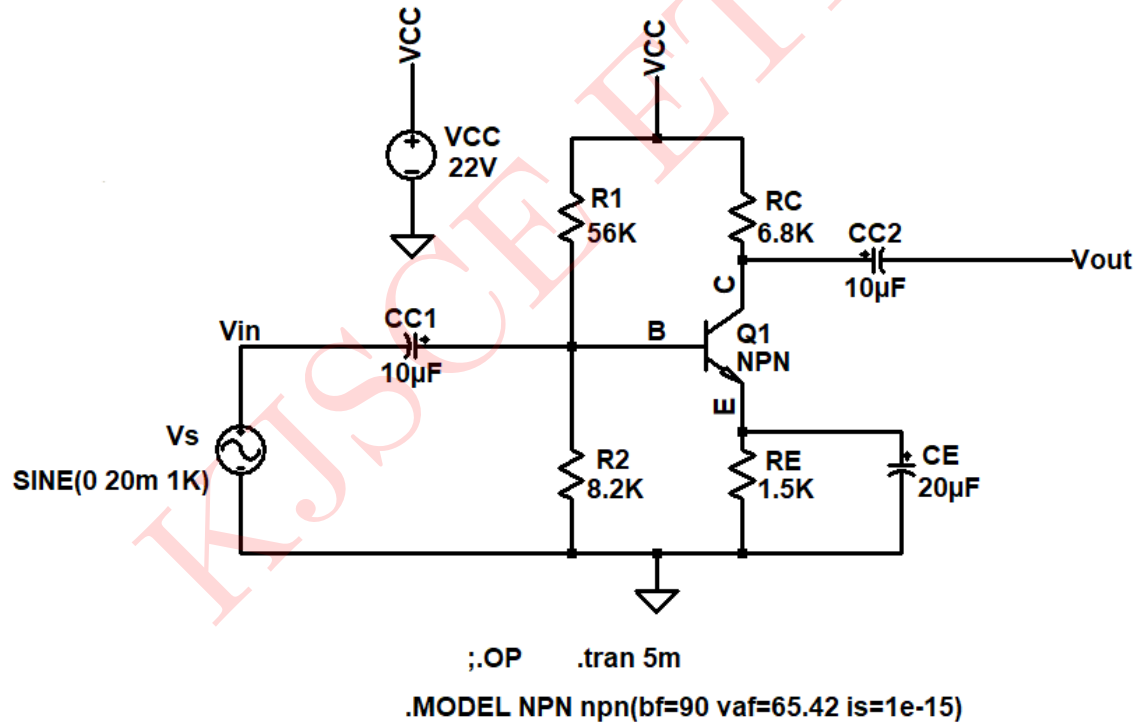


Figure 10: Circuit Schematic: Results

The input and output waveforms for both the cases are shown in figure 11 and 12 respectively:

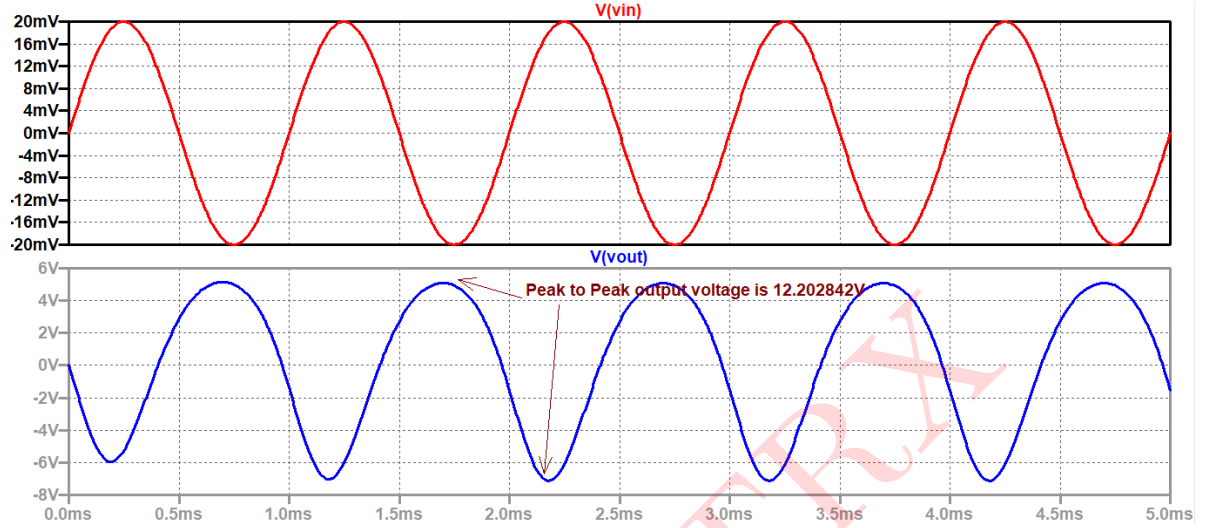


Figure 11: Input and output waveform for  $r_o = \infty$

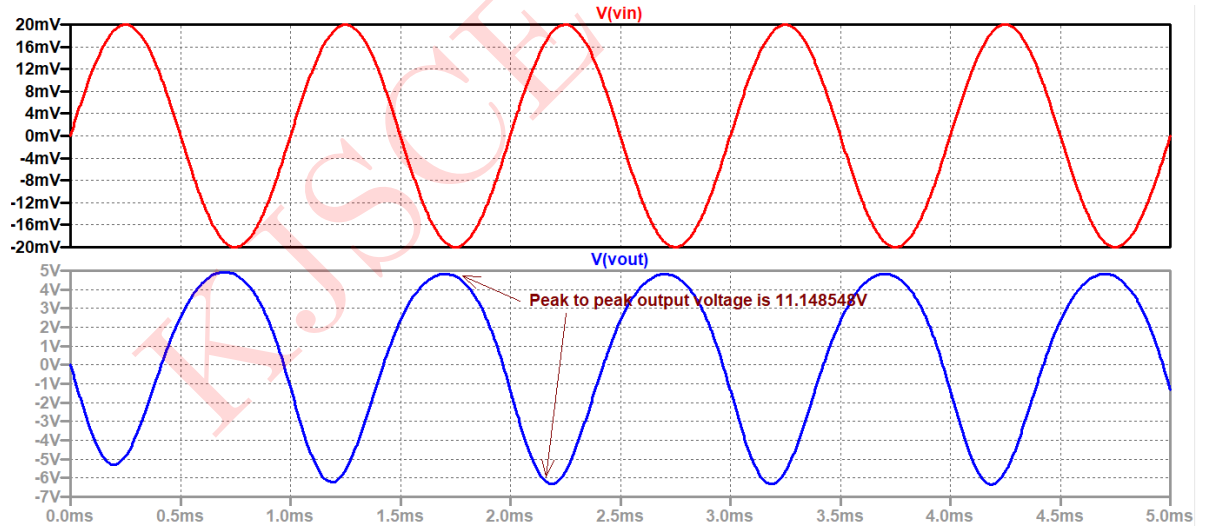


Figure 12: Input and output waveform for  $r_o = 50k\Omega$

**Comparison between theoretical and simulated values:**

Parameter	Theoretical value	Simulated value
$I_{CQ}$	1.3221mA	1.3084mA
$I_{BQ}$	14.690 $\mu$ A	14.5374 $\mu$ A
$V_{CEQ}$	11.0V	11.1187V
$V_{TH}$	2.81V	2.706V
$A_V$ (with $r_o$ )	-304.38	-278.71
$A_V$ (without $r_o$ )	-345.75	-305.71

Table 3: Numerical 2

### Numerical 3:

For the network shown in figure 13, the transistor parameters are  $\beta = 100$  and  $V_A = 100V$ . Determine  $R_i$  and  $A_V = V_{out}/V_s$ .

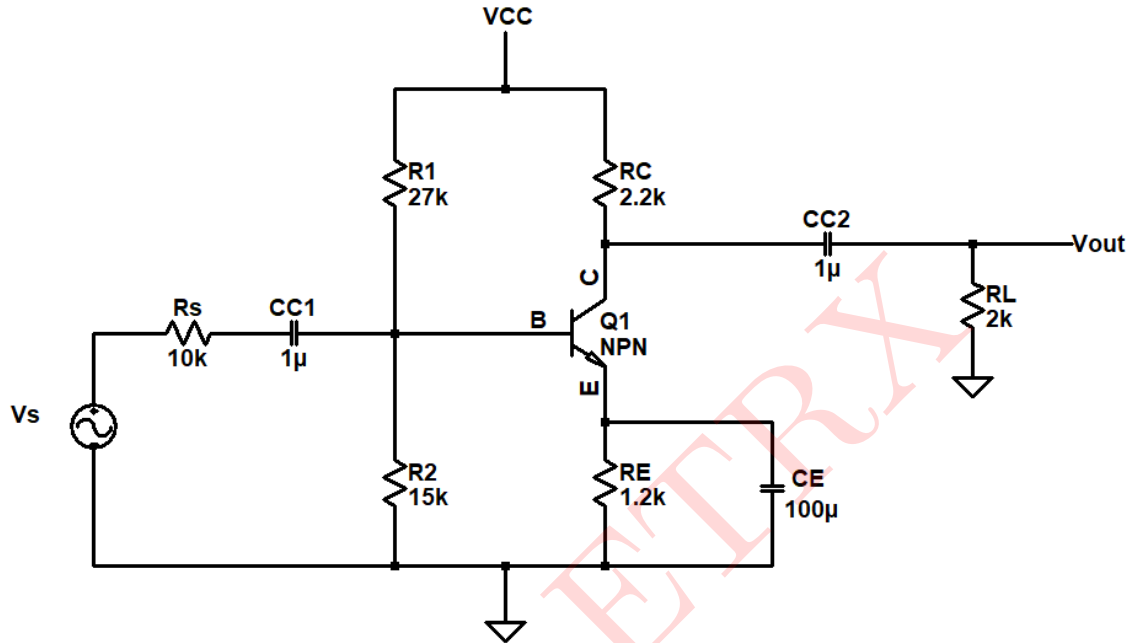


Figure 13: Circuit Diagram

**Solution:** The circuit shown in figure 13 is a common emitter BJT Amplifier.

$$V_{TH} = \frac{15k\Omega \times 9}{27k\Omega + 15k\Omega} = 3.2143V$$

$$R_{TH} = R_1 \parallel R_2 = 27k\Omega \parallel 15k\Omega = 9.6429k\Omega$$

Thevenin's equivalent circuit is shown in figure 14:

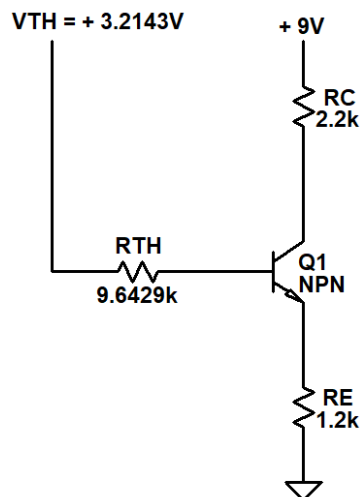


Figure 14: Thevenin's equivalent circuit

Applying KVL to B-E loop:

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$V_{TH} - I_B R_{TH} - V_{BE} - (\beta + 1)I_B R_E = 0 \quad \dots (\because I_E = (1 + \beta)I_B)$$

$$\therefore I_{BQ} = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1)R_E} = \frac{3.2143 - 0.7}{9.6429k\Omega + 101 \times 1.2k\Omega}$$

$$\therefore I_{BQ} = \mathbf{19.2162\mu A}$$

We know,  $I_{CQ} = \beta I_{BQ}$  and  $I_{EQ} = (\beta + 1)I_{BQ}$

$$\therefore I_{CQ} = 100 \times 19.2162\mu A = 1.9216mA$$

$$I_{EQ} = (100 + 1)19.2162\mu A = 1.9408mA$$

Small signal parameters:

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 26mV}{1.9216mA}$$

$$\therefore r_\pi = 1.353k\Omega, \text{ where } V_T \text{ is thermal voltage which is } 26mV \text{ at } 27^\circ C$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.9216mA}{26mV} = 73.9077 \text{ mA/V}$$

Applying KVL to C-E loop:

$$V_{CEQ} = 9 - I_C R_C - I_E R_E$$

$$\therefore V_{CEQ} = 9 - (1.9216mA)(2.2k\Omega) - (1.9408mA)(1.2k\Omega)$$

$$\therefore V_{CEQ} = 2.4435V$$

Figure 15 shows Small signal equivalent circuit:

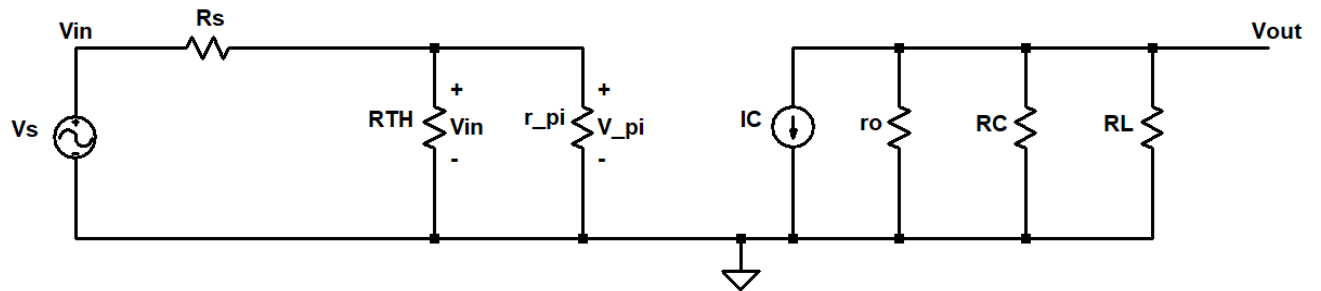


Figure 15: Small signal equivalent circuit

All capacitors are short-circuited.

Input resistance,  $R_i = R_1 \parallel R_2 \parallel r_\pi$

$$\therefore R_i = 27k\Omega \parallel 15k\Omega \parallel 1.353k\Omega = 1.1865k$$

$$\therefore \mathbf{R_i = 1.1865k\Omega}$$

$$\text{Voltage gain: } A_V = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_s} \quad \dots(1)$$

From small signal equivalent circuit,  $V_{in} = V_\pi$

$$\therefore V_{out} = -g_m V_\pi (R_C \parallel r_o \parallel R_L) \quad \dots(2)$$

$$\text{Also, } V_{in} = \frac{R_1 \parallel R_2 \parallel r_\pi}{R_s + (R_1 \parallel R_2 \parallel r_\pi)} \times V_s$$

$$\therefore \frac{1}{V_s} = \frac{R_1 \parallel R_2 \parallel r_\pi}{R_s + (R_1 \parallel R_2 \parallel r_\pi)} \times \frac{1}{V_\pi} \quad \dots(3)$$

From (1), (2) and (3):

$$A_V = \frac{-g_m V_\pi (R_C \parallel r_o \parallel R_L)}{V_\pi} \times V_\pi \times \frac{R_1 \parallel R_2 \parallel r_\pi}{R_s + (R_1 \parallel R_2 \parallel r_\pi)} \times \frac{1}{V_\pi}$$

$$\therefore A_V = \frac{-g_m (R_C \parallel r_o \parallel R_L) (R_1 \parallel R_2 \parallel r_\pi)}{R_s + (R_1 \parallel R_2 \parallel r_\pi)}$$

$$\therefore A_V = \frac{(-73.9077 \times 10^{-3})(1.0269 \times 10^3)(1.1855 \times 10^3)}{(10 + 1.1865) \times 10^3}$$

$$\mathbf{A_V = -8.05}$$

### SIMULATED RESULTS:

Above circuit was simulated in LTspice and results obtained are as follows:

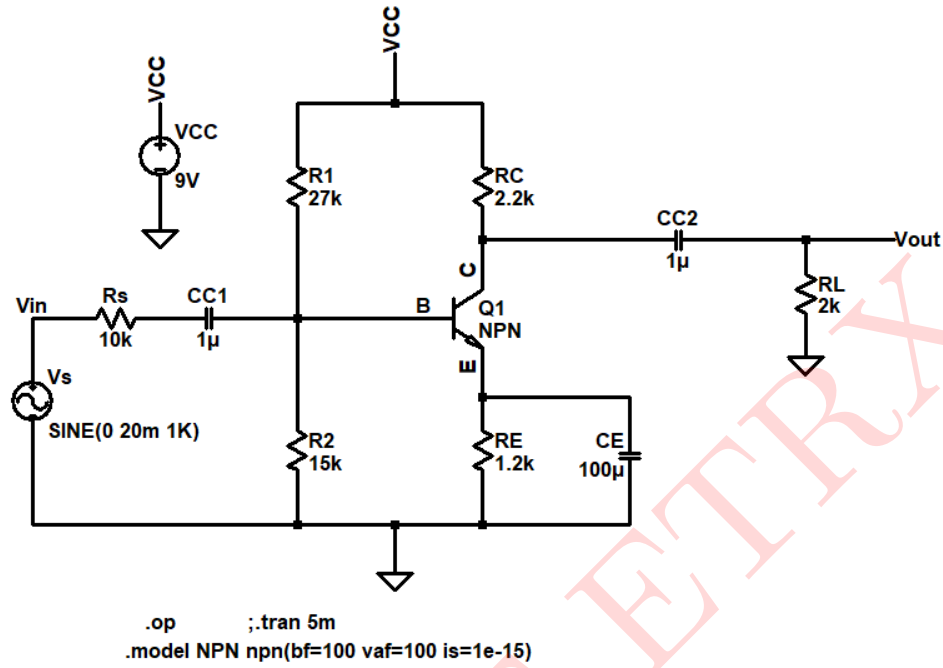


Figure 16: Circuit Schematic: Results

The input and output waveform is shown in figure 17:

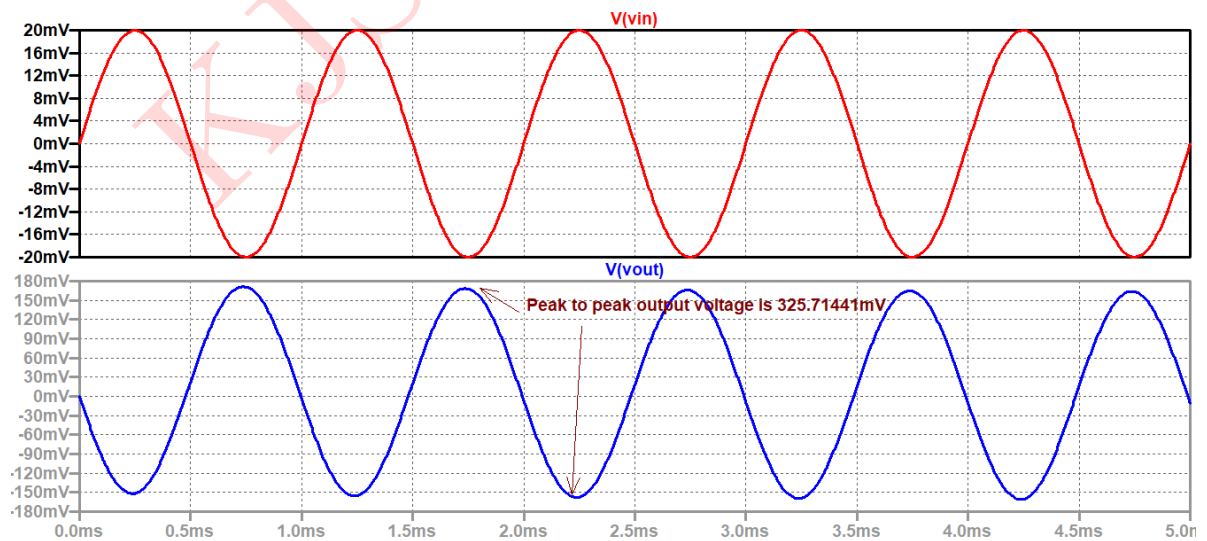


Figure 17: Input and output waveform



**Comparison between theoretical and simulated values:**

Parameter	Theoretical value	Simulated value
$I_{CQ}$	1.9216mA	1.9mA
$I_{BQ}$	19.2162 $\mu$ A	18.6749 $\mu$ A
$V_{TH}$	3.2143V	3.0342V
$V_{CEQ}$	2.4435V	2.5149V
$A_V$	-8.05	-8.15

Table 4: Numerical 3

KJSCE ETRX