

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DIODE APPLICATIONS

Numerical 1: Simulate a half wave rectifier circuit with input Amplitude = 100V peak, $f = 50 \text{ Hz}$ and $R_L = 75\Omega$ using LT spice. Select diode as 1N4148. Use 10:1 step down transformer. Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diode
- Current flowing through the circuit

Also, calculate the efficiency of the Half wave rectifier circuit

Solution:

From the given data, the half wave rectifier can be represented as shown in Circuit 1.

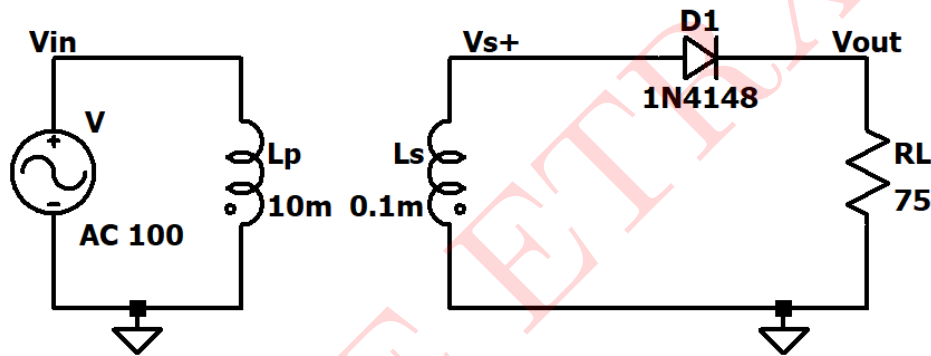


Figure 1: Circuit 1

Given:

$$V_P = 100V, f = 50\text{Hz}, R_L = 75\Omega$$

Transformer is a 10:1 step down transformer

The transformer consists of a primary coil L_P and a secondary coil L_S . The ratio of the transformer is given as 10:1

$$\frac{V_P}{V_S} = \frac{10}{1}$$

$$\therefore V_S = V_m = \frac{100}{10} = 10$$

$$\therefore V_m = 10V$$

The DC Output Power is given by:

$$P_{DC} = \frac{V_{DC}^2}{R_L} = \frac{V_m^2}{\pi^2 \times R_L} = \frac{10^2}{\pi^2 \times 75} = 0.135$$

$$\therefore P_{DC} = 0.135W$$

The AC Output Power is given by:

$$P_{AC} = \frac{V_{RMS}^2}{R_F + R_L} = \frac{V_m^2}{4 \times (R_F + R_L)} = \frac{10^2}{4 \times (75 + 0.01)} = 0.33$$

$$\therefore P_{AC} = 0.33W$$

Efficiency of the transformer is given by:

$$\eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{0.135}{0.33} \times 100 = 40.91$$

$$\therefore \eta = 40.91\%$$

The Peak Inverse Voltage Rating (PIV Rating) of the transformer is given by:

$$\text{PIV Rating} = -V_m = -10V$$

The current through the secondary can be calculated as:

$$I_m = \frac{V_m}{R_F + R_L} = \frac{10}{0.01 + 75} = 0.133$$

$$\therefore I_m = 0.133A$$

SIMULATED RESULTS

The given circuit is simulated in LTspice and the results obtained are as follows:

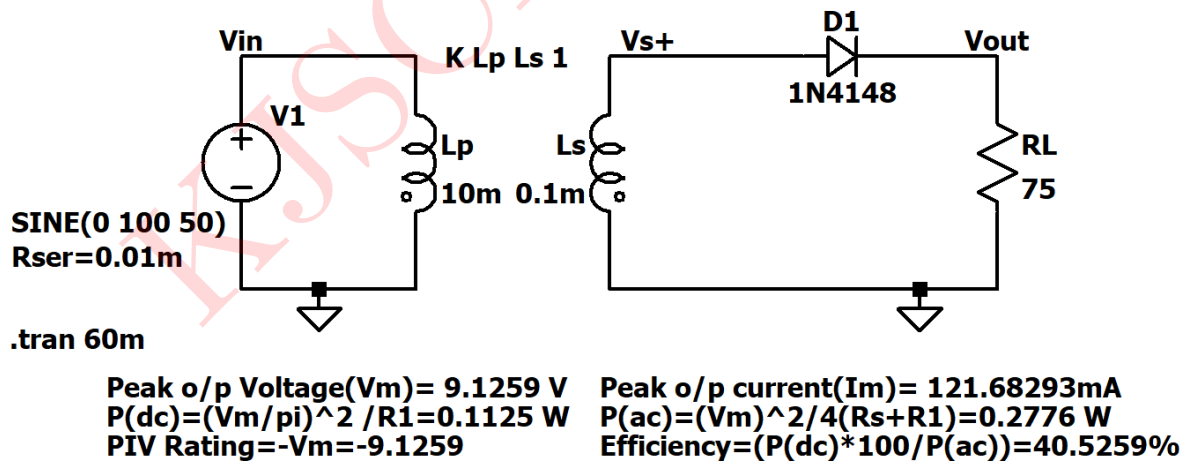


Figure 2: Circuit Schematic

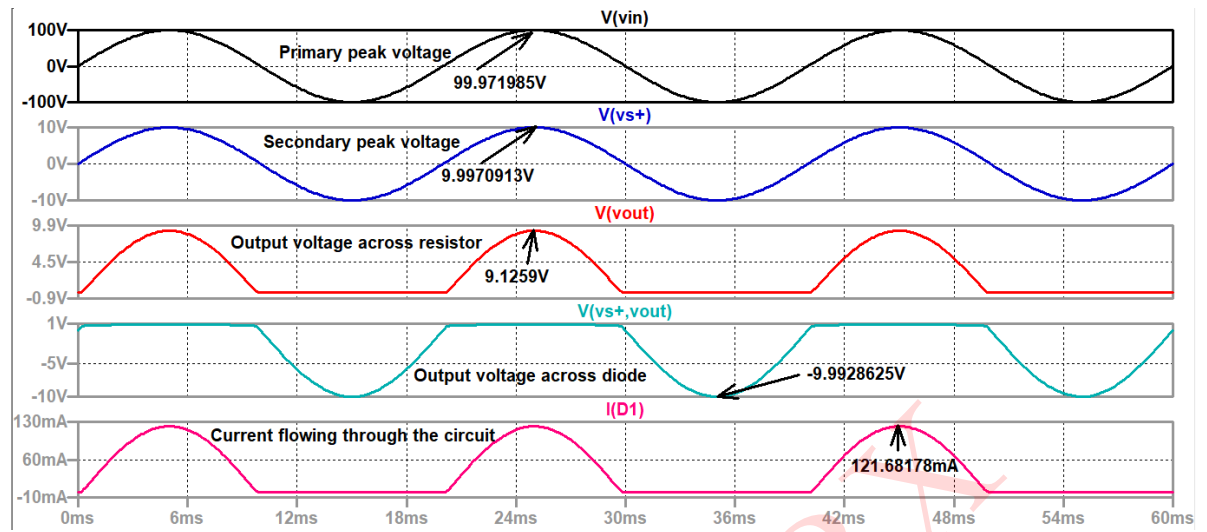


Figure 3: Simulated Results

Comparison of calculated and simulated values:

Parameter	Calculated Value	Simulated Value
V_m	10V	9.1259V
I_m	0.133A	0.12168A
P_{DC}	0.33W	0.2776W
P_{AC}	0.135W	0.1125W
η	40.91%	40.5259%
PIV Rating	-10V	-9.1259V

Table 1: Numerical 1

Numerical 2: Simulate a Full wave rectifier circuit with input Amplitude = 150V peak, $f = 50 \text{ Hz}$, and $R_L = 150\Omega$ using LT spice. Select diode as 1N4148. Use 10:1 step down center tap transformer.

Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diodes
- Current flowing through the diodes
- Current flowing through the circuit

Also, calculate the efficiency of the Full wave Center tapped rectifier circuit.

Solution:

From the given data, the centre-tapped full wave rectifier can be represented as shown in Circuit 2.

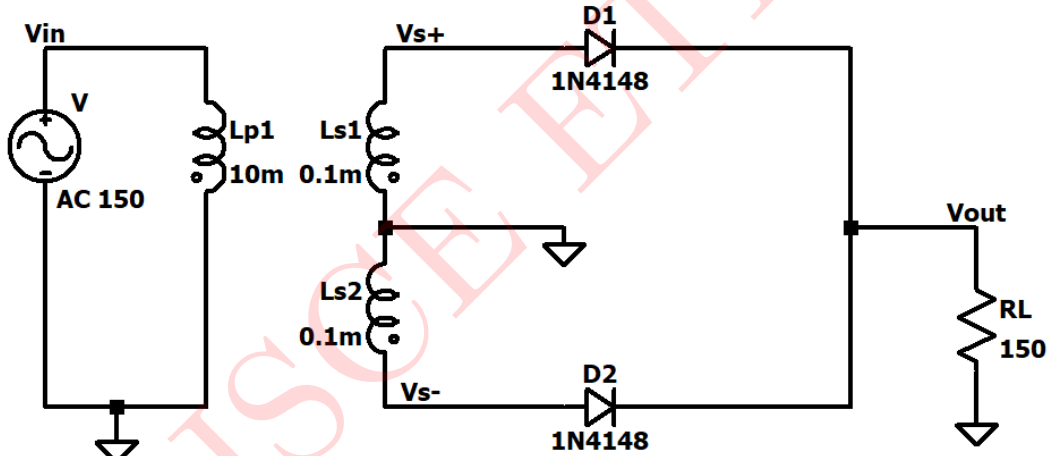


Figure 4: Circuit 2

Given:

$$V_P = 150V, f = 50\text{Hz}, R_L = 150\Omega$$

Transformer is a 10:1 step down transformer

The transformer consists of a primary coil L_{P1} and two secondary coils L_{S1} and L_{S2} which are centre-tapped. The ratio of the transformer is given as 10:1

$$\frac{V_P}{V_S} = \frac{10}{1}$$

$$\therefore V_S = V_m = \frac{V_P}{10} = \frac{150}{10} = 15$$

$$\therefore V_m = 15V$$

The current through the secondary can be calculated as:

$$I_m = \frac{V_m}{R_F + R_L} = \frac{15}{0.01 + 150} = 99.99$$

$$\therefore I_m = 99.99A$$

The DC Output Power is given by:

$$P_{DC} = \left(\frac{2 \times I_m}{\pi} \right)^2 \times R_L = \left(\frac{2 \times 99.99}{\pi} \right)^2 \times 150 = 0.6078$$

$$\therefore P_{DC} = 0.6078W$$

The AC Output Power is given by:

$$P_{AC} = \frac{I_m^2 \times (R_F + R_L)}{2} = \frac{99.99^2 \times (0.01 + 150)}{2} = 0.7499$$

$$\therefore P_{AC} = 0.7499W$$

Efficiency of the transformer is given by:

$$\eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{0.6078}{0.7499} \times 100 = 81.05$$

$$\therefore \eta = 81.05\%$$

The Peak Inverse Voltage Rating (PIV Rating) of the transformer is given by:

$$\text{PIV Rating} = -2V_m = -(2 \times 15) = -30V$$

$$\therefore \text{PIV Rating} = -30V$$

SIMULATED RESULTS

The given circuit is simulated in LTspice and the results obtained are as follows:

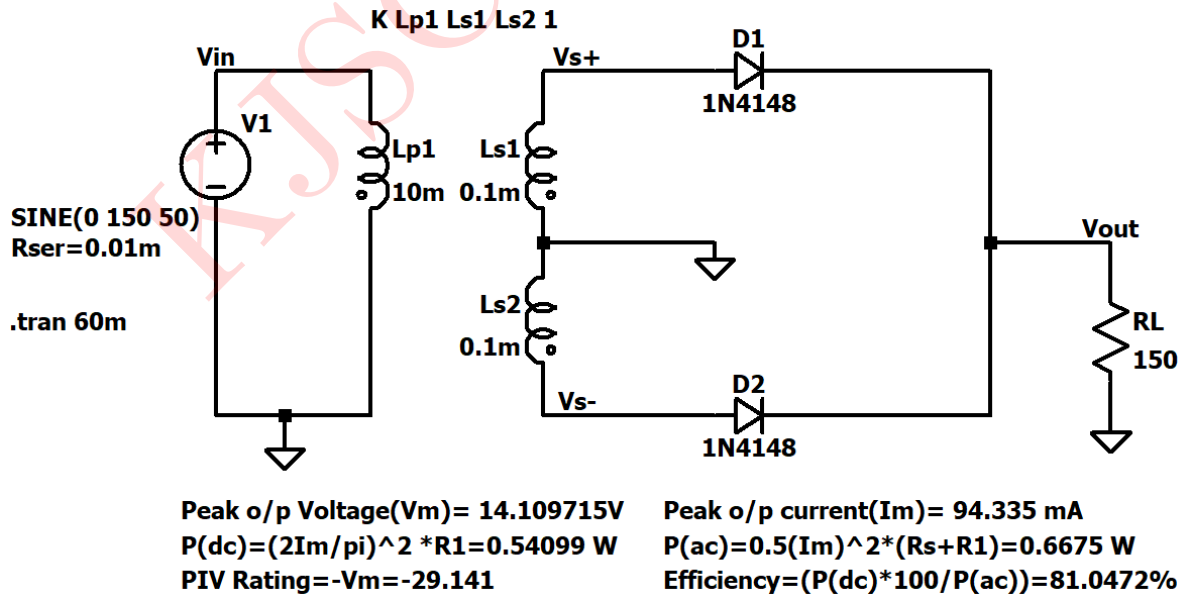


Figure 5: Circuit Schematic

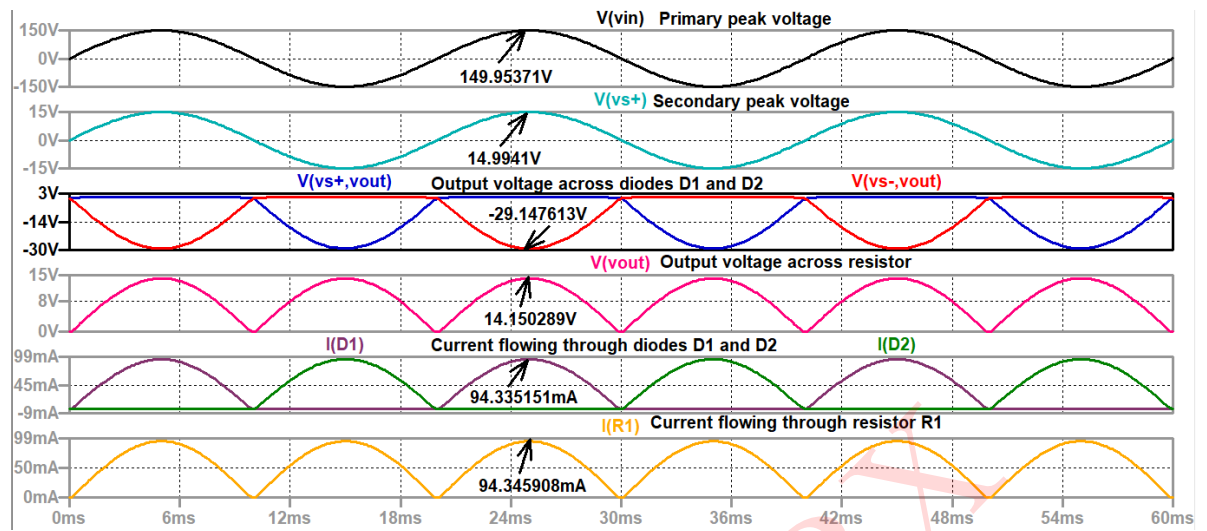


Figure 6: Simulated Results

Comparison of calculated and simulated values:

Quantity	Calculated Value	Simulated Value
V_m	15V	14.1097V
I_m	99.99mA	94.335mA
P_{DC}	0.6078W	0.54099W
P_{AC}	0.7499W	0.6675W
η	81.05%	81.0472%
PIV Rating	-30V	-29.141V

Table 2: Numerical 2