

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Cascode Amplifier

12th July, 2020

Numerical 1:

Consider cascode circuit as shown in figure 1, let $\beta = 100$, $V_{BE(ON)} = 0.7V$ and $V_A = \infty$ for each transistor. Given: $V_{CC} = 9V$ and $R_L = 10k\Omega$

Find DC parameters, A_{V1} , A_{V2} , Z_i and Z_o

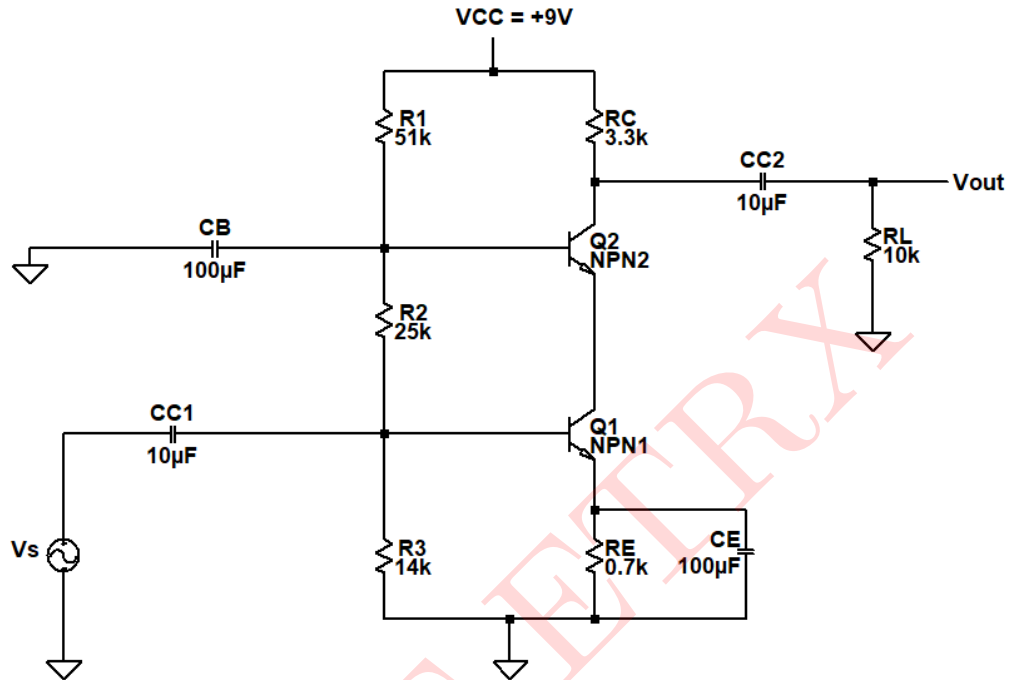


Figure 1: Circuit diagram

Solution: Circuit shown in figure 1 is a CE-CB cascode amplifier.

DC Analysis: All capacitors are open circuited and DC equivalent circuit is shown in figure 2:

 


Figure 2: DC equivalent circuit

For stage 1:

 


Figure 3: Stage 1 DC equivalent circuit

$$V_{B1} = \frac{R_3}{R_1 + R_2 + R_3} \times V_{CC}$$

$$\therefore V_{B1} = \frac{14k\Omega}{51k\Omega + 25k\Omega + 14k\Omega} \times 9$$

$$\therefore V_{B1} = 1.4V$$

$$V_{BE1} = 0.7V \quad \dots(\text{given})$$

$$\therefore V_{BE1} = V_{B1} - V_{E1}$$

$$\therefore V_{E1} = V_{B1} - V_{BE1} = 1.4 - 0.7$$

$$\therefore V_{E1} = 0.7V$$

$$\text{Also, } I_{E1} = \frac{V_{E1}}{R_E}$$

$$\therefore I_{E1} = \frac{0.7}{0.7k\Omega} = 1mA$$

$$\therefore I_{B1} = I_{B2} = \frac{I_{E1}}{(1 + \beta)}$$

$$\therefore I_{B1} = I_{B2} = 9.9\mu A$$

Assuming I_{B1} , I_{B2} very small and $I_{E1} \approx I_{E2} \approx I_{C1} \approx I_{C2}$

$$\therefore I_{E1} = I_{E2} = I_{C2} = I_{C1} = 1mA$$

For Stage 2:

 


Figure 4: Stage 2 DC equivalent circuit

$$V_{B2} = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \times V_{CC}$$

$$\therefore V_{B2} = \frac{25k\Omega + 14k\Omega}{51k\Omega + 25k\Omega + 14k\Omega} \times 9$$

$$\therefore V_{B2} = 3.9V$$

$$V_{BE2} = 0.7V \quad \dots(\text{given})$$

$$V_{BE2} = V_{B2} - V_{E2}$$

$$\therefore V_{E2} = V_{B2} - V_{BE2} = 3.9 - 0.7$$

$$\therefore V_{E2} = 3.2V$$

Applying KCL to C-E loop of stage 2:

$$V_{C2} = V_{CC} - I_{C2}R_C$$

$$\therefore V_{C2} = 9 - (1mA)(3.3k\Omega)$$

$$V_{C2} = 5.7V$$

Small signal parameters:

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} \quad \dots (\text{assuming } r_{\pi 1} = r_{\pi 2} = r_{\pi})$$

$$r_{\pi} = \frac{100 \times 26mV}{1mA}$$

$$r_{\pi} = 2.6k\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} \quad \dots (\text{assuming } g_{m1} = g_{m2} = g_m)$$

$$\therefore g_m = \frac{1}{26} = 38.4615 \text{ mA/V}$$

Small signal equivalent circuit is shown in figure 5:

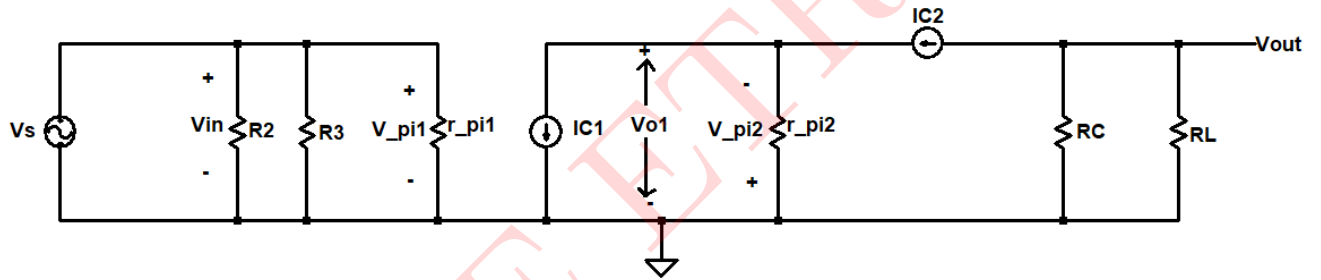


Figure 5: Small signal equivalent circuit

All capacitors are short-circuited.

$$\text{For Stage 1: } A_{V1} = \frac{V_{o1}}{V_s}$$

$$\text{Here, } V_s = V_{in}$$

$$V_{o1} = -g_{m1} V_{\pi 1} \frac{r_{\pi 2}}{(1 + \beta)}$$

$(1 + \beta)$ is due to resistance reflection rule which states that resistance looking into the base is $(1 + \beta)$ times the total emitter resistance.

$$\therefore A_{V1} = \frac{-g_{m1} V_{\pi 1} r_{\pi 2}}{V_{\pi 1} (1 + \beta)} = \frac{-g_{m1} r_{\pi 2}}{(1 + \beta)} \quad \dots (\because V_{in} = V_{\pi 1})$$

$$\therefore A_{V1} = -38.4615mA \times \frac{2.6k\Omega}{101}$$

$$\therefore A_{V1} = -0.9901 \approx 1$$

$$\text{For stage 2: } A_{V2} = \frac{V_{out}}{V_s}$$

$$V_{out} = -g_{m2} V_{\pi 2} (R_C \parallel R_L)$$

$$V_{o1} = -V_{\pi 2}$$

$$\therefore A_{V2} = \frac{-g_{m2} V_{\pi 2} (R_C \parallel R_L)}{-V_{\pi 2}} = g_{m2} (R_C \parallel R_L)$$

$$\therefore A_{V2} = (38.4615 \times 10^{-3})(3.3k\Omega \parallel 10k\Omega) = (38.4615 \times 10^{-3})(2.4812k\Omega)$$

$$\therefore A_{V2} = 95.4308$$

$$\therefore \text{Overall gain} = A_{Vt} = A_{V1} \times A_{V2}$$

$$\therefore A_{Vt} = (-1)(95.4308)$$

$$\therefore \mathbf{A_{Vt} = -95.4308}$$

$$A_{Vt} \text{ (in dB)} = 20 \log_{10}(95.4308) = \mathbf{39.5938}$$

Input impedance:

$$Z_i = R_2 \parallel R_3 \parallel r_{\pi 1} = 25k\Omega \parallel 14k\Omega \parallel 2.6k\Omega$$

$$\therefore \mathbf{Z_i = 2.0160k\Omega}$$

Output Impedance:

$$Z_o = R_C \parallel R_L = 3.3k\Omega \parallel 10k\Omega$$

$$\therefore \mathbf{Z_o = 2.4812k\Omega}$$

$$\text{Output Voltage} = V_{in} \times A_{Vt}$$

$$\therefore V_{out} = (10mV)(-95.4308)$$

$$\therefore V_{out} = -0.9543V$$

SIMULATED RESULTS:

Above circuit was simulated in LTspice and results obtained are as follows:

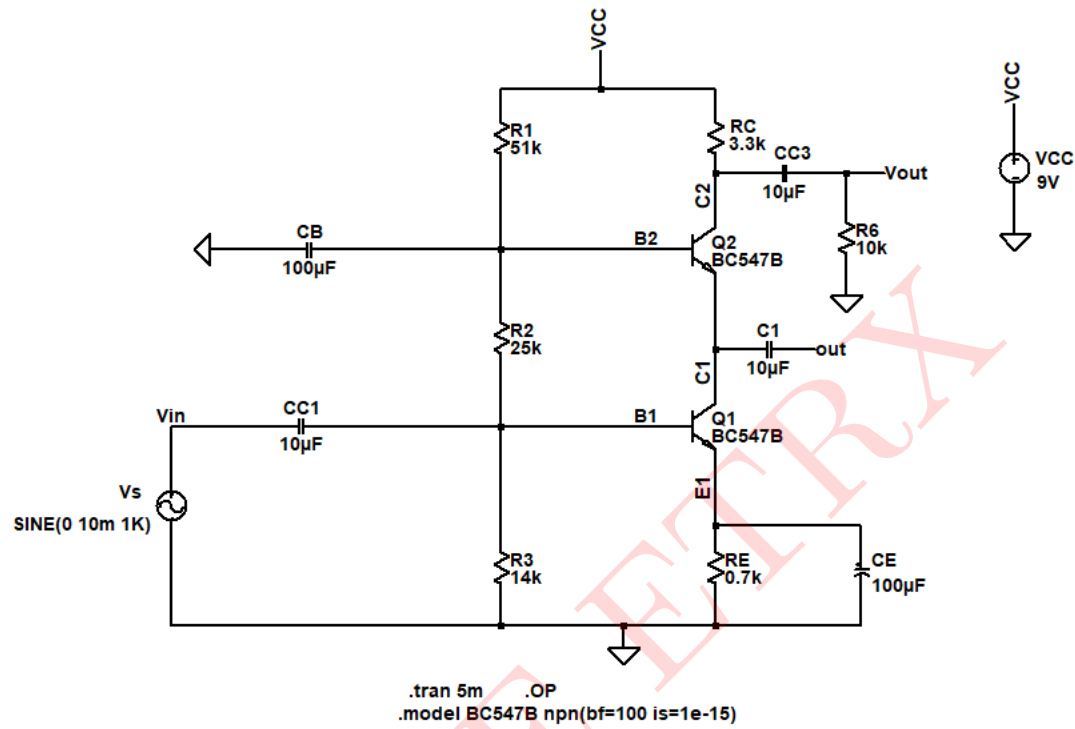


Figure 6: Circuit Schematic: Results

Input and output waveforms for each stage are shown below:

 


Figure 7: Input and output waveform for Stage 1

 


Figure 8: Input and output waveform for Stage 2

Comparison between theoretical and simulated values:

Parameter	Theoretical value	Simulated value
V_{B1}	1.4V	1.2493V
V_{C1}	3.2V	2.9046V
V_{E1}	0.7V	0.5415V
I_{C1}	1mA	0.7660mA
I_{B1}	$9.9\mu A$	$7.6596\mu A$
I_{E1}	1mA	0.7660 mA
V_{B2}	3.9V	3.67164V
V_{C2}	5.7V	6.4975V
V_{E2}	3.2V	2.9046V
I_{C2}	1mA	0.7660mA
I_{B2}	$9.9\mu A$	$7.5837\mu A$
I_{E2}	1mA	0.7660 mA
Voltage gain of stage 1: A_{V1}	-1	-0.996
Voltage gain of stage 2: A_{V2}	95.4308	72.075
Overall gain: A_{Vt} in dB	39.5938	37.1557
Input impedance of Stage 1	2.0160 k Ω	—
Output impedance of Stage 2	2.4812 k Ω	—
Output voltage	-0.9543V	-0.7207V

Table 1: Numerical 1

Numerical 2:

Consider CS-CG cascode amplifier as shown in figure 9. Let $k_{n1} = k_{n2} = 0.8mA/V^2$ & $V_{TN1} = V_{TN2} = 0.8V$; Determine:

- DC parameters of the circuits i.e. V_{G1} , V_{S1} , V_{D1} , V_{GS1} , I_{D1} , V_{G2} , V_{S2} , V_{D2} , V_{GS2} & I_{D2}
- Calculate input impedance of the circuit.
- Calculate output impedance of the circuit.
- Calculate voltage gain of the two stage circuit.

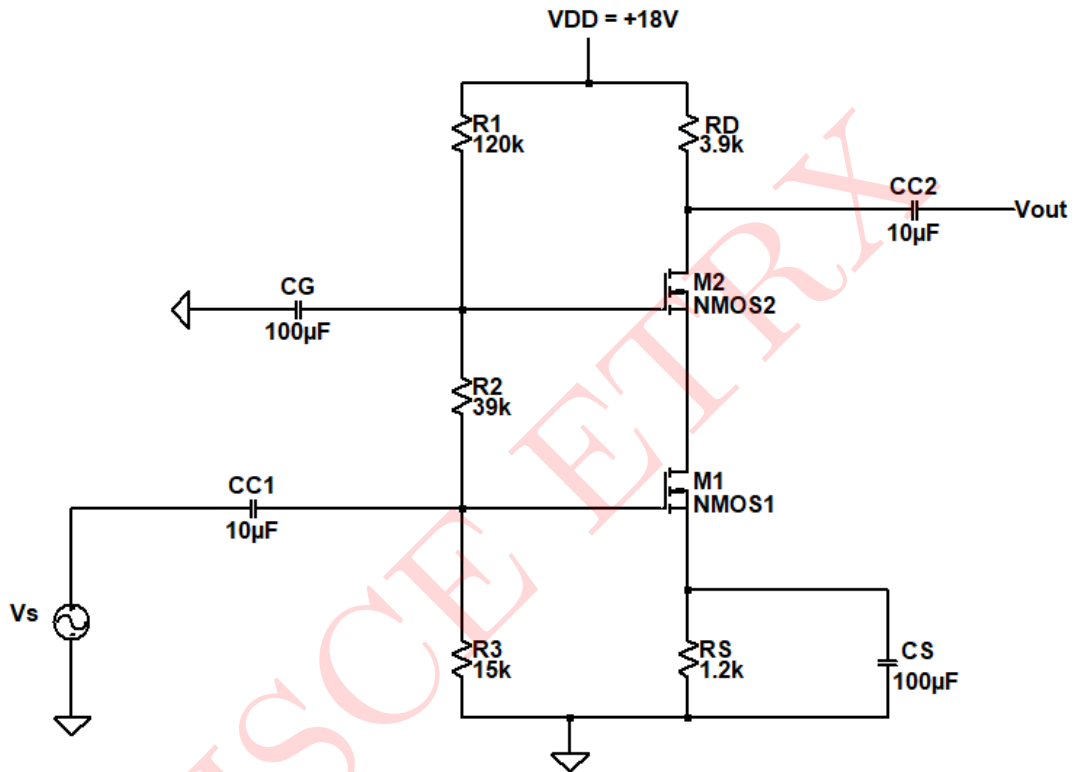


Figure 9: Circuit diagram

Solution: Circuit shown in figure 9 is a CS-CG cascode amplifier.

a. DC Analysis:

All capacitors are open circuited and DC equivalent circuit is shown in figure 10:

 


Figure 10: DC equivalent circuit

For stage 1:

 


Figure 11: Stage 1 DC equivalent circuit

$$V_{G1} = \frac{R_3}{R_1 + R_2 + R_3} \times V_{DD} = \frac{15k\Omega \times 18}{120k\Omega + 39k\Omega + 15k\Omega}$$

$$\therefore V_{G1} = 1.5517V$$

For Stage 2:

 


Figure 12: Stage 2 DC equivalent circuit

$$V_{G2} = \frac{R_2 + R_3}{R_1 + R_2 + R_3} \times V_{DD} = \frac{89k\Omega + 15k\Omega}{120k\Omega + 39k\Omega + 15k\Omega} \times 18$$

$$\therefore V_{G2} = 5.5862V$$

$$V_{GS1} = V_{G1} - V_{S1}$$

$$V_{S1} = R_S I_{D1} = (1.2k\Omega) I_{D1}$$

$$\therefore V_{GS1} = 1.5517 - (1.2k\Omega) I_{D1}$$

$$\therefore I_{D1} = \frac{1.5517 - V_{GS1}}{1.2k\Omega} \quad \dots(1)$$

$$\text{Assuming MOSFET in saturation, } I_{D1} = k_{n1}(V_{GS1} - V_{TN1})^2$$

$$\therefore k_{n1} = k_{n2} = k_n, V_{TN1} = V_{TN2} = V_{TN} \text{ and } V_{GS1} = V_{GS2} = V_{GS}$$

$$\therefore I_{D1} = (0.8 \times 10^{-3})[V_{GS} - 0.8]^2$$

$$\therefore \frac{1.5517 - V_{GS}}{1.2k\Omega} = (0.8 \times 10^{-3})[V_{GS} - 0.8]^2$$

$$1.5517 - V_{GS} = 0.96[V_{GS}^2 + 0.64 - 1.6V_{GS}]$$

$$1.5517 - V_{GS} = 0.96V_{GS}^2 + 0.6144 - 1.536V_{GS}$$

$$\therefore 0.96V_{GS}^2 - 0.586V_{GS} - 0.9373 = 0$$

$$\therefore V_{GS} = 1.3060V, -0.7464V$$

$$\text{Since } V_{GS} > V_{TN}$$

$$\therefore V_{GS} = 1.3060V$$

$$\text{Using (1), } I_{D1} = \frac{1.5517 - 1.3060}{1.2k\Omega}$$

$$\therefore \mathbf{I_{D1} = 0.20475mA}$$

$$\therefore \mathbf{I_{D1} \approx I_{D2} = 0.20475mA}$$

$$\therefore V_{S1} = I_D(R_S) = (0.20475mA)(1.2k\Omega)$$

$$\therefore \mathbf{V_{S1} = 0.2457V}$$

$$\text{Also, } V_{D2} = V_{DD} - I_{D2}R_D = 18 - (0.20475mA)(3.9k\Omega)$$

$$\therefore \mathbf{V_{D2} = 17.2015V}$$

$$V_{GS2} = V_{G2} - V_{S2}$$

$$\therefore V_{S2} = V_{G2} - V_{GS2}$$

$$V_{S2} = 5.5862 - 1.3060$$

$$\mathbf{V_{S2} = 4.2802V}$$

$$\text{Also, } \mathbf{V_{S2} = V_{D1} = 4.2802V}$$

$$\therefore V_{DS1} = V_{D1} - V_{S1} = 4.2802 - 0.2457$$

$$\therefore \mathbf{V_{DS1} = 4.0345V}$$

$$\therefore V_{DS2} = V_{D2} - V_{S2} = 17.2015 - 4.0802$$

$$\therefore \mathbf{V_{DS2} = 12.9213V}$$

Small signal parameters:

$$g_{m1} = g_{m2} = g_m$$

$$g_m = 2k_n[V_{GS} - V_{TN}]$$

$$g_m = 2(0.8 \times 10^{-3})[1.3060 - 0.8]$$

$$g_m = 1.6 \times 10^{-3}[1.3060 - 0.8]$$

$$\therefore \mathbf{g_m = 0.8096mA/V}$$

Small signal equivalent circuit is shown in figure 13:

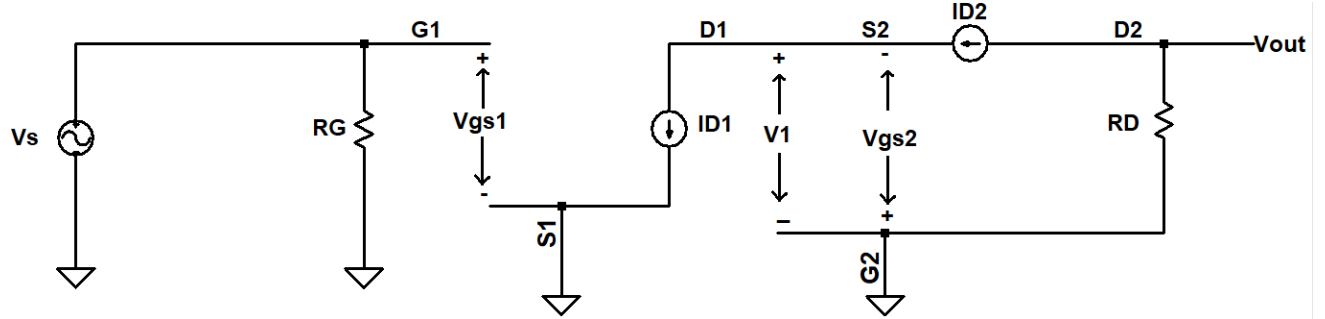


Figure 13: Small signal equivalent circuit

b. Input Impedance:

$$Z_i = R_G = R_2 \parallel R_3$$

$$\mathbf{Z_i = 10.833k\Omega}$$

c. Output Impedance:

$$Z_o = R_o = \mathbf{3.9k\Omega}$$

d. Voltage gain for stage 1, $A_{V1} = \frac{V_1}{V_s}$

$$\therefore V_1 = -V_{gs2}$$

$$\text{Also, } V_s = V_{gs1}$$

$$\therefore A_{V1} = \frac{-V_{gs2}}{V_{gs1}} = -1 \quad \dots (\because V_{gs1} = V_{gs2})$$

$$\therefore \mathbf{A_{V1} = -1}$$

Voltage gain for stage 2, $A_{V2} = \frac{V_{out}}{V_1}$

$$\therefore V_{out} = -g_{m2}R_D V_{gs2}$$

$$\therefore V_1 = V_{gs2}$$

$$\therefore A_{V2} = \frac{-g_{m2}V_{gs2}R_D}{-V_{gs2}}$$

$$\therefore A_{V2} = g_{m2}R_D$$

$$\therefore A_{V2} = (0.8069 \times 10^{-3})(3.9k\Omega)$$

$$\therefore \mathbf{A_{V2} = 3.1574}$$

Overall gain, $A_{Vt} = A_{V1} \times A_{V2}$

$$\therefore A_{Vt} = (-1) \times 3.1574$$

$$\therefore A_{Vt} = -3.1574$$

$$A_{Vt} \text{ (in dB)} = 20\log_{10}(3.1574) = 9.9866$$

Output voltage, $V_o = V_{in} \times A_{Vt}$

$$\therefore V_o = (10mV)(-3.1574)$$

$$V_o = -31.574V$$

Negative sign indicates that the output voltage is 180° out of phase with respect to input voltage.

SIMULATED RESULTS:

Above circuit was simulated in LTspice and results obtained are as follows:

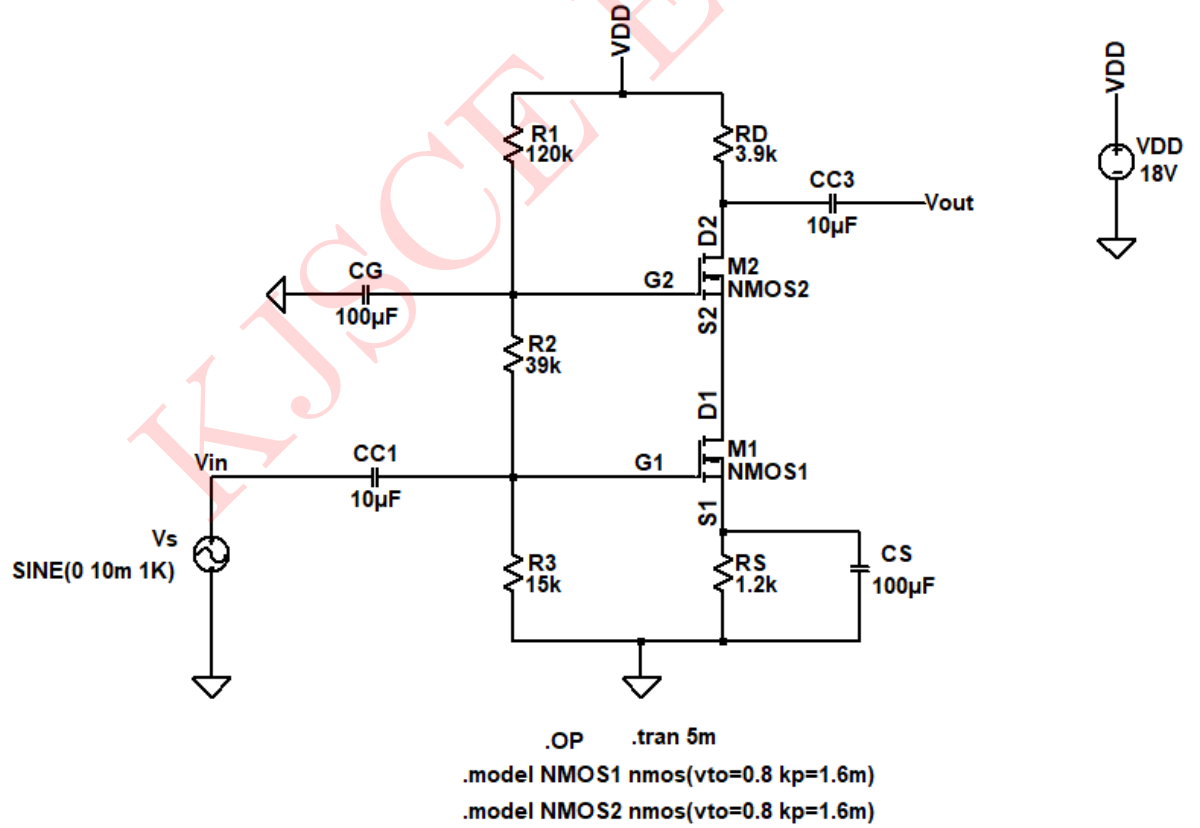


Figure 14: Circuit Schematic: Results

Input and output waveforms for each stage are shown below:

 


Figure 15: Input and output waveform for Stage 1

 


Figure 16: Input and output waveform for Stage 2

Comparsion between theoretical and simulated values:

Parameter	Theoretical value	Simulated value
V_{G1}	1.5517V	1.5517V
V_{D1}	4.2802V	4.2802V
V_{S1}	0.2457V	0.2458V
I_{D1}	0.2048mA	0.2048mA
V_{G2}	5.5862V	5.5862V
V_{D2}	17.2015V	17.2015V
V_{S2}	4.2802V	4.2802V
I_{D2}	0.2048mA	0.2048mA
Voltage gain of stage 1: A_{V1}	-1	-0.9916
Voltage gain of stage 2: A_{V2}	3.1574	3.1510
Overall gain: A_{Vt} in dB	9.9866	9.9690
Input impedance of Stage 1	10.833 k Ω	—
Output impedance of Stage 2	3.9k k Ω	—
Output voltage	-31.574mV	-31.5100mV

Table 2: Numerical 2