

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Oscillator Circuits**

Q1. Design a RC Phase shift oscillator to oscillator at 900Hz supply voltage is 10V:

**Solution:**

**1) Select transistor BC 147A:**

$h_{fe(type)} = 220$ ,  $V_{CE(sat)} = 0.25V$ ,  $\beta = 180$

**Design Specifications-**  
**Oscillation Frequency = 900Hz**  
**VCC = +10V**

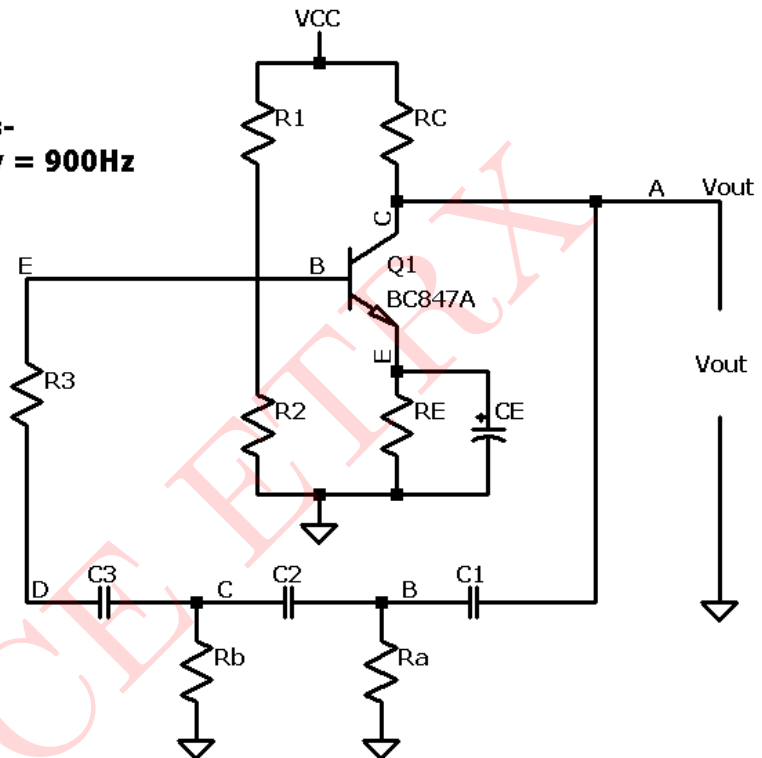


Figure 1: Self biased Circuit 1

**2) Selection of R and C:**

For RC shift oscillator

$$f = \frac{1}{2\pi RC} \times \frac{1}{\sqrt{6 + 4k}}$$

Minimum value of k is 2.7

$$900 = \frac{1}{2\pi RC} \times \frac{1}{\sqrt{6 + 4k}}$$

$$RC = 43.1451 \mu A$$

let  $C = 0.01 \mu F$

$$R = \frac{43.1451 \times 10^{-6}}{0.01 \times 10^{-6}} = 4.314 k\Omega$$

Select  $R = 4.7 k\Omega$ , 1/4 W ( H.S.V )

**3) Selection of  $R_C$ :**

$$k = \frac{R_C}{R} \quad R_C = 2.7 \times 4.7k = 12.690k\Omega$$

Select  $R_C = 15k\Omega$ , 1/4 W ( H.S.V )

**4) Selection of  $R_E$ :**

$$V_{RE} = 0.1V_{CC} = 10 \times 0.1$$

$$V_{RE} = 1V \text{ (For good stability)}$$

For maximum symmetrical o/p voltage swing, select Q point at centre of DC load line

$$V_{CEQ} = 5V$$

$$I_{CQ} = \frac{V_{CC} - V_{CE} - V_{RE}}{R_C} = \frac{10 - 6}{15k}$$

$$I_{CQ} = 0.2667mA$$

$$I_{CQ} = \alpha I_{EQ}$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{180}{181} = 0.994$$

$$I_{EQ} = I_{CQ}/\alpha = 0.2667mA/0.994 = 0.2683mA$$

$$V_{RE} = I_{EQ}R_E$$

$$R_E = \frac{V_{RE}}{I_{EQ}} = 1/0.26683mA = 3.72k$$

Select  $R_E = 3.3\Omega$ , 1/4 W ( H.S.V )

**5) Selection of  $R_1$  and  $R_2$ :**

$$S = \frac{1 + \beta}{1 + \beta \left( \frac{R_E}{R_E + R_B} \right)}$$

$$8 = \frac{1 + 180}{1 + 180 \left( \frac{3.3k}{3.3k + R_B} \right)}$$

$$R_B = 24.177k\Omega \text{ ——— ( 1 )}$$

KVL at B-E loop

$$V_B - I_{BQ}R_B - V_{BE} - I_{EQ}R_E = 0$$

$$V_B = I_{CQ}R_B/\beta + V_{BE} + I_{CQ}R_E$$

$$V_B = 124.177k \times 2.667m/180 + 0.7 + (0.2683m \times 3.3k$$

$$V_B = 1.6212 \text{ Now from ( 2 )}$$

$$1.6212 = \frac{R_2}{R_1 + R_2} V_{CC} \text{ ——— ( 2 )}$$

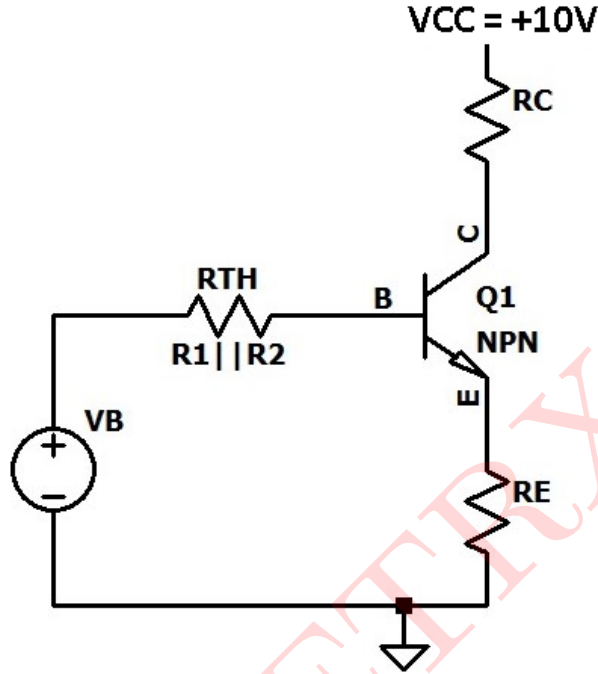


Figure 2: DC equivalent circuit

$$\frac{R_2}{R_1 + R_2} = 1.6212 \quad \text{--- ( 3 )}$$

Solving equations ( 3 ) and ( 1 )

$$R_1(1.6212) = 24.177k$$

$$R_1 = 149.86k\Omega$$

Select  $R_1 = 150k\Omega$ , 1/4 W ( H.S.V )

From ( 3 )

$$\frac{R_2}{150k + R_2} = 1.6212$$

$$R_2 = 29.023k\Omega$$

Select  $R_2 = 27k\Omega$ , 1/4 W ( H.S.V )

#### 6) Selection of $C_E$ :

$$X_{CE} \leq 0.1R_E$$

$$C_E = \frac{1}{2\pi \times f_{LCS} 0.1R_E}$$

$$C_E = \frac{1}{2\pi \times 0.1 \times 900 \times 3.3k} = 0.5358\mu F$$

Select  $C_E = 1\mu F$ , 50V ( H.S.V )

**7) Selection of  $R_3$  in  $R_C$  selection:**

To avoid loading effect of input impedance of BJT towards third ( $R_3$ ) in RC section

$$R_i = R_1 || R_2 || R_\pi = 2.415k\Omega$$

$$R_3 = R + R_i = 4.7k + 2.415k = 7.115k\Omega$$

Select  $R_3 = 7.115k\Omega$ , 1/4 W ( H.S.V )

**8) Designed Circuit is:**

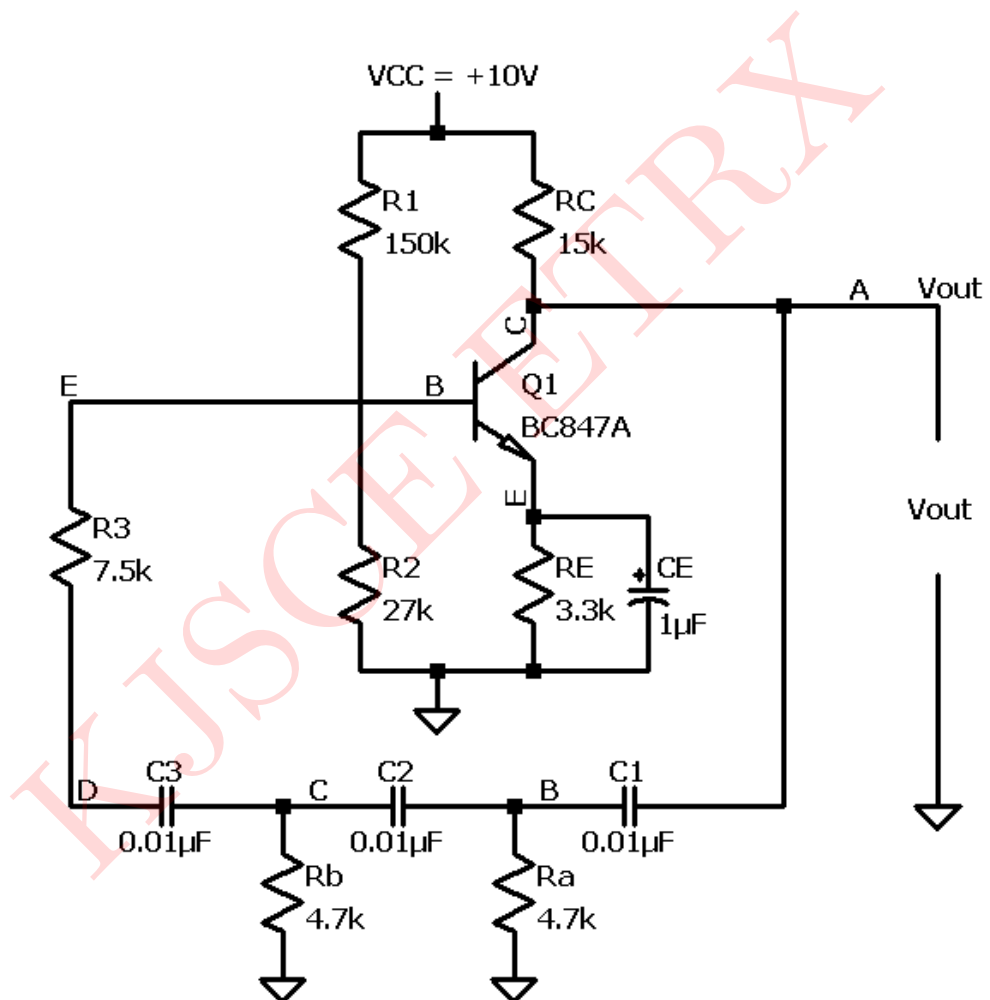


Figure 3: Designed circuit 1

## SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

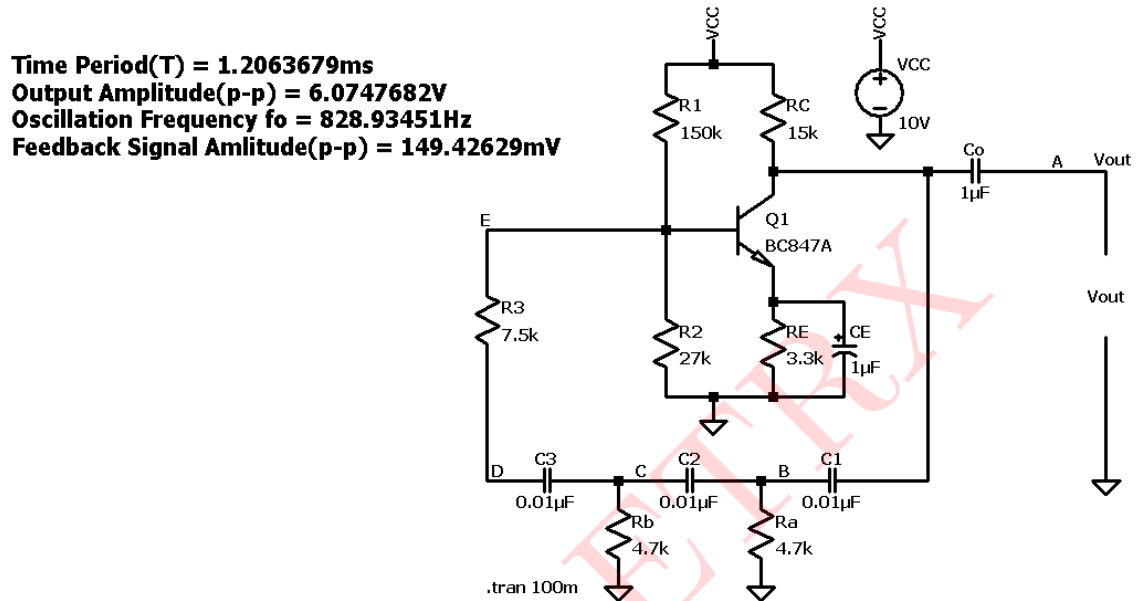


Figure 4: Circuit schematic 1

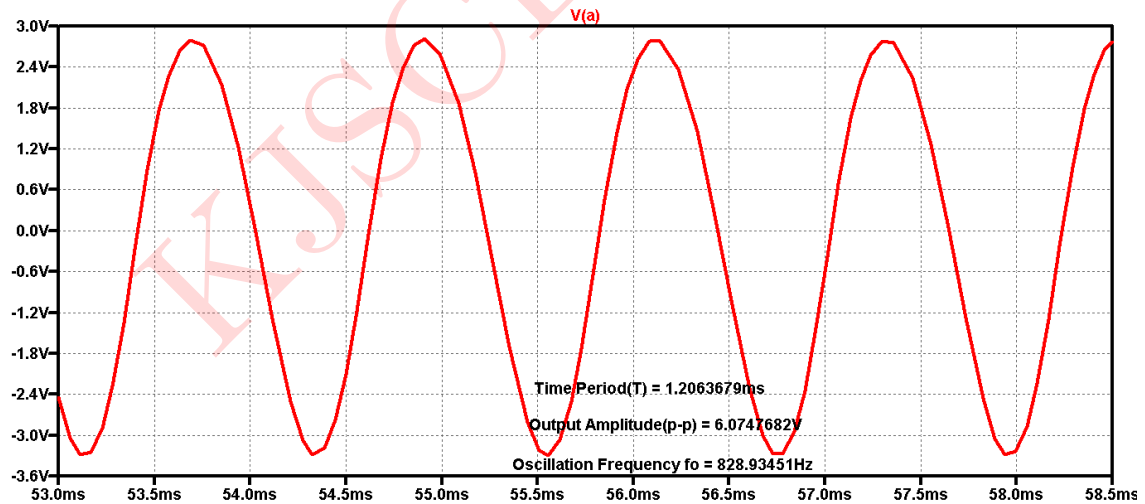


Figure 5: Expanded view of output waveforms

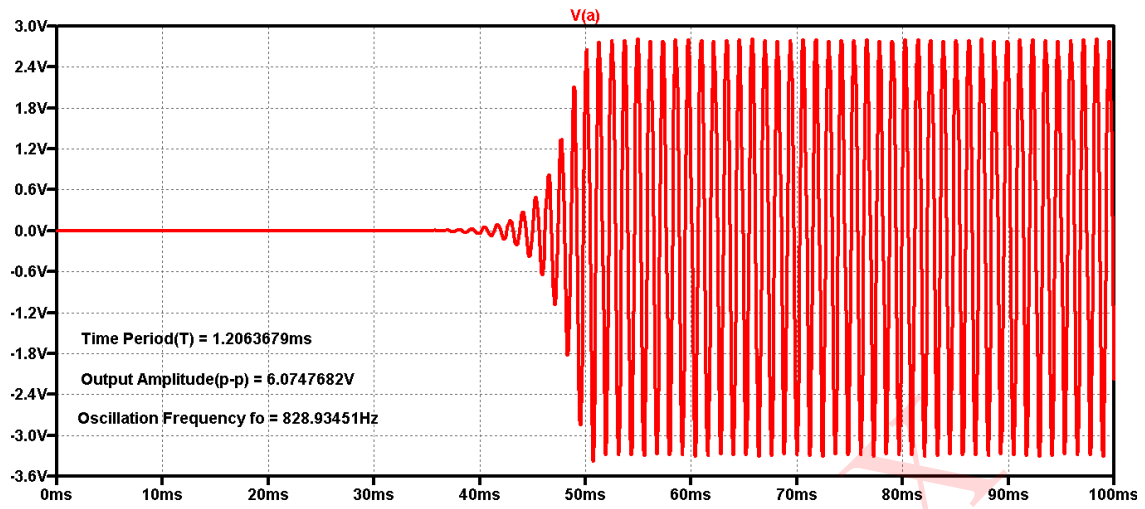


Figure 6: Output voltage Waveform

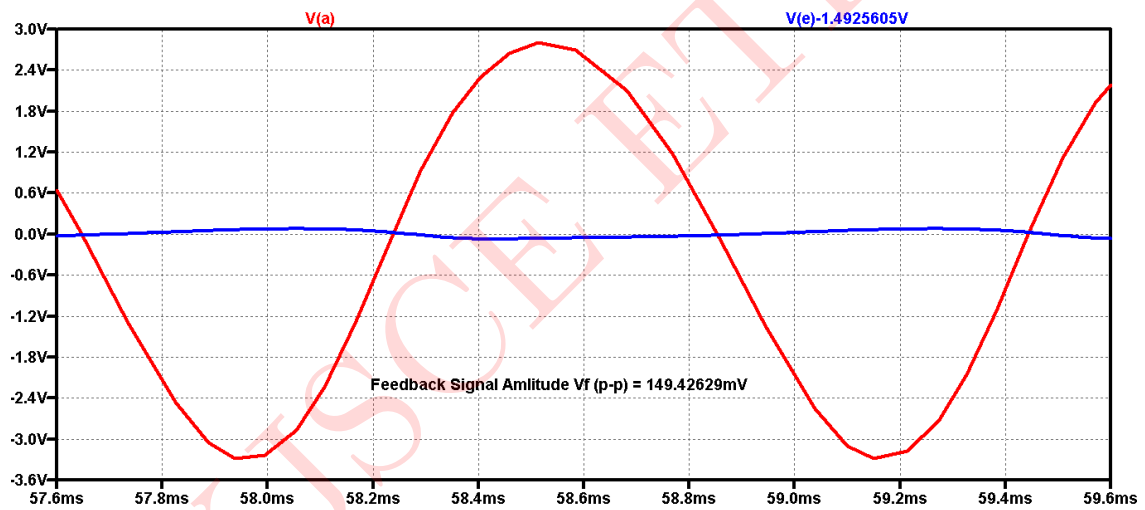


Figure 7: Output and feedback voltage Waveform

**Comparsion between Simulated and theoretical values :**

Parameters	Simulated	Theoretical
Frequency of oscillation	828.93451Hz	900Hz
Times period	1.206367ms	1.1111ms
Amplitude of output	6.074768V	—
Peak to Peak feedback signal	149.4263mA	—
Feedback fraction	0.024	0.0344
Phase shift offered by feedback network	180°	180°

Table 1: Numerical 1