

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**EEEE**

**Numerical 1:** Simulate a half wave rectifier circuit with input amplitude = 180V peak,  $f = 50\text{Hz}$ ,  $R_1 = 80$  using LTspice select diode as 1N4148 use 10:1 stepdown Transformer plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across the resistor
- Output voltage across diode
- Current flowing through the circuit

Also calculate the efficiency of the half wave rectifier circuit.

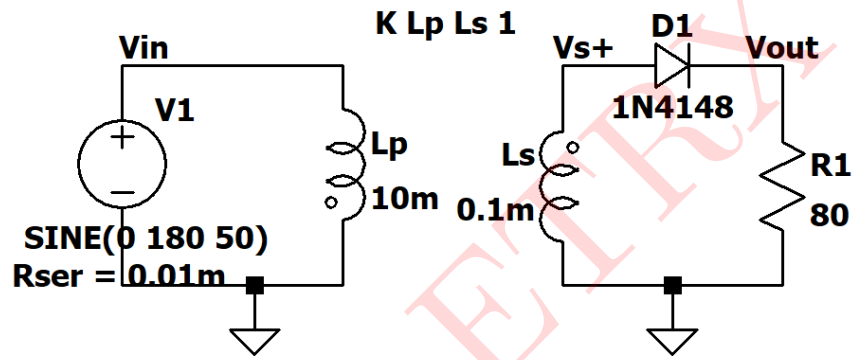


Figure 1: Circuit 1

**Solution:**

$$I_m = \frac{V_m}{R_1}$$

$$\text{Since, } V_m = \frac{180}{10} = 18V$$

$$\therefore I_m = \frac{18}{80} = 0.225A$$

$$DC_{power} = P_{dc} = \frac{I_m^2}{\pi^2} \times R_1$$

$$DC_{power} = \frac{V_m^2}{\pi^2 \times R_1} = 0.41035W \dots (I_m = \frac{V_m}{R_1})$$

$$AC_{power} = P_{ac} = \frac{V_m^2}{4(R_1 + R_s)}$$

$$AC_{power} = \frac{18^2}{320.04} = 1.01237W$$

$$\text{Efficiency } (\eta) = \frac{P_{dc}}{P_{ac}} \times 100$$

$$\eta = \frac{0.41035}{1.01237} \times 100$$

$$\therefore \eta = 40.5336\%$$

$$\text{Peak inverse voltage(PIV)} = -V_m = -18V$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

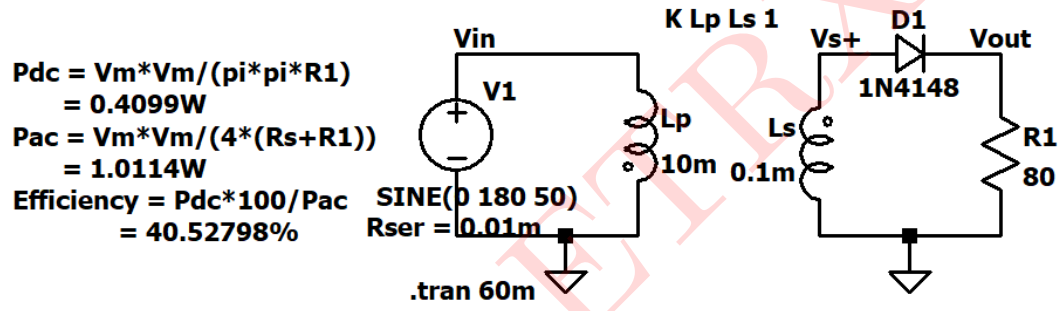


Figure 2: Circuit Schematic and simulated results

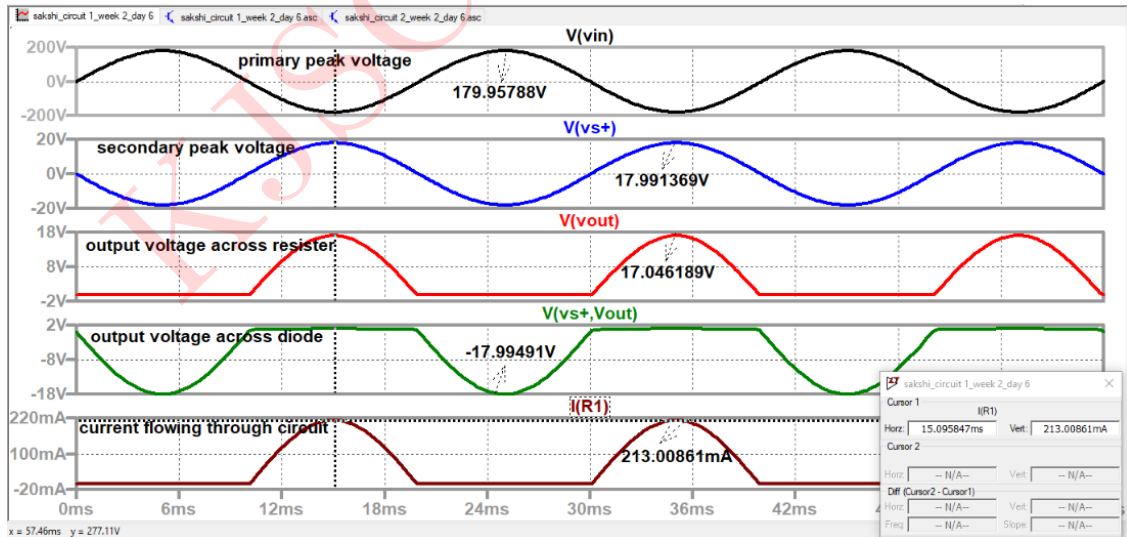


Figure 3: Plots in LTspice

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Input peak voltage $V_m$	18V	17.046189V
Output peak voltage $I_m$	0.22A	0.2130086A
$AC_{power}$	1.01237W	1.0114W
$DC_{power}$	0.41035W	0.4099W
Efficiency	40.5336%	40.52798%
PIV rating	-18V	-17.99491V

KJSCE ETRX

**Numerical 2:** Simulate a full wave rectifier circuit with input amplitude = 150V peak,  $f = 50\text{Hz}$ ,  $R_1 = 60$  using LTspice select diode as 1N4148 use 10:1 stepdown

Transformer plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across the resistor
- Output voltage across diode
- Current flowing through the diode
- Current flowing through the circuit

Also find the efficiency of the full wave centre tapped rectifier circuit.

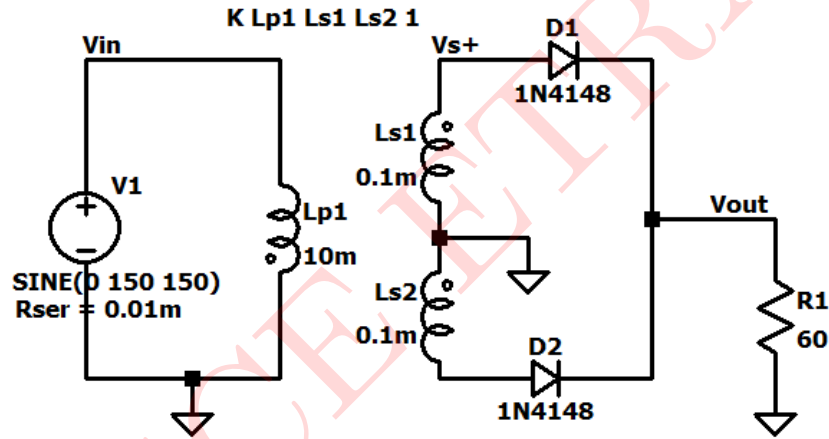


Figure 4: Circuit 2

**Solution:**

$$I_m = \frac{V_m}{R_1}$$

$$\text{Since, } V_m = \frac{150}{10} = 15V$$

$$\therefore I_m = \frac{15}{60} = 0.25A$$

$$DC_{power} = P_{dc} = \frac{2I_m^2}{\pi^2} \times R_1$$

$$DC_{power} = \frac{0.25^2 \times 4 \times 60}{\pi^2} = 1.51981775W$$

$$AC_{power} = P_{ac} = \frac{I_m^2(R_1 + R_s)}{2}$$

$$P_{ac} = \frac{0.25^2(60 + 0.01)}{2} = 1.8753125W$$

$$\text{Efficiency } (\eta) = \frac{P_{dc}}{P_{ac}} \times 100$$

$$\eta = \frac{1.51981775}{1.8753125} \times 100$$

$$\therefore \eta = 81.04344\%$$

$$\text{Peak inverse voltage(PIV)} = -2 \times V_m = -2 \times 15 = -30V$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

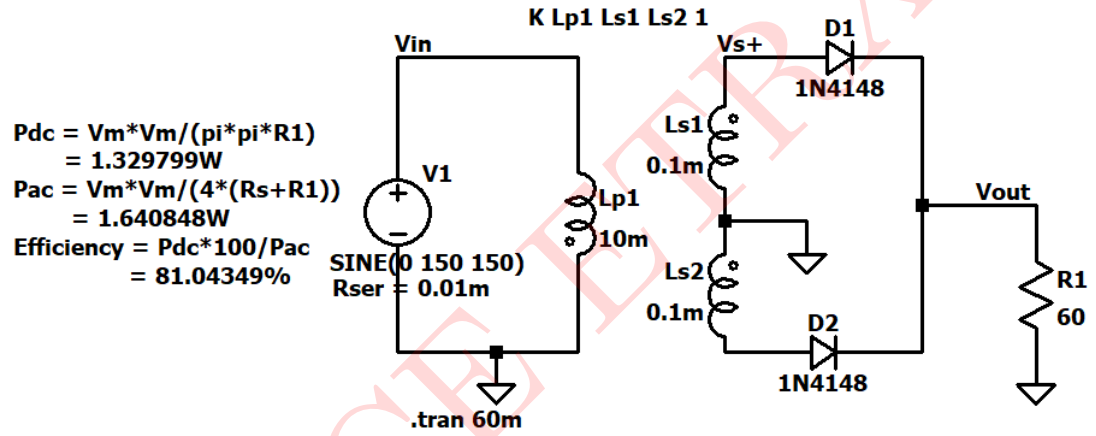


Figure 5: Circuit Schematic and simulated results

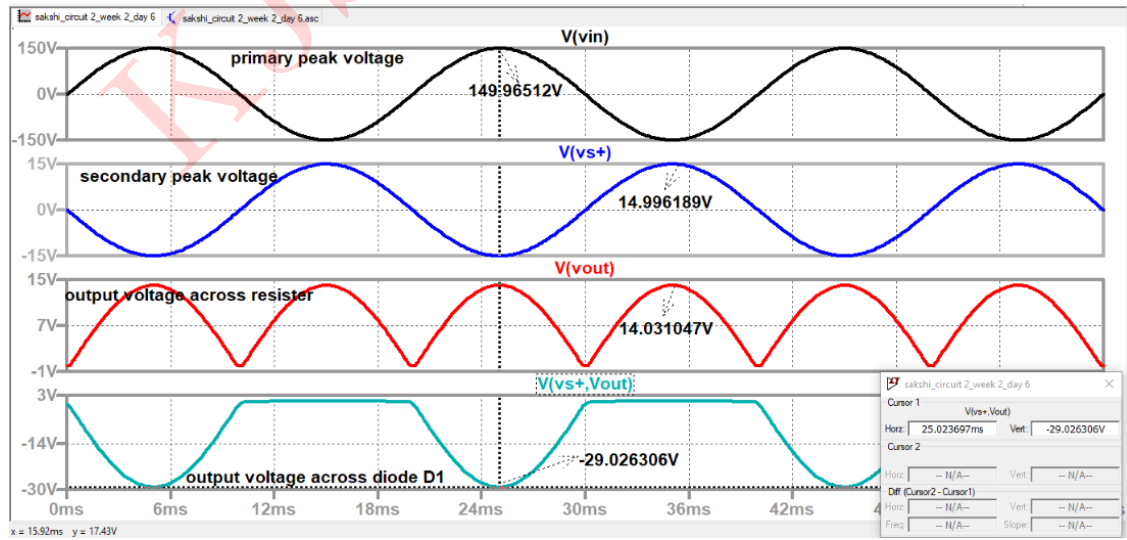


Figure 6: Plots in LTspice(i)

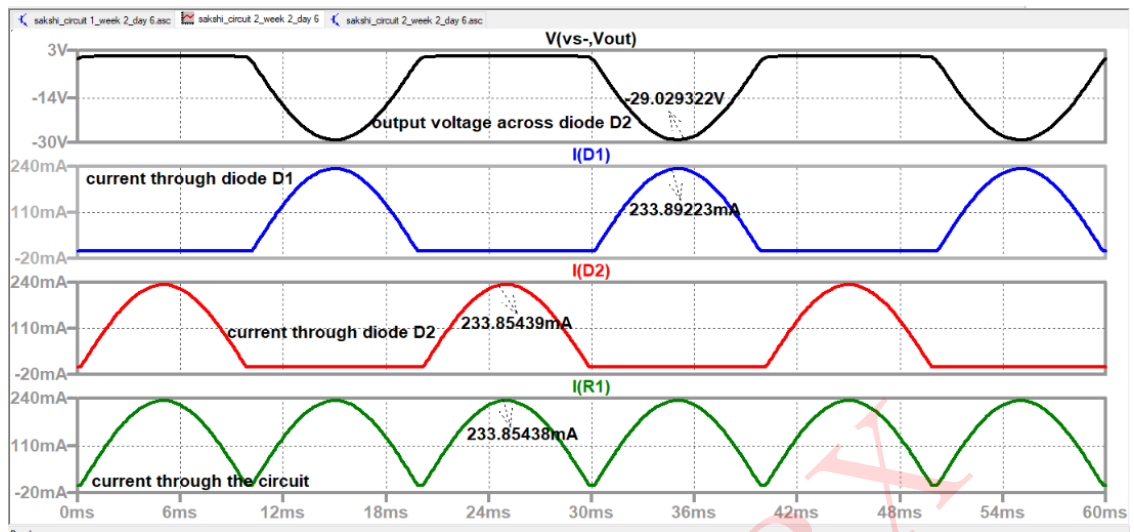


Figure 7: Plots in LTspice(ii)

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Input peak voltage $V_m$	15V	14.031047V
Output peak voltage $I_m$	0.25A	0.23385A
$AC_{power}$	1.8753125W	1.640848W
$DC_{power}$	1.519817W	1.329799W
Efficiency	81.04344%	81.04349%
PIV rating	-30V	-29.029322V

\*\*\*\*\*