

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Oscillator Circuits

Numerical 1:

In a Hartley oscillator, amplifier components are $R_1 = 100k\Omega$, $R_2 = 18k\Omega$, $R_C = 12k\Omega$, $R_E = 1k\Omega$, $C_{C1} = 1\mu F$, $C_E = 1\mu F$, $C_{C2} = 1\mu F$, $V_{CC} = 10V$. Select the LC tank circuit elements such that frequency of oscillation is close to 225kHz. BJT transistor: 2N2222

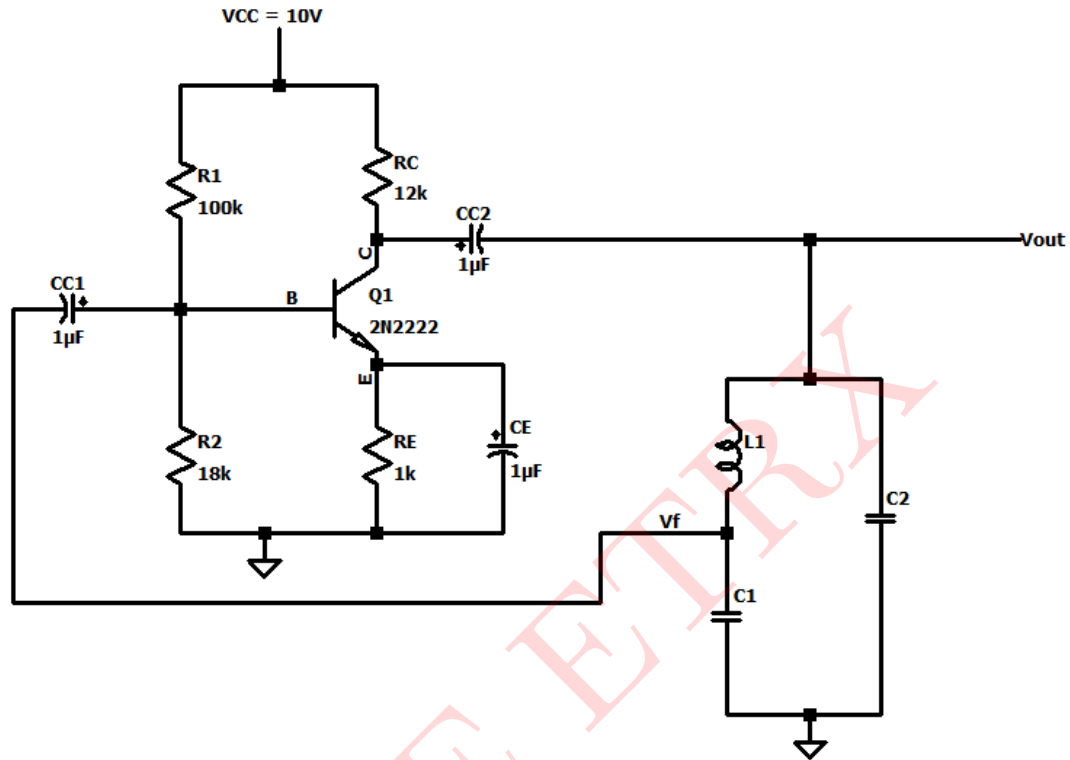


Figure 1: Circuit 1

Solution:

Frequency of oscillation,

$$f_o = \frac{1}{2\pi\sqrt{L_{eq}C_1}}$$

$$225kHz = \frac{1}{2\pi\sqrt{L_{eq}C_1}}$$

$$225kHz \times 2\pi = \frac{1}{\sqrt{L_{eq}C_1}}$$

$$\text{Let } C_1 = 47nF$$

$$225kHz \times 2\pi \times \sqrt{47nF} = \frac{1}{\sqrt{L_{eq}}}$$

$$306.331 = \frac{1}{\sqrt{L_{eq}}}$$

$$\therefore \sqrt{L_{eq}} = \frac{1}{306.331}$$

$$\sqrt{L_{eq}} = 3.264 \times 10^{-3}$$

$$\therefore L_{eq} = \mathbf{10.656\mu H}$$

$$\therefore L_{eq} = L_1 + L_2 + 2M$$

Where M is the mutual inductance and $M = 0$, if both the inductors (L_1 and L_2) are not wound on the same core.

$$\therefore L_{eq} = L_1 + L_2$$

$$\therefore L_{eq} = L_1 + L_1 \quad (\because L_1 = L_2)$$

$$\therefore L_{eq} = 2L_1$$

$$\therefore 10.656\mu F = 2L_1$$

$$\therefore L_1 = \mathbf{5.328\mu F}$$

$$\therefore L_1 = L_2$$

$$\therefore L_2 = \mathbf{5.328\mu F}$$

k(feedback fraction) of LC tank circuit,

$$k = \frac{V_f}{V_o}$$

$$k = \frac{L_2}{L_1}$$

$$= \frac{5.328\mu F}{5.328\mu F} = \mathbf{1}$$

\therefore Phase shift offered by LC tank circuit is 180°

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

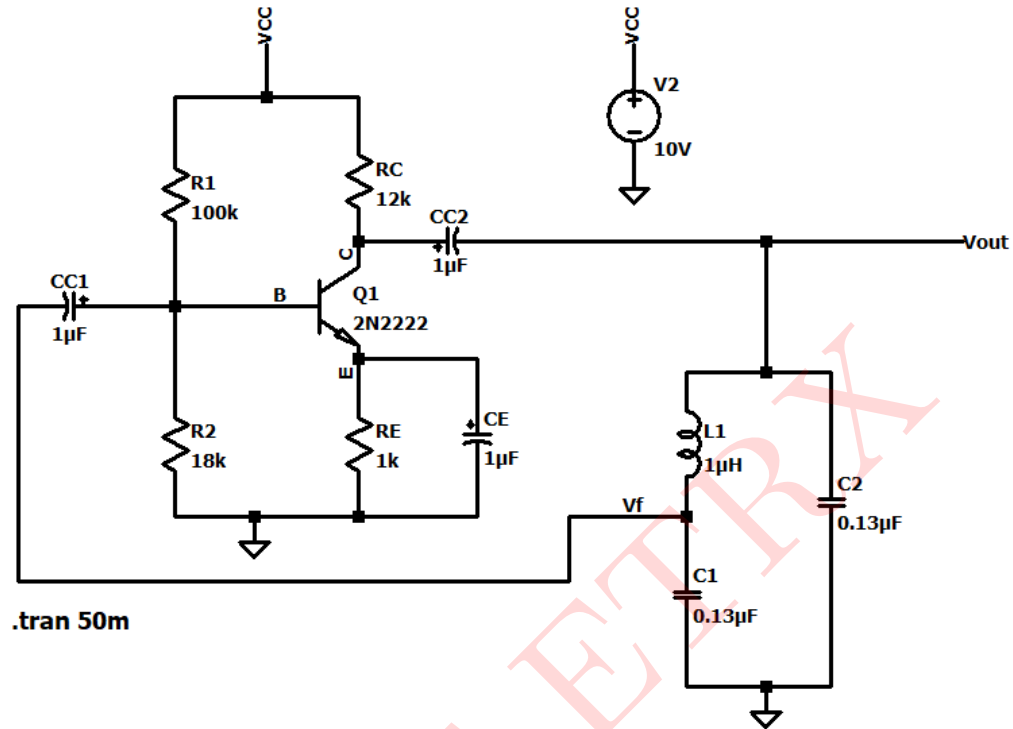


Figure 2: Circuit Schematic 1

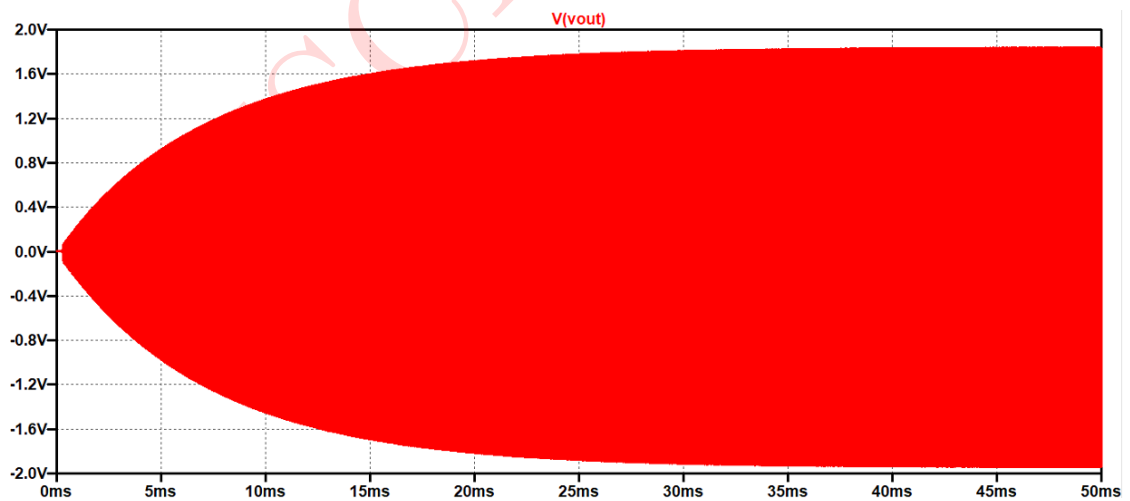


Figure 3: Output wave before zooming in

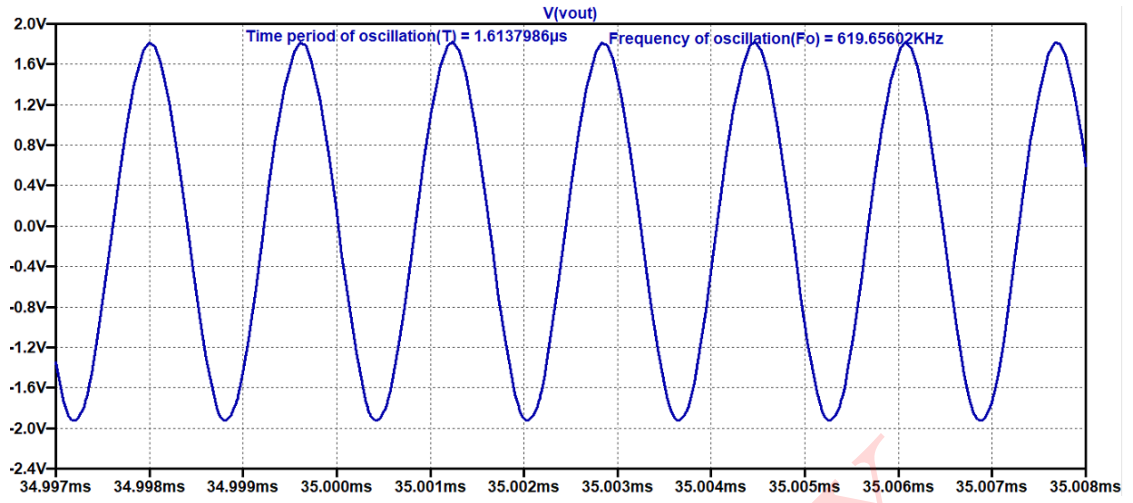


Figure 4: Output wave after zooming in

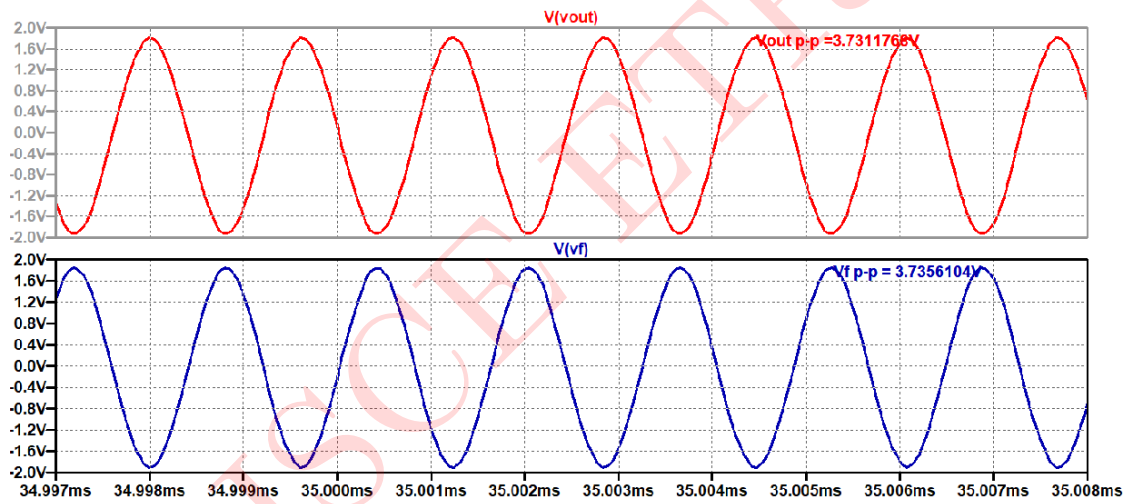


Figure 5: Peak to peak values of V_{out} and V_f

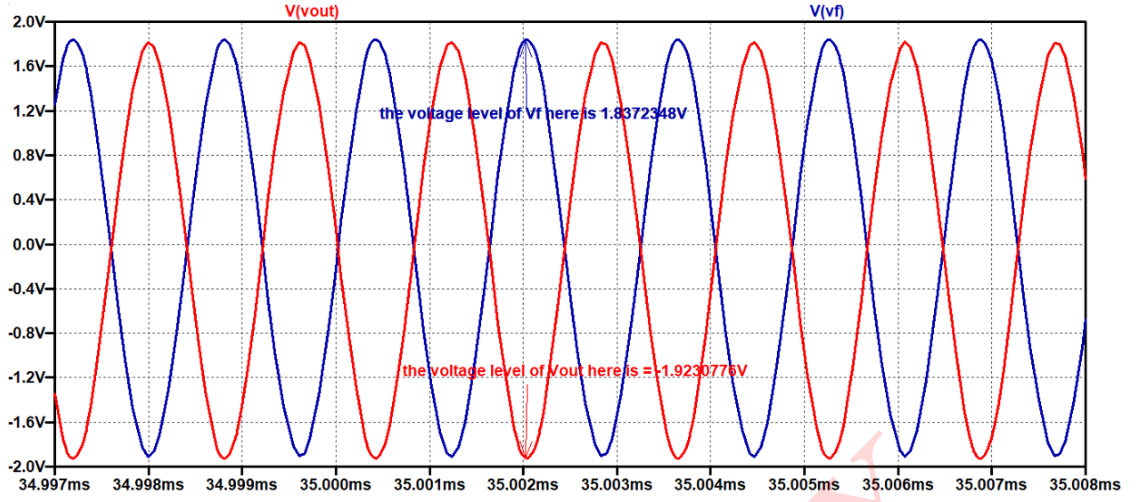


Figure 6: Phase difference between V_{out} and V_f

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
Frequency of oscillations(f_o)	225kHz	224.5370kHz
Timeperiod of oscillations(T)	4.44 μ s	4.4750 μ s
Amplitude of oscillations	—	5.4247V
Feedback signal VF amplitude and phase w.r.t V_{out}	—	5.3801V, 180°
Feedback fraction in dB	1	0.9917
Phase shift offered by LC tank circuit	180°	180°

Table 1: Numerical 1

Numerical 2:

In a Colpitts oscillator, amplifier components are $R_1 = 100k\Omega$, $R_2 = 18k\Omega$, $R_C = 12k\Omega$, $R_E = 1k\Omega$, $C_{C1} = 1\mu F$, $C_{C2} = 1\mu F$, $V_{CC} = 10V$. Select the LC tank circuit elements such that frequency of oscillation is close to 620kHz. BJT transistor: 2N2222
Comment on phase shift offered by LC tank circuit.

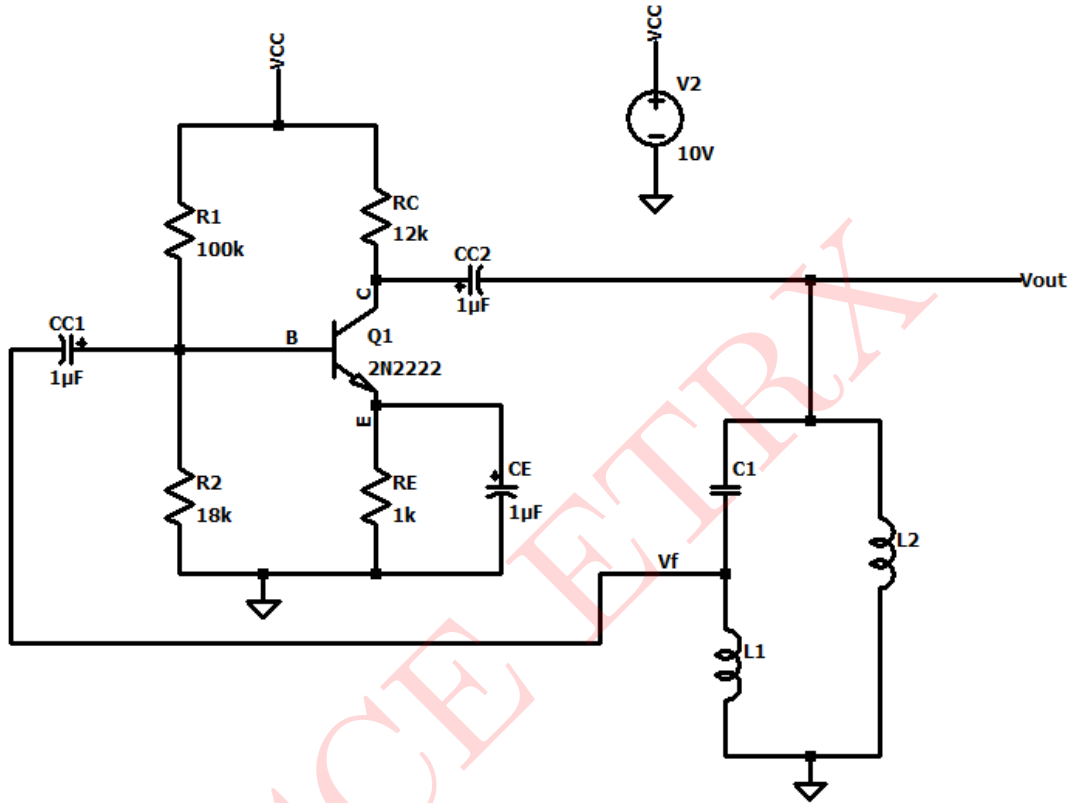


Figure 7: Circuit 2

Solution:

Frequency of oscillation,

$$f_o = \frac{1}{2\pi\sqrt{L_1 C_{eq}}}$$

$$620kHz = \frac{1}{2\pi\sqrt{L_1 C_{eq}}}$$

$$620kHz \times 2\pi = \frac{1}{\sqrt{L_1 C_{eq}}}$$

$$\text{Let } L_1 = 1\mu H$$

$$620kHz \times 2\pi \times \sqrt{1\mu H} = \frac{1}{\sqrt{C_{eq}}}$$

$$3893.6 = \frac{1}{\sqrt{C_{eq}}}$$

$$\therefore \sqrt{C_{eq}} = \frac{1}{3893.6}$$

$$\sqrt{C_{eq}} = 2.56 \times 10^{-4}$$

$$\therefore C_{eq} = \mathbf{65.96nF}$$

$$\because C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$\therefore \frac{C_1 C_2}{C_1 + C_2} = 65.96nF$$

$$\therefore \frac{C_1 C_1}{C_1 + C_1} = 65.96nF \quad (\because C_1 = C_2)$$

$$\therefore \frac{C_1^2}{2C_1} = 65.96nF$$

$$\therefore C_1 = 2 \times 65.96nF$$

$$\therefore C_1 = \mathbf{0.13\mu F}$$

$$\because C_1 = C_2$$

$$\therefore C_2 = \mathbf{0.13\mu F}$$

$$\begin{aligned} \text{Time period of oscillations}(T) &= \frac{1}{\text{frequency of oscillation}(f_o)} \\ &= \frac{1}{620kHz} = \mathbf{1.61\mu s} \end{aligned}$$

k(feedback fraction) of LC tank circuit,

$$k = \frac{V_f}{V_o}$$

$$k = \frac{C_1}{C_2}$$

$$= \frac{0.13\mu F}{0.13\mu F} = \mathbf{1}$$

\therefore Phase shift offered by LC tank circuit is 180°

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

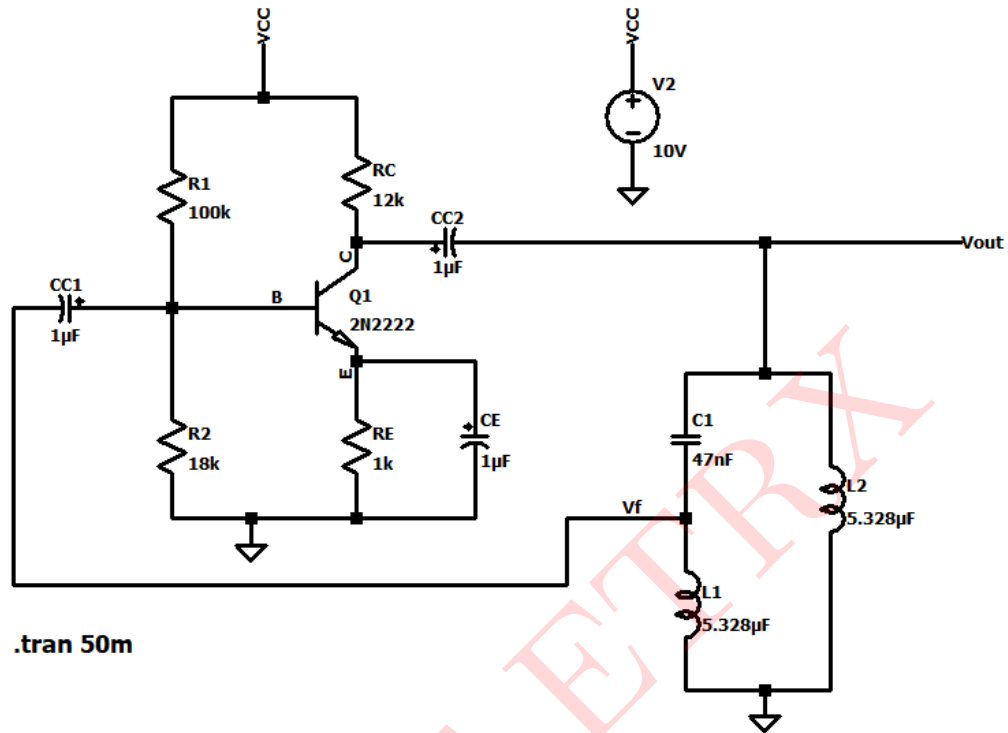


Figure 8: Circuit Schematic

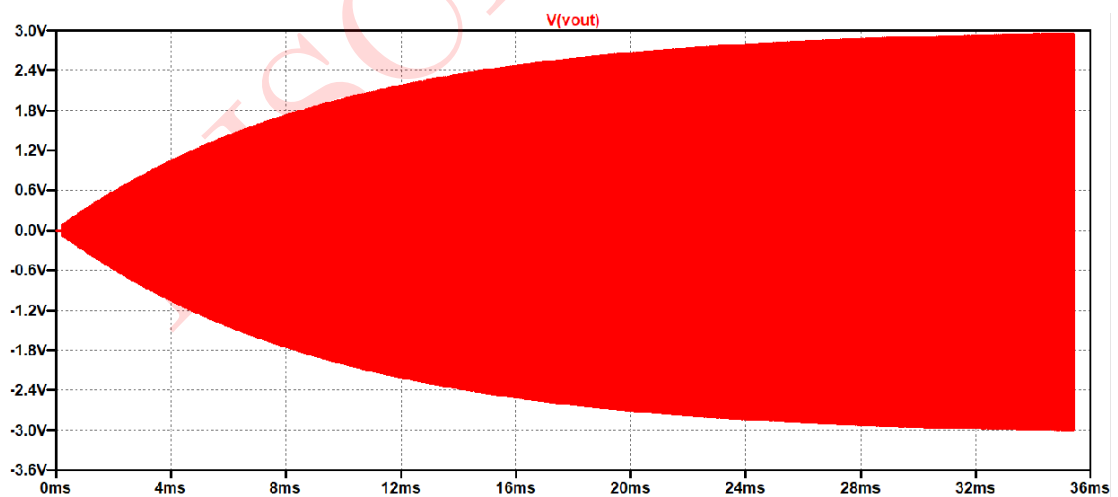


Figure 9: Output wave before zooming in

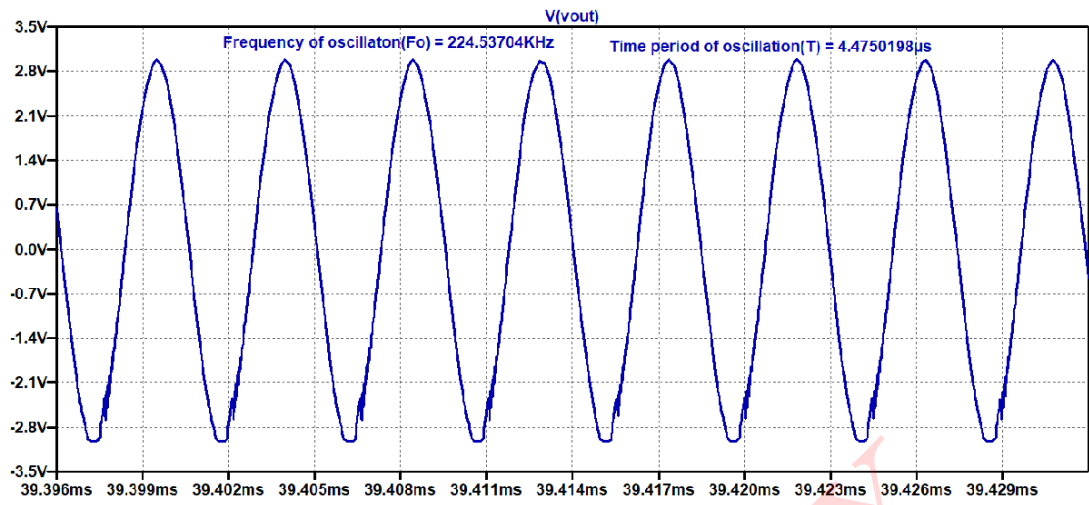


Figure 10: Output wave after zooming in

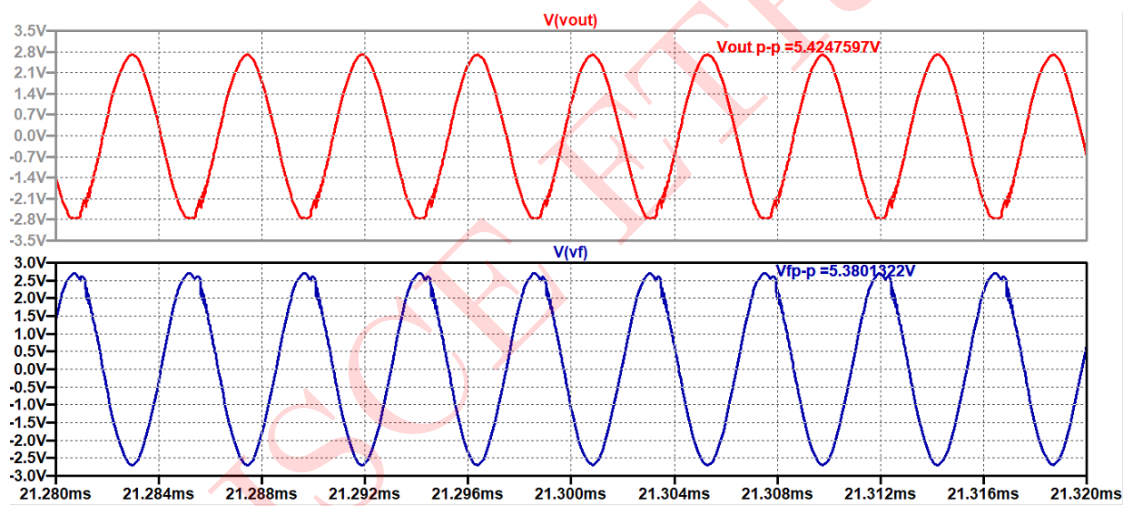


Figure 11: Peak to peak values of V_{out} and V_f

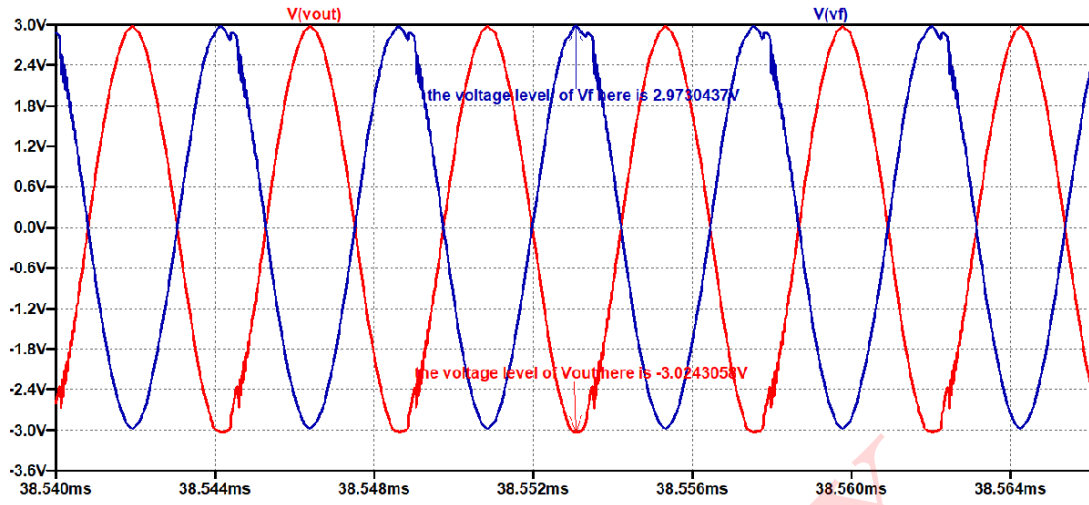


Figure 12: Phase difference between V_{out} and V_f

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
Frequency of oscillations(f_o)	620kHz	619.6560kHz
Timeperiod of oscillations(T)	1.61 μ s	1.6137 μ s
Amplitude of oscillations	—	3.7311V
Feedback signal VF amplitude and phase w.r.t V_{out}	—	3.7356V, 180°
Feedback fraction in dB	1	0.9917
Phase shift offered by LC tank circuit	180°	180°

Table 2: Numerical 2
