

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Cascade Amplifier

Design 1:

Design a two stage RC coupled cascade amplifier to meet the following specifications:-

$$V_{O_{RMS}} = 2.5V, R_i \geq 1M\Omega \text{ and } |A_V| \geq 180$$

Select suitable transistor from data-sheet

Solution:

Step 1:- For above experiment, we can use CS-CS self bias JFET Amplifier

$$g_{m_o} = 5600\mu A/V, V_P = -2.5V, r_d = 50k\Omega \text{ and } I_{DSS} = 7mA$$

Step 2:- Selection of voltage gain

$$A_V \geq 180$$

Lets select $\rightarrow A_V = 190$

$$\text{Also, let } A_{V_1} = 0.6A_{V_2}$$

$$\therefore A_V = A_{V_1} \times A_{V_2}$$

$$190 = 0.6 \times A_{V_2}^2$$

$$A_{V_2} \approx 17.79$$

$$\therefore A_{V_2} = 18 \text{ and } A_{V_1} = 11$$

Design of second stage:-

Step 3:- Calculation of Q-Point($V_{GS_{Q_2}}, I_{D_{Q_2}}$)

Using mid-point biasing

$$I_D = \frac{I_{DSS}}{2} = 3.5mA$$

$$\text{In Saturation, } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\text{On rearranging, } V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right) = -2.5 \times \left(1 - \sqrt{\frac{3.5}{7}}\right) = -0.732V$$

$$V_{GS_{Q_2}} = -0.732V$$

Step 4:- Selection of R_{D_2}

$$|A_{V_2}| = g_m(r_{d_2} || R_{D_2}) \quad \dots\dots(1)$$

$$g_m = g_{m_2} = g_{m_1} = g_{m_o} \left(1 - \frac{V_{GS}}{V_P}\right) = 5600\mu A/V \left(1 - \frac{0.732}{2.5}\right) = 3.96mA/V$$

$$g_{m_1} = g_{m_2} = 3.96mA/V$$

$$r_{d_1} = r_{d_2} = 50k\Omega$$

From equation (1)

$$18 = 3.96mA/V(50k \parallel R_{D_2})$$

$$\frac{18}{3.96 \times 10^{-3}} = \frac{50k \times R_{D_2}}{50k + R_{D_2}}$$

$$R_{D_2} = 4.99k\Omega \approx 5k\Omega$$

Select $R_{D_2} = 5.1k\Omega, 1/4W$

Step 5:- Selection of R_{S_2}

$$V_{GS_Q} = -I_{D_Q}R_{S_2}$$

$$R_{S_2} = \frac{-V_{GS_Q}}{I_{D_Q}} = \frac{0.732}{3.5mA} = 209\Omega$$

Select $R_{S_2} = 180\Omega, 1/4W$

Step 6:- Selection of R_{G_2}

For present loading for first stage

Select $R_{G_2} = 1M\Omega, 1/4W$

Step 7:- Calculation of V_{DD}

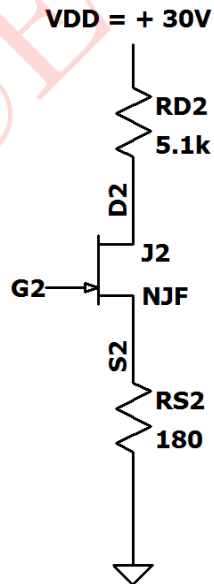


Figure 1: D to S Loop for JFET-2

Applying KVL to the D-S loop for JFET-2, we get,

$$V_{DD} - I_{DQ}R_{D_2} - V_{DS_2} - I_{D_2}R_{S_2} = 0$$

$$V_{DD} = I_{D_2}(R_{D_2} + R_{S_2}) + V_{DS_2}$$

$$V_{DS_2} \geq 1.5[|V_p| + V_{o_{peak}}]$$

$$V_{DS_2} \geq 1.5[2.5 + 2.5(\sqrt{2})]$$

$$V_{DS_2} \geq 9.053$$

$$\therefore V_{DS_2} = 9.1V$$

$$\therefore V_{DD} = 3.5m(0.18k + 5.1k) + 9.1$$

$$V_{DD} = 27.58V$$

Select $V_{DD} = 30V$

Design for first stage:-

Step 8:- Selection of R_{D_1}

$$|A_{V_1}| = g_m(r_d \parallel R_{D_2})$$

$$|A_{V_1}| = 3.96(50k \parallel 5.1k) = |8.328|$$

$$|A_{V_1}| = \frac{A_V}{|A_{V_2}|} = \frac{190}{|8.318|} = 10.36$$

$$\text{Let, } A_{V_1} = 11$$

$$|A_{V_1}| = g_{m_1}(r_{d_1} \parallel R_{D_1} \parallel R_{G_2})$$

$$11 = 3.96(50k \parallel R_{D_1} \parallel 1M)$$

$$11 = 3.96(47.62k \parallel R_{D_1})$$

$$11 = \frac{47.62k \times R_{D_1}}{47.62k + R_{D_1}}$$

$$R_{D_1} = 2.9496k\Omega$$

Select $R_{D_1} = 3.3k\Omega$, $1/4W$

Step 9:- Selection of R_{S_1}

$$V_{GS_Q} = -I_{D_1Q_1}R_{S_1}$$

$$R_{S_1} = \frac{-V_{GS_Q}}{I_{D_Q}}$$

$$R_{S_1} = \frac{0.732}{35mA} = 209.1\Omega$$

Select $R_{S_1} = 180\Omega$, $1/4W$

Step 10:- Selection of R_{G_1}

To avoid loading effect and fulfill the requirement of $R_i \geq 1M\Omega$

Select $R_{G_1} = 1M\Omega$, $1/4W$

Step 11:- Selection of coupling capacitors C_{C_2} , C_{C_1} , C_{C_3}

a) C_{C_1}

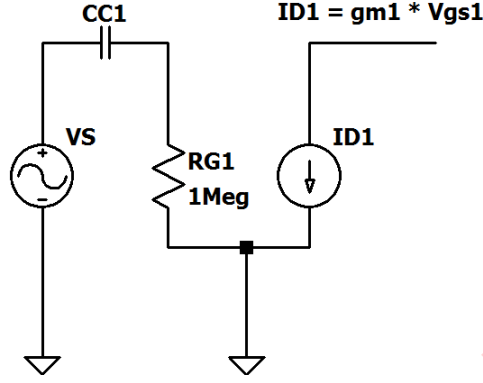


Figure 2: Small Signal low frequency equivalent circuit for C_{C_1}

$$C_{C_1} = \frac{1}{2\pi f_L R_{G_1}}$$

$$C_{C_1} = \frac{1}{2\pi \times 1.2M \times 20} = 6.63nF$$

Select, $C_{C_1} = 6.8nF/60V$

b) C_{C_2}

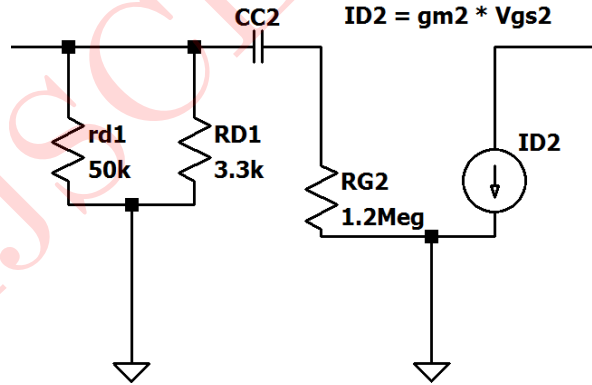


Figure 3: Small Signal low frequency equivalent circuit for C_{C_2}

$$C_{C_2} = \frac{1}{2\pi f_L R_{eq}}$$

$$R_{eq} = (r_{d_1} || R_{D_1}) + R_{G_1}$$

$$R_{eq} = (50k\Omega || 3.3k\Omega) + 1M\Omega = 3.1k + 1M\Omega = 1.0031M\Omega$$

$$C_{C_2} = \frac{1}{2\pi \times 1.0031 \times 10^6 \times 20} = 7.93nF$$

Select, $C_{C_2} = 7.93nF/60V$

c) C_{C_3}

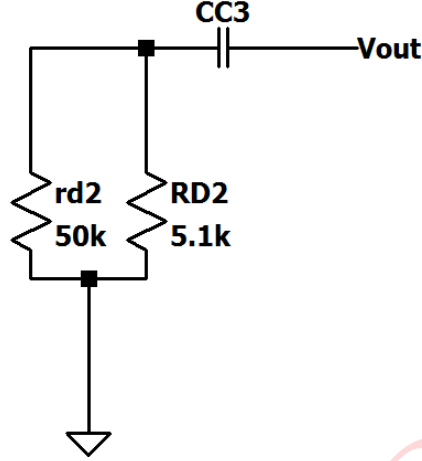


Figure 4: Small Signal low frequency equivalent circuit for C_{C_3}

$$C_{C_3} = \frac{1}{2\pi f_L R_{eq}}$$

$$R_{eq} = (r_{d2} || R_{D2})$$

$$R_{eq} = (50k\Omega || 5.1k\Omega) = 4.6279k\Omega$$

$$C_{C_3} = \frac{1}{2\pi \times 4.62 \times 10^3 \times 20} = 1.7195\mu F$$

Select, $C_{C_3} = 1.8\mu F / 60V$

Step 12:- Selection by pass capacitors

Since, $g_{m1} = g_{m2} = 3.96mA/V$

$$R_{S1} = R_{S2} = 180\Omega$$

$$C_{S1} = C_{S2} = \frac{1}{2\pi \times R_{eq} f_L}$$

$$R_{eq} = (1/g_m || R_S)$$

$$R_{eq} = (252.51\Omega || 180\Omega) = 0.1051k\Omega$$

$$C_{S1} = C_{S2} = \frac{1}{2\pi \times 105.1 \times 20} = 75.92\mu F$$

Select, $C_{S1} = C_{S2} = 100\mu F / 60V$

Step 13:- Complete designed circuit

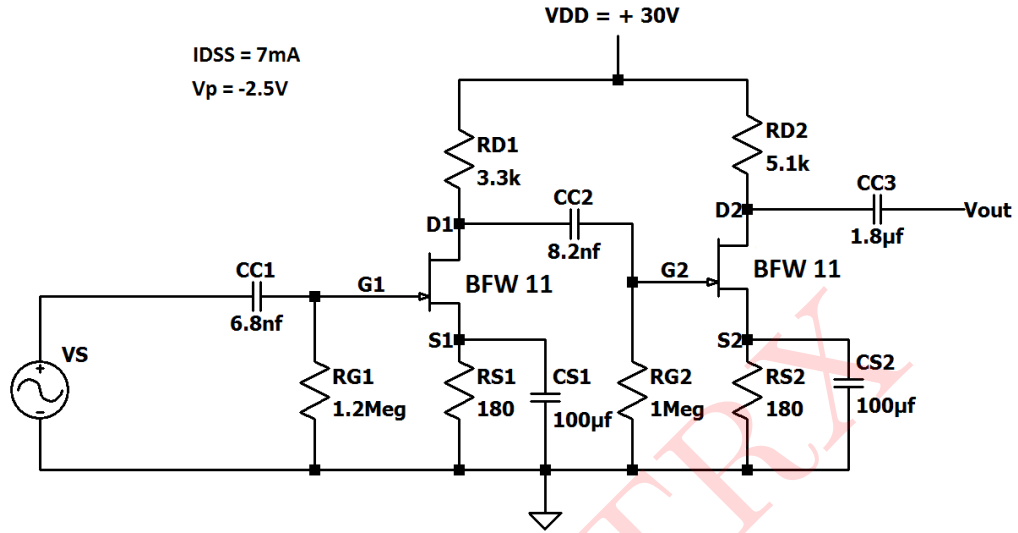


Figure 5: Designed Circuit

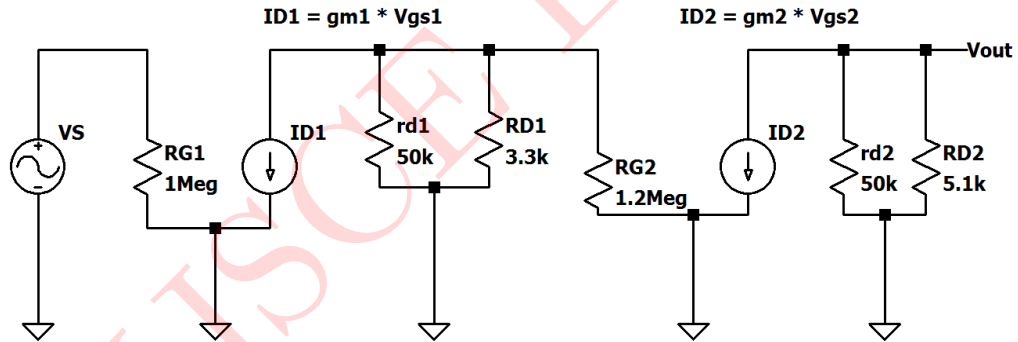


Figure 6: Small Signal Equivalent Circuit

Voltage Gain:-

$$A_{V_1} = -g_{m1}(r_{d1} \parallel R_{D1} \parallel R_{G2})$$

$$A_{V_1} = -3.96m(50k \parallel 1M \parallel 3.3k)$$

$$A_{V_1} = -3.96m(3.086k) = -12.22$$

$$\mathbf{A_{V_1} = -12.22}$$

$$A_{V_2} = -g_{m2}(r_d \parallel 5.1k)$$

$$A_{V_2} = -3.96m(50k \parallel 5.1k)$$

$$A_{V_2} = -3.96m(4.63k) = 18.35$$

$$\mathbf{A_{V_2} = -18.35}$$

$$A_{V_T} = A_{V_1} \times A_{V_2}$$

$$A_{V_T} = -12.22 \times -18.35 = 224.237$$

$$A_{V_T} = 224.237$$

$$A_{V_T} \text{ in dB} = 47.02 \text{ dB}$$

Input Impedance:-

$$Z_i = R_{G_1} = 1.2 \text{ M}\Omega$$

$$Z_i = 1.2 \text{ M}\Omega$$

Output Impedance:-

$$Z_o = R_{D_2} || r_{d_2} = 50 \text{ k}\Omega || 5.1 \text{ k}\Omega = 4.6279 \text{ k}\Omega$$

$$Z_o = 4.6279 \text{ k}\Omega$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

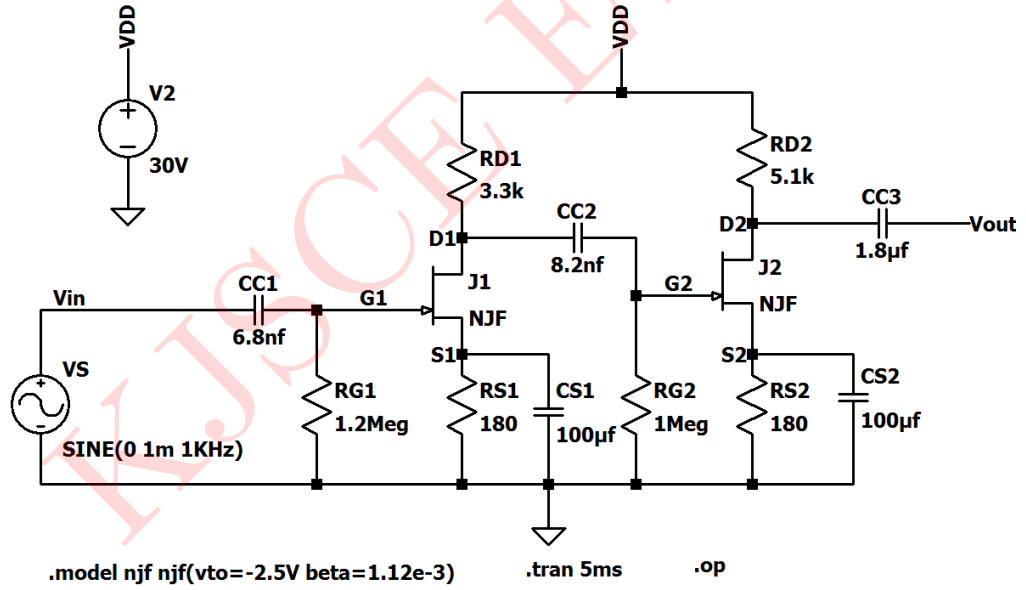


Figure 7: Circuit Schematic 1

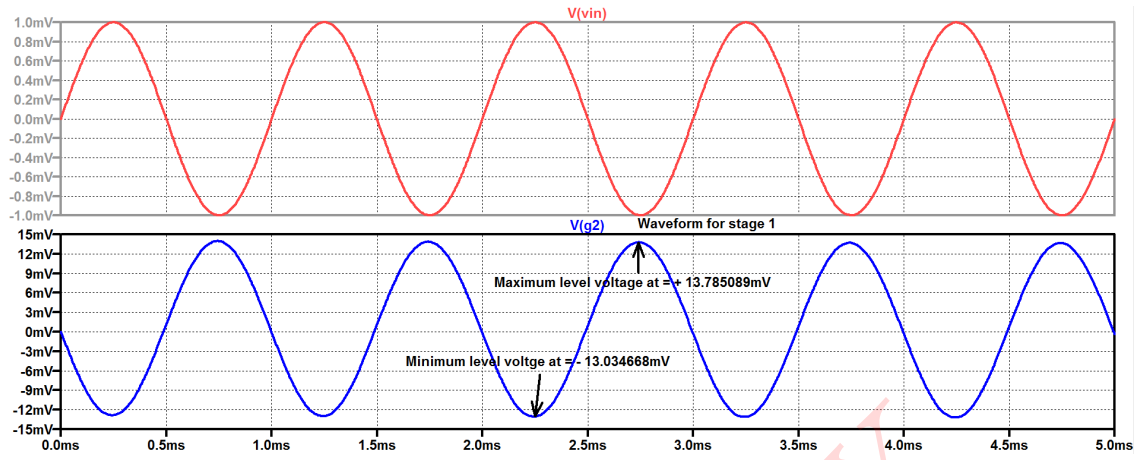


Figure 8: Input & Output waveform for 1st Stage

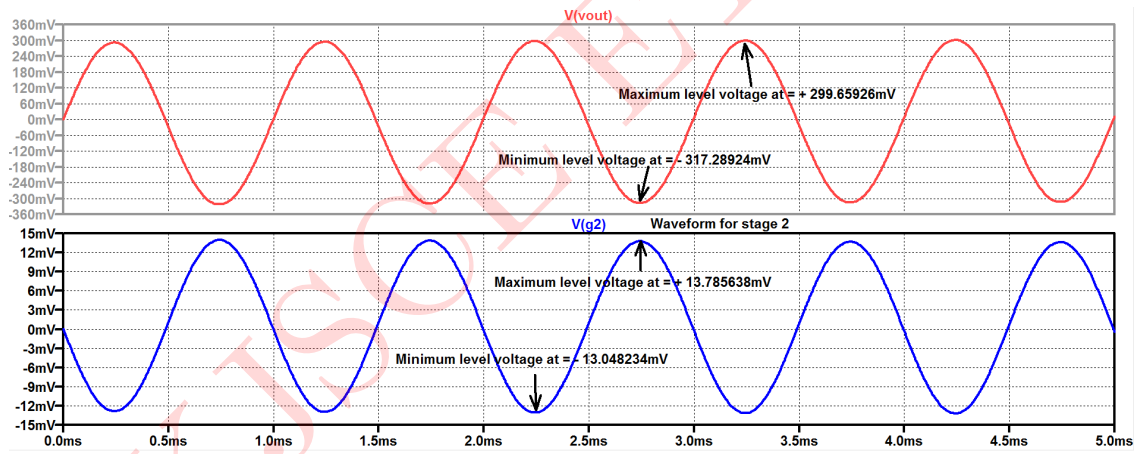


Figure 9: Input & Output waveform for 2nd Stage

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
I_{D_1}, V_{GS_1}	$3.5mA, -0.732V$	$3.73mA, -0.673V$
I_{D_2}, V_{GS_2}	$3.5mA, -0.732V$	$3.73mA, -0.673V$
A_{V_1}	-12.22	-12.5
A_{V_2}	-18.35	-22.78
$A_{V_T}(dB)$	47.02	48.84
V_{out}	$0.51V$	$0.62V$
Z_i, Z_o	$1.2M\Omega, 4.63k\Omega$	—

Table 1: Design 1

Design 2:

Design a two stage RC coupled cascade amplifier to meet the following specifications:-

$$V_{CC} = 22V, R_i \geq 1M\Omega, S \leq 10 \text{ and } |A_V| \geq 500$$

Select suitable transistor from data-sheet

Solution:

Above requirements can be fulfilled by CS-CE stage (we select CS as 1st stage since $R_i \geq 1M\Omega$)

Step 1:- Selection of transistor

Select BC147B $\rightarrow h_{fe} = 330, h_{fE} = \beta = 290, h_{ie} = 4.5k\Omega$ and $V_{CE} = 0.25V$

Select BFW11 $\rightarrow I_{DSS} = 7mA, g_{m_o} = 5600\mu A/V, V_P = -2.5V$ and $r_d = 50k\Omega$

Step 2:- Selection of voltage gain

$$A_V \geq 500$$

Also, let $A_{V_1} = 4$

$$A_{V_2} = \frac{500}{4} = 12.5$$

Let $A_{V_2} = 12.5$

Design of second stage:-**Step 3:- Selection of R_C**

$$|A_{V_2}| = \frac{h_{fe}R_C}{h_{ie}}$$

$$12.5 = \frac{330 \times R_C}{4.5k}$$

$$R_C = 1.7045k\Omega$$

Select $R_C = 1.8k\Omega, 1/4W$

Step 4:- Calculation of Q-Point(V_{CEQ}, I_{CQ})

$$V_{CC} = 22V$$

$$\text{Let, } V_{CE} = \frac{V_{CC}}{2} = 11V$$

$$V_{R_E} = 0.1V_{CC} = 0.1 \times 22 = 2.2V$$

Applying KVL to the C-E loop of BJT:-

$$V_{CC} - V_{R_C} - V_{CE} - V_{R_E} = 0$$

$$V_{R_C} = V_{CC} - V_{CE} - V_{R_E}$$

$$V_{R_C} = 22 - 11 - 2.2$$

$$V_{R_C} = 8.8V$$

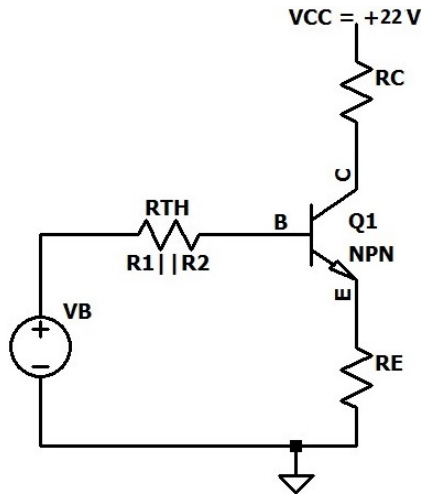


Figure 10: DC Equivalent circuit for BJT

$$V_{RC} = I_C R_C = 8.8V$$

$$I_C = \frac{8.8}{1.8k\Omega} = 4.89mA$$

Step 5:- Selection of R_E

$$V_{R_E} = 2.2V$$

$$I_E R_E = 2.2V$$

$$R_E = \frac{2.2}{I_{CQ}} = \frac{2.2}{4.89mA} = 449.89\Omega$$

Select $R_E = 420\Omega, 1/4W$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{4.89mA}{290} = 16.86\mu A$$

$$I_E = I_B + I_C = 4.91mA$$

Step 6:- Selection of biasing resistors R_1 & R_2

$$S \leq 10, \beta = 290$$

$$\text{Let, } S = 10$$

$$S = \frac{1 + \beta}{1 + \beta \left(\frac{R_E}{R_B + R_E} \right)}$$

$$10 = \frac{291}{1 + 291 \left(\frac{420}{420 + R_B} \right)}$$

$$R_B = 3.9145k\Omega = R_1 \parallel R_2$$

$$\frac{R_1 R_2}{R_1 + R_2} = 3.9145k\Omega \quad \dots(1)$$

$$V_B = V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} \quad \dots(2)$$

Applying KVL to the B-E loop of BJT:-

$$V_B = I_B R_B + V_{BE} + I_C R_E$$

$$V_B = (16.86 \times 10^{-6} \times 3.9145k) + 0.7 + 4.89 \times 10^{-3} \times 420$$

$$V_B = 0.7659 + 2.0538$$

$$V_B = 2.82V$$

From (2),

$$V_B = 2.82 = \frac{R_2}{R_1 + R_2} \times 22 \rightarrow \frac{R_2}{R_1 + R_2} = 0.128 \quad \dots(3)$$

$$V_E = I_E R_E = 4.91 \times 420 = 2.062V$$

Put (3) in (1),

$$R_1(0.128) = 3.9145k$$

$$R_1 = 30.58k\Omega$$

Select $R_1 = 33k\Omega, 1/4W$

$$\text{From (3), } \frac{R_2}{R_1 + R_2} = 0.128 \rightarrow \frac{R_2}{3.3k + R_2} = 0.128$$

$$R_2 = 4.84k\Omega$$

Select $R_2 = 5.1k\Omega, 1/4W$

Design for first stage:-

Step 7:- Selection of Q-Point V_{GSQ}, I_{DQ}

Using mid-point biasing

$$I_D = \frac{I_{DSS}}{2} = 3.5mA$$

$$\text{In Saturation, } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\text{On rearranging, } V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) = -2.5 \times \left(1 - \sqrt{\frac{3.5}{7}} \right) = -0.732V$$

$$V_{GSQ2} = -0.732V$$

$$g_{m1} = g_{m_o} \left(1 - \frac{V_{GS}}{V_P} \right) = 5600\mu A/V \left(1 - \frac{0.732}{2.5} \right) = 3.96mA/V$$

$$g_{m1} = g_{m_o} = 3.96mA/V$$

Step 8:- Selection of R_D

$$|A_{V_2}| = \frac{h_{fe} \times R_C}{h_{ie}} = \frac{300 \times 1.8k}{4.5k} = 132$$

$$|A_{V_1}| = \frac{A_V}{|A_{V_2}|} = \frac{500}{132} = 3.7878$$

$$|A_{V_1}| = g_{m_1}(r_d \parallel R_D \parallel R_1 \parallel R_2 \parallel h_{ie})$$

$$R_{L_1} = r_d \parallel R_1 \parallel R_2 \parallel h_{ie}$$

$$R_{L_1} = 80k \parallel 13k \parallel 5.9k \parallel 4.5k$$

$$R_{L_1} = 2.13k\Omega$$

$$|A_{V_1}| = g_m[R_D \parallel 2.13k]$$

$$3.7878 = \frac{3.96}{1000} \times \frac{R_D \times 2.13k}{R_D + 2.13k}$$

$$956.515(R_D + 2.13k) = 2.13k \times R_D$$

$$R_D = 1.736k\Omega$$

Select $R_D = 1.8k\Omega, 1/4W$

Step 9:- Selection of R_S

$$V_{GS_Q} = -I_{DQ_1}R_S$$

$$R_S = \frac{-V_{GS_Q}}{I_{DQ}}$$

$$R_{S_1} = \frac{0.732}{3.5mA} = 201.1\Omega$$

Select $R_S = 180\Omega, 1/4W$

Step 10:- Selection of R_G

To avoid loading effect and fulfill the requirement of $R_i \geq 1M\Omega$

Select $R_G = 1.2M\Omega, 1/4W$

Step 11:- Selection of coupling capacitors C_{C_2} , C_{C_1} , C_{C_3}

Since, f_L is not given we consider $f_L = 20Hz$

a) C_{C_1}

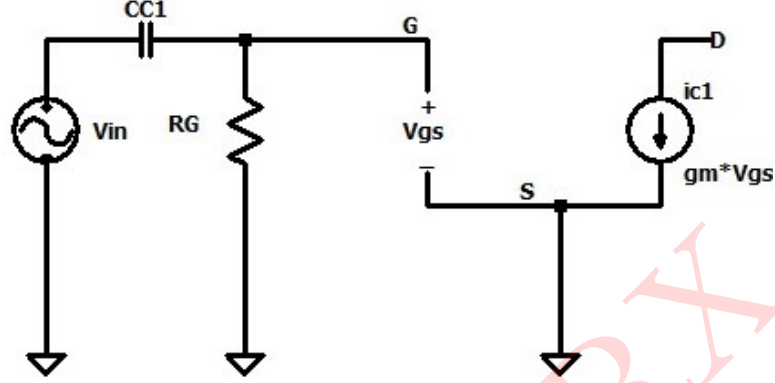


Figure 11: Small Signal low frequency equivalent circuit for C_{C_1}

$$C_{C_1} = \frac{1}{2\pi f_L R_G}$$

$$C_{C_1} = \frac{1}{2\pi \times 1.2M \times 20} = 6.63nF$$

Select, $C_{C_1} = 6.8nF/50V$

b) C_{C_2}

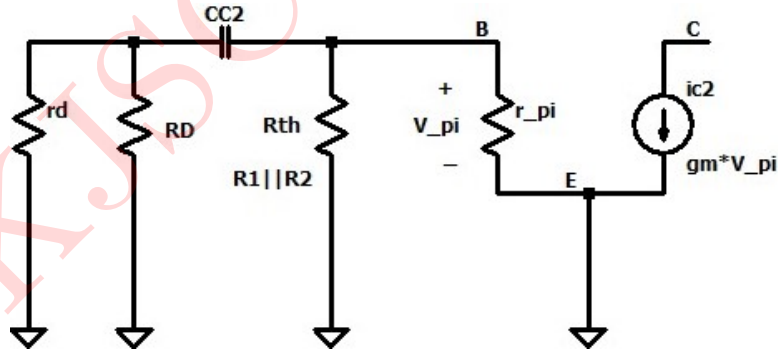


Figure 12: Small Signal low frequency equivalent circuit for C_{C_2}

$$C_{C_2} = \frac{1}{2\pi f_L R_{eq}}$$

$$R_{eq} = (r_d \parallel R_D) + (R_1 \parallel R_2 \parallel h_{ie})$$

$$R_{eq} = (50k \parallel 1.8k) + (3.3k \parallel 5.1k \parallel 4.5k)$$

$$R_{eq} = (1.737k) + (2.23k)$$

$$R_{eq} = 3.97k\Omega$$

$$C_{C_2} = \frac{1}{2\pi \times 3.97k \times 20} = 2.004\mu F$$

Select, $C_{C_2} = 2.2\mu F/50V$

c) C_{C_3}

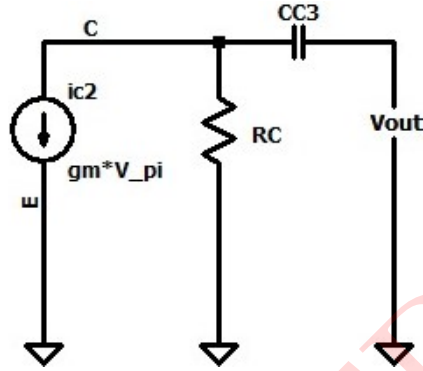


Figure 13: Small Signal low frequency equivalent circuit for C_{C_3}

$$C_{C_3} = \frac{1}{2\pi f_L R_{eq}}$$

$$R_{eq} = R_C = 1.8k$$

$$C_{C_3} = \frac{1}{2\pi \times 1 \times 10^3 \times 20} = 4.42\mu F$$

Select, $C_{C_3} = 4.47\mu F/50V$

Step 12:- Selection bypass capacitors

a) C_S

$$C_S = \frac{1}{2\pi \times R_{eq} \times f_L}$$

$$R_{eq} = \left(\frac{1}{g_m} \parallel R_S \right) = \frac{1}{3.96m} \parallel 180 = 105.09\Omega$$

$$C_S = \frac{1}{2\pi \times 105.09 \times 20} = 75.72\mu A$$

Select $C_S = 82\mu F/50V$

a) C_E

$$X_{CE} = 0.1R_E$$

$$\text{i.e } \frac{1}{2\pi \times f_L \times 0.1R_E} = 0.1R_E$$

$$C_E = \frac{1}{2\pi \times 0.1R_E \times f_L}$$

$$C_E = \frac{1}{2\pi \times 20 \times 0.1 \times 420} = 189.47\mu A$$

Select $C_E = 220\mu F/50V$

Step 13:- Small Signal Analysis

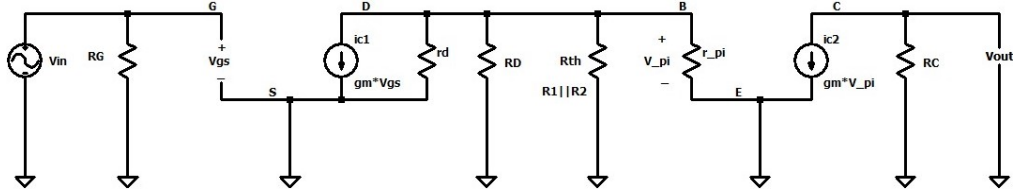


Figure 14: Small Signal Equivalent Circuit

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{4.89mA}{26mV} = 188.07mA/V$$

$$\mathbf{g_{m2} = 188.07mA/V}$$

Input Impedance:-

$$Z_i = R_G = 1.2M\Omega$$

$$\mathbf{Z_i = 1.2M\Omega}$$

Output Impedance:-

$$Z_o = R_C = 50k\Omega = 1.8k\Omega$$

$$\mathbf{Z_o = 1.8k\Omega}$$

Voltage Gain:-

$$A_{V1} = \frac{V_1}{V_S} = \frac{-g_{m1}V_{gs}(r_d || R_D || R_{th} || r_{\pi})}{V_{gs}}$$

$$A_{V1} = \frac{V_1}{V_S} = -g_{m1}(r_d || R_D || R_{th} || r_{\pi})$$

$$r_{\pi} = \frac{\beta V_T}{I_C} = \frac{290 \times 26mV}{4.89mA} = 1.54k\Omega$$

$$A_{V1} = -3.96m(50k || 1.8k || 4.42k || 1.54k) = -2.732$$

$$\mathbf{A_{V1} = -2.732}$$

$$A_{V2} = \frac{V_{out}}{V_1} = \frac{-g_{m2}V_{\pi}R_C}{V_{\pi}}$$

$$A_{V2} = -g_{m2}R_C$$

$$A_{V2} = -188.07(1.8) = -338.53$$

$$\mathbf{A_{V2} = -338.53}$$

$$A_{V_T} = A_{V_1} \times A_{V_2}$$

$$A_{V_T} = -338.53 \times -2.732 = 924.85$$

$$A_{V_T} = 924.85$$

$$A_{V_T} \text{ in dB} = 59.32 \text{ dB}$$

$$V_{out} = A_{V_T} \times V_S = 924.85 \times 2 \text{ mV} = 1.85 \text{ V}$$

$$V_{out} = 1.85 \text{ V}$$

Step 14:- Complete designed circuit

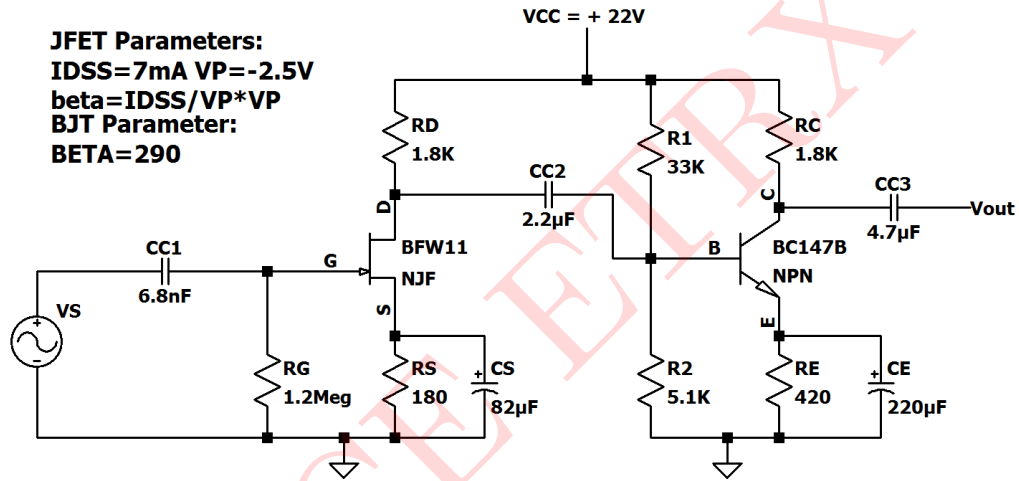


Figure 15: Designed Circuit 2

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

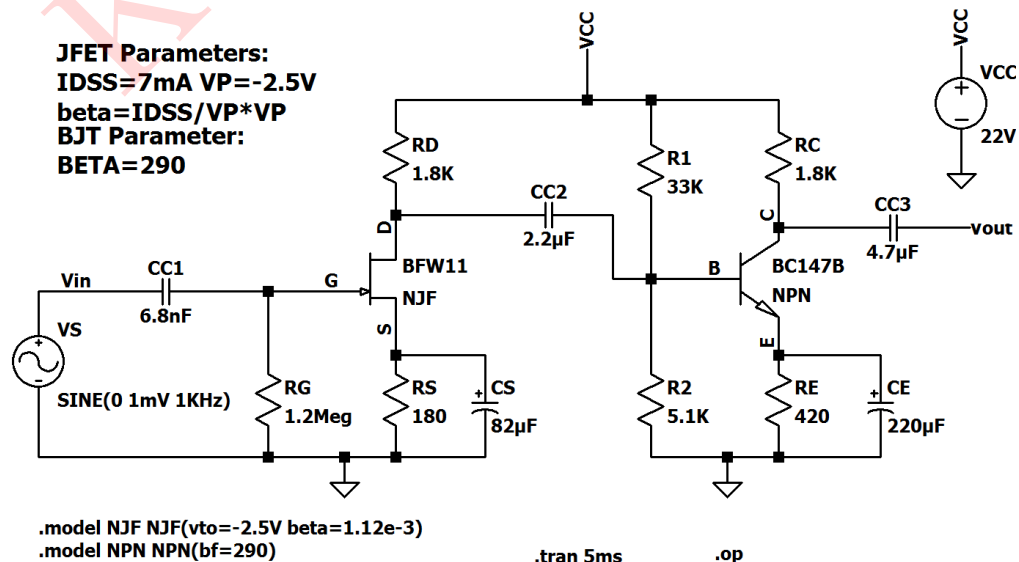


Figure 16: Circuit Schematic 2

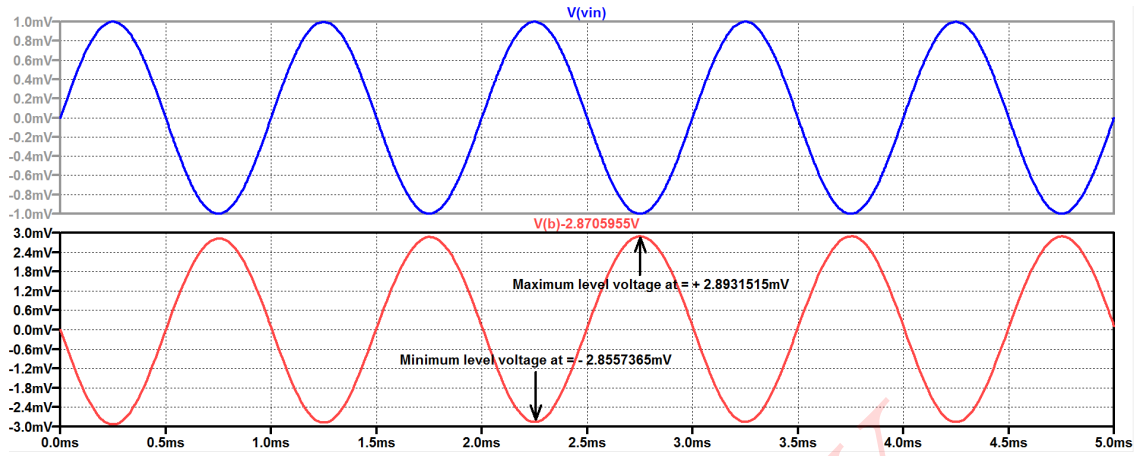


Figure 17: Input & Output waveform for 1st Stage

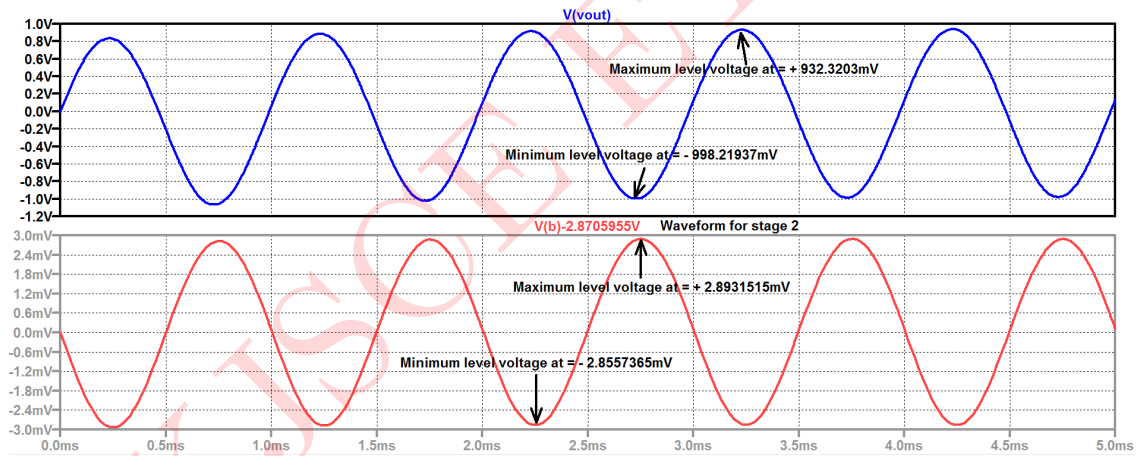


Figure 18: Input & Output waveform for 2nd Stage

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
I_{D_1}, V_{GS_1}	$3.5mA, -0.732V$	$3.73mA, -0.673V$
I_B, I_C, I_E	$16.86\mu A, 4.89mA, 4.91mA$	$16.82\mu A, 4.88mA, 4.90mA$
V_B, V_E	$2.82V, 2.062V$	$2.87V, 2.055V$
A_{V_1}	-2.732	-2.874
A_{V_2}	-338.53	-335.82
$A_{V_{in}}(dB)$	59.32	59.69
Z_i, Z_o	$1.2M\Omega, 1.8k\Omega$	—

Table 2: Design 2
