

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DC BIASING CIRCUITS

6th June, 2020

Numerical

1. For the network shown in Figure 1 below: a) Determine I_{CQ} , V_{CEQ}
 b) Find V_B , V_C , V_E and V_{BC} . Given, $\beta = 120$

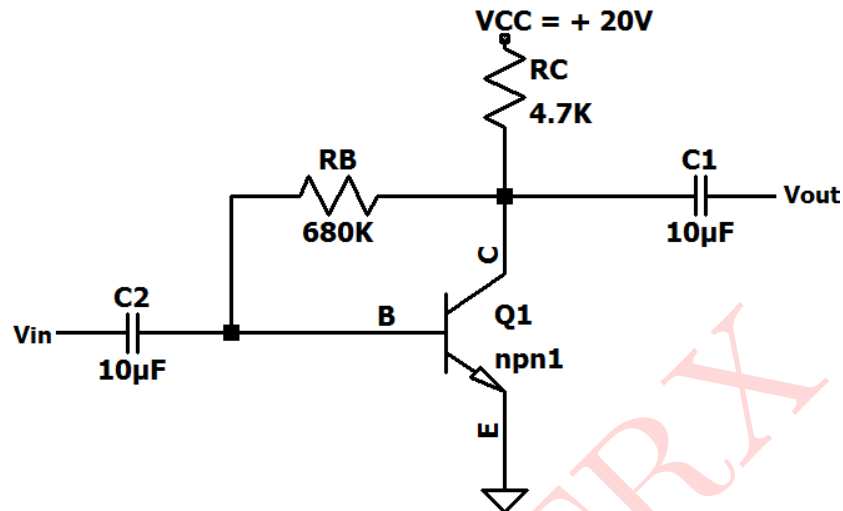


Figure 1: Circuit 1

Solution: In DC analysis, the capacitors act as open circuit.

 


Figure 2: DC equivalent circuit

Since, $f = 0$, $\therefore X_c = \frac{1}{2\pi f_c} = \infty$

Applying KVL to the input base-emitter loop

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta R_C}$$

$$I_B = \frac{20V - 0.7V}{680k\Omega + (120)(4.7k\Omega)} = \frac{19.3V}{1.244M\Omega} \quad (V_{BE} = 0.7 \text{ V})$$

$$\therefore I_B = 15.51\mu A$$

$$I_{CQ} = \beta I_B = 120 \times 15.51\mu A$$

$$\therefore I_{CQ} = \mathbf{1.86 \text{ mA}}$$

Applying KVL to the output common emitter loop

$$V_{CEQ} = V_{CC} - I_C R_C$$

$$V_{CEQ} = 20V - 1.86mA \times 4.7k\Omega$$

$$V_{CEQ} = \mathbf{11.26 \text{ V}}$$

$$V_B = V_{BE} = \mathbf{0.7 \text{ V}} \quad (\text{Since } V_{EE} = 0)$$

$$V_{CE} = V_{CEQ} = 11.26 \text{ V}$$

$$\therefore V_C = \mathbf{11.26 \text{ V}} \quad (V_E = \mathbf{0 \text{ V}})$$

$$V_{BC} = V_B - V_C = 0.7 \text{ V} - 11.26 \text{ V}$$

$$V_{BC} = \mathbf{-10.56 \text{ V}}$$

SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

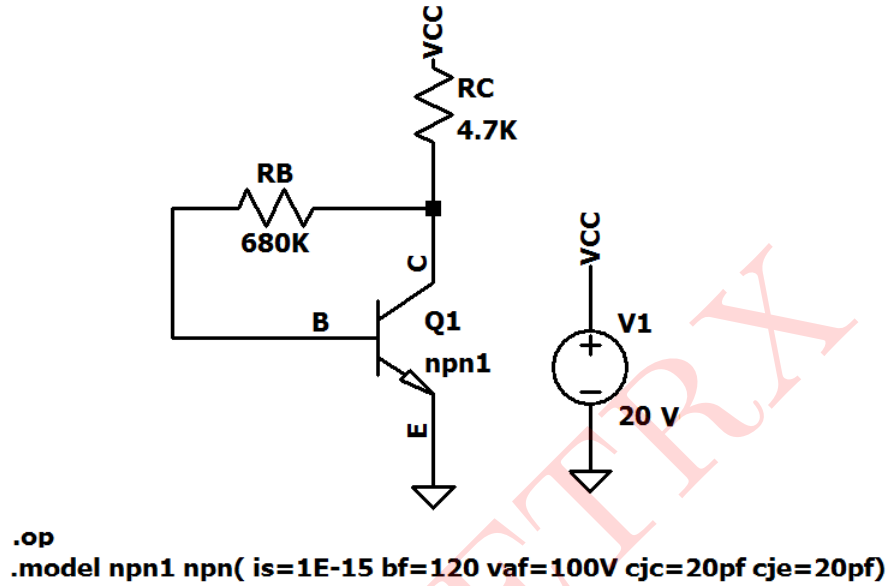


Figure 3: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
I_B	15.51 μA	14.47 μA
I_C	1.86 mA	1.949 mA
V_C	11.26 V	10.768 V
V_B	0.7 V	0.729 V
V_E	0 V	0 V

Table 1: Numerical 1

2. Determine the voltage V_{CB} and the current I_B for the common base configuration of Figure 4 given below. given that $\beta = 60$

 


Figure 4: Circuit 2

Solution :

In DC analysis, the capacitors act as open circuit.

 


Figure 5: DC equivalent circuit

$$\text{Since, } f = 0, \quad \therefore X_c = \frac{1}{2\pi f_c} = \infty$$

Applying KVL to the input base-emitter loop

$$-V_{EE} + I_E R_E + V_{BE} = 0$$

$$\therefore I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

Substituting values:

$$I_E = \frac{4V - 0.7V}{1.2k\Omega} = 2.75\text{mA}$$

Applying KVL to the output circuit gives

$$-V_{CB} + I_C R_C - V_{CC} = 0$$

$$V_{CB} = V_{CC} - I_C R_C \text{ with } I_C \approx I_E$$

$$V_{CB} = 10V - 2.75\text{mA} \times 2.4k\Omega$$

$$V_{CB} = 3.4V$$


$$I_B = \frac{I_C}{\beta}$$

$$I_B = \frac{2.75\text{mA}}{60}$$

$$I_B = 45.8 \mu\text{A}$$

SIMULATED RESULTS:

 Above circuit is simulated using LTSpice and the results are presented below



.model npn1 npn(is=1E-15 bf=60 vaf=100V cjc=20pf cje=20pf)

Figure 6: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
I_B	45.8 μA	43.0305 μA
I_E	2.75 mA	2.717 mA

Table 2: Numerical 2

3. Determine I_B , I_C , V_{CE} and stability factor for the circuit shown in Figure 7.
Given, $\beta = 100$.

 


Figure 7: Circuit 3

Solution:

The above circuit is a self-bias circuit.

Applying KVL to the input base-emitter loop:

$$V_{CC} - (I_B + I_C)R_C - I_B R_B - V_{BE} = 0$$

$$V_{CC} - (\beta + 1)I_B R_C - I_B R_B - V_{BE} = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1)R_C}$$

$$I_B = \frac{10 - 0.7}{500 \times 10^3 + 101 \times 3 \times 10^3}$$

$$\therefore I_B = 11.58 \mu\text{A}$$

$$I_{CQ} = \beta I_B = 100 \times 11.58 \mu\text{A}$$

$$\therefore I_{CQ} = 1.158 \text{ mA}$$

Applying KVL to the output common emitter loop:

$$V_C = V_{CC} - (I_B + I_C)R_C$$

$$V_C = 10 - (11.58 \times 10^{-6} + 1.158 \times 10^{-3}) \times 3 \times 10^3$$

$$\therefore V_C = 6.49 \text{ V}$$

$$V_E = (I_B + I_C)R_E$$

$$V_E = (I_B + I_C) \times 0 \quad (\text{Since } R_E = 0 \ \Omega)$$

$$V_{CE} = V_C - V_E = 6.49 - 0$$

$$\therefore V_{CE} = \mathbf{6.49 \text{ V}}$$

Stability factor:

$$S = \frac{\beta + 1}{1 + \beta \left(\frac{R_C}{R_C + R_B} \right)}$$

$$\therefore S = \frac{100 + 1}{1 + \left(\frac{100 \times 3 \times 10^3}{500 \times 10^3 + 3 \times 10^3} \right)}$$

$$\therefore S = \mathbf{63.26}$$

SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

 


Figure 8: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
I_B	$11.58 \text{ } \mu\text{A}$	$11.4847 \text{ } \mu\text{A}$
I_C	1.158 mA	1.14847 mA
V_C	6.49 V	6.52 V

Table 3: Numerical 3

4. For the circuit shown in Figure 9, find I_C , V_{CE} and stability factor. Given, $\beta = 120$

 


Figure 9: Circuit 4

Solution:

The above configuration is collector to base bias.

Applying KVL to the input base-emitter loop:

$$V_{CC} - (I_B + I_C)R_C - I_B R_B - V_{BE} - (I_B + I_C)R_E = 0$$

$$V_{CC} - (\beta + 1)I_B R_C - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)(R_C + R_E)}$$

$$I_B = \frac{10 - 0.7}{220 \times 10^3 + 101 \times (2.5 + 1) \times 10^3}$$

$$\therefore I_B = 16.21 \mu A$$

$$I_{CQ} = \beta I_B = 100 \times 16.21 \mu A$$

$$\therefore I_{CQ} = \mathbf{1.621 \text{ mA}}$$

Applying KVL to the output common emitter loop

$$V_C = V_{CC} - (I_B + I_C)R_C$$

$$V_C = 10 - (16.21 \times 10^{-6} + 1.621 \times 10^{-3}) \times 2.5 \times 10^3$$

$$\therefore V_C = 5.9069 \text{ V}$$

$$V_E = (I_C + I_B)R_E$$

$$V_E = (16.21 \times 10^{-6} + 1.621 \times 10^{-3}) \times 10^3$$

$$\therefore V_E = 1.637 \text{ V}$$

$$V_{CE} = V_C - V_E$$

$$V_{CE} = 5.9069 \text{ V} - 1.637 \text{ V}$$

$$\therefore V_{CE} = \mathbf{4.2699 \text{ V}}$$

Stability factor:

$$S = \frac{\beta + 1}{1 + \beta \left(\frac{R_E + R_C}{R_B + R_C + R_E} \right)}$$

$$S = \frac{100 + 1}{1 + 100 \times \left(\frac{1k + 2.5k}{220k + 2.5k + 1k} \right)}$$

$$\therefore S = \mathbf{39.36}$$

SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

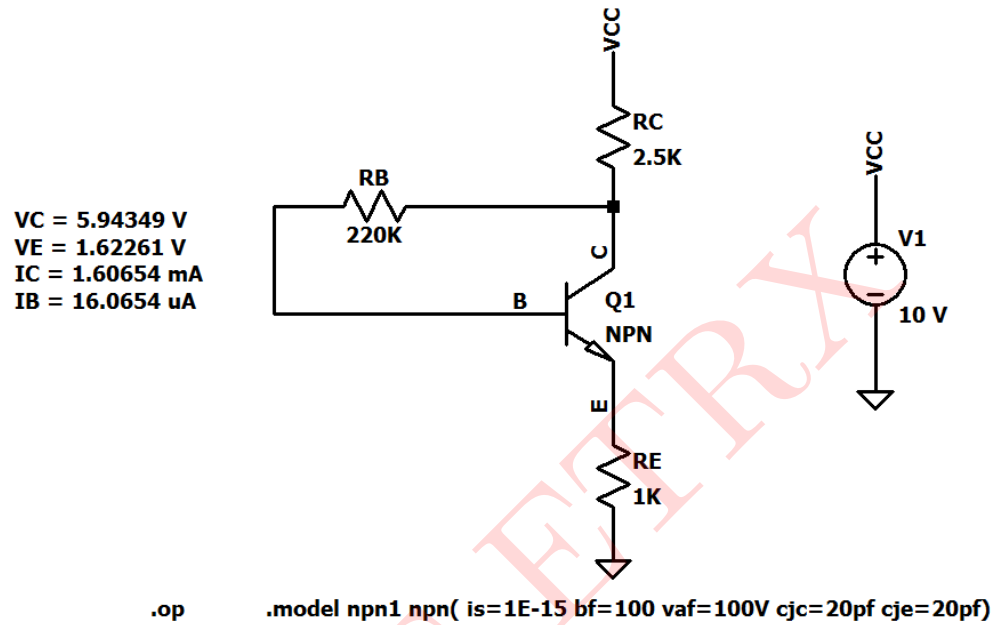


Figure 10: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
I_B	16.21 μA	16.6054 μA
I_C	1.621 mA	1.6065 mA
V_C	5.9069 V	5.94349 V
V_E	1.637 V	1.62261 V

Table 4: Numerical 4

5. For the voltage feedback network shown in Figure 11, determine I_C , V_C , V_E and V_{CE}
 Given: $\beta = 100$

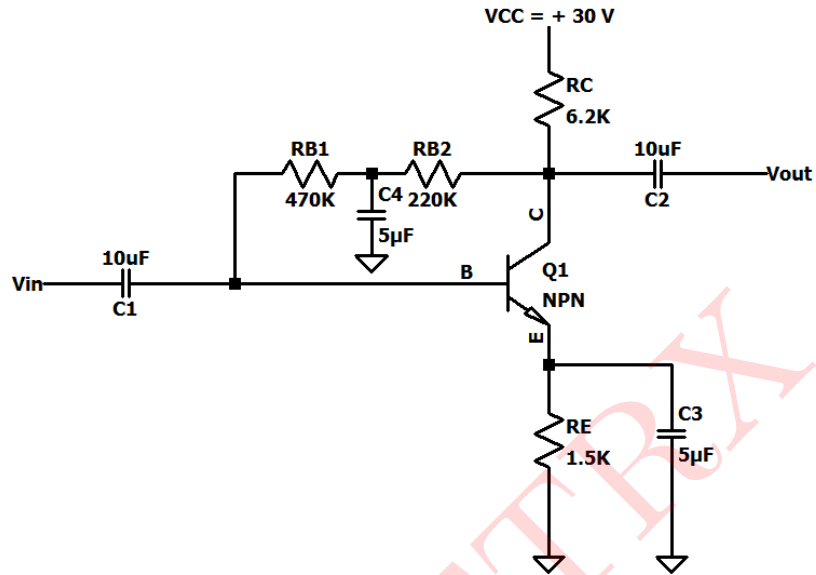


Figure 11: Circuit 5

Solution:

In DC analysis, the capacitors act as open circuit.

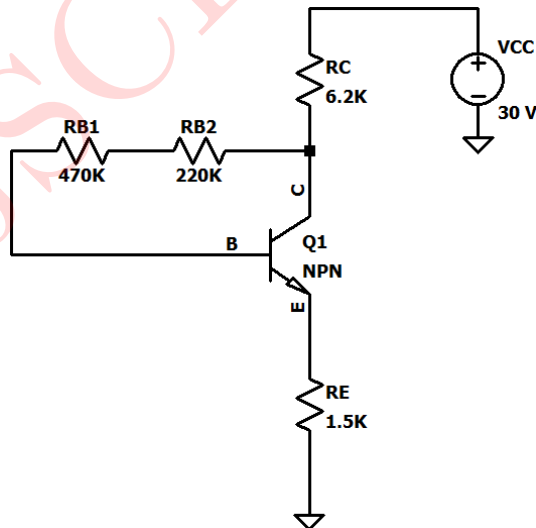


Figure 12: DC equivalent circuit

Since, $f = 0$, $\therefore X_c = \frac{1}{2\pi f_c} = \infty$

Applying KVL to the input base-emitter loop:

$$V_{CC} - (I_B + I_C)R_C - I_B(R_{B_1} + R_{B_2}) - (I_B + I_C)R_E - V_{BE} = 0$$

$$V_{CC} - (\beta + 1)I_B R_C - I_B(R_{B_1} + R_{B_2}) - (\beta + 1)I_B R_E - V_{BE} = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{(R_{B_1} + R_{B_2}) + (\beta + 1)(R_C + R_E)}$$

$$I_B = \frac{30 - 0.7}{(470k + 220k) + 101 \times (6.2k + 1.5k)}$$

$$\therefore I_B = 19.96 \mu A$$

$$I_C = \beta I_B = 100 \times 19.963 \mu A$$

$$\therefore I_C = \mathbf{1.9963 \text{ mA}}$$

Applying KVL to the output common emitter loop:

$$V_C = V_{CC} - (I_B + I_C)R_C$$

$$V_C = 30 - (19.963 \times 10^{-6} + 1.9963 \times 10^{-3}) \times (6.2 \times 10^3)$$

$$\therefore V_C = \mathbf{17.501 \text{ V}}$$

$$V_E = (I_B + I_C)R_E$$

$$V_E = (19.963 \times 10^{-6} + 1.9963 \times 10^{-3}) \times 1.5 \times 10^3$$

$$\therefore V_E = \mathbf{3.0239 \text{ V}}$$

$$V_{CE} = V_C - V_E = 17.501 \text{ V} - 3.0239 \text{ V}$$

$$\therefore V_{CE} = \mathbf{14.4771 \text{ V}}$$

SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

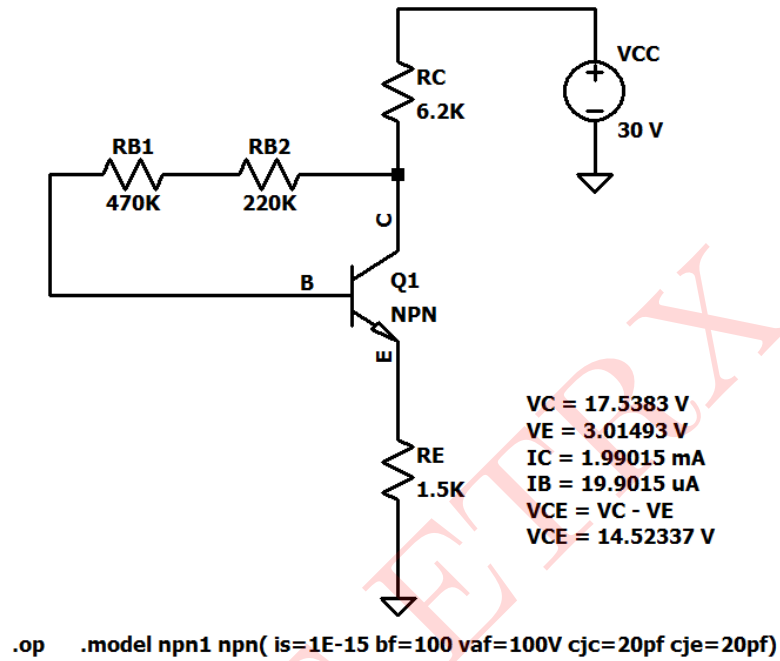


Figure 13: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
I_B	19.963 μ A	19.9015 μ A
I_C	1.9963 mA	1.99015 mA
V_{CE}	14.4771 V	14.52337 V
V_E	3.0239 V	3.01493 V

Table 5: Numerical 5

6. For the network shown in Figure 14, determine I_B , I_C , V_{CE} and V_C
 Given: $\beta = 120$

 


Figure 14: Circuit 6

Solution:

Applying KVL to the input base-emitter loop:

$$-I_B R_B - V_{BE} - (1 + \beta) I_B R_E + V_{EE} = 0$$

$$\therefore I_B = \frac{V_{EE} - V_{BE}}{R_B + (1 + \beta) R_E}$$

$$I_B = \frac{12 - 0.7}{9.1 \times 10^3 + 121 \times 15 \times 10^3}$$

$$\therefore I_B = \mathbf{6.1945 \mu A}$$

$$I_C = \beta I_B = 120 \times 6.1948 \mu A$$

$$\therefore I_C = \mathbf{0.74337 \text{ mA}}$$

Applying KVL to the output common emitter loop

$$V_{CE} = V_{CC} - I_C R_C - (I_B + I_C) R_E + V_{EE}$$

$$\therefore V_{CE} = \mathbf{7.83598 \text{ V}}$$

$$V_C = V_{CC} - I_C R_C$$

$$V_C = 16 - (0.743374 \times 10^{-3} \times 12 \times 10^3)$$

$$\therefore V_C = \mathbf{7.0795 \text{ V}}$$

SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

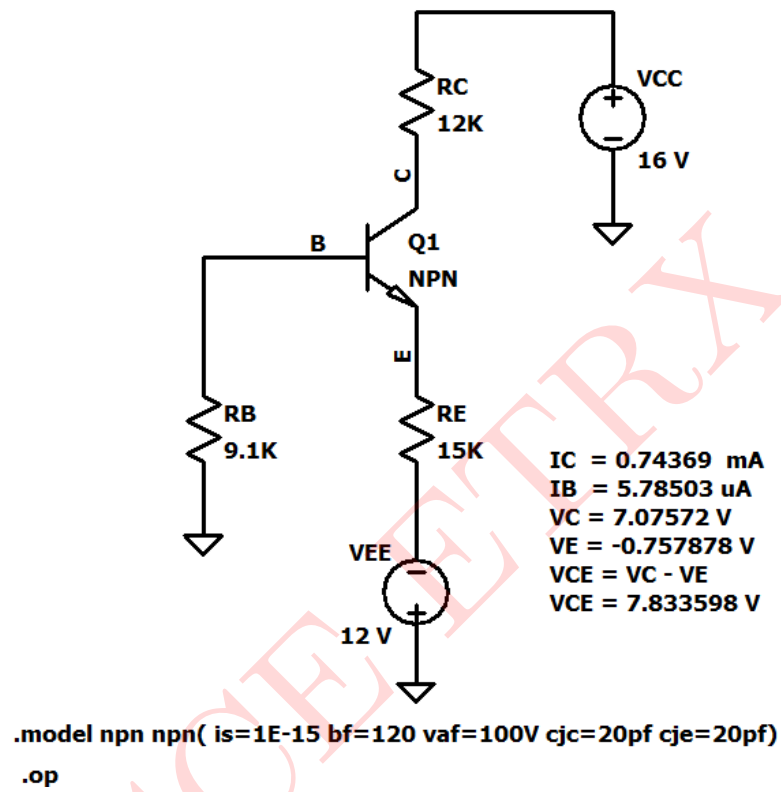


Figure 15: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
I_B	6.1948 μ A	5.7850 μ A
I_C	0.74337 mA	0.74369 mA
V_{CE}	7.83598 V	7.83359 V
V_C	7.0795 V	7.07572 V

Table 6: Numerical 6

7. In the circuit shown in Figure 14, the transistor parameters are:
 $V_{TN} = 0.8V$ and $k_n = 0.5 \text{ mA/V}^2$. Calculate V_{GS} , I_D and V_{DS}

 


Figure 16: Circuit 7

Solution:

The above Circuit 7 is a voltage divider bias circuit.

Applying Thevenin's equivalent at the gate terminal

$$R_G = R_1 || R_2 = 32k || 18k$$

$$\therefore R_G = 11.52k\Omega$$

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{18k}{32k + 18k} \times 10$$

$$\therefore V_G = 3.6V$$

 


Figure 17: Thevenin's equivalent circuit

$$V_{GS} = V_G - V_S$$

$$V_S = I_D R_S = I_D (2k)$$

$$\therefore V_{GS} = 3.6 - I_D (2k) \dots\dots (1)$$

$$\text{We know, } I_D = k_n (V_{GS} - V_T)^2$$

$$\therefore I_D = 0.5 \times 10^{-3} \times (V_{GS} - 0.8)^2 \dots\dots (2)$$

Substituting the value of I_D from equation (2) in equation (1), we get

$$V_{GS} = 3.6 - 0.5 \times 2 (V_{GS} - 0.8)^2$$

$$\therefore V_{GS} = 3.6 - (V_{GS} - 0.8)^2$$

$$\therefore V_{GS} = 3.6 - (V_{GS}^2 - 1.6V_{GS} + 0.64)$$

$$\therefore V_{GS}^2 - 0.6V_{GS} - 2.96 = 0$$

$$\therefore V_{GS} = 1.4464 \text{ V or } 2.0464 \text{ V}$$

Since, $|V_{GS}| < |V_{TN}|$,

$$\therefore V_{GS} = \mathbf{2.0464 \text{ V}}$$

$$\text{From equation (1), } I_D = 0.5 \times 10^{-3} \times (2.0464 - 0.8)^2$$

$$\therefore I_D = \mathbf{0.77675 \text{ mA}}$$

Applying KVL to the output drain-source loop

$$V_{DS} = V_{DD} - I_D(R_D + R_S) = 10 - 0.77675(4k + 2k) \times 10^{-3}$$

$$\therefore V_{DS} = \mathbf{5.3395 \text{ V}}$$

SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

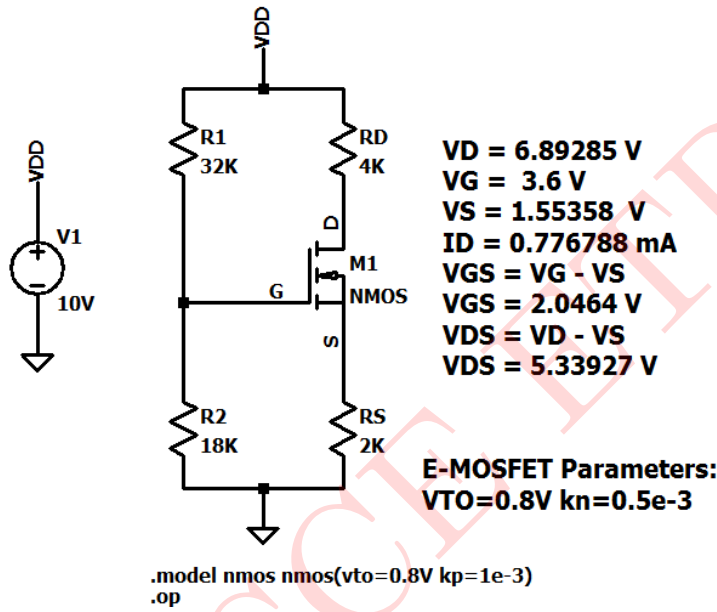


Figure 18: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
V_G	3.6 V	3.6 V
V_{GS}	2.0464 V	2.04642 V
V_{DS}	5.3395 V	5.33927 V
I_D	0.77675 mA	0.776788 mA

Table 7: Numerical 7

8. For the transistor in the circuit shown in Figure 17, the parameters are:

$$V_{TN} = 0.4V, k'_n = 0.120 \mu A/V^2 \text{ and } \frac{W}{L} = 25$$

Determine V_{GS} , I_D and V_{DS}

 


Figure 19: Circuit 8

Solution:

The above Circuit 1 is a voltage divider bias circuit.

Applying Thevenin's equivalent at the Gate terminal

 


Figure 20: Thevenin's equivalent circuit

$$R_G = R_1 || R_2 = 14k || 6k$$

$$\therefore R_G = 4.2k\Omega$$

$$V_G = \left[\frac{R_2}{R_1 + R_2} \times (V_{DD} + V_{SS}) \right] - 5 = \left[\frac{6k}{14k + 6k} \times 10 \right] - 5$$

$$\therefore V_G = -2V$$

$$V_{GS} = V_G - V_S$$

$$V_S = I_D R_S - 5$$

$$\therefore V_{GS} = -2 - [I_D(0.5k) - 5]$$

$$\therefore V_{GS} = 3 - I_D(0.5k) \dots\dots (1)$$

$$k_n = k'_n \times \frac{W}{L} = 120 \times 10^{-6} \times 25 = 3mA/V^2$$

$$\text{We know, } I_D = k_n(V_{GS} - V_T)^2$$

$$\therefore I_D = 3 \times 10^{-3} \times (V_{GS} - 0.4)^2 \dots\dots (2)$$

Substituting the value of I_D from equation (2) in equation (1), we get

$$V_{GS} = 3 - \times 10^{-3} \times 0.5 \times 10^3 \times (V_{GS} - 0.4)^2$$

$$\therefore V_{GS} = 3 - 1.5 \times (V_{GS} - 0.4)^2$$

$$\therefore V_{GS} = 3 - 1.5V_{GS}^2 + 1.2V_{GS} - 0.24$$

$$\therefore 1.5V_{GS}^2 - 0.2V_{GS} - 2.76 = 0$$

$$\therefore V_{GS} = 1.42476V \text{ or } -1.2914V$$

Since, $|V_{GS}| < |V_{TN}|$,

$$\therefore V_{GS} = \mathbf{1.42476 \text{ V}}$$

$$\text{From equation (1), } I_D = 3 \times 10^{-3} \times (1.42476 - 0.4)^2 = \mathbf{3.15039 \text{ mA}}$$

Applying KVL to the output drain-source loop

$$V_{DS} = V_{DD} - I_D(R_D + R_S) - (-5) = 10 - 3.15039(1.2k + 0.5k) \times 10^{-3}$$

$$\therefore V_{DS} = \mathbf{4.644 \text{ V}}$$

SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

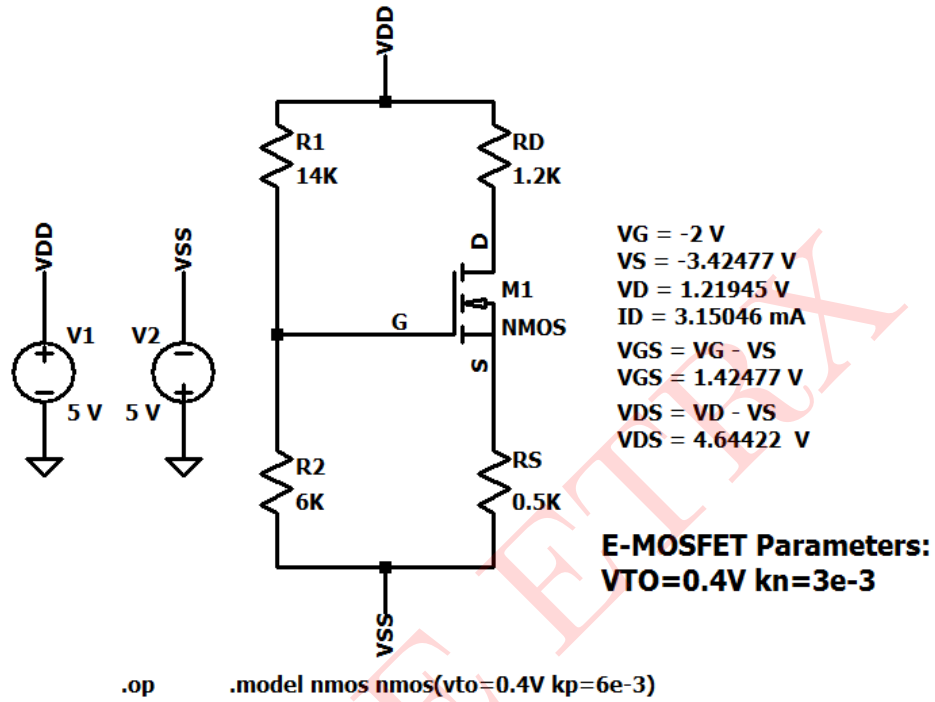


Figure 21: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
V_G	3.6 V	3.6 V
V_{GS}	2.0464 V	2.04642 V
V_{DS}	5.3395 V	5.33927 V
I_D	0.77675 mA	0.776788 mA

Table 8: Numerical 8

9. For the circuit shown in Figure 20, calculate V_{GS} , I_D and V_{DS}
 Given: $V_P = -3 \text{ V}$ and $I_{DSS} = 12 \text{ mA}$

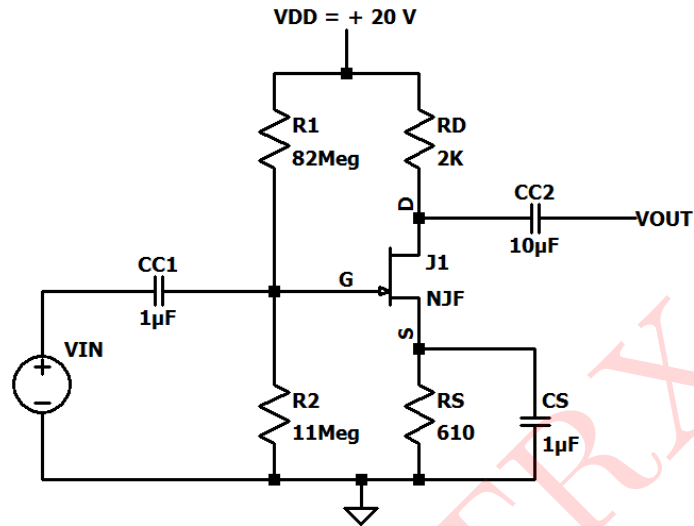


Figure 22: Circuit 9

Solution:

In DC analysis, the capacitors act as open circuit.

Since $f = 0$, $\therefore X_c = \frac{1}{2\pi f_c} = \infty$

 


Figure 23: DC equivalent circuit

$$R_G = R_1 || R_2 = 82\text{M} || 11\text{M} = 9.69 \text{ M}\Omega$$

$$V_G = \left[\frac{R_2}{R_1 + R_2} \times V_{DD} \right] = \left[\frac{11\text{M}\Omega}{(11\text{M} + 82\text{M})\Omega} \times 20 \right]$$

$$\therefore V_G = 2.36\text{V}$$

$$V_{GS} = V_G - V_S$$

$$V_S = I_D R_S = I_D(610)$$

$$\therefore V_{GS} = 2.36 - I_D(610) \quad \dots\dots\dots (1)$$

Assuming that the JFET is working in saturation region

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 12\text{mA} \left(1 + \frac{V_{GS}}{-3} \right)^2 \quad \dots\dots\dots (2)$$

Substituting the value of I_D from equation (2) in equation (1), we get

$$V_{GS} = 2.36 - 7.32 \times \left(1 + \frac{2V_{GS}}{3} + \frac{V_{GS}^2}{9} \right)$$

$$\therefore 0.8133V_{GS}^2 + 5.88V_{GS} + 4.96 = 0$$

$$\therefore V_{GS} = -0.975 \text{ V or } -6.25 \text{ V}$$

Since, $V_{GS} > V_P$,

$$\therefore V_{GS} = -0.975 \text{ V}$$

From equation (2):

$$I_D = 12\text{mA} \left(1 - \frac{-0.975}{-3} \right)^2$$

$$\therefore I_D = 5.4675 \text{ mA}$$


$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$\therefore V_{DS} = 20 - 5.4675 \times 10^{-3}(2k + 610)$$

$$\therefore V_{DS} = 5.729825 \text{ V}$$

SIMULATED RESULTS:

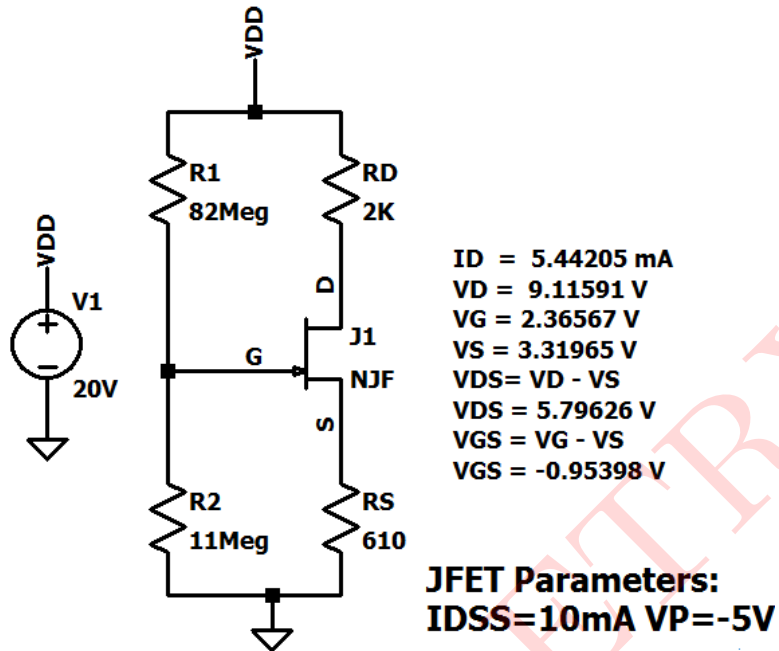Above circuit is simulated using LTspice and the results are presented below:



.op .model njf njf(vto=-3V beta=1.3e-3)

Figure 24: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
I_D	5.4675 mA	5.44205 mA
V_{GS}	-0.975 V	-0.95398 V
V_{DS}	5.729825 V	5.79626 V

Table 9: Numerical 9

10. For the circuit shown in Figure 23, find V_{GS} , I_D and V_{DS}
 Given: $V_{GS(th)} = 5 \text{ V}$, $V_{GS(on)} = 10 \text{ V}$ and $I_D(on) = 3 \text{ mA}$

 


Figure 25: Circuit 10

Solution:

Circuit 10 is a voltage divider bias circuit.

 


Figure 26: DC equivalent circuit

$$R_G = R_1 || R_2 = 22\text{M} || 18\text{M} = 9.9 \text{ M}\Omega$$

$$V_G = \left[\frac{R_2}{R_1 + R_2} \times V_{DD} \right] = \left[\frac{18\text{M}\Omega}{(22\text{M} + 18\text{M})\Omega} \times 40 \right]$$

$$\therefore V_G = 18\text{V}$$

$$\text{For E-NMOS transistor, } k_n = \frac{I_D(on)}{[V_{GS}(on) - V_{GS}(th)]^2}$$

$$\therefore k_n = \frac{3}{[10 - 5]^2} = 0.12 \text{ mA/V}^2$$

$$V_{GS} = V_G - V_S$$

$$V_S = I_D R_S = I_D(820)$$

$$\therefore V_{GS} = 18 - I_D(820) \quad \text{..... (1)}$$

Assuming that the given E-NMOS transistor is working in saturation region

$$I_D = k_n[V_{GS} - V_{GS}(th)]^2$$

$$\therefore I_D = 0.12 \times 10^{-3}(V_{GS} - 5)^2 \quad \text{..... (2)}$$

Substituting the value of I_D from equation (2) in equation (1), we get

$$V_{GS} = 18 - 820 \times 0.12 \times 10^{-3} \times (V_{GS} - 5)^2$$

$$\therefore 0.0984V_{GS}^2 + 0.016V_{GS} - 15.54 = 0$$

$$\therefore V_{GS} = 12.48 \text{ V or } -12.64 \text{ V}$$

Since, $V_{GS} < V_{GS}(th)$,

$$\therefore V_{GS} = \mathbf{12.48 \text{ V}}$$

From equation (2):

$$I_D = k_n(V_{GS} - 5)^2 = 0.12 \times 10^{-3} \times (12.48 - 5)^2$$

$$\therefore I_D = \mathbf{6.72 \text{ mA}}$$

Applying KVL to the output drain- source loop

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$\therefore V_{DS} = 40 - 6.72 \times 10^{-3}(3k + 820)$$

$$\therefore V_{DS} = \mathbf{14.32 \text{ V}}$$

SIMULATED RESULTS:

Above circuit is simulated using LTspice and the results are presented below:

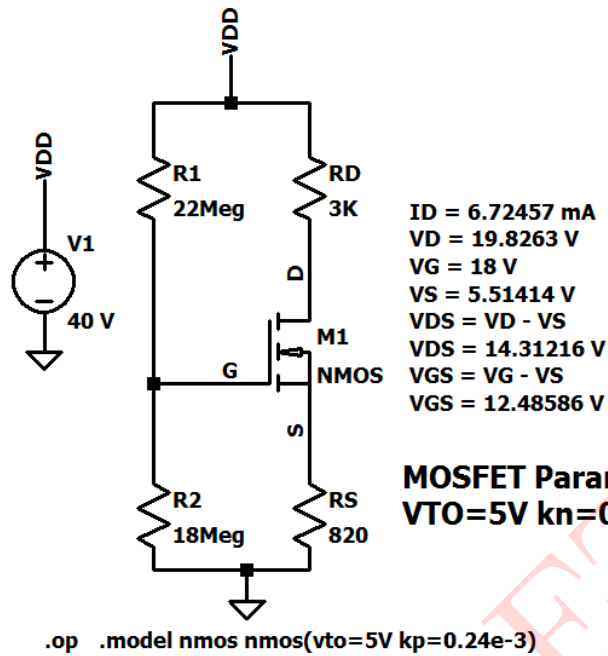


Figure 27: Circuit schematic: Results

Comparison of theoretical and simulated values:

Parameters	Theoretical	Simulated
I_D	6.72 mA	6.72457 mA
V_{GS}	12.48 V	12.48586 V
V_{DS}	14.32 V	14.31216 V

Table 10: Numerical 10
