

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DIODE APPLICATIONS

Numerical 1: Simulate a half wave rectifier circuit given in Figure 1 with input Amplitude = 110V peak, $f = 60\text{Hz}$, and $R_L = 75\Omega$ using LT spice. Use 10:1 step down transformer. Plot the following using LTspice:

- i) Primary peak voltage
- ii) Secondary peak voltage
- iii) Output voltage across resistor
- iv) Output voltage across diode
- v) Current flowing through the circuit

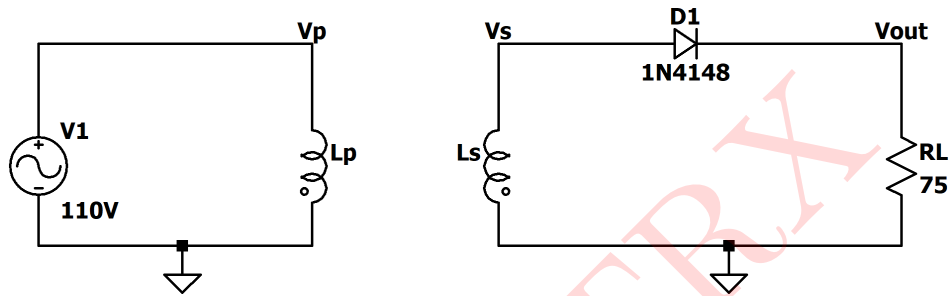


Figure 1: Circuit 1

Solution:

Transformer ratio is 10:1,

$$\frac{V_p}{V_s} = \frac{10}{1}$$

$$V_s = V_m = \frac{110}{10} = 11V$$

DC output power is,

$$P_{DC} = \frac{V_{DC}^2}{R_L} = \frac{V_m^2}{\pi^2 \times R_L}$$

$$\therefore P_{DC} = 0.16346W$$

AC output power is,

$$P_{AC} = \frac{\left(\frac{V_m}{2}\right)^2}{R_f + R_L} = \frac{\left(\frac{11}{2}\right)^2}{(0.01 \times 10^{-3}) + 75}$$

$$\therefore P_{AC} = 0.4033W$$

Efficiency,

$$\eta = \frac{P_{DC}}{P_{AC}} \times 100$$

$$\therefore \eta = 40.53\%$$

$$\text{PIV Rating} = -V_m = -11V$$

$$I_m = \frac{V_m}{R_f + R_L} = \frac{11}{(0.01 \times 10^{-3}) + 75}$$

$$\therefore I_m = 0.1466A$$

SIMULATED RESULTS

The given circuit is simulated in LTspice and the results obtained are as follows:

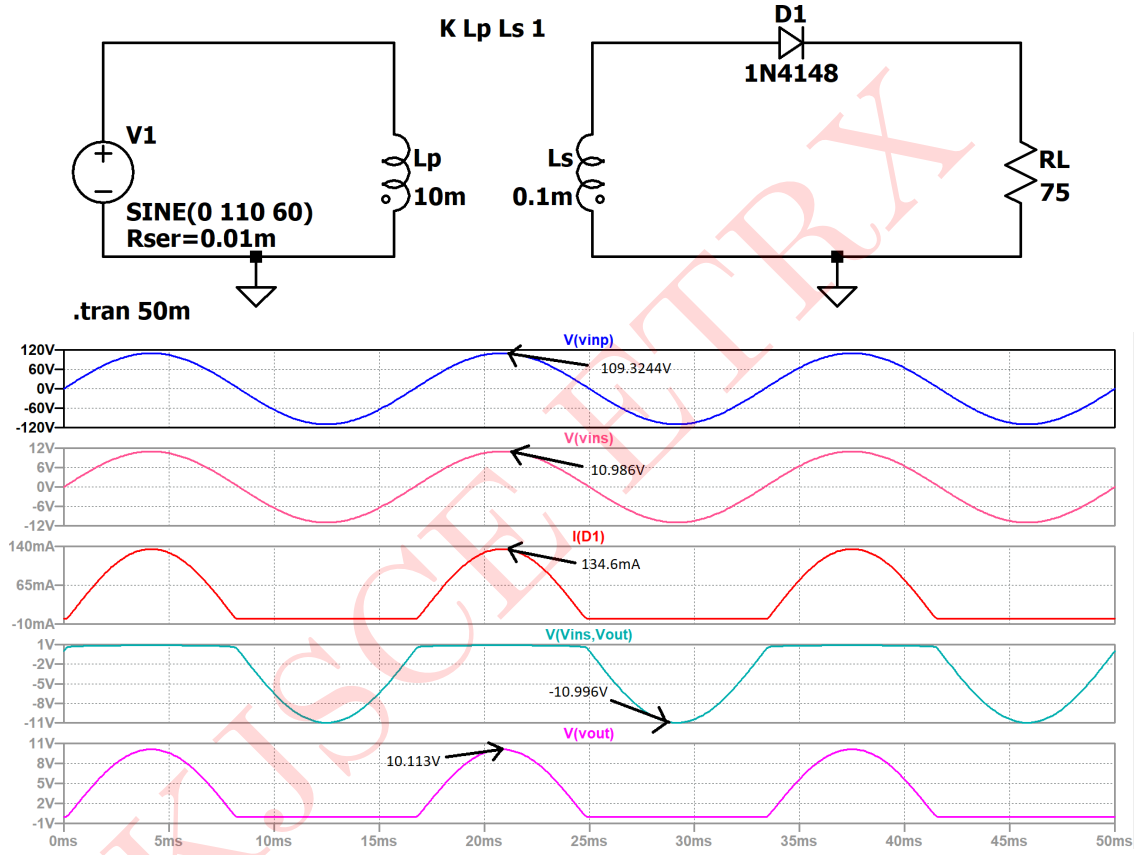


Figure 2: Circuit Schematic and Simulated Results

Verifying the Calculated Values with Simulated Values:

Parameter	Calculated Value	Simulated Value
V_m	11V	10.996V
I_m	0.1466A	0.1346A
P_{DC}	0.4033W	0.4031W
P_{AC}	0.16346W	0.16334W
η	40.53%	40.521%
PIV Rating	-11V	-10.9965V

Table 1: Numerical 1

Numerical 2: Simulate a full wave rectifier circuit given in Figure 3 with input Amplitude = 120V peak, $f = 50\text{Hz}$, and $R_L = 50\Omega$ using LT spice. Use 10:1 step down transformer. Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diodes
- Current flowing through the diodes
- Current flowing through the circuit

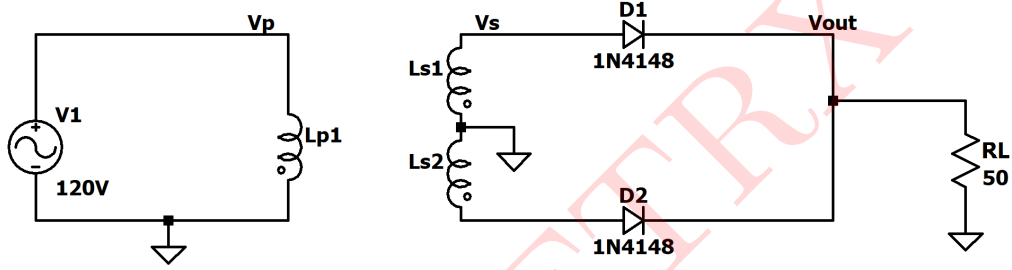


Figure 3: Circuit 2

Solution:

Transformer ratio is 10:1,

$$\frac{V_p}{V_s} = \frac{10}{1}$$

$$V_s = V_m = \frac{120}{10} = 12V$$

DC output power is,

$$P_{DC} = \left(\frac{2I_m}{\pi} \right)^2 \times R_L = \left(\frac{2 \times 0.2399}{\pi} \right)^2 \times 50$$

$$\therefore P_{DC} = 1.16624W$$

AC output power is,

$$P_{AC} = 0.5 \times (I_m)^2 (R_f + R_L)$$

$$\therefore P_{AC} = 1.4388W$$

Efficiency,

$$\eta = \frac{P_{DC}}{P_{AC}} \times 100$$

$$\therefore \eta = 81.056\%$$

$$\text{PIV Rating} = -2 \times V_m = -24V$$

$$I_m = \frac{V_m}{R_f + R_L} = \frac{12}{(0.01 \times 10^{-3}) + 50}$$

$$\therefore I_m = 0.2399A$$

SIMULATED RESULTS

The given circuit is simulated in LTspice and the results obtained are as follows:

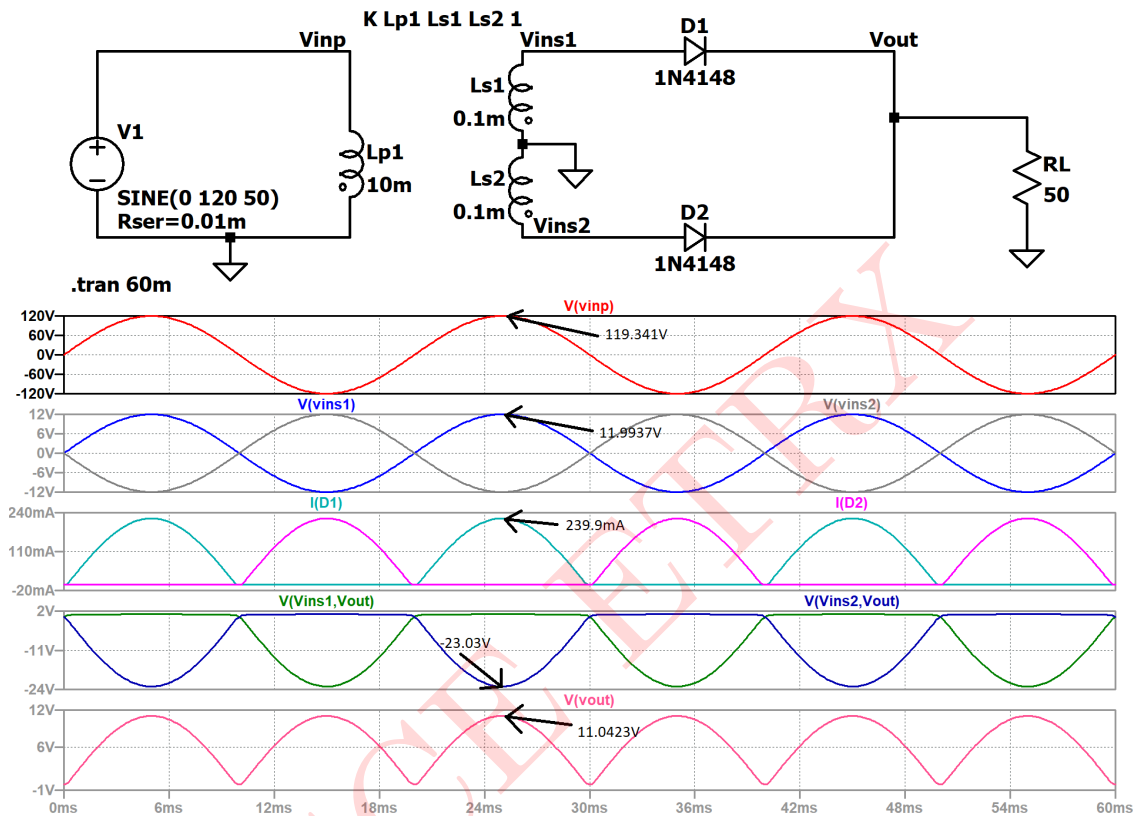


Figure 4: Circuit Schematic and Simulated Results

Verifying the Calculated Values with Simulated Values:

Parameter	Calculated Value	Simulated Value
V_m	12V	11.9937V
I_m	0.2399A	0.2208A
P_{DC}	1.16624W	0.988W
P_{AC}	1.4388W	1.218W
η	81.056%	81.116%
PIV Rating	-24V	-23.03V

Table 2: Numerical 2
