

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DIODE APPLICATIONS

Numerical 1: Simulate a half wave rectifier circuit with input Amplitude = 110V peak, $f = 60 \text{ Hz}$ and $R_L = 75\Omega$ using LT spice. Select diode as 1N4148. Use 10:1 step down transformer. Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diode
- Current flowing through the circuit

Also, calculate the efficiency of the Half wave rectifier circuit.

Solution:

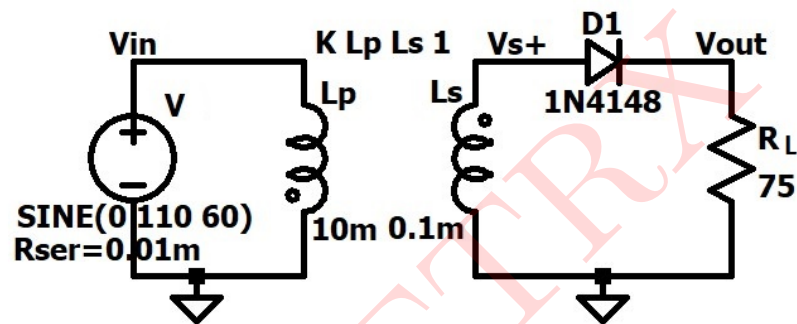


Figure 1: Circuit 1

$$\frac{N_1}{N_2} = \frac{E_1}{E_2}$$

$$\frac{N_1}{N_2} = \frac{10}{1}$$

$$V_{in} = E_1 = 110\text{V}$$

$$V_{out} = E_2 = 11\text{V}$$

$$\begin{aligned} \text{Current through the circuit } I_M &= \frac{V_M}{R_f + R_L} \\ &= \frac{10.3}{0.00001 + 75} \\ &= 0.1373\text{A} \end{aligned}$$

$$I_M = 0.1373\text{A}$$

$$\begin{aligned} \text{Output voltage across resistor } (V_M) &= E_2 - V_{D,ON} \\ &= 11 - 0.7 \\ &= 10.3\text{V} \end{aligned}$$

$$V_M = 10.3\text{V}$$

$$\begin{aligned}
 \text{DC Power } (P_{DC}) &= \frac{V_M^2}{\pi^2 \times R_L} \\
 &= \frac{10.3^2}{\pi^2 \times 75} \\
 &= 0.1433\text{W}
 \end{aligned}$$

$$\begin{aligned}
 \text{AC Power } (P_{AC}) &= \frac{V_M^2}{4(R_f + R_L)} \\
 &= \frac{10.3^2}{4(0.00001 + 75)} \\
 &= 0.3536\text{W}
 \end{aligned}$$

$$P_{DC} = \mathbf{0.1433W}$$

$$P_{AC} = \mathbf{0.3536W}$$

$$\begin{aligned}
 \text{Efficiency } (\eta) &= \frac{P_{DC} \times 100}{P_{AC}} \\
 &= \frac{0.1433 \times 100}{0.3536} \\
 &= 40.526\%
 \end{aligned}$$

$$\eta = \mathbf{40.526\%}$$

$$\text{PIV rating on D} = -V_M = -11\text{V}$$

Waveforms:

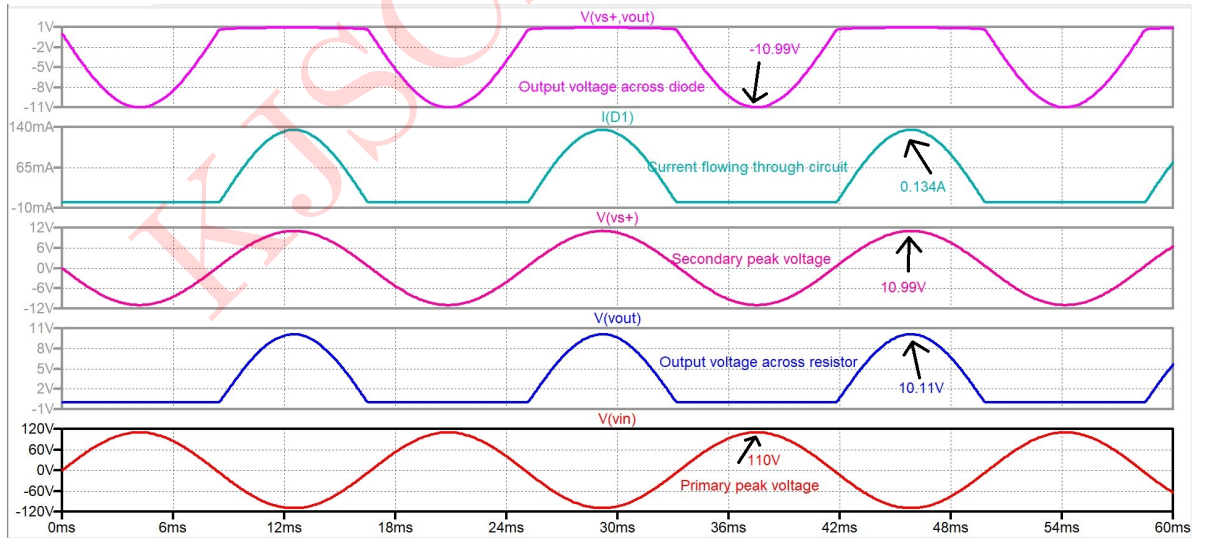


Figure 2: Circuit Waveforms

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

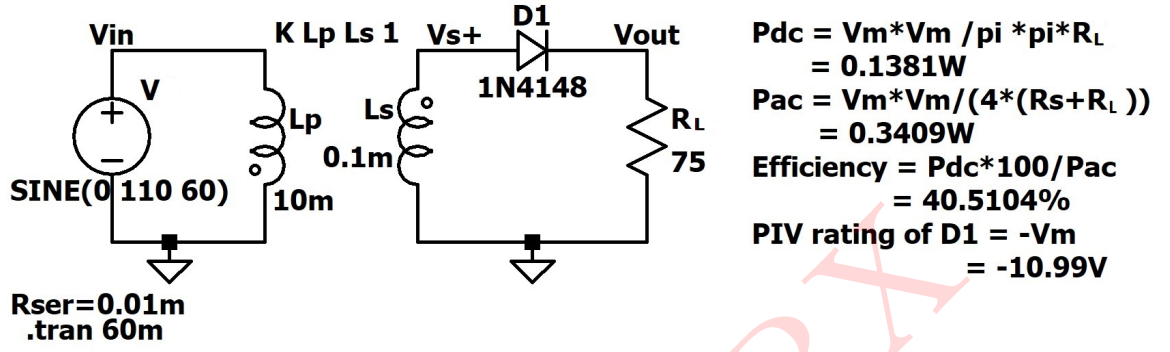


Figure 3: Circuit Schematic and Simulated Results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Output peak voltage (V_M)	10.3V	10.11V
Output peak current (I_M)	0.1373A	0.134A
AC Power	0.3536W	0.3409W
DC Power	0.1433W	0.1381W
Efficiency (η)	40.526%	40.5104%
PIV rating	-11V	-10.99V

Table 1: Numerical 1

Numerical 2: Simulate a full wave rectifier circuit with input Amplitude = 1210V peak, $f = 50$ Hz and $R_L = 50\Omega$ using LT spice. Select diode as 1N4148. Use 10:1 step down transformer. Plot the following using LTspice:

- Primary peak voltage
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diode
- Current flowing through the diodes
- Current flowing through the circuit
- Efficiency of the full wave rectifier circuit.

Solution:

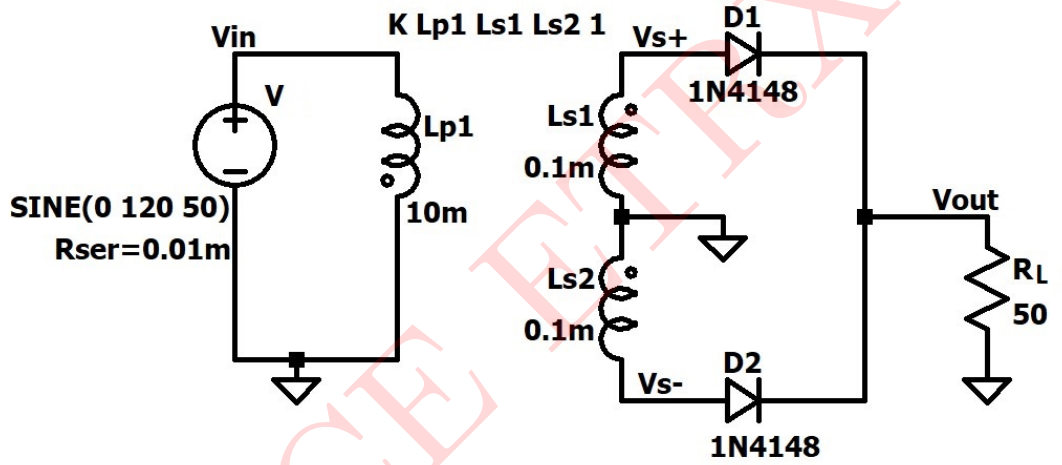


Figure 4: Circuit 2

$$\frac{N_1}{N_2} = \frac{E_1}{E_2}$$

$$\frac{N_1}{N_2} = \frac{10}{1}$$

$$V_{in} = E_1 = 120V$$

$$V_{out} = E_2 = 12V$$

$$\begin{aligned} \text{Current through the circuit } I_M &= \frac{V_M}{R_f + R_L} \\ &= \frac{11.3}{0.00001 + 50} \\ &= 0.226A \end{aligned}$$

$$I_M = 0.226A$$

$$\begin{aligned} \text{Output voltage across resistor } (V_M) &= E_2 - V_{D,ON} \\ &= 10 - 0.7 \\ &= 11.3V \end{aligned}$$

$$V_M = 11.3V$$

$$I_{D1} = I_{D2} = I_M = 0.226A$$

$$\begin{aligned}
 \text{DC Power } (P_{DC}) &= \frac{(2I_M)^2 \times R_L}{\pi^2} \\
 &= \frac{(2 \times 0.226)^2 \times 50}{\pi^2} \\
 &= 1.035\text{W}
 \end{aligned}$$

$$\begin{aligned}
 \text{AC Power } (P_{AC}) &= \frac{I_M^2 (R_f + R_L)}{2} \\
 &= \frac{0.226^2 (0.00001 + 50)}{2} \\
 &= 1.276\text{W}
 \end{aligned}$$

$$P_{DC} = 1.035\text{W}$$

$$P_{AC} = 1.276\text{W}$$

$$\begin{aligned}
 \text{Efficiency } (\eta) &= \frac{P_{DC} \times 100}{P_{AC}} \\
 &= \frac{1.035 \times 100}{1.276} \\
 &= 81.112\%
 \end{aligned}$$

$$\eta = 81.112\%$$

$$\text{PIV rating on D1} = -2V_M = -22.6\text{V}$$

$$\text{PIV rating on D2} = -2V_M = -22.6\text{V}$$

Waveforms:

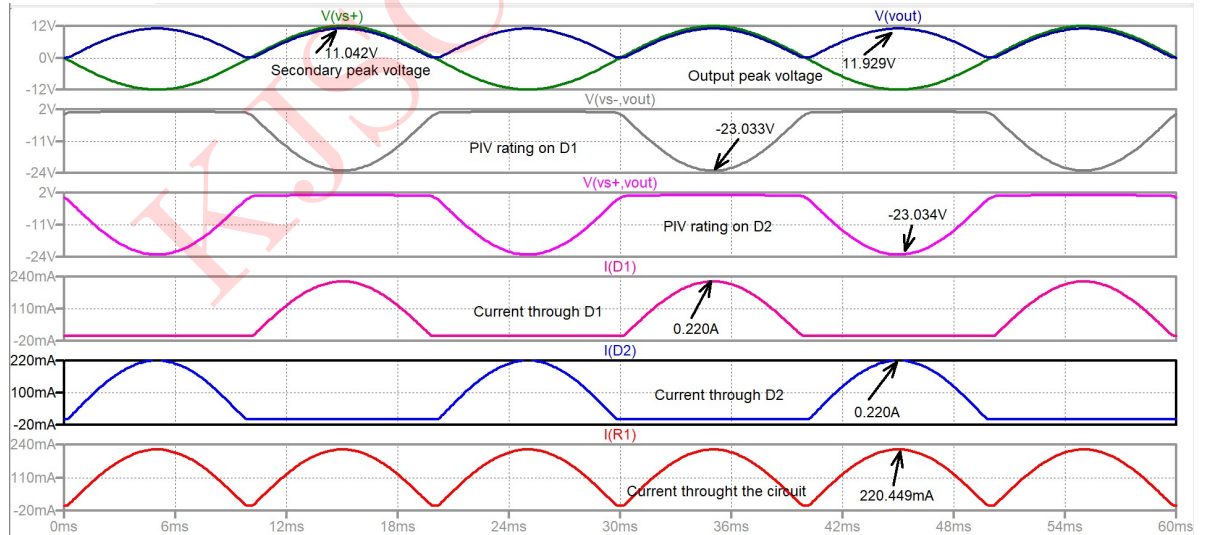


Figure 5: Circuit Waveforms

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

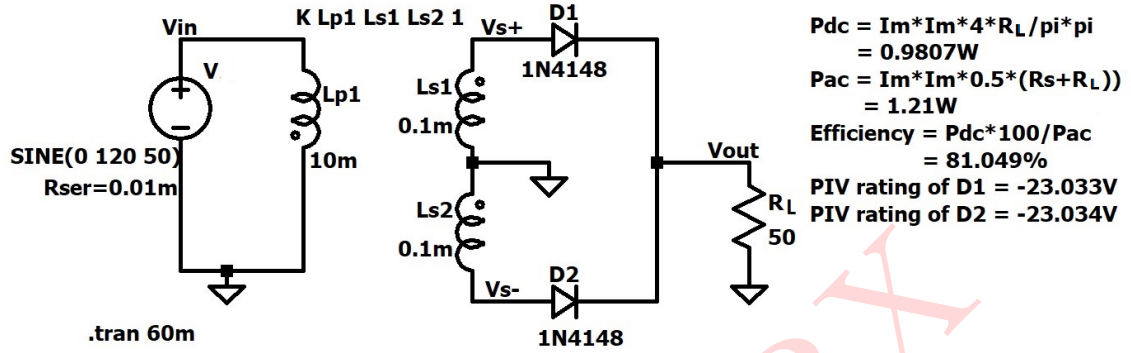


Figure 6: Circuit Schematic and Simulated Results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Output peak voltage (V_M)	11.3V	11.04V
Output peak current (I_M)	0.226A	0.220A
AC Power	1.276W	1.219W
DC Power	1.035W	0.9807W
Efficiency (η)	81.112%	81.049%
PIV rating on D1	-22.6V	-23.033V
PIV rating on D2	-22.6V	-23.034V

Table 2: Numerical 2