

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Differential Amplifier Circuits**

**Numerical 1:**

For the differential shown in figure 1 Find, a) Name of the circuit b) Q-point c) Differential voltage gain d) Common mode gain e) CMRR

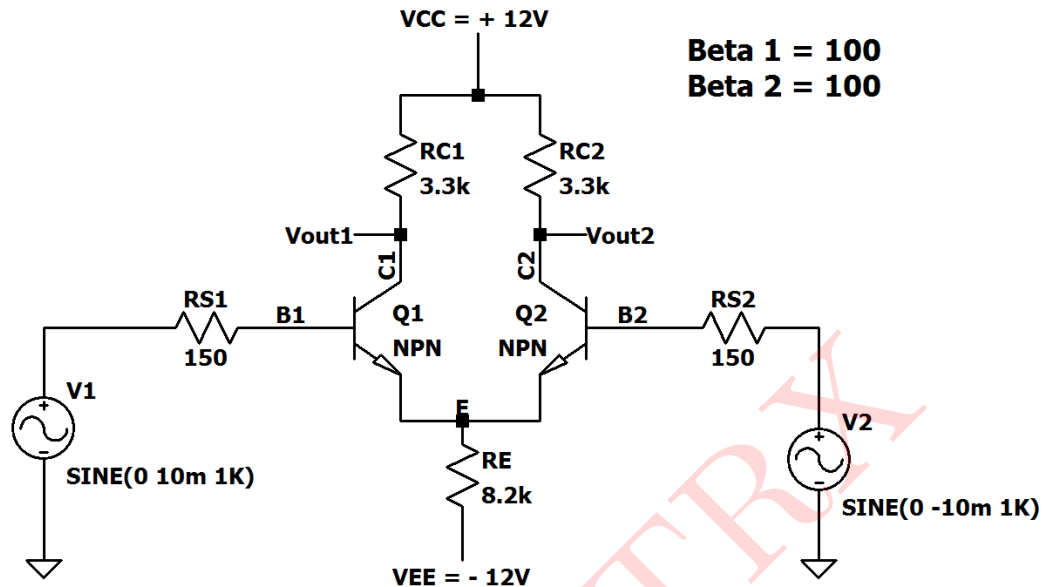


Figure 1: Circuit 1

**Solution:**

Above circuit 1 is a Dual Input Balanced Output(DIBO) differential amplifier

DC Analysis:-

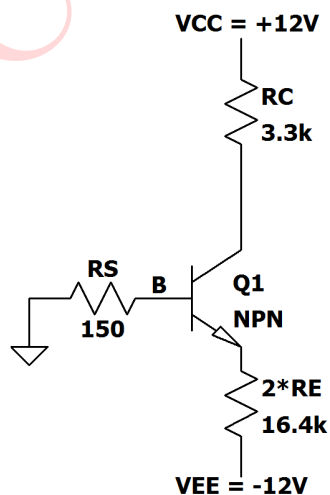


Figure 2: DC Equivalent Circuit

$$I_B = \frac{V_{EE} - V_{BE}}{R_S + 2(1 + \beta)R_E} = \frac{12 - 0.7}{150 + (2 \times 101 \times 8.2k)} = 6.82\mu A$$

$$\mathbf{I_B = 6.82\mu A}$$

$$I_C = \beta I_B = 100 \times 6.82\mu A = 0.68mA$$

$$\mathbf{I_C = 0.68mA}$$

$$\mathbf{I_{C_1} = I_{C_2} = I_C = 0.68mA}$$

$$V_{CE} = V_{CC} + V_{EE} - I_C(R_C + 2R_E) = 12 + 12 - 0.68mA(3.3k + 2 \times 8.2k) = 10.6V$$

$$\mathbf{V_{CE} = 10.6V}$$

$$V_{C_1} = V_{C_2} = V_{CC} - I_C R_C = 12 - (0.68 \times 3.3) = 9.756V$$

$$\mathbf{V_{C_1} = V_{C_2} = 9.756V}$$

$$V_{CE} = V_C - V_E$$

$$V_E = V_C - V_{CE} = 9.756 - 10.6 = -0.844V$$

$$\mathbf{V_{E_1} = V_{E_2} = -0.844V}$$

$$r_\pi = \frac{\beta V_T}{I_C} = \frac{100 \times 26mV}{0.68mA} = 3.82k\Omega$$

$$\mathbf{r_\pi = 3.82k\Omega}$$

$$|A_d| = \frac{\beta R_C}{R_S + r_\pi} = \frac{100 \times 3.3k}{150 + 3.82k} = 83.12$$

$$\mathbf{|A_d| = 83.12}$$

$$A_{cm} = \left| \frac{R_C}{2R_E} \right| = \left| \frac{3.3k}{2 \times 8.2k} \right| = 0.201$$

$$\mathbf{A_{cm} = 0.201}$$

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| = \frac{83.12}{0.201} = 413.53$$

$$CMRR = 413.53$$

$$CMRR_{dB} = 20 \log_{10}(413.53) = 52.33dB$$

$$\mathbf{CMRR_{dB} = 52.33dB}$$

### SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

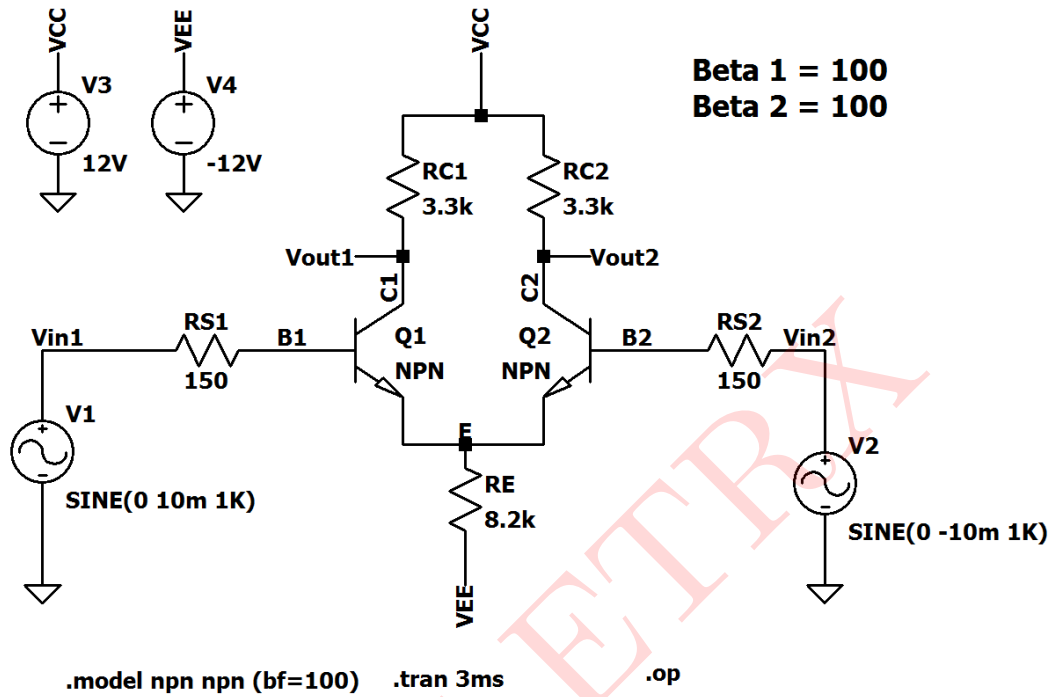


Figure 3: Circuit Schematic 1

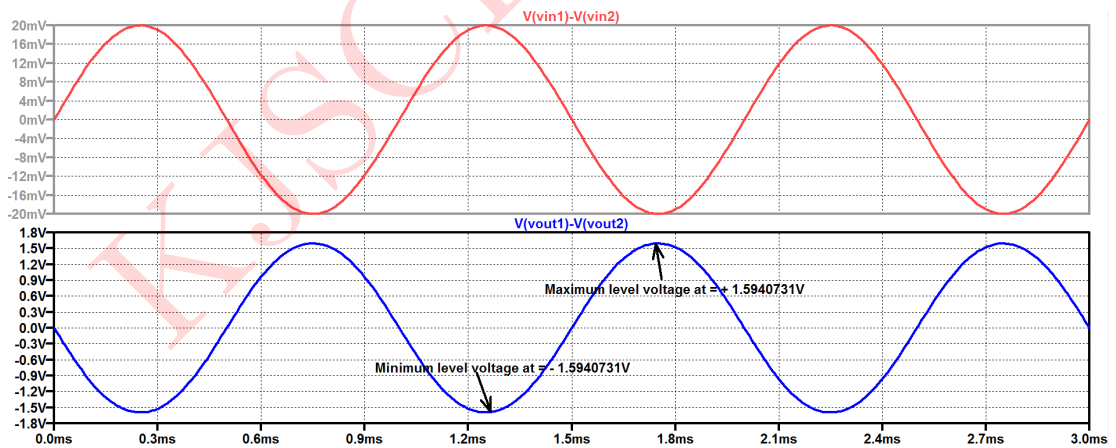


Figure 4: Input and Output Waveforms

**Comparison of Theoretical and Simulated Values:**

Parameters	Theoretical	Simulated
$I_{C_1}, I_{C_2}$	$0.68mA, 0.68mA$	$0.68mA, 0.68mA$
$V_{C_1}, V_{C_2}$	$9.76V, 9.76V$	$9.76V, 9.76V$
$V_{CE_1}, V_{CE_2}$	$10.6V, 10.6V$	$10.6V, 10.6V$
$ A_d $	83.12	79.71
$A_{cm}$	0.201	—
$CMRR_{dB}$	52.33	—

Table 1: Numerical 1

**Numerical 2:**

For the differential shown in figure 5 Find, a) Name of the circuit b) Current through  $R_{D1}$ ,  $R_{D2}$ ,  $R_{S1}$ ,  $R_{S2}$  c)  $V_{D1}$ ,  $V_{D2}$ ,  $V_{GS1}$ ,  $V_{GS2}$  d) Differential voltage gain e) Common mode gain f) CMRR in dB

Assume:  $V_{TN1} = V_{TN2} = 1V$ ,  $k_{n1} = k_{n2} = 50mA/V^2$

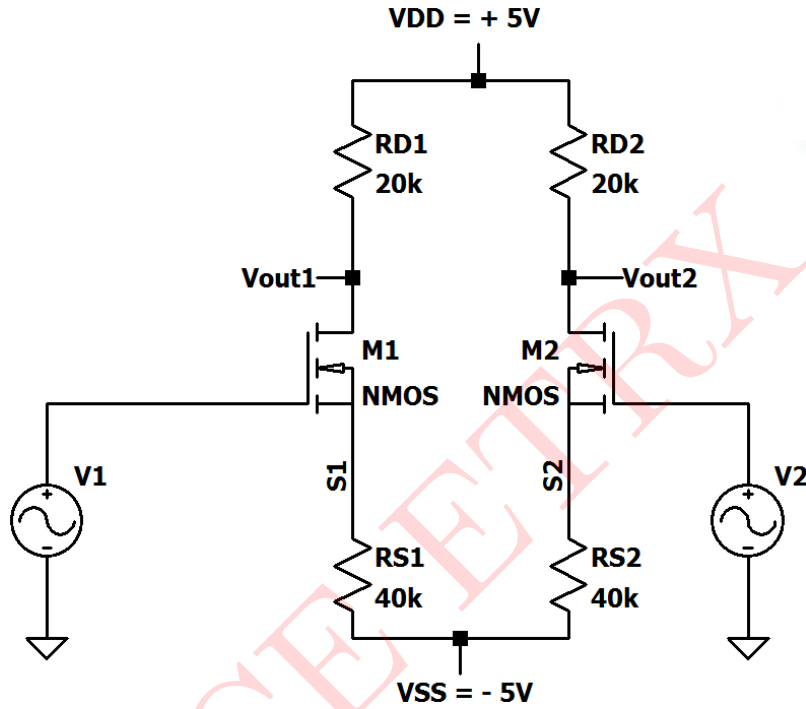


Figure 5: Circuit 2

**Solution:**

Above circuit 2 is a Dual Input Balanced Output(DIBO) differential amplifier

DC Analysis:-

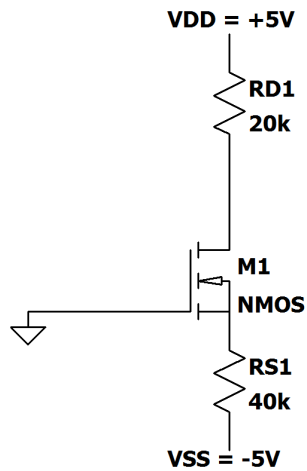


Figure 6: DC Equivalent Circuit

Apply KVL to the Gate-Source loop:-

$$V_{GS} = V_{SS} - I_D R_S$$

$$V_{GS} = 5 - I_D(40k) \quad \text{.....(1)}$$

$$I_D = k_n(V_{GS} - V_{TN})^2$$

$$I_D = 50 \times 10^{-6}(V_{GS} - 1)^2 \quad \text{.....(2)}$$

Putting 2 in 1, we get

$$V_{GS} = 5 - (40k \times 50 \times 10^{-6}(V_{GS} - 1)^2)$$

$$V_{GS} = 5 - 2(V_{GS}^2 + 1 - 2V_{GS})$$

$$V_{GS} = 5 - 2V_{GS}^2 - 2 + 4V_{GS}$$

$$2V_{GS}^2 - 3V_{GS} - 3 = 0$$

$$V_{GS} = 2.18V$$

or

$$V_{GS} = -0.686V \text{ [We reject this values as, } (V_{GS} > V_{TN})]$$

$$\therefore V_{GS} = \mathbf{2.18V}$$

From 1,

$$I_D = \frac{5 - V_{GS}}{40k} = \frac{5 - 2.18}{40k} = 70.5\mu A$$

$$\mathbf{I_D = 70.5\mu A}$$

Applying KVL to the Drain-Source loop:-

$$V_{DD} - I_D R_{D1} - V_{DS} - I_D R_{S1} - V_{GS} = 0$$

$$V_{DS1} = V_{DS2} - V_{DD} - I_D(R_{D1} + R_{S1}) - V_{GS}$$

$$V_{DS1} = 5 - (-5) - \frac{70.5}{10^6}(20k + 40k) = 5.77V$$

$$\mathbf{V_{DS1} = 5.77V}$$

$$V_{D1} = V_{DD} - I_D R_{D1} = 5 - (70.5\mu A \times 20k) = 3.59V$$

$$\mathbf{V_{D1} = V_{D2} = 3.59V}$$

$$g_{m1} = g_{m2} = g_m = 2k_n(V_{GS} - V_{TN}) = 2 \times 50 \times 10^{-6}(2.18 - 1) = 1.18 \times 10^{-4} A/V$$

$$\mathbf{g_{m1} = g_{m2} = g_m = 1.18 \times 10^{-4} A/V}$$

$$|A_d| = g_m R_D = 1.18 \times 10^{-4} \times 20 \times 10^3 = 2.36$$

$$|A_d| = \mathbf{2.36}$$

$$A_{cm} = \left| \frac{g_m R_D}{1 + g_m R_S} \right| = \left| \frac{1.18 \times 10^{-4} \times 20k}{1 + (1.18 \times 10^{-4} \times 40k)} \right| = 0.413$$

$$A_{cm} = \mathbf{0.413}$$

$$CMRR = \left| \frac{A_d}{A_{cm}} \right| = \frac{2.36}{0.413} = 5.714$$

$$CMRR = 5.714$$

$$CMRR_{dB} = 20 \log_{10}(5.714) = 15.14dB$$

$$CMRR_{dB} = \mathbf{15.14dB}$$

### SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

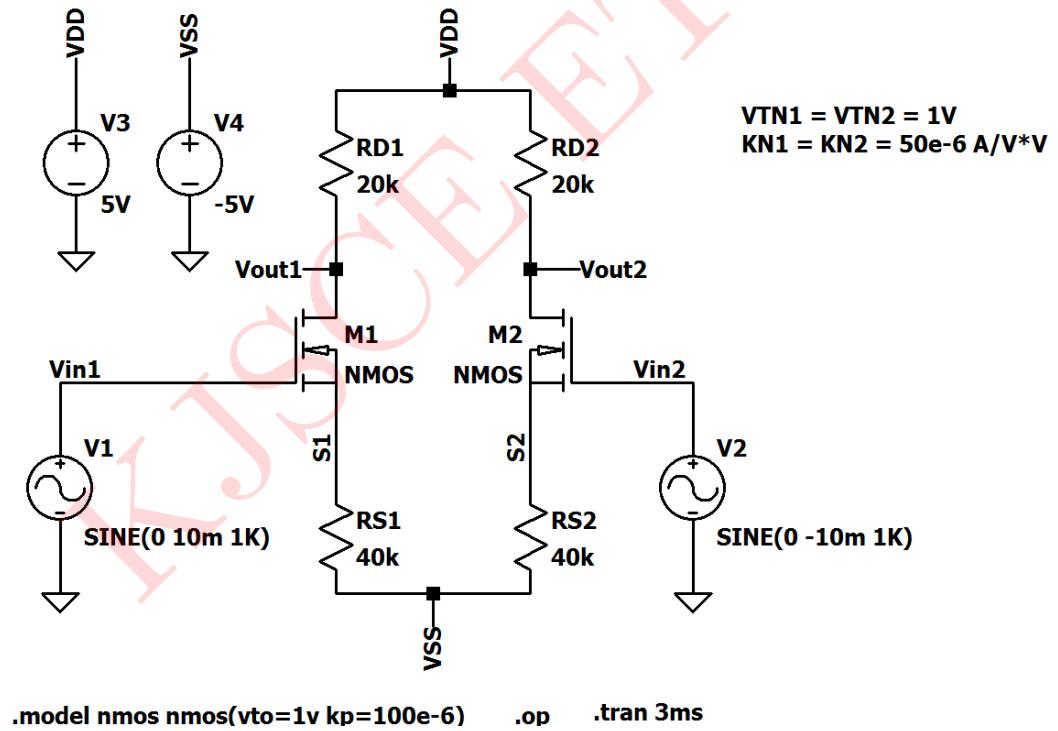


Figure 7: Circuit Schematic 2

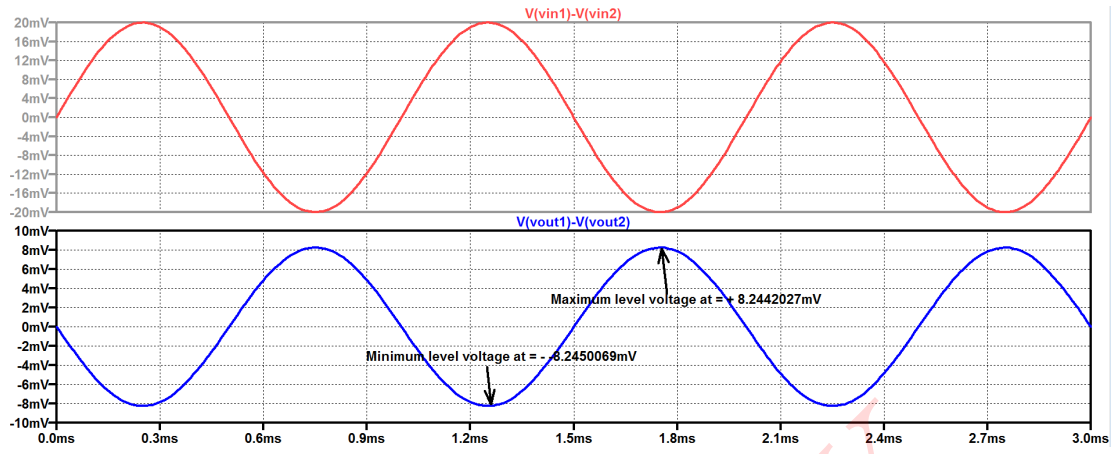


Figure 8: Input and Output Waveforms

#### Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
$I_{D_1}, I_{D_2}$	$70.5\mu A, 70.5\mu A$	$70.4\mu A, 70.4\mu A$
$V_{D_1}, V_{D_2}$	$3.59V, 3.59V$	$3.59V, 3.59V$
$V_{DS_1}, V_{DS_2}$	$5.77V, 5.77V$	$5.77V, 5.77V$
$ A_d $	2.36	2.41
$A_{cm}$	0.413	—
$CMRR_{dB}$	15.14	—

Table 2: Numerical 2



**Numerical 3:**

For the differential amplifier shown in figure 9, Find:- a) DC values of  $V_{out1}$ ,  $V_{out2}$   
b) Double ended output gain( $A_d$ ).

Given:  $\beta_1 = \beta_2 = 100$

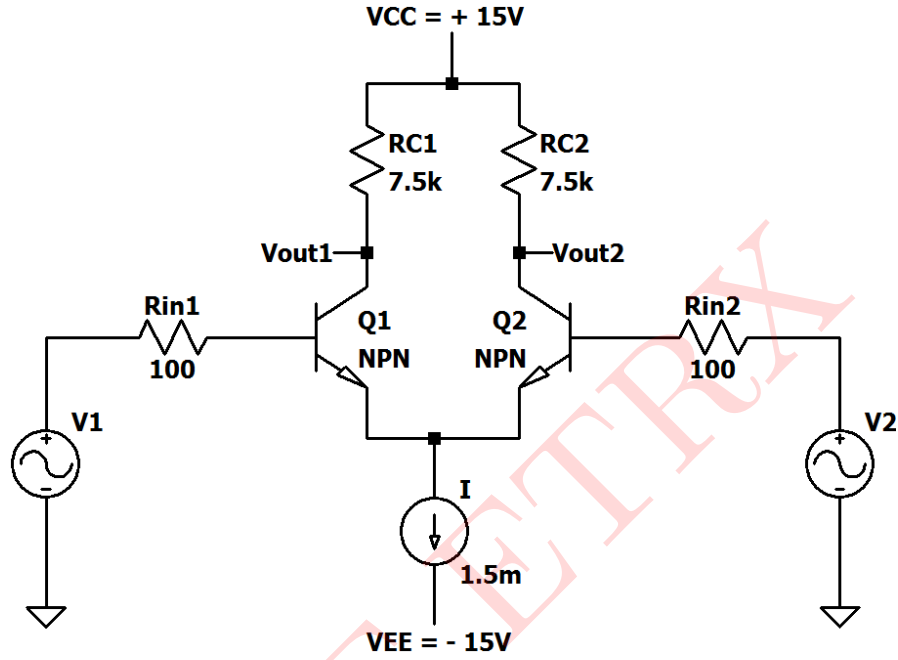


Figure 9: Circuit 3

**Solution:**

$$I_{E1} = I_{E2} = \frac{I}{2} = \frac{1.5mA}{2} = 0.75mA$$

Let,  $I_{C1} \approx I_{E1}$  &  $I_{C2} \approx I_{E2}$

$$\therefore I_{C1} = I_{C2} = 0.75mA$$

$$\text{DC value of } V_{out1} = V_{CC} - I_{C1}R_{C1} = 15 - (0.75mA \times 7.5k) = 9.375V$$

$$\therefore V_{out1} = V_{C1} = 9.375V \quad [\because V_{C1} = V_{out1}]$$

$$\text{DC value of } V_{out2} = V_{CC} - I_{C2}R_{C2} = 15 - (0.75mA \times 7.5k) = 9.375V$$

$$\therefore V_{out2} = V_{C2} = 9.375V \quad [\because V_{C2} = V_{out2}]$$

$$r_{\pi} = \frac{\beta V_T}{I_C} = \frac{100 \times 26mV}{0.75mA} = 3.467k\Omega$$

$$r_{\pi} = 3.467k\Omega$$

$$A_d = \frac{V_{out1} - V_{out2}}{V_1 - V_2} = \frac{-\beta R_C}{r_\pi + R_{in}}$$

$$A_d = \frac{-100 \times 7.5k}{3.467k + 100} = -210.26$$

$$A_d = -120.26$$

### SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

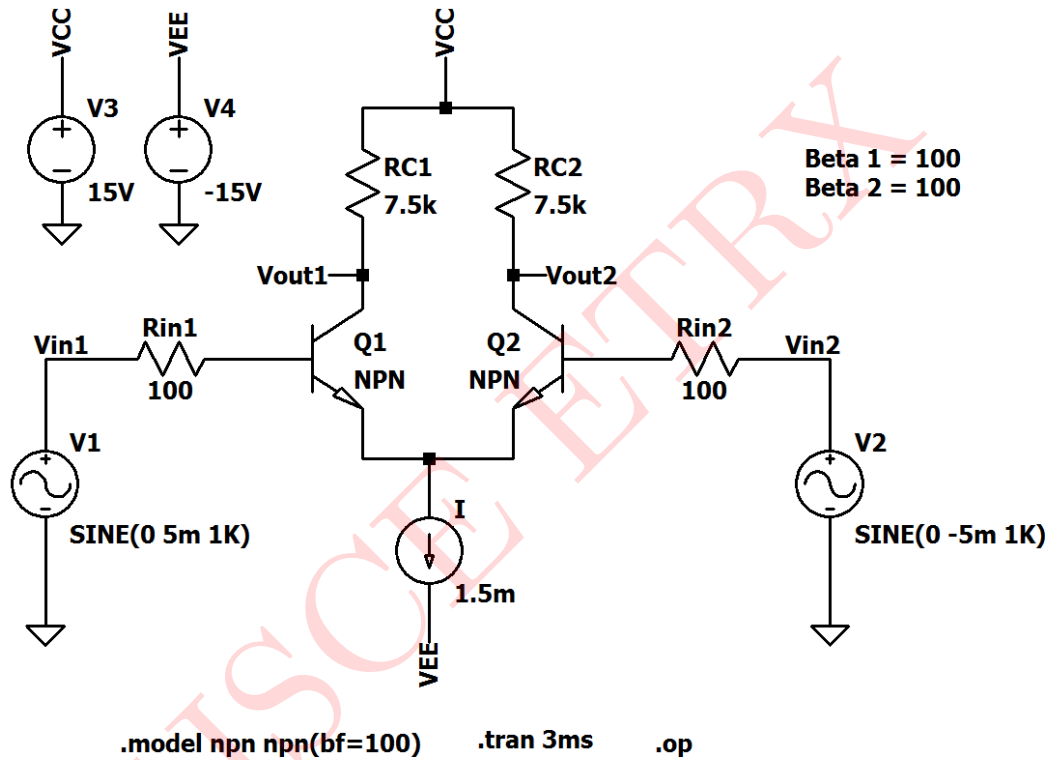


Figure 10: Circuit Schematic 3

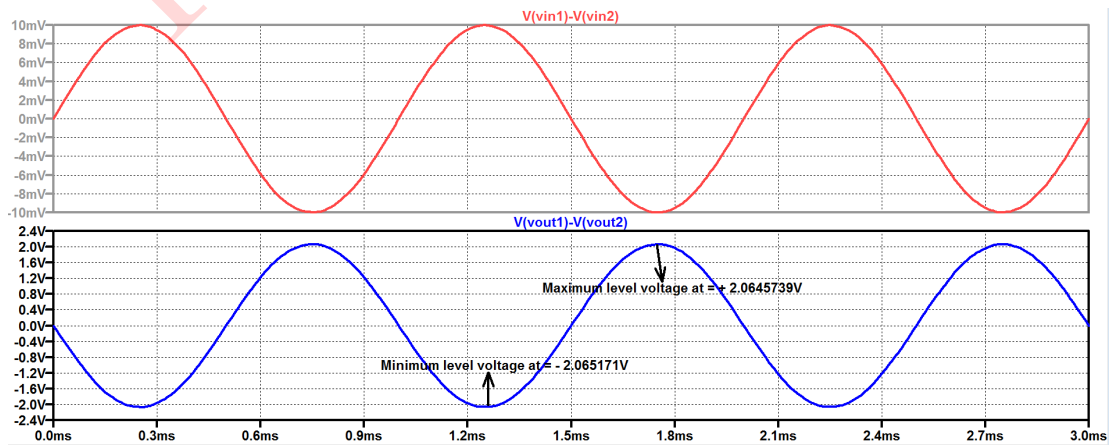


Figure 11: Input and Output waveforms

**Comparison of Theoretical and Simulated Values:**

Parameters	Theoretical	Simulated
$I_{C_1}, I_{C_2}$	$0.75mA, 0.75mA$	$0.74mA, 0.74mA$
$V_{C_1}, V_{C_2}$	$9.375V, 9.375V$	$9.43V, 9.43V$
$ A_d $	210.26	206.49

Table 3: Numerical 3

\*\*\*\*\*

KJSCE ETRX