

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Single Stage FET Amplifier**

**Numerical 1:**

For the circuit shown in figure 1, determine

a.  $I_{DQ}$ ,  $V_{GSQ}$  &  $V_{DSQ}$

b.  $A_V$ ,  $R_i$  &  $R_o$

JFET having  $I_{DSS} = 8mA$  &  $V_p = -4V$

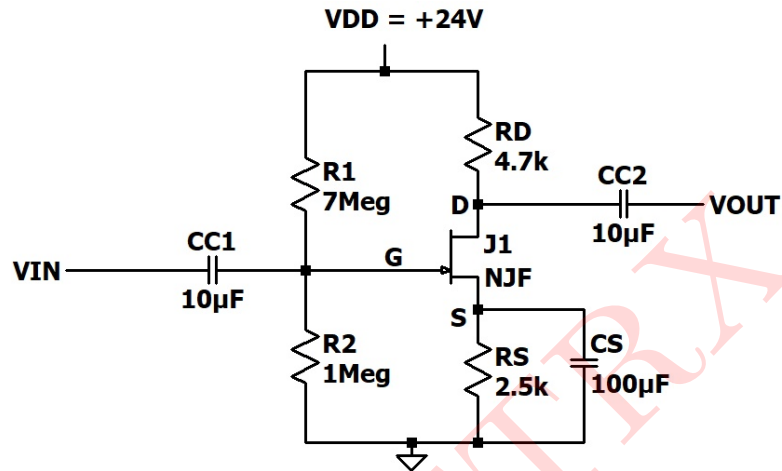


Figure 1: Circuit 1

**Solution:** The above circuit 1 is a common source JFET amplifier employing a n-channel JFET in voltage divider bias configuration

**DC Analysis:**

All capacitors acts as open circuited, since  $f = 0$

 


Figure 2: DC Equivalent Circuit

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$$

$$= \frac{1M\Omega}{1M\Omega + 7M\Omega} \times 24V = 3V$$

$$\begin{aligned}
V_S &= I_D R_S \\
V_{GS} &= 3 - I_D R_S \\
V_{GS} &= 3 - I_D (2.5k\Omega)
\end{aligned}
\tag{1}$$

Assuming JFET is working in saturation region,

$$\begin{aligned}
I_D &= I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2 \\
&= (8mA) \left( 1 + \frac{V_{GS}}{4} \right)^2
\end{aligned}
\tag{2}$$

Substituting equation (2) in equation (1), we get

$$\begin{aligned}
V_{GS} &= 3 - (20) \left( 1 + \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16} \right) \\
&= 3 - 20 - 10V_{GS} - 1.25V_{GS}^2 \\
1.25V_{GS}^2 + 11V_{GS} + 17 &= 0 \\
V_{GS} &= -2V \quad \text{or} \quad V_{GS} = -6.8V
\end{aligned}$$

Since  $V_{GS} > V_p$  for saturation,

$$\therefore V_{GSQ} = -2V$$

Applying KVL to input Gate Source loop,

$$V_{GS} = 3 - I_D R_S$$

$$I_D = \frac{3 - V_{GS}}{R_S}$$

$$I_D = \frac{3 - (-2)}{2.5k\Omega}$$

$$I_{DQ} = \mathbf{2mA}$$

Applying KVL to outer Drain Source loop,

$$V_{DD} - I_D R_S - V_{DS} - I_D R_S = 0$$

$$V_{DS} = 24 - I_D (R_D + R_S)$$

$$V_{DS} = 24 - (2mA)(4.7k\Omega + 2.5k\Omega)$$

$$V_{DSQ} = \mathbf{9.6V}$$

**Small Signal Analysis:**

$$\begin{aligned}
g_m &= \frac{2I_{DSS}}{|V_p|} \left( 1 - \frac{V_{GS}}{V_p} \right) \\
&= \frac{2 \times 8mA}{|4V|} \left( 1 - \frac{(-2V)}{-4V} \right) \\
&= \mathbf{2mA/V}
\end{aligned}$$

 


Figure 3: Small Signal Equivalent Circuit

#### Small Signal Voltage Gain ( $A_V$ ):

$$\begin{aligned} A_V &= -g_m R_D \\ &= (-2\text{mA/V})(4.7\text{k}\Omega) \\ &= -9.4 \end{aligned}$$

Negative sign of  $A_V$  indicates that the output waveform is  $180^\circ$  out of phase with input waveform

#### Input and Output Impedance:

Input Impedance ( $R_i$ ) =  $R_1 \parallel R_2$

$$R_i = 1\text{M}\Omega \parallel 7\text{M}\Omega = \mathbf{875\text{k}\Omega}$$

Output Impedance ( $R_o$ ) =  $R_D$

$$R_o = \mathbf{2\text{k}\Omega}$$

## SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

### JFET Parameters:

$V_p = -4V$

$IDSS = 8mA$

$V_{TO} = -4V$

$\beta = IDSS/V_p^2$   
 $= 0.5e-3mA/V^2$

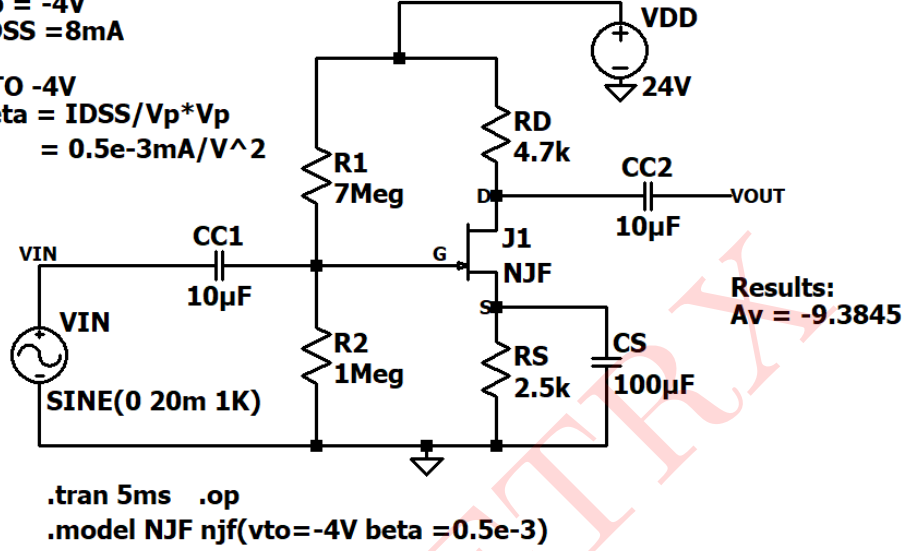


Figure 4: Circuit Schematic

The input and output waveform are shown in figure 5

 


Figure 5:  $V_{IN}(t)$  &  $V_{OUT}(t)$

**Comparison of Theoretical and Simulated results:**

Parameters	Theoretical	Simulated
$V_{GSQ}$	$-2V$	$-2V$
$V_{DSQ}$	$9.6V$	$9.6V$
$I_{DQ}$	$2mA$	$2mA$
$A_V$	$-9.4$	$-9.3845$

Table 1: Numerical 1

KJSCE ETRX

### Numerical 2:

Determine  $Z_i$ ,  $Z_o$  &  $A_V$  for the amplifier given in figure 6. Given  $k_n = 0.3\text{mA}/\text{V}^2$

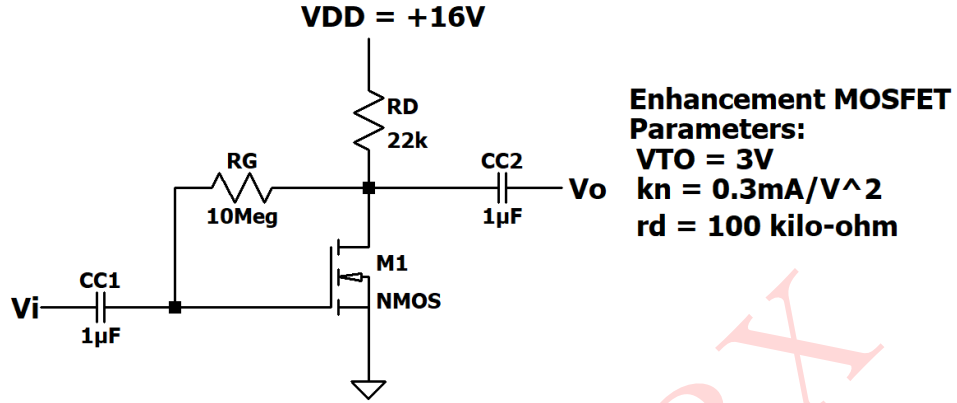


Figure 6: Circuit 2

**Solution:** The above circuit 2 is a common source enhancement type n-channel MOSFET amplifier in drain feedback configuration

### DC Analysis:

We remove all the capacitors as frequency is 0 and thus they are open circuited.

 


Figure 7: DC Equivalent Circuit

Since,  $I_G = 0$

$$\therefore V_{GS} \approx V_{DS}$$

Applying KVL to Drain Source loop,

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_{GS} = 16 - I_D(22k\Omega) \quad [\text{Since, } V_{GS} \approx V_{DS}] \quad \dots(1)$$

$$\begin{aligned} I_D &= k_n(V_{GS} - V_{TN})^2 \\ &= (0.3\text{mA}/\text{V}^2)(V_{GS} - 3\text{V})^2 \end{aligned} \quad \dots(2)$$

Substituting equation (2) in equation (1),

$$\begin{aligned} V_{GS} &= 16 - 6.6(V_{GS}^2 - 6V_{GS} + 9) \\ &= 16 - 6.6V_{GS}^2 + 39.6V_{GS} - 59.4 \end{aligned}$$

$$6.6V_{GS}^2 - 38.6V_{GS} + 43.4 = 0$$

$$\therefore V_{GS} = 4.3292V \quad \text{or} \quad V_{GS} = 1.5187V$$

$$\therefore V_{GS} > V_{TN}$$

$$\text{Thus, } V_{GSQ} = \mathbf{4.3297V}$$

From equation (1),

$$\begin{aligned} I_{DQ} &= \frac{16 - V_{GSQ}}{22k\Omega} \\ &= \frac{16 - 4.3297}{22k\Omega} \\ &= \mathbf{0.53046mA} \end{aligned}$$

Given that  $r_d = 100k\Omega$

$$\text{Also, } r_d = \frac{1}{\lambda I_{DQ}} \Rightarrow \lambda = \mathbf{0.01885V^{-1}}$$

**Small Signal Analysis:**

$$\begin{aligned} g_m &= 2k_n(V_{GSQ} - V_{TN}) \\ &= 2 \times (0.3mA/V^2)(4.3297 - 3) \\ &= \mathbf{0.7978mA/V} \end{aligned}$$

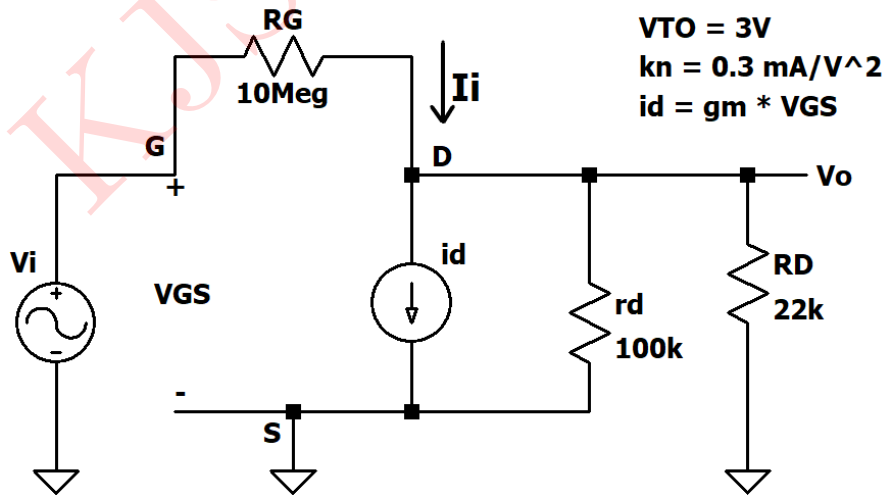


Figure 8: Small Signal Equivalent Circuit

From the figure 3 we can observe,

$$\begin{aligned} I_i &= g_m V_{gs} + \frac{V_o}{r_d \parallel R_D} \\ &= g_m V_i + \frac{V_o}{r_d \parallel R_D} \end{aligned}$$

[Since,  $V_{GS} = V_i$ ]

$$I_i - g_m V_i = \frac{V_o}{r_d \parallel R_D}$$

$$V_o = (r_d \parallel R_D)(I_i - g_m V_i)$$

$$I_i = \frac{V_i - V_o}{R_G} = \frac{V_i - (r_d \parallel R_D)(I_i - g_m V_i)}{R_G}$$

$$I_i R_G = V_i - (r_d \parallel R_D)I_i + (r_d \parallel R_D) g_m V_i$$

$$V_i[1 + g_m(r_d \parallel R_D)] = I_i[R_G + r_d \parallel R_D]$$

$$\frac{V_i}{I_i} = \frac{R_G + (r_d \parallel R_D)}{1 + g_m(r_d \parallel R_D)}$$

**Input and Ouput Impedance:**

$$\text{Input Impedance } (Z_i) = \frac{V_i}{I_i}$$

$$\begin{aligned} \therefore Z_i &= \frac{R_G + (r_d \parallel R_D)}{1 + g_m(r_d \parallel R_D)} \\ &= \frac{10M\Omega + (100k\Omega \parallel 22k\Omega)}{1 + (0.7978mA/V)(100k\Omega \parallel 22k\Omega)} \\ &= \frac{10M\Omega}{15.38655} \\ &= \mathbf{649.918k\Omega} \end{aligned}$$

For Ouput Impedance ( $Z_o$ ), we substitute  $V_i = 0V$ ,  $V_{GS} = 0$  &  $g_m V_{GS} = 0$ , with a short circuit from gate to ground

$$\begin{aligned} Z_o &= R_G \parallel r_d \parallel R_D \\ &= 10M\Omega \parallel 100k\Omega \parallel 22k\Omega \\ &= 99.009k\Omega \parallel 22k\Omega \\ &= \mathbf{18k\Omega} \end{aligned}$$

**Small Signal Voltage Gain ( $A_V$ ):**

$$A_V = \frac{V_o}{V_i}$$

From the small signal equivalent circuit,

Applying KCL at D,

$$I_i = g_m V_{gs} + \frac{V_o}{r_d \parallel R_D}$$

$$I_i = \frac{V_i - V_o}{R_G}$$

[Since,  $V_i = V_{gs}$ ]

$$\frac{V_i - V_o}{R_G} = g_m V_i + \frac{V_o}{r_d \parallel R_D}$$

$$V_i \left[ \frac{1}{R_G} - g_m \right] = V_o \left[ \frac{1}{R_G} + \frac{1}{r_d \parallel R_D} \right]$$



$$\therefore \frac{1}{R_G} \approx \text{very small}$$

$$\left[ \frac{1}{R_G} - g_m \right] \approx -g_m$$

$$\therefore V_i(-g_m) = V_o \left[ \frac{1}{R_G} + \frac{1}{r_d \parallel R_D} \right]$$

$$\frac{V_o}{V_i} = \frac{-g_m}{\frac{1}{R_G \parallel r_d \parallel R_D}}$$

$$\begin{aligned} \therefore A_V &= \frac{V_o}{V_i} = -g_m(R_G \parallel r_d \parallel R_D) \\ &= -(0.7978 \text{ mA/V})(10 \text{ M}\Omega \parallel 100 \text{ k}\Omega \parallel 22 \text{ k}\Omega) \\ &= -(0.7978 \text{ mA/V})(99.009 \text{ k}\Omega \parallel 22 \text{ k}\Omega) \\ &= -(0.7978 \text{ mA/V})(18 \text{ k}\Omega) \\ &= -14.3604 \end{aligned}$$

Negative sign of  $A_V$  indicates that the output waveform is  $180^\circ$  out of phase with input waveform

### SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

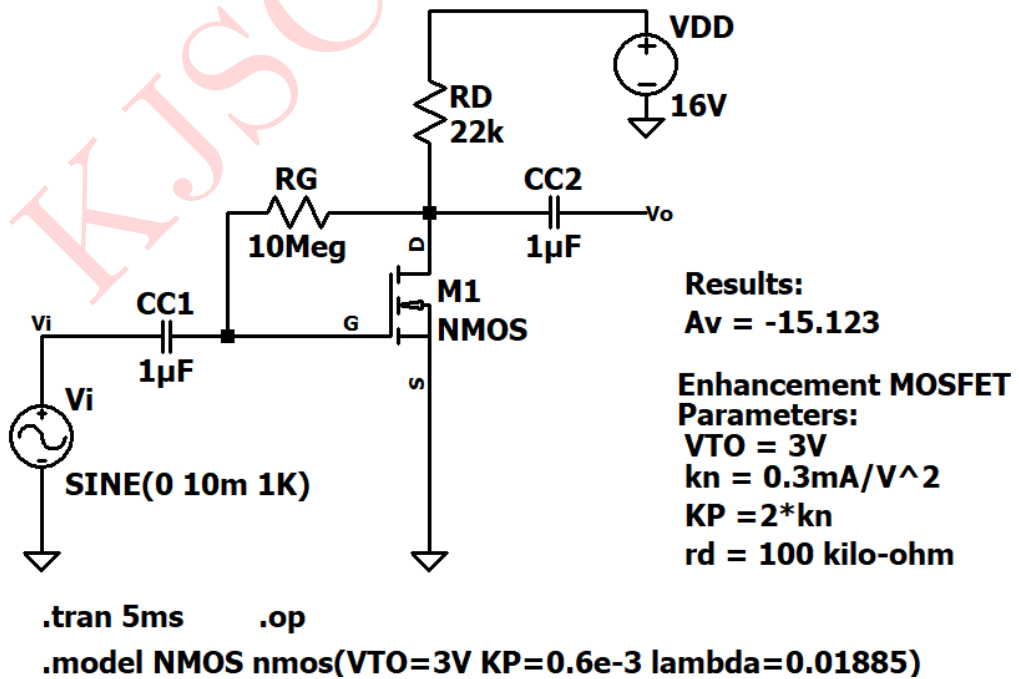


Figure 9: Circuit Schematic

The input and output waveform are shown in figure 10

 


Figure 10:  $V_{IN}(t)$  &  $V_{OUT}(t)$

#### Comparison of Theoretical and Simulated results:

Parameters	Theoretical	Simulated
$I_{DQ}$	$0.53046mA$	$0.532648mA$
$V_{GSQ}$	$4.3297V$	$4.28175V$
$A_V$	$-14.3604$	$-15.123$

Table 2: Numerical 2

\*\*\*\*\*