

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Cascade Amplifier Design

- Q1. Design a two stages RC coupled cascade amplifier for the following specifications:
 $V_o = 3V$, $R_i \geq 1M\Omega$, $|A_v| \geq 220$
 Calculate A_v , R_i , R_o

Solution:

- 1) For the above requirement we can use CS-CS self bias JFET amplifier:

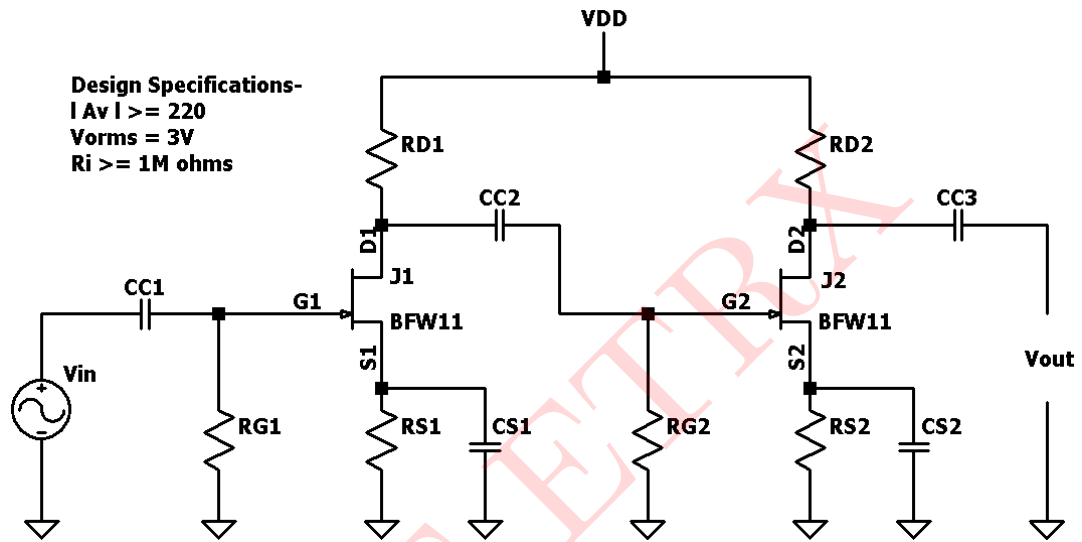


Figure 1: Self biased Circuit 1

We select n channel JFET BFW11 from the datasheet with the following specifications:

$$g_{mo} = 5600\mu S, V_p = -2.5V, r_d = 50k\Omega, I_{DSS} = 7mA$$

2) Selection of voltage gain:

$$A_v \geq 220$$

$$\text{let } A_v = 240 \text{ also, let } A_{V_1} = 0.6A_{V_2}$$

$$A_{V_t} = A_{V_1} \times A_{V_2}$$

$$240 = 0.6A_{V_1}^2$$

$$A_{V_1} = 12 \text{ and } A_{V_2} = 20$$

3) Selection of Q point:

a) For mid point biasing: $I_D = \frac{I_{DSS}}{2} = \frac{7}{2} = 3.5mA$

b) $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$

$$\frac{3.5}{7} = \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$0.5 = \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$V_{GS} = V_p \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$$

$$V_{GS} = -2.5 \left(1 - \sqrt{\frac{1}{2}}\right)$$

$$V_{GS} = -0.732V$$

c) Calculation g_m :

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p}\right)$$

$$g_m = 5600 \times 10^{-6} \left(1 - \frac{-0.732}{-2.5}\right)$$

$$g_m = 3.96m\Omega$$

4) Selection of R_{S2} :

$$V_{GS2} = V_G - V_S \quad (V_G = 0 \because \text{self biased})$$

$$V_{GS2} = -V_S$$

$$V_{GS2} = -I_D R_{S2}$$

$$R_{S2} = -V_{GS2}/I_D = -(-0.732)/3.5mA = 209.142\Omega, 1/4 \text{ W (H.S.V)}$$

Select $R_S = 180\Omega, 1/4 \text{ W (H.S.V)}$

5) Selection of R_{D2} :

$$A_v = g_m(r_d || R_{D2})$$

$$20 = 3.96 \times 10^{-3}(50 \times 10^3 || R_{D2})$$

$$R_{D2} = 5.617k\Omega$$

Select $R_{D2} = 6.2k\Omega, 1/4 \text{ W (H.S.V)}$

6) Selection of R_{G2} :

Select $R_{G2} = 1M\Omega, 1/4 \text{ W (H.S.V)}$

7) Selection of V_{DD} :

Applying KVL at DS loop for JFET

$$V_{DD} - I_{DQ2}R_{D2} - V_{DSQ2} - I_{DQ2}R_{S2} = 0$$

$$V_{DD} = I_{DQ2}(R_{D2} + R_{S2}) + V_{DSQ2}$$

$$V_{DS} \geq V_{o(peak)} + |V_p|$$

$$V_{DS} = 1.5(V_{o(peak)} + 2.5)$$

$$V_{DS} = 1.5(2\sqrt{3} + 2.5)$$

$$V_{DS} \geq 10.113V$$

$$V_{DS} = 10.2V$$

$$V_{DD} = 3.5 \times 10^{-3}(6.2 \times 10^3 + 180) + 10.2$$

$$V_{DD} = 32.53V$$

Select $V_{DD} = 34V$

8) Selection of R_{D1} :

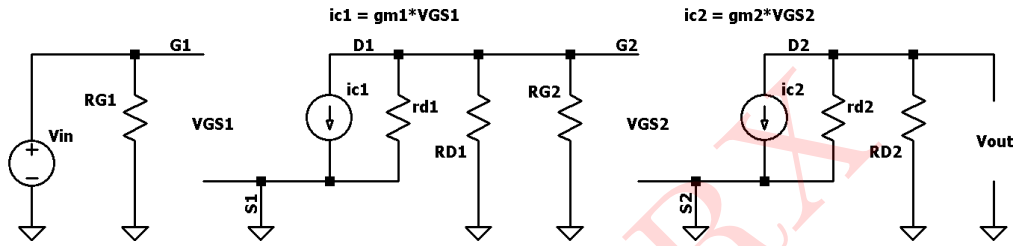


Figure 2: Mid Band AC equivalent circuit

$$A_{V_2} = g_m(r_d || R_{D2}) = 3.96(50k || 6.2k)$$

$$A_{V_2} = 21.8450$$

$$A_{V_1} = \frac{A_V}{A_{V_2}} = \frac{240}{21.8450} = 10.986$$

$$A_{V_1} = 11$$

$$A_{V_1} = g_m(r_{d1} || R_{D1} || R_{G2})$$

$$11 = 3.9063m(R_{D1} || 47.62k)$$

$$R_{D1} = 2.949k\Omega \text{ (select H.S.V)}$$

$$\text{Select } R_{D1} = 3.3k\Omega, 1/4W$$

9) Selection of R_{S1} :

$$V_{GS} = V_G - V_S \quad (V_G = 0 \because \text{self biased})$$

$$V_{GS} = -V_S$$

$$V_{GS} = -I_D R_S$$

$$R_S = -V_{GS}/I_D = -(-0.732)/3.5mA = 209.142\Omega, 1/4 W \text{ (H.S.V)}$$

$$\text{Select } R_S = 180\Omega, 1/4 W \text{ (H.S.V)}$$

10) Selection of R_{G1} :

To avoid the effect and fulfill requirement

$$R_{G1} \geq 1M\Omega$$

$$\text{Select } R_{G1} \geq 1M\Omega, 1/4 W \text{ (H.S.V)}$$

11) Selection of C_{C1} , C_{C2} , C_{C3} :

a) Selection of C_{C1} :

$$C_{C1} = \frac{1}{2\pi \times f_{LCC1} R_{G1}} \quad (f_{LCC1} = f_L \leq 20Hz)$$

$$R_{eq} = R_G = 1.2M\Omega$$

$$C_{C1} = \frac{1}{2\pi \times 20 \times 1.2 \times 10^6}$$

$$C_{C1} = 6.631 \text{ nF}$$

Small signal equivalent circuit:

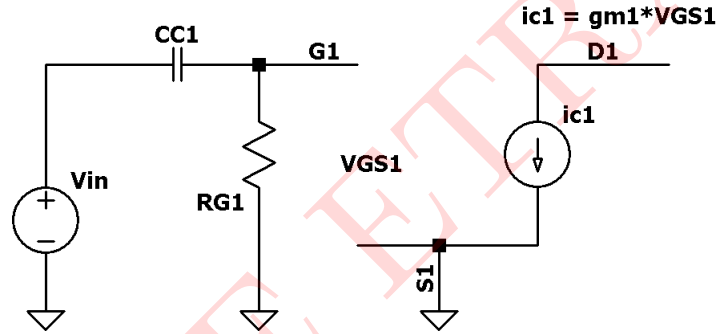


Figure 3: Small signal equivalent circuit for CC1

Select $C_{C1} = 8.2 \text{ nF}$, 50V (H.S.V)

b) Selection of C_{C2} :

$$C_{C2} = \frac{1}{2\pi \times f_{LCC2} R_{eq}} \quad (f_{LCC2} = f_L \leq 20Hz)$$

$$R_{eq} = (r_d || R_D) + R_{G2} = (2.7 \times 10^3 || 20 \times 10^3) 1.2 \times 10^6 = 1.00309M\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 1.00309 \times 10^6 \times 20}$$

$$C_{C2} = 7.9332\text{nF}$$

Select $C_{C2} = 8.2\mu\text{F}$, 50V (H.S.V)

Small signal equivalent circuit:

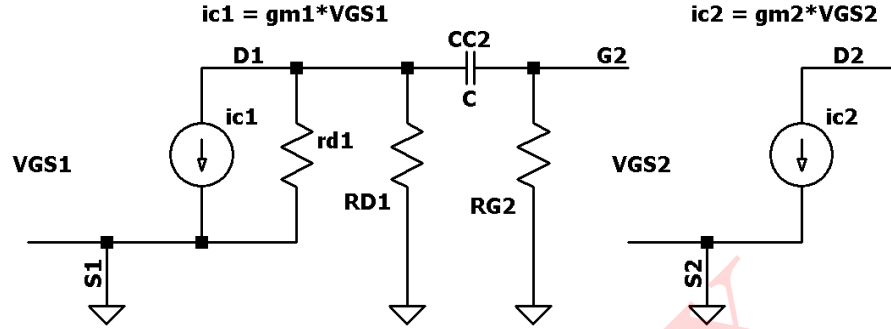


Figure 4: Small signal equivalent circuit for CC2

c) Selection of C_{C3} :

$$C_{C3} = \frac{1}{2\pi \times f_{LCC2} R_{eq}} \quad (f_{LCC3} = f_L \leq 20Hz)$$

$$R_{eq} = (r_{d2} || R_{D2}) = 5.516k\Omega$$

$$C_{C3} = \frac{1}{2\pi \times 5.516 \times 10^3 \times 20}$$

$$C_{C3} = 1.442nF$$

Select $C_{C3} = 1.5 \mu F, 50V$ (H.S.V)

12) Selection of C_{S1}, C_{S2} :

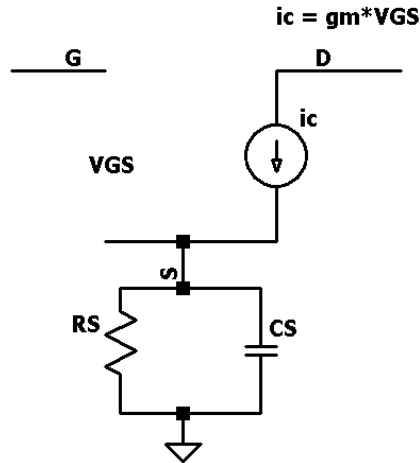


Figure 5: Small signal equivalent circuit for CS

$$g_m = g_{m1} = g_{m2} \text{ and } R_{S1} = R_{S2} = 180\Omega$$

$$C_{S1} = C_{S2} = \frac{1}{2\pi \times f_{LCS} R_{eq}}$$

$$R_{eq} = \frac{1}{g_m} || R_S = \frac{1}{3.9603 \times 10^{-3}} || 180 = 105.0887$$

$$C_{S1} = C_{S2} = \frac{1}{2\pi \times 105.0877 \times 20} = 75.724\mu F$$

$$C_S \geq 361.715\mu F$$

Select $C_{S1} = C_{S2} = 82\mu F$, 50V (H.S.V)

13) Designed Circuit is:

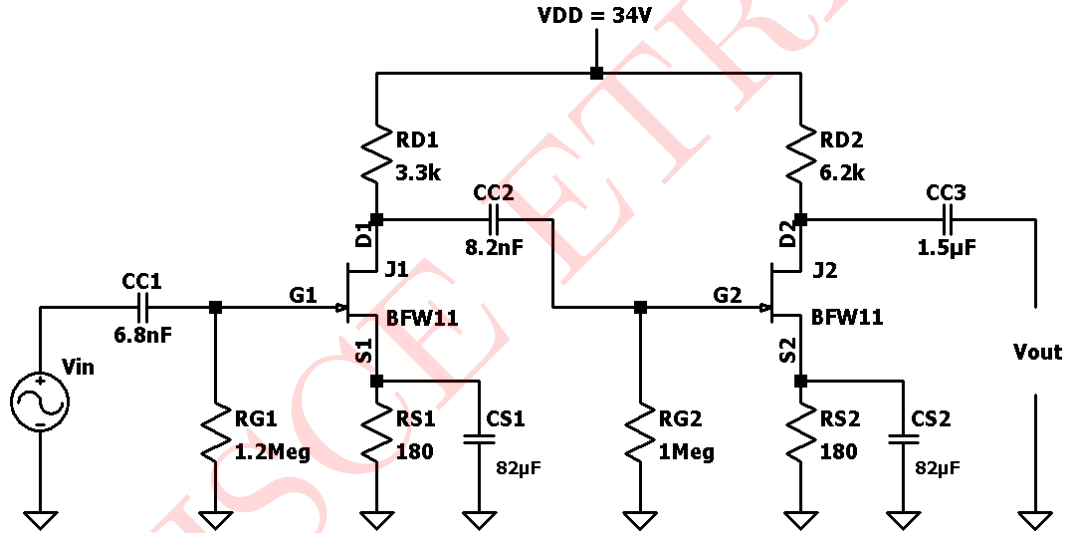


Figure 6: Designed circuit 1

Verification of overall gain:

$$Z_i = R_g$$

$$Z_o = r_{d2} || R_{D2}$$

$$A_{V_2} = g_m(r_{d2} || R_{D2}) = 3.96m(50k || 6.2k)$$

$$A_{V_2} = -21.8450$$

$$A_{V_1} = g_m(r_{d1} || R_{D1} || R_{G2}) = 3.96m(50k || 3.3k || 1.2M)$$

$$A_{V_1} = -12.22$$

$$A_{V_T} = A_{V_2} \times A_{V_1} = -21.845 \times -12.22$$

$$A_{V_T} = \mathbf{266.94} (\because A_V \geq 220)$$

$$A_{V_T} = 20\log_{10}(266.94)$$

$$A_{V_T} = \mathbf{48.528 \text{ dB}}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

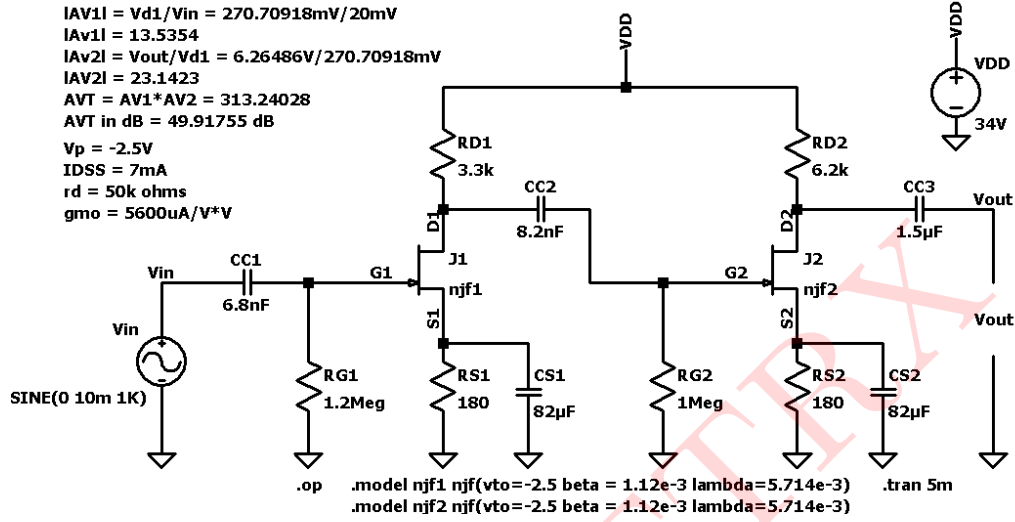


Figure 7: Circuit schematic 1

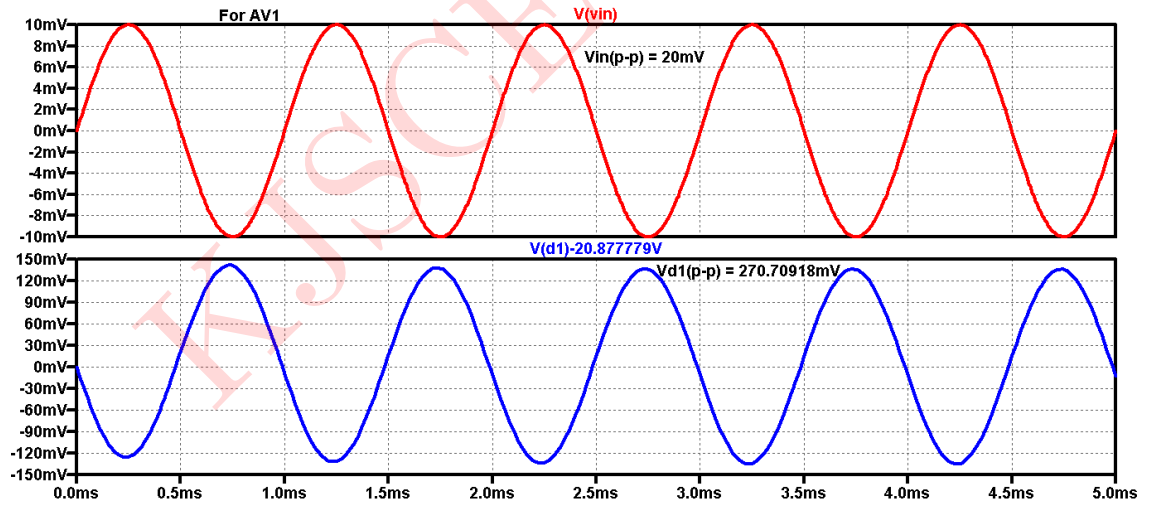


Figure 8: Circuit Schematic: Input Output Waveform AV_1

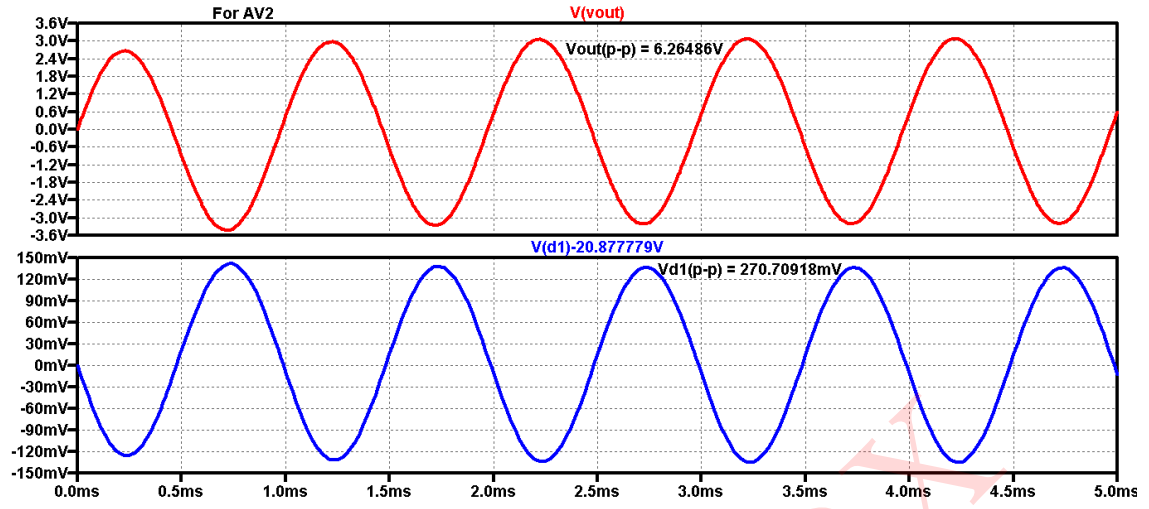


Figure 9: Circuit Schematic: Input Output Waveform A_{V_2}

Comparision between observed and theoretical values :

Parameters	Observed	Theoretical
I_{DQ1}, V_{GSQ1}	3.738mA, $-0.6729V$	3.5mA, $-0.732V$
I_{DQ2}, V_{GSQ2}	3.738mA, $-0.6729V$	3.5mA, $-0.732V$
A_{V_1}	-13.5354	-12.22
A_{V_2}	-23.1423	-21.845
A_{V_T} in dB	49.9175	48.5284
Z_i	$-$	$1.2M\Omega$
Z_o	$-$	$5.516k\Omega$

Table 1: Numerical 1

- Q2. Design a two stages RC coupled cascade amplifier for the following specifications:
 $V_{CC} = 20V$, $R_i \geq 1M\Omega$, $|A_v| \geq 450$, $S \leq 8$
 Calculate A_v , R_i , R_o

Solution:

1) For the above requirement we can use CS-CE self bias JFET amplifier:

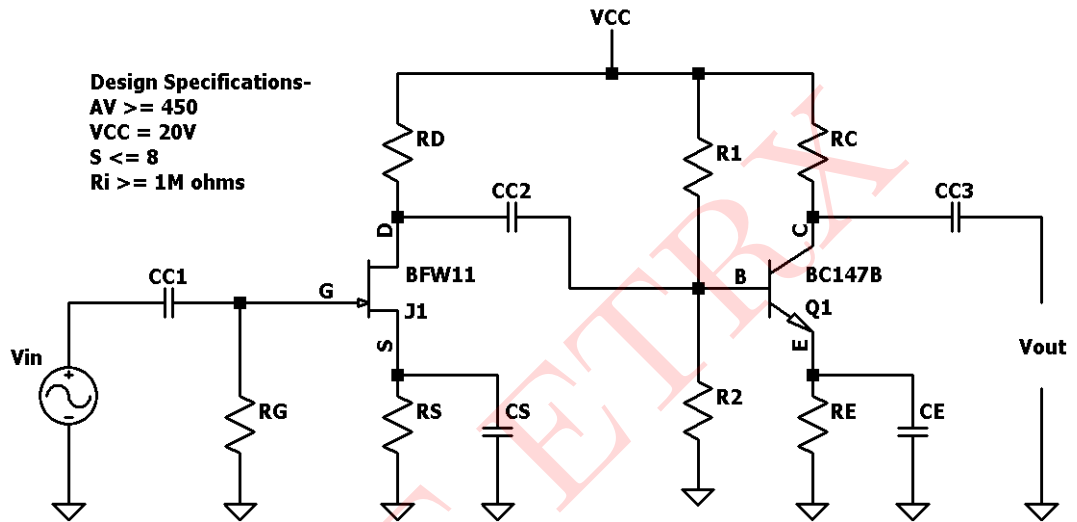


Figure 10: Self biased Circuit 2

We select n channel JFET BFW11 from the datasheet with the following specifications:

$$g_{mo} = 5600\mu S, V_p = -2.5V, r_d = 50k\Omega, I_{DSS} = 7mA$$

We select BC147B BJT amplifier from the datasheet with the following specifications:

$$h_{fe(typ)} = 330, \beta = 290, V_{ce(sat)} = 0.25V, h_{ie} = 4.5k\Omega$$

2) Selection of voltage gain:

$$A_v \geq 450$$

$$\text{let } A_v = 450 \text{ also, let } A_{V_1} = 4, A_{V_2} = 450/4 = 112.2 \approx 120$$

$$A_{V_1} = 4 \text{ and } A_{V_2} = 120$$

Design of 2nd Stage:

3) Selection of R_C :

$$A_{V_2} = \frac{h_{fe(typ)} R_C}{h_{ie}}$$

$$120 = \frac{330 \times R_C}{4.5k}$$

$$R_C = 1.636k\Omega$$

Select $R_C = 1.636k\Omega$, $1/4$ W (H.S.V)

4) Selection of Q point:

$$V_{CC} = 20V$$

$$V_{CEQ} = V_{CC}/2 = 10V$$

$$V_{RE} = 0.1V_{CC} = 0.1 \times 20 = 2$$

KVL to C-E loop of BJT

$$V_{CC} - V_{RC} - V_{CEQ} = V_{RE} = 0$$

$$V_{RC} = V_{CC} - V_{CEQ} - V_{RE} = 20 - 12 = 8$$

$$V_{RC} = I_{CQ}R_C = 8$$

$$I_{CQ} = \frac{V_{RC}}{R_C} = \frac{8}{1.8k} = 4.44mA$$

5) Selection of R_E :

$$V_{RE} = 2V$$

$$I_{EQ}R_E = 2$$

$$R_E = \frac{2}{I_{CQ}} = \frac{2}{4.44mA} = 450.45\Omega$$

Select $R_E = 420\Omega$, $1/4$ W (H.S.V)

6) Selection of R_1 and R_2 :

$S \leq 8$, let $S = 7$

$$S = \frac{1 + \beta}{1 + \beta \left(\frac{R_E}{R_B + R_E} \right)}$$

$$7 = \frac{1 + 290}{1 + 290 \left(\frac{420}{R_B + 420} \right)}$$

$$R_B = 2.582k\Omega$$

$$R_B = R_1 || R_2 = 2.582k \text{ ——— (1) }$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} \text{ ——— (2) }$$

KVL at B-E loop

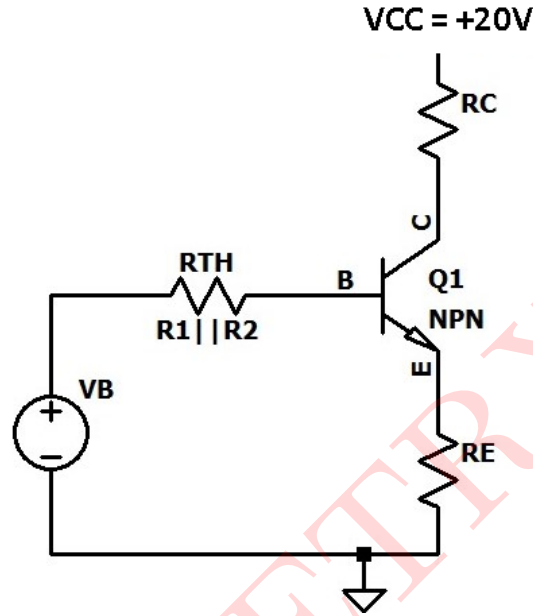


Figure 11: DC equivalent circuit

$$V_B - I_{BQ}R_B - V_{BE} - I_{EQ}R_E = 0$$

$$V_B = I_{CQ}R_B/\beta + V_{BE} + I_{CQ}R_E$$

$$V_B = 4.44 \times 2.582/290 + 0.7 + 4.44m \times 420 = 2.6V$$

Now from (2)

$$2.6 = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$\frac{R_2}{R_1 + R_2} = 0.13 \text{ ——— (3)}$$

Solving equations (3) and (1)

$$R_1(0.13) = 2.582k$$

$$R_1 = 19.86k\Omega$$

Select $R_1 = 22k\Omega$, 1/4 W (H.S.V)

From (3)

$$\frac{R_2}{22k + R_2} = 0.13$$

$$R_2 = 3.287k\Omega$$

Select $R_2 = 3.3k\Omega$, 1/4 W (H.S.V)

Design of 1st Stage:

7) Selection of Q point:

a) For mid point biasing: $I_D = \frac{I_{DSS}}{2} = \frac{7}{2} = 3.5\text{mA}$

b) $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$

$$\frac{3.5}{7} = \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$0.5 = \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$V_{GS} = V_p \left(1 - \sqrt{\frac{I_D}{I_{DSS}}}\right)$$

$$V_{GS} = -2.5 \left(1 - \sqrt{\frac{1}{2}}\right)$$

$$V_{GS} = -0.732\text{V}$$

c) Calculation g_m :

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_p}\right)$$

$$g_m = 5600 \times 10^{-6} \left(1 - \frac{-0.732}{-2.5}\right)$$

$$g_m = 3.96\text{mS}$$

8) Selection of R_S :

$$V_{GS} = -I_D R_S$$

$$R_S = -V_{GS}/I_D = -(-0.732)/3.5\text{mA} = 209.142\Omega, 1/4 \text{ W (H.S.V)}$$

Select $R_S = 180\Omega, 1/4 \text{ W (H.S.V)}$

9) Selection of R_D :

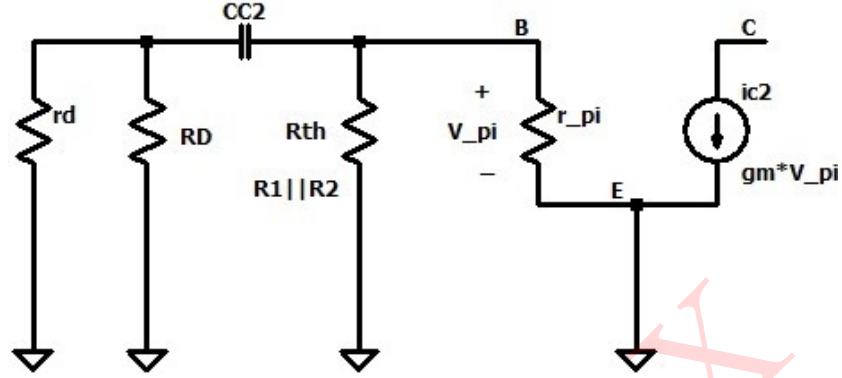


Figure 12: Small signal equivalent circuit for R_D

$$A_{V_2} = \frac{h_{fe(typ)R_C}}{h_{ie}} = \frac{330 \times 1.8k}{4.5k} = 132$$

$$A_{V_1} = \frac{A_V}{A_{V_2}} = 450/132 \approx 3.41$$

$$A_{V_1} = 3.5$$

$$A_{V_1} = -g_m(r_d || R_D || R_1 || R_2 || h_{ie})$$

$$3.5 = 3.96 \times 10^{-3}(R_D || 1.69k)$$

$$R_{D2} = 1.853k\Omega$$

Select $R_{D2} = 2.2k\Omega$, 1/4 W (H.S.V)

10) Selection of R_G :

Select $R_G = 1M\Omega$, 1/4 W (H.S.V)

11) Selection of C_{C1} , C_{C2} , C_{C3} :

a) Selection of C_{C1} :

$$C_{C1} = \frac{1}{2\pi \times f_{LCC1} R_G} \quad (f_{LCC1} = f_L \leq 20Hz)$$

$$R_{eq} = R_G = 1.2M\Omega$$

$$C_{C1} = \frac{1}{2\pi \times 20 \times 1.2 \times 10^6}$$

$$C_{C1} = 6.631 \text{ nF}$$

Select $C_{C1} = 6.8 \text{ nF}$, 50V (H.S.V)

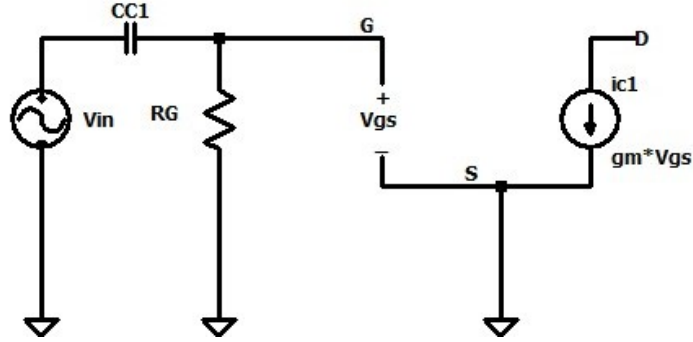


Figure 13: Small signal equivalent circuit for CC1

b) Selection of C_{C2} :

$$C_{C2} = \frac{1}{2\pi \times f_{LCC2} R_{eq}} \quad (f_{LCC2} = f_L \leq 20Hz)$$

$$R_{eq} = (r_d || R_D) + R_1 || R_2 || h_{ie} = (50k || 2.2k) 22k || 3.3k || 4.5k = 3.856k\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 3.856 \times 10^3 \times 20}$$

$$C_{C2} = 2.06\mu F$$

Select $C_{C2} = 2.2\mu F$, 50V (H.S.V)

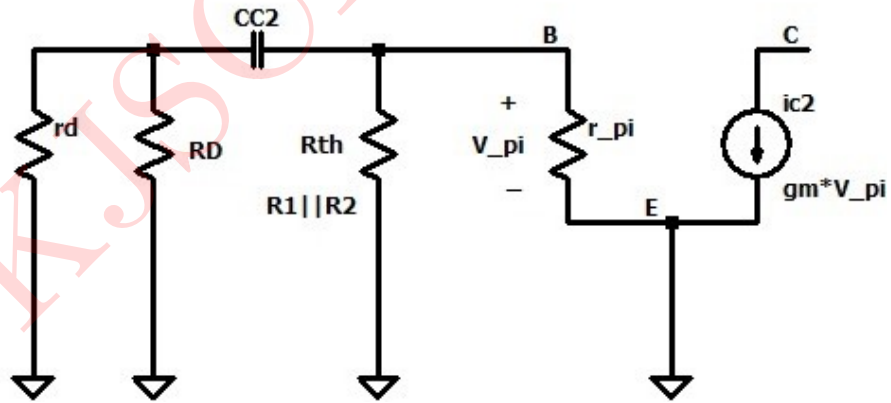


Figure 14: Small signal equivalent circuit for CC2

c) Selection of C_{C3} :

$$C_{C3} = \frac{1}{2\pi \times f_{LCC3} R_{eq}} \quad (f_{LCC3} = f_L \leq 20Hz)$$

$$R_{eq} = 1.8k\Omega$$

$$C_{C3} = \frac{1}{2\pi \times 1.8 \times 10^3 \times 20}$$

$$C_{C3} = 4.42nF$$

Select $C_{C3} = 4.7\mu F$, 50V (H.S.V)

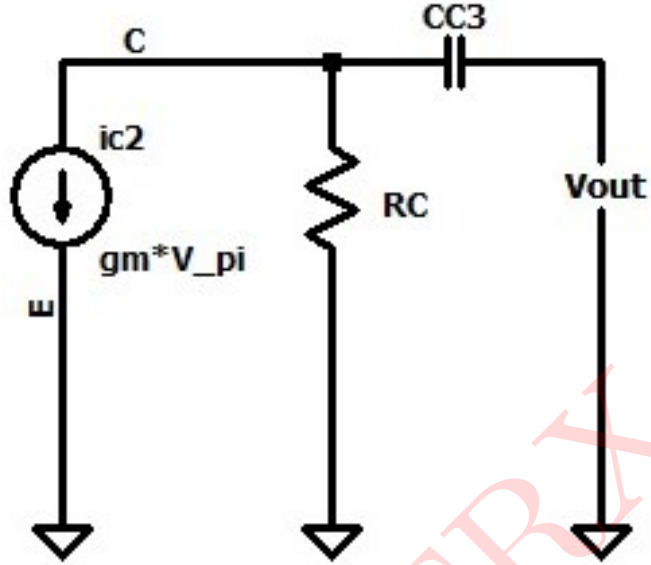


Figure 15: Small signal equivalent circuit for CC3

12) Selection of C_S , C_E :

a) Selection of C_S :

$$C_S = \frac{1}{2\pi \times f_{LCS} R_{eq}}$$

$$R_{eq} = \frac{1}{g_m} || R_S = \frac{1}{3.9603 \times 10^{-3}} || 180 = 105.0887$$

$$C_{S1} = C_{S2} = \frac{1}{2\pi \times 105.0877 \times 20} = 75.724 \mu F$$

$$C_S \geq 361.715 \mu F$$

Select $C_S = 82 \mu F$, 50V (H.S.V)

b) Selection of C_E :

$$X_{CE} = 0.1 R_E$$

$$C_E = \frac{1}{2\pi \times f_{LCS} 0.1 R_E}$$

$$C_{S1} = C_{S2} = \frac{1}{2\pi \times 0.1 \times 420 \times 20} = 189.47 \mu F$$

Select $C_S = 220 \mu F$, 50V (H.S.V)

13) Designed Circuit is:

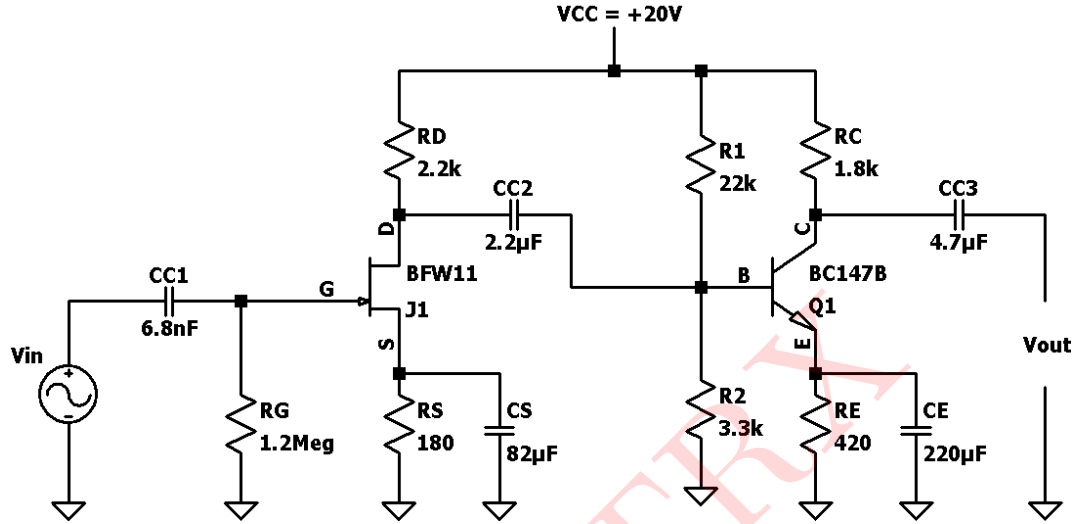


Figure 16: Designed circuit 1

Verification of overall gain:

$$Z_i = R_G = 1.2M\Omega$$

$$Z_o = R_C = 1.8k\Omega$$

$$A_{V_2} = -g_{m2}R_C = 3.96m(50k || 6.2k)$$

$$g_{m2} = I_{CQ}/V_T = 170.76mA$$

$$A_{V_2} = -307.368$$

$$A_{V_1} = g_m(r_d || R_D || R_1 || R_2 || r_\pi) = 3.96m(50k || 2.2k || 22k || 3.3k || 111.698k)$$

$$A_{V_1} = -2.799$$

$$A_{V_T} = A_{V_2} \times A_{V_1} = -307.368 \times -2.799$$

$$A_{V_T} = \mathbf{860.544} (\because A_V \geq 220)$$

$$A_{V_T} = 20\log_{10}(860.544)$$

$$A_{V_T} = \mathbf{58.6954 \text{ dB}}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

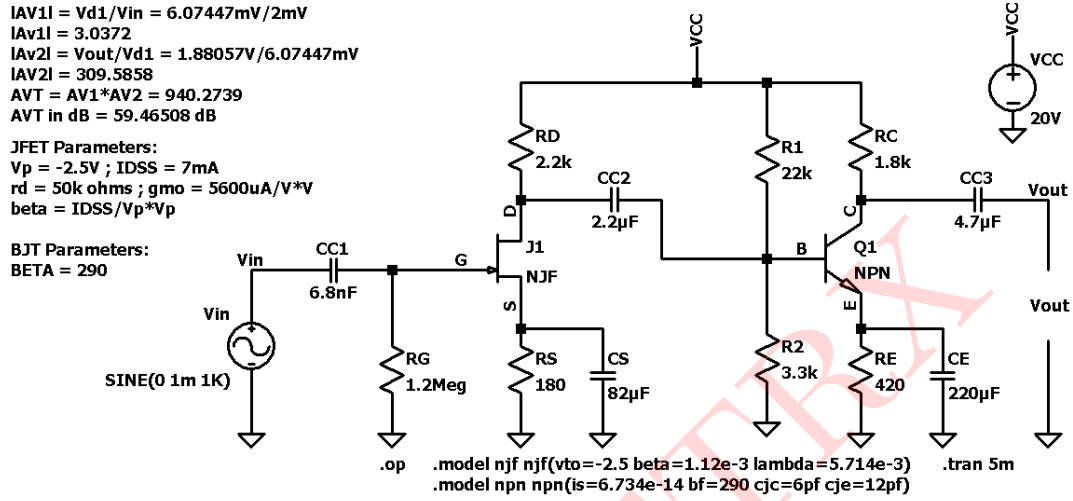


Figure 17: Circuit schematic 1

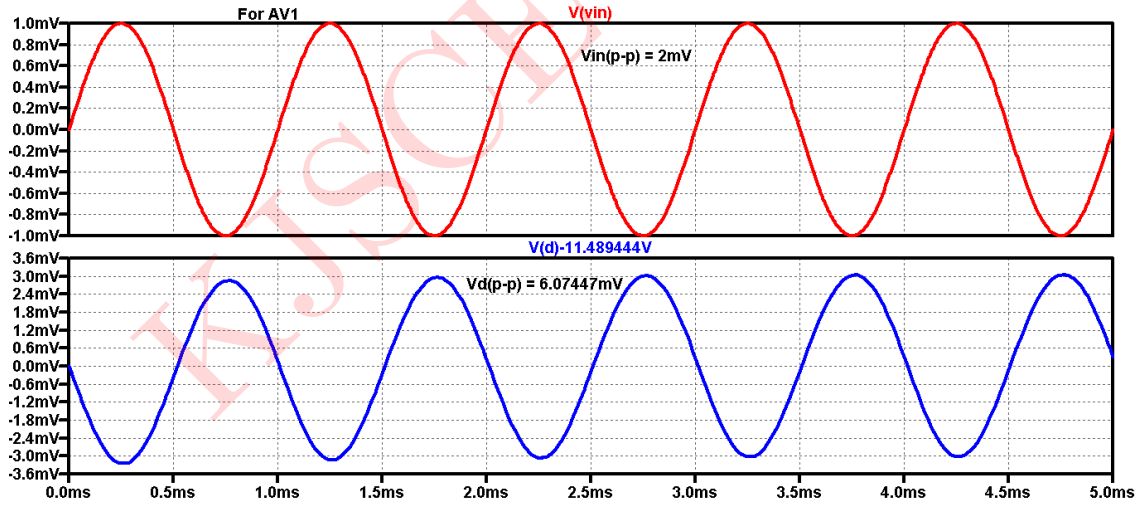


Figure 18: Circuit Schematic: Input Output Waveform A_{V1}

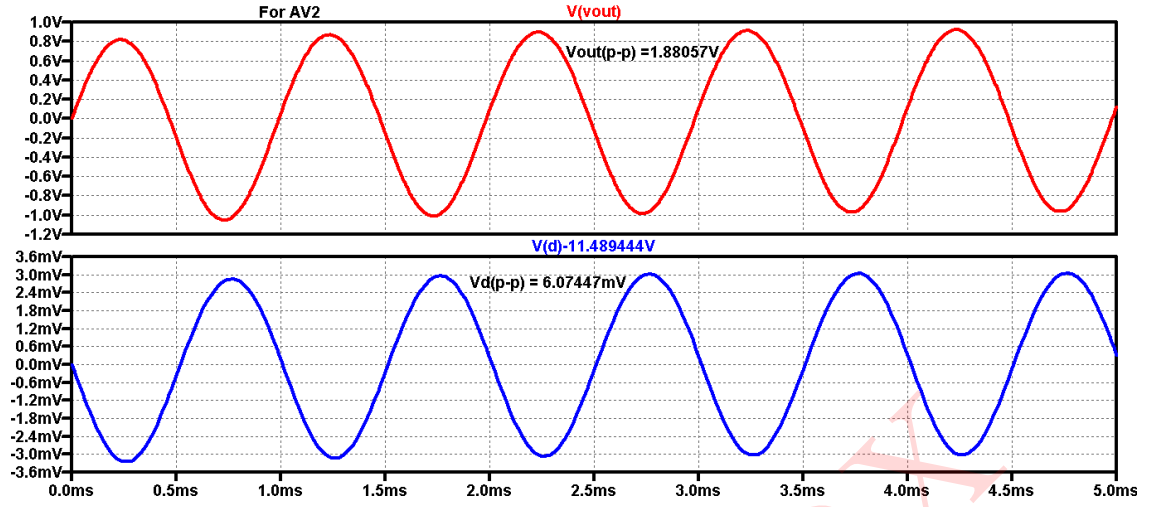


Figure 19: Circuit Schematic: Input Output Waveform A_{V_2}

Comparson between observed and theoretical values :

Parameters	Observed	Theoretical
I_{DQ}, V_{GSQ}	3.86mA, $-0.6963V$	3.5mA, $-0.732V$
I_B, V_C	15.598 μ A, 4.552mA	15.3103 μ A, 4.44mA
V_B, V_E	2.563V, 1.9186V	2.6V, 1.871V
A_{V_1}	-3.0372	-2.799
A_{V_2}	-309.5858	-307.368
A_{V_T} in dB	59.465	58.6954
Z_i	-	1.2M Ω
Z_o	-	1.8k Ω

Table 2: Numerical 2