

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**DC CIRCUITS**

**Numerical 1:** Compute the value of battery current  $I$  in the Figure 1:  
All resistances are in ohms.

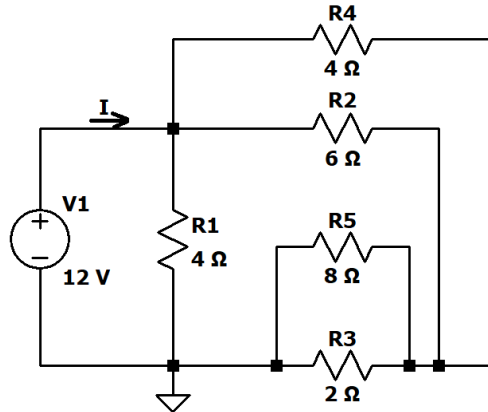


Figure 1: Circuit 1

**Solution:**

The given circuit can be reduced as:

The  $4\ \Omega$  resistor and the  $6\ \Omega$  resistor are connected in parallel.

The  $8\ \Omega$  resistor and the  $2\ \Omega$  resistor also are connected in parallel.

( $8\ \Omega \parallel 2\ \Omega = 2.4\ \Omega$  and  $6\ \Omega \parallel 4\ \Omega = 1.6\ \Omega$ )

The circuit will be reduced to:

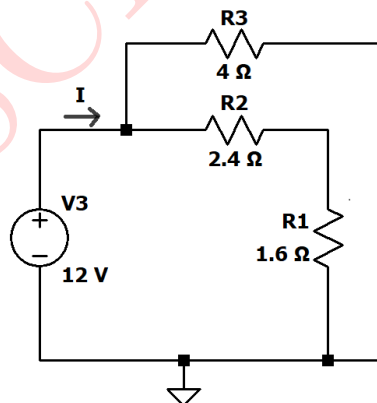


Figure 2: Modified Circuit for Figure 1

Now, the  $2.4\ \Omega$  and  $1.6\ \Omega$  resistors are in series.

$$(2.4 + 1.6)\ \Omega = 4\ \Omega$$

So, the circuit is reduced to:

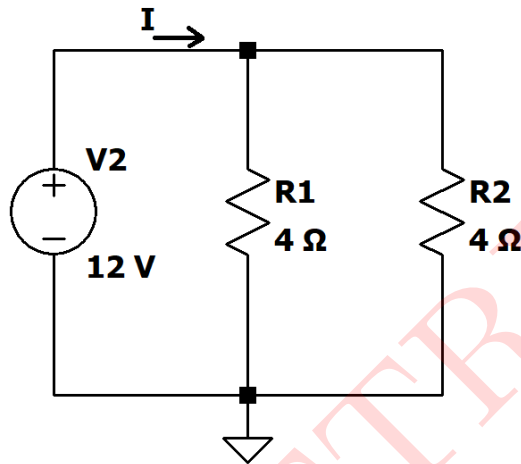


Figure 3: Modified Circuit for Figure 2

The two  $4\ \Omega$  resistors form a parallel combination.

$$(4 \parallel 4)\ \Omega = 2\ \Omega$$

The circuit is further reduced to:

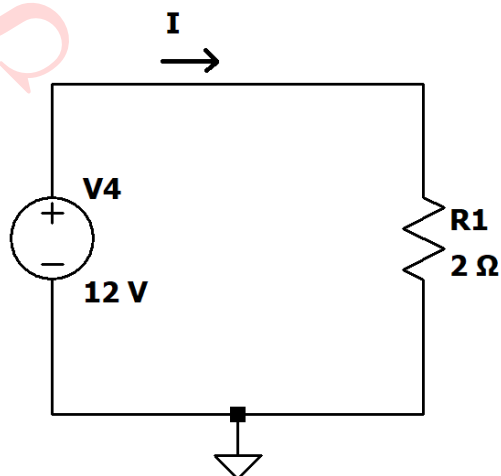


Figure 4: Modified Circuit for Figure 3

Applying Ohm's Law to the circuit,

$$I = \frac{V}{R} = \frac{12}{2} = 6A$$

The value of the battery current in the circuit is 6A

### SIMULATED RESULTS:

Given circuit is simulated in LTspice. The results are presented below:

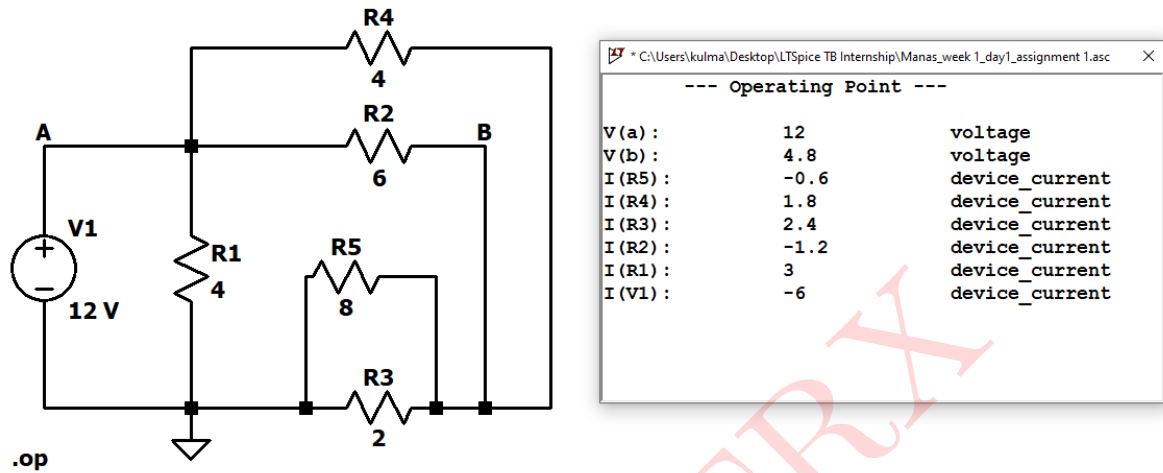


Figure 5: Circuit Schematic and Simulated Results

Comparison of calculated and simulated values:

Parameters	Theoretical Values	Simulated Values
Current ( $I$ )	6A	6A

Table 1: Numerical 1

**Numerical 2:** In the circuit of Figure 6, find the value of supply voltage  $V_1$  so that  $20\ \Omega$  resistor can dissipate  $180\text{ W}$ .

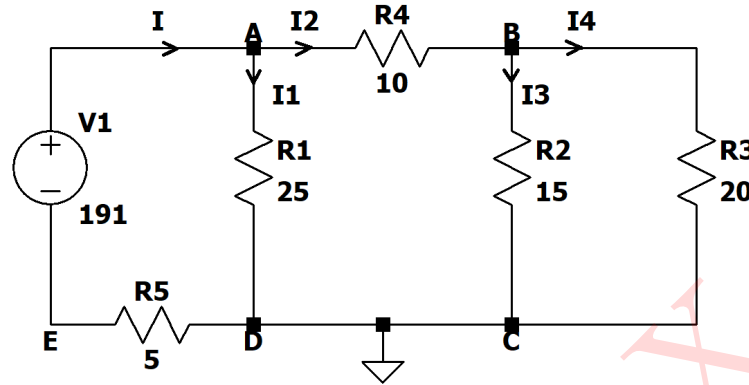


Figure 6: Circuit 2

**Solution:**

$$I_4^2 \times 20 = 180W$$

$$I_4 = 3\text{ A}$$

Since  $15\ \Omega$  and  $20\ \Omega$  are in parallel,

$$I_3 \times 15 = 3 \times 20$$

$$\therefore I_3 = 4\text{ A}$$

$$I_2 = I_3 + I_4 = 4 + 3 = 7\text{ A}$$

Now, resistance of the circuit to the right of point A is

$$= 10 + \frac{15 \times 20}{35} = \frac{130}{7}\ \Omega$$

$$\therefore I_1 \times 25 = 7 \times \frac{130}{7}$$

$$\therefore I_1 = \frac{26}{5}\text{ A} = 5.2\text{ A}$$

$$\therefore I = I_1 + I_2 = 5.2 + 7 = 12.2\text{ A}$$

$$\text{Total circuit resistance } (R_{AE}) = (5 + 25) \parallel \frac{130}{7} = \frac{955}{61}\ \Omega$$

$$V = I \times R_{AE} = 12.2 \times \frac{955}{61} = 191\text{ V}$$

**The value of the supply voltage is 191V**

### SIMULATED RESULTS:

The given circuit is simulated in LT Spice. The results are presented below:

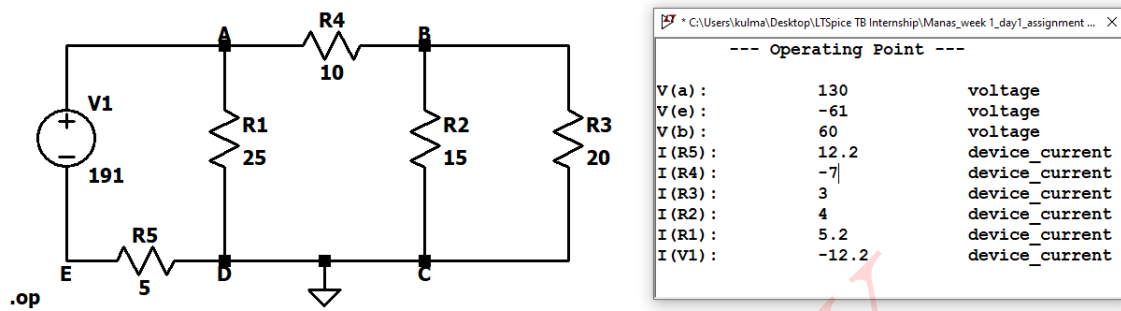


Figure 7: Circuit Schematic and Simulated Results

### Comparison of calculated and simulated values:

Parameters	Calculated Values	Simulated Values
$I$	12.2A	12.2A
$I_1$	5.2A	5.2A
$I_2$	7A	7A
$I_3$	4A	4A
$I_4$	3A	3A
Supply Voltage (V)	191V	191V

Table 2: Numerical 2

**Numerical 3:** Find  $V_0$  and the power absorbed by each element in Circuit 3.

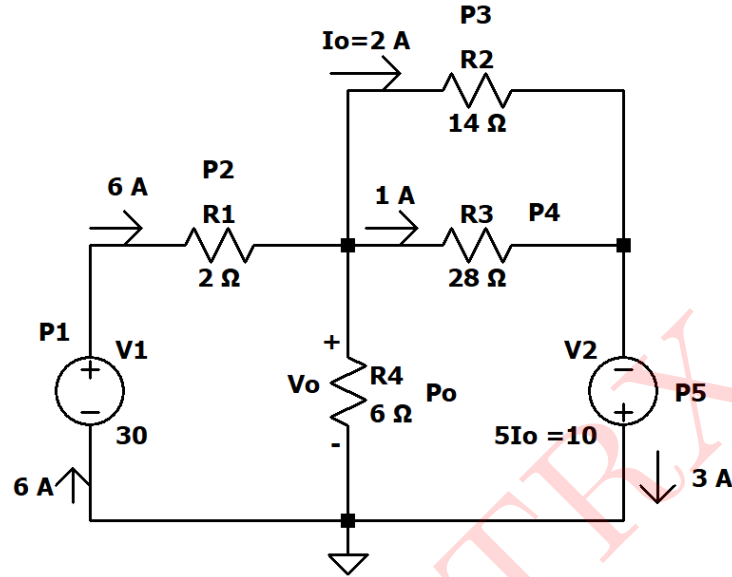


Figure 8: Circuit 3

**Solution:**

We consider all the elements to be resistors.

Let the power absorbed/dissipated by the elements be  $P_1$ ,  $P_2$ ,  $P_3$ ,  $P_4$ ,  $P_5$ ,  $P_0$  respectively.

Power across any element is given by the formula  $P = V \times I$

$$\begin{aligned}\therefore P_1 &= 30 \times -6 = -180W \\ \therefore P_2 &= 12 \times 6 = 72W \\ \therefore P_3 &= 28 \times 2 = 56W \\ \therefore P_4 &= 28 \times 1 = 28W \\ \therefore P_5 &= (5 \times 2) \times -3 = -30W\end{aligned}$$

We know that, the total of the values of power absorbed/dissipated by all the elements must be equal to zero. i.e  $P_{Total} = 0$

$$\text{But, } P_{Total} = P_1 + P_2 + P_3 + P_4 + P_5 + P_0$$

$$\begin{aligned}\therefore P_0 &= -180 + 72 + 56 + 28 - 30 \\ \therefore P_0 &= 54W\end{aligned}$$

We know that,  $P = V \times I$

$$\therefore P_0 = V_0 \times 3$$

$$\therefore V_0 = 18V$$

### SIMULATED RESULTS:

Given circuit is simulated in LTspice. The results are presented below:

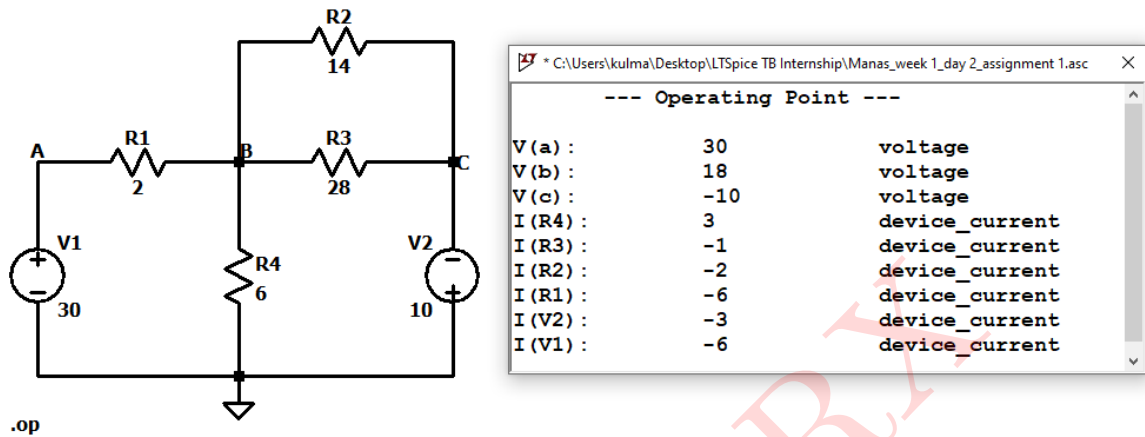


Figure 9: Circuit Schematic and Simulated Results

Comparison of given and simulated values:

Parameters	Calculated Value	Simulated Value
$P_1$	$-180W$	$-180W$
$P_2$	$72W$	$72W$
$P_3$	$56W$	$56W$
$P_4$	$28W$	$28W$
$P_5$	$-30W$	$-30W$
$P_0$	$54W$	$54W$
$V_0$	$18V$	$18V$

Table 3: Numerical 3

**Numerical 4:** For the Circuit 4, find the branch currents and using mesh analysis.

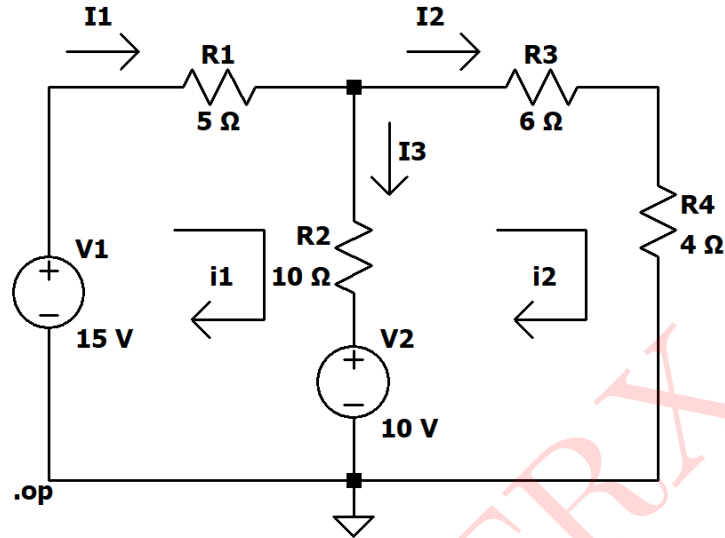


Figure 10: Circuit 4

**Solution:**

We first obtain the mesh currents using K.V.L

Applying K.V.L to mesh 1,

$$-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$

$$\therefore 3i_1 + 2i_2 = 1 \text{ ..... (1)}$$

Applying K.V.L to mesh 2,

$$6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$$

$$\therefore i_1 = 2i_2 - 1 \text{ ..... (2)}$$

Substituting the value of  $i_1$  from equation (2) to equation (1), we get

$$6i_2 - 3 - 2i_2 = 1$$

$$\therefore i_2 = 1 \text{ A}$$

$$\therefore i_1 = 2i_2 - 1 = 2 - 1 = 1 \text{ A}$$

$$\therefore i_1 = 1 \text{ A}$$

$$I_1 = i_1 = 1\text{A}, I_2 = i_2 = 1\text{A}, I_3 = i_1 - i_2 = 0\text{A}$$

The three branch currents  $I_1, I_2$  and  $I_3$  are 1A, 1A and 0A respectively.



### SIMULATED RESULTS:

The given circuit is simulated in LT Spice. The results are presented below:

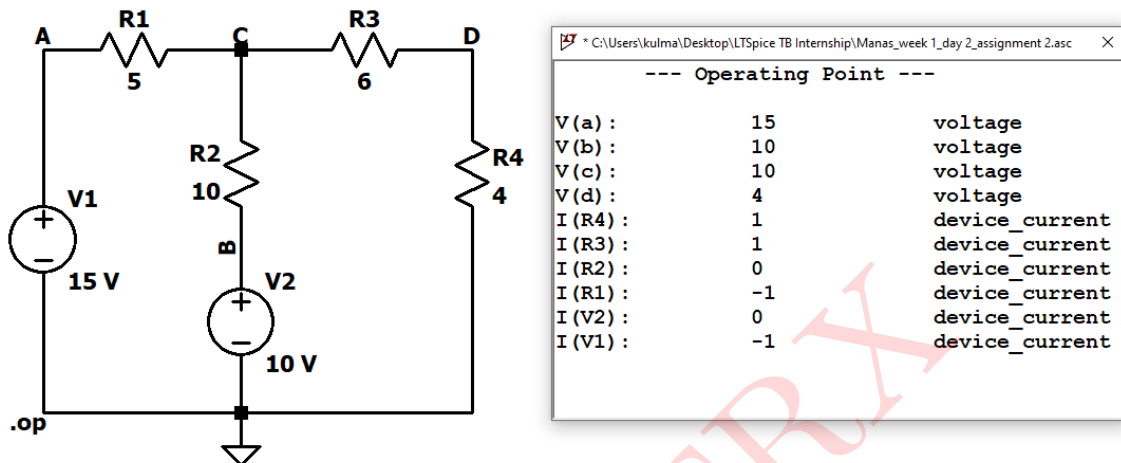


Figure 11: Circuit Schematic and Simulated Results

### Comparison of calculated and simulated values:

Parameters	Calculated Values	Simulated Values
$I_1$	1A	1A
$I_2$	1A	1A
$I_3$	0A	0A

Table 4: Numerical 4

**Numerical 5:** Apply Superposition theorem to the circuit of Figure 12 for finding the voltage drop  $V$  across the  $5\Omega$  resistor.

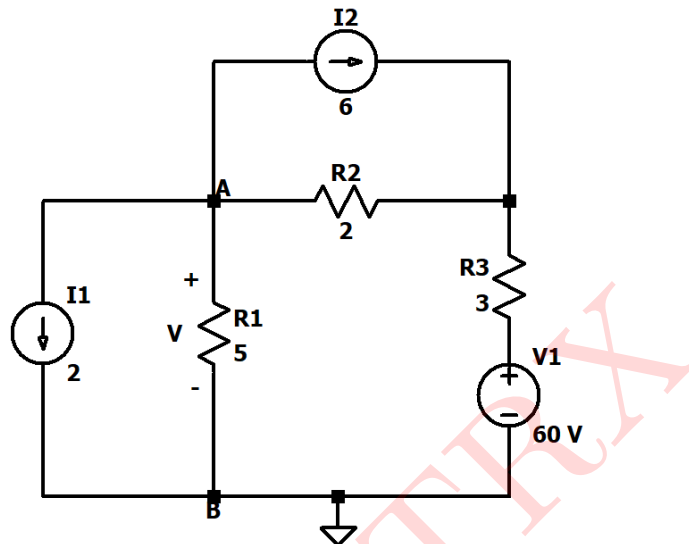


Figure 12: Circuit 5

**Solution:**

CASE I:

Figure 13 shows the redrawn circuit with the voltage source acting alone while the two current sources have been replaced by open circuits.

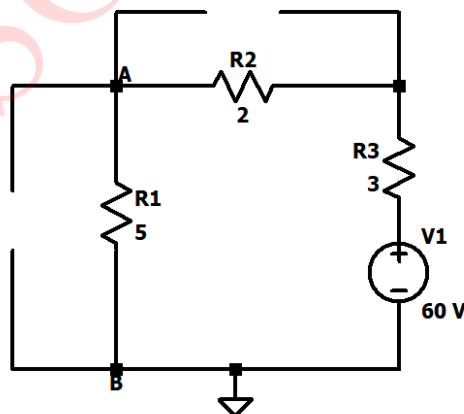


Figure 13: Modified Circuit when 60V source is active

Using voltage-divider principle, we get

$$V_1 = 60 \times \frac{5}{(5 + 2 + 3)} = 30V$$

It would be taken as positive, because current through the  $5\Omega$  resistances flows from A to B, thereby making the upper end of the resistor positive and the lower end negative.

$$\therefore V_1 = 30V$$

CASE II:

Figure 14 shows the same circuit with the 6A source acting alone while the two other sources have been replaced by open or short circuit respectively. It will be seen that 6A source has to parallel circuits across it, one having a resistance of  $2\Omega$  and the other  $(3 + 5) = 8\Omega$ .

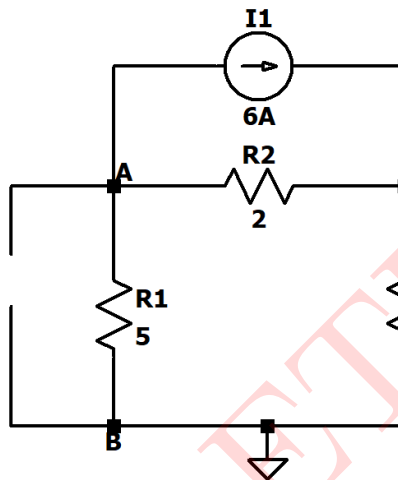


Figure 14: Modified Circuit when 6A source is active

Using the current-divider rule,

$$\text{The current through the } 5\Omega \text{ resistor} = 6 \times \frac{2}{(2 + 3 + 5)} = 1.2A$$

$$\therefore V_2 = 1.2 \times 5 = 6V$$

It would be taken negative because current is flowing from B to A. i.e. point B is at a higher potential as compared to point A.

$$\therefore V_2 = -6V$$

CASE III:

Figure 15 shows the case when 2A source acts alone, while the other two sources are dead. As seen, this current divides equally at point B, because the two parallel paths have equal resistances of  $5\Omega$  each.

So, the circuit is reduced to:

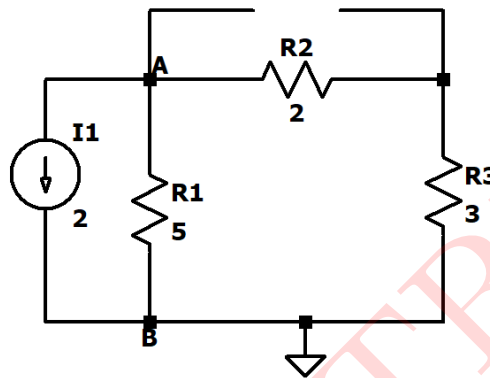


Figure 15: Modified Circuit when 2A source is active

Hence,  $V_3 = 5 \times 1 = 5V$

It would be taken as negative because current flows from B to A.

Hence,  $V_3 = -5V$

Using Superposition principle, we get

$$V = V_1 + V_2 + V_3 = 30 - 6 - 5 = 19V$$

$$\therefore \mathbf{V = 19V}$$

### SIMULATED RESULTS:

Given circuit is simulated in LTSpice. The results are presented below:

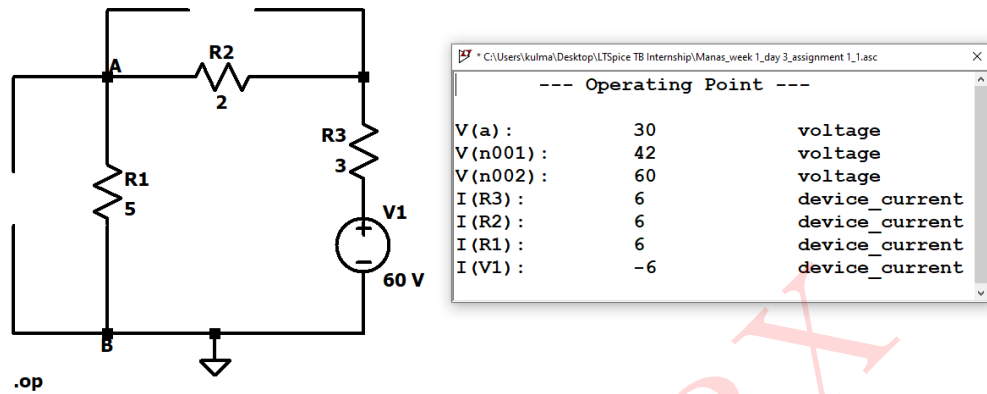


Figure 16: Circuit Schematic and Simulated Results when 60V source is active

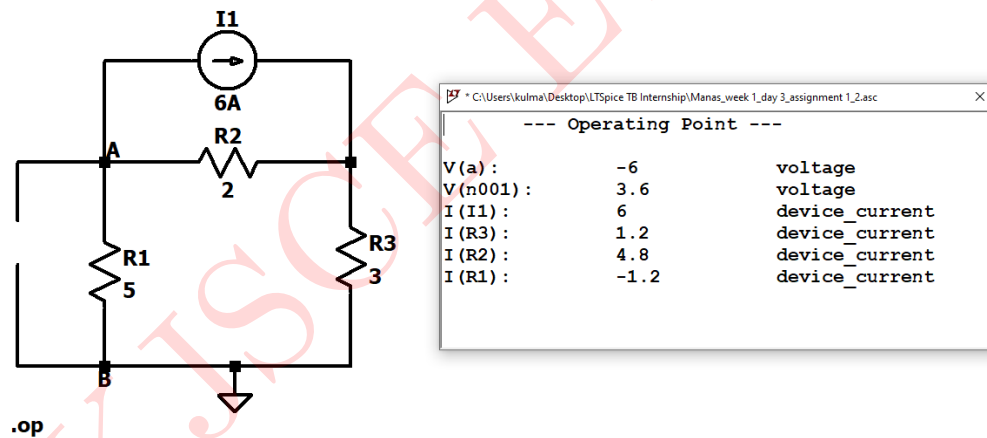


Figure 17: Circuit Schematic and Simulated Results when 6A source is active

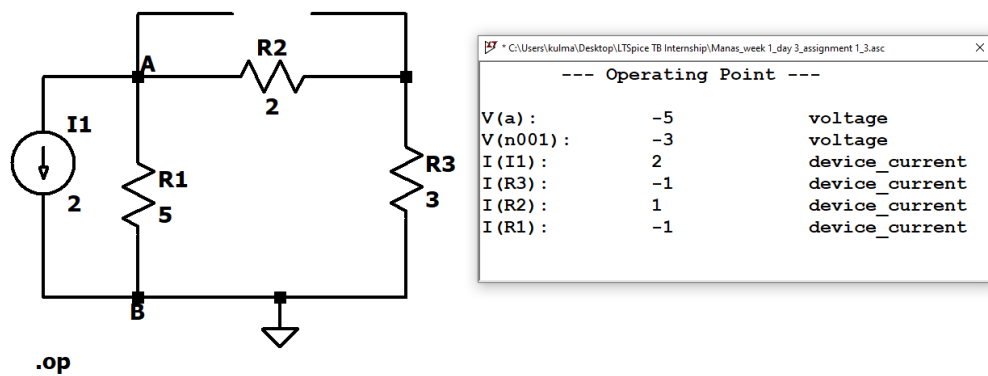


Figure 18: Circuit Schematic and Simulated Results when 2A source is active

Comparison of calculated and simulated values:

Parameters	Calculated Values	Simulated Values
$V_1$	30V	30V
$V_2$	-6V	-6V
$V_3$	-5V	-5V

Table 5: Numerical 5

**Numerical 6 :** Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the Circuit 6. Then find current  $I$  flowing through the resistor  $R_4$ .

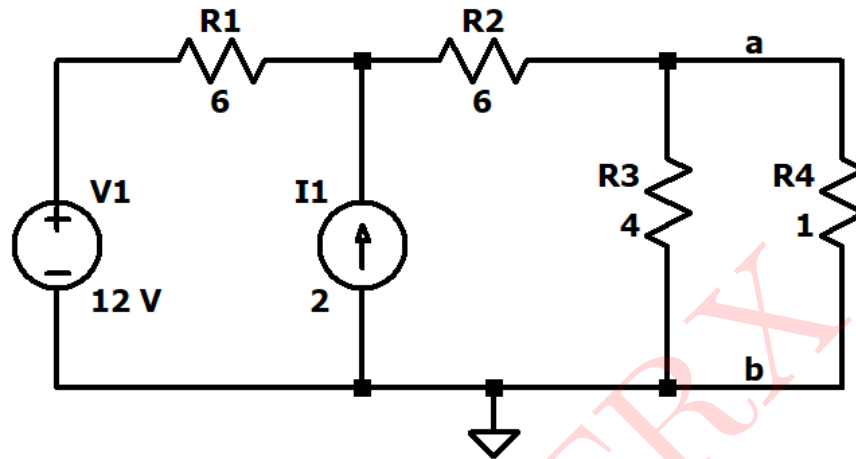


Figure 19: Circuit 6

**Solution:**

STEP I: Calculation of  $V_{TH}$

To find  $V_{TH}$ , we replace the  $1\Omega$  resistor with open circuit.

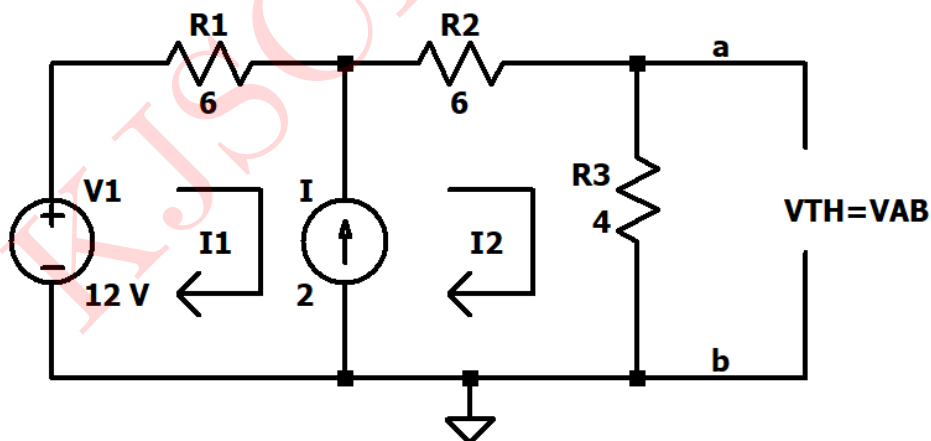


Figure 20: Modified circuit to find  $V_{TH}$

Let  $I_1$  and  $I_2$  be the currents through mesh 1 and mesh 2 respectively.

The two meshes 1 and 2 form a super-mesh.

$$\therefore I_2 - I_1 = 2 \quad \dots (1)$$

Applying KVL to the entire loop,

$$+12 - 6I_1 - 6I_2 - 4I_2 = 0$$

$$6I_1 + 10I_2 = 0 \quad \dots (2)$$

Solving equations (1) and (2) simultaneously, we get

$$\therefore I_1 = -0.5A = 0.5A(\downarrow)$$

$$\text{Now, } V_{TH} = I_2 \times 4$$

$$\therefore V_{TH} = 1.5 \times 4$$

$$\therefore V_{TH} = 6V$$

STEP II: Calculation of  $R_{TH}$

To find  $R_{TH}$ , we replace the voltage source with short circuit and the current source with open circuit.

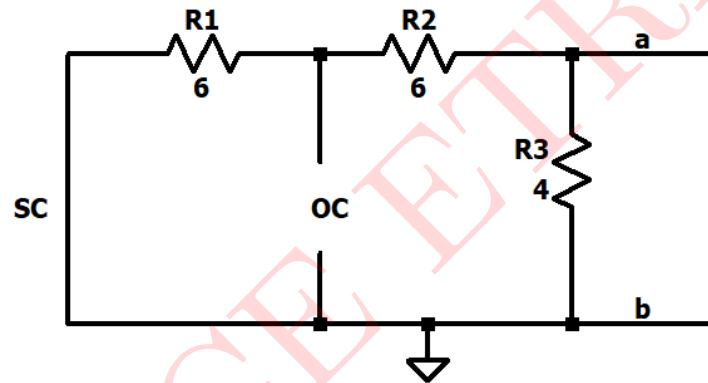


Figure 21: Modified circuit to find  $R_{TH}$

$$\therefore R_{TH} = (6 + 6) || 4$$

$$\therefore R_{TH} = \frac{12 \times 4}{12 + 4}$$

$$\therefore R_{TH} = 3\Omega$$



Thevenin's Equivalent Circuit:

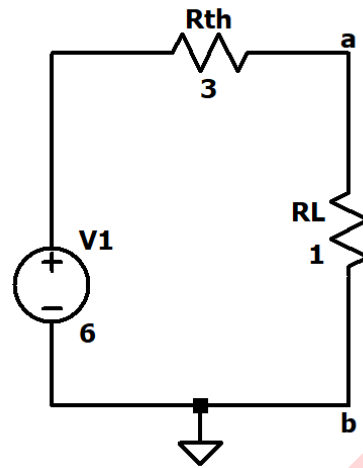


Figure 22: Thevenin's Equivalent Circuit

$$I = \frac{V_{TH}}{R_{TH} + R_L} = \frac{6}{3 + 1} = 1.5A$$

$$\therefore I = 1.5A$$

**The value of current I is 1.5A**

### SIMULATED RESULTS:

The given circuit is simulated in LT Spice. The results are presented below:

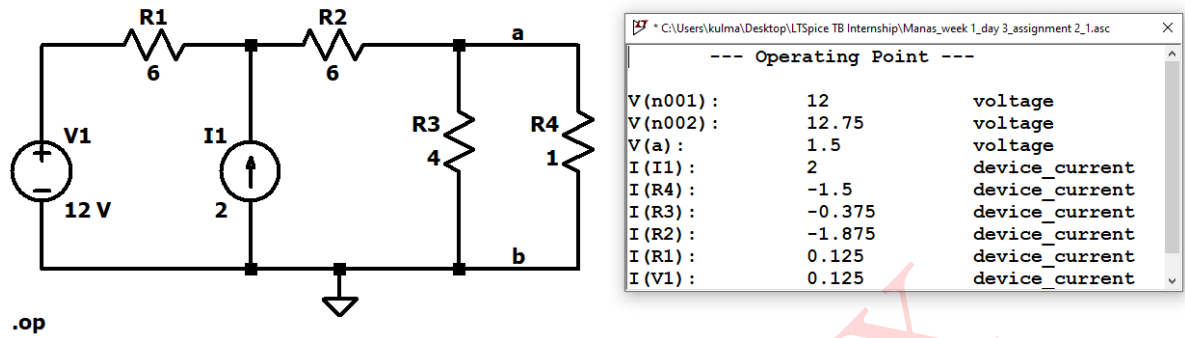


Figure 23: Circuit Schematic and Simulated Results for directly finding current I

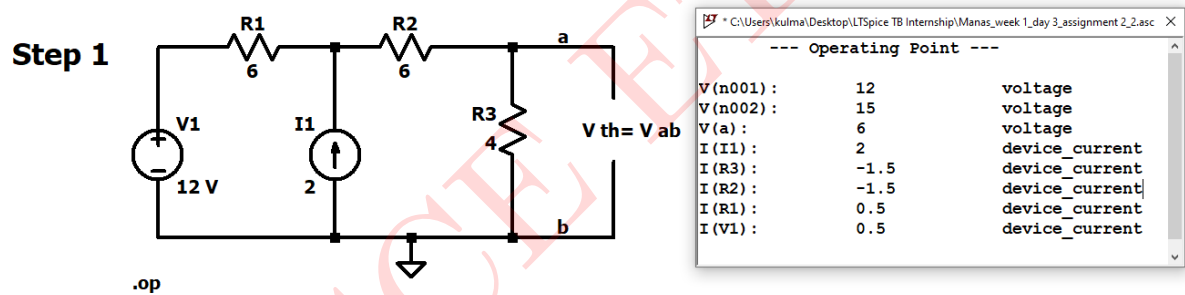


Figure 24: Circuit Schematic and Simulated Results for finding  $V_{TH}$

### Step 2

$$R_{th} = R_{eq} = (6+6) \parallel 4 = 3\Omega$$

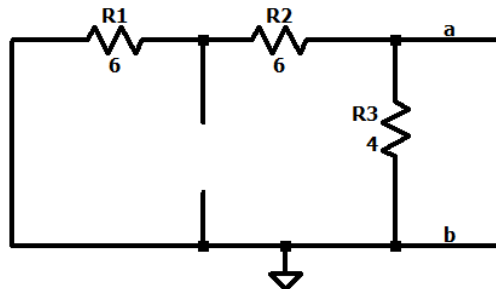


Figure 25: Circuit Schematic finding  $R_{TH}$

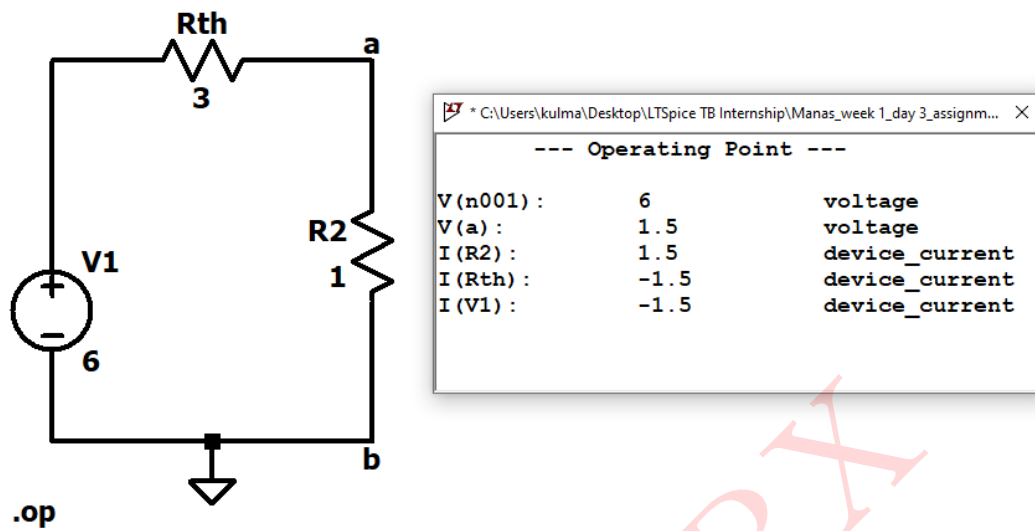


Figure 26: Circuit Schematic and Simulated Results for Thevenin's Equivalent circuit

Comparison of calculated and simulated values:

Parameters	Calculated Value	Simulated Value
$V_{TH}$	6V	6V
$R_{TH}$	3Ω	3Ω
$I$	1.5A	1.5A

Table 6: Numerical 6

**Numerical 7:** Using Norton's theorem, find the current which would flow in a  $25\Omega$  resistor connected between points N and O in Circuit 7. All resistance values are in ohms.

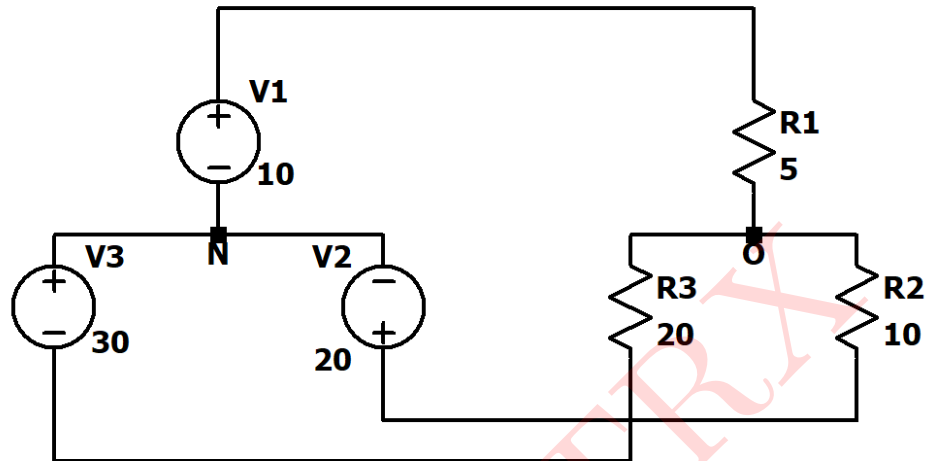


Figure 27: Circuit 7

**Solution:**

For case of understanding, the given circuit may be redrawn as shown in Figure 28.

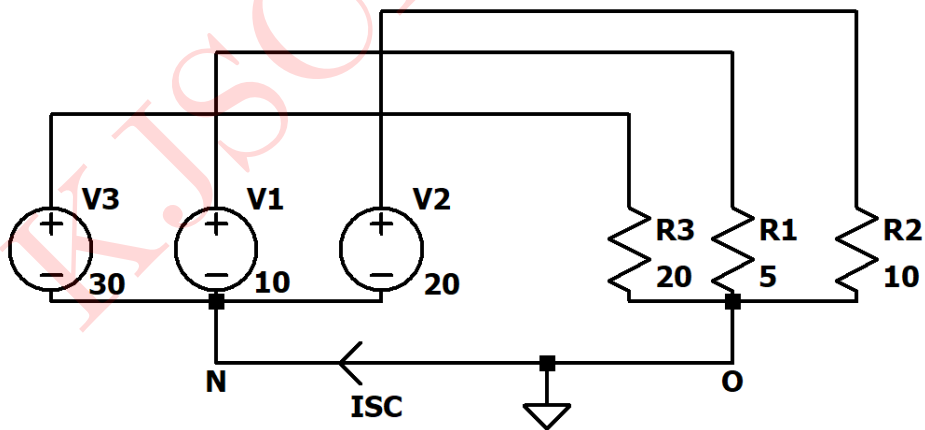


Figure 28: Modified Circuit for Figure 1

Total current in short-circuit across ON is equal to the sum of currents driven by different batteries through their respective resistances.

$$I_{SC} = \frac{10}{5} + \frac{20}{10} + \frac{30}{20} = 5.5A$$

The resistance  $R_L$  of the circuit when looked into from point N and O is

$$\frac{1}{R_L} = \frac{1}{5} + \frac{1}{10} + \frac{1}{20} = \frac{7}{20}\Omega$$

$$\therefore R_L = \frac{20}{7} = 2.86\Omega$$

Hence, given circuit reduces to that shown in Figure 3.

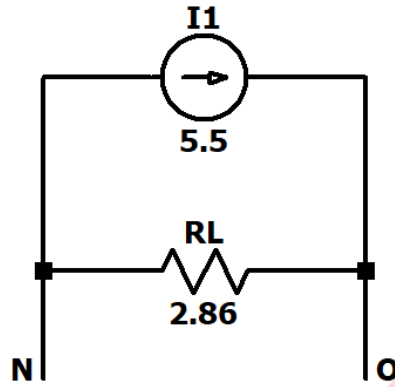


Figure 29: Modified Circuit for Figure 2

Open-circuit voltage across NO is  $= I_{SC} \times R_L = 5.5 \times 2.86 = 15.73V$

Now, we connect the  $25\Omega$  resistor across N and O.

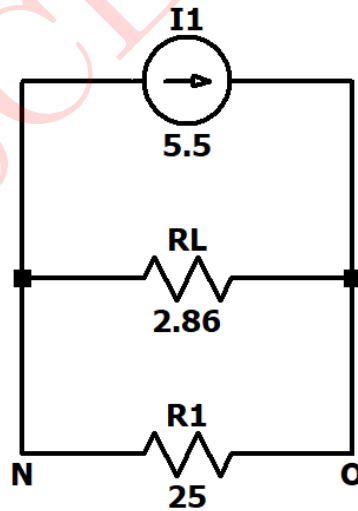


Figure 30: Modified Circuit after connecting  $25\Omega$  resistor

Hence, current through  $25\Omega$  resistor connected across NO is

$$I = 5.5 \times \frac{2.86}{2.86 + 25} = 0.565A$$

The current flowing through the  $25\Omega$  resistor is **0.565A**

## SIMULATED RESULTS:

Given circuit is simulated in LTSpice. The results are presented below:

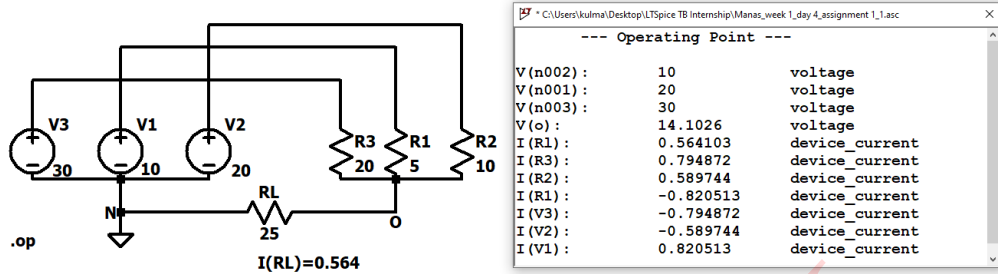


Figure 31: Circuit Schematic and Simulated Results to directly find  $I_{RL}$

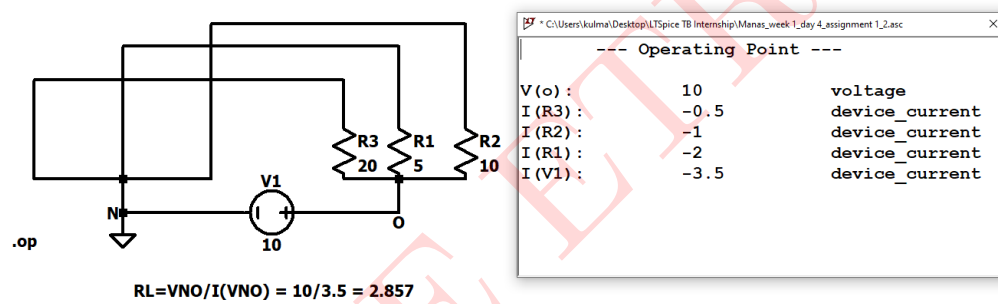


Figure 32: Circuit Schematic and Simulated Result to find  $R_L$

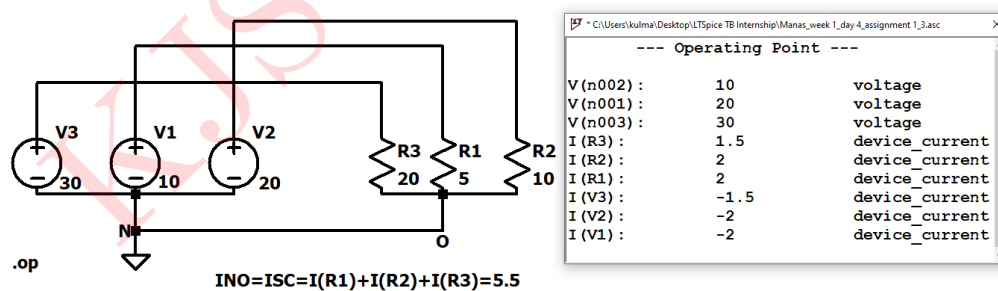


Figure 33: Circuit Schematic and Simulated Results to find  $I_{NO}$

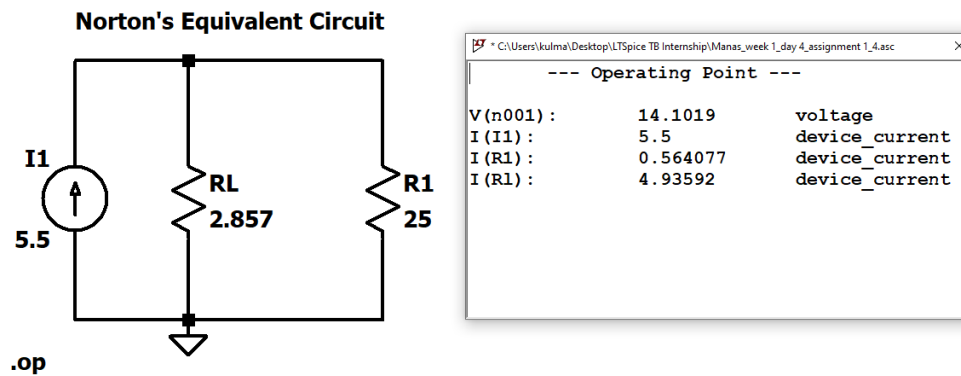


Figure 34: Circuit Schematic and Simulated Results for Norton's Equivalent Circuit

Comparison of calculated and simulated values:

Parameters	Calculated Values	Simulated Values
$I_{SC}$	$5.5A$	$5.5A$
$R_L$	$2.86\Omega$	$2.857\Omega$
$I$	$0.565A$	$0.56077A$

Table 7: Numerical 7

**Numerical 8 :** In the network shown in Circuit 8, determine the maximum power delivered to  $R_L$

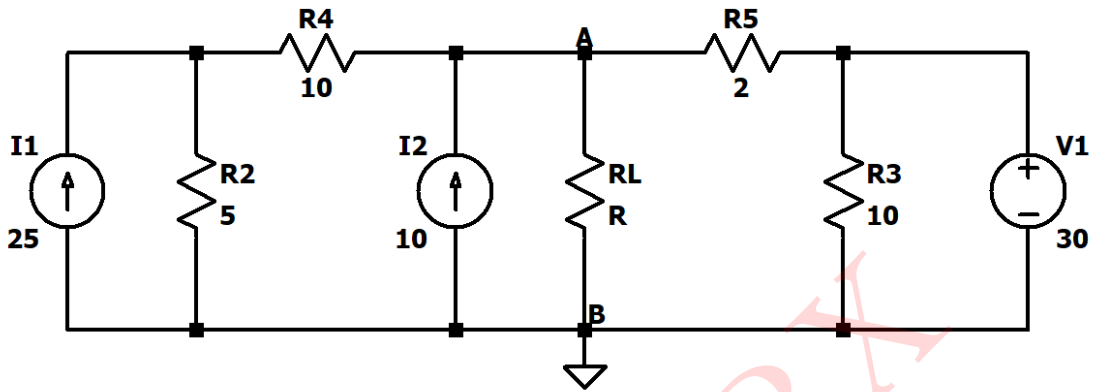


Figure 35: Circuit 8

**Solution:**

STEP I: Calculation of  $V_{TH}$

To find  $V_{TH}$ , we replace  $R_L$  with open circuit.

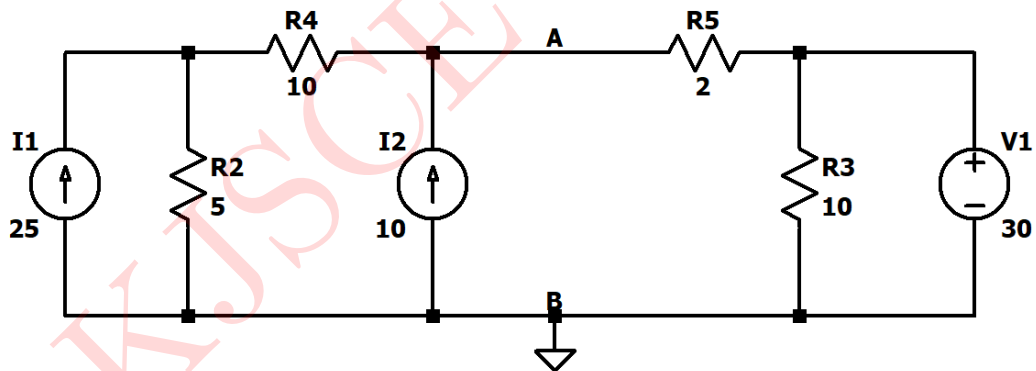


Figure 36: Modified circuit to find  $V_{TH}$



Using source transformation, we convert the 25A source to a voltage source.  
The circuit is reduced to:

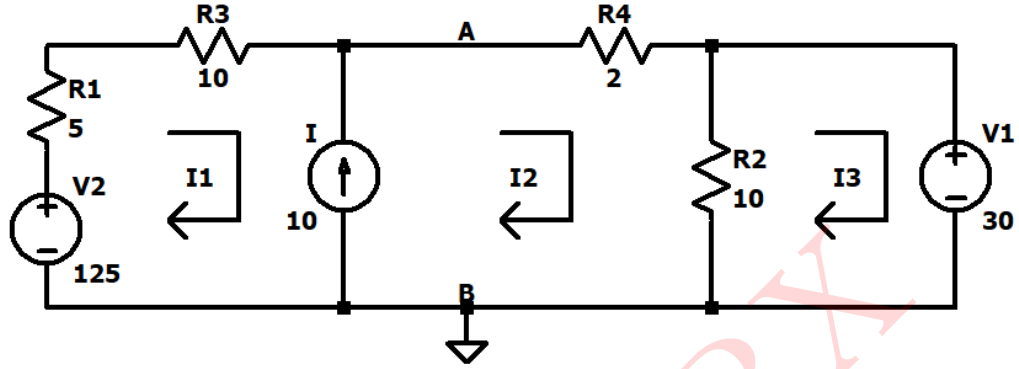


Figure 37: Simplified circuit of Figure 36

Let  $I_1$ ,  $I_2$  and  $I_3$  be the currents through mesh 1, mesh 2 and mesh 3 respectively.  
Mesh 1 and mesh 2 form a super-mesh.

Expressing the current in the common branch, we get the current equation as:

$$\therefore I_2 - I_1 = 10 \quad \dots (1)$$

Applying KVL in the super mesh,

$$\begin{aligned} -10I_1 - 2I_2 - 10(I_2 - I_3) + 125 - 5I_1 &= 0 \\ \therefore 15I_1 + 12I_2 - 10I_3 &= 125 \quad \dots (2) \end{aligned}$$

Applying K.V.L to mesh 3,

$$\begin{aligned} -10(I_3 - I_2) - 30 &= 0 \\ \therefore 10I_2 - 10I_3 &= 30 \quad \dots (3) \end{aligned}$$

Solving equations (1), (2) and (3) simultaneously,

$$\therefore I_2 = 14.41A$$

Hence,  $I_{2\Omega} = 14.41A (\rightarrow)$

Further, we get  $V_{TH} = V_{AB}$

$$\therefore V_{TH} = 30 + (2 \times 14.41)$$

$$\therefore V_{TH} = 58.82V$$

STEP II: Calculation of  $R_{TH}$

To find  $R_{TH}$ , we replace the voltage sources with short circuit and the current source with open circuit.

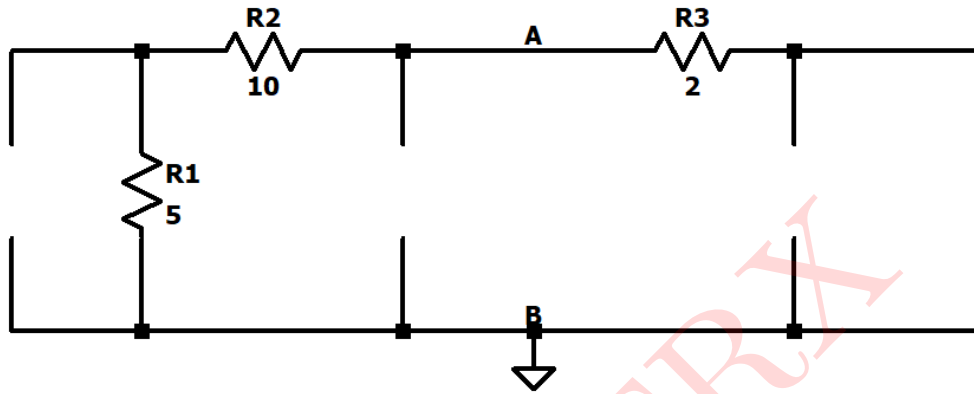


Figure 38: Modified circuit to find  $R_{TH}$

Since the  $10\Omega$  and  $5\Omega$  resistor are in series,  
 $(10 + 5) = 15\Omega$

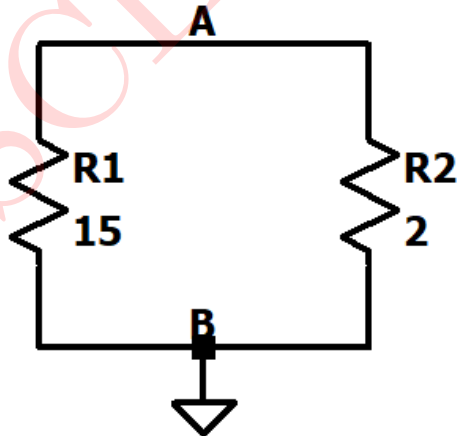


Figure 39: Simplified circuit of Figure 38

$$\therefore R_{TH} = (15 || 2)\Omega$$

$$\therefore R_{TH} = \frac{15 \times 2}{15 + 2}$$

$$\therefore R_{TH} = 1.76\Omega$$

THEVENIN'S EQUIVALENT CIRCUIT:

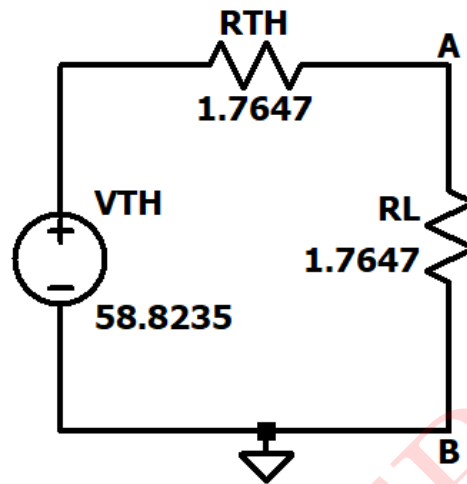


Figure 40: Thevenin's Equivalent Circuit

$P_{max}$  can be calculated as:

$$P_{max} = \frac{V_{TH}^2}{4 \times R_{TH}}$$

$$\therefore P_{max} = \frac{58.82^2}{4 \times 1.76}$$


$$\therefore P_{max} = 491.45W$$

The maximum power transferred in the circuit through  $R_L$  is 491.45W

## SIMULATED RESULTS:

The given circuit is simulated in LT Spice. The results are presented below:


### STEP 1: Finding $V_{TH}$

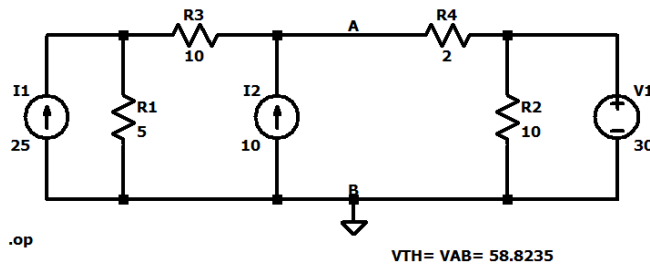

--- Operating Point ---		
V(n001):	102.941	voltage
V(a):	58.8235	voltage
V(n002):	30	voltage
I(I2):	10	device_current
I(I1):	25	device_current
I(R4):	-14.4118	device_current
I(R3):	-4.41176	device_current
I(R2):	3	device_current
I(R1):	20.5882	device_current
I(V1):	11.4118	device_current

Figure 41: Circuit Schematic and Simulated Results to find  $V_{TH}$

### STEP 2: Finding $R_{TH}$

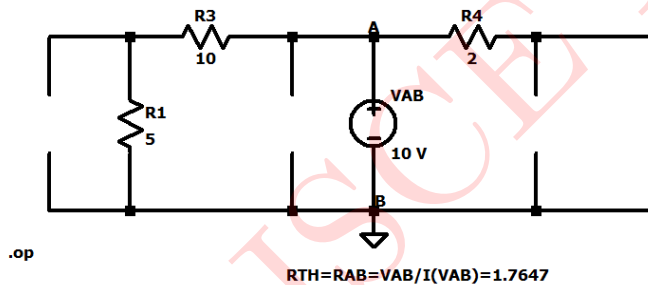


--- Operating Point ---		
V(n001):	3.33333	voltage
V(a):	10	voltage
I(R4):	-5	device_current
I(R3):	0.666667	device_current
I(R1):	0.666667	device_current
I(Vab):	-5.66667	device_current

Figure 42: Circuit Schematic and Simulated Results to find  $R_{TH}$
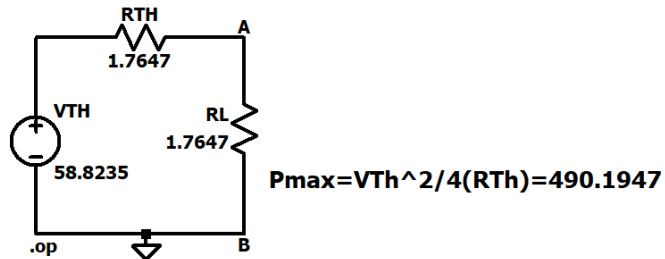
## Thevenin's Equivalent Circuit

Maximum Power is transferred when  $R_{TH}=R_L=1.7647$



```

--- Operating Point ---

V(n001) :      58.8235      voltage
V(a) :        29.4118      voltage
I(Rl) :       -16.6667      device_current
I(Rth) :       -16.6667      device_current
I(Vth) :       -16.6667      device_current
  
```

Figure 43: Circuit Schematic and Simulated Results for Thevenin's Equivalent Circuit

Comparison of calculated and simulated values:

Parameters	Calculated Value	Simulated Value
$V_{TH}$	58.82V	58.8235V
$R_{TH}$	1.76Ω	1.7647Ω
$P_{max}$	491.45W	490.1947W

Table 8: Numerical 8

**Numerical 9:** For the network given in circuit 9, determine the value of  $R_L$  for maximum power at the load. Also determine the maximum power.

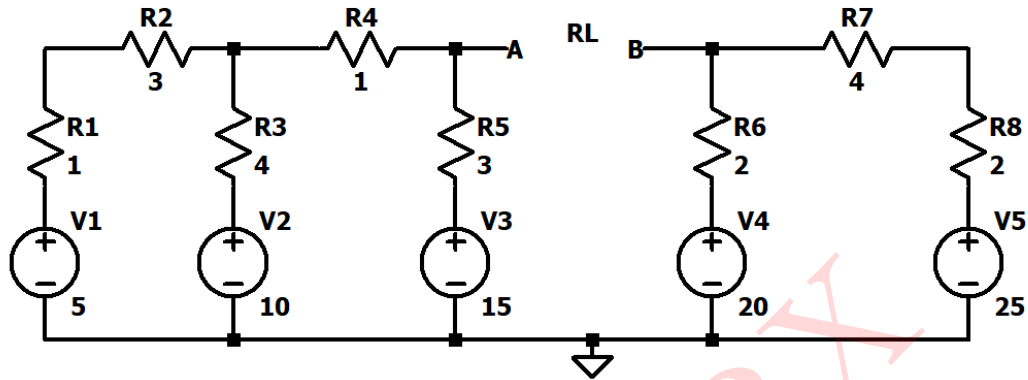


Figure 44: Circuit 9

**Solution:**

STEP I: Calculation of  $V_{TH}$

In the circuit, with terminals A and B kept open, from the right hand side,  $V_B$  (w.r.t reference node 0) can be calculated.  $V_4$  and  $V_5$  will have a net voltage of 10V circulating a current of  $\left(\frac{5}{8}\right) = 0.625A$  in clockwise direction.

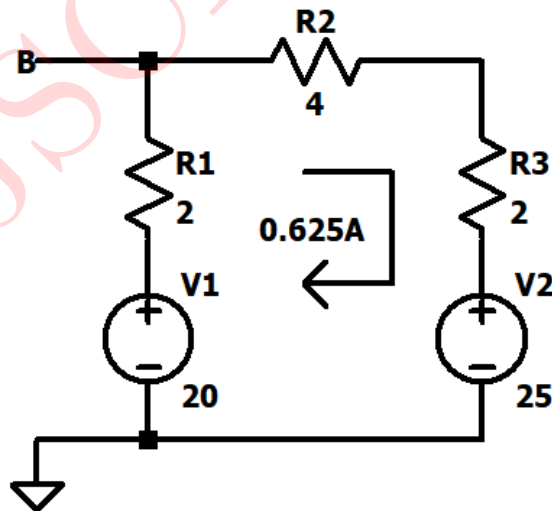


Figure 45: Modified circuit to find  $V_{TH}$

$$\therefore V_B = 20 + (0.625 \times 2) = 21.25V$$

On the Left-hand part of the circuit, there are two loops.  $V_A$  (w.r.t 0) has to be evaluated. Let the first loop (with  $V_1$  and  $V_2$  as the sources) carry a clockwise current of  $i_1$  and the second loop (with  $V_2$  and  $V_3$  as the sources), a clockwise current of  $i_2$ .

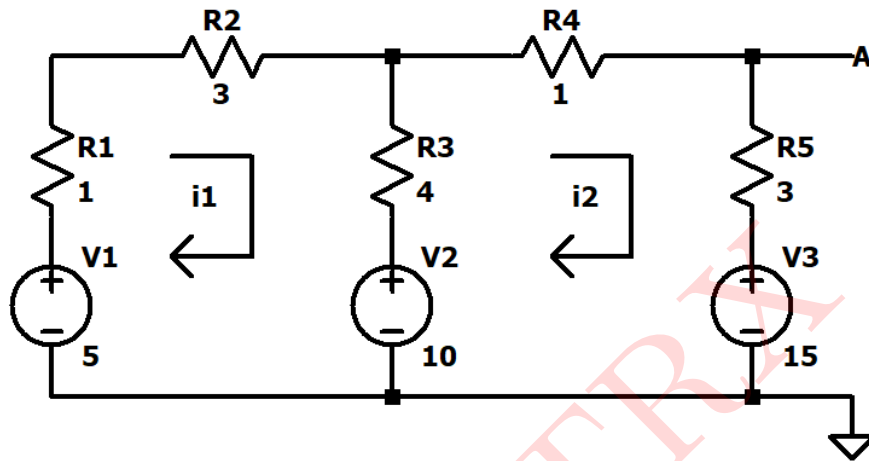


Figure 46: Simplified circuit for Figure 45

Writing the circuit equations:

$$\therefore 8i_1 - 4i_2 = -5 \quad \text{.....(1)}$$

$$\therefore -4i_1 + 8i_2 = -5 \quad \text{.....(2)}$$

Solving equations (1) and (2) simultaneously, we get

$$i_1 = 1.25A, i_2 = 1.25A$$

$$\therefore V_A = 10 + (1.25 \times 1) = 11.25V$$

The Thevenin's equivalent voltage can be calculated as:

$$V_{TH} = V_A - V_B = 11.25 - 21.25 = -10V$$

$$\therefore V_{TH} = 10V$$

STEP II: Calculation of  $R_{TH}$

To find  $R_{TH}$ , we replace the voltage source with short circuit.

The circuit reduces to:

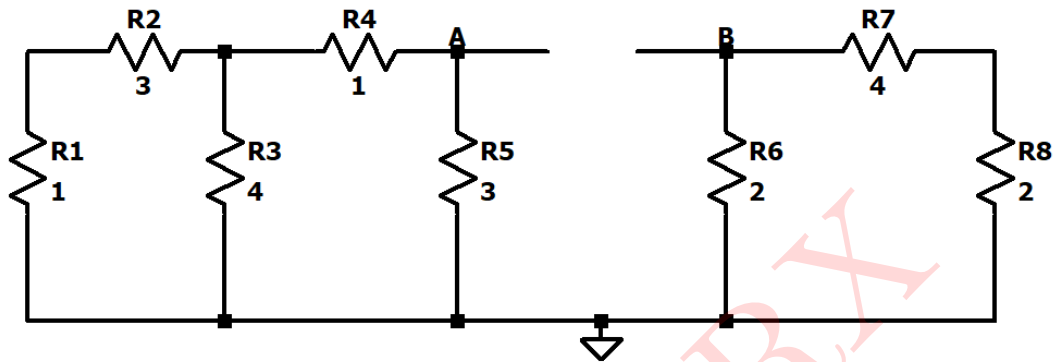


Figure 47: Modified circuit to find  $R_{TH}$

On the left hand side, the equivalent resistance is calculated as  $[(4||4) + 1] || 3 = 1.5\Omega$

Similarly, on the right hand side, the equivalent resistance is calculated as

$$(4 + 2)||2 = 1.5\Omega$$

The circuit further reduces to:

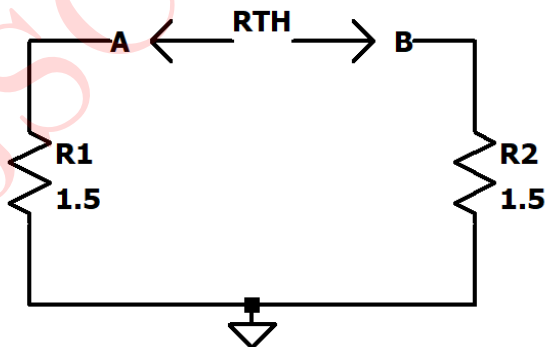


Figure 48: Simplified circuit for Figure 47

$$\therefore R_{TH} = 1.5 + 1.5 = 3\Omega$$

$$\therefore R_{TH} = 3\Omega$$



Thevenin's Equivalent Circuit:

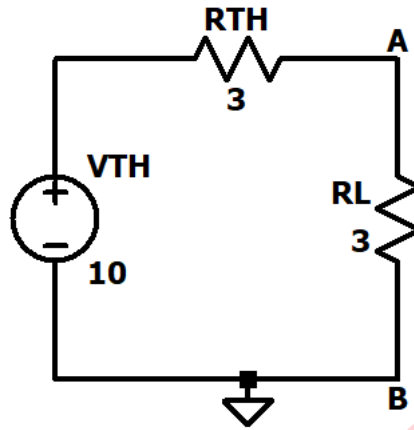


Figure 49: Thevenin's Equivalent Circuit

For maximum power to be transferred,  $R_L = R_{TH} = 3\Omega$

Current( $I$ ) flowing through the circuit is given by:

$$I = \frac{V_{TH}}{R_{TH} + R_L} = \frac{10}{3 + 3} = 1.67A$$

The maximum power transferred can be calculated as:


$$P_{max} = I^2 \times R_{TH} = 1.67^2 \times 3 = 8.3667W$$

**$\therefore$  The maximum power transferred to the load is 8.3667W**

## SIMULATED RESULTS:

The given circuit is simulated in LT Spice. The results are presented below:

### Calculation Of RTH

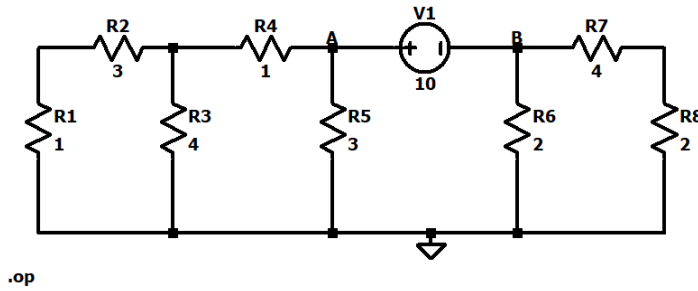


$$R_{TH} = R_{AB} = V_{AB} / I(V_{AB}) = 10 / 3.333 = 3$$

--- Operating Point ---		
V(n001):	0.833333	voltage
V(n002):	3.33333	voltage
V(a):	5	voltage
V(b):	-5	voltage
V(n003):	-1.66667	voltage
I(R8):	-0.833333	device_current
I(R7):	0.833333	device_current
I(R6):	-2.5	device_current
I(R5):	1.66667	device_current
I(R4):	-1.66667	device_current
I(R3):	0.833333	device_current
I(R2):	0.833333	device_current
I(R1):	0.833333	device_current
I(V1):	-3.33333	device_current

Figure 50: Circuit Schematic and Simulated Results for finding  $V_{TH}$
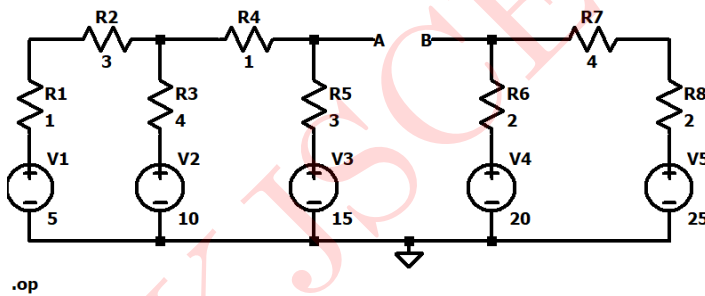
### CALCULATION OF VTH

$$V_{TH} = V_A - V_B = 21.25 - 11.25 = 10$$




--- Operating Point ---		
V(n001):	6.25	voltage
V(n004):	5	voltage
V(n002):	10	voltage
V(n005):	10	voltage
V(a):	11.25	voltage
V(n006):	15	voltage
V(b):	21.25	voltage
V(n007):	20	voltage
V(n003):	23.75	voltage
V(n008):	25	voltage
I(R8):	-0.625	device_current
I(R7):	0.625	device_current
I(R6):	0.625	device_current
I(R5):	-1.25	device_current
I(R4):	-1.25	device_current
I(R3):	0	device_current
I(R2):	1.25	device_current
I(R1):	1.25	device_current

Figure 51: Circuit Schematic finding  $R_{TH}$

**Maximum Power is Transferred when  $R_L = R_{TH} = 3$**

$$P_{max} = (1.67^2) * 3 = 8.3667$$

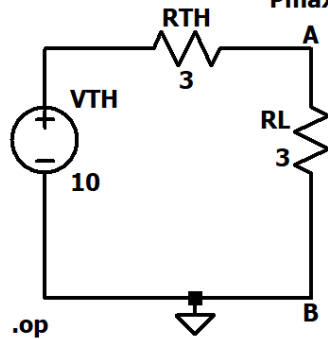

--- Operating Point ---		
V(a) :	5	voltage
V(n001) :	10	voltage
I(R1) :	-1.66667	device_current
I(Rth) :	-1.66667	device_current
I(Vth) :	-1.66667	device_current

Figure 52: Circuit Schematic and Simulated Results for Thevenin's Equivalent circuit

**Comparison of calculated and simulated values:**

Parameters	Calculated Value	Simulated Value
$V_{TH}$	10V	10V
$R_{TH}$	3Ω	3Ω
$P_{max}$	8.3667W	8.3667W

Table 9: Numerical 9