

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Diode Application

Numerical 1: For the circuit shown in figure 1, plot:

- Input $V_{in}(t)$ and output $V_{out}(t)$ waveforms
- VTC curve

Given: $V_{in}(t) = 10V_{p-p}$ sinusoidal signal with frequency of 5000 Hz.

Use constant voltage model i.e. $V_{D1ON} = 0.7 \text{ V}$, $V_B = 1 \text{ V}$, $R_1 = 1 \text{ k}\Omega$

 


Figure 1: Circuit 1

Solution:

The given circuit 1 is a positive bias positive clipper circuit. Assuming constant voltage model for diode D.

$$\therefore V_{D1ON} = 0.7 \text{ V}$$

The diode will be on when anode voltage will be greater than cathode voltage.

Case 1: During positive half cycle, the diode is off. But diode is on for a particular time due to bias voltage.

 


Figure 2: Diode is OFF

Applying KVL to the input loop,

$$V_{in} + V_{D1ON} - V_B - V_{out} = 0$$

$$V_{out} = V_{in} + V_{D1ON} - V_B$$

As the diode is off for positive half cycle, $V_{in} = 0$

$$\therefore V_{out} = 0 + 0.7 - 1 = -0.3 \text{ V}$$

This is the clipping level.

Case 2: During negative half cycle, the diode is on.

 


Figure 3: Diode is ON

Applying KVL to the input loop,

$$V_{in} + V_{D1ON} - V_B - V_{out} = 0$$

$$V_{out} = V_{in} + V_{D1ON} - V_B$$

$$V_{out} = -5 + 0.7 - 1 = -5.3 \text{ V}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

 


Figure 4: Circuit Schematic

The input and output waveforms are shown in figure 5.

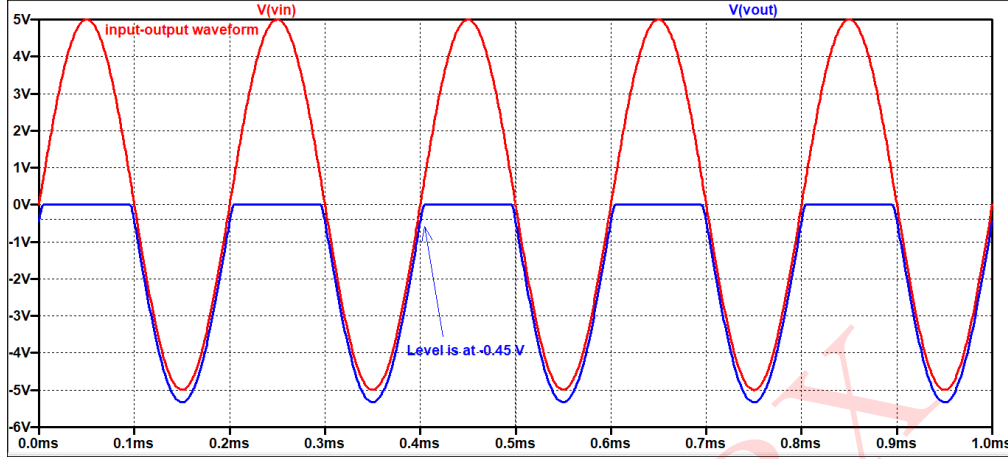


Figure 5: Input & Output waveforms

The VTC curve for the following circuit is given below in figure 6.

 


Figure 6: VTC Curve

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Level of voltage clipped	-0.3 V	-0.45 V

Table 1: Numerical 1

Numerical 2: For the circuit shown in figure 7, plot:

Input $V_{in}(t)$ and output $V_{out}(t)$ waveforms

Given: $V_{in}(t) = 40V_{p-p}$ sinusoidal signal with frequency of 1000 Hz.

For S_i diode: $V_{DON} = 0.7$ V

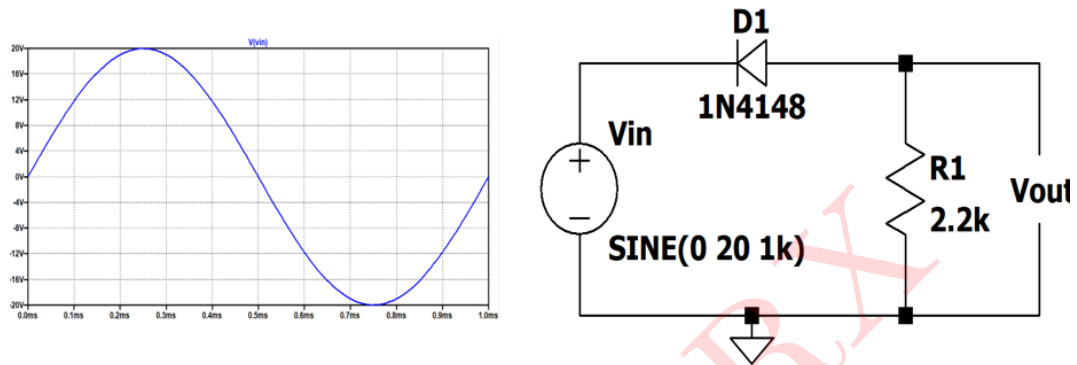


Figure 7: Circuit 2

Solution:

The given circuit 2 is a positive clipper circuit.

Case 1: During positive half cycle, the diode is OFF.

 


Figure 8: Diode is OFF

$\therefore V_o = 0$ V $\dots(\because \text{Diode is OFF})$

This is the clipping level.

Diode will be ON when anode voltage will be greater than cathode voltage.

Case 2: During negative half cycle, the diode is ON, beyond the cathode voltage.

 


Figure 9: Diode is ON

Applying KVL to the input loop,

$$V_{in} + V_{DON} - V_{out} = 0$$

$$V_{out} = V_{in} + V_{DON}$$

$$V_{out} = -20 + 0.7 = -19.3 \text{ V}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

 


Figure 10: Circuit Schematic

The input and output waveforms are shown in figure 11.

 


Figure 11: Input & Output waveforms

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Level of outut voltage clipped	0 V	0 V

Table 2: Numerical 2

Numerical 3: For the circuit shown in figure 12, plot:

Input $V_{in}(t)$ and output $V_{out}(t)$ waveforms

Given: $V_{in}(t) = 40 V_{p-p}$ square wave with frequency of 1000 Hz.

$C = 10 \mu F$, $R = 10 k\Omega$, Diode D_1 is Si diode i.e. $V_{D1ON} = 0.7 V$, $V_1 = 5 V$ DC

 


Figure 12: Circuit 3

Solution:

The given circuit 3 is a positive clamper with neagitive bias.

Since given diode is Si, $V_{D1ON} = 0.7 V$

Assumption:

RC time constant is large enough to ensure that voltage across capacitor does not discharge significantly during the period diode is OFF.

Operation:

a) During negative half cycle, diode D is ON due to biasing voltage which is greater than V_{D1ON} . The circuit becomes,

 


Figure 13: Diode is ON

Voltage across output will be,

$$V_{out} = -V_{D1ON} - V_1$$

$$V_{out} = -0.7 - 5 = -5.7 V$$

At the same time, voltage across capacitor V_c charges upto $-V_{in}$.

Applying KVL to the input loop,

$$V_{in} + V_C + V_{D1ON} + V_1 = 0$$

$$V_C = -V_{in} - V_{D1ON} - V_1$$

$$V_C = 20 - 0.7 - 5 = \mathbf{14.3 \text{ V}}$$

b) During positive half cycle, diode D is OFF. The circuit becomes,

 


Figure 14: Diode is OFF

Note: During positive half cycle, capacitor C holds the charge $V_C = 14.3 \text{ V}$ and acts as a battery.

Applying KVL to the input loop,

$$V_{in} + V_C - V_{out} = 0$$

$$V_{out} = V_{in} + V_C$$

$$V_{out} = 20 + 14.3 = \mathbf{34.3 \text{ V}}$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

 


Figure 15: Circuit Schematic

The input and output waveforms are shown in figure 16.

 


Figure 16: Input & Output waveforms

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Positive Clamping Voltage	34.3 V	34.3885 V
Negative Clamping Voltage	-5.7 V	-5.6158 V

Table 3: Numerical 3
