

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Design of single-stage Amplifier

Design 1:

Design a single stage RC coupled JFET amplifier for following specifications:

$V_o = 2.5V$, $f_L \leq 20Hz$, $|A_V| \geq 10$. Select transistor BFW 11 from the datasheet. Use zero-temperature Drift technique. Calculate A_V , Z_i and Z_o of the amplifier you have designed.

Solution:

We use zero-temperature drift biasing:

1) Data:

$$|A_V| \leq 10, V_o = 2.5V, f_L \leq 20Hz$$

2) Selection of JFET:

We select N-channel JFET BFW 11 from the datasheet with following specifications:

$$g_{m_o} = 5600\mu S, V_P = -2.5V, r_d = 50k\Omega, I_{DSS} = 7mA$$

3) Selection of biasing network:

We select self-bias circuit for our design

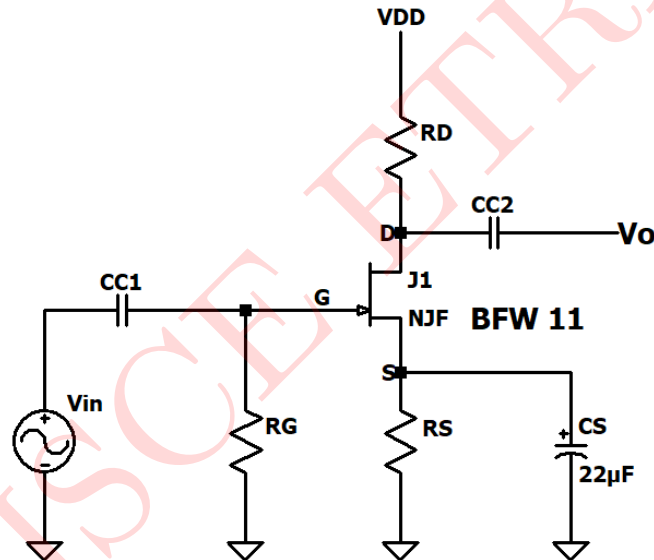


Figure 1: Circuit 1

4) Selection of Q-point:

i) For zero temperature drift,

$$|V_P| - |V_{GS}| = 0.63$$

$$2.5 - |V_{GS}| = 0.63$$

$$\therefore |V_{GS}| = 1.87$$

$$\text{i.e } V_{GS} = -1.87V$$

$$\text{ii) } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 7mA \left(1 - \frac{(-1.87)}{(-2.5)}\right)^2$$

$$I_D = 7mA(1 - 0.748)^2 = 7mA(0.252)^2 = 0.44mA$$

$$\text{iii) } g_m = g_{m_o} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$g_m = 5600 \times 10^{-6} \left(1 - \frac{(-1.87)}{(-2.5)} \right)$$

$$g_m = 5600 \times 10^{-6} (1 - 0.748) = \mathbf{1.4112mA/V}$$

5) Selection of R_S :

$$V_{GS} = -R_S I_D \quad \dots (\text{for self-bias network})$$

$$\text{i.e } R_S = \frac{-V_{GS}}{I_D} = \frac{1.87}{0.44mA} = 4.25k\Omega$$

Select lower standard value(L.S.V) to maintain Q-point in middle of transfer curve.

Select $R_S = \mathbf{3.9k\Omega, 1/4W}$

6) Selection of R_D :

$$A_V = -g_m(r_d \parallel R_D)$$

$$-10 = -g_m \left(\frac{r_d R_D}{r_d + R_D} \right)$$

$$-10 = -1.4112 \times 20^{-3} \left(\frac{50k\Omega \times R_D}{50k\Omega + R_D} \right)$$

$$10R_D + 500k\Omega = 70.56 \times R_D$$

$$500k\Omega = 70.56R_D - 10R_D$$

$$500k\Omega = 60.56R_D$$

$$R_D = \frac{500k\Omega}{60.56} = 8.256k\Omega$$

Select higher standard value(H.S.V) to increase the gain.

Select $R_D = \mathbf{9.1k\Omega, 1/4W}$

7) Selection of R_G :

To prevent loading of preceding stage,

Select $R_G = \mathbf{1M\Omega, 1/4W}$

8) Selection of V_{DD} :

$$V_{DS} \geq V_{o_{peak}} + |V_P| \quad \dots (\text{condition for undistorted output})$$

$$V_{DS} = 1.5(V_{o_{peak}} + |V_P|)$$

$$V_{DS} = 1.5(V_{o_{peak}} + 2.5)$$

The value is multiplied by 1.5 to take care of saturation voltages, tolerance in resistance value, variation in supply voltage and device parameter variation.

$$V_{or_{ms}} = 2.5V$$

$$\therefore V_{o_{peak}} = 2.5\sqrt{2} \quad (\because V_{o_{peak}} = \sqrt{2}V_{or_{ms}})$$

$$\text{i.e } V_{DS} = 1.5(2.5\sqrt{2} + 2.5) = 1.5(6.03) = \mathbf{9.05V}$$

Applying KVL to drain source loop,

 


Figure 2: JFET DC circuit: D-S loop

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$\therefore V_{DD} = V_{DS} + I_D (R_D + R_S)$$

$$V_{DD} = 9.05 + 0.44 \times 10^{-3} (9.1k\Omega + 3.9k\Omega)$$

$$V_{DD} = 9.05 + 0.44 \times 10^{-3} (13k\Omega)$$

$$V_{DD} = 9.05 + 5.72 = 14.77$$

Select $V_{DD} = 15V$

9) Selection of C_S :

$$f_L = 20Hz$$

$$Y_{CS} \leq 0.1R_S$$

$$\text{i.e } \frac{1}{2\pi f_L C_S} \leq 0.1R_S$$

$$\text{i.e } C_S \geq \frac{1}{2\pi f_L \times 0.1R_S}$$

$$\text{i.e } C_S \geq \frac{1}{2\pi \times 20 \times 0.1 \times 3.9k\Omega}$$

$$\text{i.e } C_S \geq 20.4\mu F$$

Select $C_S = 22\mu F / 25V$ (H.S.V)

10) Selection of C_{C1} :

 


Figure 3: Small Signal low frequency equivalent circuit for C_{C1}

$$C_{C1} = \frac{1}{2\pi f_{L_{C_{C1}}} R_{eq}}$$

$$f_{L_{C_{C1}}} = f_L = 20Hz$$

$$R_{eq} = R_G = 1M\Omega$$

$$\therefore C_{C1} = \frac{1}{2\pi \times 20 \times 1M\Omega} = 7.957nF$$

Select $C_{C1} = \mathbf{8.2nF/25V}$ (H.S.V)

11) Selection of C_{C2} :

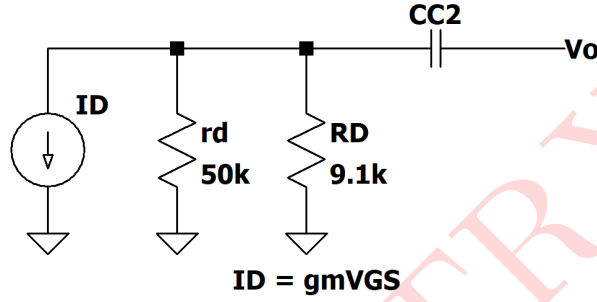


Figure 4: Small Signal Low frequency equivalent circuit for C_{C2}

$$C_{C2} = \frac{1}{2\pi f_{L_{C_{C2}}} R_{eq}}$$

$$R_{eq} = r_d \parallel R_D$$

$$R_{eq} = 50k\Omega \parallel 9.1k\Omega$$

$$R_{eq} = \frac{50k\Omega \times 9.1k\Omega}{50k\Omega + 9.1k\Omega} = 7.698k\Omega$$

$$f_{L_{C_{C2}}} = f_L = 20Hz$$

$$\therefore C_{C2} = \frac{1}{2\pi \times 20 \times 7.698k\Omega} = 1.03\mu F$$

Select $C_{C2} = \mathbf{1.2\mu F}$ (H.S.V)

12) Designed circuit is,

 


Figure 5: Designed Circuit

Small signal equivalent circuit:

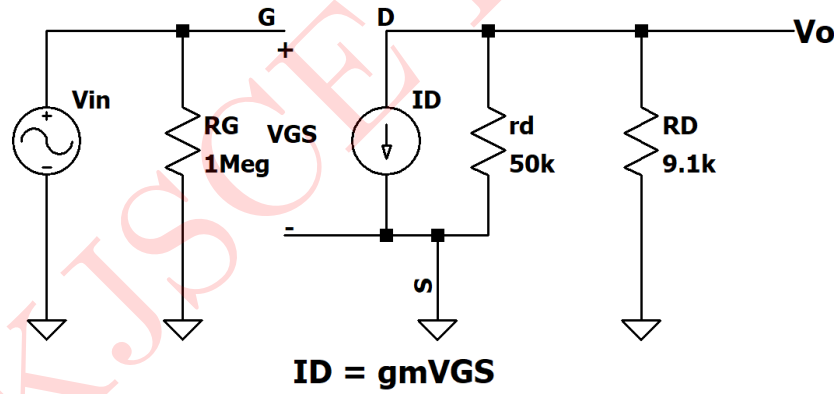


Figure 6: Small signal equivalent circuit

$$A_V = -g_m(r_d \parallel R_D)$$

$$\begin{aligned} \therefore A_V &= -1.4112 \text{mA/V} (50 \text{k}\Omega \parallel 9.1 \text{k}\Omega) \\ &= -1.4112 \text{mA/V} \left(\frac{50 \text{k}\Omega \times 9.1 \text{k}\Omega}{50 \text{k}\Omega + 9.1 \text{k}\Omega} \right) \\ &= -1.4112 \text{mA/V} (7.698 \text{k}\Omega) = -10.86 \end{aligned}$$

Input impedance,
 $Z_i = R_G = 1\text{M}\Omega$

Output impedance,
 $Z_o = r_d \parallel R_D$
 $= 50\text{k}\Omega \parallel 9.1\text{k}\Omega$
 $= \frac{50\text{k}\Omega \times 9.1\text{k}\Omega}{50\text{k}\Omega + 9.1\text{k}\Omega} = 7.698\text{k}\Omega$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

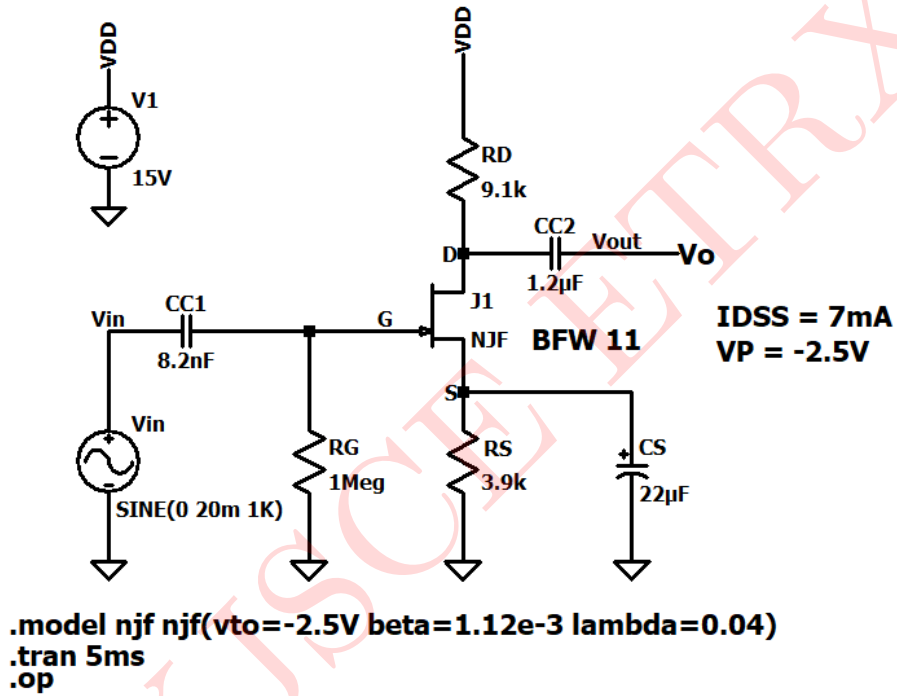


Figure 7: Circuit Schematic

The input and output waveforms are shown in figure 8.

 


Figure 8: Input-Output waveforms

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_D	0.44mA	0.4741mA
$ A_V $	≥ 10	13.79

Table 1: Design 1
