

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Diode Application**

**Numerical 1:**

For the circuit shown below in figure 1, plot

a) Input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms

b) VTC curve

Given:  $V_{in}(t) = 10V_{p-p}$  Sinusoidal signal with frequency of 5000Hz

$V_{D_{ON}} = 0.7V$

$V_{B_1} = 1V$  DC,  $V_{B_2} = 1V$  DC,  $R_1 = 1k\Omega$

 


Figure 1: Circuit 1

**Solution:**

Assuming constant voltage models for diodes  $D_1$  and  $D_2$

When input voltage  $V_{in}$  is greater than  $(V_{D_{ON}} + V_{B_1})$  i.e  $0.7V + 1V = 1.7V$ , diode  $D_1$  is ON and  $D_2$  is OFF.

$\therefore V_{out} = V_{D_{ON}} + V_{B_1} = 0.7 + 1 = 1.7V$

$\therefore$  figure 1 reduces to,

 


Figure 2: diode  $D_1$  is ON and diode  $D_2$  is OFF

When input voltage  $V_{in}$  is less than  $(-V_{D_{2ON}} - V_{B_2})$  i.e  $-0.7V - 1V = -1.7V$ , diode  $D_2$  is ON and  $D_1$  is OFF.

$$\therefore V_{out} = -V_{D_{2ON}} - V_{B_2} = -0.7 - 1 = -1.7V$$

$\therefore$  figure 1 reduces to,

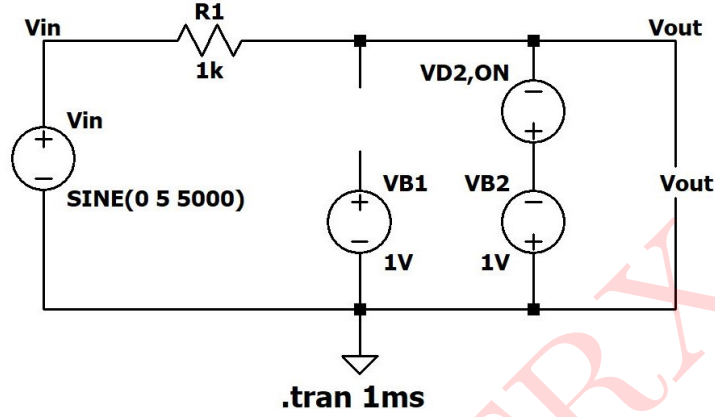


Figure 3: diode  $D_2$  is ON and diode  $D_1$  is OFF

When  $V_{in}$  is less than  $(V_{B_1} + V_{D_{1ON}})$  and also greater than  $(-V_{D_{2ON}} - V_{B_2})$ , both diodes  $D_1$  and  $D_2$  are OFF.

$$\therefore V_{out} = V_{in}$$

$\therefore$  figure 1 reduces to,

 


Figure 4: diode  $D_1$  and diode  $D_2$  are OFF

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

 


Figure 5: Circuit Schematic

The input and output waveforms are shown in figure 6.

 


Figure 6: Input-Output waveforms

The VTC curve for the following circuit is given below in figure 7.

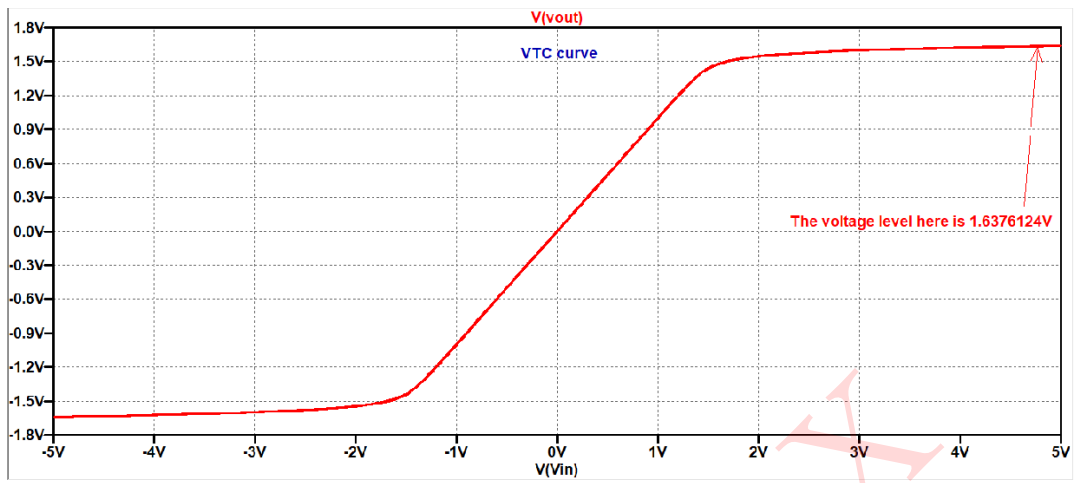


Figure 7: VTC curve

**Comparison between theoretical and simulated values:**

Parameters	Theoretical values	Simulated values
Clipped output voltage level	$\pm 1.7V$	$\pm 1.640017$

Table 1: Question 1

**Numerical 2:**

For the circuit shown below in figure 8,

Plot: Input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms

Given:  $V_{in}(t)$  is a square wave as shown in figure 9

 


Figure 8: Circuit 2

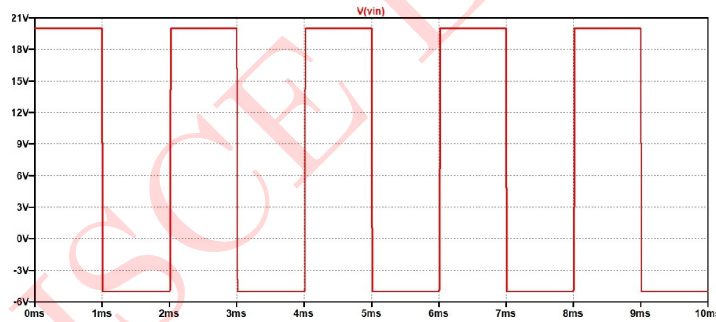


Figure 9: Square wave input

**Solution:**

Assuming constant voltage model for diode  $D_1$ ,

When input voltage  $V_{in}$  is greater than  $(V_{D_{1ON}} + V_B)$  i.e  $0.7V + 5V = 5.7V$ , diode  $D_1$  is ON.

$$\therefore V_{out} = V_{in} - V_{D_{ON}}$$

∴ figure 8 reduces to,

 


Figure 10: diode  $D_1$  is ON

$$\therefore V_{out} = V_{in} - V_{D_{ON}}$$

$$\text{i.e } V_{out} = V_m - V_{D_{ON}} = 20.0.7 = \mathbf{19.3V}$$

i.e output tracks input but with a shift of  $V_{D_{ON}}$  i.e 0.7V

When  $V_{in}$  is less than  $(V_{D_{ON}} + V_B)$  i.e  $0.7V + 5V = 5.7V$ , diode  $D_1$  is OFF.

∴ figure 8 reduces to,

 


Figure 11: diode  $D_1$  is OFF

$$\therefore V_{out} = V_B$$

$$\text{i.e } V_{out} = \mathbf{5V}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

 


Figure 12: Circuit Schematic

The input and output waveforms are shown in figure 13.

 


Figure 13: Input-Output waveforms

**Comparison between theoretical and simulated values:**

Parameters	Theoretical values	Simulated values
Clipped maximum output voltage level	19.3V	19.3272V
Clipped minimum output voltage level	5V	4.999V

Table 2: Question 2

KJSCE ETRX



**Numerical 3:**

For the circuit shown below in figure 14,

Plot: Input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms

Given:  $10V_{p-p}$  square wave of frequency 1000Hz

$C = 10\mu\text{F}$  and  $R = 10\text{k}\Omega$ , diode  $D_1$  is Si diode i.e  $V_{D_{ON}} = 0.7\text{V}$ ,  $V_1 = 2.7\text{V}$  DC

 


Figure 14: Circuit 3

 


Figure 15: Square wave input

**Solution:**

Since given diode  $D_1$  is Si diode, we will use constant voltage model i.e  $V_{D_{ON}} = 0.7\text{V}$

Given:  $V_{in} = 10V_{p-p}$  i.e  $V_m = 5\text{V}$

Assumption: RC time constant is large enough (than time period of input signal) to ensure that voltage across capacitor does not discharge significantly during the period diode is off.

Operation:

- During negative half cycle,  $D_1$  is ON when  $V_{in} < (-V_{D_{ON}} + V_1)$  i.e  $V_{in} < (-0.7\text{V} + 2.7\text{V})$  i.e  $V_{in} < 2\text{V}$

∴ figure 14 reduces to,

 


Figure 16: diode  $D_1$  is ON

$$\therefore V_{out} = V_{D_{ON}} + V_1 = -0.7V + 2.7V = 2V$$

i.e  $V_{out} = 2V$  during negative half cycle

b) At the same time, voltage across capacitor  $V_C$  charges upto  $-V_m$

KVL gives us:

$$V_{in} + V_C + V_{D_{ON}} - V_1 = 0$$

$$V_C = -V_{in} - V_{D_{ON}} + V_1 \quad (\because \text{In negative half cycle, } V_{in} = V_m)$$

$$V_C = -(-V_m) - 0.7 + 2.7 = 5 - 0.7 + 2.7 = 7V$$

i.e  $V_C = 7V$  is voltage across capacitor  $C_1$  during positive half cycle

c) During positive half cycle, diode  $D_1$  is OFF for entire positive half cycle

∴ figure 14 reduces to,

 


Figure 17: diode  $D_1$  is OFF

During positive half cycle, capacitor  $C_1$  holds the charge  $V_C = 7V$  and acts as a battery  
 $\therefore$  KVL gives us:  
 $V_{in} + V_C - V_{out} = 0$   
 $\therefore V_{out} = V_{in} + V_C$   
 $V_{out} = V_m + V_C$  ( $\because$  In positive half cycle,  $V_{in} = V_m$ )  
 $V_{out} = 5 + 7 = 12V$   
 i.e  $V_{out} = 12V$  during positive half cycle

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

 


Figure 18: Circuit Schematic

The input and output waveforms are shown in figure 19.

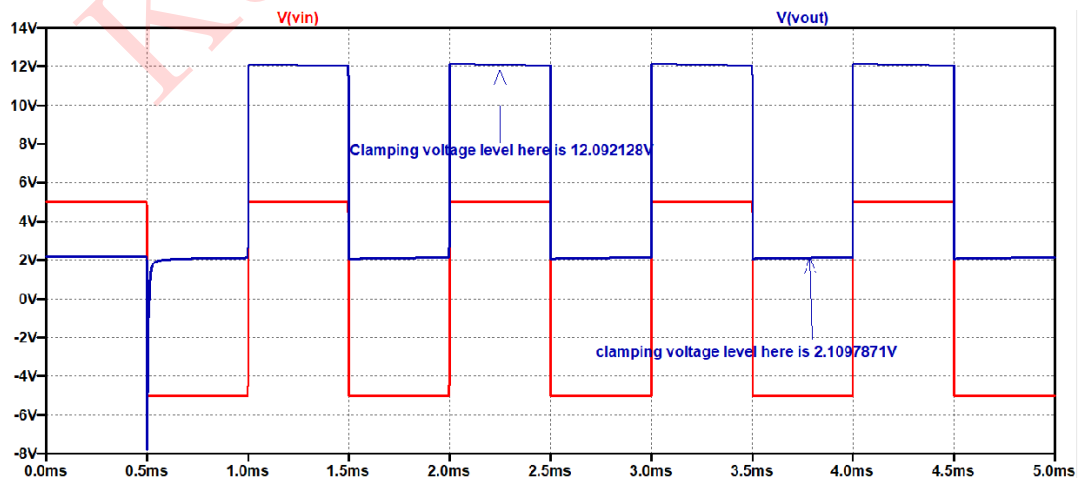


Figure 19: Input-Output waveforms

**Comparison between theoretical and simulated values:**

Parameters	Theoretical values	Simulated values
Upper level of clamped output voltage	12V	12.0921V
Lower level of clamped output voltage	2V	2.1097V

Table 3: Question 3

\*\*\*\*\*

KJSCE ETRX