

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Power Amplifier Circuits

Numerical 1:

In class AB-push pull power amplifier, load R_L is 15Ω , $V_{CC} = 22V$, $V_{EE} = -22V$. AC Input voltage is $20V$ peak, frequency is $1000Hz$. Calculate efficiency of the circuit

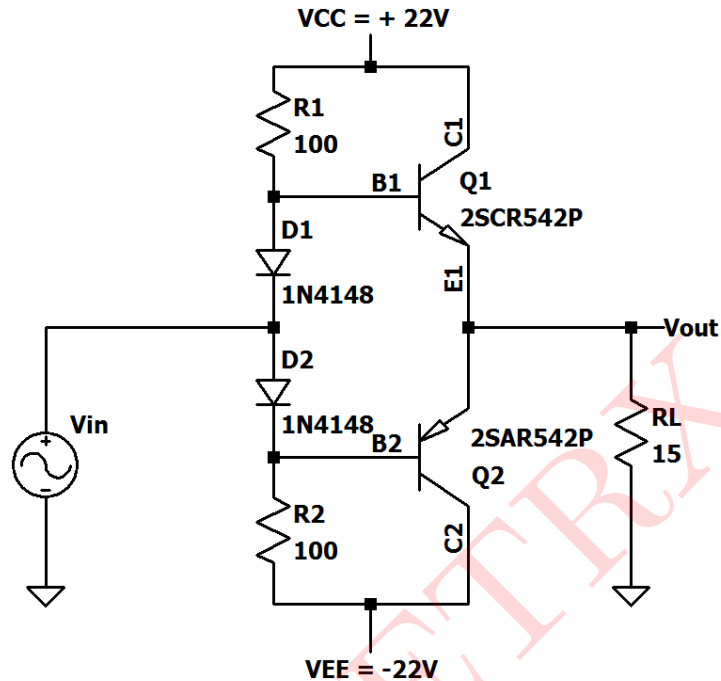


Figure 1: Circuit 1

Solution:

$$V_{in} = V_m \sin(\omega t) = V_m \sin(2\pi f t) = 20 \times \sin(2\pi 1000 t)$$

$$V_m = 20V$$

$$P_{ac} = \frac{V_m^2}{2R_L} = \frac{20^2}{2 \times 15} = 13.33W$$

$$P_{ac} = 13.33W$$

$$I_m = \frac{V_m}{R_L} = \frac{20}{15} = 1.333A$$

$$I_m = 1.333A$$

$$P_{dc} = \frac{2V_{CC}I_m}{\pi} = \frac{2 \times 22 \times 1.333}{\pi} = 18.67W$$

$$P_{dc} = 18.67W$$

$$\text{Efficiency } \eta = \frac{P_{ac}}{P_{dc}} = \frac{13.33W}{18.67W} = 0.714 = 71.4\%$$

$$\eta = 71.4\%$$

SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

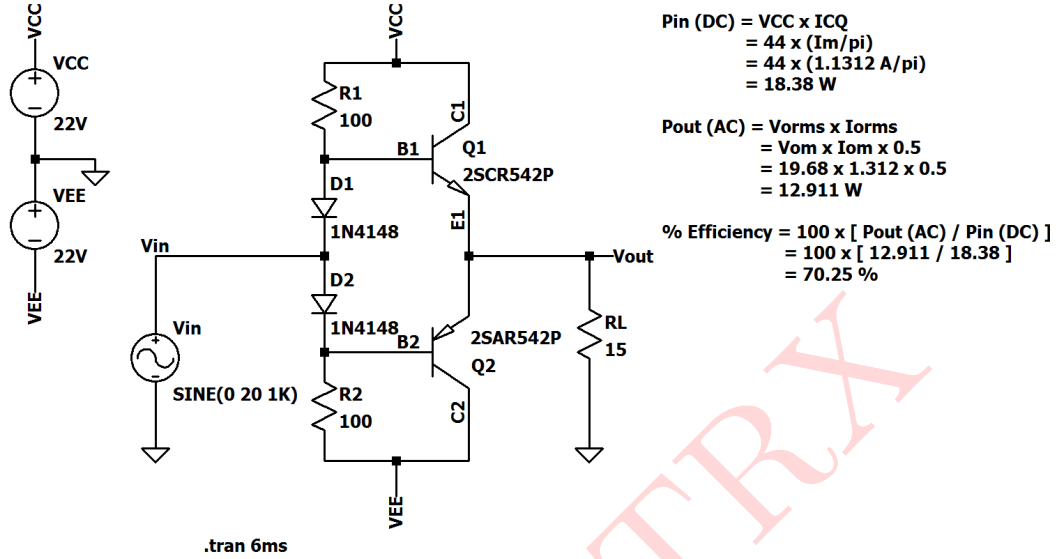


Figure 2: Circuit Schematic 1 Results

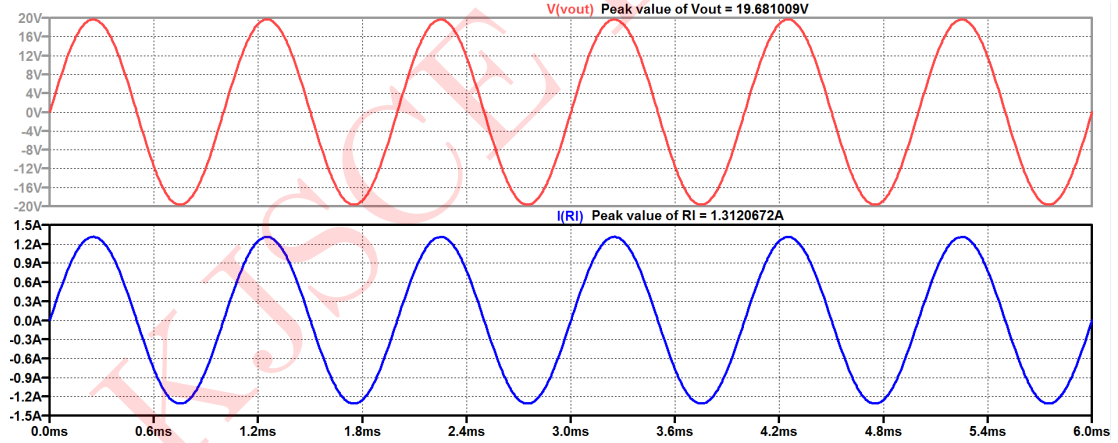


Figure 3: Output load voltage and load current waveforms

Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
Input DC power	18.67W	18.38W
Input AC power	13.333W	12.911W
Efficiency	71.4%	70.25%

Table 1: Numerical 1

KJSCE ETRX