

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DIODE APPLICATIONS

Numerical 1: Simulate a half wave rectifier circuit with input Amplitude = 220V peak, $f = 50\text{Hz}$ and $R_1 = 95\ \Omega$ using LTspice. Select diode as 1N4148. Use 10:1 step down transformer. Plot the following using LTspice:

- Primary peak voltage.
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diodes
- Current flowing through the circuit

Also calculate the efficiency of the Half wave rectifier circuit.

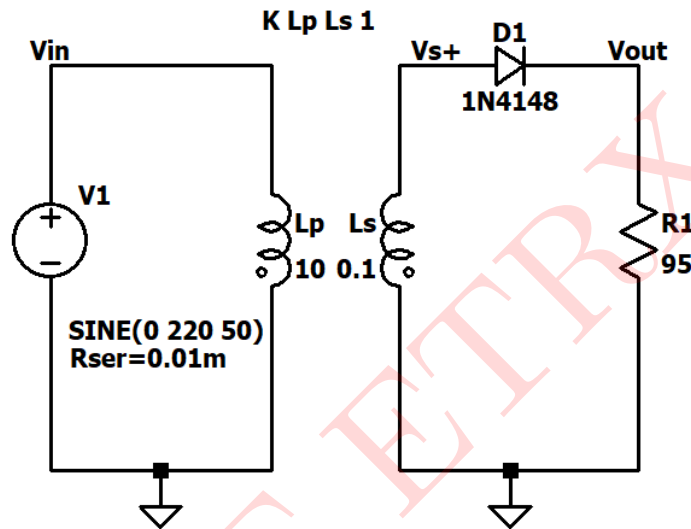


Figure 1: Circuit 1

Given:

$$R_1 = 95\ \Omega$$

$$R_S = 0.01\text{m}\ \Omega$$

$$V_{in} = 220\text{V}$$

$$f = 50\text{Hz}$$

Solution:

Since, $V_{in} = 220\text{V}$

\therefore Primary peak voltage = 220V

Also, turn ratio is 10:1

$$\therefore V_m = \frac{220}{10}$$

$$\therefore V_m = 22\text{V}$$

\therefore Secondary peak voltage = 22V

Current:

$$I_m = \frac{V_m}{R_1 + R_S}$$
$$\therefore I_m = \frac{22}{95 + 0.01 \times 10^{-3}}$$
$$\therefore I_m = 0.231578$$
$$\therefore I_m = \mathbf{231.578mA}$$

DC output power:

$$P_{DC} = \left(\frac{I_m}{\pi} \right)^2 R_1$$
$$\therefore P_{DC} = \left(\frac{231.578 \times 10^{-3}}{\pi} \right)^2 \times 95$$
$$\therefore P_{DC} = \mathbf{0.489W}$$

AC output power:

$$P_{AC} = \left(\frac{I_m}{2} \right)^2 (R_1 + R_S)$$
$$\therefore P_{AC} = \left(\frac{231.578 \times 10^{-3}}{2} \right)^2 \times (95 + 0.01 \times 10^{-3})$$
$$\therefore P_{AC} = \mathbf{1.27367W}$$

Efficiency:

$$\eta = \frac{P_{AC}}{P_{DC}} \times 100$$
$$\therefore \eta = \frac{1.27367}{0.489} \times 100$$
$$\therefore \eta = \mathbf{40.5 \%}$$

PIV rating of diode:

$$\text{PIV rating} = -V_m$$
$$\therefore \mathbf{\text{PIV rating} = -22V}$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

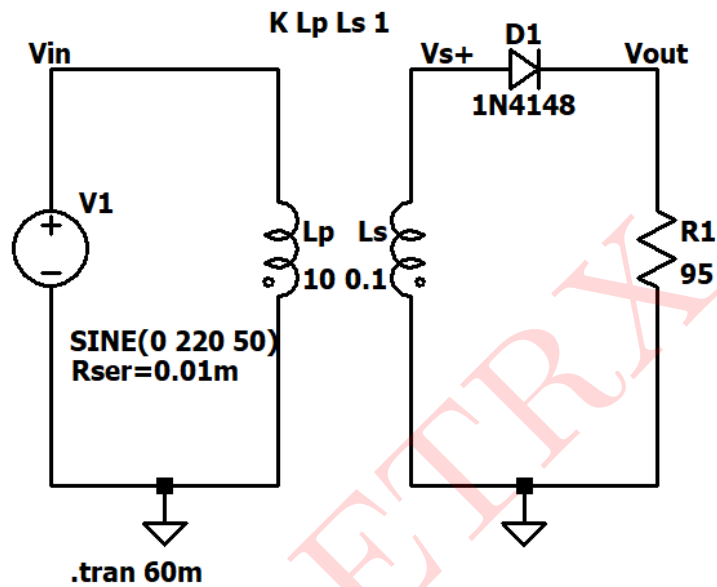


Figure 2: Circuit Schematic and Simulated Results

The waveforms are shown in figure 3

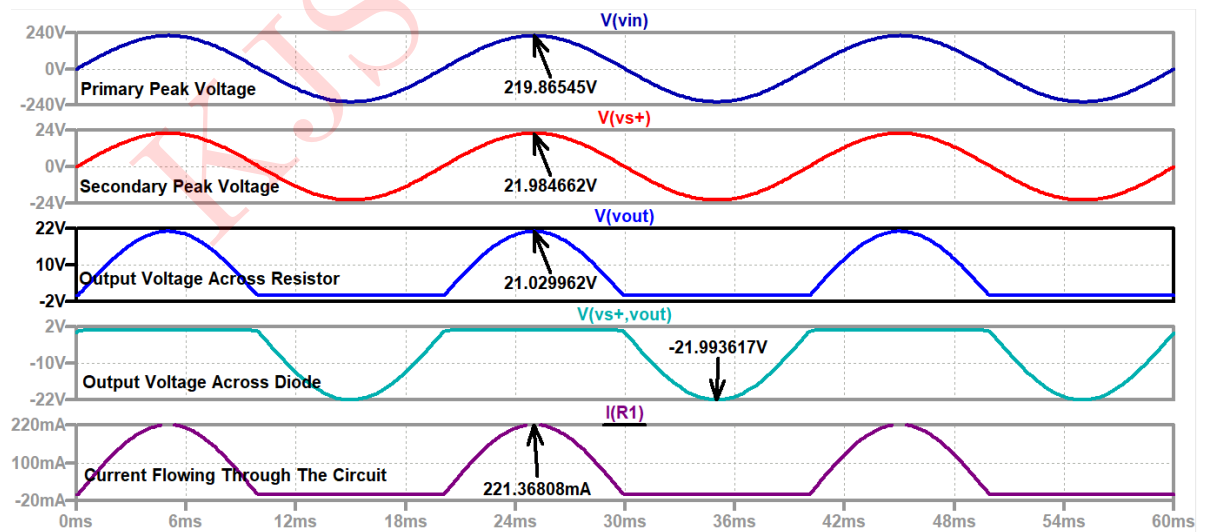


Figure 3: waveforms obtained

Calculation:

DC output power:

$$P_{DC} = \frac{V_m^2}{\pi^2 R_1}$$

$$\therefore P_{DC} = \frac{21.0299^2}{\pi^2 \times 95}$$

$$\therefore P_{DC} = \mathbf{0.471W}$$

AC output power:

$$P_{AC} = \frac{V_m^2}{4(R_1 + R_S)}$$

$$\therefore P_{AC} = \frac{21.0299^2}{4(95 + 0.01 \times 10^{-3})}$$

$$\therefore P_{AC} = \mathbf{1.1638W}$$

Efficiency:

$$\eta = \frac{P_{AC}}{P_{DC}} \times 100$$

$$\therefore \eta = \frac{1.1638}{0.471} \times 100$$

$$\therefore \eta = \mathbf{40.5282 \%}$$

PIV rating of diode:

$$\text{PIV rating} = -V_m$$

$$\therefore \text{PIV rating} = - \mathbf{21.984V}$$

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Output peak value (V_m)	22V	21.0299V
Output Peak current (I_m)	231.578mA	221.368mA
AC power	1.2736W	1.1638W
DC power	0.489W	0.471W
Efficiency	40.5 %	40.52 %
PIV rating	– 22V	– 21.9846V

Table 1: Numerical 1

Numerical 2: Simulate a Full wave rectifier circuit with input Amplitude = 220V peak, $f = 50\text{Hz}$ and $R_1 = 90\ \Omega$ using LTspice. Select diode as 1N4148. Use 10:1 step down transformer. Plot the following using LTspice:

- Primary peak voltage.
- Secondary peak voltage
- Output voltage across resistor
- Output voltage across diodes
- Current flowing through the diodes
- Current flowing through the circuit

Also calculate the efficiency of the Full wave Center tapped rectifier circuit.

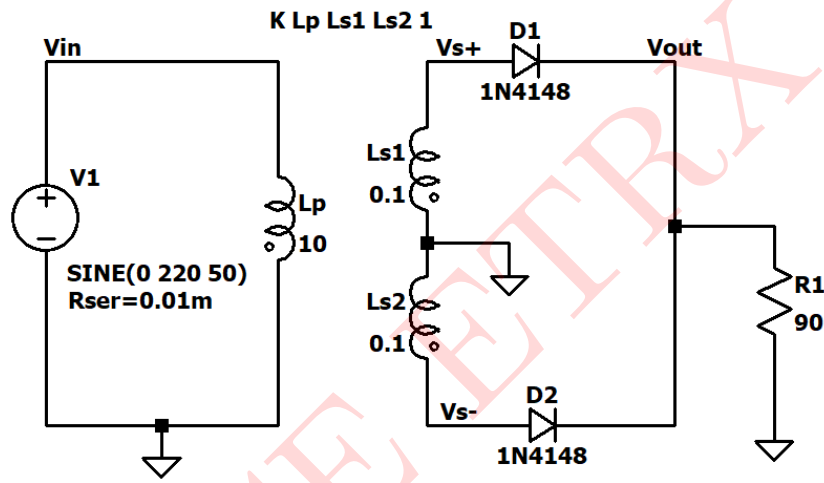


Figure 4: Circuit 2

Given:

$$R_1 = 90\ \Omega$$

$$R_S = 0.01\text{m}\ \Omega$$

$$V_{in} = 220\text{V}$$

$$f = 50\text{Hz}$$

Solution:

$$\text{Since, } V_{in} = 220\text{V}$$

$$\therefore \text{Primary peak voltage} = 220\text{V}$$

Also, turn ratio is 10:1

$$\therefore V_m = \frac{220}{10}$$

$$\therefore V_m = 22\text{V}$$

$$\therefore \text{Secondary peak voltage} = 22\text{V}$$

Current:

$$I_m = \frac{V_m}{R_1 + R_S}$$
$$\therefore I_m = \frac{22}{90 + 0.01 \times 10^{-3}}$$
$$\therefore I_m = 0.244444$$
$$\therefore I_m = \mathbf{244.444mA}$$

DC output power:

$$P_{DC} = \left(\frac{2I_m}{\pi} \right)^2 R_1$$
$$\therefore P_{DC} = \left(\frac{2 \times 244.444 \times 10^{-3}}{\pi} \right)^2 \times 90$$
$$\therefore P_{DC} = \mathbf{2.1795W}$$

AC output power:

$$P_{AC} = \frac{I_m^2}{2} (R_1 + R_S)$$
$$\therefore P_{AC} = \frac{(244.444 \times 10^{-3})^2}{2} \times (90 + 0.01 \times 10^{-3})$$
$$\therefore P_{AC} = \mathbf{2.6888W}$$

Efficiency:

$$\eta = \frac{P_{AC}}{P_{DC}} \times 100$$
$$\therefore \eta = \frac{2.1795}{2.6888} \times 100$$
$$\therefore \eta = \mathbf{81.05 \%}$$

PIV rating of diode:

$$\text{PIV rating} = -2V_m$$

$$\therefore \text{PIV rating of Diode } D_1 = -44V$$

$$\therefore \text{PIV rating of Diode } D_2 = -44V$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

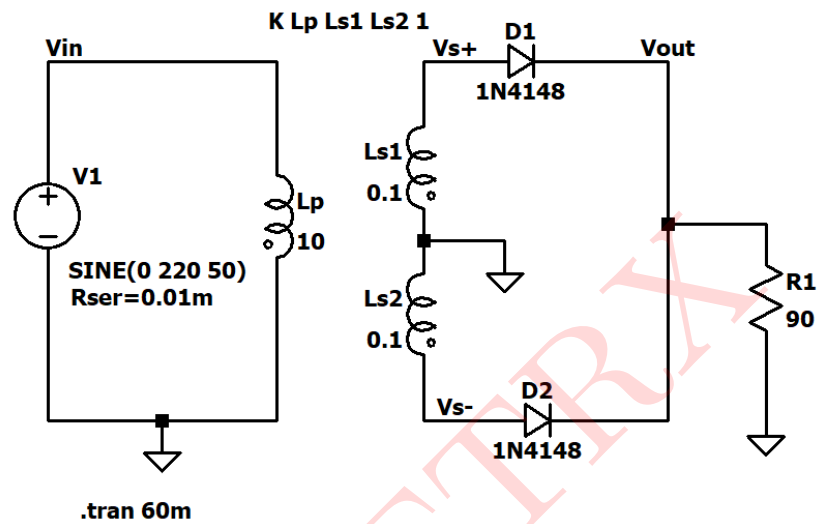


Figure 5: Circuit Schematic and Simulated Results

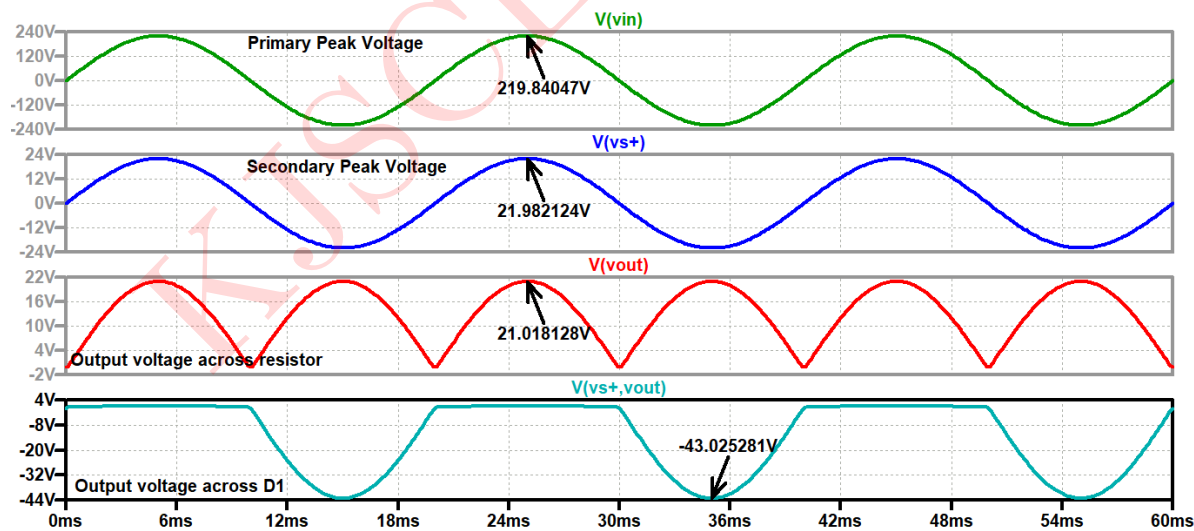


Figure 6: Waveforms obtained

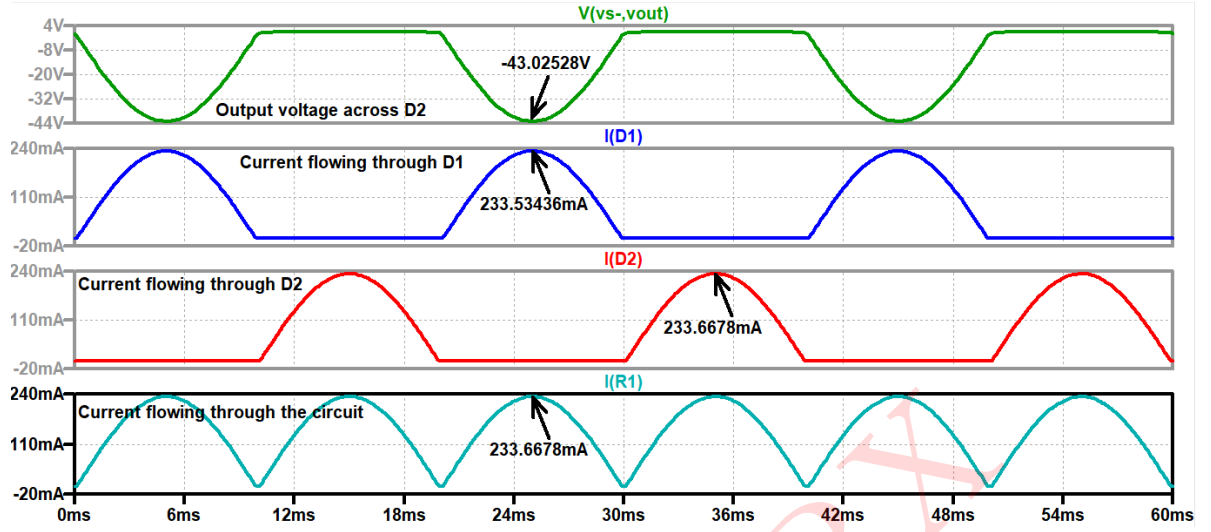


Figure 7: Waveforms obtained

Calculation:

DC output power:

$$P_{DC} = \frac{4I_m^2 R_1}{\pi^2}$$

$$\therefore P_{DC} = \frac{4 \times (233.6678 \times 10^{-3})^2 \times 90}{\pi^2}$$

$$\therefore P_{DC} = \mathbf{1.9915W}$$

AC output power:

$$P_{AC} = \frac{I_m^2}{2} (R_1 + R_S)$$

$$\therefore P_{AC} = \frac{(233.6678 \times 10^{-3})^2}{2} (90 + 0.01 \times 10^{-3})$$

$$\therefore P_{AC} = \mathbf{2.457W}$$

Efficiency:

$$\eta = \frac{P_{AC}}{P_{DC}} \times 100$$

$$\therefore \eta = \frac{1.9915}{2.457} \times 100$$

$$\therefore \eta = \mathbf{81.05659 \%}$$

PIV rating of diode:

$$\text{PIV rating} = -2V_m$$

$$\therefore \text{PIV rating of } D_1 = -43.025\text{V}$$

$$\therefore \text{PIV rating of } D_2 = -43.025\text{V}$$

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Output peak voltage (V_m)	22V	21.018V
Output peak current (I_m)	244.444mA	233.667mA
AC power	2.688W	2.457W
DC power	2.179W	1.9915W
Efficiency	81.05 %	81.05 %
PIV rating	- 44V	- 43.025V

Table 2: Numerical 2