

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Single Stage BJT Amplifier**

11<sup>th</sup> July, 2020

Numericals

**Numerical 1:** For the circuit shown below in figure 1. Determine:

- a)  $r_{\pi}$
- b)  $Z_i$  and  $Z_o$
- c)  $A_v$  (voltage gain)

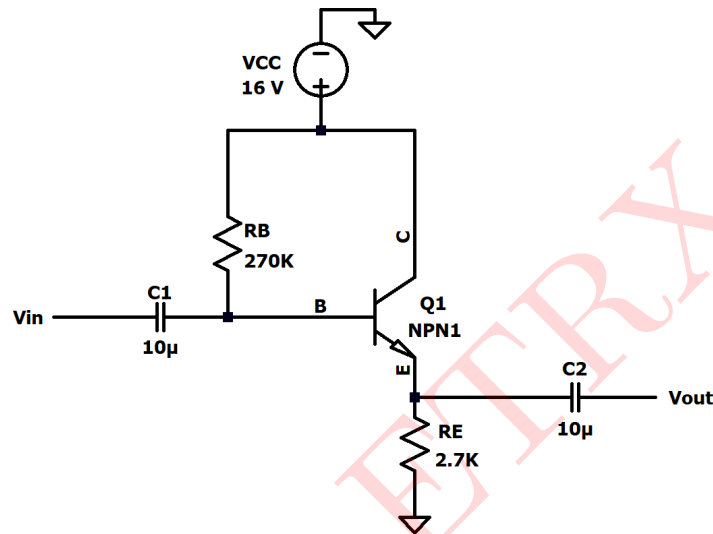


Figure 1: Circuit 1

**Solution: DC ANALYSIS:**

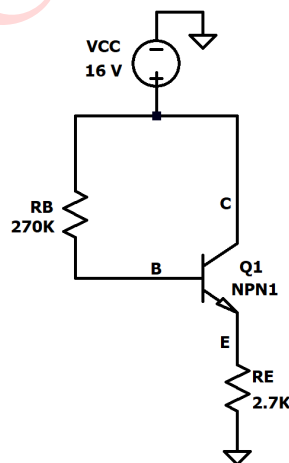


Figure 2: DC Equivalent Circuit

By applying KVL to base - emitter loop,

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = (\beta + 1)I_B$$

$$\therefore V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{[R_B + (\beta + 1)R_E]} = \frac{16 - 0.7}{[270k + (11)(2.7k)]} = \frac{15.3}{5697 \times 10^3} = \mathbf{26.8\mu A}$$

$$I_C = \beta I_B = 110 \times 26.8 \times 10^{-6} = \mathbf{2.95mA}$$

Applying KVL to the collector emitter loop:

$$V_{CC} - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - (1 + \beta)I_B R_E = 16 - (111)(26.8 \times 10^{-6})(2.7 \times 10^3) = \mathbf{8V}$$

(As  $I_E = (1 + \beta)I_B$ )

### AC ANALYSIS:

a) Small Signal Parameter:

$$g_m = \frac{I_{CQ}}{V_T}$$

Here,  $V_T = 26mV$

$$g_m = \frac{2.95 \times 10^{-3}}{26 \times 10^{-3}} = 0.11346 = \mathbf{113.46mA/V}$$

$r_o = 50k\Omega$  (given)

$$r_\pi = \frac{V_T}{I_{BQ}} = \frac{26 \times 10^{-3}}{26.8 \times 10^{-6}} = \mathbf{970.14\Omega}$$

b) Small-Signal Equivalent Circuit shown in figure 3.

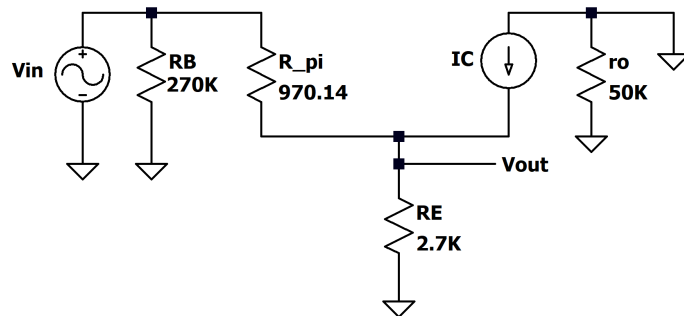


Figure 3: Small Signal Equivalent Circuit

c)  $Z_i$  (Input Impedence)

$$Z_i = R_B \parallel (r_\pi + (1 + \beta)R_E) = 270 \times 10^3 \parallel (970.14 + (111)(2.7 \times 10^3))$$

$$Z_i = 270 \times 10^3 \parallel 300.67 \times 10^3 = \mathbf{142.25k\Omega}$$

d)  $Z_o$  (Output Impedence)

$$Z_o = R_E \parallel \frac{1}{g_m} \parallel r_o = (R_E \parallel r_o) \parallel \frac{1}{g_m} = 270 \times 10^3 \parallel 50 \times 10^3 \parallel \frac{1}{113.46 \times 10^{-3}} = \mathbf{0.113\Omega}$$

e)  $A_V$  (Voltage Gain)

$$\frac{V_{out}}{V_{in}} = A_V = \frac{g_m R_E}{1 + g_m R_E} = \frac{113.46 \times 10^{-3} \times 2.7 \times 10^3}{1 + (113.46 \times 10^{-3})(2.7 \times 10^3)} = 1$$

#### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

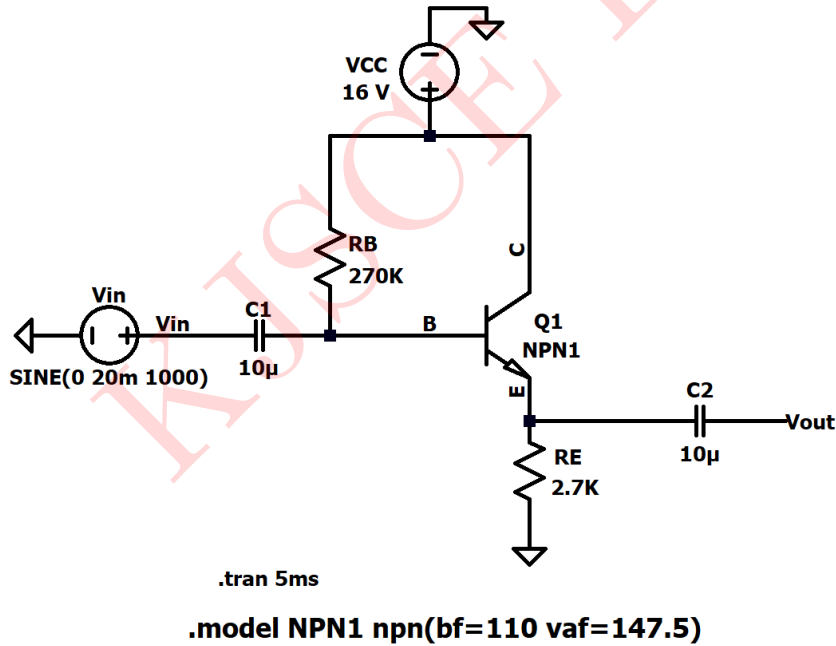


Figure 4: Circuit Schematic

The input and output waveforms are shown in figure 5.

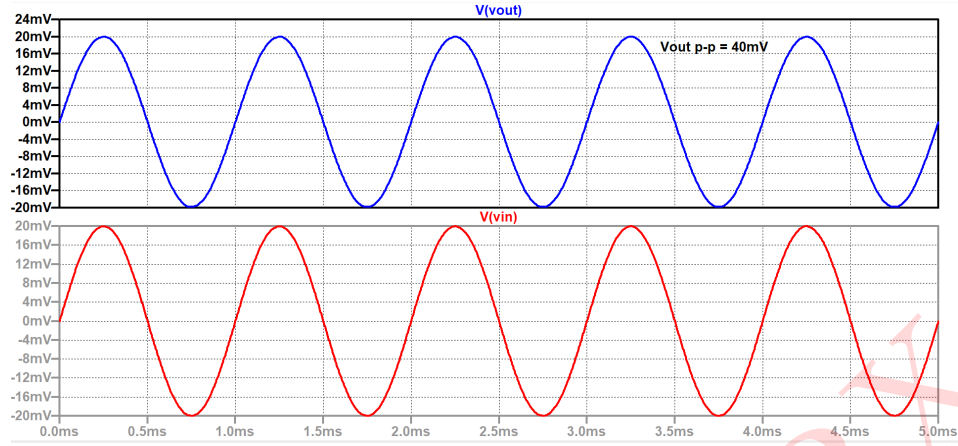


Figure 5: Input and output waveform

**Comparison between Theoretical and Simulated values :-**

Parameter	Simulated	Theoretical
$I_C$	2.9mA	2.95mA
$I_B$	$26\mu A$	$26.8\mu A$
$V_{CE}$	7.9V	8V
$A_V$	1	1

Table 1: Numerical 1

**Numerical 2:** For the circuit shown below in figure 6. Determine:

- a)  $r_\pi$
- b)  $Z_i$  and  $Z_o$
- c)  $A_v$  (voltage gain)

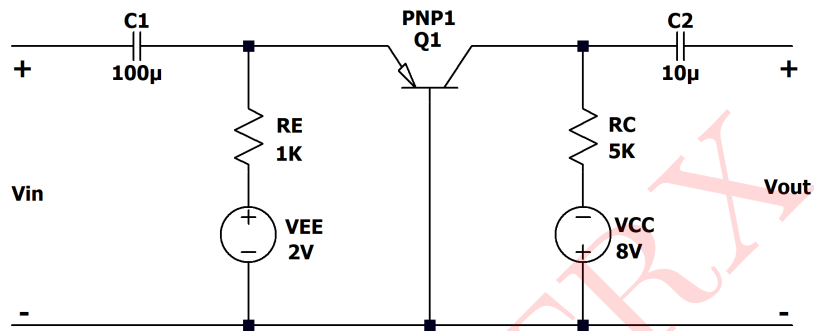


Figure 6: Circuit 2

**Solution:** The above circuit consists of a common base configuration employing pnp configuration

**DC ANALYSIS:**

For DC equivalent circuit,  $f = 0$ ,  $X_C = \frac{1}{2\pi fC} = \infty$

So capacitors are replaced by an open circuit

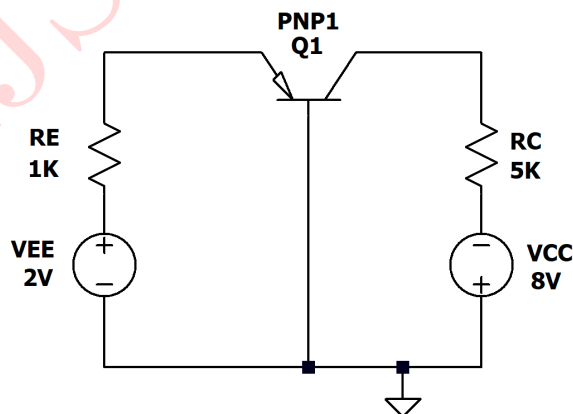


Figure 7: DC Equivalent Circuit

By applying KVL to base - emitter loop,

$$V_{EE} - I_E R_E - V_{BE} = 0$$

$$I_E = \frac{V_{EE} - V_{BE}}{R_E} = \frac{2 - 0.7}{1 \times 10^3} = \mathbf{1.3mA}$$

$$I_C = \alpha I_E = 0.98 \times 1.3 \times 10^{-3} = \mathbf{1.27mA}$$

### AC ANALYSIS:

All the DC sources are open circuited and the capacitors are replaced by short circuit.

a) Small Signal Parameter:

$$g_m = \frac{I_{CQ}}{V_T}$$

$$\text{Here, } V_T = 26mV$$

$$g_m = \frac{1.27 \times 10^{-3}}{26 \times 10^{-3}} = 0.049 = \mathbf{49mA/V}$$

$$r_o = 1M\Omega$$

$$r_\pi = \frac{\beta V_T}{I_{BQ}}$$

$$\alpha = 0.98$$

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.98}{1 - 0.98} = \mathbf{49}$$

$$r_\pi = \frac{49 V_T}{I_{BQ}} = \frac{49 \times 26 \times 10^{-3}}{1.27 \times 10^{-3}} = \mathbf{1003.14\Omega}$$

b) Small-Signal Equivalent Circuit shown in figure 8.

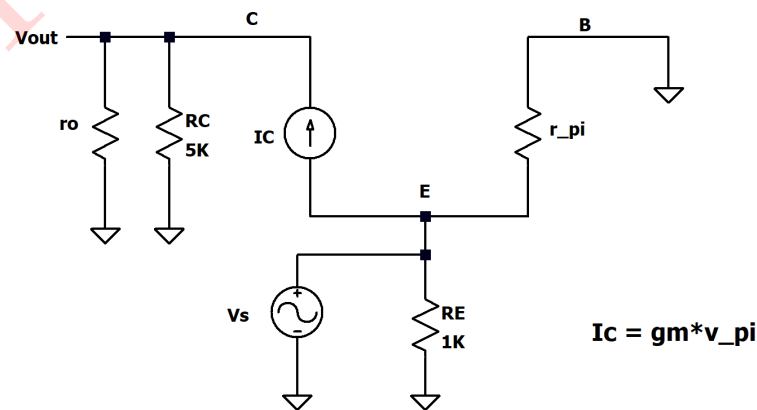


Figure 8: Small Signal Equivalent Circuit

c)  $A_V$  (Small Signal Voltage Gain)

$$\frac{V_{out}}{V_{in}} = A_V = g_m(R_C \parallel r_o) = 49 \times 10^{-3} \times (5 \times 10^3 \parallel 1 \times 10^6) = \mathbf{245}$$

d)  $Z_i$  (Input Impedance)

$$Z_i = \frac{1}{g_m} \parallel R_E = \frac{1}{49 \times 10^{-3}} \parallel 1 \times 10^3 = 20.408 \parallel 1000 = 20\Omega$$

e)  $Z_o$  (Output Impedance)

$$Z_o = R_C \parallel r_o = 1M \parallel 5k = 4975.12\Omega$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

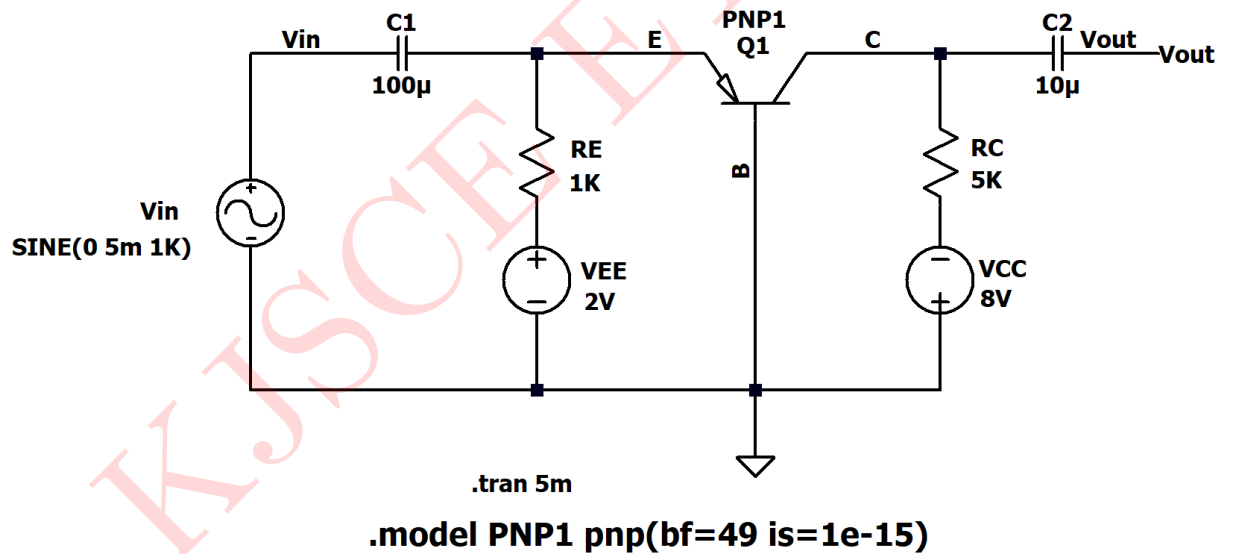


Figure 9: Circuit Schematic

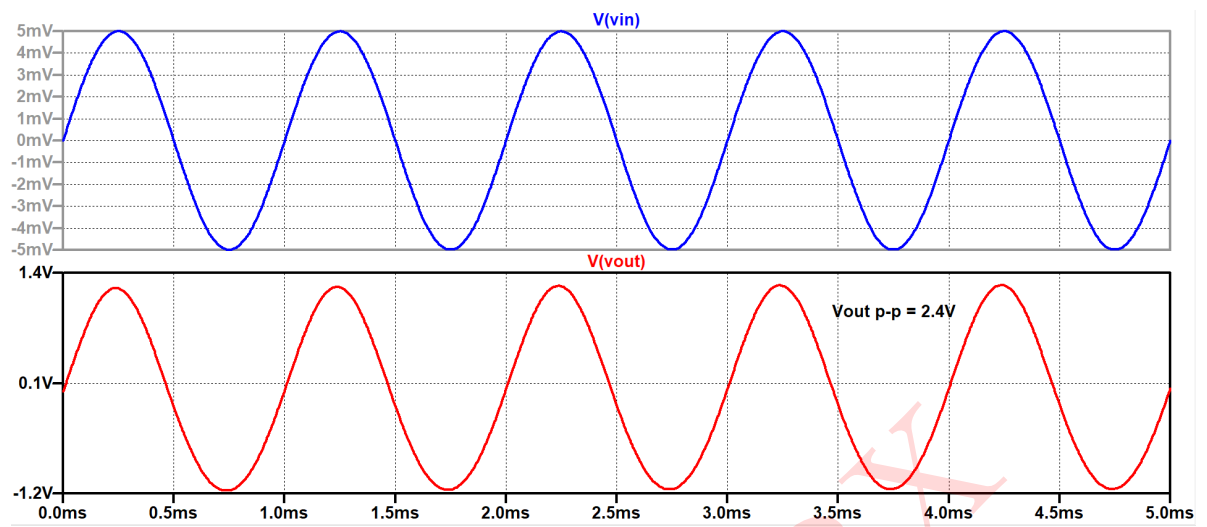


Figure 10: Input and Output Waveforms

**Comparison between Theoretical and Simulated values :-**

Parameter	Simulated	Theoretical
$I_{CQ}$	1.2mA	1.27mA
$A_V$	240	245

Table 2: Numerical 2



**Numerical 3:** The transistor in the circuit shown in figure 11 has  $\beta = 100$  and  $V_A = \infty$ . Determine: a)  $I_{CQ}$  and  $V_{ECQ}$  b) Small - Signal voltage gain  $A_V = V_{out}/V_{in}$

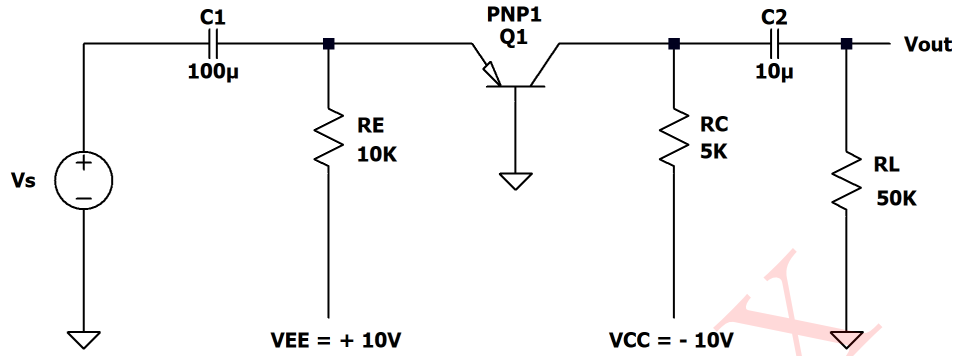


Figure 11: Circuit 1

**Solution:** The above circuit consists of a common base configuration employing pnp configuration

#### DC ANALYSIS:

By applying KVL to base - emitter loop,

$$V_{EE} - I_E R_E - V_{BE} = 0$$

$$I_E = \frac{V_{EE} - V_{BE}}{R_E} = \frac{10 - 0.7}{10 \times 10^3} = 0.93 \text{mA}$$

$$I_C = \frac{\beta}{\beta + 1} I_E = \frac{100}{101} \times 0.93 \times 10^{-3} = 0.92 \text{mA} \quad (\text{As } I_C = \beta I_B \text{ and } I_E = (\beta + 1) I_B)$$

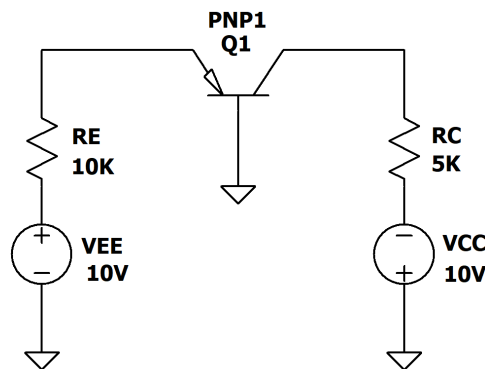


Figure 12: DC Equivalent Circuit

Applying KVL to the emitter - collector loop,

$$V_{EE} - I_E R_E - V_{EC} - I_C R_C + V_{CC} = 0$$

$$\text{As } V_{EC} = -V_{CE}$$

$$V_{CE} = I_E R_E + I_C R_C - V_{EE} - V_{CC}$$

$$= (0.93 \times 10^{-3})(10 \times 10^3) + (0.92 \times 10^{-3})(5 \times 10^3) - 10 - 10 = -\mathbf{6.1V}$$

$$V_{ECQ} = \mathbf{6.1V}$$

### AC ANALYSIS:

All the DC sources are open circuited and the capacitors are replaced by short circuit.

a) Small Signal Parameter:

$$g_m = \frac{I_{CQ}}{V_T}$$

$$\text{Here, } V_T = 26mV$$

$$g_m = \frac{0.92 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{35.38mA/V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_\pi = \frac{100 \times 26 \times 10^{-3}}{0.92 \times 10^{-3}} = \mathbf{2826\Omega}$$

b) Small-Signal Equivalent Circuit shown in figure 13.

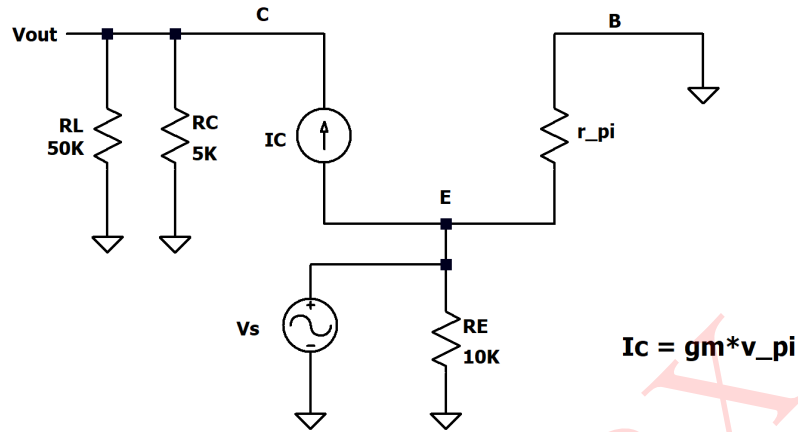


Figure 13: Small Signal Equivalent Circuit

c)  $A_V$  (Small Signal Voltage Gain)

$$\frac{V_{out}}{V_{in}} = A_V = g_m(R_C \parallel R_L) = 35.38 \times 10^{-3} \times (5 \times 10^3 \parallel 50 \times 10^3) = 160$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

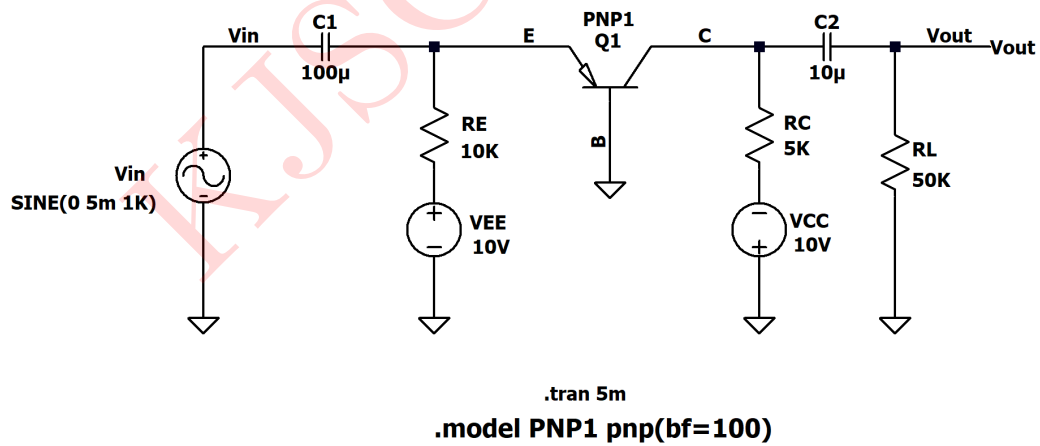


Figure 14: Circuit Schematic

The input and output waveforms are shown in figure 15.

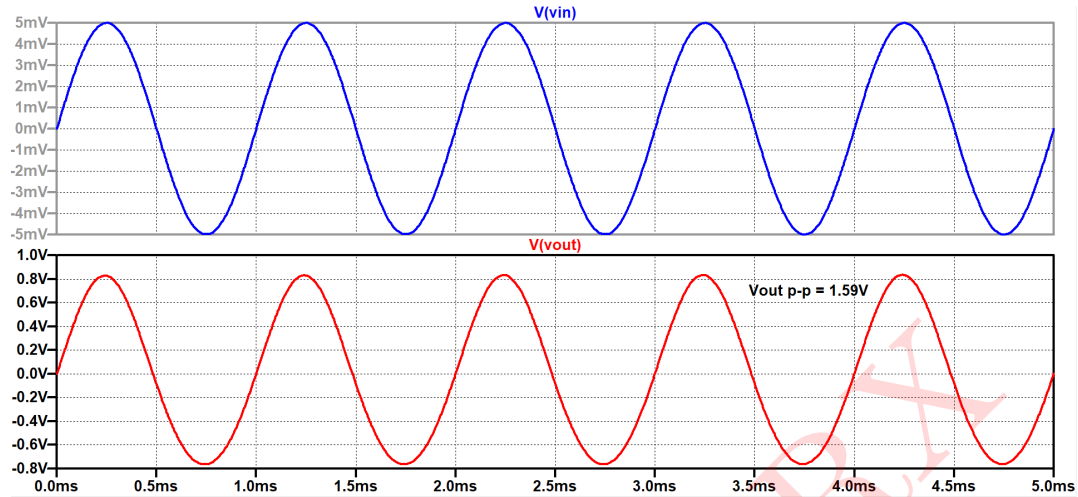


Figure 15: Input and Output Waveforms

**Comparison between Theoretical and Simulated values :-**

Parameter	Simulated	Theoretical
$I_{CQ}$	0.92mA	0.914mA
$V_{ECQ}$	6.1V	6.2V
$A_V$	160	159

Table 3: Numerical 3

\*\*\*\*\*