

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Cascade Amplifier Design**

**Design 1:**

Design a two stage RC coupled cascade amplifier to meet the following specifications,  
 $A_V \geq 130$ ,  $V_{ORMS} = 3V$ ,  $R_i \geq 1M\Omega$ . Select a suitable transistor from data-sheet.

**Solution:**

Step 1: For above requirements, we can use CS-CS self bias JFET amplifier

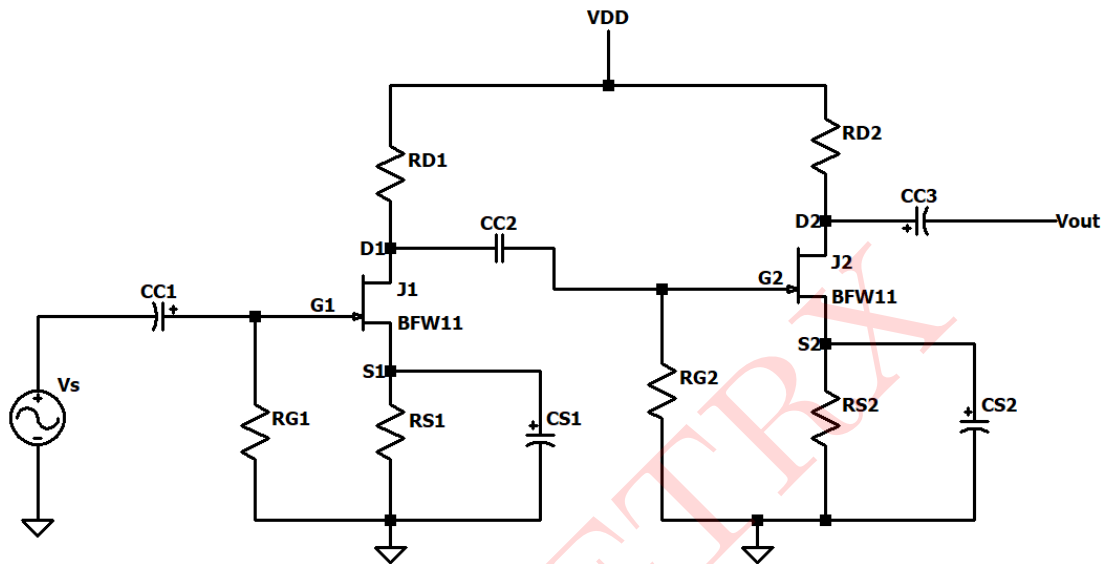


Figure 1: Circuit 1

JFET BFW-11 parameters

$$I_{DSS} = 7mA, V_P = -2.5V$$

$$r_d = 50k\Omega, g_{mo} = 5600\mu S$$

Step 2: Selection of voltage gain:

$$A_V \geq 130$$

$$\text{Let } A_V = 140$$

$$\text{Also, let } A_{V_1} = 0.6A_{V_2}$$

$$\therefore A_V = A_{V_1} A_{V_2}$$

$$\therefore 140 = 0.6A_{V_2}^2$$

$$A_{V_2} = \mathbf{15.275}$$

$$\therefore A_{V_1} = 0.6A_V$$

$$= 0.6 \times 15.275 = \mathbf{9.165}$$

$$\therefore \text{Voltage gain of 2nd stage}(A_{V_2}) \approx \mathbf{16}$$

$$\therefore \text{Voltage gain of 1st stage}(A_{V_1}) \approx \mathbf{9}$$

Design of 2nd stage:

Step 3: Calculation of Q-point( $V_{GSQ_2}$ ,  $I_{DQ_2}$ )

a) Zero-temperature drift

$$|V_P| - |V_{GS}| = 0.63$$

$$2.5 - |V_{GS}| = 0.63 \quad [V_P = -2.5V \text{ from datasheet(BFW-11)}]$$

$$|V_{GS}| = 2.5 - 0.63$$

$$|V_{GS}| = 1.87V$$

$$V_{GS} = -1.87V$$

$$\therefore V_{GSQ_2} = -\mathbf{1.87V}$$

In JFET,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 7mA \left[1 - \frac{(-1.87)}{(-2.5)}\right]^2 \quad [I_{DSS} = 7mA \text{ from datasheet(BFW-11)}]$$

$$I_D = 7mA \left[1 - \frac{1.87}{2.5}\right]^2$$

$$I_D = 7mA(0.252)^2$$

$$I_D = 7mA \times 0.063 = 0.4445mA$$

$$\therefore I_{DQ_2} = \mathbf{0.4445mA}$$

Calculation for  $R_{D_2}$ :

$$|A_{V_2}| = g_{m_2}(r_{d_2} \parallel R_{D_2})$$

$$\begin{aligned} g_m = g_{m_1} = g_{m_2} &= g_{m_o} \left(1 - \frac{V_{GSQ}}{V_P}\right) \\ &= 5600 \times 10^{-6} \left[1 - \frac{(-1.87)}{(-2.5)}\right] \\ &= 5600 \times 10^{-6} \left[1 - \frac{1.87}{2.5}\right] \\ &= 5600 \times 10^{-6} \times 0.252 = \mathbf{1.4112mA/V} \end{aligned}$$

$$r_d = r_{d_1} = r_{d_2} = \mathbf{50k\Omega}$$

$$\therefore |A_{V_2}| = g_{m_2}(r_{d_2} \parallel R_{D_2})$$

$$16 = 1.4112 \times 10^{-3}A/V(50k\Omega \parallel R_{D_2})$$

$$\frac{16}{1.4112 \times 10^{-3}A/V} = \frac{R_{D_2} \times 50k\Omega}{R_{D_2} + 50k\Omega}$$

$$11337.868\Omega = \frac{R_{D_2} \times 50k\Omega}{R_{D_2} + 50k\Omega}$$

$$11337.868(R_{D_2} + 50k\Omega) = R_{D_2}(50k\Omega)$$

$$11337.868R_{D_2} + 566893.424k\Omega = R_{D_2}(50k\Omega)$$

$$566893.424k\Omega = R_{D_2}(50 \times 10^3 - 11337.868)$$

$$566893.424k\Omega = R_{D_2}(38662.132)$$

$$R_{D_2} = \frac{566893.424k\Omega}{38662.132\Omega} = \mathbf{14.662k\Omega}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $R_{D_2}$ ,

Select  $R_{D_2} = \mathbf{15k\Omega_{(std)}}$ ,  $\mathbf{1/4W}$

Step 5: Calculation of  $R_{S_2}$ :

$$\therefore V_{GSQ_2} = -I_{DQ_2}R_{S_2}$$

$$\therefore -1.87V = -0.4445 \times 10^{-3} \times R_{S_2}$$

$$\therefore R_{S_2} = \frac{-1.87V}{-0.4445 \times 10^{-3}A} = \mathbf{4.2k\Omega}$$

$\therefore$  We have to select lower standard value(L.S.V) for  $R_{S_2}$ ,

Select  $R_{S_2} = \mathbf{3.9k\Omega_{(std)}}$ ,  $\mathbf{1/4W}$

Step 6: Calculation of  $R_{G_2}$ :

Let,  $R_{G_2} = 1.2M\Omega$ ,  $1/4W$

We select  $R_{G_2} = \mathbf{11.2M\Omega}$ ,  $\mathbf{1/4W}$  to prevent loading for first stage

Step 7: Calculation of  $V_{DD}$ :

 


Figure 2: D-S loop for JFET

Applying KVL to drain-source loop for JFET 2,

$$V_{DD} - I_{DQ_2}R_{D_2} - V_{DSQ_2} - I_{DQ_2}R_{S_2} = 0$$

$$\therefore V_{DD} = I_{DQ_2}(R_{D_2} + R_{S_2}) + V_{DSQ_2}$$

We know,

$$V_{DSQ_2} \geq 1.5 [ |V_P| + V_{o_{peak}} ]$$

The value is multiplied by 1.5 to take care of saturation voltages, variation in resistance, variation in supply voltage and device parameter variation

$$V_{DSQ_2} \geq 1.5 [ |V_P| + V_{o_{peak}} ]$$

$$V_{DSQ_2} \geq 1.5 [ 2.5V + \sqrt{2}V_{ORMS} ]$$

$$V_{DSQ_2} \geq 1.5 [ 2.5V + \sqrt{2} \times 3V ]$$

$$V_{DSQ_2} \geq 1.5 [ 2.5V + 4.24V ]$$

$$V_{DSQ_2} \geq 1.5 [ 6.74V ]$$

$$V_{DSQ_2} \geq \mathbf{10.11V}$$

$$\text{Let } V_{DSQ_2} \approx 10.2V$$

$$\begin{aligned} \because V_{DD} &= I_{DQ_2}(R_{D_2} + R_{S_2}) + V_{DSQ_2} \\ &= 0.4445 \times 10^{-3}(15k\Omega + 3.9k\Omega) + 10.2V \\ &= 0.4445 \times 10^{-3}(18.9k\Omega) + 10.2V \\ &= 0.4445 \times 10^{-3}(18.9 \times 10^{-3}\Omega) + 10.2V = \mathbf{18.6V} \end{aligned}$$

$$\text{Select } V_{DD} = \mathbf{20V}$$

Design of 1st stage:

Step 8: Selection of  $R_{D_1}$ :

$$|A_{V_1}| = g_{m_1}(r_{d_2} \parallel R_{D_1} \parallel R_{G_2})$$

$$\text{i.e } |A_{V_1}| = g_{m_1}(r_{d_2} \parallel R_{G_2} \parallel R_{D_1})$$

$$\therefore 9 = 1.4112mA/V(50k\Omega \parallel 1.2M\Omega \parallel R_{D_1})$$

$$9 = 1.4112mA/V \left( \frac{50k\Omega \times 1.2M\Omega}{50k\Omega + 1.2M\Omega} \parallel R_{D_1} \right)$$

$$9 = 1.4112mA/V (48k\Omega \parallel R_{D_1})$$

$$\frac{9}{1.4112mA/V} = 48k\Omega \parallel R_{D_1}$$

$$6.378k\Omega(48k\Omega + R_{D_1}) = (48k\Omega)(R_{D_1})$$

$$306.144k\Omega + (6.378k\Omega)(R_{D_1}) = (48k\Omega)(R_{D_1})$$

$$306.144k\Omega = R_{D_1}(48k\Omega - 6.378k\Omega)$$

$$306.144k\Omega = R_{D_1}(41.622k\Omega)$$

$$R_{D_1} = \frac{306.144k\Omega}{41.622k\Omega} = 7.355k\Omega$$

$\therefore$  We have to select higher standard value(H.S.V) for  $R_{D_1}$ ,

$$\text{Select } R_{D_1} = \mathbf{7.5k\Omega_{(std)}}, \mathbf{1/4W}$$

Step 9: Selection of  $R_{G_1}$ :

To avoid loading effect and fulfill the requirement of  $R_i \geq 1M\Omega$

$$\text{Select } R_{G_1} = \mathbf{1.5M\Omega_{(std)}}, \mathbf{1/4W}$$

Step 10: Selection of  $R_{S_1}$ :

$$\because V_{GSQ_1} = V_{GSQ_2}$$

$$\therefore V_{GSQ_1} = \mathbf{-1.87V}$$

$$\because V_{GSQ_1} = -I_{DQ}R_{S_1}$$

$$\therefore -1.87V = -0.4445 \times 10^{-3}A \times R_{S1}$$

$$R_{S1} = \frac{-1.87V}{-0.4445 \times 10^{-3}A} = \mathbf{4.206k\Omega}$$

$\therefore$  We have to select lower standard value(L.S.V) for  $R_{S1}$ ,

Select  $R_{S1} = \mathbf{3.9k\Omega, 1/4W}$

Step 11: Selection of coupling capacitors( $C_{C1}, C_{C2}, C_{C3}$ ):

a)  $C_{C1}$ :

$$C_{C1} = \frac{1}{2\pi R_{eq} f_L}$$

$$R_{eq} = R_{G1} = 1.5M\Omega$$

$$f_L = 20Hz \quad (\text{Since } f_L \text{ is not given, we assume audio frequency, } f_L=20Hz)$$

$$C_{C1} = \frac{1}{2\pi \times 1.5M\Omega \times 20Hz} = \mathbf{5.30 \times 10^{-9}F}$$

We have to select higher standard value(H.S.V) for  $C_{C1}$ ,

Select  $C_{C1} = \mathbf{5.6nF/50V}$

b)  $C_{C2}$ :

 


Figure 3: Low frequency equivalent circuit for  $C_{C2}$

$$C_{C2} = \frac{1}{2\pi R_{eq} f_L}$$

$$\begin{aligned} R_{eq} &= (r_{d1} \parallel R_{D1}) + R_{G2} \\ &= (50k\Omega \parallel 7.5k\Omega) + R_{G2} \\ &= \left( \frac{50k\Omega \times 7.5k\Omega}{50k\Omega + 7.5k\Omega} \right) + 1.2M\Omega \\ &= 6.52k\Omega + 1.2M\Omega = \mathbf{1.206M\Omega} \end{aligned}$$

$$C_{C2} = \frac{1}{2\pi \times 1.206M\Omega \times 20Hz} = \mathbf{6.601 \times 10^{-9}F}$$

We have to select higher standard value(H.S.V) for  $C_{C2}$ ,

Select  $C_{C2} = \mathbf{6.8nF/50V}$

c)  $C_{C_3}$ :

 


Figure 4: Low frequency equivalent circuit for  $C_{C_3}$

$$C_{C_3} = \frac{1}{2\pi R_{eq} f_L}$$

$$\begin{aligned} R_{eq} &= r_{d2} \parallel R_{D2} \\ &= 50k\Omega \parallel 15k\Omega \\ &= \frac{50k\Omega \times 15k\Omega}{50k\Omega + 15k\Omega} = \mathbf{11.538k\Omega} \end{aligned}$$

$$C_{C_3} = \frac{1}{2\pi \times 11.538k\Omega \times 20Hz} = \mathbf{0.690\mu F}$$

∴ We have to select higher standard value(H.S.V) for  $C_{C_3}$ ,

Select,  $C_{C_3} = \mathbf{1\mu F/50V}$

Step 12: Selection of bypass capacitors( $C_{S_1}$ ,  $C_{S_2}$ ):

Since  $g_{m1} = g_{m2} = g_m = 1.4112mA/V$  and  $R_{S_1} = R_{S_2} = 3.9k\Omega$

$$\therefore C_{S_1} = C_{S_2} = \frac{1}{2\pi R_{eq} f_L}$$

$$\begin{aligned} R_{eq} &= \frac{1}{g_m} \parallel R_S \\ &= \frac{1}{1.4112mA/V} \parallel 3.9k\Omega \\ &= 708.8\Omega \parallel 3.9k\Omega \\ &= \frac{708.8\Omega \times 3.9k\Omega}{708.8\Omega + 3.9k\Omega} = \mathbf{599.72\Omega} \end{aligned}$$

$$\therefore C_{S_1} = C_{S_2} = \frac{1}{2\pi \times 599.72\Omega \times 20Hz} = \mathbf{13.27\mu F}$$

∴ We have to select higher standard value(H.S.V) for  $C_{S_1}$  and  $C_{S_2}$ ,

Select,  $C_{S_1} = C_{S_2} = \mathbf{15\mu F/50V}$

Step 13: Complete Designed Circuit:

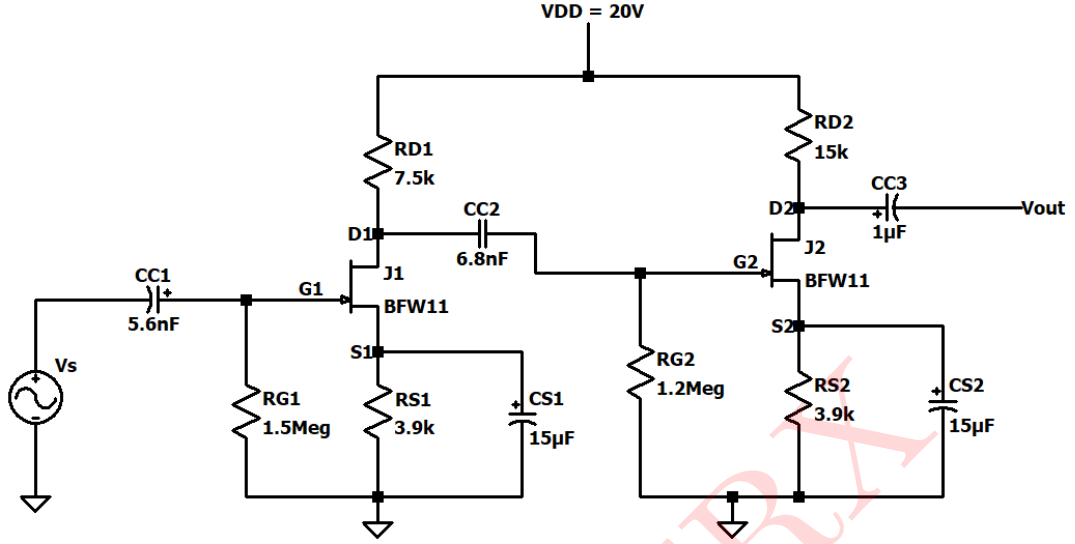


Figure 5: Complete Designed Circuit

Mid-frequency AC equivalent circuit:

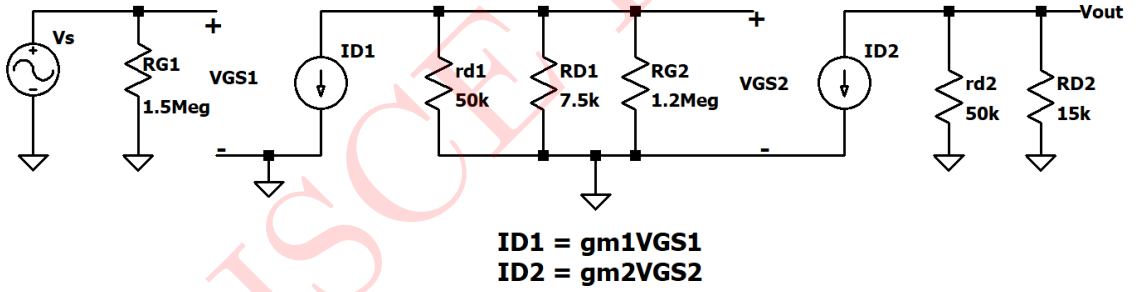


Figure 6: Mid-frequency AC equivalent circuit

Input impedance,

$$Z_i = R_{G1} = 1.5\text{M}\Omega$$

Output impedance,

$$\begin{aligned} Z_o &= r_{d2} \parallel R_{D2} \\ &= 50\text{k}\Omega \parallel 15\text{k}\Omega \\ &= \frac{50\text{k}\Omega \times 15\text{k}\Omega}{50\text{k}\Omega + 15\text{k}\Omega} = 11.53\text{k}\Omega \end{aligned}$$

$$\begin{aligned}
|A_{V_1}| &= g_m(r_d \parallel R_D \parallel R_{G_2}) \\
&= 1.4112\text{mA/V}(50\text{k}\Omega \parallel 7.5\text{k}\Omega \parallel 1.2\text{M}\Omega) \\
&= 1.4112\text{mA/V} \left( \frac{50\text{k}\Omega \times 7.5\text{k}\Omega}{50\text{k}\Omega + 7.5\text{k}\Omega} \parallel 1.2\text{M}\Omega \right) \\
&= 1.4112\text{mA/V}(6.52\text{k}\Omega \parallel 1.2\text{M}\Omega) \\
&= 1.4112\text{mA/V} \left( \frac{6.52\text{k}\Omega \times 1.2\text{M}\Omega}{6.52\text{k}\Omega + 1.2\text{M}\Omega} \right) \\
&= 1.4112\text{mA/V} \times 6.484\text{k}\Omega = \mathbf{9.15}
\end{aligned}$$

$$\begin{aligned}
|A_{V_2}| &= g_m(r_d \parallel R_{D_2}) \\
&= 1.4112\text{mA/V}(50\text{k}\Omega \parallel 15\text{k}\Omega) \\
&= 1.4112\text{mA/V} \left( \frac{50\text{k}\Omega \times 15\text{k}\Omega}{50\text{k}\Omega + 15\text{k}\Omega} \right) \\
&= 1.4112\text{mA/V} \times 11.53\text{k}\Omega = \mathbf{16.28}
\end{aligned}$$

$$\begin{aligned}
A_V &= A_{V_1} A_{V_2} \\
&= 9.15 \times 16.28 = \mathbf{148.99}
\end{aligned}$$

$\therefore$  Achieved gain  $A_V$  is 148.99 and designed gain is greater than 130

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

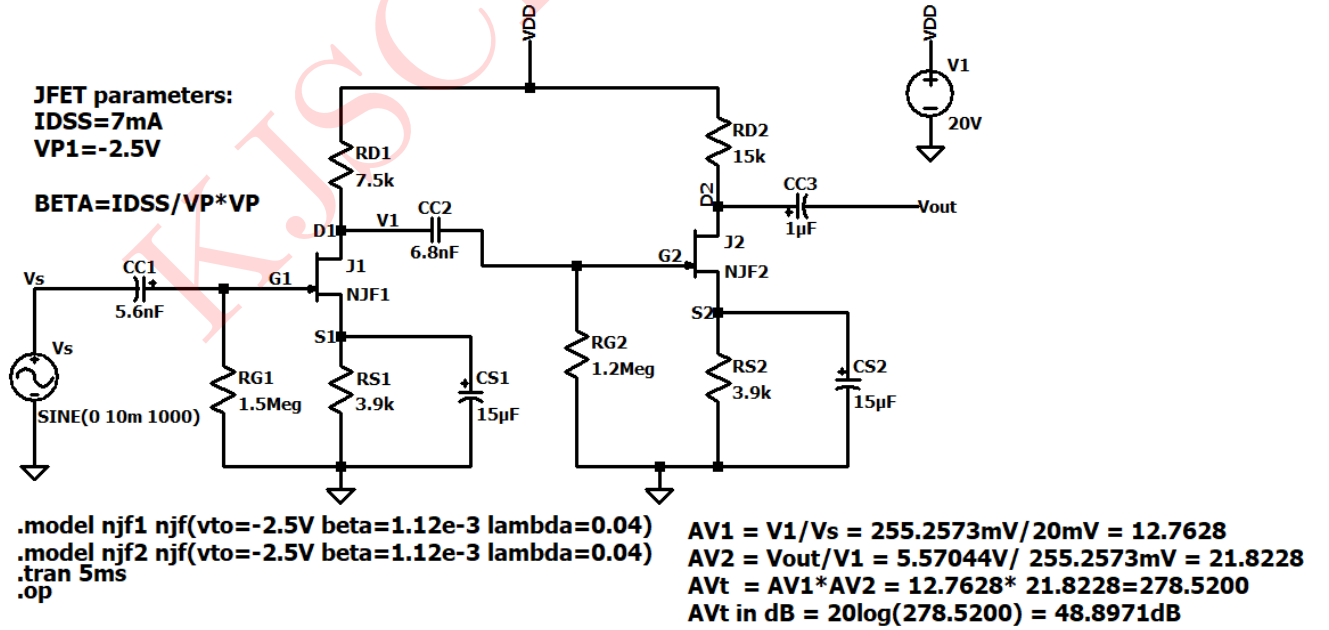


Figure 7: Circuit Schematic



 


Figure 8: Input and output waveforms for Stage 1 current gain

 


Figure 9: Input and output waveforms for Stage 2 current gain

**Comparison between theoretical and simulated values:**

Parameters	Theoretical values	Simulated values
1st stage DC parameters: $I_{DQ_1}, V_{GSQ_1}$	0.4445mA, -1.87V	0.5037mA, -1.9412V
2nd stage DC parameters: $I_{DQ_2}, V_{GSQ_2}$	0.4445mA, -1.87V	0.5037mA, -1.9412V
Voltage gain of 1st stage $A_{V_1}$	>9	12.7682
Voltage gain of 2nd stage $A_{V_2}$	>16	21.8228
Overall voltage gain $A_{V_T}$ in dB	>42.27dB	48.8971dB
Input impedance of 1st stage	1.5M $\Omega$	—
Output impedance of 2nd stage	11.53k $\Omega$	—

Table 1: Design 1

**Design 2:**

Design a two stage RC coupled cascade amplifier for following specifications,  
 $A_V \geq 600$ ,  $V_{CC} = 20V$ ,  $S \leq 10$ ,  $R_i \geq 1M\Omega$ . Select a suitable transistor from data-sheet.

**Solution:**

Above requirements can be fulfilled by CS-CE stage.

We select CS as 1st stage since  $R_i \geq 1M\Omega$

Step 1: Circuit diagram and selection of transistor

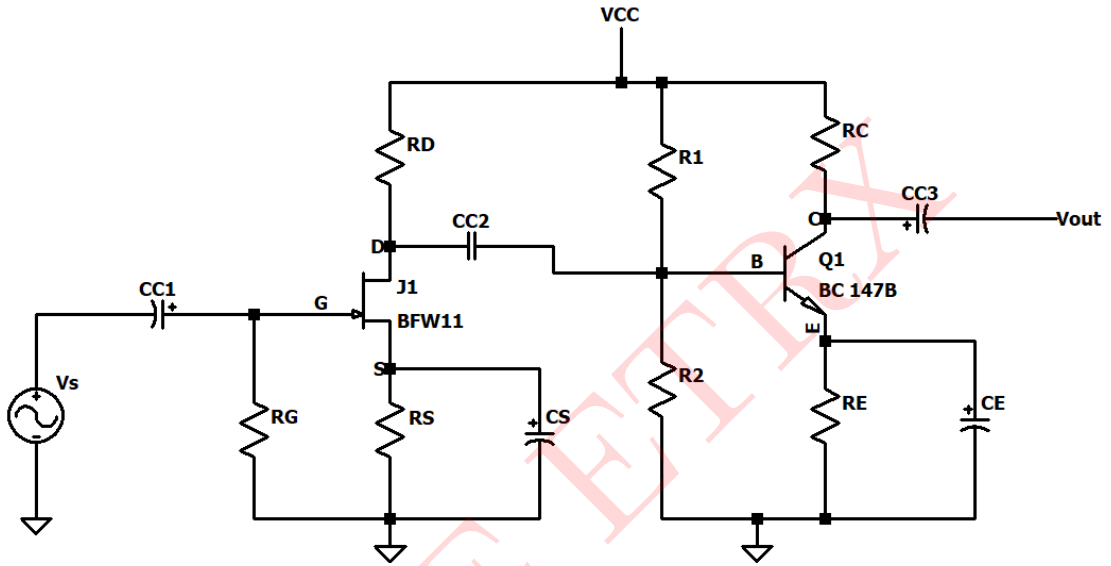


Figure 10: Circuit 2

Select BC 147B:  $h_{fc}(\text{typ}) = 330$ ;  $h_{FE}(\text{typ}) = 290 = \beta$ ;  $h_{ie} = 4.5k\Omega$ ;  $V_{CE}(\text{sat}) = 0.25V$

We select BC 147B because its  $h_{fc}(\text{typ})$  and  $h_{ie}$  is higher

Select BFW11:  $I_{DSS} = 7mA$ ;  $g_{m_o} = 5600\mu S$ ;  $V_P = -2.5V$ ;  $r_d = 50k\Omega$

Step 2: Selection of gains:

$$A_V \geq 600$$

Let  $A_{V_1} = 4$  (Since gain of JFET amplifier is less)

$$\therefore A_V = A_{V_1} A_{V_2}$$

$$\therefore 600 = 4 A_{V_2}$$

$$A_{V_2} = \mathbf{150}$$

$\therefore$  Voltage gain of 2nd stage( $A_{V_2}$ )= **150**

$\therefore$  Voltage gain of 1st stage( $A_{V_1}$ )= **4**

Design of 2nd stage:

Step 3: Selection of  $R_C$ :

$$|A_{V_2}| = \frac{hfe(typ)R_C}{h_{ie}}$$

$$150 = \frac{330 \times R_C}{4.5k\Omega}$$

$$R_C = \frac{650k\Omega}{330} = \mathbf{2.04k\Omega}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $R_C$ ,

Select  $R_C = \mathbf{2.2k\Omega}$ ,  $\mathbf{1/4W}$

Step 4: Selection of Q-point( $V_{CEQ}$ ,  $I_{CQ}$ ):

$$V_{CC} = 20V$$

$$\text{Let } V_{CEQ} = \frac{V_{CC}}{2} = 10V$$

$$\begin{aligned} V_{RE} &= 0.1V_{CC} \\ &= 0.1 \times 20 = \mathbf{2V} \end{aligned}$$

Applying KVL to collector-emitter loop of BJT,

 


Figure 11: C-E output loop for BJT

$$V_{CC} - V_{RC} - V_{CEQ} - V_{RE} = 0$$

$$\therefore V_{RC} = V_{CC} - V_{CEQ} - V_{RE}$$

$$\therefore V_{RC} = 20 - 10 - 2 = \mathbf{8V}$$

$$\therefore V_{RC} = I_{CQ}R_C$$

$$8V = I_{CQ}(2.2k\Omega)$$

$$I_B = \frac{I_{CQ}}{\beta}$$

$$I_B = \frac{3.6363mA}{290} = \mathbf{12.5389\mu A}$$

$$\begin{aligned}
I_E &= (\beta + 1)I_B \\
&= (290 + 1)(12.53\mu A) \\
&= (291)(12.53\mu A) = \mathbf{3.6462mA}
\end{aligned}$$

Step 5: Calculation of  $R_E$ :

$$\therefore V_{RE} = 2V$$

$$\therefore V_{RE} = I_{EQ}R_E$$

$$2V = 3.6462mA \times R_E$$

$$\therefore R_E = \frac{2V}{3.6462mA} = \mathbf{548.51\Omega}$$

$\therefore$  We have to select lower standard value(L.S.V) for  $R_E$ ,

Select  $R_E = \mathbf{510\Omega, 1/4W}$

Step 6: Selection of biasing resistors( $R_1, R_2$ ):

$$S \leq 10$$

$$\text{Let } S = 9$$

$$S = \frac{1 + 290}{1 + 290 \left[ \frac{R_E}{R_E + R_B} \right]}$$

$$9 = \frac{1 + 290}{1 + 290 \left[ \frac{510\Omega}{510\Omega + R_B} \right]}$$

$$9 = \frac{291}{\frac{510 + R_B + 147900}{510 + R_B}}$$

$$\frac{9}{510 + R_B} = \frac{291}{R_B + 148410}$$

$$9(R_B + 148410) = 291(510 + R_B)$$

$$9R_B + 1335690 = 148410 + 291R_B$$

$$1187280 = R_B(282)$$

$$R_B = \frac{1187280}{282} = \mathbf{4.210k\Omega}$$

$$R_B = R_1 \parallel R_2$$

$$R_1 \parallel R_2 = 4.210k\Omega$$

$$\frac{R_1 \times R_2}{R_1 + R_2} = 4.210k\Omega \quad \dots(1)$$

$$V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} \quad \dots(2)$$

Applying KVL to base-emitter loop of BJT,

 


Figure 12: Thevenin's equivalent circuit for BJT

$$V_{th} - I_{BQ}R_B - V_{BE} - I_{EQ}R_E = 0$$

$$\therefore V_{th} = \frac{I_{CQ}}{\beta} R_B + V_{BE} + I_{EQ}R_E \quad (\because I_{CQ} = \beta I_{BQ}, I_{CQ} \approx I_{EQ})$$

$$\therefore V_{th} = \frac{3.6363mA}{290} \times 4.210k\Omega + 0.7 + 3.6363mA \times 510\Omega$$

$$\therefore V_{th} = 0.05V + 0.7 + 1.85V = \mathbf{2.6V}$$

$$\therefore V_B = V_{th} = \mathbf{2.6V}$$

$$\therefore V_{BE} = 0.7$$

$$\therefore V_B - V_E = 0.7V$$

$$\therefore 2.6V - V_E = 0.7V$$

$$\therefore V_E = 2.6 - 0.7 = \mathbf{1.9V}$$

From (2),

$$V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC}$$

$$2.6V = \frac{R_2}{R_1 + R_2} \times 20V$$

$$\frac{R_2}{R_1 + R_2} = \frac{2.6V}{20V}$$

$$\frac{R_2}{R_1 + R_2} = 0.13 \quad \dots(3)$$

Put (3) in (1), we get

$$R_1 \times 0.13 = 4.210k\Omega$$

$$R_1 = \frac{4.210k\Omega}{0.13} = \mathbf{32.38k\Omega}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $R_1$ ,

Select  $R_1 = \mathbf{33k\Omega, 1/4W}$

From (3),

$$\frac{R_2}{R_1 + R_2} = 0.13$$

$$\therefore \frac{R_2}{33k\Omega + R_2} = 0.13$$

$$R_2 = 0.13(33k\Omega + R_2)$$

$$R_2 = 4.29k\Omega + 0.13R_2$$

$$0.87R_2 = 4.29k\Omega$$

$$R_2 = \frac{4.29k\Omega}{0.87} = \mathbf{4.931k\Omega}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $R_2$ ,

Select  $R_2 = \mathbf{5.1k\Omega, 1/4W}$

Design of 1st stage:

Step 7: Selection of Q-point ( $I_{DQ}, V_{GSQ}$ ):

Using mid-point biasing,

$$I_{DQ} = \frac{I_{DSS}}{2} = \frac{7mA}{2} \approx \mathbf{3.5mA}$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GSQ}}{V_P}\right)^2$$

$$\begin{aligned} V_{GSQ} &= V_P \left(1 - \sqrt{\frac{I_{DQ}}{I_{DSS}}}\right) \\ &= -2.5 \left(1 - \sqrt{\frac{3.5}{7}}\right) = \mathbf{-0.732V} \end{aligned}$$

$$\begin{aligned} \therefore g_{m1} &= g_{m0} \left(1 - \frac{V_{GSQ}}{V_P}\right) \\ &= 5600 \times 10^{-6} \left[1 - \frac{(-0.732)}{(-2.5)}\right] \\ &= 5600 \times 10^{-6} \left[1 - \frac{0.732}{2.5}\right] \\ &= 5600 \times 10^{-6} (0.7072) = \mathbf{3.96mA/V} \end{aligned}$$

Step 8: Selection of  $R_D$ :

$$\begin{aligned} |A_{V2}| &= \frac{hfc(typ) \times R_C}{hie} \\ &= \frac{330 \times 2.2k\Omega}{4.5k\Omega} = \mathbf{161.33} \end{aligned}$$

$$\begin{aligned} |A_{V1}| &= \frac{A_V}{|A_{V2}|} \\ &= \frac{600}{161.33} = \mathbf{3.71} \end{aligned}$$

Let  $|A_{V1}| = 3.5$

$$|A_{V1}| = g_{m1} [R_D \parallel r_d \parallel R_1 \parallel R_2 \parallel hie]$$

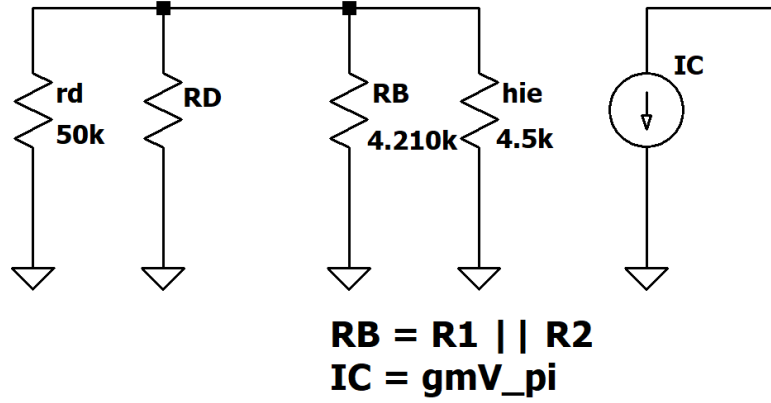


Figure 13: Small signal equivalent circuit for selection of  $R_D$

$$\begin{aligned}
 R_{L_1} &= r_d \parallel R_1 \parallel R_2 \parallel h_{ie} \\
 &= 50k\Omega \parallel 33k\Omega \parallel 5.1k\Omega \parallel 4.5k\Omega \\
 &= \left( \frac{50k\Omega \times 33k\Omega}{50k\Omega + 33k\Omega} \right) \parallel \left( \frac{5.1k\Omega \times 4.5k\Omega}{5.1k\Omega + 4.5k\Omega} \right) \\
 &= 19.87k\Omega \parallel 2.39k\Omega \\
 &= \frac{19.87k \times 2.39k\Omega}{19.87k\Omega + 2.39k\Omega} = \mathbf{2.13k\Omega}
 \end{aligned}$$

$$\begin{aligned}
 |A_{V_1}| &= g_{m_1} [R_D \parallel 2.13k\Omega] \\
 3.5 &= 3.96 \times 10^{-3} A/V \left( \frac{R_D \times 2.13k\Omega}{R_D + 2.13k\Omega} \right) \\
 883.838 &= \frac{R_D \times 2.13k\Omega}{R_D + 2.13k\Omega} \\
 883.838(R_D + 2.13k\Omega) &= R_D(2.13k\Omega) \\
 883.838R_D + 1885.57k\Omega &= R_D(2.13k\Omega) \\
 1885.57k\Omega &= R_D(2.13k\Omega - 883.838) \\
 R_D &= \frac{1885.57k\Omega}{1246.16k\Omega} = \mathbf{1.513k\Omega}
 \end{aligned}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $R_D$ ,  
Select  $R_D = \mathbf{1.8k\Omega, 1/4W}$

Step 9: Selection of  $R_S$ :

$$\begin{aligned}
 \therefore V_{GSQ} &= I_{DQ} \times R_S \\
 -0.732 &= -3.5mA \times R_S \\
 \therefore R_S &= \frac{-0.732V}{3.5mA} = \mathbf{209.14\Omega}
 \end{aligned}$$

$\therefore$  We have to select lower standard value(L.S.V) for  $R_S$ ,  
Select  $R_S = \mathbf{180\Omega, 1/4W}$

Step 10: Selection of  $R_G$ :

Let  $R_G = \mathbf{1.2M\Omega, 1/4W}$



Since  $R_i \geq 1M\Omega$  is required and to prevent loading we take  $R_G = 1.2M\Omega$

Step 11: Selection of coupling capacitors( $C_{C_1}$ ,  $C_{C_2}$ ,  $C_{C_3}$ ):

 


Figure 14: Low frequency equivalent circuit for  $C_{C_1}$

Since  $f_L$  is not given, we consider audio frequency,  $f_L = 20Hz$

a)  $C_{C_1}$ :

$$C_{C_1} = \frac{1}{2\pi R_{eq} f_L}$$

$$R_{eq} = R_G = 1.2M\Omega$$

$$C_{C_1} = \frac{1}{2\pi \times 1.2M\Omega \times 20Hz} = \mathbf{6.63nF}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $C_{C_1}$ ,

Select  $C_{C_1} = \mathbf{6.8nF/50V}$

b)  $C_{C_2}$ :

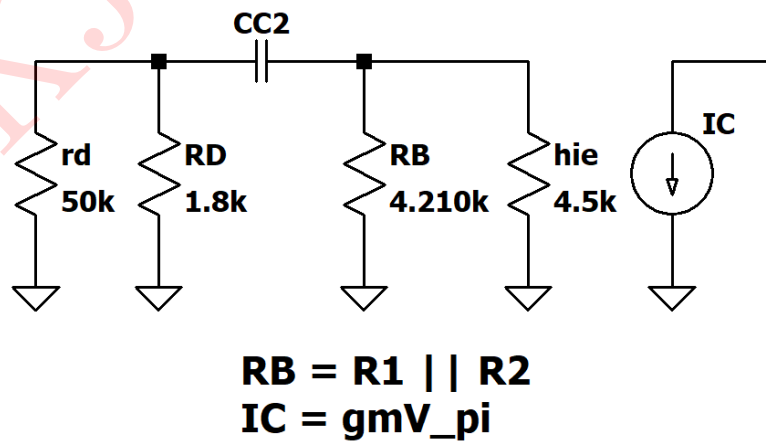


Figure 15: Low frequency equivalent circuit for  $C_{C_2}$

$$\begin{aligned}
C_{C_2} &= \frac{1}{2\pi R_{eq} f_L} \\
R_{eq} &= (r_d \parallel R_D) + R_1 \parallel R_2 \parallel h_{ie} \\
&= (50k\Omega \parallel 1.8k\Omega) + 33k\Omega \parallel 5.1k\Omega \parallel 4.5k\Omega \\
&= \left( \frac{50k\Omega \times 1.8k\Omega}{50k\Omega + 1.8k\Omega} \right) + 33k\Omega \parallel \left( \frac{5.1k\Omega \times 4.5k\Omega}{5.1k\Omega + 4.5k\Omega} \right) \\
&= 1.73k\Omega + 33k\Omega \parallel 2.39k\Omega \\
&= 1.73k\Omega + \frac{33k\Omega \times 2.39k\Omega}{33k\Omega + 2.39k\Omega} \\
&= 1.73k\Omega + 2.22k\Omega = \mathbf{3.95k\Omega}
\end{aligned}$$

$$C_{C_2} = \frac{1}{2\pi \times 3.95k\Omega \times 20Hz} = \mathbf{2.015\mu F}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $C_{C_2}$ ,

Select  $C_{C_2} = \mathbf{2.2\mu F/50V}$

c)  $C_{C_3}$ :

 


Figure 16: Low frequency equivalent circuit for  $C_{C_3}$

$$C_{C_3} = \frac{1}{2\pi R_{eq} f_L}$$

$$R_{eq} = R_C = 2.2k\Omega$$

$$C_{C_3} = \frac{1}{2\pi \times 2.2k\Omega \times 20Hz} = \mathbf{3.61\mu F}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $C_{C_3}$ ,

Select,  $C_{C_3} = \mathbf{3.9\mu F/50V}$

Step 12: Selection of bypass capacitors:

a)  $C_S$ :

$$\begin{aligned}C_S &= \frac{1}{2\pi R_{eq} f_L} \\R_{eq} &= \frac{1}{g_m} \parallel R_S \\&= \frac{1}{3.96 \times 10^{-3}} \parallel 180\Omega \\&= 252.52\Omega \parallel 180\Omega \\&= \frac{252.52 \times 180}{252.52 + 180} = \mathbf{105.09\Omega}\end{aligned}$$

$$\therefore C_S = \frac{1}{2\pi \times 105.09\Omega \times 20Hz} = \mathbf{75.72\mu F}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $C_S$ ,

Select,  $C_S = \mathbf{32\mu F/50V}$

a)  $C_E$ :

$$X_{CE} = 0.1R_E \quad (\text{ensures complete bypass of } R_E)$$

$$\frac{1}{2\pi f_L C_E} = 0.1R_E$$

$$\begin{aligned}C_E &= \frac{1}{2\pi f_L \times 0.1R_E} \\&= \frac{1}{2\pi \times 20 \times 0.1 \times 510\Omega} = \mathbf{156.11\mu F}\end{aligned}$$

$\therefore$  We have to select higher standard value(H.S.V) for  $C_E$ ,

Select,  $C_E = \mathbf{180\mu F/50V}$

Step 13: Complete Designed Circuit:

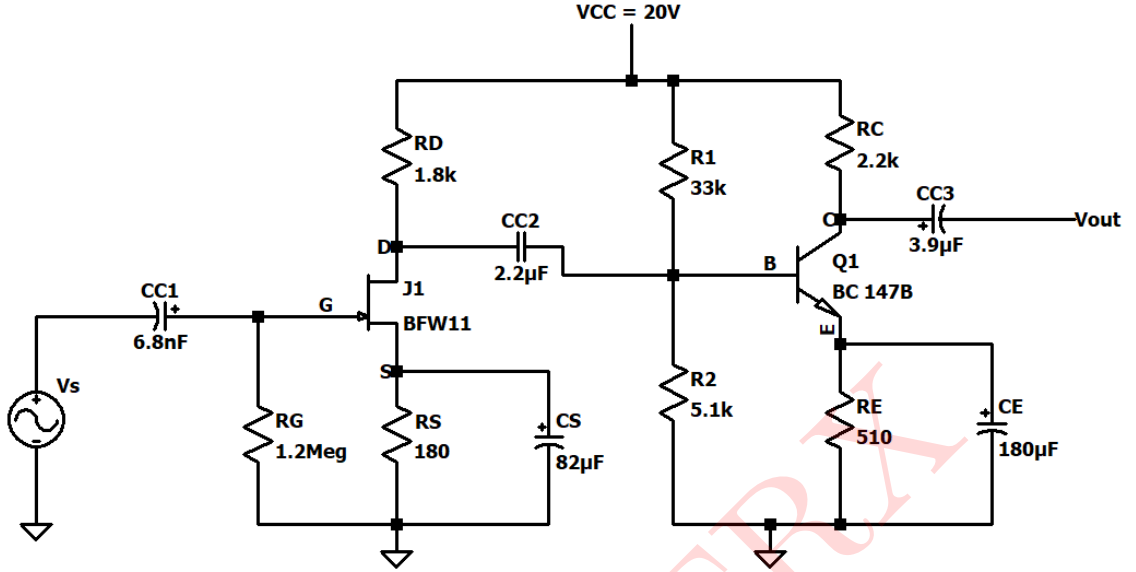


Figure 17: Complete Designed Circuit

Mid-frequency AC equivalent circuit:

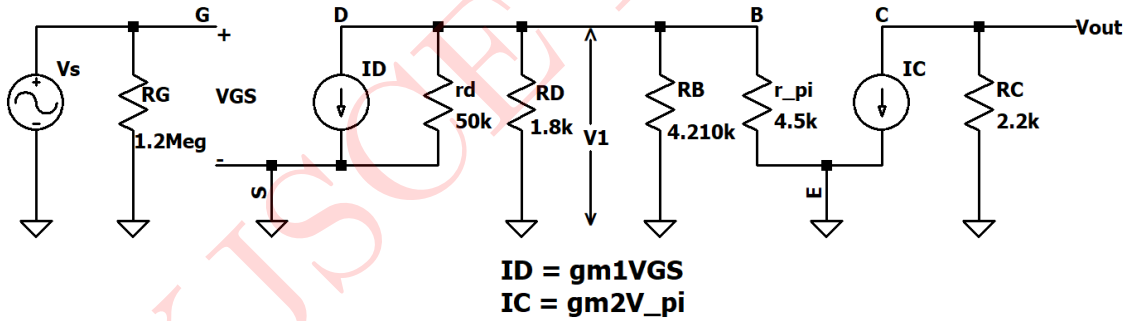


Figure 18: Mid-frequency AC equivalent circuit

Input impedance of 1st stage,

$$Z_i = R_G = 1.2\text{M}\Omega$$

Output impedance of 2nd stage,

$$Z_o = R_C = 2.2\text{k}\Omega$$

$$\begin{aligned} |A_{V_1}| &= g_{m_1}(r_d \parallel R_D \parallel R_B \parallel r_{\pi}) \\ &= 3.96\text{mA/V}(50\text{k}\Omega \parallel 1.8\text{k}\Omega \parallel 4.210\text{k}\Omega \parallel 4.5\text{k}\Omega) \\ &= 3.96\text{mA/V} \left( \frac{50\text{k}\Omega \times 7.5\text{k}\Omega}{50\text{k}\Omega + 7.5\text{k}\Omega} \parallel \frac{4.210\text{k}\Omega \times 4.5\text{k}\Omega}{4.210\text{k}\Omega + 4.5\text{k}\Omega} \right) \\ &= 3.96\text{mA/V}(1.73\text{k}\Omega \parallel 2.17\text{k}\Omega) \\ &= 3.96\text{mA/V} \left( \frac{1.73\text{k}\Omega \times 2.17\text{k}\Omega}{1.73\text{k}\Omega + 2.17\text{k}\Omega} \right) \\ &= 1.4112\text{mA/V} \times 0.96\text{k}\Omega = 3.811 \end{aligned}$$

$$|A_{V_2}| = g_{m_2}(R_C)$$

$$= 1.39.85mA/V(2.2k\Omega) = \mathbf{307.686}$$

$$A_{V_t} = A_{V_1}A_{V_2}$$

$$= 3.811 \times 307.686 = \mathbf{1172.594}$$

$\therefore$  Achieved gain  $A_{V_t}$  is 148.99 and designed gain is greater than 600

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

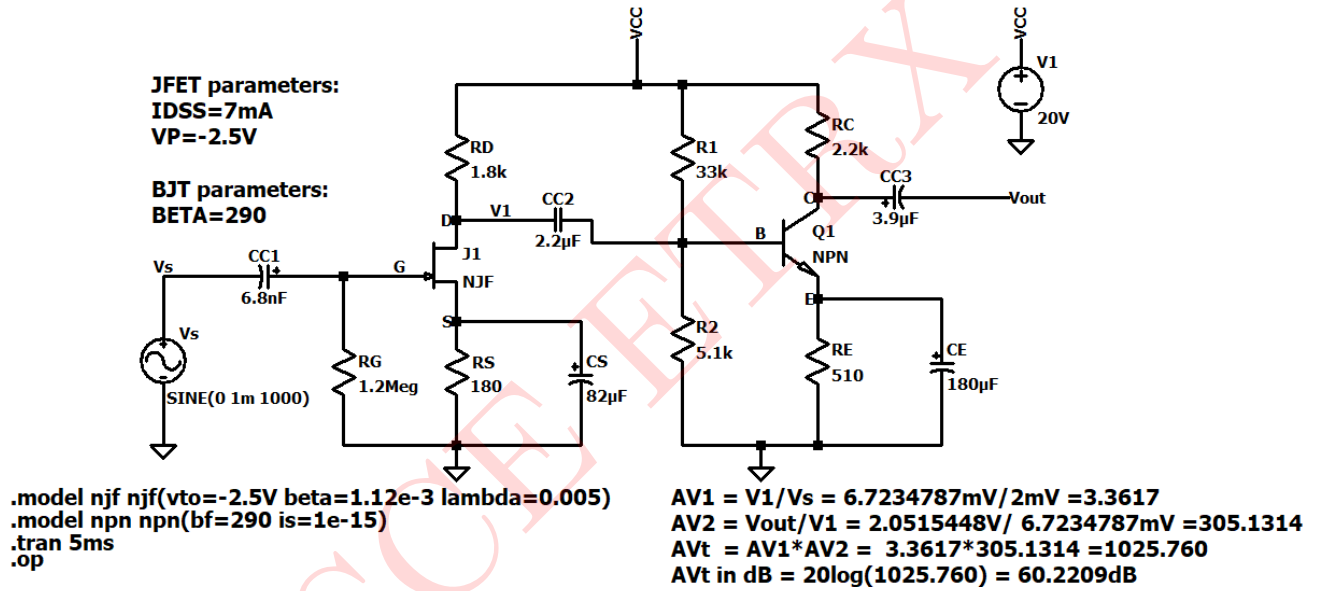


Figure 19: Circuit Schematic

 


Figure 20: Input and output waveforms for Stage 1 voltage gain

 


Figure 21: Input and output waveforms for Stage 2 voltage gain

#### Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
1st stage DC parameters: $I_{DQ}$ , $V_{GSQ}$	3.5mA, -0.732V	3.8685mA, -0.69633V
2nd stage DC parameters: $I_B$ , $I_C$ , $I_E$ , $V_E$ , $V_B$	12.5389 $\mu$ A, 3.6363mA, 3.6462mA, 1.9V, 2.6V	12.6216 $\mu$ A, 3.6602mA, 3.6728mA, 1.8731V, 2.6214V
Voltage gain of 1st stage $ A_{V1} $	3.5	3.3617
Voltage gain of 2nd stage $ A_{V2} $	161.33	305.1314
Overall voltage gain $A_{VT}$ in dB	55.56dB	60.220dB
Input impedance of 1st stage	1.2M $\Omega$	—
Output impedance of 2nd stage	2.2k $\Omega$	—

Table 2: Design 2

\*\*\*\*\*