

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Design of single-stage Amplifier

Design 1

Design a single stage RC coupled JFET amplifier for the following $V_o = 2.5V$, $f_L \leq 20Hz$, $|A_V| \geq 10$. Calculate A_V , Z_i & Z_o of the amplifier. Select suitable transistor from datasheet. Use Mid Point Biasing technique.

Solution:

1) Data:

$$|A_V| \geq 10, V_o = 2.5V, f_L \leq 20Hz$$

2) Selection of JFET:

We select N-channel JFET BFW 11 from the data sheet with the following specifications:

$$V_P = -2.5V, r_d = 50\Omega, I_{DSS} = 7mA \text{ \& } g_{mo} = 5600\mu S$$

3) Selection of biasing network

We select self bias circuit for our design

 


Figure 1: Circuit for Design 1

4) Selection of Q-Point:

i) Calculation of I_D

$$\text{For mid point biasing, } I_D = \frac{I_{DSS}}{2}$$

$$\text{i.e. } I_D = \frac{7mA}{2}$$

$$\therefore I_D = 3.5mA$$

ii) Calculation of V_{GS}

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\text{i.e. } V_{GS} = V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) = -2.5 \left(1 - \sqrt{\frac{3.5}{7}} \right)$$

$$V_{GS} = -0.732V$$

iii) Calculation of g_m

$$g_m = g_{mo} \left(1 - \frac{V_{GS}}{V_P} \right) = 5600 \times 10^{-6} \left(1 - \frac{(-0.732)}{(-2.5)} \right)$$

$$\therefore g_m = 3.96mS$$

5) Calculation of R_S :

For self-bias,

$$V_{GS} = -I_D R_S$$

$$R_S = \frac{-V_{GS}}{I_D} = \frac{-(-0.732)}{3.5mA}$$

$$\therefore R_S = 209\Omega$$

Select $R_S = 220\Omega_{(std)}, 1/4W.....(HSV)$

6) Selection of R_D :

$$A_V = -g_m (r_d \parallel R_D)$$

$$-10 = -3.96 \times 10^{-3} (50k \parallel R_D) = -3.96 \times 10^{-3} \left(\frac{50k\Omega \times R_D}{50k\Omega + R_D} \right)$$

Solving the above equation we get,

$$\therefore R_D = 2.67k\Omega$$

Select $R_D = 2.7k\Omega_{(std)}, 1/4W.....(HSV)$

7) Selection of R_G :

Select $R_G = 1M\Omega_{(std)}, 1/4W$

8) Selection of V_{DD} :

$$V_{DS} \geq V_{o_{peak}} + |V_P| \dots\dots (\text{Condition for undistorted output})$$

$$V_{DS} = 1.5(V_{o_{peak}} + |V_P|)$$

$$V_{DS} = 1.5(V_{o_{peak}} + 2.5)$$

The value is multiplied by 1.5 to take care of saturation voltages, tolerance in resistance value, variation in supply voltage and device parameter variation.

$$V_{rms} = 2.5V$$

$$\therefore V_{o_{peak}} = 2.5\sqrt{2}$$

i.e. $V_{DS} = 1.5(2.5\sqrt{2} + 2.5) = 9.045V$

Select $V_{DS} = 9V$

 


Figure 2: JFET Circuit D-S loop

Applying KVL to the D-S loop shown in figure 2 we get,

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$V_{DD} = V_{DS} + I_D (R_D + R_S)$$

$$V_{DD} = 9 + 3.5 \times 10^{-3} (2.7k + 220)$$

$$\therefore V_{DD} = 19.22V$$

Select $V_{DD} = 20V$

9) Selection of C_S :

$$f_L = 20Hz$$

$$X_{C_S} \leq 0.1R_S$$

$$\text{i.e. } \frac{1}{2\pi f_L C_S} \leq 0.1R_S$$

$$\text{i.e. } C_S \geq \frac{1}{2\pi f_L \times 0.1R_S} \geq \frac{1}{2\pi \times 20 \times 0.1 \times 220}$$

$$\therefore C_S \geq 361.715\mu F$$

Select $C_S = 390\mu F/25V$(H.S.V)

10) Selection of C_{C1} :

 


Figure 3: JFET Small Signal Equivalent Input Circuit

$$C_{C1} = \frac{1}{2\pi f_{L_{CC1}} R_{eq}}$$

$$f_{C_{C1}} = f_L = 20Hz$$

$$R_{eq} = R_G = 1M\Omega$$

$$C_{C1} = \frac{1}{2\pi \times 20 \times 1M\Omega} = 7.957nF$$

Select $C_{C1} = 8.2nF/25V....(H.S.V)$

11) Selection of C_{C2} :

 


Figure 4: JFET Small Signal Equivalent Output Circuit

$$C_{C2} = \frac{1}{2\pi f_{L_{CC2}} R_{eq}}$$

$$f_{L_{CC2}} = f_L = 20Hz$$

$$R_{eq} = r_d || R_D + R_L$$

If R_L is not given,

Select $R_L = R_i(\text{nextstage})$

$$R_L = R_G = 1M\Omega$$

$$R_{eq} = 50k || 2.7k + 1M\Omega$$

$$R_{eq} = 2.562k + 1M\Omega = 1.00256M\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 20 \times 1.00256M\Omega}$$

$$C_{C2} = 7.937nF$$

Select $C_{C2} = 8.2nF/25V \dots (H.S.V)$

12) Designed circuit:

 


Figure 5: Designed JFET Amplifier Circuit using Mid-Point Biasing Technique

AC Analysis:

The small signal equivalent circuit is shown in figure 6

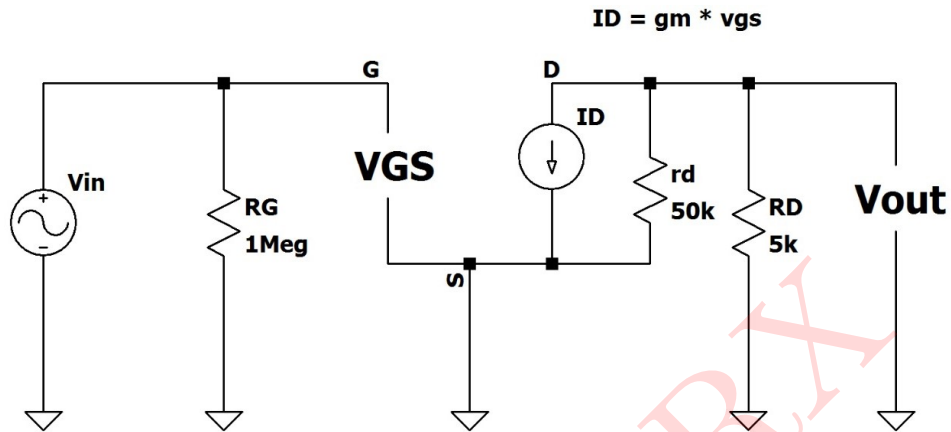


Figure 6: Small Signal Equivalent Circuit

Calculation of voltage gain (A_V)

$$A_V = -g_m(R_D \parallel r_d) = -3.96 \times 10^{-3} \times (2.7k \parallel 50k)$$

$$\therefore A_V = -10.15$$

Calculation of Z_i & Z_o

From figure 2 we get,

$$Z_i = R_G$$

$$Z_i = 1M\Omega$$

$$Z_o = r_d \parallel R_D = 50k \parallel 2.7k$$

$$Z_o = 2.56k\Omega$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

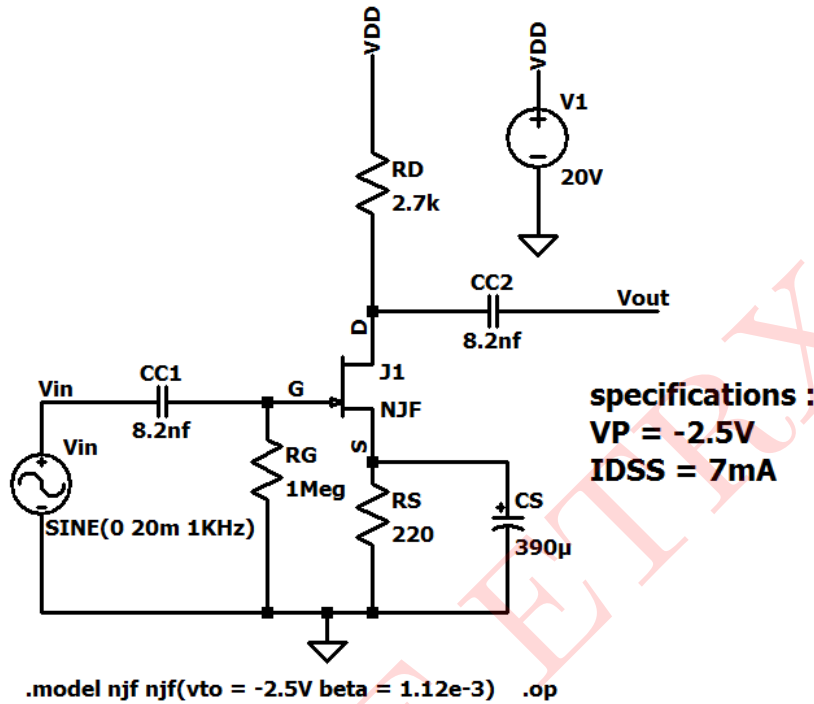


Figure 7: Circuit Schematic: Results

The input and output waveforms are shown in figure 4

 


Figure 8: Input and Output Waveforms

Comparison between theoretical and simulated values is given below:

Parameters	Simulated Values	Theoretical Values
I_{DQ}	$3.4mA$	$3.5mA$
A_V	> -10	-10.15

Table 1: Design 1

KJSCE ETRX