

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**DC CIRCUITS**

**Numerical 1:**

Find the voltage of point A w.r.t point B in the Figure 1. Is it positive w.r.t B?

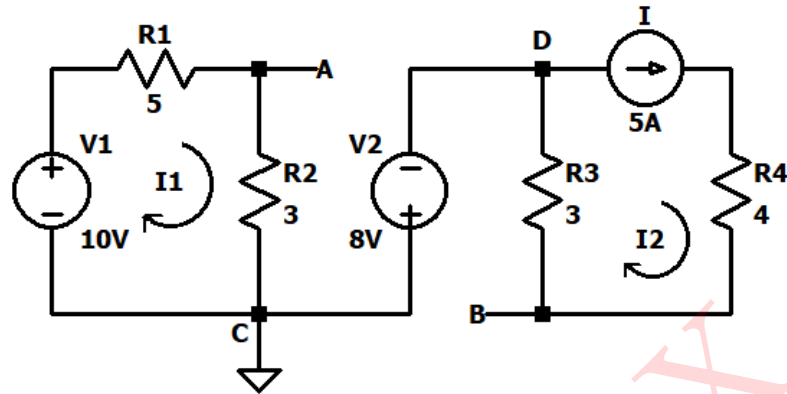


Figure 1: Circuit 1

**Solution:**

In the circuit 1,

For loop 1;

$$I_1 = \frac{V_1}{R_1 + R_2} = \frac{10}{5 + 3} = 1.25A \quad \dots(\text{By Ohm's Law})$$

For loop 2;

$$I_2 = I = 5A \quad \dots(\text{From circuit 1})$$

Applying KVL to the path from A to B,

$$V_A - 3I_1 - 8 + 3I_2 - V_B = 0$$

$$V_A - 3 \times 1.25 - 8 + 3 \times 5 - V_B = 0$$

$$V_A - V_B = -3.25V$$

$$\therefore V_{AB} = -3.25V$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

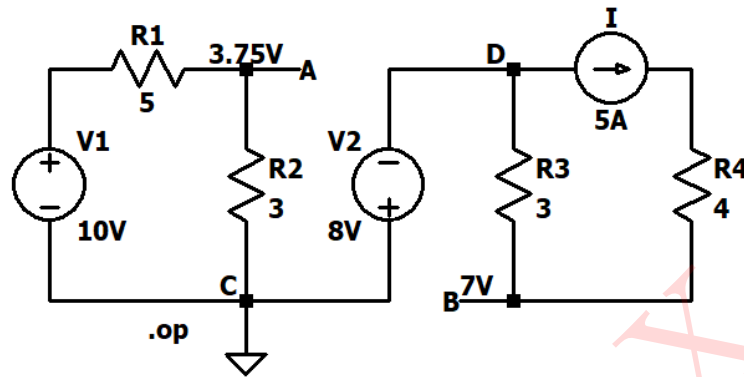


Figure 2: Circuit Schematic

Simulated results are shown in Figure 3.

```
* C:\Users\lenovo\Desktop\LTspiceXVII\sanika_week1_day1_circuit1.asc
--- Operating Point ---
V(a) :          3.75      voltage
V(n002) :        -8      voltage
V(b) :          7       voltage
V(n003) :        27      voltage
V(n001) :        10      voltage
I(I) :          5       device_current
I(R1) :        -1.25     device_current
I(R4) :          5       device_current
I(R3) :         -5       device_current
I(R2) :          1.25     device_current
I(V2) :       -4.44089e-016 device_current
I(V1) :        -1.25     device_current
```

Figure 3: Simulated Results

### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_1$	1.25A	1.25A
$I_2$	5A	5A
$V_A$	3.75V	3.75V
$V_B$	7V	7V

Table 1: Numerical 1

**Numerical 2:**

Find the value of  $V_{R_1}$  in the circuit of Figure 4.

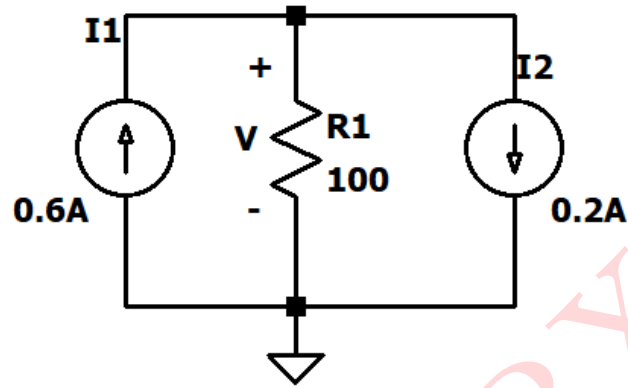


Figure 4: Circuit 2

**Solution:**

$$I_1 = 0.6A, I_2 = 0.2A$$

...(From Circuit 2)

Applying KVL to circuit 2,

$$V_{R_1} - 100(I_1 - I_2) = 0$$

$$V_{R_1} = 100 \times (0.6 - 0.2)$$

$$V_{R_1} = 100 \times 0.4$$

$$\therefore V_{R_1} = 40V$$

**SIMULATED RESULTS:**

Above circuit is simulated in LTspice. The results are presented below:

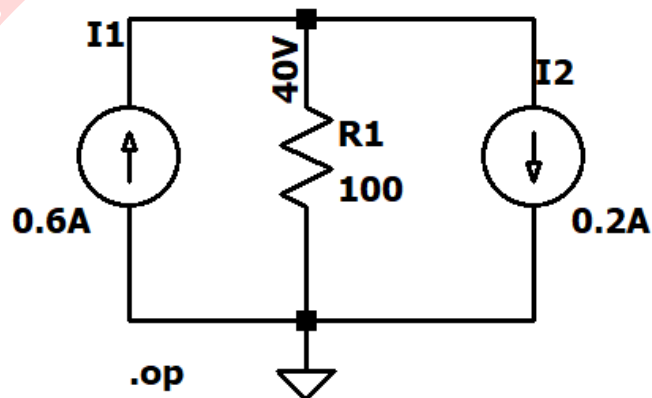


Figure 5: Circuit Schematic

Simulated results are shown in Figure 6.

```

* C:\Users\lenovo\Desktop\LTspiceXVII\sanika_week1_day1_circuit2(a).asc
--- Operating Point ---
V(n001) :      40      voltage
I(I2) :      0.2      device_current
I(I1) :      0.6      device_current
I(R1) :      0.4      device_current

```

Figure 6: Simulated Results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$V_{R_1}$	40V	40V

Table 2: Numerical 2

**Numerical 3:**

Find the value of  $V_1$ ,  $V_2$  in the circuit of Figure 7.

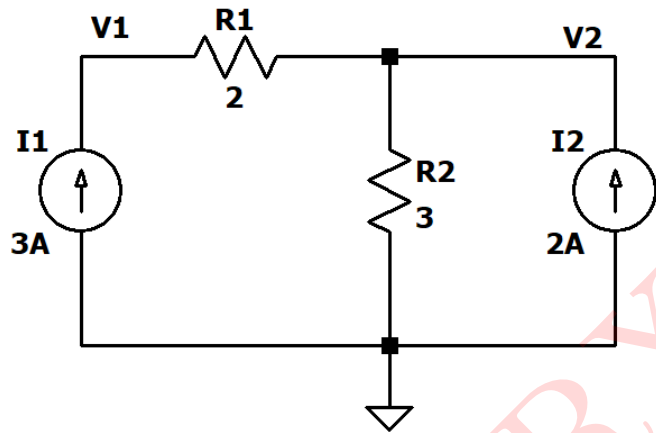


Figure 7: Circuit 3

**Solution:**

$$I_1 = 3A, I_2 = 2A$$

...(From Circuit 3)

Applying KVL to circuit 3,

$$V_1 - 3(I_1 + I_2) - 2I_1 = 0$$

$$V_2 - 3(I_1 + I_2) = 0$$

$$\therefore V_1 = 15 + 6 = 21V$$

$$\therefore V_2 = 15V$$

**SIMULATED RESULTS:**

Above circuit is simulated in LTspice. The results are presented below:

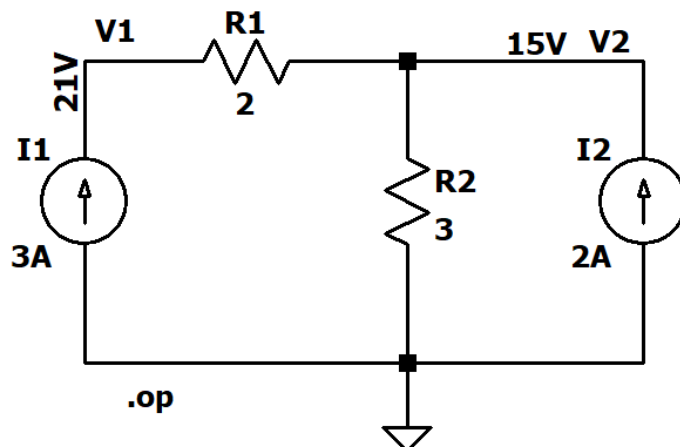


Figure 8: Circuit Schematic

Simulated results are shown in Figure 9.

```
* C:\Users\lenovo\Desktop\LTspiceXVII\sanika_week1_day1_circuit2(b).asc

--- Operating Point ---

V(n002) :      15      voltage
V(n001) :      21      voltage
I(I2) :        2      device_current
I(I1) :        3      device_current
I(R2) :        5      device_current
I(R1) :       -3      device_current
```

Figure 9: Simulated Results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$V_1$	21V	21V
$V_2$	15V	15V

Table 3: Numerical 3

#### Numerical 4:

Find the value of  $i_1$ ,  $i_2$  in the circuit of Figure 10.

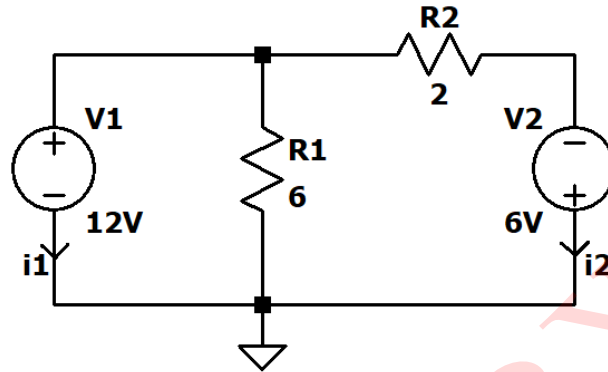


Figure 10: Circuit 4

#### Solution:

$$V_1 = 12V, V_2 = 6V$$

...(From Circuit 4)

Applying KVL to loop 1 in circuit 4,

$$V_1 + 6(i_1 + i_2) = 0$$

$$\therefore i_1 + i_2 = -2$$

...(1)

Applying KVL to loop 2 in circuit 4,

$$6(i_1 + i_2) + 2i_2 = 6$$

$$6i_1 + 8i_2 = 6$$

$$3i_1 + 4i_2 = 3$$

...(2)

Solving (1) and (2) simultaneously,

$$\therefore i_2 = 9A \quad \therefore i_1 = -11A$$

#### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

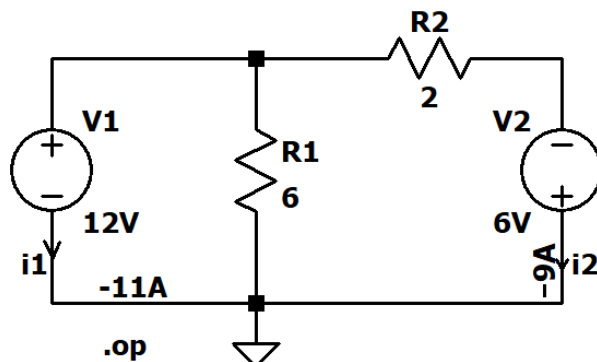


Figure 11: Circuit Schematic

Simulated results are shown in Figure 12.  
 ( $i_2$  is negative due to its direction.)

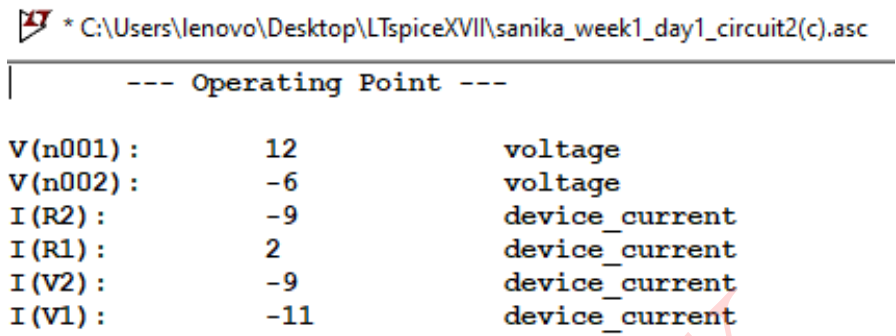


Figure 12: Simulated Results

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$i_1$	-11A	-11A
$i_2$	9A	9A(↓)

Table 4: Numerical 4



**Numerical 5:**

Find the current  $I$  and the power absorbed by each element in the circuit of Figure 13.

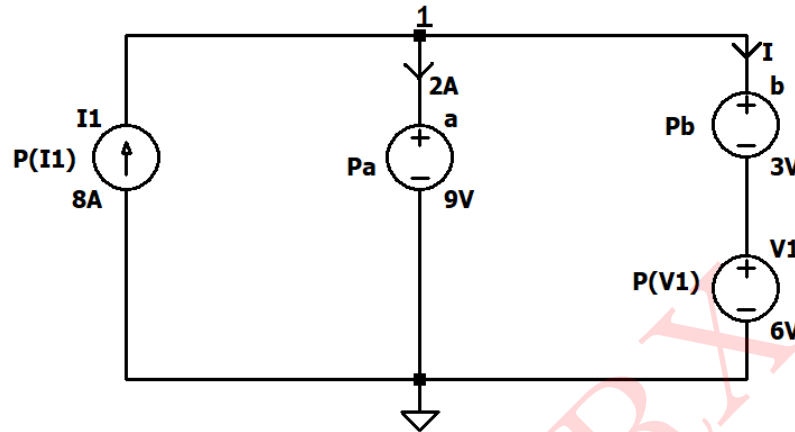


Figure 13: Circuit 5

**Solution:**

Applying KCL at node 1 in circuit 5,

$$I + 2A = 8A$$

$$\therefore I = 8 - 2$$

$$\therefore I = 6A$$

$$R_a = \frac{V_a}{I_a} = \frac{9}{2} = 4.5\Omega$$

$$R_b = \frac{V_b}{I_b} = \frac{3}{6} = 0.5\Omega$$

$\therefore$  Power absorbed by each element,

$$P_{I_1} = V_{I_1} \times I_1 = 9 \times -8 = -72W$$

$$P_a = V_a \times I_a = 9 \times 2 = 18W$$

$$P_b = V_b \times I_b = 6 \times 3 = 18W$$

$$P_{V_1} = V_1 \times I_{V_1} = 6 \times 6 = 36W$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

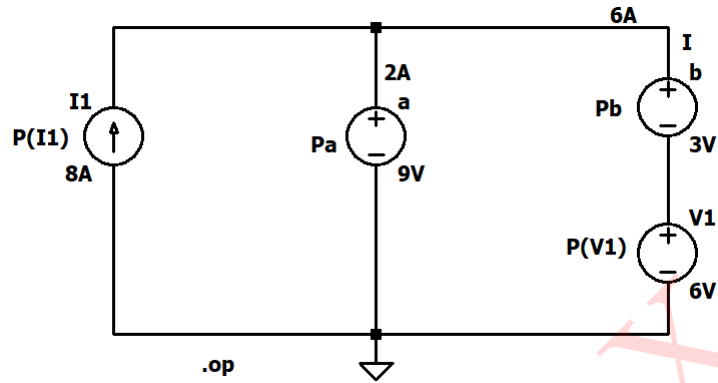


Figure 14: Circuit Schematic

Simulated results are shown in Figure 15.

```
* C:\Users\lenovo\Desktop\LTspiceXVII\task\sanika.p_week1_day2_circuit1.asc

--- Operating Point ---
V(n001) :      9      voltage
V(n002) :      6      voltage
I(I1) :      8      device_current
I(R2) :      6      device_current
I(R1) :      2      device_current
I(V1) :      6      device_current
```

Figure 15: Simulated Results

### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I$	6A	6A
$P_{I_1}$	-72W	-72W
$P_a$	18W	18W
$P_b$	18W	18W
$P_{V_1}$	36W	36W

Table 5: Numerical 5

**Numerical 6:**

Find  $v$  (voltage across  $R_2$ ) and  $i$  (current through  $R_3$ ) in the circuit of Figure 16.

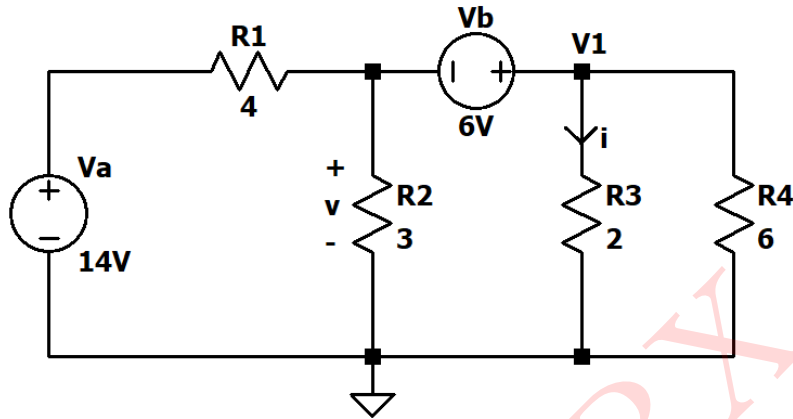


Figure 16: Circuit 6

**Solution:**

Using nodal analysis in the circuit 6,

$$V_1 - v = 6V \quad (\text{Supernode}) \quad \dots(1)$$

Applying KCL at supernode,

$$\frac{v - 14}{4} + \frac{v}{3} + \frac{V_1}{2} + \frac{V_1}{6} = 0$$

$$\therefore \frac{v}{4} + \frac{v}{3} + \frac{V_1}{2} + \frac{V_1}{6} = 3.5$$

$$\frac{3v + 4v + 6V_1 + 2V_1}{12} = 3.5$$

$$7v + 8V_1 = 42$$

$$7v + 8 \times (6 + v) = 42 \quad \dots(\text{from (1)})$$

$$15v + 48 = 42$$

$$v = -\frac{6}{15}$$

$$\therefore v = -0.4V$$

$$V_1 = 6 + v = 6 - 0.4$$

$$\therefore V_1 = 5.6V$$

$$i = \frac{V_1}{R_3} = \frac{5.6}{2}$$

$$\therefore i = 2.8A$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

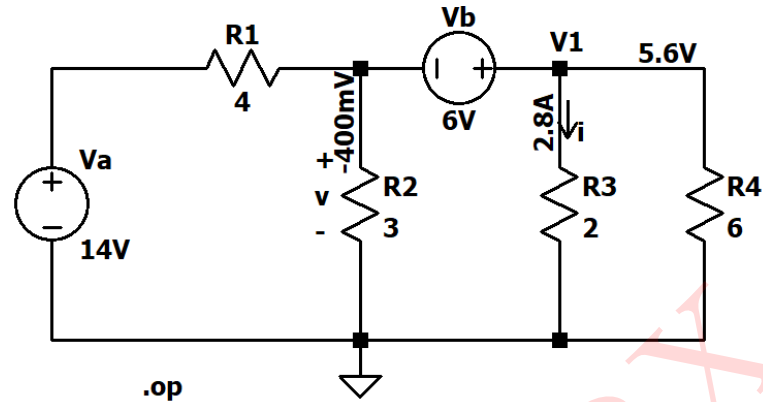


Figure 17: Circuit Schematic

Simulated results are shown in Figure 18.

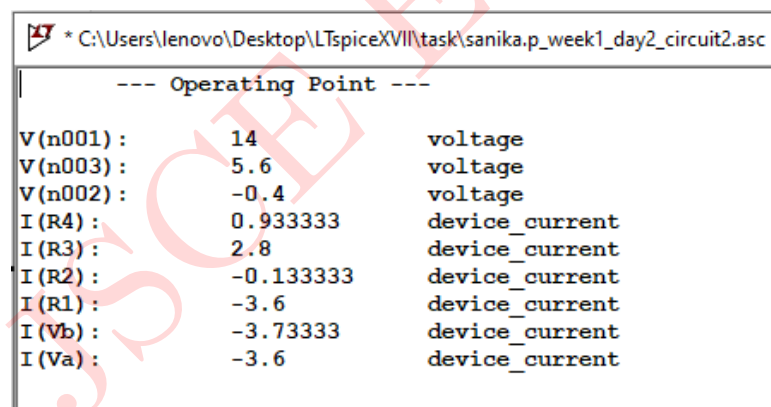


Figure 18: Simulated Results

### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$v_{R_2}$	-0.4V	-0.4V
$V_1$	5.6V	5.6V
$i_{R_3}$	2.8A	2.8A

Table 6: Numerical 6

### Numerical 7:

Find the current  $I_{XY}$  flowing in the branch XY in the circuit of Figure 19 by superposition theorem.

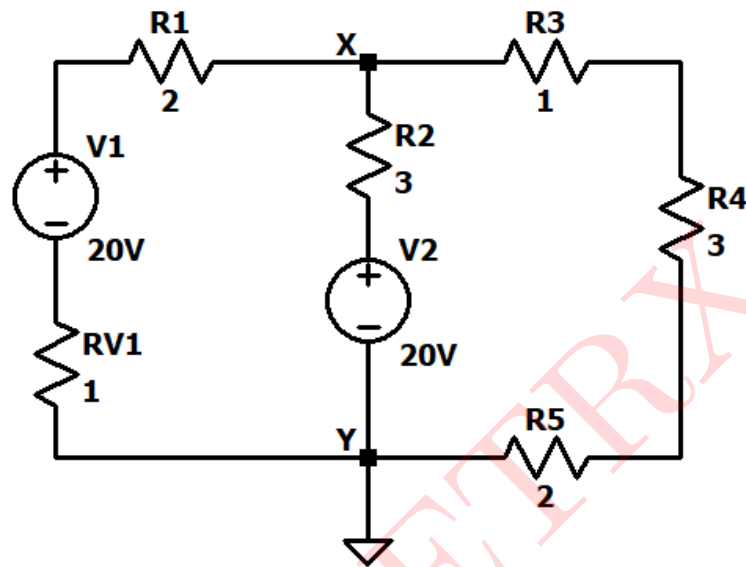


Figure 19: Circuit 7(a)

### Solution:

In the circuit 7(a),

$$R_O = R_3 + R_4 + R_5$$

**CASE 1:** Only  $V_1$  is active

...(Refer Figure 20)

In circuit 7(b),

$$R_T = (R_{V1} + R_1) + (R_2 || R_O)$$

$$R_T = (1 + 2) + (3 || 6)$$

$$R_T = 5\Omega$$

$$I_{V1} = \frac{V_1}{R_T} = \frac{20}{5} = 4A$$

$$I_{R2} = \frac{I_{V1} \times R_O}{R_O + R_2} = \frac{4 \times 6}{6 + 3}$$

$$\therefore I_{R2} = 2.667A(\downarrow)$$

$$\therefore I_{(XY)_1} = 2.667A(\downarrow)$$

...(1)

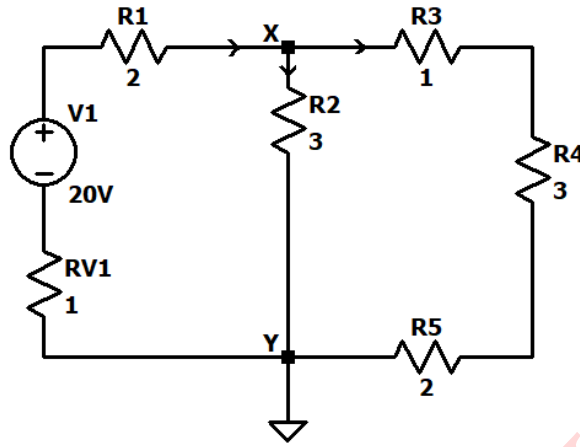


Figure 20: Circuit 7(b) - only  $V_1$  is active

**CASE 2:** Only  $V_2$  is active

...(Refer Figure 21)

In circuit 7(c),

$$R_T = R_2 + (R_{V1} + R_1 || R_O)$$

$$R_T = 3 + (3 || 6)$$

$$R_T = 5\Omega$$

$$I_{V2} = \frac{V_2}{R_T} = \frac{20}{5} = 4A$$

$$\therefore I_{(XY)_2} = 4A(\uparrow) \quad \dots(2)$$

$\therefore$  From (1) and (2),

$$I_{XY} = 4 - 2.667$$

$$\therefore I_{XY} = 1.33A(\uparrow)$$

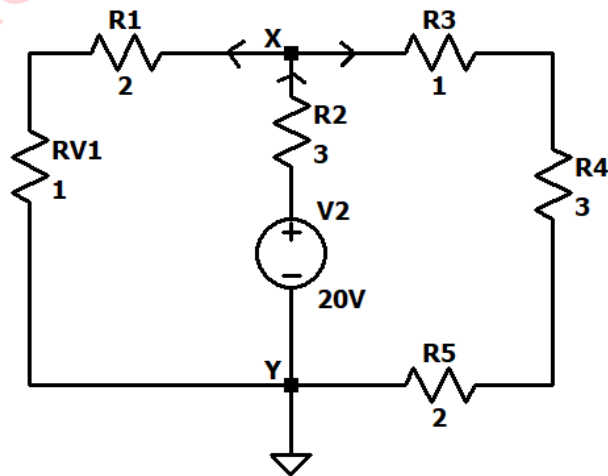


Figure 21: Circuit 7(c) - only  $V_2$  is active

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

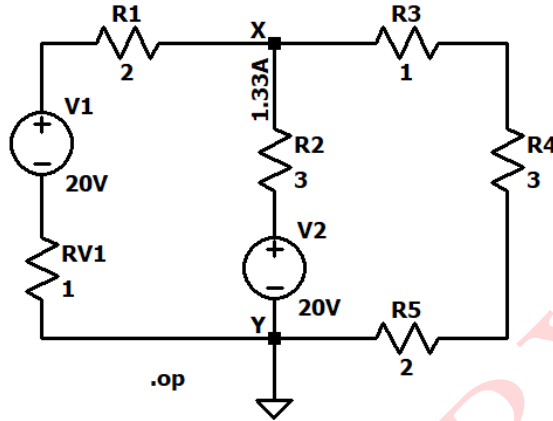


Figure 22: Circuit Schematic

Simulated results are shown in Figure 23.

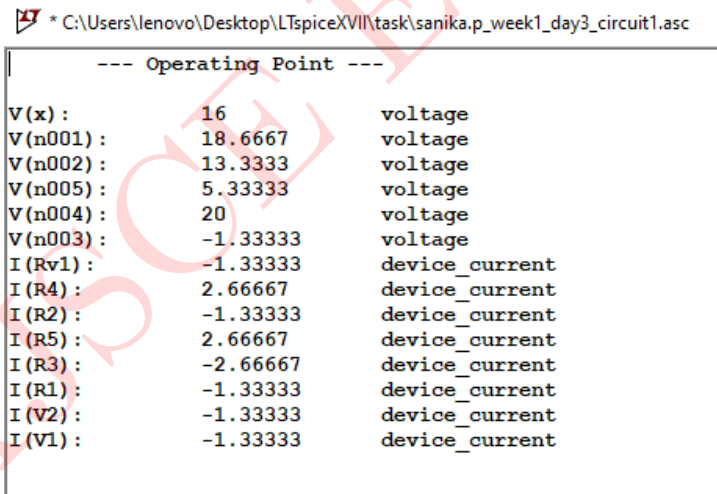


Figure 23: Simulated Results

### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{(XY)_1}$	2.667A	2.667A
$I_{(XY)_2}$	4A	4A
$I_{XY}$	1.33A(↑)	1.33A (↑)

Table 7: Numerical 7

**Numerical 8:**

Find the Norton equivalent circuit in the Figure 24 at terminals a-b.

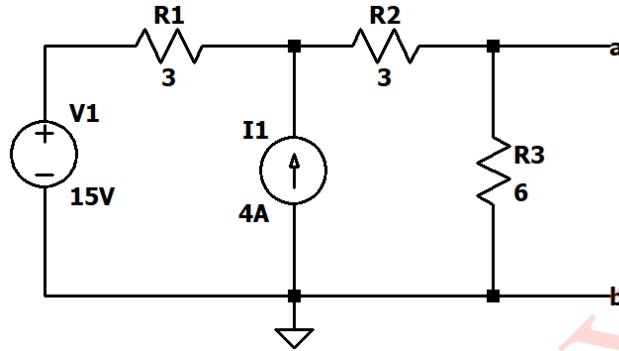


Figure 24: Circuit 8(a)

**Solution:**

1. For calculating  $R_N$

...(Refer Figure 25)

$$R_N = (R_1 + R_2) \parallel R_3$$

$$R_N = (3 + 3) \parallel 6 = 6 \parallel 6$$

$$R_N = 3\Omega$$

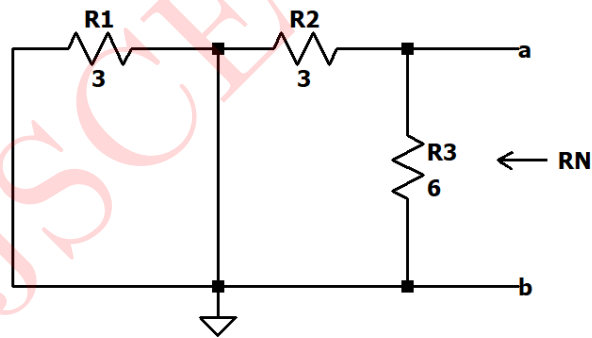


Figure 25: Circuit 8(b) - calculating  $R_N$

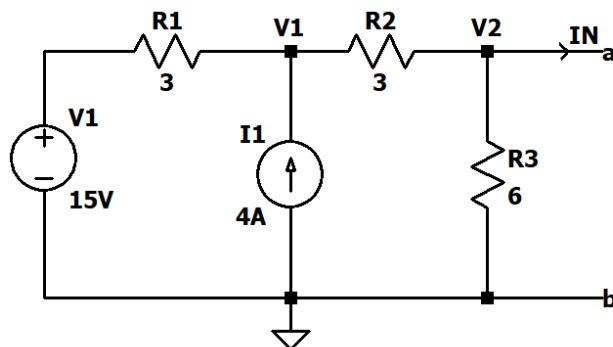


Figure 26: Circuit 8(c) - calculating  $I_N$



2. For calculating  $I_N$  ... (Refer Figure 26)

Using nodal analysis in the circuit 8(c),

For  $V_1$ ,

$$\frac{V_1 - 15}{3} + \frac{V_1 - V_2}{3} = 4$$

$$\therefore 2V_1 - V_2 = 27 \quad \dots(1)$$

For  $V_2$ ,

$$\frac{V_2 - V_1}{3} + \frac{V_2}{6} = 0$$

$$\therefore 3V_2 = 2V_1 \quad \dots(2)$$

Substituting (2) in (1),

$$3V_2 - V_2 = 27$$

$$\therefore V_2 = \frac{27}{2} = 13.5V$$

$$I_N = \frac{V_2}{R_N} = \frac{13.5}{3}$$

$$\therefore I_N = 4.5A$$

$\therefore$  Norton equivalent circuit is shown in Figure 27.

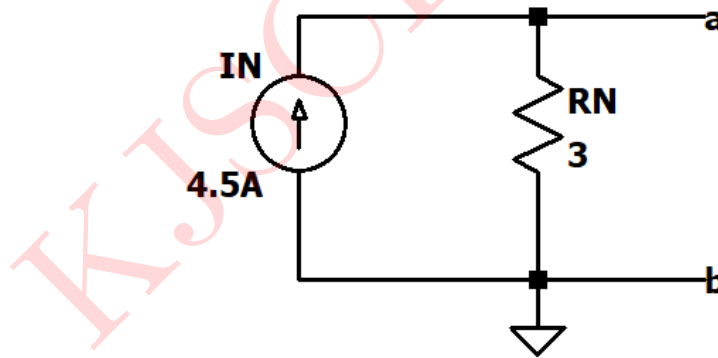


Figure 27: Norton equivalent circuit

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

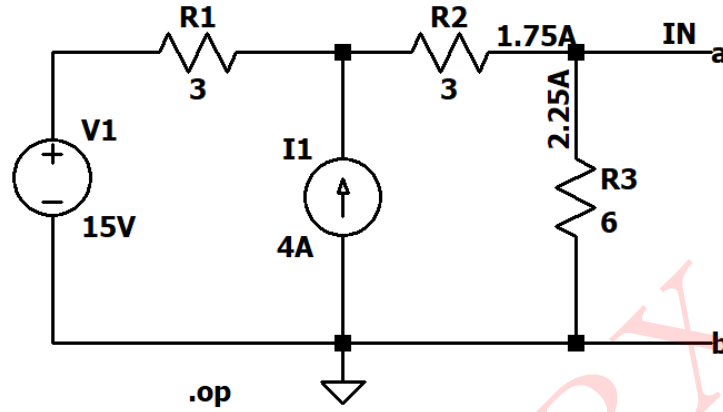


Figure 28: Circuit Schematic

Simulated results are shown in Figure 29.

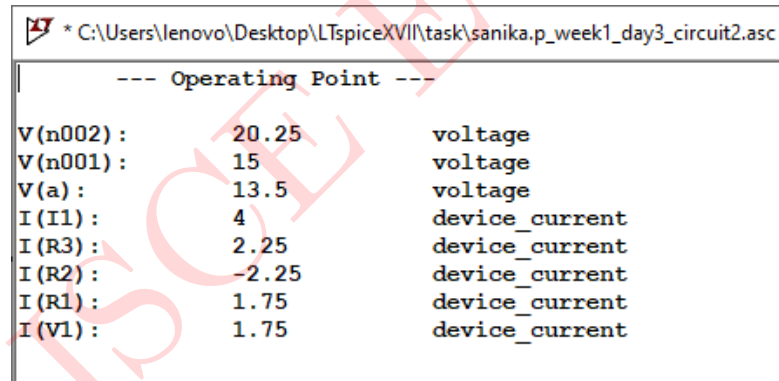


Figure 29: Simulated Results

$$(I_N = I_{R_1} + I_{R_3})$$

### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$R_N$	$3\Omega$	$3\Omega$
$I_N$	4.5A	4.5A

Table 8: Numerical 8

### Numerical 9:

For the circuit shown in Figure 30, calculate the current in  $6\Omega$  resistor by using Norton's Theorem.

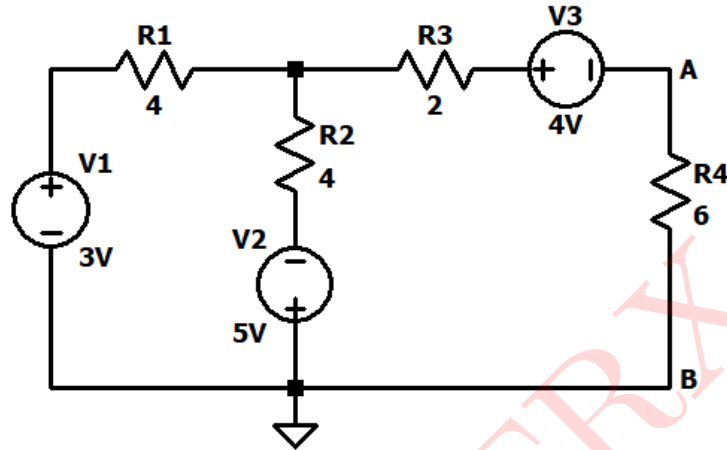


Figure 30: Circuit 9(a)

### Solution:

1. Calculating  $I_N$ , ... (Refer Figure 31)

Using Mesh analysis,

For Mesh 1,

$$3 - 4I_1 - 4(I_1 - I_2) + 5 = 0$$

$$-4I_1 - 4I_1 + 4I_2 + 8 = 0$$

$$8I_1 - 4I_2 = 8$$

$$\therefore 2I_1 - I_2 = 2 \quad \dots(1)$$

For Mesh 2,

$$-2I_2 - 4 - 5 - 4(I_2 - I_1) = 0$$

$$-2I_2 - 9 - 4I_2 + 4I_1 = 0$$

$$\therefore 4I_1 - 6I_2 = 9 \quad \dots(2)$$

Solving (1) and (2) simultaneously,

$$4I_2 = -5$$

$$\therefore I_2 = -1.25A \quad I_1 = 0.375A$$

From Figure 31,  $I_2 = I_N$

$$\therefore I_N = \mathbf{1.25A}(\uparrow) \quad \dots(\text{direction of current is different from assumed})$$

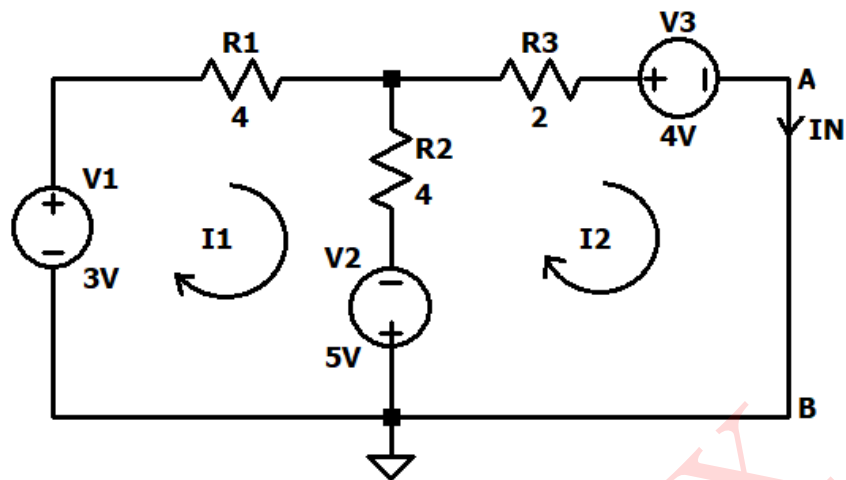


Figure 31: Circuit 9(b) - calculating  $I_N$

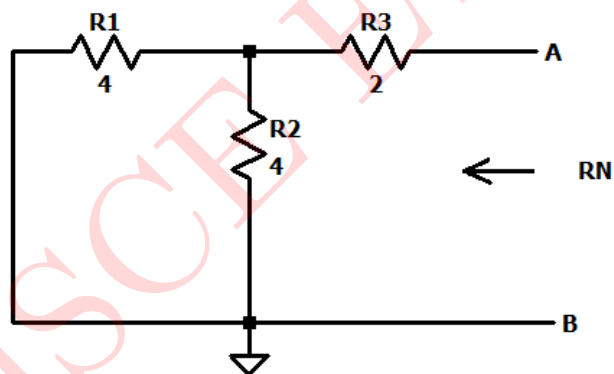


Figure 32: Circuit 9(c) - calculating  $R_N$

2. Calculating  $R_N$ ,

...(Refer Figure 32)

$$R_N = (R_1 || R_2) + R_3$$

$$R_N = (4 || 4) + 2 = 2 + 2$$

$$R_N = 4\Omega$$

∴ Norton equivalent circuit will be as shown in Figure 33.

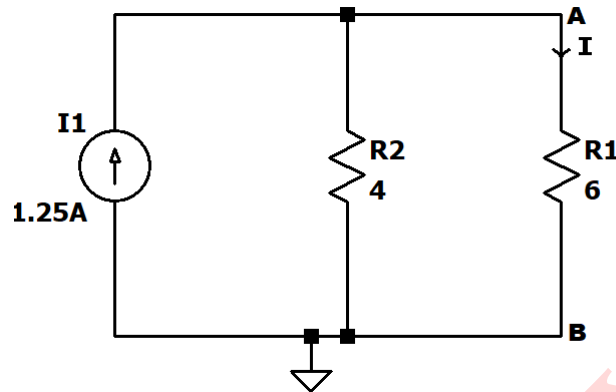


Figure 33: Norton equivalent circuit

∴ current in  $6\Omega$  resistor is,

$$I = -\frac{5}{4} \times \frac{4}{10}$$

$$I = -0.5\text{A}$$

#### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

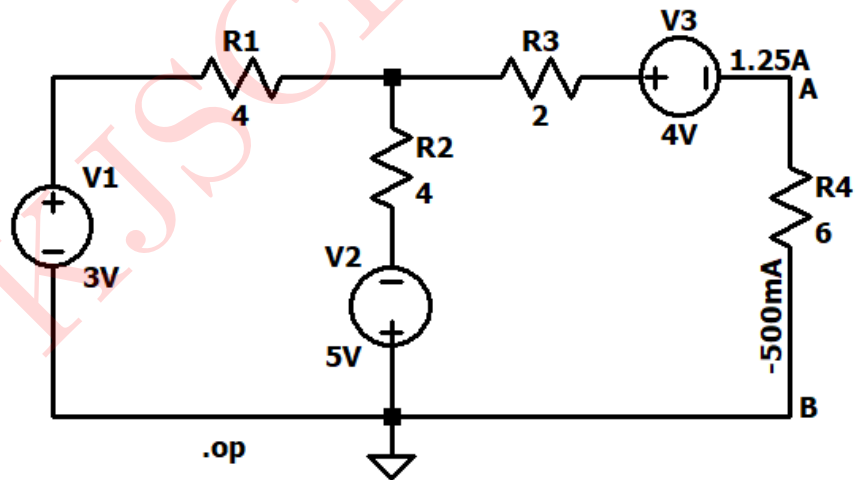


Figure 34: Circuit Schematic

Simulated results are shown in Figure 35.

```

* C:\Users\lenovo\Desktop\LTspiceXVII\task\sanika.p_week1_day4_circuit1.asc

--- Operating Point ---
V(n002) :      0      voltage
V(n001) :      3      voltage
V(n005) :     -5      voltage
V(n003) :      1      voltage
V(n004) :     -3      voltage
I(R4) :     -0.5      device_current
I(R3) :      0.5      device_current
I(R2) :      1.25      device_current
I(R1) :     -0.75      device_current
I(V3) :     -0.5      device_current
I(V2) :     -1.25      device_current
I(V1) :     -0.75      device_current

```

Figure 35: Simulated Results

**Comparison of theoretical and simulated values:**

Parameters	Theoretical Values	Simulated Values
$I_N$	1.25A(↑)	1.25A(↑)
$I$	-0.5A	-0.5A
$I_1$	0.375A	0.375A

Table 9: Numerical 9

**Numerical 10:**

Find the value of current flowing through  $6\Omega$  resistor using Thevenin Theorem.

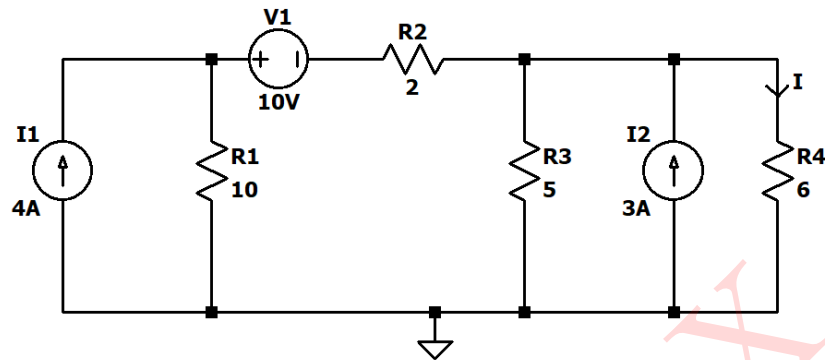


Figure 36: Circuit 10(a)

**Solution:**

Using source transformation, the circuit can be drawn as :

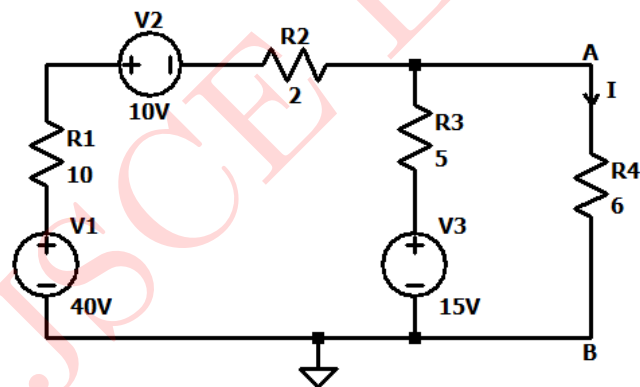


Figure 37: Circuit 10(b)

**1. Calculating  $V_{th}$**

..(Refer Figure 38)

Using Mesh analysis,

$$40 - 10I_1 - 10 - 2I_1 - 5 - 15I_1 = 0$$

$$27I_1 = 25$$

$$\therefore I_1 = \frac{25}{27} = 0.9259A$$

writing  $V_{th}$  equation,

$$-V_{th} + 5I_1 + 15 = 0$$

$$V_{th} = (5 \times 0.9259) + 15$$

$$\therefore V_{th} = 19.629V$$

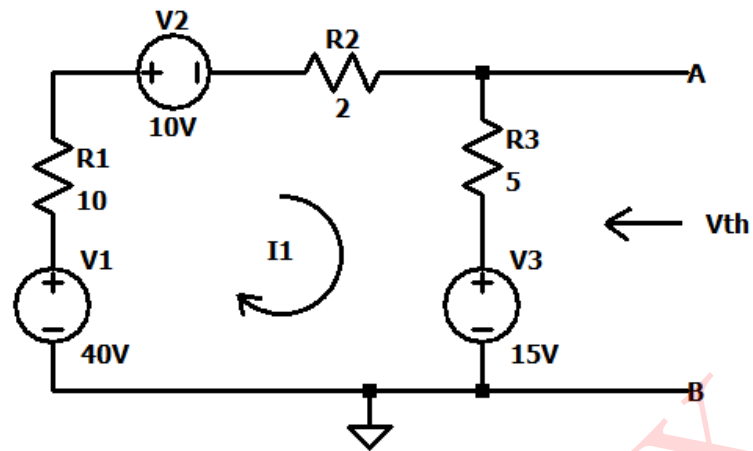


Figure 38: Circuit 10(c) - calculating  $V_{th}$

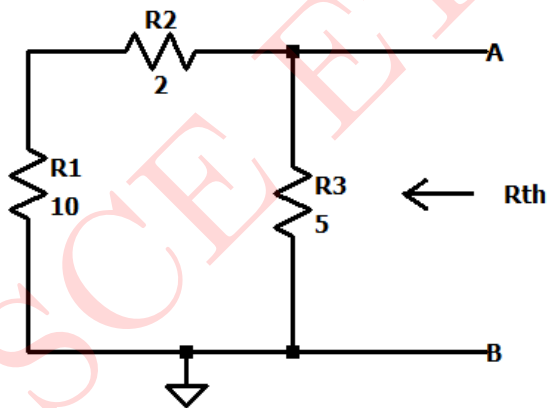


Figure 39: Circuit 10(d) - calculating  $R_{th}$

2. Calculating  $R_{th}$ ,

...(Refer Figure 39)

$$R_{th} = (R_1 + R_2) || R_3$$

$$R_{th} = (10 + 2) || 5$$

$$R_{th} = 12 || 5 = \frac{60}{17}$$

$$\therefore R_{th} = \mathbf{3.5294\Omega}$$



∴ Thevenin equivalent circuit will be as shown in Figure 40.

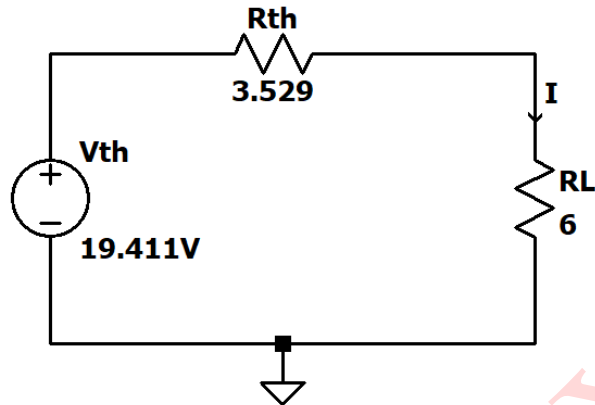


Figure 40: Thevenin equivalent circuit

$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{19.629}{3.5294 + 6}$$

$$\therefore I = 2.059A$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

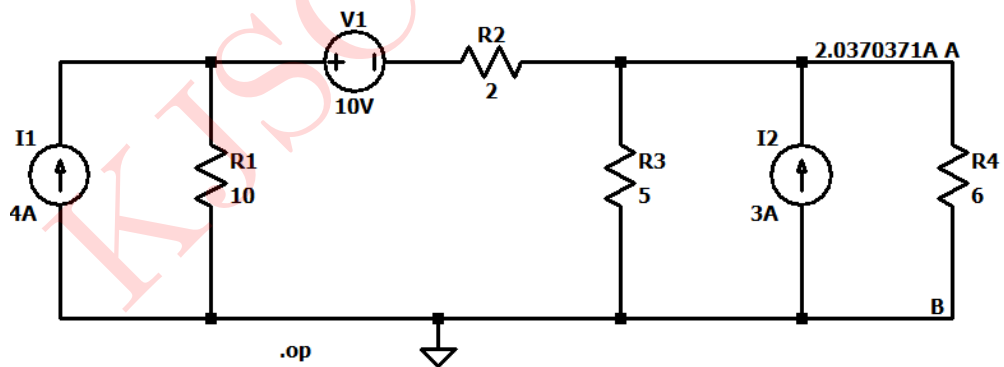


Figure 41: Circuit Schematic

Simulated results are shown in Figure 42.

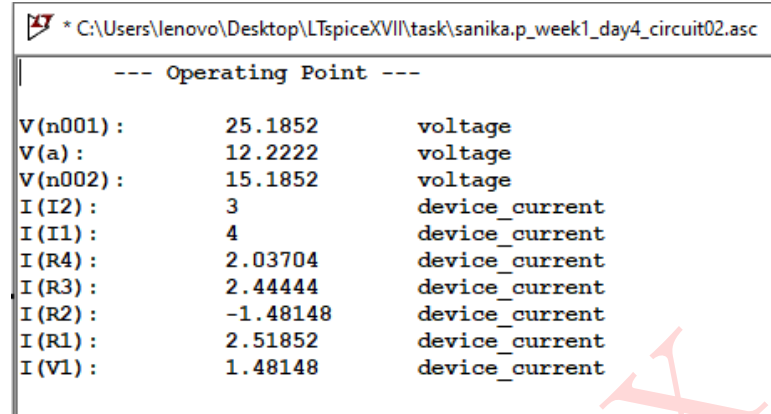


Figure 42: Simulated Results

**Comparison of theoretical and simulated values:**

Parameters	Theoretical Values	Simulated Values
$V_{th}$	19.629V	19.411V
$I$	2.059A	2.037A

Table 10: Numerical 10

**Numerical 11:**

For the circuit given in Figure 43, what will be the  $R_L$  to get the maximum power? What is the maximum power delivered to the load?

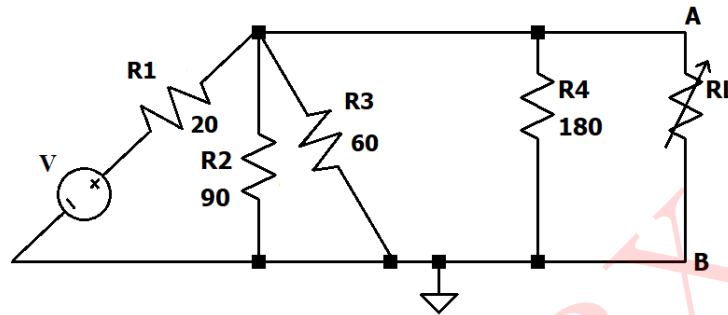


Figure 43: Circuit 11(a)

**Solution:**

The circuit given in Figure 43 can also be drawn as shown in Figure 44.

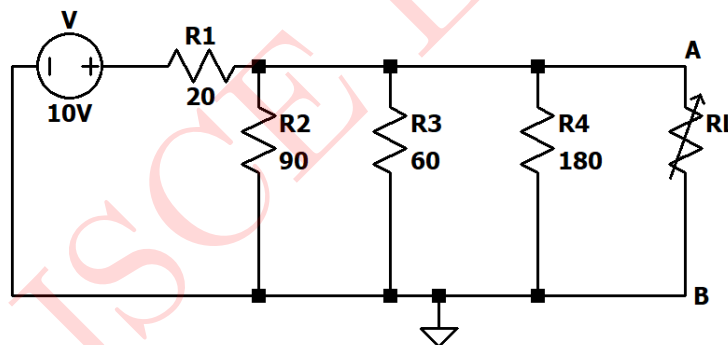


Figure 44: Simplified Circuit

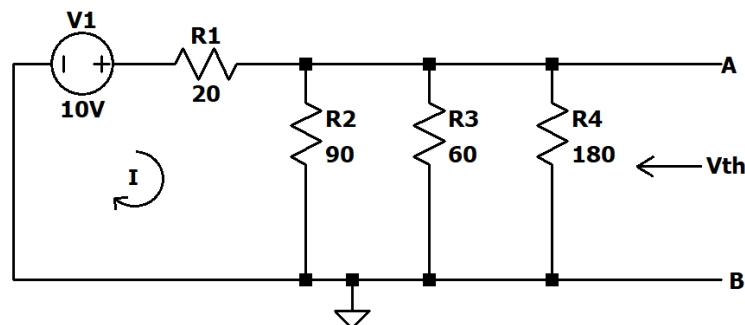


Figure 45: Circuit 11(b) - For calculating  $V_{th}$

1. Calculating  $V_{th}$ :

Applying Mesh analysis in Figure 45.

$$10 - 20I - 30I = 0$$

$$50I = 10$$

$$\therefore I = 0.2A$$

Writing  $V_{th}$  equation,

$$-V_{th} + 30I = 0$$

$$V_{th} = 30I$$

$$V_{th} = 30 \times 0.2$$

$$\therefore V_{th} = 6V$$

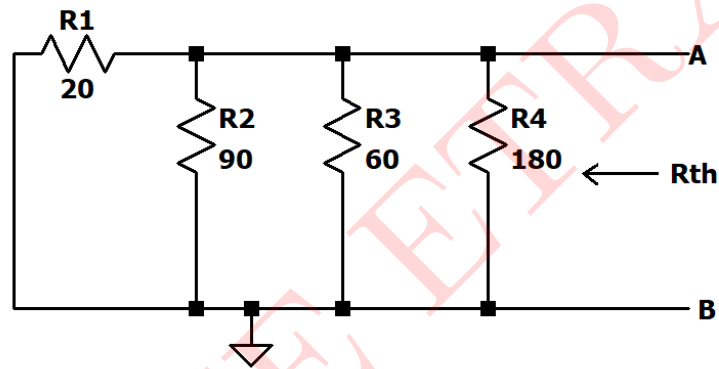


Figure 46: Circuit 11(c) - For calculating  $R_{th}$

2. Calculating  $R_{th}$ :

$$R_{th} = R_1 || R_2 || R_3 || R_4$$

$$R_{th} = 20 || 90 || 60 || 180$$

$$\therefore R_{th} = 12\Omega$$

For Maximum Power Transfer,

$$R_L = R_{th}$$

$$\therefore R_L = 12\Omega$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{6^2}{4 \times 12} = \frac{36}{48}$$

$$\therefore P_{max} = 0.75W$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

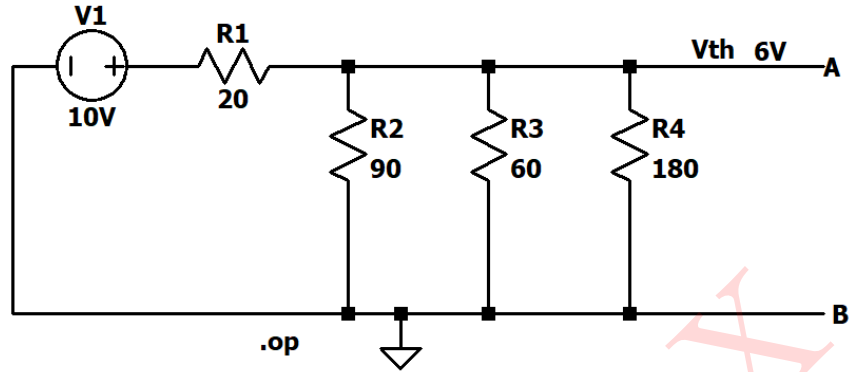


Figure 47: Circuit Schematic

Simulated results are shown in Figure 48.

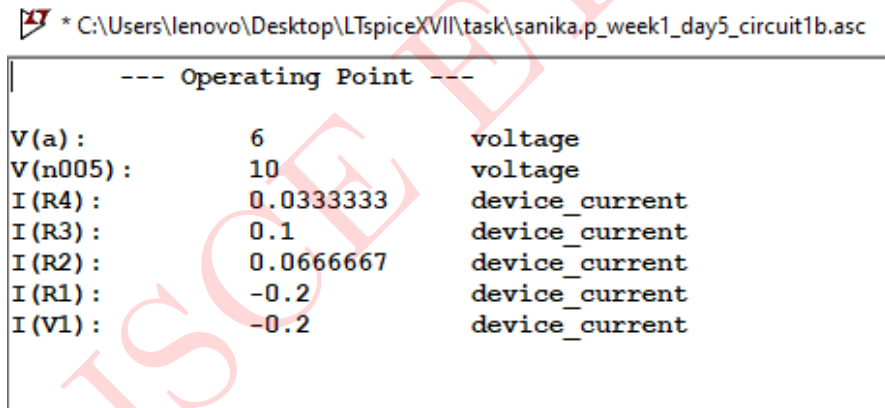


Figure 48: Simulated Results

For the circuit in Figure 47,

$$P_{max} = \frac{V_a^2}{4R_{th}} = \frac{6^2}{4 \times 12} = \frac{36}{48}$$

$$\therefore P_{max} = 0.75W$$

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$P_{max}$	0.75W	0.75W
$V_{th}$	6V	6V
$I$	0.2A	0.2A

Table 11: Numerical 11

\*\*\*\*\*