

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Differential Amplifier Circuits**

**Numerical 1:** Determine the following for the circuit shown in figure 1:

$I_{C1}$ ,  $I_{C2}$ ,  $V_{C1}$ ,  $V_{C2}$ ,  $V_{CE1}$ ,  $V_{CE2}$ , differential voltage gain:  $A_d$ , common mode gain:  $A_{cm}$  and CMRR in dB. Assume  $\beta_1 = \beta_2 = 100$

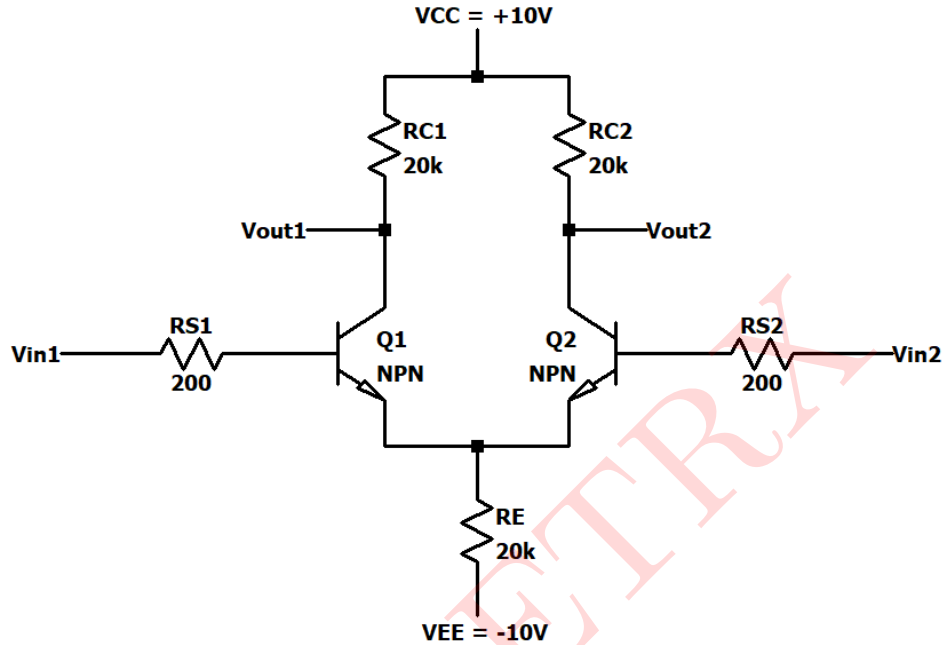


Figure 1: Circuit 1

**Solution:**

The given circuit 1 is a dual input balanced output (DIBO) configuration differential amplifier.

For DC Analysis, consider only one transistor as both the transistors are identical.

**DC Analysis:**

Applying KVL at the B-E loop,

$$R_{S1} I_{B1} - V_{BE} - 2R_E I_E - V_{EE} = 0$$

$$I_{B1} R_{S1} + (1 + \beta) I_{B1} 2R_E = -V_{EE} - V_{BE}$$

$$I_{B1} = \frac{-V_{EE} - V_{BE}}{R_{S1} + (1 + \beta) 2R_E}$$

$$I_B = \frac{10 - 0.7}{200 + (1 + 100) \times 2 \times 20 \times 10^3} = 2.3 \mu A$$

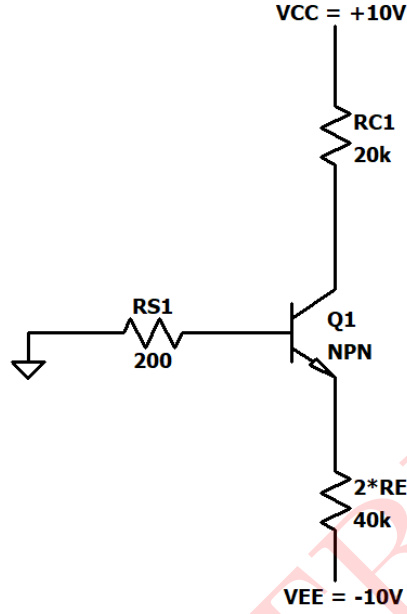


Figure 2: DC Equivalent Circuit

$$I_{C1} = \beta I_{B1}$$

$$I_{CQ} = 100 \times 2.3 \times 10^{-6} = \mathbf{0.23 \text{ mA}}$$

$$I_{E1} = (1 + \beta) I_{B1}$$

$$I_E = (1 + 100) \times 2.3 \times 10^{-6} = \mathbf{0.23 \text{ mA}}$$

As both the transistors are identical,

$$I_{C1} = I_{C2} = \mathbf{0.23 \text{ mA}}$$

$$I_{E1} = I_{E2} = \mathbf{0.23 \text{ mA}}$$

$$V_{C1} = V_{CC} - I_{C1} R_{C1} = 0$$

$$V_{C1} = 10 - 0.23 \times 10^{-3} \times 20 \times 10^3 = \mathbf{5.4 \text{ V}}$$

Applying KVL at C-E loop,

$$V_{CC} - I_C R_{C1} - V_{CE1} - I_{E1} 2R_{E1} - V_{EE} = 0$$

$$V_{CE1} = V_{CC} - I_{C1} R_{C1} - I_{E1} 2R_{E1} - V_{EE}$$

$$V_{CE1} = 10 - 0.23 \times 10^{-3} \times 20 \times 10^3 - 0.23 \times 10^{-3} \times 20 \times 10^3 \times 2 + 10 = \mathbf{6.2 \text{ V}}$$

As both the transistors are identical,

$$V_{C1} = V_{C2} = \mathbf{5.4 \text{ V}}$$

$$V_{CE1} = V_{CE2} = \mathbf{6.2 \text{ V}}$$

### AC Analysis:

$$r_{\pi} = \frac{\beta V_T}{I_C}$$

$$r_o = \frac{100 \times 26 \times 10^{-3}}{0.23 \times 10^{-3}} = \mathbf{11.304 \text{ k}\Omega}$$

$$|A_d| = \frac{\beta R_C}{(r_{\pi} + R_S)}$$

$$|A_d| = \frac{100 \times 20 \times 10^3}{(11.304 \times 10^3 + 200)} = \mathbf{173.85}$$

$$A_{cm} = \left| \frac{R_C}{2R_E} \right| = \frac{20 \times 10^3}{2 \times 20 \times 10^3} = \mathbf{0.5}$$

$$\text{CMRR} = \left| \frac{A_d}{A_{cm}} \right| = \frac{173.85}{0.5} = \mathbf{347.7}$$

$$\text{CMRR in dB} = 20 \log_{10}(347.7) = \mathbf{50.824 \text{ dB}}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

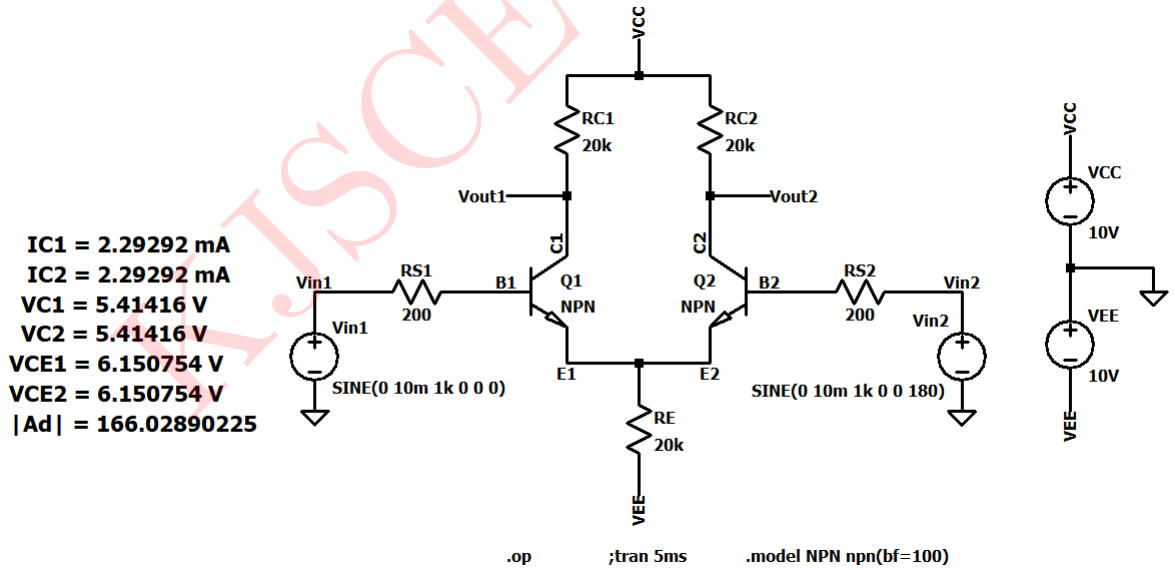


Figure 3: Circuit Schematic 1: Results

The input and output waveforms are shown in figure 4.

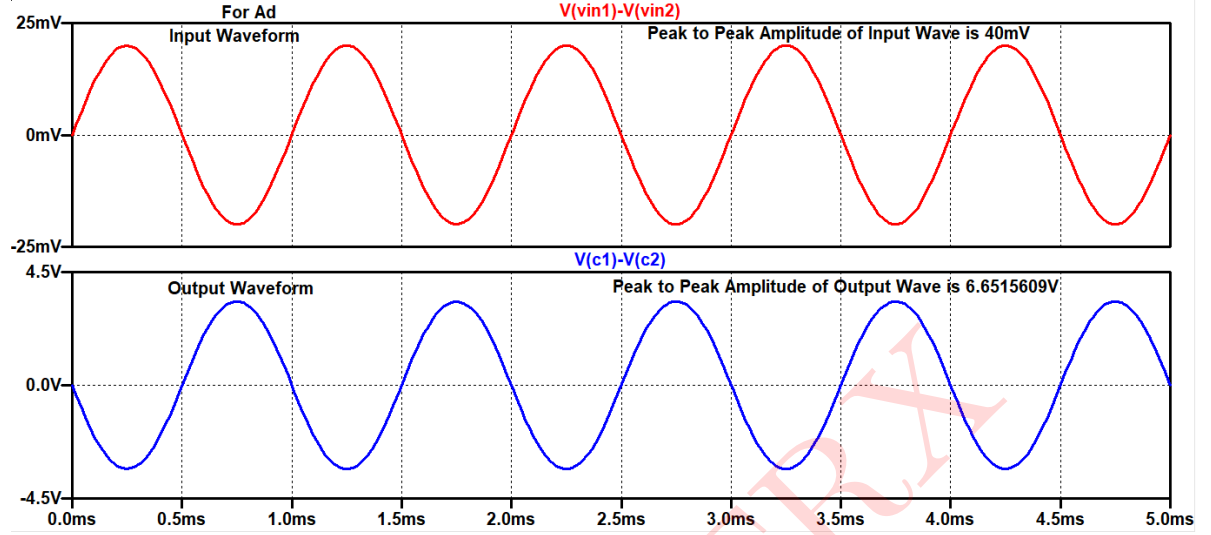


Figure 4: Input & Output waveforms

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{C_1}$	0.23 mA	0.22929 mA
$I_{C_2}$	0.23 mA	0.22929 mA
$V_{C_1}$	5.4 V	5.41416 V
$V_{C_2}$	5.4 V	5.41416 V
$V_{CE_1}$	6.2 V	6.1507 V
$V_{CE_2}$	6.2 V	6.1507 V
Differential voltage gain: $ A_d $	173.85	166.2890
Common mode voltage gain: $A_{cm}$	0.5	—
CMRR is dB	50.824 dB	—

Table 1: Numerical 1

**Numerical 2:** Consider the circuit given in figure 5, the transistor parameters are  $k_{n_1} = k_{n_2} = 50 \mu A/V^2$ ,  $\lambda_1 = \lambda_2 = 0.02 V^{-1}$  &  $V_{TN_1} = V_{TN_2} = 1 V$ . Determine  $I_S$ ,  $I_{D_1}$ ,  $I_{D_2}$ ,  $V_{D_1}$ ,  $V_{D_2}$ ,  $V_{DS_1}$ ,  $V_{DS_2}$ . Calculate differential mode voltage gain:  $A_{d_1}$  common mode gain:  $A_{cm}$  and CMRR in dB.

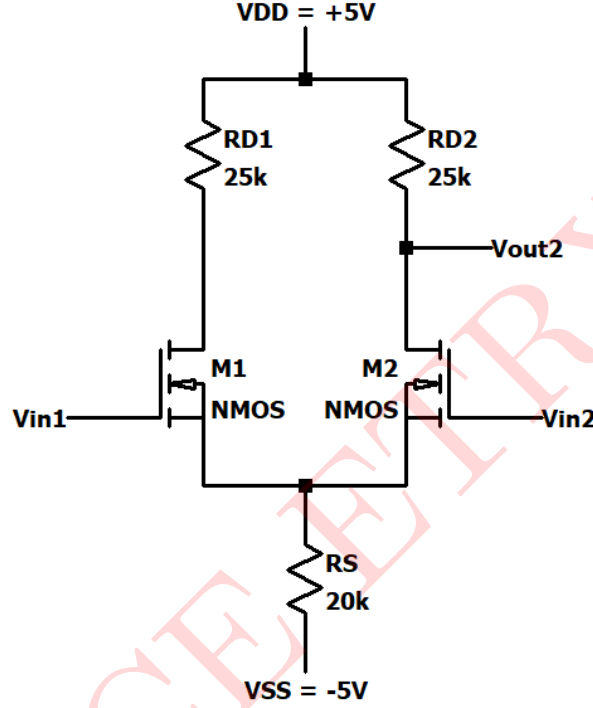


Figure 5: Circuit 2

**Solution:**

The given circuit 2 is a dual input unbalanced output (DIUO) differential amplifier. For DC Analysis, consider only one transistor as both the transistors are identical.

**DC Analysis:**

Applying KVL at the G-S loop,

$$-V_{GS_1} - 2I_{D_1}R_S - V_{SS} = 0$$

$$V_{GS_1} = -V_{SS} - 2I_{D_1}R_S$$

$$V_{GS_1} = 5 - 2I_{D_1}20 \times 10^3$$

$$V_{GS_1} = 5 - I_{D_1}40 \times 10^3 \quad \dots(1)$$

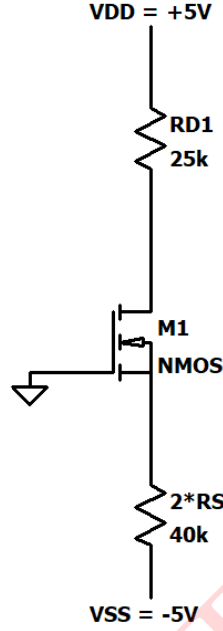


Figure 6: DC Equivalent Circuit

Applying KVL at the D-S loop,

$$V_{DD} - I_{D1}R_{D1} - V_{DS1} - I_{D1}2R_S - V_{SS} = 0$$

$$V_{DS1} = V_{DD} - I_{D1}R_{D1} - I_{D1}2R_S - V_{SS}$$

$$V_{DS1} = 5 - I_{D1}25 \times 10^3 - I_{D1}40 \times 10^3 + 5$$

$$V_{DS1} = 10 - I_{D1}65 \times 10^3 \quad \dots(2)$$

From current equation,

$$I_{D1} = k_n(V_{GS1} - V_{TN})^2(1 + \lambda V_{DS1})$$

$$I_{D1} = 50 \times 10^{-6}(5 - I_{D1}40 \times 10^3 - 1)^2 \times (1 + 0.02(10 - I_{D1}65 \times 10^3))$$

$$I_{D1} = 50 \times 10^{-6}(4 - I_{D1}40 \times 10^3)^2 \times (1 + 0.2 - I_{D1}1.3 \times 10^3)$$

$$I_{D1} = 50 \times 10^{-6}(4 - I_{D1}40 \times 10^3)^2 \times (1.2 - I_{D1}1.3 \times 10^3)$$

$$I_{D1} = 50 \times 10^{-6}(16 - I_{D1}320 \times 10^3 + I_{D1}^2 1600 \times 10^6) \times (1.2 - I_{D1}1.3 \times 10^3)$$

$$I_{D1} = 50 \times 10^{-6}(19.2 - I_{D1}384 \times 10^3 + I_{D1}^2 1920 \times 10^6 - I_{D1}20.8 \times 10^3 + I_{D1}^2 416 \times 10^6 - I_{D1}^3 2080 \times 10^9)$$

$$I_{D1} = 50 \times 10^{-6}(19.2 - I_{D1}404.8 \times 10^3 + I_{D1}^2 2336 \times 10^6 - I_{D1}^3 2080 \times 10^9)$$

$$I_{D1} = 9.6 \times 10^{-4} - I_{D1}20.24 + I_{D1}^2 116.8 \times 10^3 - I_{D1}^3 104 \times 10^6$$

$$I_{D1}^3 104 \times 10^6 - I_{D1}^2 116.8 \times 10^3 + I_{D1}21.24 - 9.6 \times 10^{-4} = 0$$

$$I_{D1} = 9.09 \times 10^{-4} \text{ A or } I_{D1} = 1.41 \times 10^{-4} \text{ A or } I_{D1} = 7.15 \times 10^{-5} \text{ A}$$

Let,  $I_{D_1} = 9.09 \times 10^{-4}$  A

$$V_{GS_1} = 5 - 9.09 \times 10^{-4} \times 40 \times 10^3 = -\mathbf{31.36 \text{ V}}$$

Let,  $I_{D_1} = 1.41 \times 10^{-4}$  A

$$V_{GS_1} = 5 - 1.41 \times 10^{-4} \times 40 \times 10^3 = -\mathbf{0.64 \text{ V}}$$

Let,  $I_{D_1} = 7.15 \times 10^{-5}$  A

$$V_{GS_1} = 5 - 7.15 \times 10^{-5} \times 40 \times 10^3 = \mathbf{2.14 \text{ V}}$$

$V_{GS_1}$  cannot be negative and  $V_{GS_1}$  should be greater than  $V_{TN_1}$

$$V_{GS_1} = 2.14 \text{ V}$$

$$I_{D_1} = 7.15 \times 10^{-5} \text{ A}$$

$$I_{D_1} = \mathbf{0.0715 \text{ mA}}$$

$$V_{DS_1} = 10 - 0.0715 \times 10^{-3} \times 65 \times 10^3 = \mathbf{5.3525 \text{ V}}$$

$$V_{D_1} = V_{DD} - I_{D_1} R_{D_1}$$

$$V_{D_1} = 5 - 0.0715 \times 10^{-3} \times 25 \times 10^3 = \mathbf{3.2125 \text{ V}}$$

As both the transistors are identical,

$$I_{D_1} = I_{D_2} = \mathbf{0.0715 \text{ mA}}$$

$$V_{DS_1} = V_{DS_2} = \mathbf{5.3525 \text{ V}}$$

$$V_{D_1} = V_{D_2} = \mathbf{3.2125 \text{ V}}$$

$$I_S = 2 \times I_{D_1}$$

$$I_S = 2 \times 0.0715 \times 10^{-3} = \mathbf{0.143 \text{ mA}}$$

**AC Analysis:**

$$g_{m_1} = 2k_n(V_{GS_1} - V_{TN_1})(1 + \lambda V_{DS_1})$$

$$g_{m_1} = 2 \times 50 \times 10^{-6}(2.14 - 1)(1 + 0.02 \times 5.3525) = \mathbf{0.126 \text{ mA/V}}$$

$$r_{d_1} = \frac{1}{\lambda I_{D_1}}$$

$$r_{d_1} = \frac{1}{0.02 \times 0.0715 \times 10^{-3}} = \mathbf{699.3 \text{ k}\Omega}$$

As both the transistors are identical,

$$g_{m_1} = g_{m_2} = \mathbf{0.126 \text{ mA/V}}$$

$$r_{d_1} = r_{d_2} = \mathbf{699.3 \text{ k}\Omega}$$

$$|A_d| = \frac{g_m(r_d \parallel R_D)}{2}$$

$$|A_d| = \frac{0.126 \times 10^{-3}(699.3 \times 10^3 \parallel 25 \times 10^3)}{2} = \mathbf{1.52}$$

$$A_{cm} = \frac{g_m(r_d \parallel R_D)}{1 + 2g_m R_S}$$

$$A_{cm} = \frac{0.126 \times 10^{-3}(699.3 \times 10^3 \parallel 25 \times 10^3)}{1 + 2 \times 0.126 \times 10^{-3} \times 20 \times 10^3} = \mathbf{0.503}$$

$$\text{CMRR} = \left| \frac{A_d}{A_{cm}} \right| = \frac{1.52}{0.503} = \mathbf{3.02}$$

$$\text{CMRR in dB} = 20 \log_{10}(3.02) = \mathbf{9.6 \text{ dB}}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

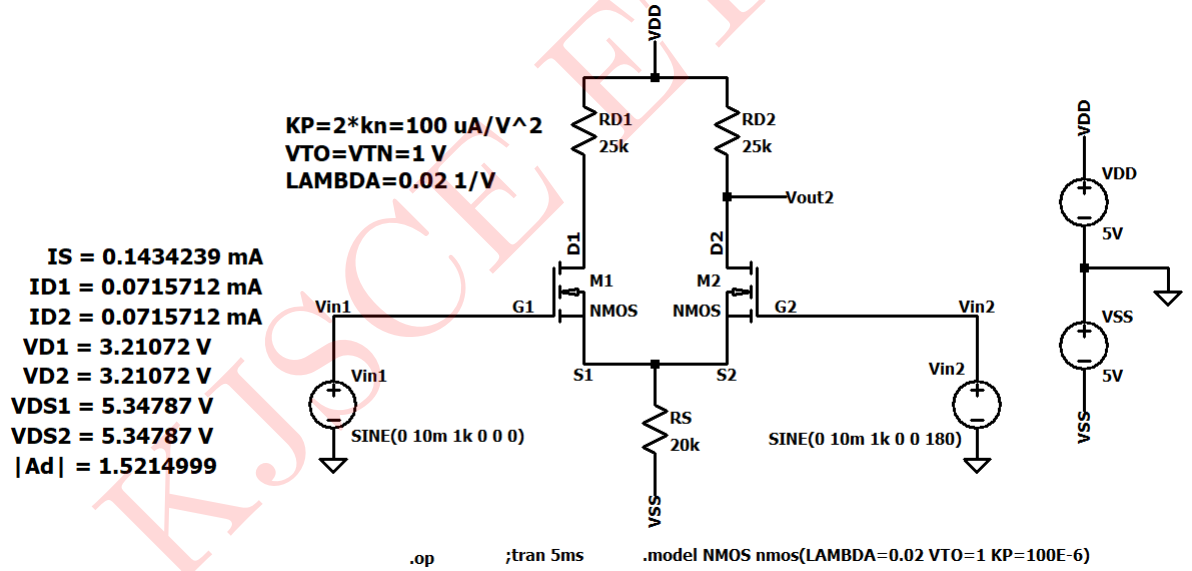


Figure 7: Circuit Schematic 2: Results



The input and output waveforms are shown in figure 8.

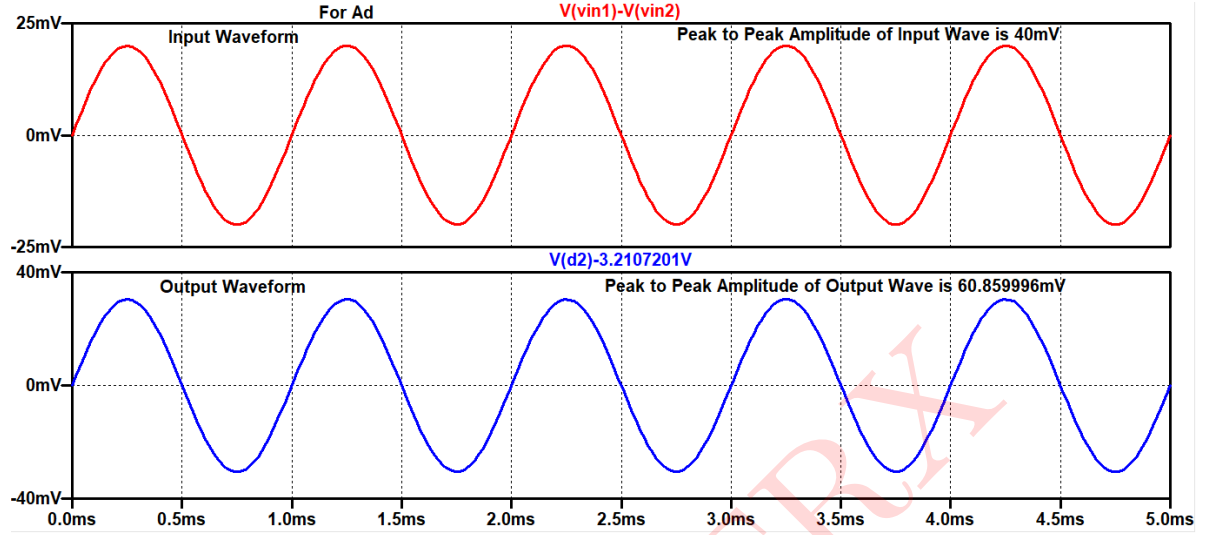


Figure 8: Input & Output waveforms

**Comparison of theoretical and simulated values:**

Parameters	Theoretical Values	Simulated Values
$I_S$	0.143 mA	0.1434 mA
$I_{D_1}$	0.0715 mA	0.0715 mA
$I_{D_2}$	0.0715 mA	0.715 mA
$V_{D_1}$	3.2125 V	3.2107 V
$V_{D_2}$	3.2125 V	3.2107 V
$V_{DS_1}$	5.3525 V	5.3478 V
$V_{DS_2}$	5.3525 V	5.3478 V
Differential voltage gain: $ A_d $	1.52	1.5214
Common mode voktage gain: $A_{cm}$	0.503	—
CMRR is dB	9.6 dB	—

Table 2: Numerical 2

**Numerical 3:** Determine the following for the differential amplifier shown in figure 9:

a)  $I_{C1}, I_{C2}, V_{C1}, V_{C2}$

b) Single ended output gain  $\left( \frac{V_{o1}}{V_{i1} - V_{i2}} \right)$

Given  $\beta_1 = \beta_2 = 100$

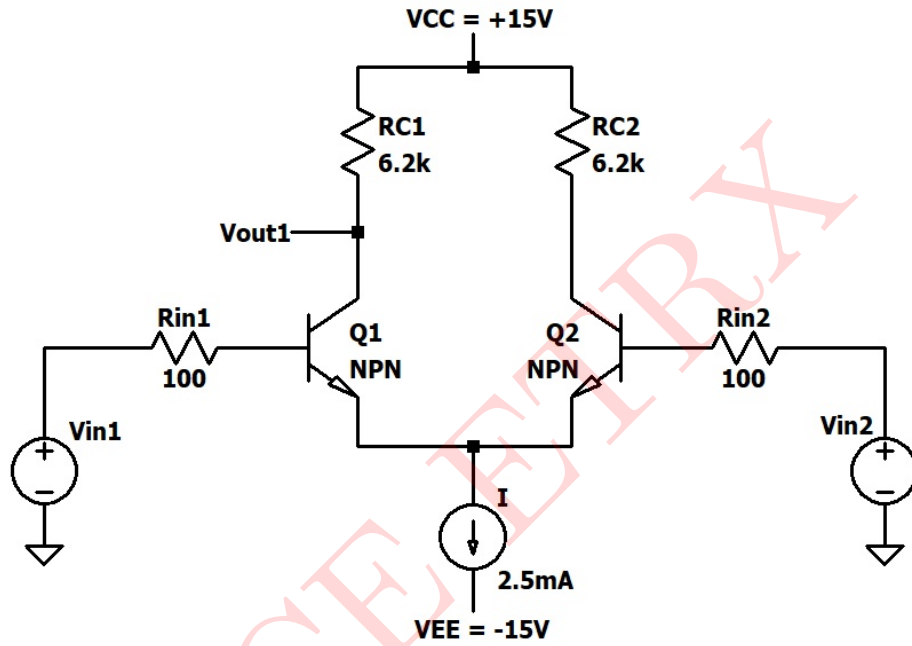


Figure 9: Circuit 3

**Solution:**

The given circuit 3 is a dual input unbalanced output (DIUO) differential amplifier.

a) As there is a current source at terminal E,

$$I_{E1} = I_{E2} = \frac{I}{2} = \frac{2.5 \times 10^{-3}}{2}$$

$$I_{E1} = I_{E2} = \mathbf{1.25 \text{ mA}}$$

$$I_{B1} = \frac{I_{E1}}{1 + \beta} = \frac{1.25 \times 10^{-3}}{101} = \mathbf{12.3 \text{ } \mu\text{A}}$$

$$I_{C1} = \beta I_{B1} = 100 \times 12.3 \times 10^{-6} = \mathbf{1.23 \text{ mA}}$$

Since,  $R_{C1} = R_{C2}$

$$\therefore I_{C1} = I_{C2} = \mathbf{1.23 \text{ mA}}$$

$$V_{C_1} = V_{CC} - I_{C_1} R_{C_1}$$

$$V_{C_1} = 15 - 1.23 \times 10^{-3} \times 6.2 \times 10^3 = \mathbf{7.374 \text{ V}}$$

$$V_{C_1} = V_{C_2} = \mathbf{7.374}$$

$$\text{b) } |A_d| = \frac{V_{o1}}{V_{in1} - V_{in2}} = \frac{\beta R_C}{2(r_\pi + R_{in})}$$

$$\text{where, } r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 26 \times 10^{-3}}{1.23 \times 10^{-3}} = \mathbf{2.11 \text{ k}\Omega}$$

$$|A_d| = \frac{100 \times 6.2 \times 10^{-3}}{2(2.11 \times 10^3 + 100)} = \mathbf{140.27}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

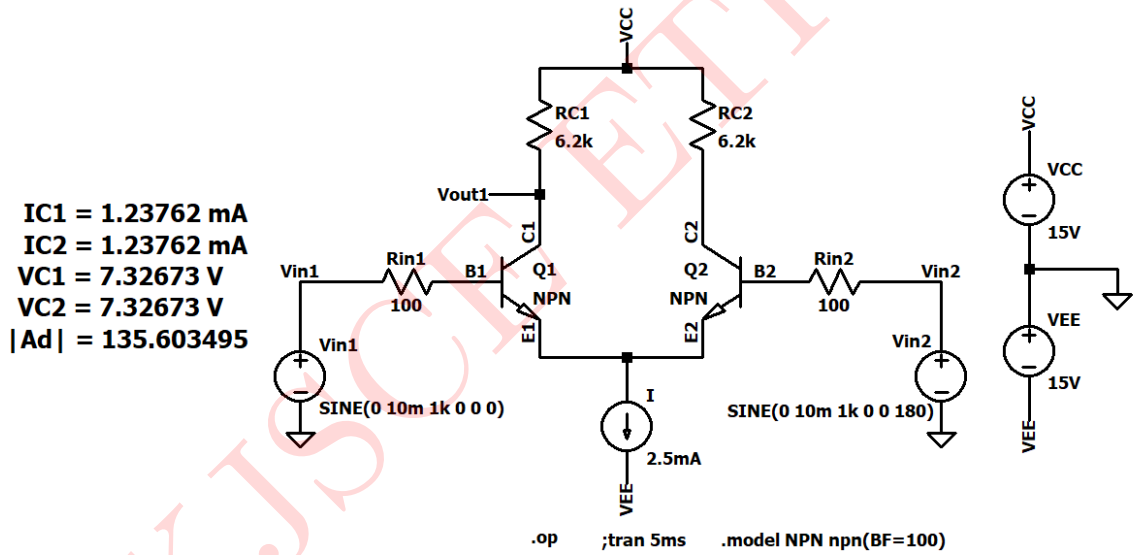


Figure 10: Circuit Schematic 3: Results

The input and output waveforms are shown in figure 11.

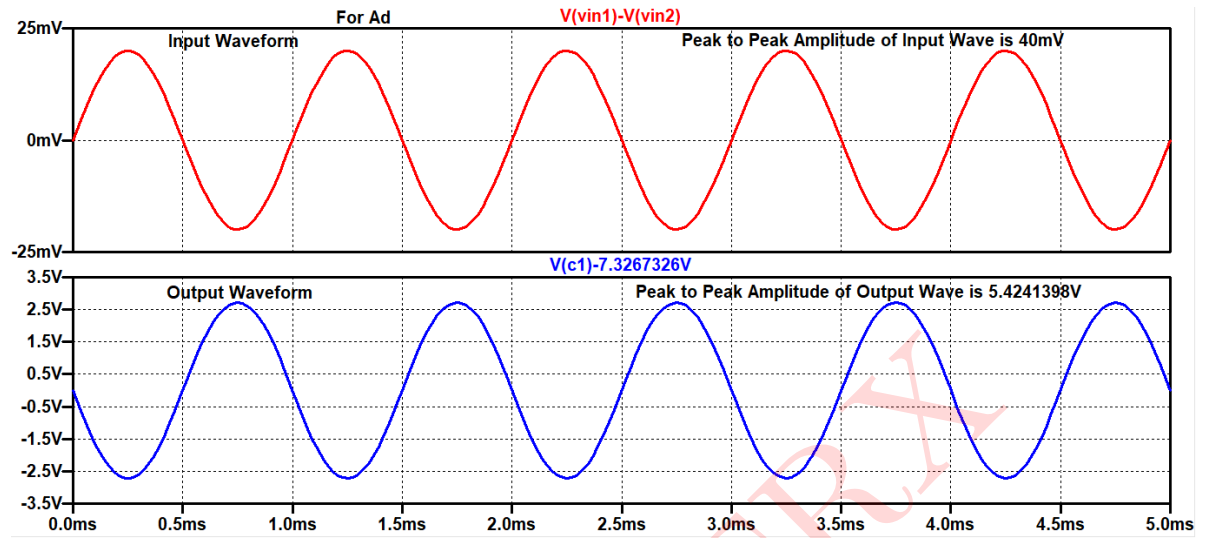


Figure 11: Input & Output waveforms

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{C_1}$	1.23 mA	1.2376 mA
$I_{C_2}$	1.23 mA	1.2376 mA
$V_{C_1}$	7.374 V	7.3267 V
$V_{C_2}$	7.374 V	7.3267 V
Differential voltage gain: $ A_d $	140.27	135.6034

Table 3: Numerical 3

\*\*\*\*\*