

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**AC CIRCUITS**

**Numerical 1:** A series RLC circuit consisting of resistance of  $40\Omega$ , inductance of  $0.3\text{H}$  and capacitor of  $120\mu\text{F}$  are connected in series across a  $120\text{V}$ ,  $60\text{Hz}$  supply.

- Current drawn by the circuit
- $V_R$ ,  $V_L$  and  $V_C$
- Power Factor
- Draw voltage phasor diagram

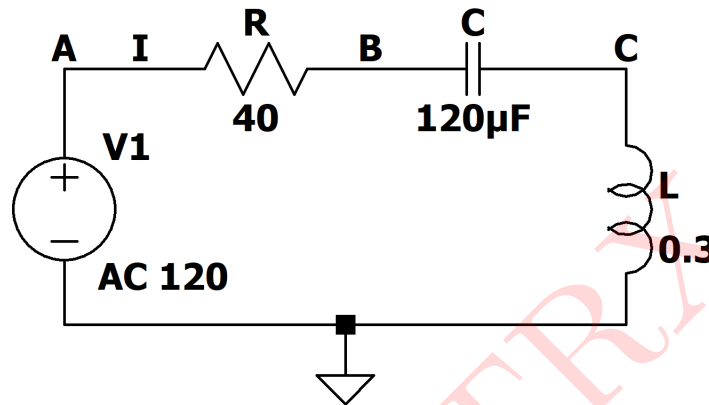


Figure 1: Circuit 1

**Solution:**

$$\begin{aligned} \text{a) } X_L &= 2\pi fL \\ &= 2 \times \pi \times 60 \times 0.3 \\ X_L &= 113.0973\Omega \end{aligned}$$

$$X_C = \frac{1}{2 \times \pi \times 60 \times 120 \times 10^{-6}}$$

$$X_C = 22.1048\Omega$$

$$\begin{aligned} \text{Impedance}(Z) &= \sqrt{R^2 + (X_L - X_C)^2} \\ &= \sqrt{40^2 + (113.0973 - 22.1048)^2} \end{aligned}$$

$$\Phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

$$\Phi = \tan^{-1} \left( \frac{113.0973 - 22.1048}{40} \right)$$

$$\Phi = 66.2698^\circ$$

$$Z = 99.3693 \angle 66.2698^\circ$$

$$I = \frac{V}{Z}$$

$$I = \frac{120}{99.3693 \angle 66.2698^\circ}$$

$$\mathbf{I} = 1.2076 \angle -66.2698^\circ$$

$$\begin{aligned} \text{b) } V_R &= R \times I \\ &= 40 \times 1.2076 \\ V_R &= 48.304V \end{aligned}$$

$$\begin{aligned} V_L &= X_L \times I \\ &= 113.0973 \times 1.2076 \\ V_L &= 136.576V \end{aligned}$$

$$\begin{aligned} V_C &= X_C \times I \\ &= 22.6937 \times 1.2076 \\ V_C &= 26.6937V \end{aligned}$$

$$\begin{aligned} \text{c) Power Factor} &= \cos(\Phi) \\ &= \cos(66.2698) \quad \dots(\text{Lagging}) \\ \mathbf{Power Factor} &= \mathbf{0.4025} \end{aligned}$$

d) Phasor Diagram:

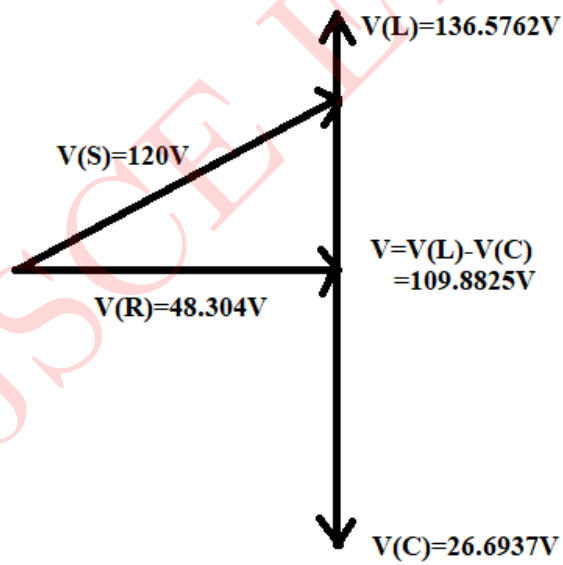


Figure 2: Phasor Diagram

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the result obtained are as follows:

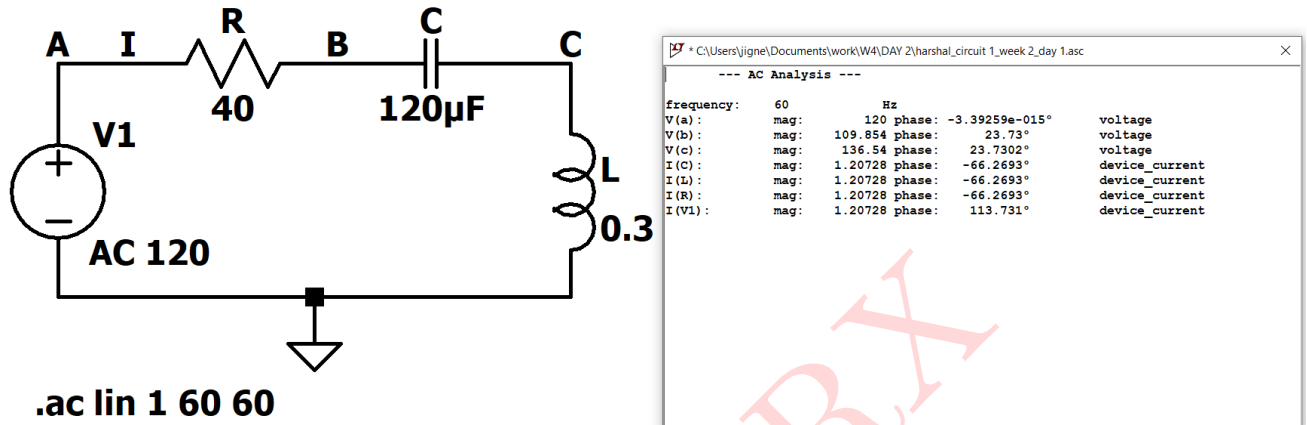


Figure 3: Circuit schematic and Simulated Results

### Comparison of Theoretical and Simulated values:

Parameters	Theoretical Values	Simulated Values
I	$1.2076 \angle 66.269^\circ A$	$1.2072 \angle -66.2693^\circ A$
$V_R$	48.634V	48.2913V
$V_L$	136.5762V	136.54V
$V_C$	26.6937V	26.6868V
Power Factor	0.4025	0.40243

Table 1: Numerical 1

\*\*\*\*\*

**Numerical 2:** A voltage  $V = 100 \sin(314t)$  is applied to a circuit consisting of  $27\Omega$  resistor and  $90\mu F$  capacitor in series. Determine

- An expression for the value of current flowing at any instant
- $V_R$  and  $V_C$
- Power Factor

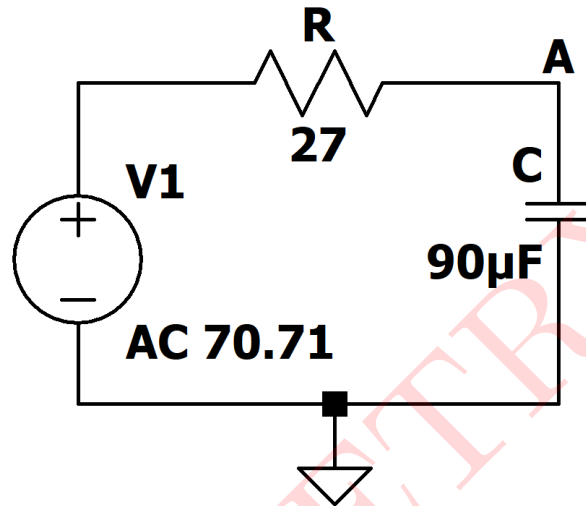


Figure 4: Circuit 2

**Solution:**

$$X_C = \frac{1}{2 \times \pi \times f \times c}$$

$$X_C = \frac{1}{314 \times 90 \times 10^{-6}}$$

$$X_C = 35.3857$$

$$\begin{aligned} \text{Impedance}(Z) &= \sqrt{R^2 + X_C^2} \\ &= \sqrt{27^2 + 35.3857^2} \end{aligned}$$

$$\Phi = \tan^{-1} \left( \frac{X_C}{R} \right)$$

$$\Phi = \tan^{-1} \left( \frac{35.3857}{27} \right)$$

$$\Phi = 52.8112^\circ$$

$$Z = 44.6692 \angle 52.8112^\circ$$

$$I_{RMS} = \frac{V_{RMS}}{Z}$$

$$I_{RMS} = \frac{100}{44}$$

$$I_{RMS} = 2.2727 A$$

$$I = 2.2727 \sin(314t - 52.8112)$$

$$\begin{aligned} \text{b) } V_R &= R \times I \\ &= 27 \times 1.607 \\ V_R &= 43.389V \end{aligned}$$

$$\begin{aligned} V_C &= X_C \times I \\ &= 35 \times 1.607 \\ V_C &= 57.1862V \end{aligned}$$

$$\begin{aligned} \text{c) Power Factor} &= \frac{R}{Z} \\ &= \frac{27}{44.692} \end{aligned}$$

$$\text{Power Factor} = 0.6044W$$

#### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the result obtained are as follows:

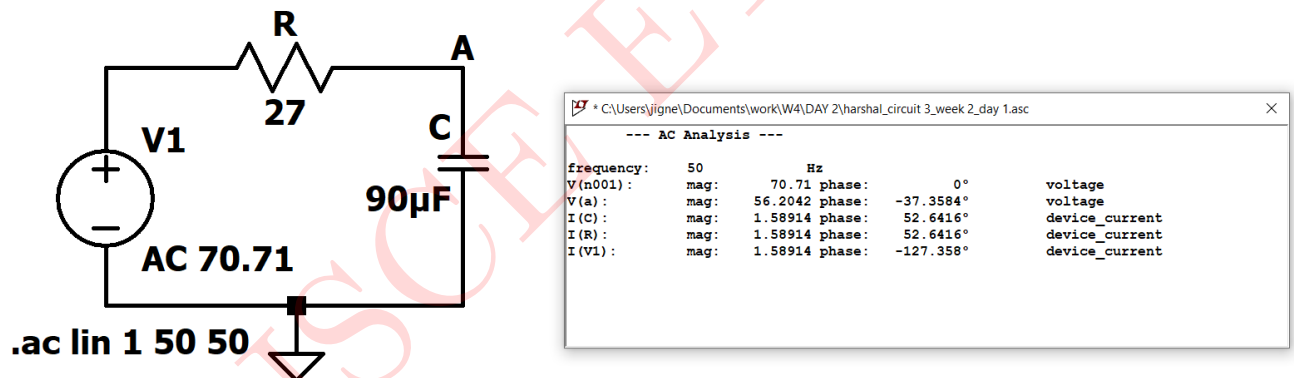


Figure 5: Circuit schematic and Simulated Results

#### Comparison of Theoretical and Simulated values:

Parameters	Theoretical Values	Simulated Values
I	1.607 A	1.58914A
Power Factor	0.6044	0.60679
$V_R$	43.389V	42.9067V
$V_C$	57.1862V	56.2042V

Table 2: Numerical 2

\*\*\*\*\*

**Numerical 3:** A circuit consists of resistance of  $10\Omega$ , an inductor of  $24\text{mH}$  and a capacitor of  $40\mu\text{F}$  are connected in parallel across a  $110\text{V}$ ,  $50\text{Hz}$  supply.

Calculate: a) Individual current by each element

b) Total current

c) Overall Power Factor

d) Phasor Diagram

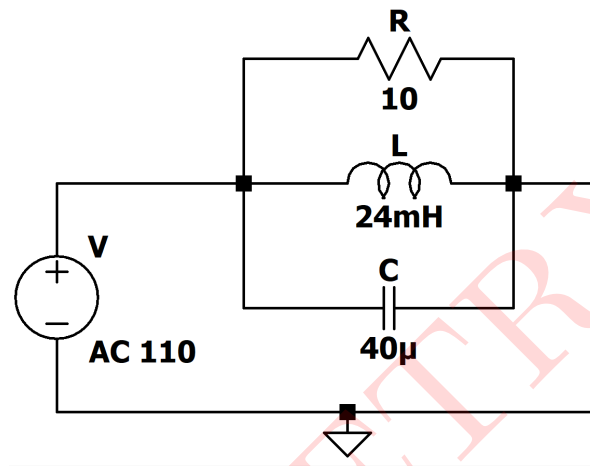


Figure 6: Circuit 3

**Solution:**

$$\begin{aligned} \text{a) } X_L &= 2\pi fL \\ &= 2 \times \pi \times 50 \times 0.024 \\ X_L &= 7.5398\Omega \end{aligned}$$

$$X_C = \frac{1}{2 \times \pi \times 50 \times 40 \times 10^{-6}}$$

$$X_c = 79.5774\Omega$$

$$R = Z_1 = 10\Omega$$

$$Z_2 = jX_L = 7.5398j\Omega$$

$$Z_3 = jX_C = -79.5774j\Omega$$

$$I_1 = \frac{V}{Z_1}$$

$$I_1 = \frac{110}{10}$$

$$I_1 = 11\text{A}$$

$$I_2 = \frac{V}{Z_2}$$

$$I_2 = \frac{110}{7.5398j}\text{A}$$

$$I_2 = 14.5892 \angle -90^\circ \text{A}$$

$$I_3 = \frac{V}{Z_3}$$

$$I_3 = \frac{110}{-79.5774j} A$$

$$I_3 = 1.3826 \angle 90^\circ A$$

b) Total Current:

$$I = I_1 + I_2 + I_3$$

$$I = (11 \angle 0 + 14.5892 \angle -90^\circ + 1.3823 \angle 90^\circ) A$$

$$I = 17.1878 \angle -50.2091^\circ A$$

c) Power Factor:

$$\text{Power Factor} = \cos(\Phi)$$

$$\text{Power Factor} = \cos(50.2091^\circ)$$

$$\text{Power Factor} = 0.6399 \text{ (lagging)}$$

d) Phasor Diagram:

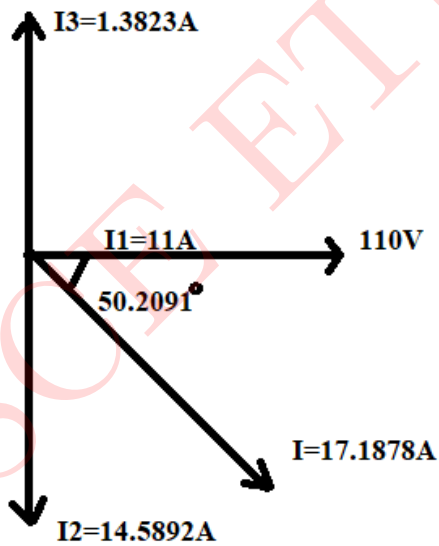


Figure 7: Phasor Diagram

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the result obtained are as follows:

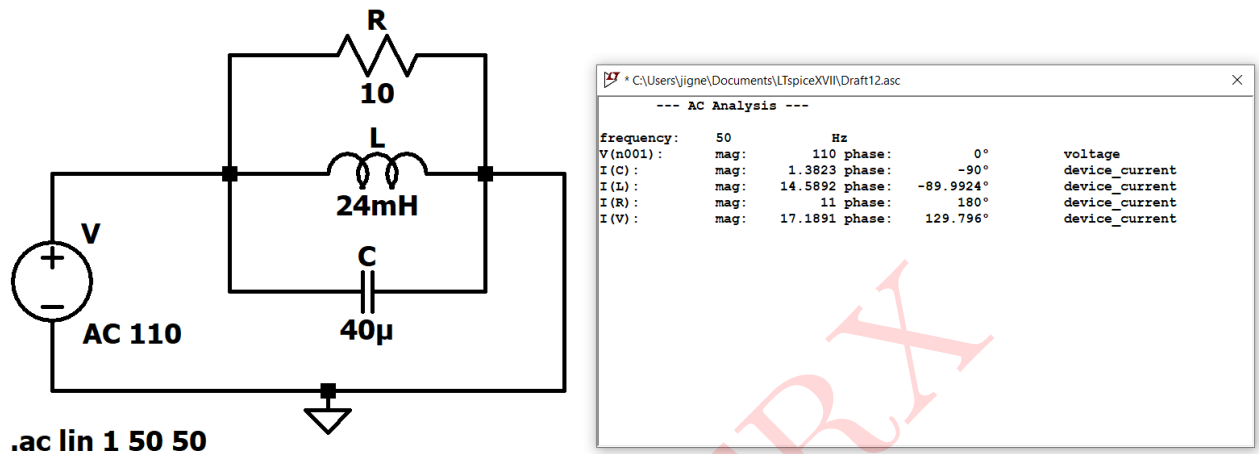


Figure 8: Circuit schematic and Simulated Results

### Comparison of Theoretical and Simulated values:

Parameters	Theoretical Values	Simulated Values
$I_R$	11A	11A
$I_L$	$14.5892 \angle -90^\circ A$	$14.5892 \angle -89.99^\circ A$
$I_C$	$1.3826 \angle 90^\circ A$	$1.3823 \angle 90^\circ A$
Power Factor	0.6399	0.6400

Table 3: Numerical 3

\*\*\*\*\*



**Numerical 4:** A coil having a resistance of  $R_1 = 4.5\Omega$  and inductance of  $L_1 = 0.01H$  is arranged in parallel with another coil having  $R_2 = 2\Omega$  and  $L_2 = 0.06H$ . Calculate  $I$ ,  $I_1$  and  $I_2$  when voltage  $V_1 = 110V$  at  $60Hz$  is applied. Also calculate the power factor.

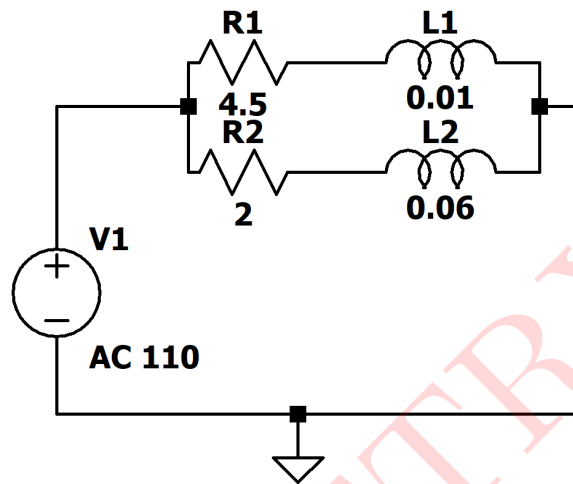


Figure 9: Circuit 4

**Solution:**

$$\begin{aligned} X_{L1} &= 2\pi f L_1 \\ &= 2 \times \pi \times 60 \times 0.01 \\ X_{L1} &= 3.7699\Omega \end{aligned}$$

$$\begin{aligned} X_{L2} &= 2\pi f L_2 \\ &= 2 \times \pi \times 60 \times 0.06 \\ X_{L2} &= 22.6914\Omega \end{aligned}$$

$$\begin{aligned} Z_1 &= R + jX_{L1} \\ Z_1 &= 4.5 + 3.7699j \\ Z_1 &= 5.8704 \angle 39.954^\circ \Omega \end{aligned}$$

$$\begin{aligned} Z_2 &= R + jX_{L2} \\ Z_2 &= 2 + 22.6194j \\ Z_2 &= 22.7076 \angle 84.947^\circ \Omega \end{aligned}$$

$$I_1 = \frac{V}{Z_1}$$

$$I_1 = \frac{110}{5.8704 \angle 39.954^\circ}$$

$$I_1 = 18.7380 \angle -39.954^\circ A$$

$$I_2 = \frac{V}{Z_2}$$

$$I_2 = \frac{110}{22.7076 \angle 84.947^\circ}$$

$$I_2 = 4.8441 \angle -84.947^\circ A$$

Total Current:

$$I = I_1 + I_2$$

$$I = (18.7380\angle -39.54^\circ + 4.8441\angle -84.94^\circ)A$$

$$I = 22.4268\angle -43.7388^\circ A$$

$$\text{Power Factor} = \cos(\Phi)$$

$$\text{Power Factor} = \cos(48.7388^\circ)$$

$$\text{Power Factor} = 0.6594 \text{ (lagging)}$$

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the result obtained are as follows:

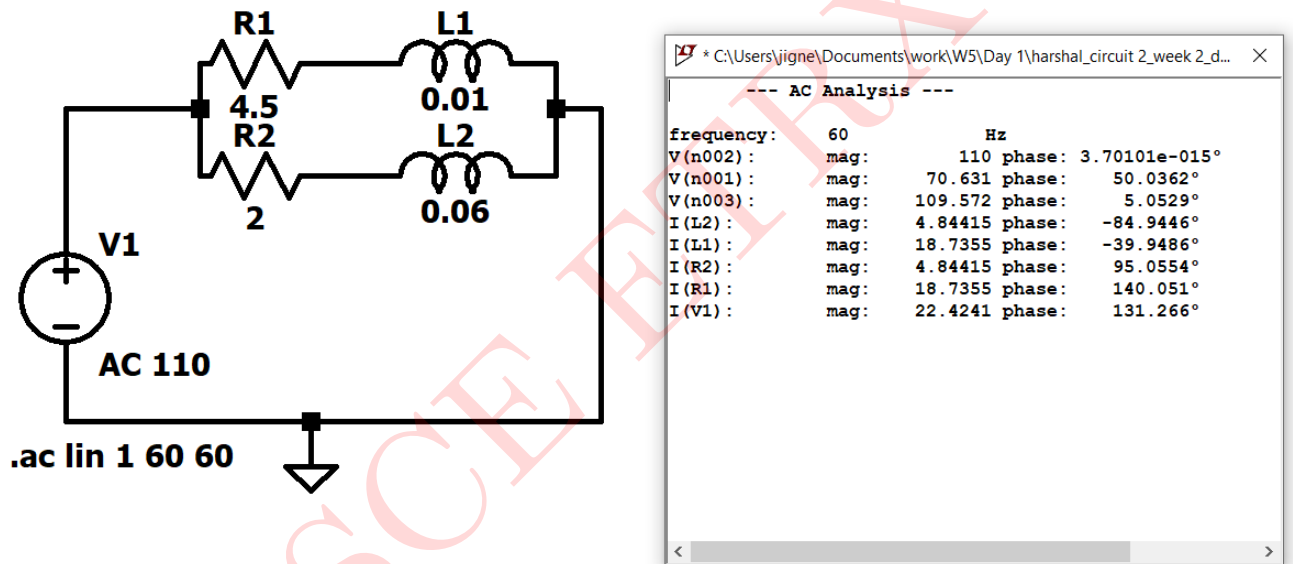


Figure 10: Circuit schematic and Simulated Results

### Comparison of Theoretical and Simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{R1}$	$18.7380\angle -39.954^\circ A$	$18.7355\angle -39.9486^\circ A$
$I_{R2}$	$4.8441\angle -84.947^\circ A$	$4.84415\angle 95.0554^\circ A$
$I_{Total}$	$22.4268\angle -43.7388^\circ A$	$22.4241\angle 131.266^\circ A$
Power Factor	0.6594	0.6595

Table 4: Numerical 4

\*\*\*\*\*

**Numerical 5:** Find  $I$ ,  $I_1$  and  $I_2$  and voltage drop in the circuit 3. If  $R_1 = 6\Omega$ ,  $L_1 = 4j\Omega$ ,  $R_2 = 20\Omega$ ,  $L_2 = 8j\Omega$ ,  $R_3 = 9\Omega$ ,  $C_1 = -6j\Omega$ ,  $V = 100V$  and  $f = 50Hz$ .

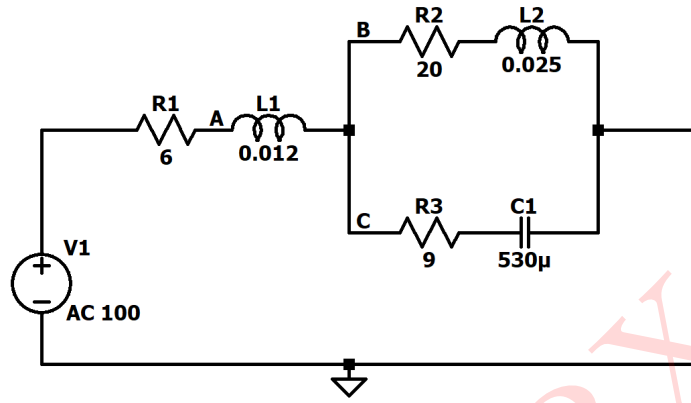


Figure 11: Circuit 5

**Solution:**

$$Z_1 = 6 + 4j = 7.211\angle 33.690^\circ$$

$$Z_2 = 20 + 8j = 21.54\angle 21.801^\circ$$

$$Z_3 = 9 - 6j = 10.8166\angle -33.690^\circ$$

$$Z = Z_1 + \frac{Z_2 \cdot Z_3}{Z_2 + Z_3}$$

$$Z = (6+4j) \times \frac{(20+8j)(9-6j)}{20+8j+9-6j}$$

$$Z = 13.830\angle 7.533^\circ \Omega$$

$$I = \frac{V}{Z}$$

$$I = \frac{100}{13.830\angle 7.533^\circ}$$

$$I = 7.2306\angle -7.533^\circ A$$

By Current Division Rule,

$$I_1 = \frac{I \times Z_3}{Z_2 + Z_3}$$

$$I_1 = \frac{7.2306\angle -7.533^\circ \times 10.8166\angle -33.690^\circ}{10.8166\angle -33.690^\circ + 21.54\angle 21.801^\circ}$$

$$I_1 = 2.6905\angle -10.634^\circ A$$

$$I_2 = I - I_1$$

$$I_2 = 7.2306\angle -7.533^\circ - 2.6905\angle -10.634^\circ$$

$$I_2 = 5.343\angle 44.9071^\circ A$$

Voltage drop across branch B,

$$V_B = I \times Z_1$$

$$V_B = 7.2306 \angle -7.533^\circ \times 7.2111 \angle 33.690^\circ$$

$$V_B = 52.140 \angle 26.157^\circ V$$

Voltage drop across branch C,

$$V_B = I \times \frac{Z_2 \times Z_3}{Z_2 + Z_3}$$

$$V_B = 57.9525 \angle -23.66^\circ V$$

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the result obtained are as follows:

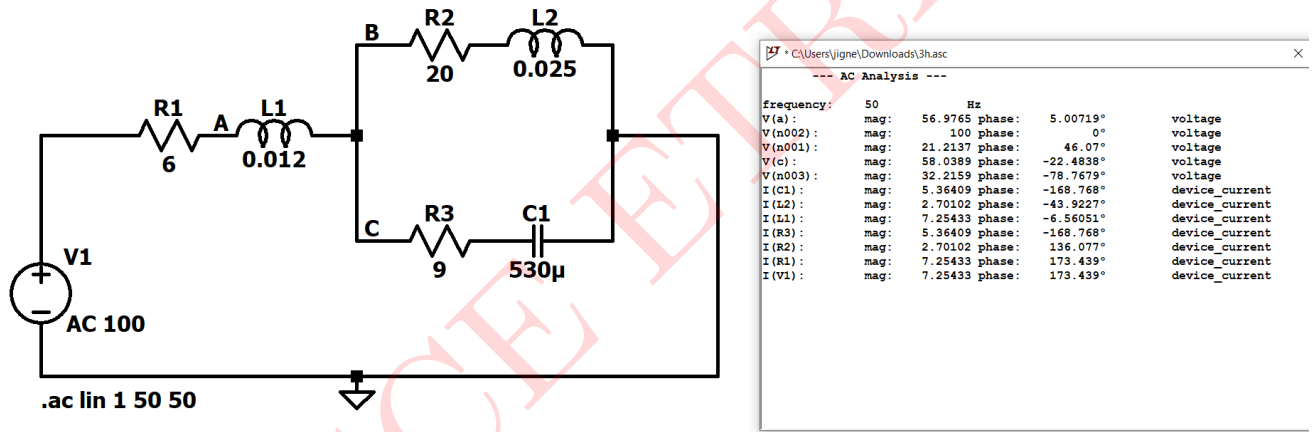


Figure 12: Circuit schematic and Simulated Results

### Comparison of Theoretical and Simulated values:

Parameters	Theoretical Values	Simulated Values
I	$7.2306 \angle -7.533^\circ A$	$7.254 \angle -6.5605^\circ A$
$I_1$	$2.6905 \angle -10.634^\circ A$	$2.7010 \angle -43.9227^\circ A$
$I_2$	$5.343 \angle 44.9071^\circ A$	$5.3640 \angle -168.768^\circ A$
$V_B$	$52.140 \angle 26.157^\circ V$	$56.9765 \angle 5.00719^\circ V$
$V_C$	$57.9525 \angle -23.66^\circ V$	$58.0389 \angle -22.4838^\circ V$

Table 5: Numerical 5

\*\*\*\*\*

**Numerical 6:** A 60Hz sinusoidal voltage  $V = 141 \sin \omega t$  is applied to a series R-L circuit. The values of resistance and inductor are  $4\Omega$  and  $0.02\text{H}$ .

- Calculate peak voltage across resistor and inductor and also find the peak value of source current.
- Plot  $V_S(t)$  vs  $I_S(t)$
- Measure phase delay between  $V_S(t)$  and  $I_S(t)$
- Plot  $V_S(t)$  vs  $V_R(t)$
- Measure phase delay between  $V_S(t)$  and  $V_R(t)$
- Plot  $V_S(t)$  vs  $V_L(t)$
- Measure phase delay between  $V_S(t)$  and  $V_L(t)$
- Calculate the Power Factor

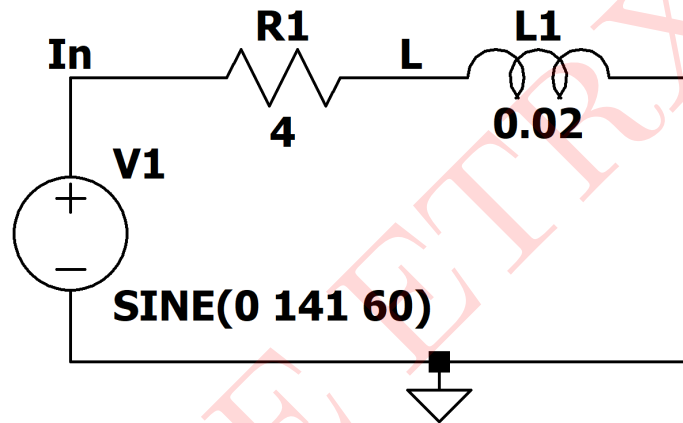


Figure 13: Circuit 6

**Solution:**

$$\begin{aligned} \text{a) } X_L &= 2\pi f \times L_1 \\ &= 2 \times \pi \times 60 \times 0.02 \\ X_L &= 7.539\Omega \end{aligned}$$

$$\begin{aligned} \text{Impedance}(Z) &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{4^2 + 7.539^2} \end{aligned}$$

$$\Phi = \tan^{-1} \left( \frac{X_{L1}}{R_1} \right)$$

$$\Phi = \tan^{-1} \left( \frac{7.539}{4} \right)$$

$$\Phi = 63.05^\circ$$

$$Z = 8.534 \angle 63.05^\circ$$

$$I_{peak} = \frac{V_{peak}}{Z}$$

$$I_{peak} = \frac{141}{8.534 \angle 63.05^\circ}$$

$$I_{peak} = 16.5221 \angle -63.05^\circ \text{ A}$$

$$\begin{aligned}\text{Peak value of voltage across resistor} &= I_{peak} \times R \\ &= 66.0884 \angle -63.050^\circ \text{ V}\end{aligned}$$

$$\begin{aligned}\text{Peak value of voltage across inductor} &= I_{peak} \times X_L \\ &= 124.5601 \angle 26.95^\circ \text{ V}\end{aligned}$$

b)  $V_S(t)$  vs  $I_S(t)$

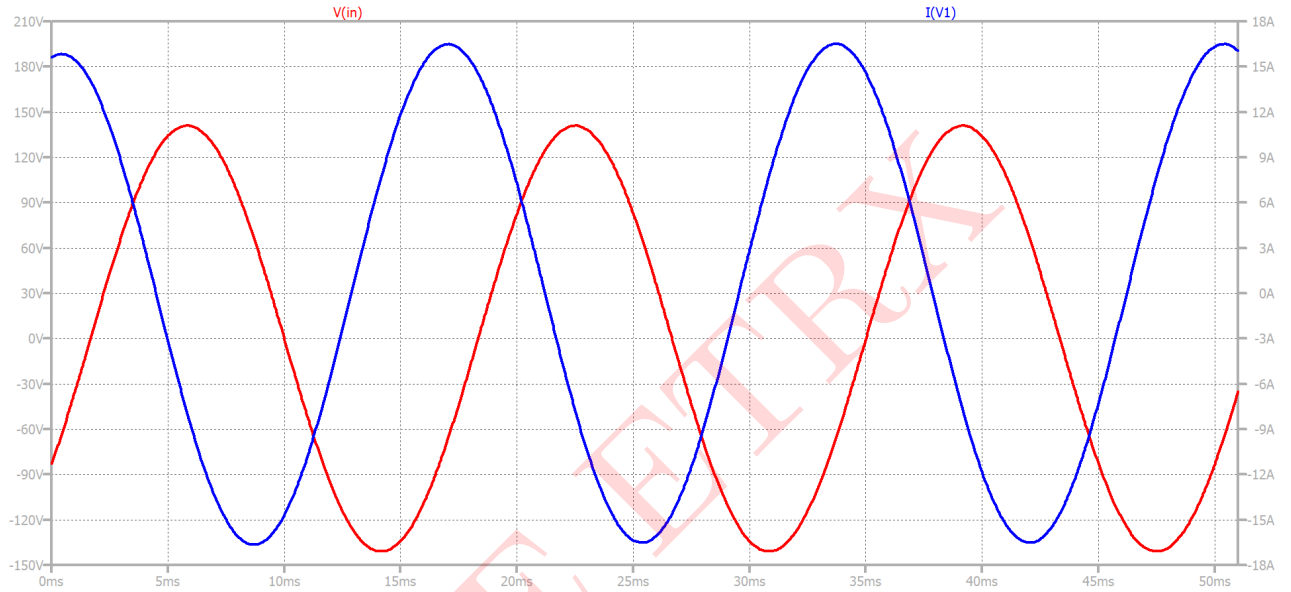


Figure 14: Plot of  $V_S(t)$  vs  $I_S(t)$

c) Phase delay between  $V_S(t)$  vs  $I_S(t)$ :

$$V = 140 \angle 0^\circ$$

$$I = 16.5221 \angle -63.050^\circ \text{ A}$$

$$\phi = 180 - 63.05^\circ$$

$$\phi = 116.95^\circ$$

$$\Delta t = \frac{\phi}{T}$$

$$\Delta t = \frac{116.95^\circ \times 20}{360^\circ}$$

$$\Delta t = 6.4972 \text{ ms}$$

d)  $V_S(t)$  vs  $V_R(t)$

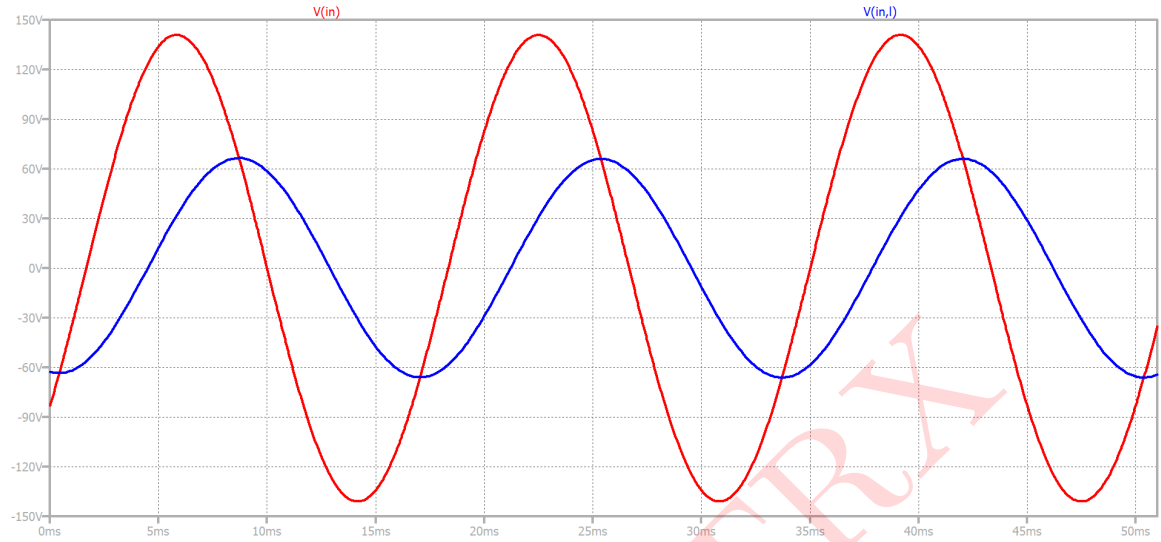


Figure 15: Plot of  $V_S(t)$  vs  $V_R(t)$

e) Phase delay between  $V_S(t)$  vs  $V_R(t)$ :

$$V = 140\angle 0^\circ$$

$$V_R = 66.0884\angle -63.050^\circ \text{ V}$$

$$\phi = 63.05^\circ$$

$$\Delta t = \frac{\phi}{T}$$

$$\Delta t = \frac{63.05^\circ \times 20}{360^\circ}$$

$$\Delta t = 3.50277\text{ms}$$

f)  $V_S(t)$  vs  $V_L(t)$

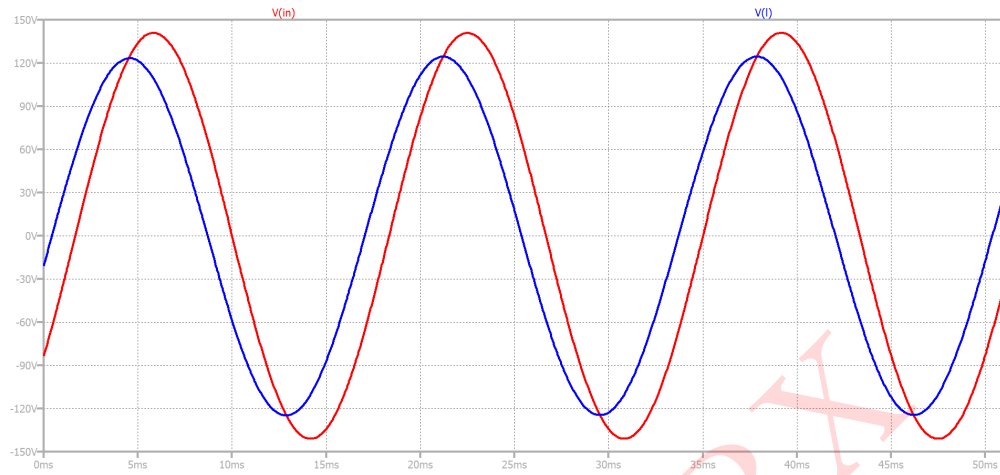


Figure 16: Plot of  $V_S(t)$  vs  $V_L(t)$

g) Phase delay between  $V_S(t)$  vs  $V_L(t)$ :

$$V = 140\angle 0^\circ$$

$$V_L = 124.5601\angle 26.95^\circ \text{ V}$$

$$\phi = 26.95^\circ$$

$$\Delta t = \frac{\phi}{T}$$

$$\Delta t = \frac{26.95^\circ \times 20}{360^\circ}$$

$$\Delta t = 1.49722 \text{ ms}$$

h) Power Factor :

$$\text{Power Factor} = \cos(\Phi)$$

$$\text{Power Factor} = \cos(63.050^\circ)$$

$$\text{Power Factor} = 0.4532 \text{ (lagging)}$$



### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the result obtained are as follows:

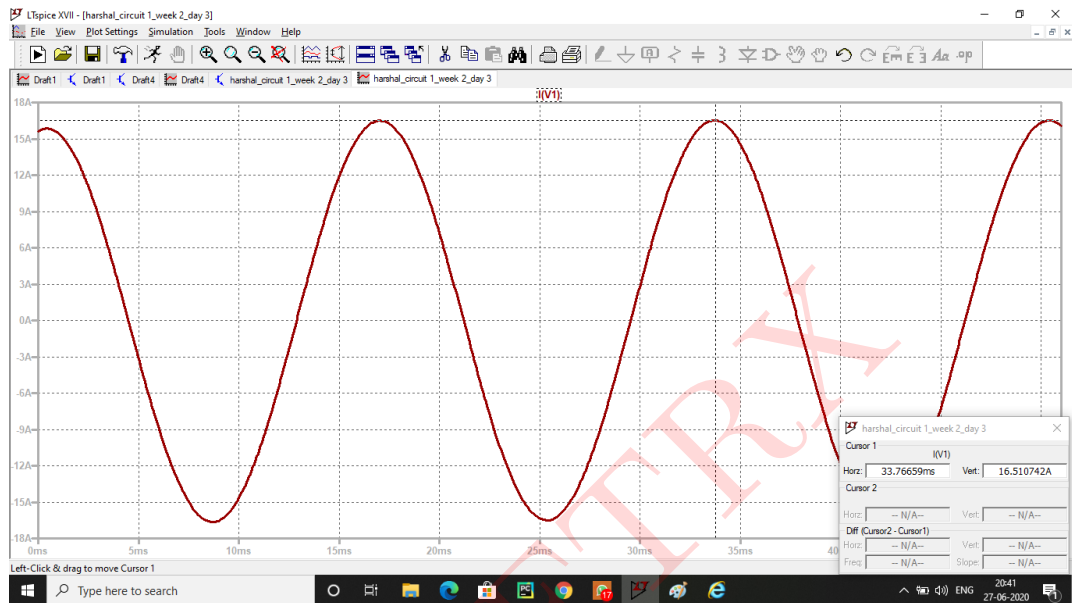


Figure 17: Simulated Results of Source Current

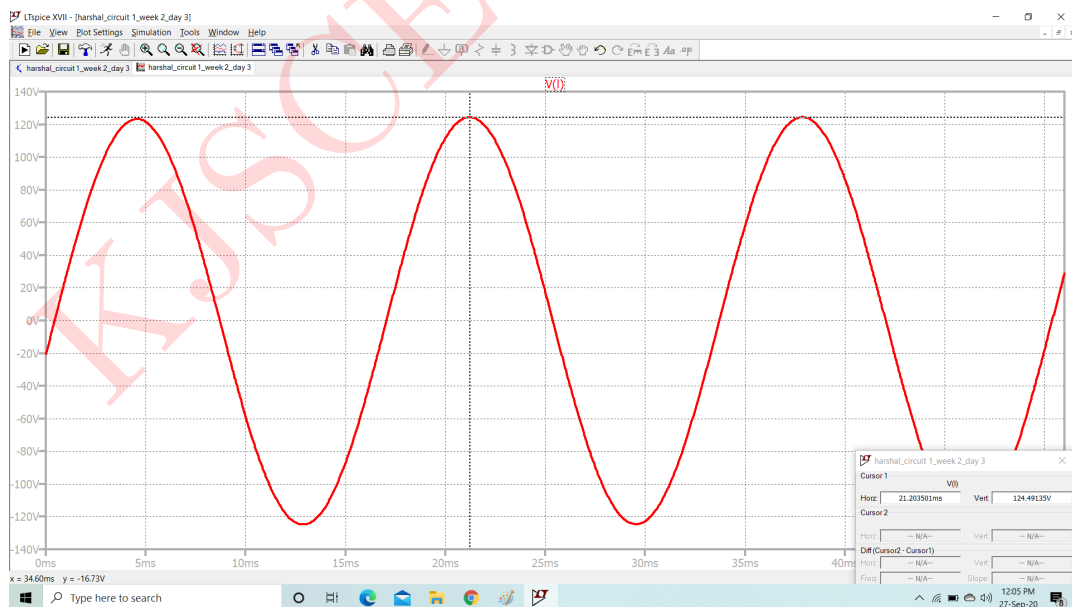


Figure 18: Simulated Results of Voltage across Resistor

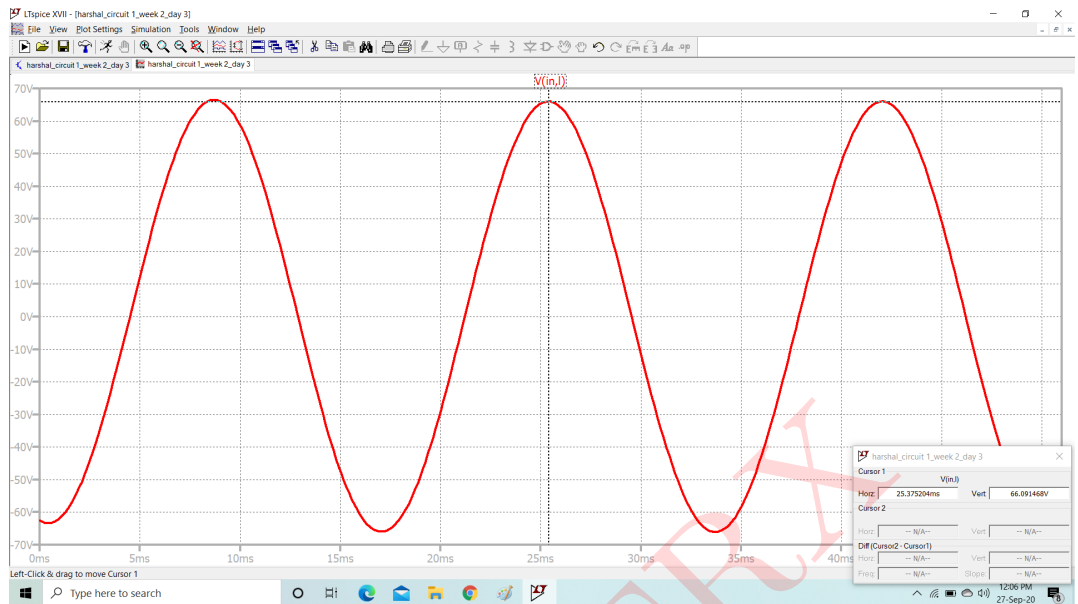


Figure 19: Simulated Results of Voltage across Inductor

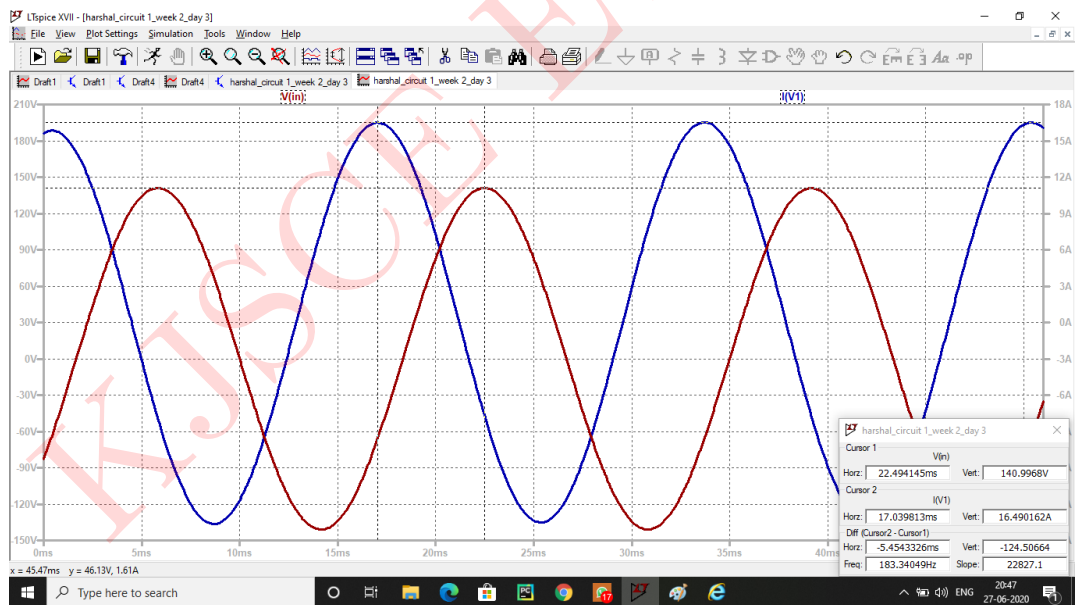


Figure 20: Simulated Results of Voltage for  $V_S(t)$  vs  $I_S(t)$

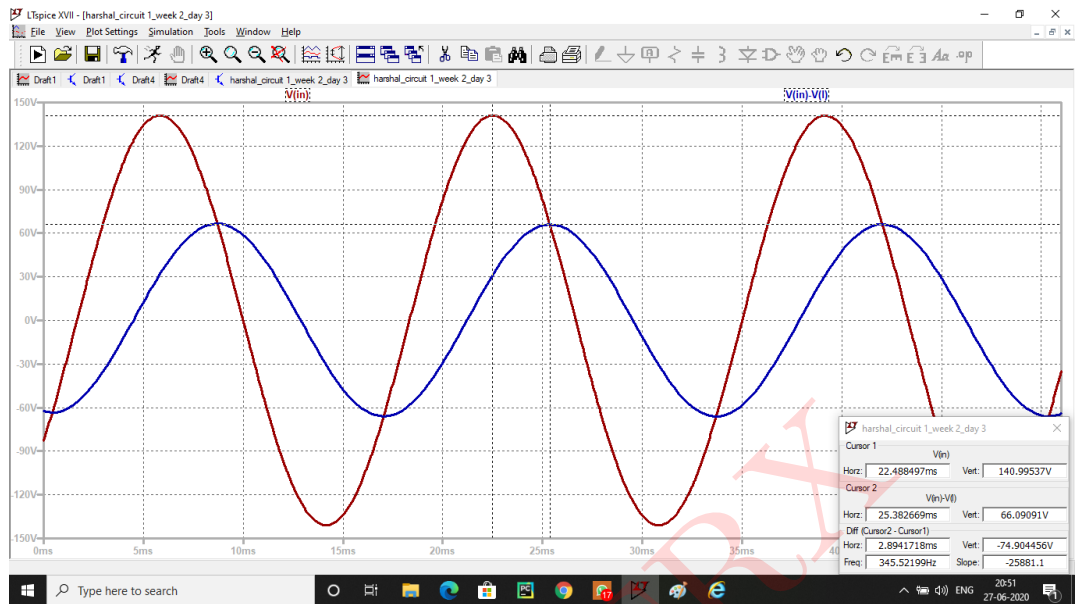


Figure 21: Simulated Results of Voltage for  $V_S(t)$  vs  $V_R(t)$

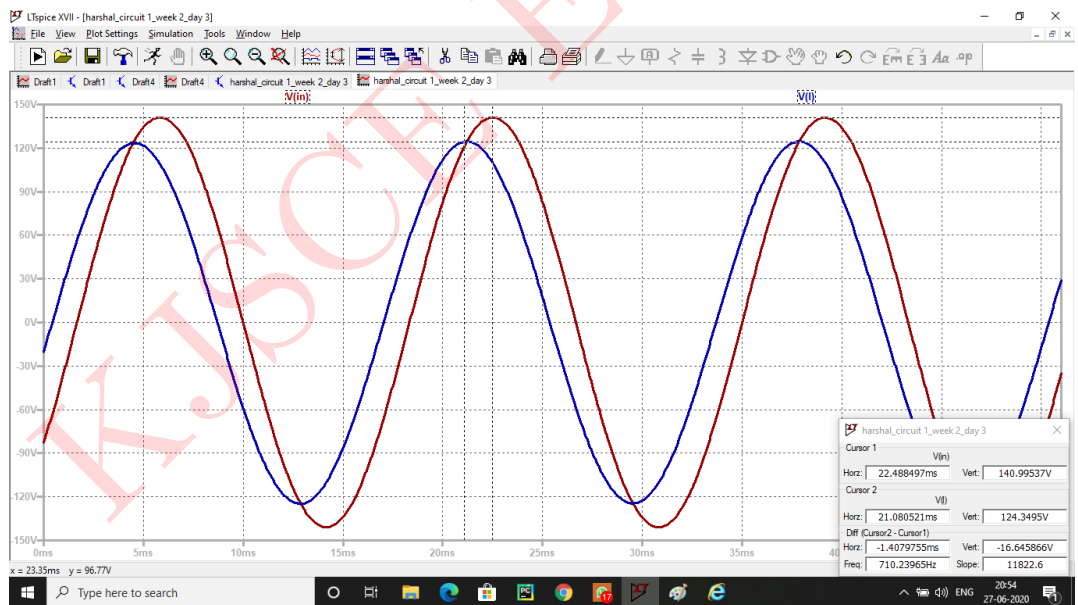


Figure 22: Simulated Results of Voltage for  $V_S(t)$  vs  $V_L(t)$

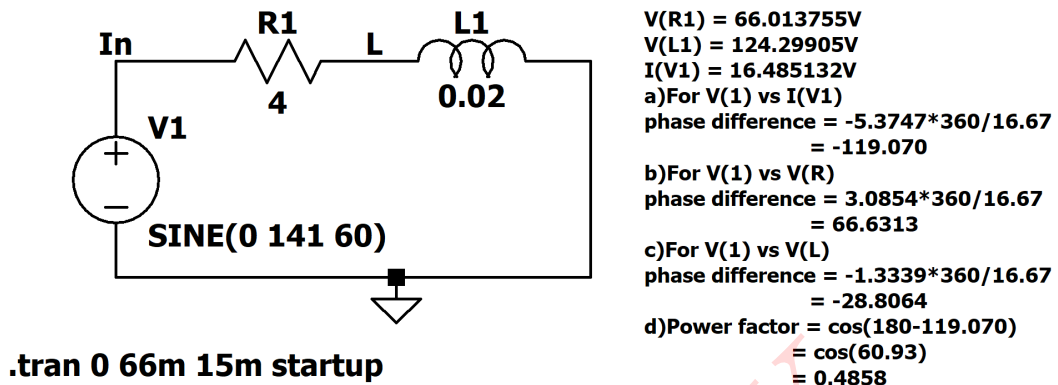


Figure 23: Simulated Circuit

#### Comparison of Theoretical and Simulated values:

Parameters	Theoretical Values	Simulated Values
Peak Voltage(Resistor)	66.0884V	66.013755V
Peak Voltage(Inductor)	124.5601V	124.29905V
Peak Value(Source Current)	16.5221A	16.485132A
Phase difference $V_S(t)$ vs $I_S(t)$	$63.050^\circ$ , 6.4972ms	$60.93^\circ$ , 5.4554ms
Phase difference $V_S(t)$ vs $V_R(t)$	$63.050^\circ$ , 3.50277ms	$63.050^\circ$ , 2.89417ms
Phase difference $V_S(t)$ vs $V_L(t)$	$26.95^\circ$ , 1.49722ms	$28.80^\circ$ , 1.40797ms
Power Factor	0.4532(lagging)	0.4858(lagging)

Table 6: Numerical 6

\*\*\*\*\*

**Numerical 7:** A pure resistor of  $30\Omega$  in series with capacitor of  $100\mu F$ . It is connected across  $120V, 50Hz$ .

- Calculate peak voltage across resistor and capacitor and also find the peak value of peak current.
- Plot  $V_S(t)$  vs  $I_S(t)$
- Measure phase difference between  $V_S(t)$  and  $I_S(t)$
- Plot  $V_S(t)$  vs  $V_R(t)$
- Measure phase difference between  $V_S(t)$  and  $V_R(t)$
- Plot  $V_S(t)$  vs  $V_C(t)$
- Measure phase delay between  $V_S(t)$  and  $V_C(t)$
- Calculate the Power Factor

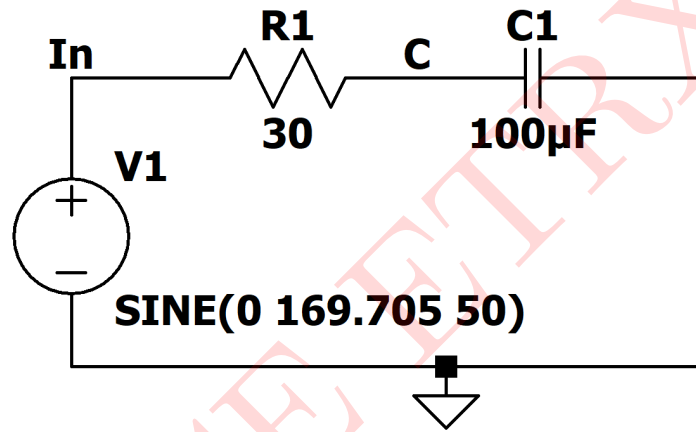


Figure 24: Circuit 7

**Solution:**

$$X_{C1} = \frac{1}{2 \times \pi \times f \times C_1}$$

$$X_{C1} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}}$$

$$X_{C1} = 31.8359\Omega$$

$$\begin{aligned} \text{Impedance}(Z) &= \sqrt{R^2 + X_C^2} \\ &= \sqrt{30^2 + 31.8359^2} \end{aligned}$$

$$\Phi = \tan^{-1} \left( \frac{X_{C1}}{R_1} \right)$$

$$\Phi = \tan^{-1} \left( \frac{31.8359}{30} \right)$$

$$\Phi = 46.6961^\circ$$

$$Z = 43.7402 \angle 46.6961^\circ$$

$$I_{peak} = \frac{V_{peak}}{Z}$$

$$I_{peak} = \frac{120 \times 1.414}{43.7402 \angle -46.6961^\circ} A$$

$$I_{peak} = 3.8798 \angle -46.6961$$

$$\begin{aligned} \text{Peak value of voltage across resistor} &= I_{peak} \times R \\ &= 116.394 \angle -46.6961^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} \text{Peak value of voltage across capacitor} &= I_{peak} \times X_C \\ &= 123.4975 \angle -136.6961^\circ \text{ V} \end{aligned}$$

b)  $V_S(t)$  vs  $I_S(t)$

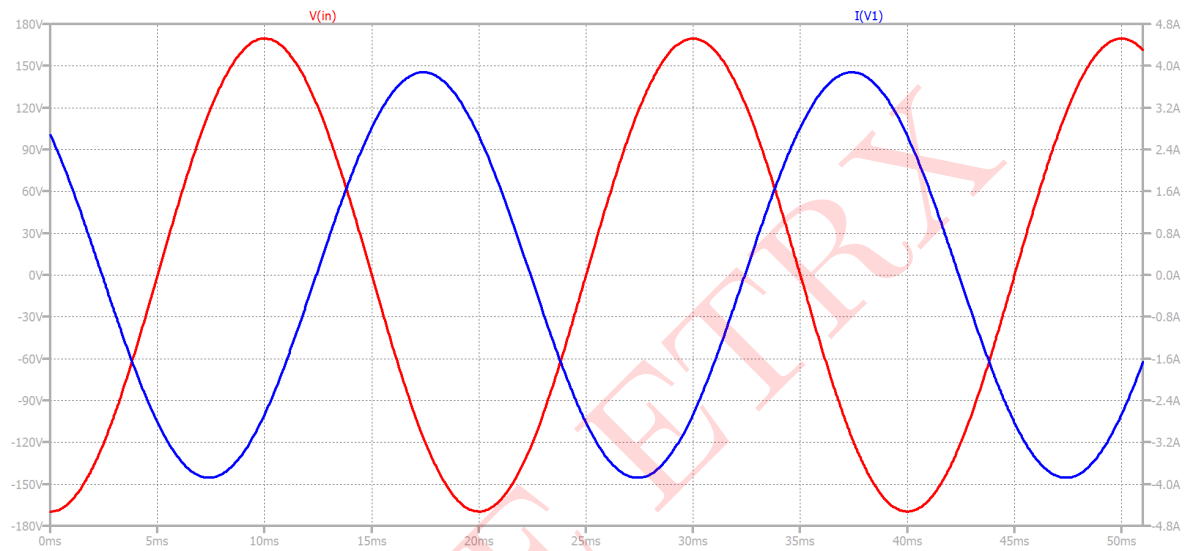


Figure 25: Plot of  $V_S(t)$  vs  $I_S(t)$

c) Phase delay between  $V_S(t)$  vs  $I_S(t)$ :

$$V = 12 \angle 0^\circ$$

$$I = 3.8798 \angle -46.6961$$

$$\phi = 180 - 46.6961^\circ$$

$$\phi = 133.3039^\circ$$

$$\Delta t = \frac{\phi}{T}$$

$$\Delta t = \frac{133.30395^\circ \times 20}{360^\circ}$$

$$\Delta t = 7.4057 \text{ ms}$$

d)  $V_S(t)$  vs  $V_R(t)$

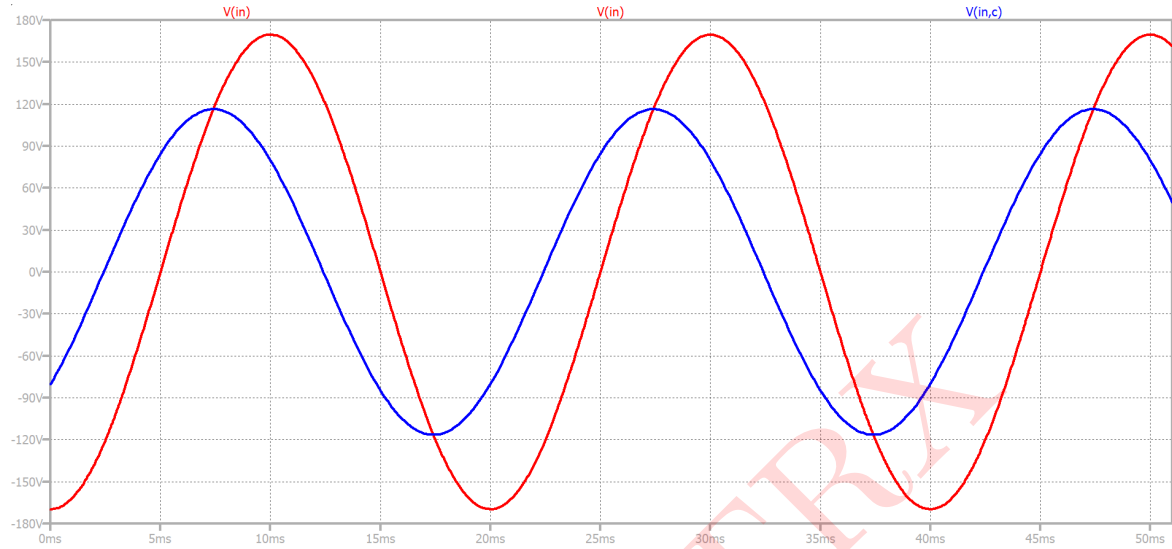


Figure 26: Plot of  $V_S(t)$  vs  $V_R(t)$

e) Phase delay between  $V_S(t)$  vs  $V_R(t)$ :

$$V = 140\angle 0^\circ$$

$$V_R = 116.394\angle -46.6961^\circ \text{ V}$$

$$\phi = 46.6961^\circ$$

$$\Delta t = \frac{\phi}{T}$$

$$\Delta t = \frac{46.6961^\circ \times 20}{360^\circ}$$

$$\Delta t = 2.5942\text{ms}$$

f)  $V_S(t)$  vs  $V_C(t)$

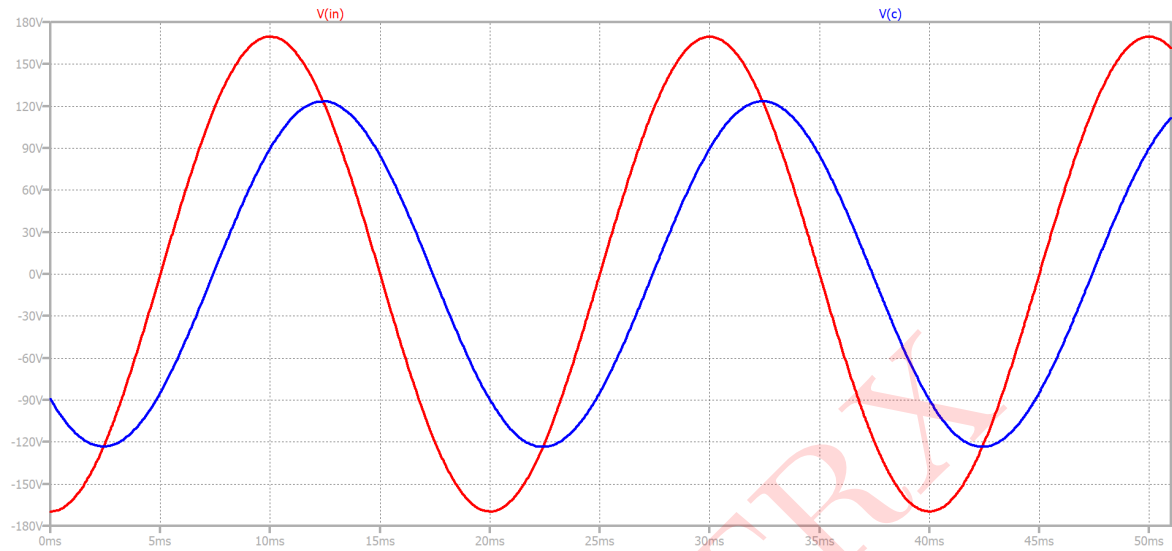


Figure 27: Plot of  $V_S(t)$  vs  $V_C(t)$

g) Phase delay between  $V_S(t)$  vs  $V_C(t)$ :

$$V = 140 \angle 0^\circ$$

$$V_C = 123.4975 \angle -136.6961^\circ \text{ V}$$

$$\phi = 43.3039^\circ$$

$$\Delta t = \frac{\phi}{T}$$

$$\Delta t = \frac{43.3039^\circ \times 20}{360^\circ}$$

$$\Delta t = 2.40577 \text{ ms}$$

h) Power Factor :

$$\text{Power Factor} = \cos(\Phi)$$

$$\text{Power Factor} = \cos(46.6961^\circ)$$

$$\text{Power Factor} = 0.6858$$



## SIMULATED RESULTS:

The given circuit is simulated in LTspice and the result obtained are as follows:

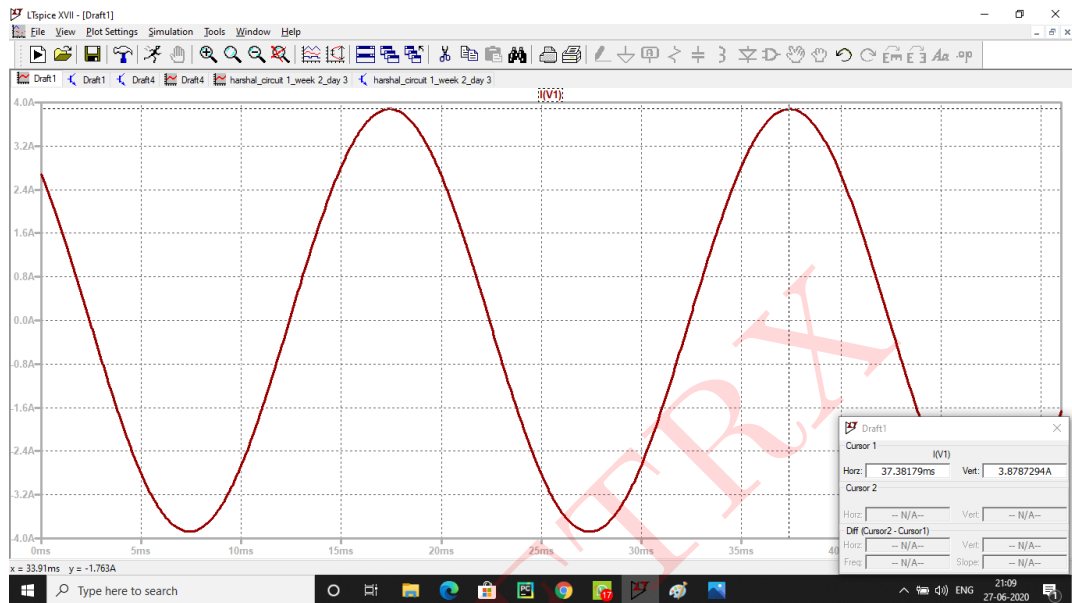


Figure 28: Simulated Results of Source Current

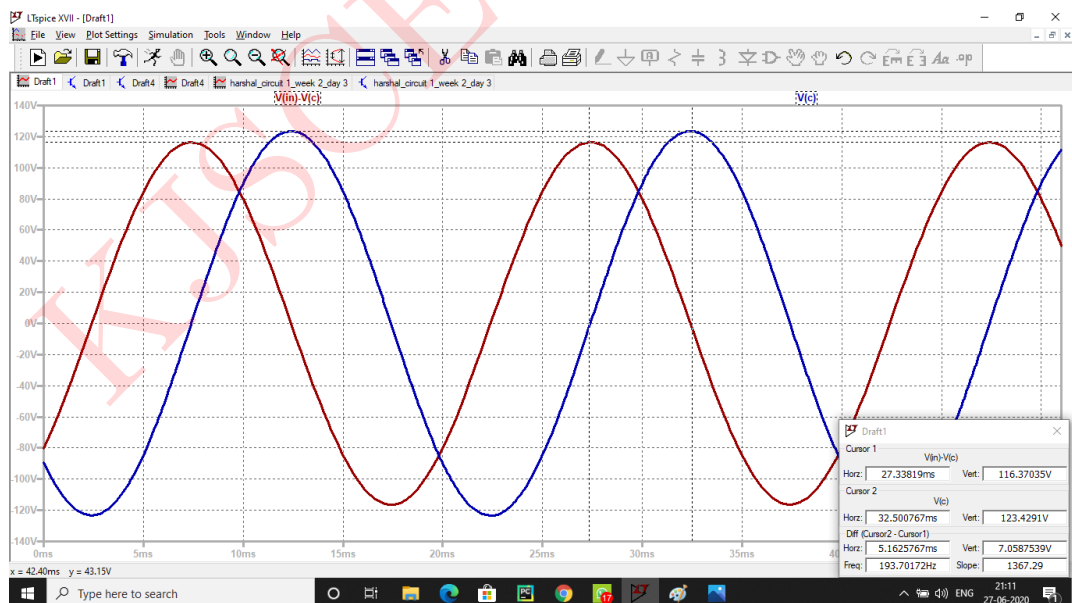


Figure 29: Simulated Results of Voltage across Resistor and Capacitor

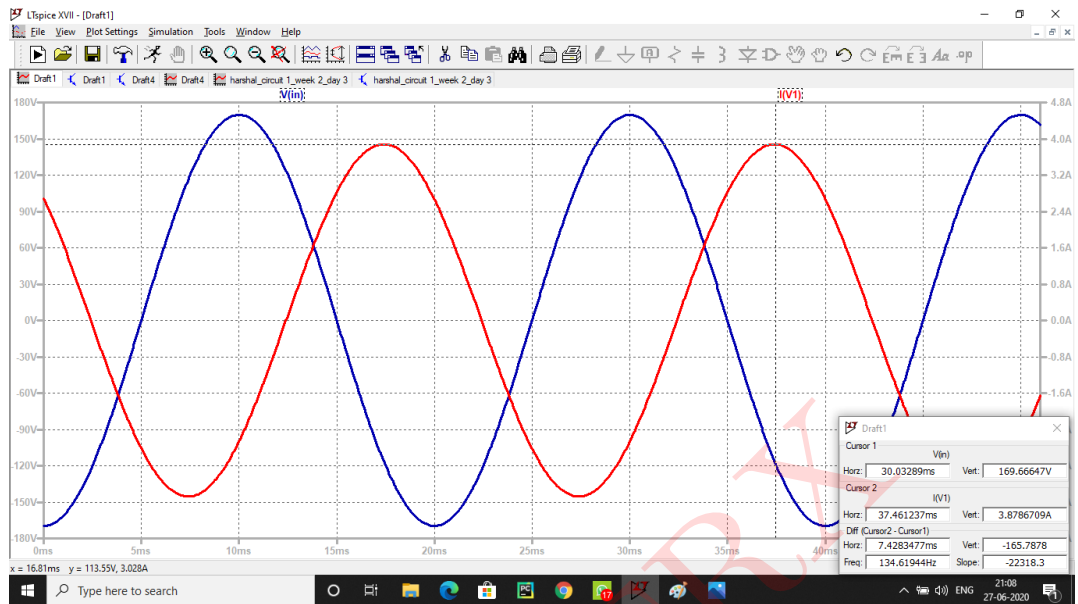


Figure 30: Simulated Results of Voltage for  $V_S(t)$  vs  $I_S(t)$

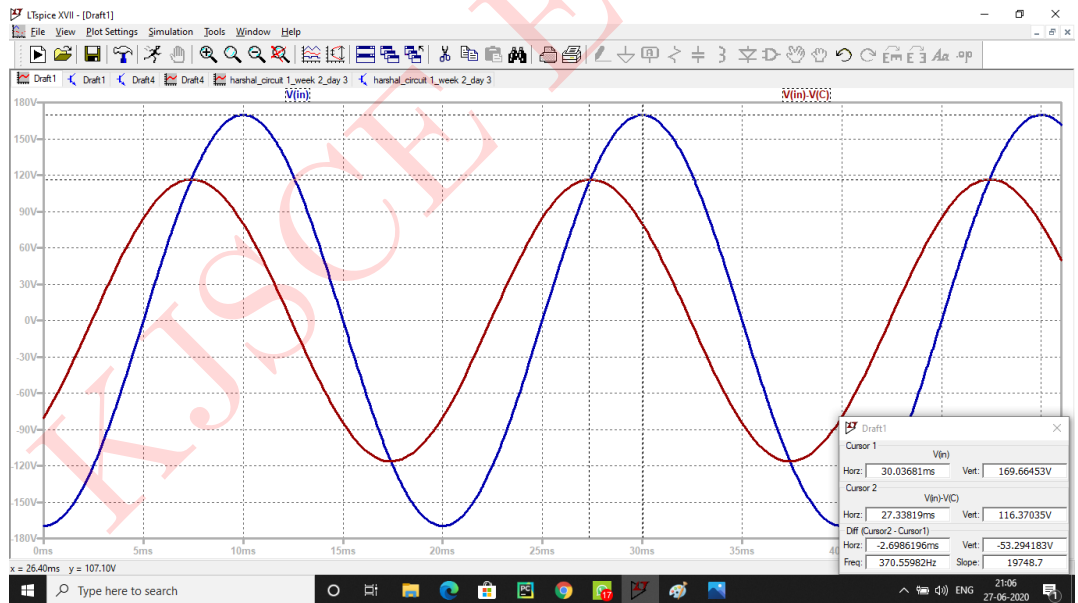


Figure 31: Simulated Results of Voltage for  $V_S(t)$  vs  $V_R(t)$

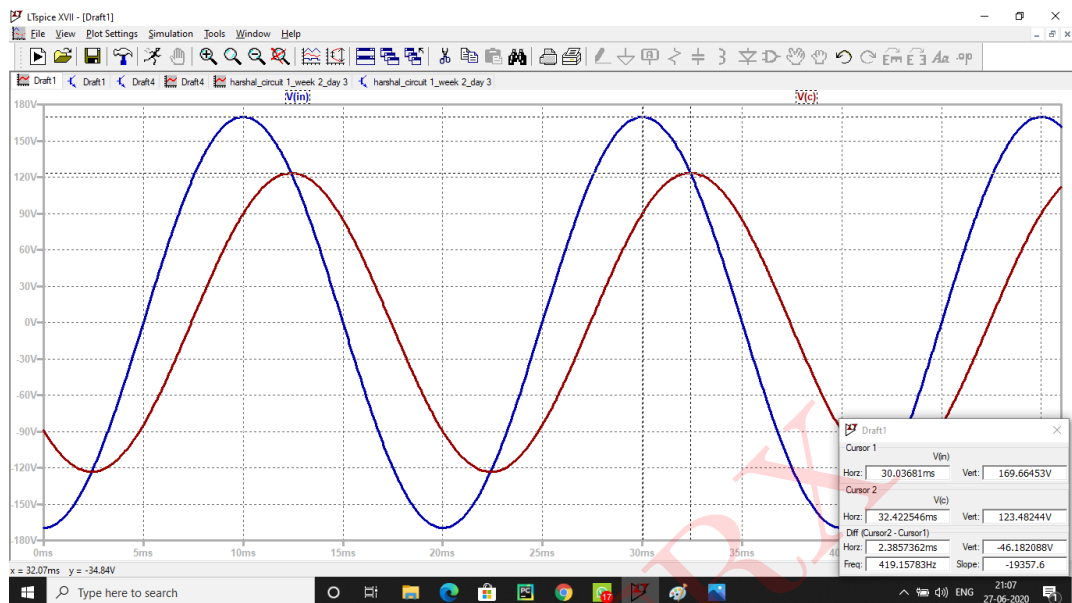


Figure 32: Simulated Results of Voltage for  $V_S(t)$  vs  $V_C(t)$

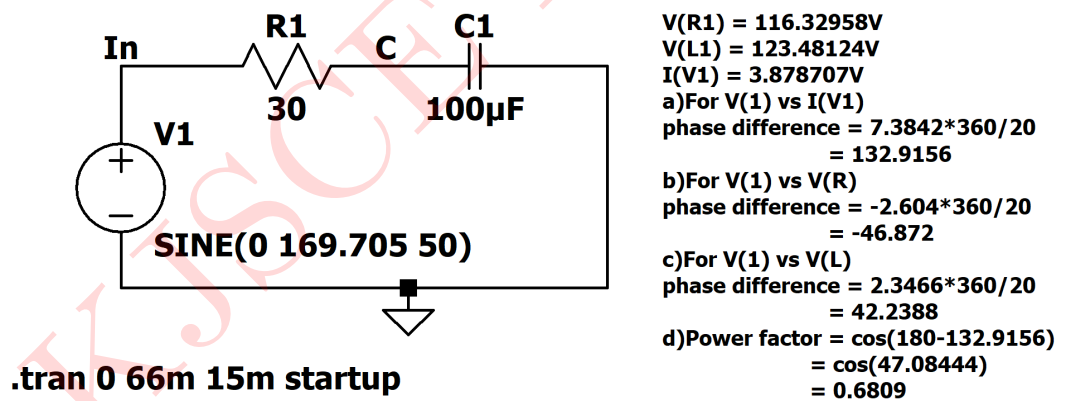


Figure 33: Simulated Circuit

**Comparison of Theoretical and Simulated values:**

Parameters	Theoretical Values	Simulated Values
Peak Voltage(Resistor)	116.394V	116.3295V
Peak Voltage(Capacitor)	123.4975V	123.4812V
Peak Value(Source Current)	3.8798A	3.8787A
Phase difference $V_S(t)$ vs $I_S(t)$	$46.6961^\circ$ , $7.4057ms$	$47.0844^\circ$ , $7.4283ms$
Phase difference $V_S(t)$ vs $V_R(t)$	$-46.6961^\circ$ , $2.5942ms$	$-46.872^\circ$ , $2.6986ms$
Phase difference $V_S(t)$ vs $V_C(t)$	$43.3039^\circ$ , $2.40577ms$	$42.2388^\circ$ , $2.3857ms$
Power Factor	0.6858	0.6809

Table 7: Numerical 7

\*\*\*\*\*

**Numerical 8:** A series resonance network consisting of  $40\Omega$  resistor,  $3\mu F$  capacitor and  $35mH$  inductor is connected to sinusoidal supply of AC 9Volts. Calculate resonant frequency, current at resonance, voltage across inductor and capacitor at resonance quality factor and bandwidth.

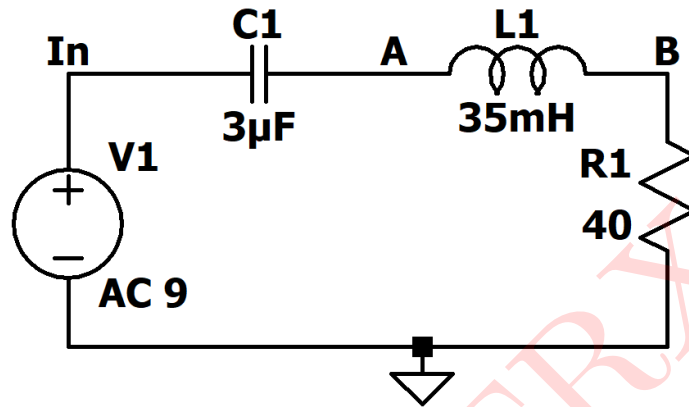


Figure 34: Circuit 8

**Solution:**

$$\text{Resonant frequency} = \frac{1}{2\pi\sqrt{L_1 C_1}}$$

$$\text{Resonant frequency} = \frac{1}{2\pi\sqrt{35 \times 10^{-3} \times 3 \times 10^{-6}}}$$

$$\text{Resonant frequency (f}_0\text{)} = 491.162Hz$$

Current at resonance

$$I_{rms} = \frac{V}{R_1}$$

$$I_{rms} = \frac{9}{40}$$

$$I_{rms} = 225mA$$

$$I_{peak} = I_{rms} \times \sqrt{2}$$

$$I_{peak} = 318.198A$$

At resonance voltage through L and C are same

$$V_c = V_L$$

$$V_L = I \times X_L$$

$$V_L = 225 \times 10^{-3} \times 2\pi \times 491.162 \times 35 \times 10^{-3}$$

$$(V_L)_{peak} = (V_C)_{peak} = (V_L)_{rms} \times \sqrt{2} = 34.3692V$$

$$\text{Quality Factor} = \frac{X_L}{R}$$

$$\text{Quality Factor} = \frac{2\pi 491.162 \times 35 \times 10^{-3}}{40}$$

$$\text{Quality Factor} = 2.7$$

$$\text{Bandwidth} = \frac{F_0}{Q}$$

$$\text{Bandwidth} = \frac{491.161}{2.7}$$

$$\text{Bandwidth} = 181.9118\text{Hz}$$

Graph of current at resonance

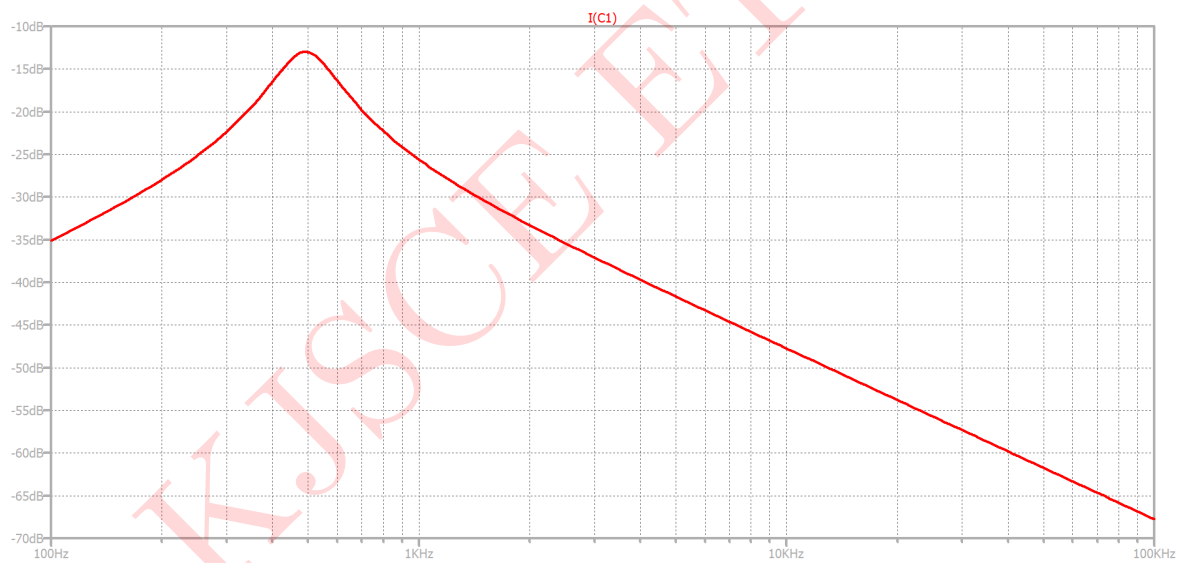


Figure 35: Current at resonance

Graph of resonance curve

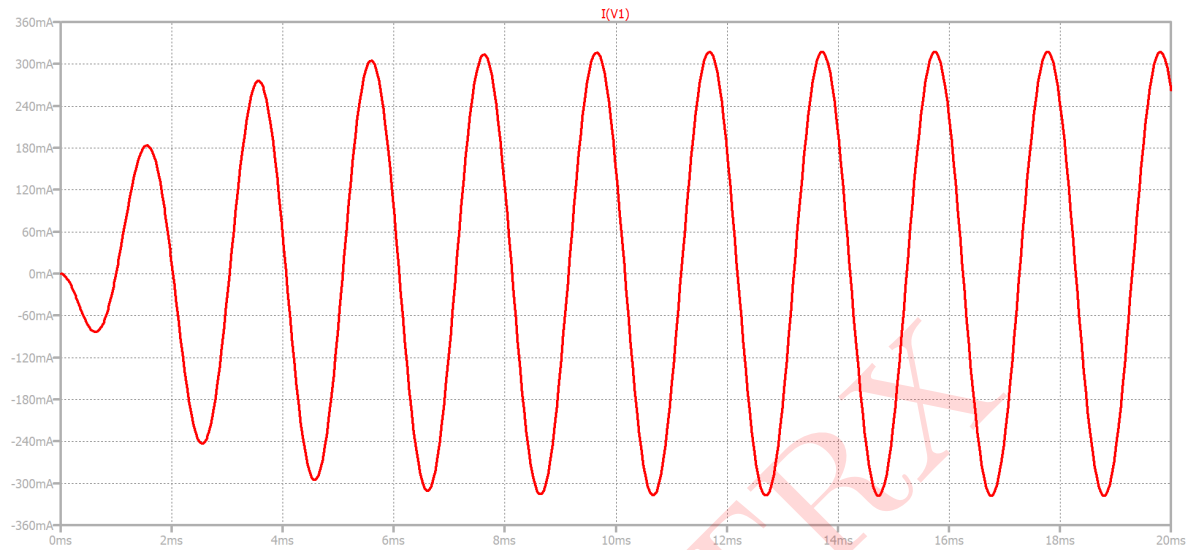


Figure 36: Voltage at resonance

Graph of voltage across inductor

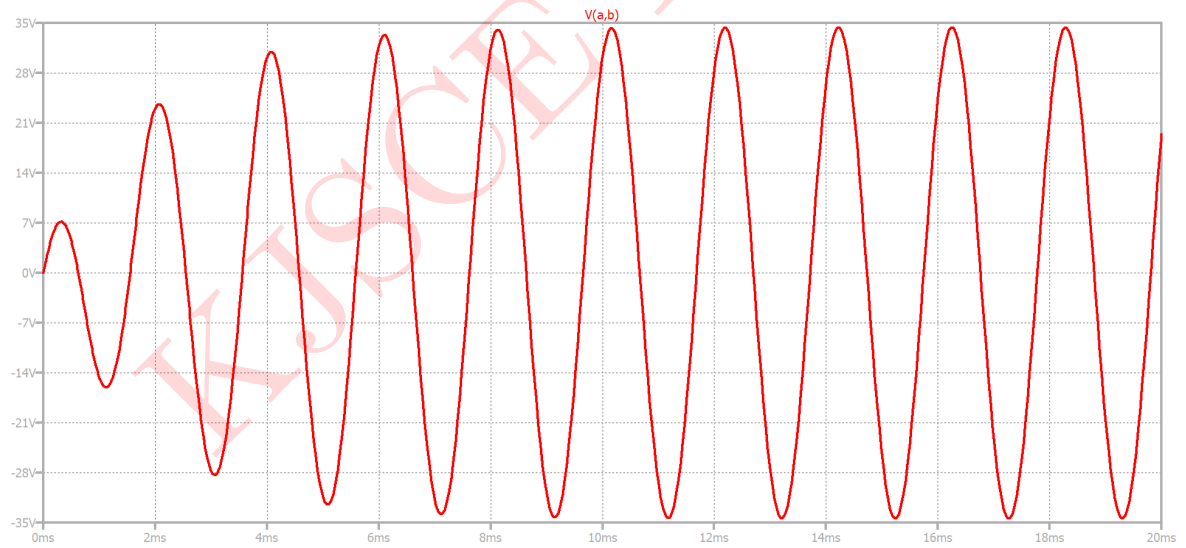


Figure 37: Voltage at resonance

Graph of voltage across capacitor

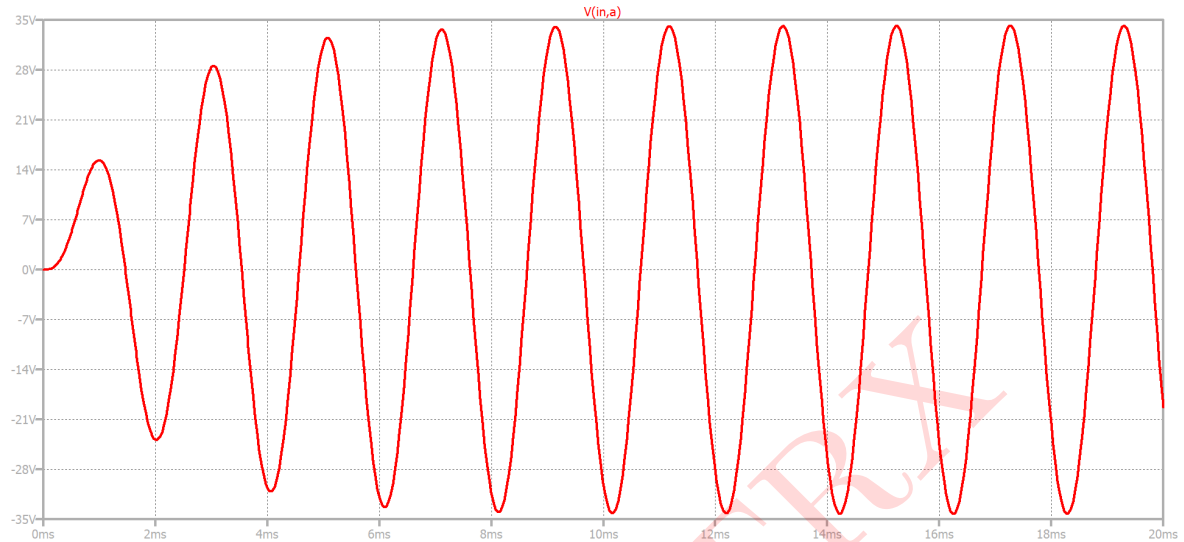


Figure 38: Voltage at resonance

### SIMULATED RESULTS:

The given circuit is simulated in LTspice and the result obtained are as follows:

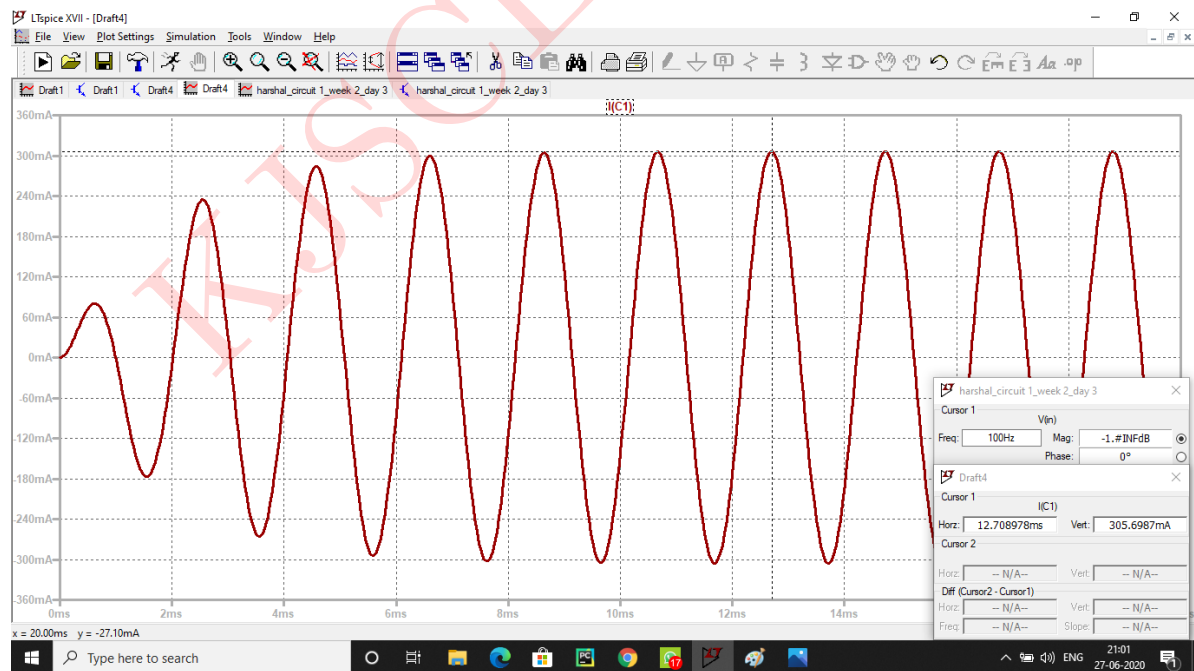


Figure 39: Simulated Results for resonance curve



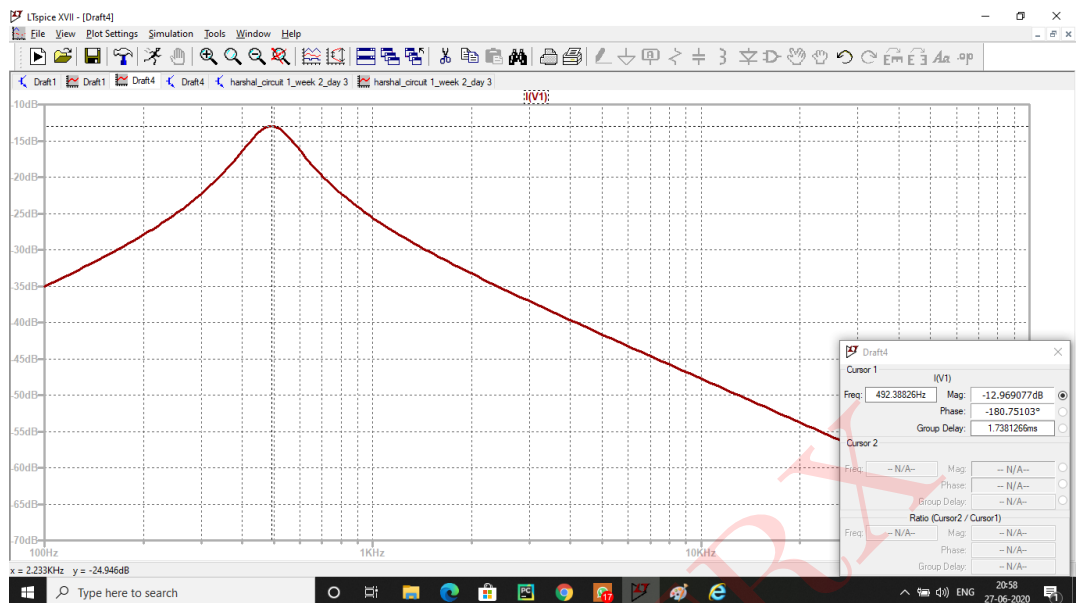


Figure 40: Simulated Results for current at resonance

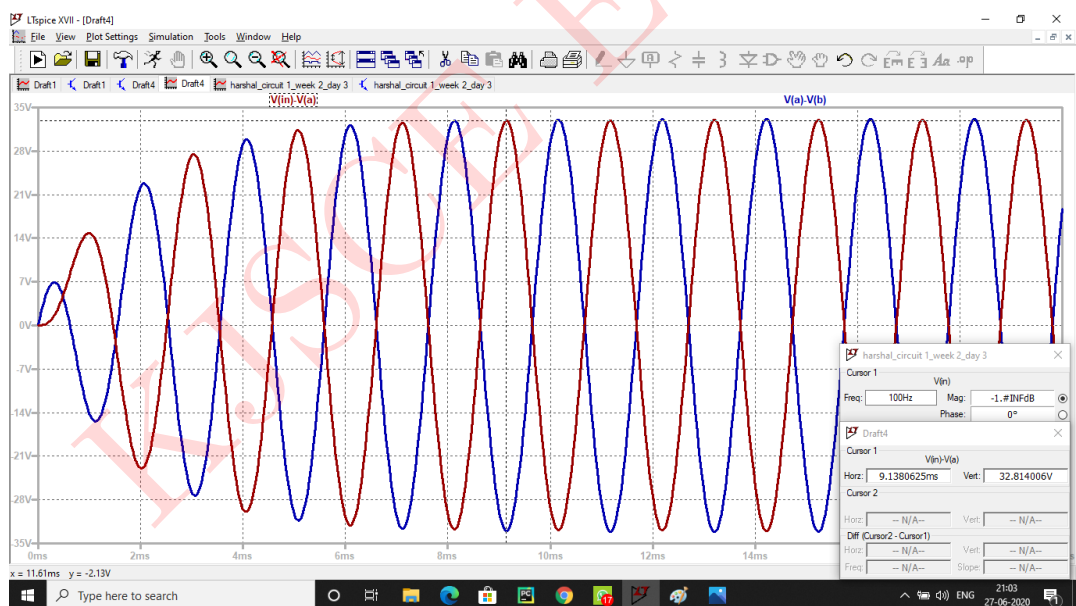


Figure 41: Simulated Results for voltages across capacitor and inductor

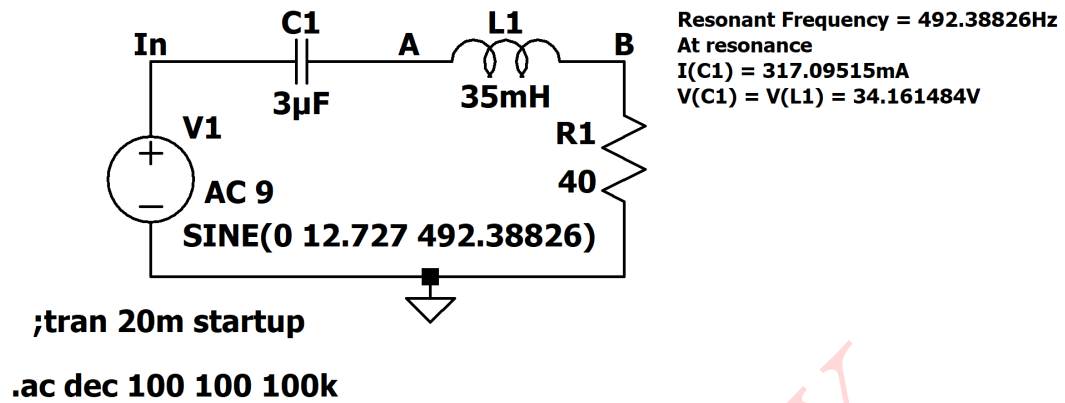


Figure 42: Simulated Circuit

Comparison of Theoretical and Simulated values:

Parameters	Theoretical Values	Simulated Values
Resonant Frequency	491.162Hz	492.38826Hz
Current in resonance	381.168mA	317.09515mA
$V_L = V_C$	34.3692V	34.1614V

Table 8: Numerical 8

\*\*\*\*\*