

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Differential Amplifier Circuits**

**Numerical 1:**

Determine the following for the circuit shown below in figure 1. Assume  $\beta_1 = \beta_2 = 100$ .

- Name the circuit
- Currents  $I_{C1}$  and  $I_{C2}$
- $V_{C1}$ ,  $V_{C2}$ ,  $V_{CE1}$ ,  $V_{CE2}$
- Differential voltage gain ( $A_d$ )
- Common mode voltage gain ( $A_{cm}$ )
- CMRR in dB

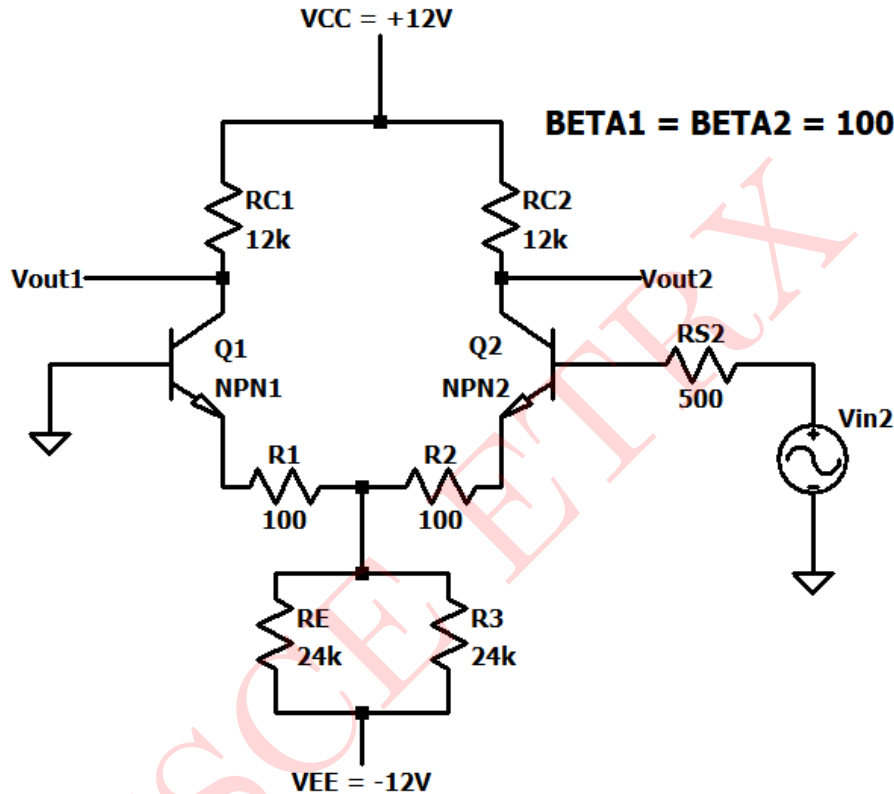


Figure 1: Circuit 1

**Solution:**

DC analysis for  $Q_1$ :

$$\begin{aligned}
 I_{C1} &= \beta_1 \left( \frac{V_{EE} - V_{BE}}{\beta_1 [2(R_E \parallel R_3) + R_1]} \right) \\
 &= 100 \left( \frac{12V - 0.7V}{100 [2(24k\Omega \parallel 24k\Omega) + 100\Omega]} \right) \\
 &= 100 \left( \frac{11.3V}{100 \left[ 2 \times \frac{24k\Omega \times 24k\Omega}{24k\Omega + 24k\Omega} \right] + 100\Omega} \right) \\
 &= 100 \left( \frac{11.3V}{100 \times 24k\Omega + 100\Omega} \right)
 \end{aligned}$$

$$= 100 \left( \frac{11.3V}{2400.1k\Omega} \right)$$

$$\therefore I_{C_1} = \mathbf{0.470mA}$$

$$\therefore I_{CQ_1} = \mathbf{0.470mA}$$

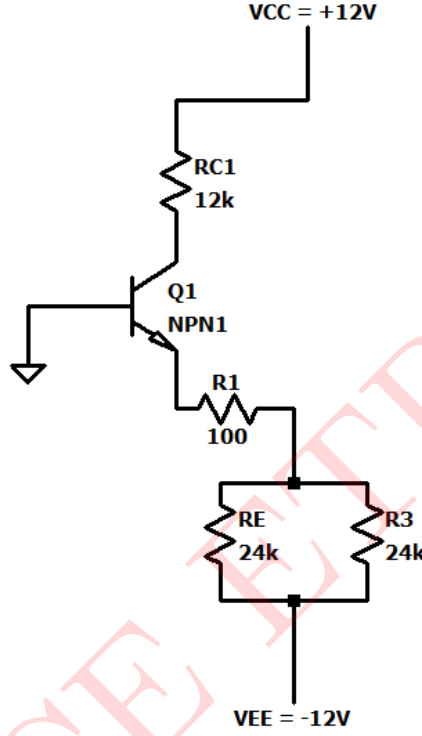


Figure 2: DC equivalent circuit for  $Q_1$

$$\begin{aligned} V_{CEQ_1} &= V_{CC} + V_{EE} - I_{CQ_1}[R_{C_1} + 2(R_E \parallel R_3) + R_1] \\ &= 12V + 12V - 0.470mA[12k\Omega + 2(24k\Omega \parallel 24k\Omega) + 100\Omega] \\ &= 12V + 12V - 0.470mA \left[ 12k\Omega + 2 \left( \frac{24k\Omega \times 24k\Omega}{24k\Omega + 24k\Omega} \right) + 100\Omega \right] \\ &= 24V - 0.470mA [12k\Omega + 2(12k\Omega) + 100\Omega] \\ &= 24V - 0.470mA [12k\Omega + 24k\Omega + 100\Omega] \\ &= 24V - 0.470mA [36.1k\Omega] \\ &= 24V - 16.97V = \mathbf{7.033V} \end{aligned}$$

$$\begin{aligned} V_{C_1} &= V_{CC} - I_{C_1} R_{C_1} \\ &= 12V - (0.470mA)(12k\Omega) \\ &= 12V - 5.6V = \mathbf{6.36V} \end{aligned}$$

DC analysis for  $Q_2$ :

$$\begin{aligned}
 I_{C_2} &= \beta_2 \left( \frac{V_{EE} - V_{BE}}{R_S + \beta_2 [2(R_E \parallel R_3) + R_2]} \right) \\
 &= 100 \left( \frac{12V - 0.7V}{500\Omega + 100[2(24k\Omega \parallel 24k\Omega) + 100\Omega]} \right) \\
 &= 100 \left( \frac{11.3V}{500\Omega + 100 \left[ 2 \times \frac{24k\Omega \times 24k\Omega}{24k\Omega + 24k\Omega} \right] + 100\Omega} \right) \\
 &= 100 \left( \frac{11.3V}{500\Omega + 100 \times 24k\Omega + 100\Omega} \right) \\
 &= 100 \left( \frac{11.3V}{2400.6k\Omega} \right)
 \end{aligned}$$

$$\therefore I_{C_2} = \mathbf{0.470mA}$$

$$\therefore I_{CQ_2} = \mathbf{0.470mA}$$

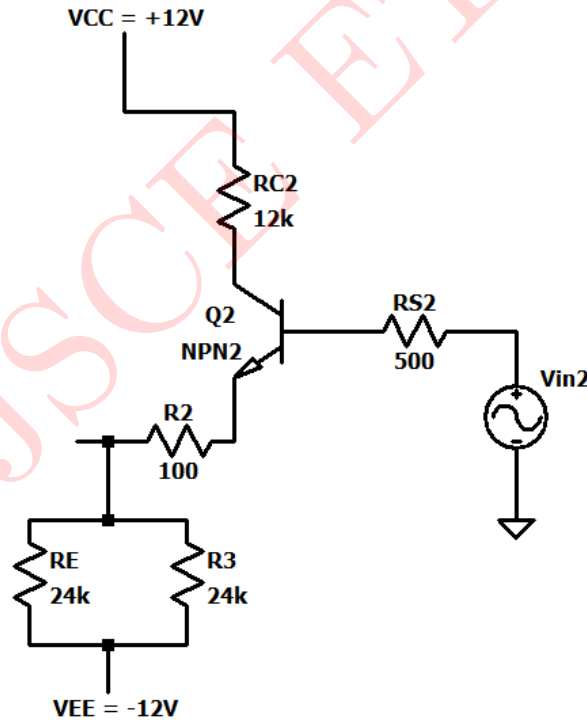


Figure 3: DC equivalent circuit for  $Q_2$

$$\begin{aligned}
 V_{CEQ_2} &= V_{CC} + V_{EE} - I_{CQ_2} [R_{C_2} + 2(R_E \parallel R_3) + R_2] \\
 &= 12V + 12V - 0.470mA [12k\Omega + 2(24k\Omega \parallel 24k\Omega) + 100\Omega] \\
 &= 12V + 12V - 0.470mA \left[ 12k\Omega + 2 \left( \frac{24k\Omega \times 24k\Omega}{24k\Omega + 24k\Omega} \right) + 100\Omega \right] \\
 &= 24V - 0.470mA [12k\Omega + 2(12k\Omega) + 100\Omega] \\
 &= 24V - 0.470mA [12k\Omega + 24k\Omega + 100\Omega]
 \end{aligned}$$

$$= 24V - 0.470mA [36.1k\Omega]$$

$$= 24V - 16.97V = \mathbf{7.033V}$$

$$V_{C_2} = V_{CC} - I_{C_2} R_{C_2}$$

$$= 12V - (0.470mA)(12k\Omega)$$

$$= 12V - 5.64V = \mathbf{6.36V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$= \frac{100 \times 26mV}{0.470mA} \quad (\because \beta_1 = \beta_2 = \beta = 100, I_{CQ_1} = I_{CQ_2} = I_{CQ} = 0.470mA)$$

$$= 100 \times 55.31 = \mathbf{5.531k\Omega}$$

Differential voltage gain( $A_d$ ):

$$A_d = \frac{\beta R_C}{R_S + r_\pi + \beta R_{Eswamp}}$$

$$= \frac{100 \times 12k\Omega}{500\Omega + 5.531k\Omega + 100 \times 100\Omega} (\because R_{C_1} = R_{C_2} = R_C = 12k\Omega, R_1 = R_2 = R_{Eswamp})$$

$$= \frac{1200k\Omega}{500\Omega + 5.531k\Omega + 10000\Omega} = \mathbf{74.85}$$

Common mode voltage gain( $A_{cm}$ ):

$$A_{cm} = \frac{R_C}{2(R_E \parallel R_3)}$$

$$= \frac{12k\Omega}{2(24k\Omega \parallel 24k\Omega)}$$

$$= \frac{12k\Omega}{2 \left( \frac{24k\Omega \times 24k\Omega}{24k\Omega + 24k\Omega} \right)}$$

$$= \frac{12k\Omega}{2 \times 12k\Omega} = \mathbf{0.5}$$

$$CMRR = \left| \frac{A_d}{A_{cm}} \right|$$

$$= \frac{74.85}{0.5} = \mathbf{149.70}$$

$$CMRR \text{ in dB} = 20 \log_{10} 149.70 = \mathbf{43.50dB}$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

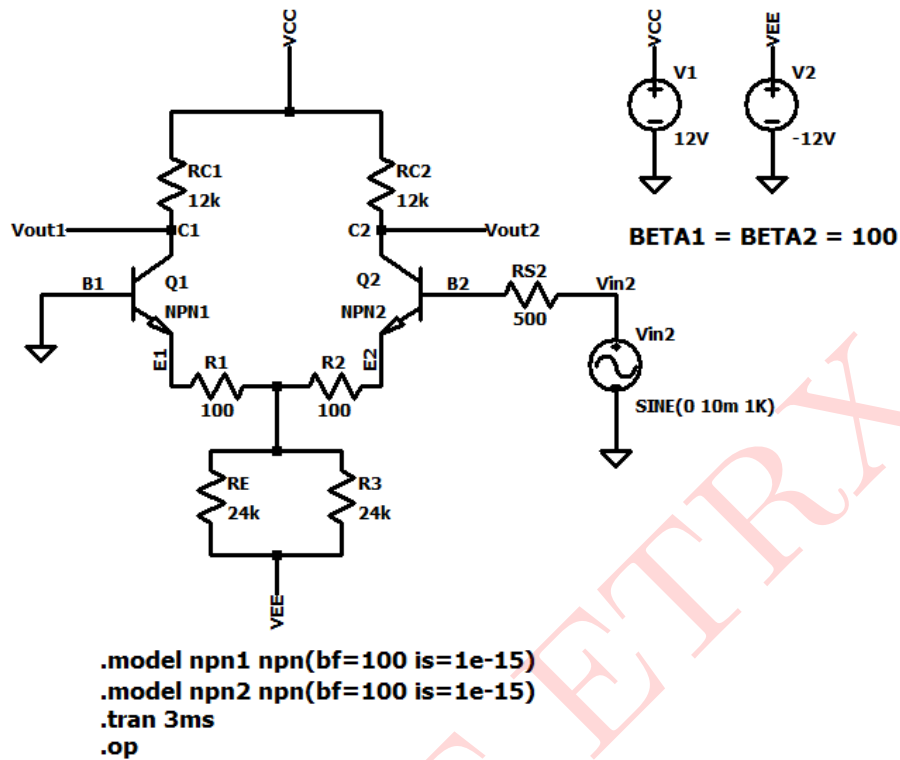


Figure 4: Circuit Schematic

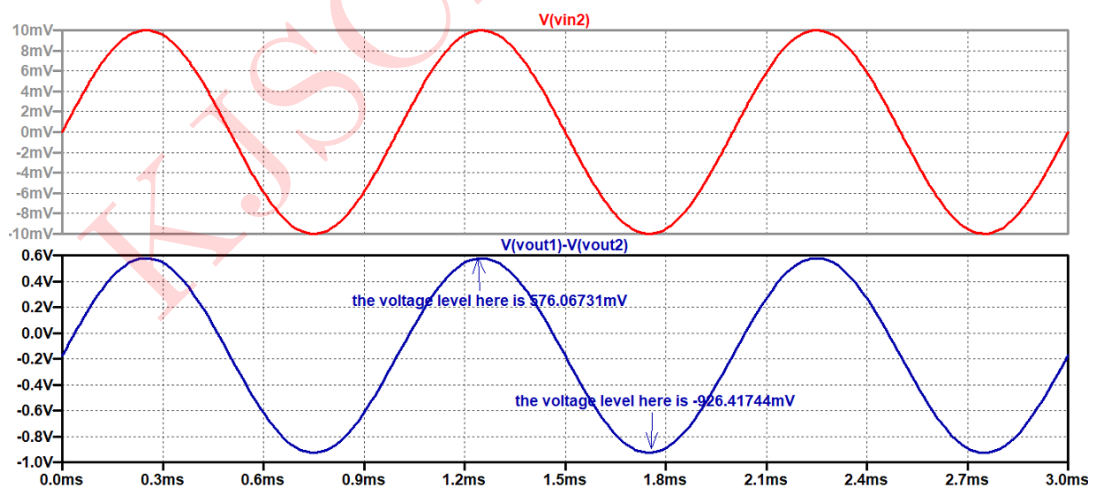


Figure 5: Input and output voltage waveform

**Comparison between theoretical and simulated values:**

Parameters	Theoretical values	Simulated values
$I_{C_1}, I_{C_2}$	0.470mA, 0.470mA	0.4716mA, 0.4751mA
$V_{C_1}, V_{C_2}$	6.36V, 6.36V	6.3396V, 6.5146V
$V_{CE_1}, V_{CE_2}$	7.033V, 7.033V	7.0348V, 7.211V
Differential voltage gain( $A_d$ )	74.85	75.1242
Common mode voltage gain( $A_{cm}$ )	0.5	—
CMRR in dB	43.50dB	—

Table 1: Numerical 1

**Numerical 2:**

Consider the differential amplifier given below in figure 6. The transistor parameters are  $k_{n1} = k_{n2} = 55\mu A/V^2$ ,  $\lambda_1 = \lambda_2 = 0.02V^{-1}$  and  $V_{TN1} = V_{TN2} = 1V$ .

- Determine  $I_S$ ,  $I_{D1}$ ,  $I_{D2}$  and  $V_{o2}$  for  $V_1 = V_2 = 0$
- Determine the differential mode voltage gain  $A_d$ , common mode voltage gain  $A_{cm}$  and the CMRR in dB

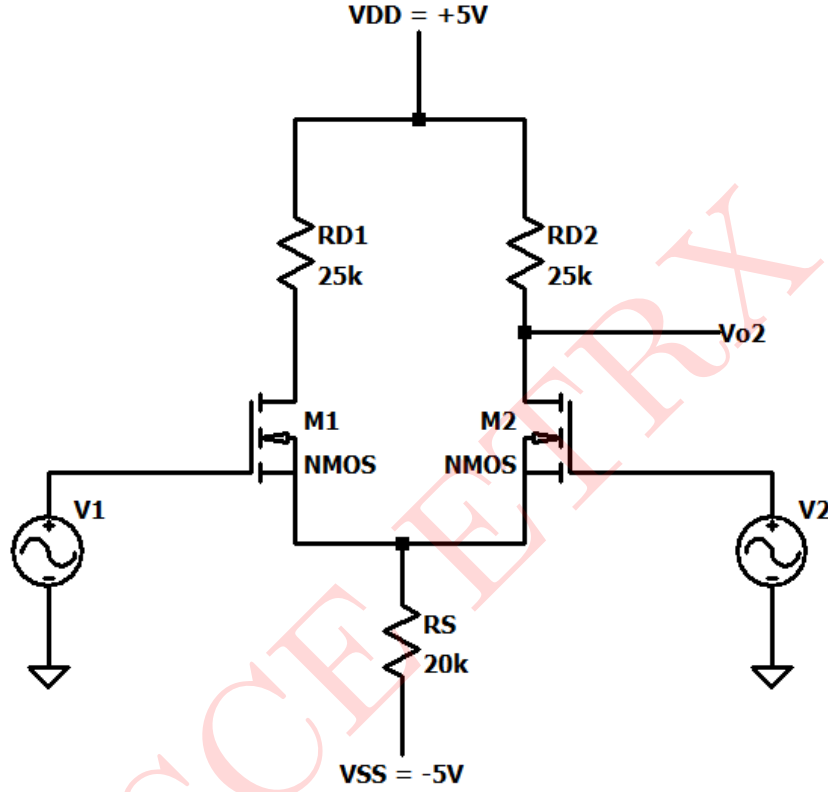


Figure 6: Circuit 2

**Solution:**

DC analysis:

Applying KVL to gate-source loop,

$$-V_{GS1} - 2I_{D1}R_S - V_{SS} = 0$$

$$\therefore V_{GS1} = -V_{SS} - 2I_{D1}R_S$$

$$= 5V - 2I_{D1}(20k\Omega)$$

$$= 5V - I_{D1}(40k\Omega) \quad \dots(1)$$

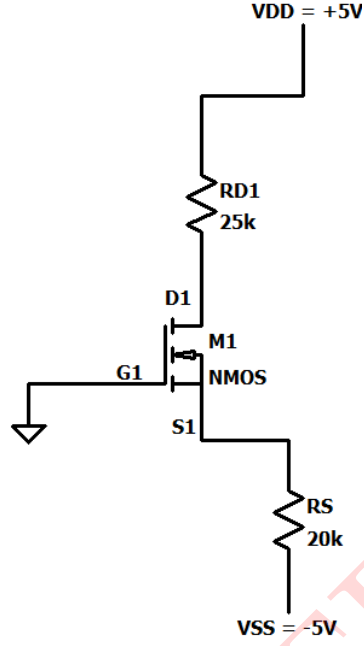


Figure 7: DC equivalent circuit

Applying KVL at drain-source loop,

$$V_{DD} - I_{D1}R_{D1} - V_{DS1} - 2I_{D1}R_S - V_{SS} = 0$$

$$V_{DS1} = V_{DD} - I_{D1}R_{D1} - 2I_{D1}R_S - V_{SS}$$

$$V_{DS1} = 5 - I_{D1}(25k\Omega) - I_{D1}(40k\Omega) + 5$$

$$V_{DS1} = 10 - I_{D1}(65k\Omega) \quad \dots(2)$$

In MOSFET,

$$I_{D1} = k_{n1}(V_{GS1} - V_{TN1})^2(1 + \lambda V_{DS1})$$

$$I_{D1} = 55 \times 10^{-6}[5 - I_{D1}(40k\Omega) - 1V]^2 \times [1 + 0.02(10 - I_{D1}(65k\Omega))] \quad [from(1)and(2)]$$

$$I_{D1} = 55 \times 10^{-6}[4 - I_{D1}(40k\Omega)]^2 \times [1 + 0.2 - I_{D1}(1.3k\Omega)]$$

$$I_{D1} = 55 \times 10^{-6}[4 - I_{D1}(40k\Omega)]^2 \times [1.2 - I_{D1}(1.3k\Omega)]$$

$$I_{D1} = 55 \times 10^{-6}[16 - I_{D1}(320 \times 10^3) + I_{D1}^2(1600 \times 10^6)] \times [1.2 - I_{D1}(1.3k\Omega)]$$

$$I_{D1} = 55 \times 10^{-6}[19.2 - I_{D1}(304.8 \times 10^3) + I_{D1}^2(2336 \times 10^6) - I_{D1}^3(2080 \times 10^9)]$$

$$I_{D1} = 1.056 \times 10^{-3} - I_{D1}(22.264) + I_{D1}^2(128.48 \times 10^3) - I_{D1}^3(114.4 \times 10^6)$$

$$I_{D1}^3(114.4 \times 10^6) - I_{D1}^2(128.48 \times 10^3) + I_{D1}(23.264) - 1.056 \times 10^{-3} = 0$$

$$I_{D1} = 0.9109mA \text{ or } I_{D1} = 0.1394mA \text{ or } I_{D1} = 0.0726mA$$

Let  $I_{D1} = 0.9109mA$

$$\therefore V_{GS1} = 5 - (0.9109mA)(40k\Omega) = -\mathbf{31.436V}$$

Let  $I_{D1} = 0.1394mA$

$$\therefore V_{GS1} = 5 - (0.1394mA)(40k\Omega) = -\mathbf{0.56V}$$



Let  $I_{D_1} = 0.0726mA$

$$\therefore V_{GS_1} = 5 - (0.0726mA)(40k\Omega) = \mathbf{2.096V}$$

We reject both negative values of  $V_{GS_1}$  because  $V_{GS_1} > V_{TN_1}$

$$\therefore V_{GS_1} = \mathbf{2.096V}$$

$$\begin{aligned} V_{DS_1} &= 10 - I_{D_1}(65k\Omega) \\ &= 10 - (0.0726mA)(65k\Omega) = \mathbf{5.281V} \end{aligned}$$

Now,

$$\begin{aligned} V_{D_1} &= V_{DD} - I_{D_1}R_{D_1} \\ &= 5V - (0.0726mA)(25k\Omega) = \mathbf{3.185V} \end{aligned}$$

$\therefore$  Both the transistor are identical,

$$\therefore I_{D_1} = I_{D_2} = \mathbf{0.0726mA}$$

$$V_{DS_1} = V_{DS_2} = \mathbf{5.281V}$$

$$V_{D_1} = V_{D_2} = \mathbf{3.185V}$$

$$\begin{aligned} \therefore I_S &= I_{D_1} + I_{D_2} \\ &= 0.0726mA + 0.0726mA = \mathbf{0.1452mA} \end{aligned}$$

Applying KVL at drain-source loop of  $M_2$ ,

$$V_{DD} - V_{O_2} - V_{DS_2} - I_S R_S + V_{SS} = 0$$

$$5V - V_{O_2} - 2.096V - (0.1452mA)(20k\Omega) + 5V = 0$$

$$10V - 2.096V - 2.904V + 5V = V_{O_2}$$

$$V_{O_2} = 10V - 5V = \mathbf{5V}$$

Small signal parameters:

$$\begin{aligned} g_{m_1} &= 2k_n(V_{GS_1} - V_{TN_1})(1 + \lambda V_{DS_1}) \\ &= 2 \times 55 \times 10^{-6}(2.096V - 1V)[1 + (0.02)(5.281V)] \\ &= 110 \times 10^{-6}(1.096V)[1.105] = \mathbf{0.133mA/V} \end{aligned}$$

$$\therefore g_{m_1} = g_{m_2} = g_m = \mathbf{0.133mA/V}$$

$$\begin{aligned} r_{d_1} &= \frac{1}{\lambda_1 I_{D_1}} \\ &= \frac{1}{0.02 \times 0.0726mA} = \mathbf{688.70k\Omega} \end{aligned}$$

$$\therefore r_{d_1} = r_{d_2} = \mathbf{688.70k\Omega}$$

Differential voltage gain( $A_d$ ):

$$\begin{aligned} A_d &= \frac{g_m(R_D \parallel r_d)}{2} \\ &= \frac{0.133mA/V(25k\Omega \parallel 688.70k\Omega)}{2} \\ &= \frac{0.133mA/V \left( \frac{25k\Omega \times 688.70k\Omega}{25k\Omega + 688.70k\Omega} \right)}{2} \\ &= \frac{0.133mA/V \times 24.12k\Omega}{2} \\ &= \frac{3.208}{2} = \mathbf{1.60} \end{aligned}$$

Common mode voltage gain( $A_{cm}$ ):

$$\begin{aligned} A_{cm} &= \frac{g_m(r_d \parallel R_D)}{1 + 2g_mR_S} \\ &= \frac{0.133mA/V(25k\Omega \parallel 688.70k\Omega)}{1 + 2(0.133mA/V)(20k\Omega)} \\ &= \frac{0.133mA \times 24.12k\Omega}{1 + 5.32} \\ &= \frac{3.207}{6.32} = \mathbf{0.50} \end{aligned}$$

$$\begin{aligned} CMRR &= \left| \frac{A_d}{A_{cm}} \right| \\ &= \frac{1.60}{0.50} = \mathbf{3.2} \end{aligned}$$

$$CMRR \text{ in dB} = 20 \log_{10} 3.2 = \mathbf{10.10dB}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

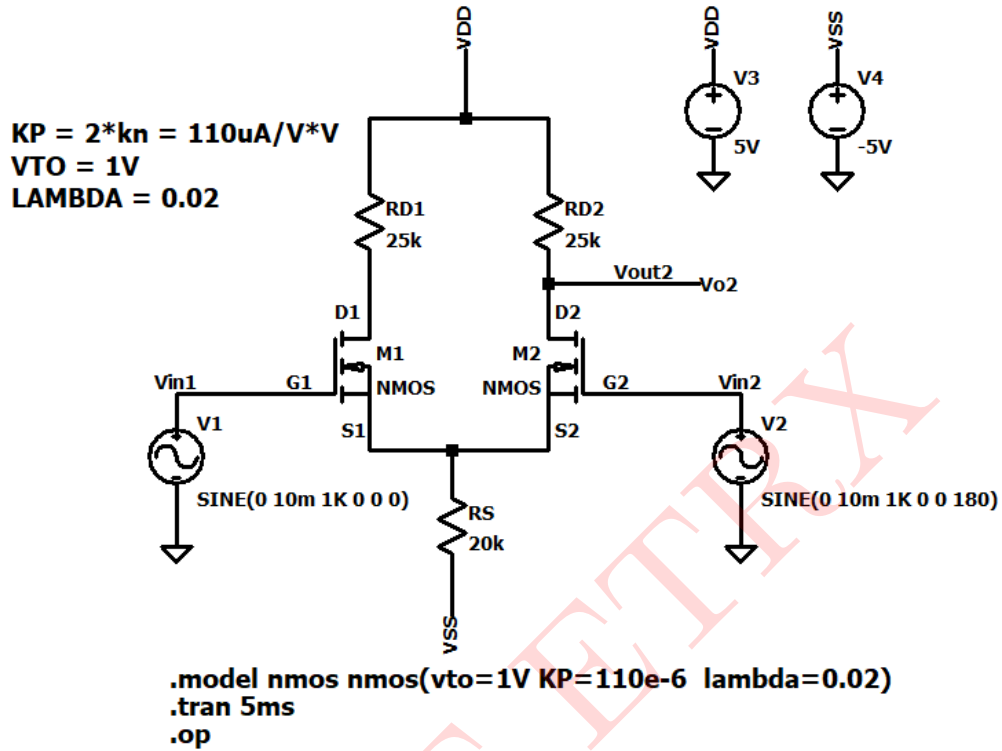


Figure 8: Circuit Schematic

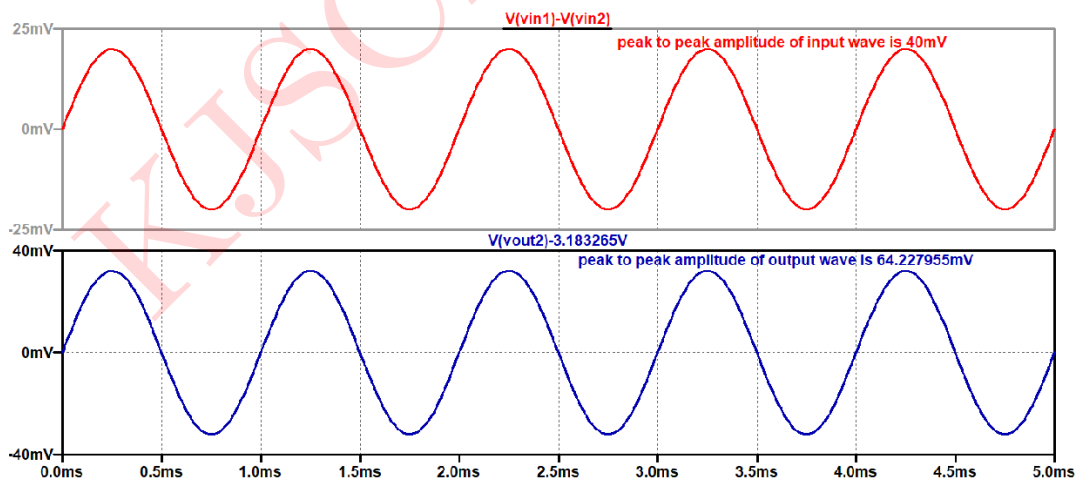


Figure 9: Input and output voltage waveform

**Comparison between theoretical and simulated values:**

Parameters	Theoretical values	Simulated values
$I_S, I_{D_1}, I_{D_2}$	0.1452mA, 0.0726mA, 0.0726mA	0.1453mA, 0.0726mA, 0.0726mA
$V_{D_1}, V_{D_2}$	3.185V, 3.185	3.1832V, 3.1832V
$V_{DS_1}, V_{DS_2}$	5.281V, 5.281V	5.2764V, 5.2764V
Differential voltage gain( $A_d$ )	1.60	1.6056
Common mode voltage gain( $A_{cm}$ )	0.50	—
CMRR in dB	10.10dB	—

Table 2: Numerical 2

**Numerical 3:**

For the amplifier shown below, JFET parameters are  $I_{DSS1} = I_{DSS2} = 12mA$  and  $V_{P1} = V_{P2} = -2.5V$ . Find

- $I_{D1}$ ,  $I_{D2}$ ,  $V_{D1}$ ,  $V_{D2}$
- DC values of  $V_{o1}$  and  $V_{o2}$
- Double ended gain  $\left( \frac{V_{o1} - V_{o2}}{V_1 - V_2} \right)$

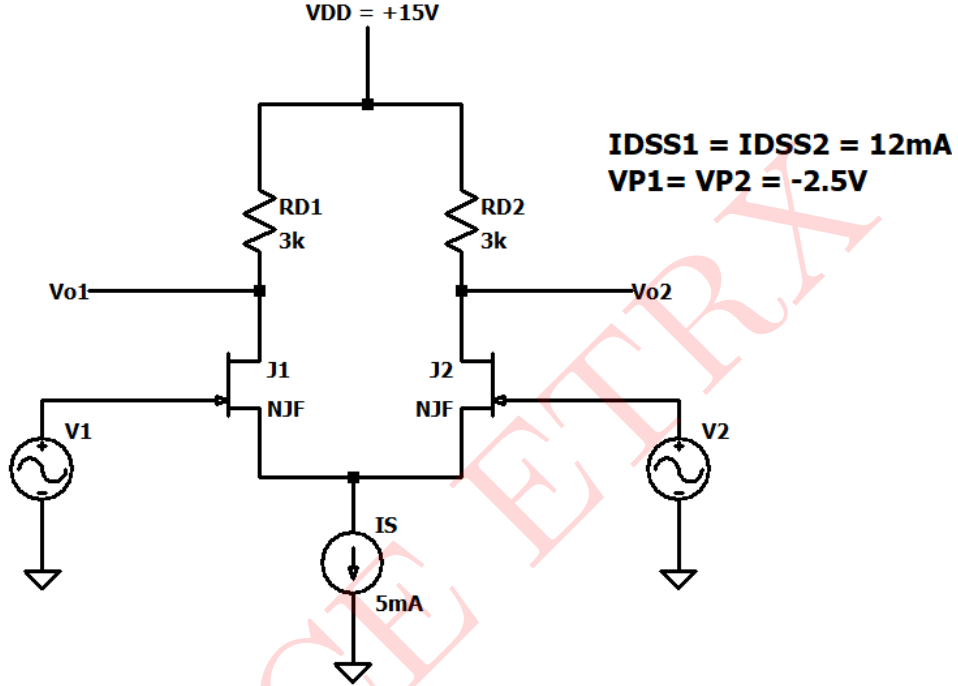


Figure 10: Circuit 3

**Solution:**

Above circuit is dual input balanced output(DIBO) differential amplifier consisting of JFETs. The circuit consists of identical transistors and circuit is vertically symmetric.

$$I_{D1} = I_{D2} = \frac{I_S}{2}$$

$$I_{D1} = I_{D2} = \frac{5mA}{2}$$

$$I_{D1} = I_{D2} = \mathbf{2.5mA}$$

Now,

$$\begin{aligned} \text{DC value of } V_{o1} = V_{o2} &= V_{DD} - I_D R_D \\ &= 15V - (2.5mA)(3k\Omega) \quad (I_{D1} = I_{D2} = I_D = 2.5mA) \\ &= 15V - 7.5V = \mathbf{7.5V} \end{aligned}$$

$$\therefore V_{D1} = \text{DC value of } V_{o1} \text{ and } V_{D2} = \text{DC value of } V_{o2}$$

$$\therefore V_{D1} = V_{D2} = \mathbf{7.5V}$$

Small signal parameters:

In JFET,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\therefore \frac{I_D}{I_{DSS}} = \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\therefore \sqrt{\frac{I_D}{I_{DSS}}} = 1 - \frac{V_{GS}}{V_P} \quad \dots(1)$$

$$\therefore g_m = \frac{2I_{DSS}}{|V_P|} \times \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$\therefore g_m = \frac{2I_{DSS}}{|V_P|} \times \sqrt{\frac{I_D}{I_{DSS}}} \quad (\text{from (1)})$$

$$\therefore g_m = \frac{2 \times 12mA}{2.5V} \times \sqrt{\frac{2.5mA}{12mA}}$$

$$\therefore g_m = 2 \times 4.8mA/V \times 0.45 = \mathbf{4.38mA/V}$$

$$\therefore g_{m1} = g_{m2} = g_m = \mathbf{4.38mA/V}$$

Differential ended gain( $A_d$ ):

$$A_d = \frac{V_{o1} - V_{o2}}{V_1 - V_2} \quad (\text{assuming } V_{o2} > V_{o1})$$

$$\begin{aligned} \therefore A_d &= -g_m R_D \\ &= -4.38mA/V \times 3k\Omega = \mathbf{-13.14} \end{aligned}$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

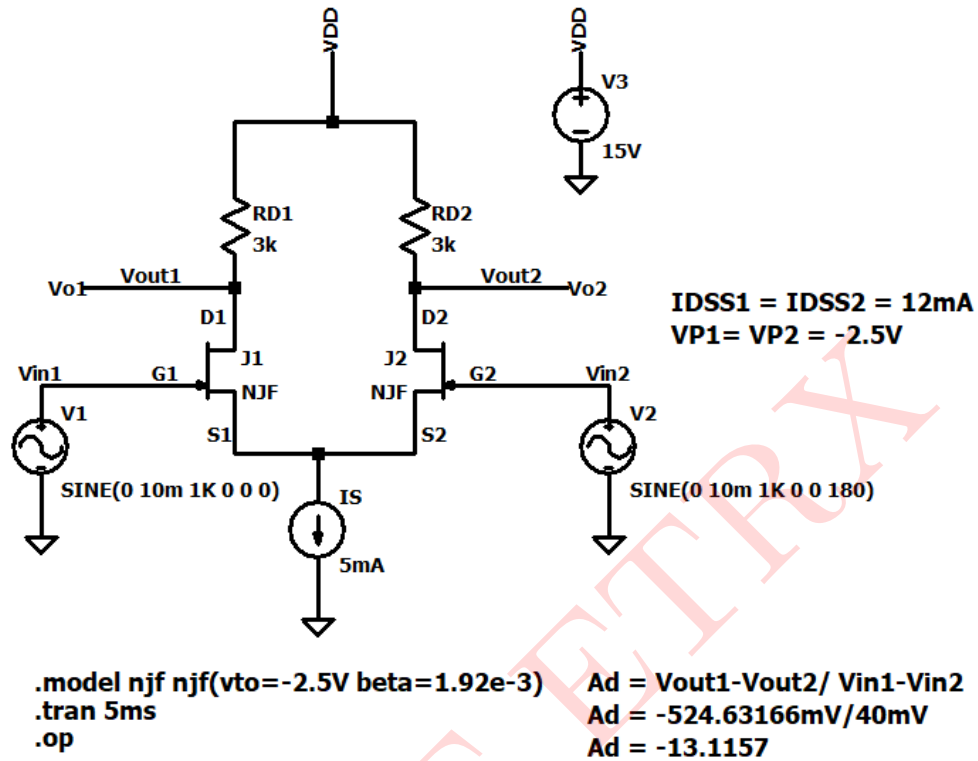


Figure 11: Circuit Schematic

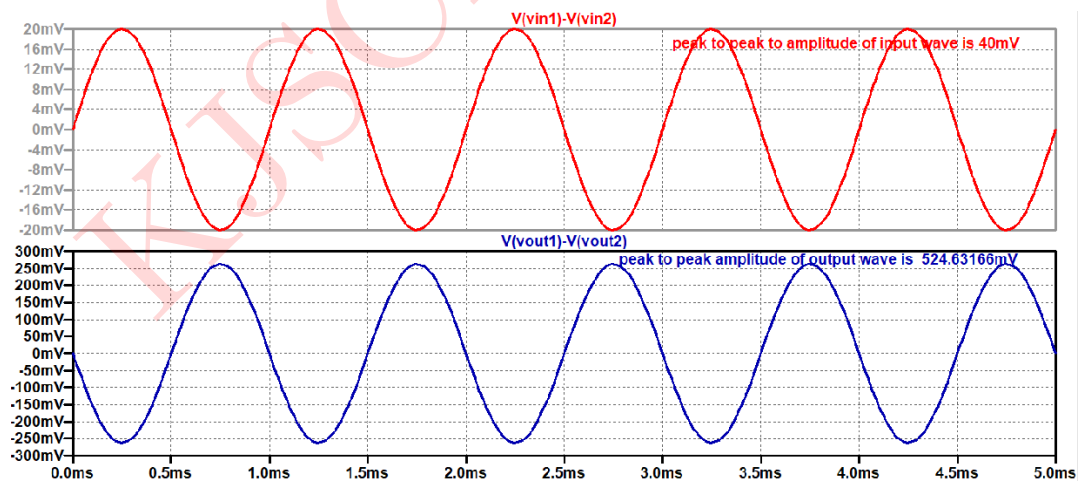


Figure 12: Input and output voltage waveform

**Comparison between theoretical and simulated values:**

Parameters	Theoretical values	Simulated values
$I_{D_1}, I_{D_2}$	2.5mA, 2.5mA	2.500mA, 2.500mA,
$V_{D_1}, V_{D_2}$	7.5V, 7.5V	7.5V, 7.5V
Differential voltage gain( $A_d$ )	-13.14	-13.1157

Table 3: Numerical 3

\*\*\*\*\*

KJSCE ETRX