

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DC Biasing Circuits

Numerical 1:

Determine the following for the common gate configuration shown in figure 1: V_{GSQ} , I_{DQ} , V_D , V_G , V_S , V_{DS}

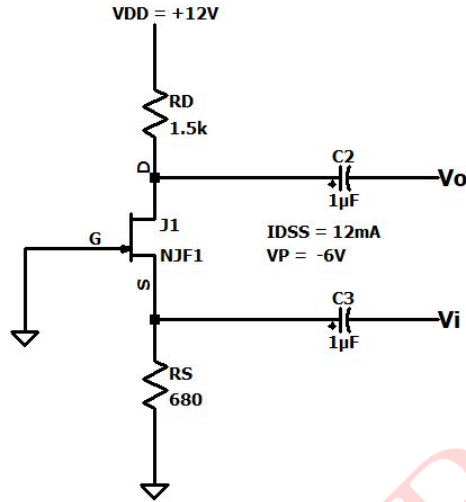


Figure 1: Circuit 1

Solution:

To find these parameters we will perform DC analysis so all capacitors are open circuited.

 


Figure 2: DC Equivalent Circuit

$$V_{GS} = -I_D R_S$$

$$I_D = -\frac{V_{GS}}{R_S}$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = (12mA) \left(1 - \frac{V_{GS}}{-6} \right)^2$$

$$\frac{-V_{GS}}{R_S} = (12mA) \left(1 + \frac{V_{GS}}{6}\right)^2$$

$$\frac{-V_{GS}}{680} = (12mA) \left(1 + \frac{V_{GS}}{6}\right)^2$$

$$\frac{-V_{GS}}{680} = (12 \times 10^{-3}) \left(1 + \frac{V_{GS}}{3} + \frac{V_{GS}^2}{36}\right)$$

$$\frac{-V_{GS}}{680} = 0.012 + 4V_{GS} \times 10^{-3} + \frac{V_{GS}^2}{3} \times 10^{-3}$$

$$0 = 0.012 + 5.47V_{GS} \times 10^{-3} + \frac{V_{GS}^2}{3} \times 10^{-3}$$

$$0 = 0.012 + (5.47 \times 10^{-3})V_{GS} + (0.33 \times 10^{-3})V_{GS}^2$$

$$V_{GS} = -2.602 \text{ or } V_{GS} = -13.97$$

We reject the value $V_{GS} = -13.97$ because magnitude of V_{GS} cannot be greater than V_P

$$V_{GS} = \mathbf{-2.602V}$$

$$I_{DQ} = \frac{-V_{GS}}{R_S} = \frac{2.602}{680} = 3.826 \times 10^{-3}A = \mathbf{3.83mA}$$

$$V_D = V_{DD} - I_D R_D$$

$$= 12V - (3.8mA)(1.5k)$$

$$= 12V - 5.7V = \mathbf{6.3V}$$

$$V_G = \mathbf{0}$$

$$V_S = I_D R_S = (3.8mA)(680\Omega) = \mathbf{2.58V}$$

$$V_{DS} = V_D - V_S = 6.3V - 2.58V = \mathbf{3.72V}$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below.

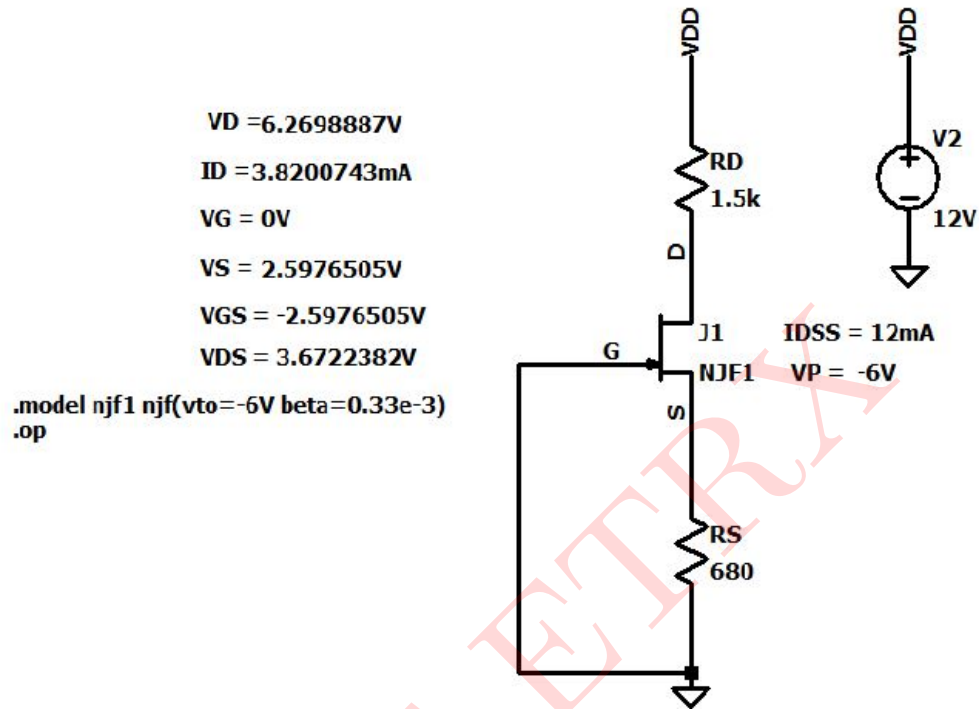


Figure 3: Circuit Schematic: Result

Comparison between theoretical and simulated value

Parameters	Theoretical values	Simulated values
V_{GS}	-2.602V	-2.597V
I_{DQ}	3.83mA	3.820mA
V_D	6.3V	6.269V
V_G	0V	0V
V_S	2.58V	2.597V
V_{DS}	3.72V	3.672V

Table 1: Question 1

Numerical 2:

Determine the following for the network shown in figure 4 : V_{GSQ} , I_{DQ} , V_D , V_{DS} , V_S , V_{DG}

 


Figure 4: Circuit 2

Solution:

To find the parameters we will perform DC analysis so all capacitors are open circuited.

 


Figure 5: Circuit Schematic

$$\begin{aligned}
 R_G &= \frac{R_1 R_2}{R_1 + R_2} \\
 &= \frac{270k\Omega \times 2.1M\Omega}{270k\Omega + 2.1M\Omega} = 239.24k\Omega
 \end{aligned}$$

$$\begin{aligned}
 V_G &= \frac{R_2}{R_1 + R_2} \times V_{DD} \\
 &= \frac{270k\Omega}{2.1M\Omega + 270k\Omega} \times 16V = 1.822V
 \end{aligned}$$

Applying KVL to gate source circuit,

$$V_G - V_{GS} - I_D R_S = 0$$

$$V_{GS} = V_G - I_D R_S$$

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{1.822 - V_{GS}}{1.5k\Omega}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\frac{1.822 - V_{GS}}{1.5k} = 8mA \left(1 - \frac{V_{GS}}{-4} \right)^2$$

$$\frac{1.822 - V_{GS}}{1.5} = 8 \times 10^{-3} \left(1 + \frac{V_{GS}}{4} \right)^2$$

$$\frac{1.822 - V_{GS}}{1.5} \times 10^{-3} = 8 \times 10^{-3} \left(1 + \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16} \right)$$

$$\frac{1.822 - V_{GS}}{1.5} \times 10^{-3} = 8 \left(1 + \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16} \right)$$

$$1.822 - V_{GS} = 12 \left(1 + \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16} \right)$$

$$1.822 - V_{GS} = 12 + 6V_{GS} + 0.75V_{GS}^2$$

$$0 = 10.178 + 7V_{GS} + 0.75V_{GS}^2$$

$$0.75V_{GS}^2 + 7V_{GS} + 10.178 = 0$$

$$V_{GS} = -1.801V \text{ or } V_{GS} = -7.53V$$

We reject the value $V_{GS} = -7.53V$ because magnitude of V_{GS} cannot be greater than V_p .

$$V_{GS} = -1.801V$$

$$I_D = \frac{1.822 - V_{GS}}{1.5k}$$

$$I_D = \frac{1.822 + 1.801}{1.5 \times 10^3} = \mathbf{2.4153mA}$$

$$V_D = V_{DD} - I_D R_D$$

$$= -16V - (2.4mA)(2.4k\Omega) = \mathbf{10.24V}$$

$$V_S = I_D R_S = (2.4mA)(1.5k) = \mathbf{3.6V}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 16V - (2.4mA)(2.4k\Omega + 1.4k\Omega) = \mathbf{6.64V}$$

$$V_{DG} = V_D - V_G$$

$$= 10.24 - 1.82 = \mathbf{8.42V}$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below:

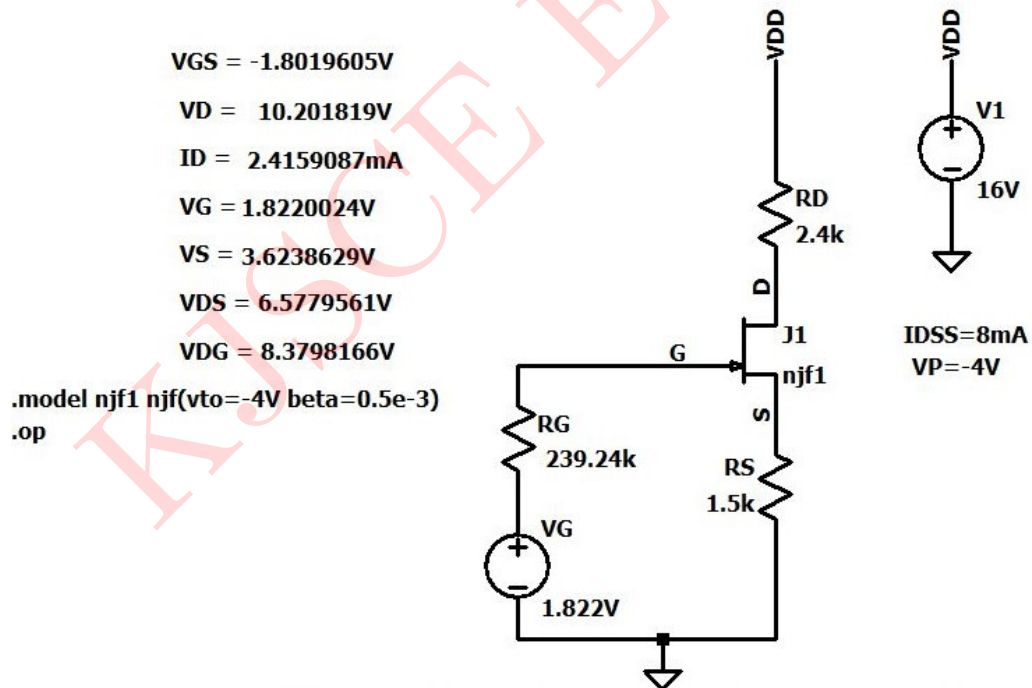


Figure 6: Circuit Schematic: Result

Comparison between theoretical and simulated value:

Parameter	Theoretical values	Simulated values
V_{GS}	-1.801V	-1.8019V
I_D	2.4153mA	2.415mA
V_D	10.24V	10.201V
V_S	3.6V	3.624V
V_{DS}	6.64V	6.5779V
V_{DG}	8.42V	8.3798V

Table 2: Question 2

KJSCE ETRX

Numerical 3:

For the fixed-bias of figure given below, determine: I_D and V_{DS}

 


Figure 7: Circuit 3

Solution:

The above circuit is a fixed-bias configuration consisting of a N-channel JFET

Applying KVL to the gate-source loop i.e input loop,

$$-V_G - V_{GS} = 0$$

$$V_{GS} = -V_G = -1.5V$$

For JFET,

$$\begin{aligned} I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \\ &= (12mA) \left(1 - \frac{(-1.5)}{-4} \right)^2 \\ &= (12 \times 10^{-3}) \left(1 - \frac{1.5}{4} \right)^2 = \mathbf{4.69mA} \end{aligned}$$

Applying KVL to drain-source loop i.e output loop,

$$V_{DD} - I_D R_D - V_{DS} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$= 12 - 4.69 \times 10^{-3} \times 1.2 \times 10^3 = \mathbf{6.372V}$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below:

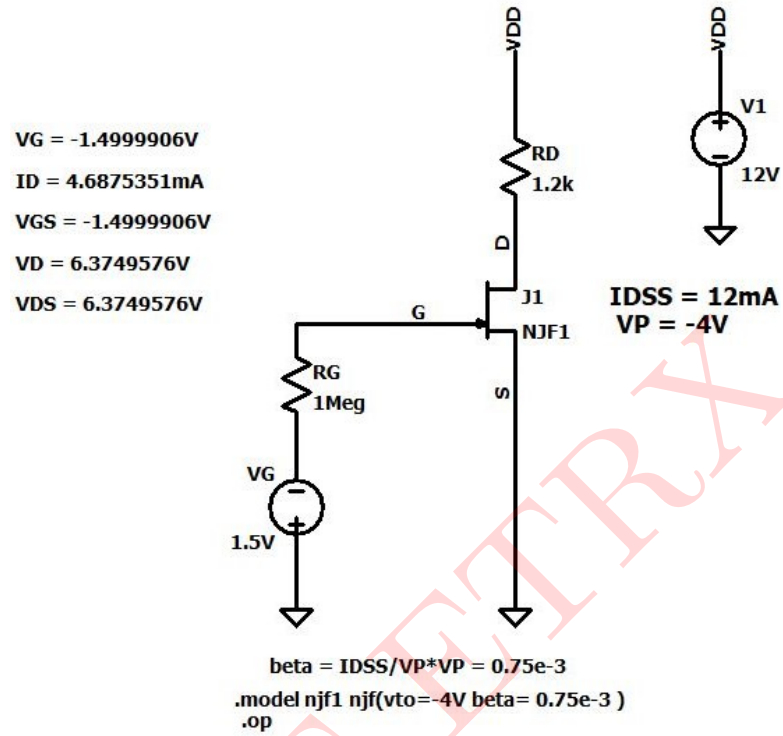


Figure 8: Circuit Schematic: Result

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
V_{GS}	-1.5V	-1.499V
I_D	4.69mA	4.687mA
V_{DS}	6.372V	6.374V

Table 3: Question 3

Numerical 4:

For the circuit given below, determine: I_D , V_{DS} , V_{GS} and V_D

 


Figure 9: Circuit 4

Solution:

The above circuit is a fixed-bias configuration consisting of a N-channel JFET

In JFET the current through gate is minimised,

$$I_G = 0$$

$$R_G I_G = 0$$

Applying KVL to the gate-source loop i.e input loop,

$$-V_G - V_{GS} = 0$$

$$V_{GS} = -V_G = -2\text{V}$$

For JFET,

$$\begin{aligned} I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \\ &= (10\text{mA}) \left(1 - \frac{(-2)}{-4} \right)^2 \\ &= (10 \times 10^{-3}) \left(1 - \frac{2}{4} \right)^2 = \mathbf{2.5\text{mA}} \end{aligned}$$

Applying KVL to drain-source loop i.e output loop,

$$V_{DD} - I_D R_D - V_{DS} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$= 8 - 2.5 \times 10^{-3} \times 1 \times 10^3 = 5.5V$$

$$V_D = V_{DS} = \mathbf{5.5V}$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below:

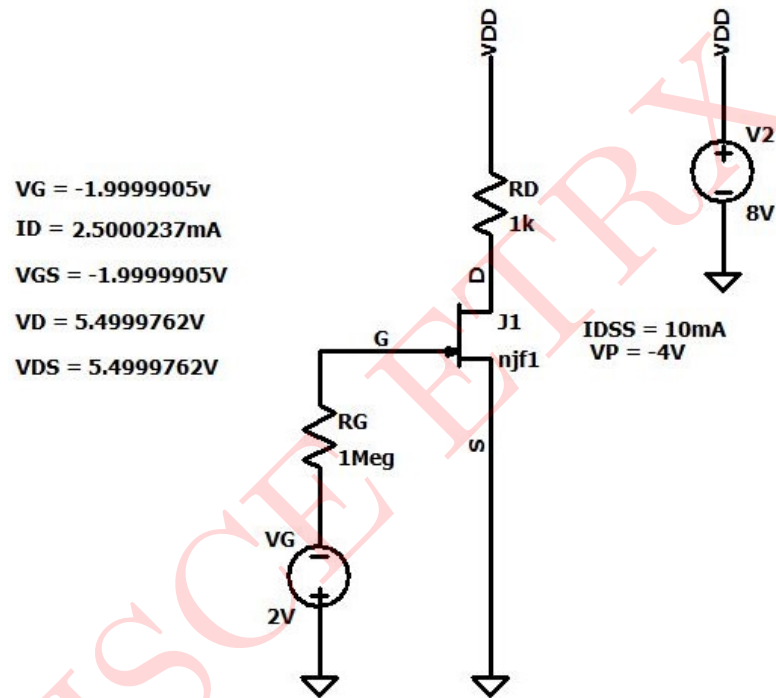


Figure 10: Circuit Schematic: Result

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
V_{GS}	-2V	-1.999V
I_D	2.5mA	2.50mA
V_D	5.5V	5.499V
V_{DS}	5.5V	5.499V

Table 4: Question 4

Numerical 5:

For the circuit given below, $\beta = 125$. Find I_{CQ} and V_{CEQ}

 


Figure 11: Circuit 5

Solution:

The above circuit is a voltage-bias configuration consisting of a npn BJT.

To determine R_B and V_{TH}

$$R_B = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{58k \times 42k}{58k + 42k} = \frac{609k}{25k} = 24.36k\Omega$$

$$V_{TH} = \frac{R_2 \times V_{CC}}{R_1 + R_2} = \frac{42k \times 24k}{42k + 24k} = 10.08V$$

 


Figure 12: Thevenin's equivalent Circuit

Applying KVL in the base-emitter i.e input loop

$$V_{TH} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{TH} - I_B R_B - V_{BE} - [(1 + \beta)I_B]R_E = 0$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_B + (1 + \beta)R_E}$$

$$I_B = \frac{10.08 - 0.7}{24.36K + (126)(10k)} = 7.303 \times 10^{-6} A = 7.303 \mu A$$

$$I_C = \beta I_B = (125)(7.303 \mu A) = \mathbf{0.913mA}$$

Applying KVL to collector-emitter loop i.e output loop,

$$V_{CC} - V_{CE} - I_E R_E = 0$$

$$V_{CC} - V_{CE} - I_C R_E = 0 \quad (\because I_C = I_E)$$

$$24 - V_{CE} - (0.913mA)(10k\Omega) = 0$$

$$V_{CE} = 24 - 9.13 = \mathbf{14.87V}$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below:

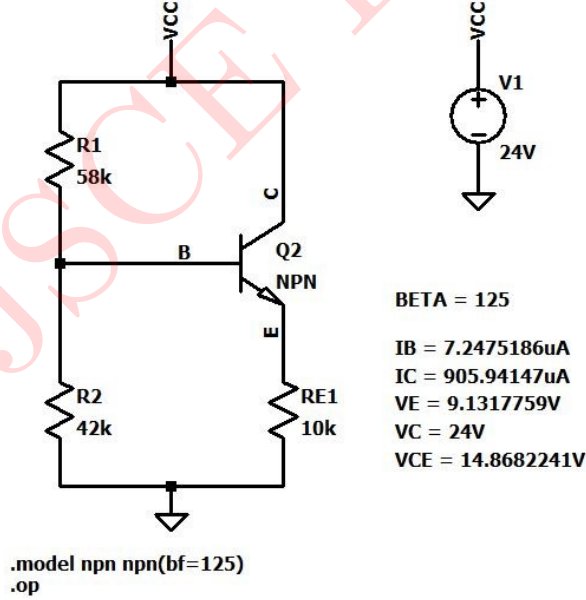


Figure 13: Circuit Schematic: Results

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_C	0.913mA	0.90594mA
V_{CE}	14.87V	14.8682V

Table 5: Question 5

Numerical 6:

For the circuit given below in figure 14, determine V_{GSQ} , I_{DQ} , V_{DS} , V_D , V_G , V_S

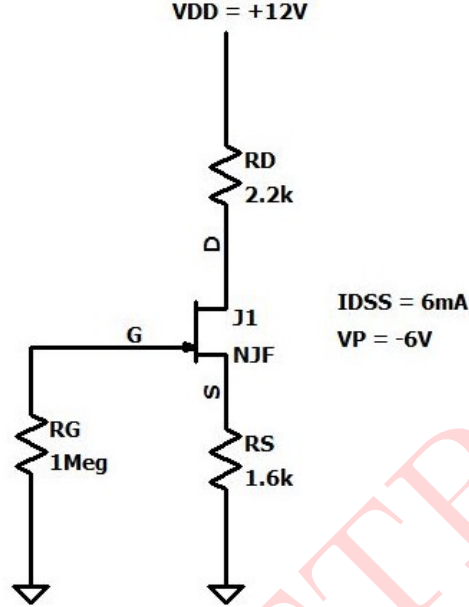


Figure 14: Circuit 6

Solution:

The above circuit is a fixed-bias configuration consisting of N-channel JFET.

In JFET the current through gate is negligible,

$$\text{i.e } I_G = 0$$

$$R_G I_G = 0$$

Applying KVL to the gate-source loop i.e input loop,

$$-V_{GS} - I_D R_S = 0$$

$$V_{GS} = -I_D R_S = -I_D (1.6k\Omega)$$

$$I_D = \frac{-V_{GS}}{1.6k\Omega}$$

For JFET, the drain current is given by

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\frac{-V_{GS}}{1.6k} = 6mA \left(1 - \frac{V_{GS}}{-6} \right)^2$$

$$\frac{-V_{GS}}{1.6k} = 6mA \left(1 + \frac{V_{GS}}{6} \right)^2$$

$$\frac{-V_{GS}}{1.6k} = 6mA \left(1 + \frac{V_{GS}}{3} + \frac{V_{GS}^2}{36} \right)$$

$$\frac{-V_{GS}}{1.6} \times 10^{-3} = 6 \times 10^{-3} \left(1 + \frac{V_{GS}}{3} + \frac{V_{GS}^2}{36} \right)$$

$$\frac{-V_{GS}}{1.6} = 6 \left(1 + \frac{V_{GS}}{3} + \frac{V_{GS}^2}{36} \right)$$

$$-V_{GS} = 9.6 \left(1 + \frac{V_{GS}}{3} + \frac{V_{GS}^2}{36} \right)$$

$$-V_{GS} = 9.6 + 3.2V_{GS} + 0.266V_{GS}^2$$

$$0 = 9.6 + 4.2V_{GS} + 0.266V_{GS}^2$$

$$V_{GS} = -2.774V \text{ or } V_{GS} = -13.01V$$

We reject the value $V_{GS} = -13.01V$ $\because |V_{GS}| < |V_P|$

$$V_{GS} = -2.774V$$

$$I_D = \frac{-V_{GS}}{1.6k\Omega} = \frac{-2.774V}{1.6k\Omega} = \mathbf{1.7337mA}$$

$$V_D = V_{DD} - I_D R_D$$

$$= 12 - (1.73mA)(2.2k\Omega)$$

$$= 12 - 3.806 = \mathbf{8.194V}$$

$$V_S = I_D R_S$$

$$= 12 - (1.73mA)(1.6k\Omega) = \mathbf{2.768V}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 12 - (1.73mA)(2.2k\Omega + 1.6k\Omega)$$

$$= 12 - 6.574 = \mathbf{5.426V}$$

$$V_G = \mathbf{0V}$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below:

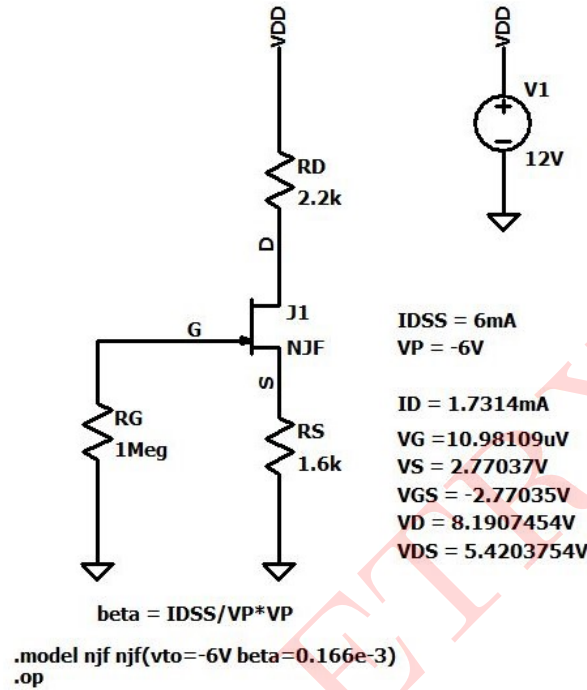


Figure 15: Circuit Schematic: Results

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_D	1.733mA	1.7314mA
V_{GS}	-2.774V	-2.77037V
V_D	8.18V	8.1907V
V_S	2.768V	2.7703V
V_{DS}	5.426V	5.4204V
V_G	0V	0.00001V

Table 6: Question 6

Numerical 7:

The transistor given in the circuit below in figure 16, has parameters $I_{DSS} = 8\text{mA}$ and $V_P = -4\text{V}$. Determine V_G , I_{DQ} , V_{GSQ} and V_{DSQ}

 


Figure 16: Circuit 7

Solution:

The above circuit is a voltage-bias configuration consisting of N-channel JFET.

To determine R_G and V_{TH} ,

$$\text{i.e } R_G = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{140\text{k} \times 60\text{k}}{140\text{k} + 60\text{k}} = 42\text{k}\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{60}{140 + 60} \times 20\text{V} = 6\text{V}$$

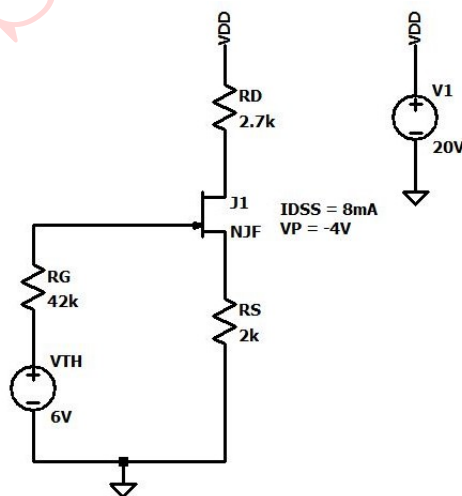


Figure 17: Thevenin's equivalent circuit

In JFET, current through gate is zero, i.e $I_G = 0$

Applying KVL in gate-source loop i.e input loop,

$$V_{TH} - I_G R_G - I_D R_S = 0 \quad (\because I_G = 0, I_G R_G = 0)$$

$$V_{TH} - V_{GS} - I_D R_S = 0$$

$$V_{GS} = V_{TH} - I_D R_S$$

$$V_{GS} = 6V - I_D(2k\Omega)$$

$$\therefore I_D = \frac{6 - V_{GS}}{2k\Omega}$$

In JFET,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 8mA \left(1 - \frac{V_{GS}}{-4}\right)^2$$

$$I_D = 8mA \left(1 + \frac{V_{GS}}{4}\right)^2$$

$$\frac{6 - V_{GS}}{2k\Omega} = 8mA \left(1 + \frac{V_{GS}}{4}\right)^2$$

$$6 - V_{GS} = (2 \times 10^{-3})(8 \times 10^{-3}) \left(1 + \frac{V_{GS}}{4}\right)^2$$

$$6 - V_{GS} = 16 \left(1 + \frac{V_{GS}}{2} + \frac{V_{GS}^2}{16}\right)$$

$$6 - V_{GS} = 16 + 8V_{GS} + V_{GS}^2$$

$$0 = 16 - 6 + 8V_{GS} + V_{GS}^2$$

$$0 = 10 + 9V_{GS} + V_{GS}^2$$

$$V_{GS} = -1.298V \text{ or } V_{GS} = -7.7015V$$

We reject the value $V_{GS} = -7.7015V$ $\because |V_{GS}| < |V_P|$

$$\therefore V_{GS} = -1.298V$$

$$I_D = \frac{6 - V_{GS}}{2k\Omega} = \frac{6 - (-1.293)}{2 \times 10^3} = 3.649mA$$

Applying KVL to drain source loop i.e output loop,

$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$V_{DS} = V_{DD} - I_D R_D - I_D R_S$$

$$= 20V - (3.649mA)(2.7k\Omega) - (3.649mA)(2k\Omega) = 2.8497V$$

$$V_{TH} = V_G = 6V$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below:

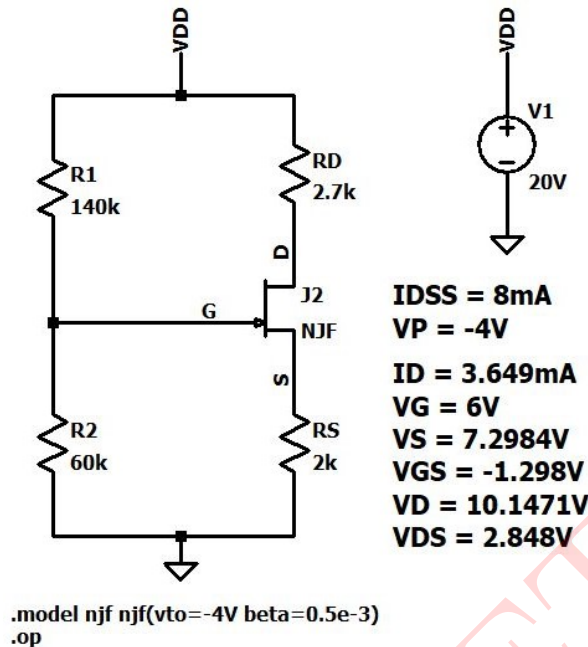


Figure 18: Circuit Schematic: Results

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_D	3.649mA	3.6492mA
V_{GS}	-1.298V	-1.29844V
V_{DS}	2.8497V	2.84366V
V_G	6V	6V

Table 7: Question 7

Numerical 8:

Consider the circuit given below in figure 19. The quiescent value of V_{DS} is found to be $V_{DSQ} = 5V$. If $I_{DSS} = 10mA$, determine I_{DQ} , V_{GSQ} and V_P

 


Figure 19: Circuit 8

Solution:

The above circuit 8 is a voltage-biased network consisting of a N-channel JFET.

For DC analysis all capacitors will be open circuited.

 


Figure 20: Thevenin's equivalent circuit

To find R_G and V_{TH} :

$$R_G = \frac{R_1 R_2}{R_1 + R_2} = \frac{450k\Omega \times 20k\Omega}{450k\Omega + 20k\Omega} = \mathbf{19.14k\Omega}$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{DD} = \frac{20k\Omega}{450k\Omega + 20k\Omega} \times 12V = \mathbf{0.51V}$$

Applying KVL to the drain-source loop i.e output loop,

$$\text{i.e } V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

$$12 - I_D(1k\Omega) - 5V - I_D(0.5k\Omega) = 0$$

$$7 - 1.5I_D \times 10^3 = 0$$

$$1.5 \times 10^3 I_D = 7$$

$$I_D = \frac{7}{1.5 \times 10^3} = \mathbf{4.66mA}$$

Applying KVL to the gate-source loop i.e input loop,

$$V_{TH} - I_G R_G - V_{GS} - I_D R_S = 0 \quad (\because I_G = 0, I_G R_G = 0)$$

$$\therefore V_{TH} - V_{GS} - I_D R_S = 0$$

$$V_{GS} = V_{TH} - I_D R_S$$

$$= 0.51V - (4.66mA)(0.5k\Omega) = 0.51 - 2.33 = \mathbf{-1.82V}$$

For JFET,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$4.66mA = 10mA \left(1 + \frac{1.82}{V_P}\right)^2$$

$$4.66 \times 10^{-3} = 10 \times 10^{-3} \left(1 + \frac{V_{GS}}{6}\right)^2$$

$$1 = \frac{10}{4.66} \left(\frac{V_P + 1.82}{V_P}\right)^2$$

$$1 = 2.145 \frac{(V_P + 1.82)^2}{V_P^2}$$

$$V_P^2 = 2.145(V_P + 1.82)^2$$

$$V_P^2 = 2.145(V_P^2 + 3.64V_P + 3.3124)$$

$$V_P^2 = 2.145V_P^2 + 7.8078V_P + 7.10598$$

$$0 = 1.145V_P^2 + 7.8078V_P + 7.10598$$

$$V_P = -1.08V \text{ or } V_P = -5.73V$$

We reject the value $V_P = -1.08V$ $\because |V_{GS}| < |V_P|$

$$\therefore V_P = \mathbf{-5.73V}$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below:

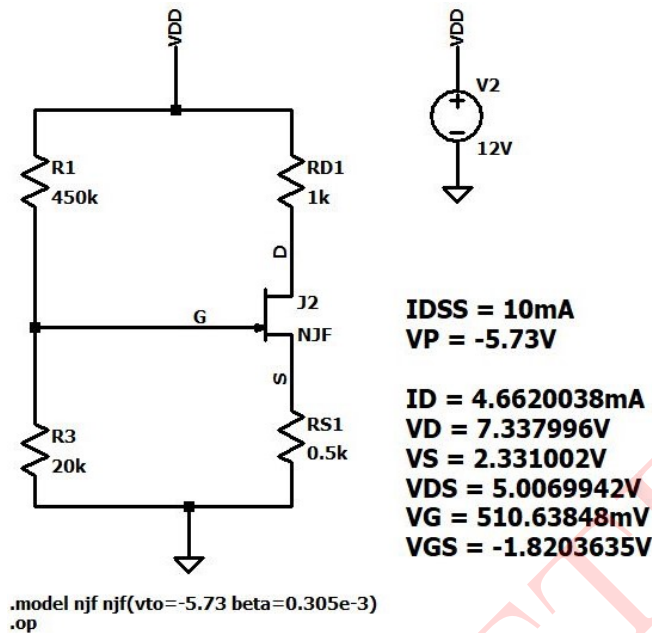


Figure 21: Circuit Schematic: Results

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_D	4.66mA	4.66200mA
V_{GS}	-1.82V	-1.8206V

Table 8: Question 8

Numerical 9:

The emitter follower for the circuit given below in figure 22 has $R_1 = 100k\Omega$, $R_2 = 150k\Omega$, $R_E = 750\Omega$, $R_L = 20k\Omega$, $R_C = 200\Omega$, $V_{CC} = 15V$ and $V_{BE} = 0.7V$. Assume that $\beta_F = 100$. Find the Q-point defined by I_B , I_C and V_{CE}

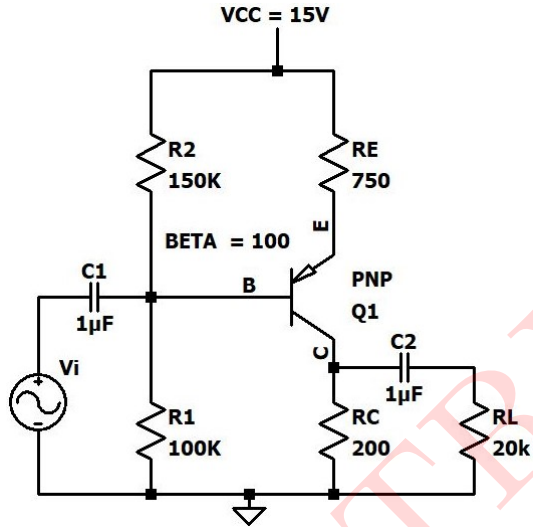


Figure 22: Circuit 9

Solution:

The above figure 22 is a circuit consisting of voltage bias configuration.

To find the parameters we need to perform DC analysis and for that we require a DC equivalent circuit.

For DC analysis all capacitors will be open circuited.

 


Figure 23: Thevenin's equivalent circuit

To find R_B and V_{TH} :

$$R_B = \frac{R_1 R_2}{R_1 + R_2} = \frac{100k\Omega \times 150k\Omega}{100k\Omega + 150k\Omega} = 60k\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{100k\Omega}{100k\Omega + 150k\Omega} \times 15V = 6V$$

Applying KVL to the emitter-base loop,

$$\text{i.e } V_{CC} - I_E R_E - V_{EB} - I_B R_B - V_{TH} = 0$$

$$15V - (1 + \beta)I_B(750\Omega) - 0.7V - I_B(60k\Omega) = 0$$

$$\therefore I_B = \frac{15V - 0.76V}{75750 + 60k} = 61.14\mu A$$

$$\therefore I_C = \beta I_B = 100(61.14\mu A) = 6.114mA$$

Applying KVL to the emitter-collector loop,

$$V_{CC} - I_E R_E - V_{EC} - I_C R_C = 0$$

$$\therefore V_{EC} = V_{CC} - (1 + \beta)I_B R_E - I_C R_C$$

$$\begin{aligned} \therefore V_{EC} &= 15V - (101)(61.14 \times 10^{-6})750 - (6.114 \times 10^{-3})(200) \\ &= 15 - 4.63 - 1.2228 = 9.147V \end{aligned}$$

$$\therefore V_{CE} = -9.147V$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below:

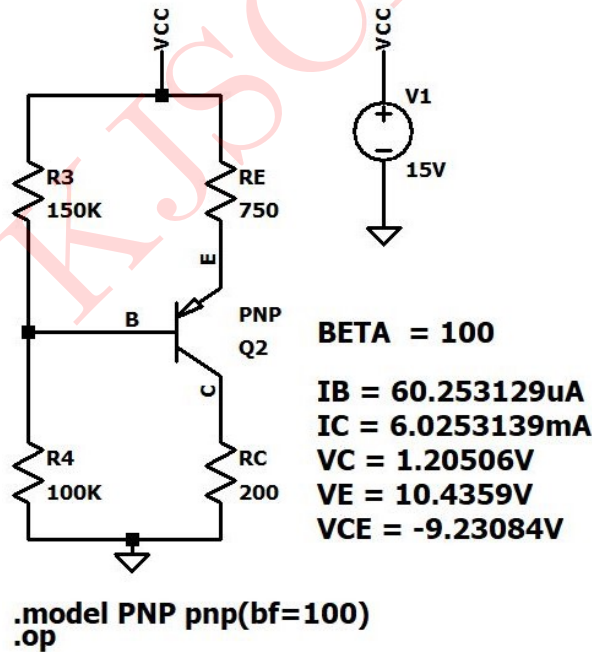


Figure 24: Circuit Schematic: Results

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_B	$61.14\mu\text{A}$	$60.253\mu\text{A}$
I_C	6.114mA	6.0253mA
V_{CE}	-9.147V	-9.23079V

Table 9: Question 9

KJSCE ETRX

Numerical 10:

The NMOS biasing circuit given below in figure 25 has $R_D = 1.5k\Omega$, $R_G = 500k\Omega$ and $V_{DD} = 12V$. The MOS parameters are $k_n = 0.5mA/V^2$, $V_{GS_{th}} = 1V$ and $\lambda = 0.01$. Determine the drain current I_D , the gate to source voltage V_{GS} and the drain to source voltage V_{DS}

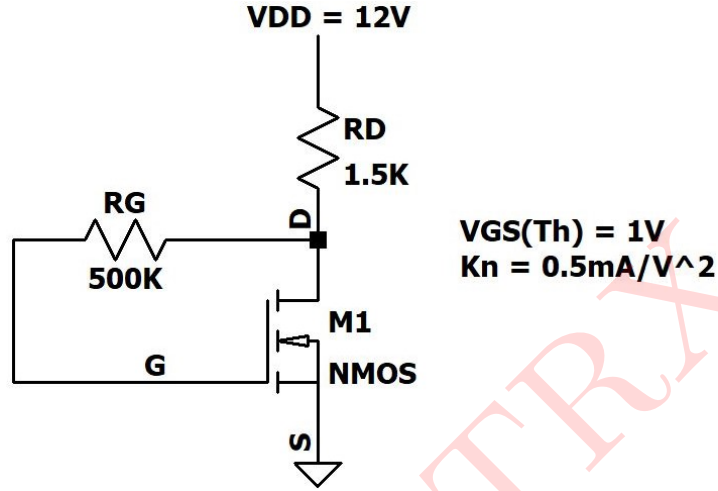


Figure 25: Circuit 10

Solution:

The above circuit in figure 25 is drain feedback bias consisting of N-channel E-MOSFET. The gate current is zero, $I_G = 0$

\therefore resistance R_G is redundant

$$\therefore V_{GS} = V_{DS} = V_{DD} - I_D R_D$$

$$\therefore V_{GS} = 12 - I_D(1.5k)$$

$$I_D = \frac{12 - V_{GS}}{1.5k}$$

In MOSFET,

$$\text{i.e } I_D = k_n(V_{GS} - V_{GS_{th}})^2(1 + \lambda V_{DS})$$

$$\frac{12 - V_{GS}}{1.5k} = k_n(V_{GS} - 1)^2(1 + \lambda V_{DS})$$

$$\frac{12 - V_{GS}}{1.5k} = 0.5m(V_{GS}^2 - 2V_{GS} + 1)(1 + 0.01V_{GS})$$

$$12 - V_{GS} = (0.5m)(1.5k)(V_{GS}^2 - 2V_{GS} + 1)(1 + 0.01V_{GS})$$

$$12 - V_{GS} = 0.75(0.01V_{GS}^3 + 0.98V_{GS}^2 - 1.99V_{GS} + 1)$$

$$12 - V_{GS} = (7.5 \times 10^{-3})V_{GS}^3 + 0.735V_{GS}^2 - 1.4925V_{GS} + 0.75$$

$$\therefore (7.5 \times 10^{-3})V_{GS}^3 + 0.735V_{GS}^2 - 1.4925V_{GS} - 11.25 = 0$$

$$V_{GS} = -98.51V \text{ or } V_{GS} = 4.1665V \text{ or } V_{GS} = -3.65V$$

$$V_{GS} = 4.1665V \quad (\because |V_{GS}| > |V_t|)$$

$$\therefore I_D = \frac{12 - V_{GS}}{1.5k} = \frac{12 - 4.166}{1.5k} = 5.22mA$$

$$V_{DS} = V_{GS} = 4.1665V$$

SIMULATED RESULTS:

The above circuit is simulated in LTspice whose results are given below:

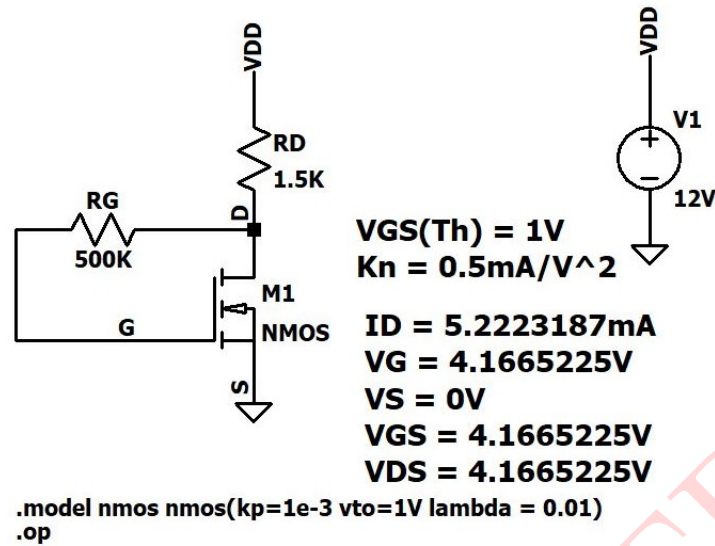


Figure 26: Circuit Schematic: Results

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
I_D	5.22mA	5.22231mA
V_{GS}	4.1665V	4.16652V
V_{DS}	4.1665V	4.16652V

Table 10: Question 10
