

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Cascade Amplifier Design

Numerical 1:

Design a two stage RC coupled cascade amplifier for following specifications: $A_v \geq 1700$, $V_{o_{rms}} = 2.5V$, $S \leq 10$, $f_L \geq 20Hz$. Use transistor BC147A from data sheet.

Solution:

1. Given Data:

$$A_V \geq 1700, V_{o_{rms}} = 2.5V, S \leq 10, f_L \geq 20Hz$$

2. Circuit Diagram and Selection of Transistor:

Transistor BC147A is selected with following specifications:

$$h_{FE(min)} = 115, h_{FE(typ)} = 180, h_{FE(max)} = 220$$

$$h_{ie} = 2.7k\Omega, V_{CE(sat)} = 0.25V$$

$$h_{fe(min)} = 125, h_{fe(typ)} = 220, h_{fe(max)} = 260$$

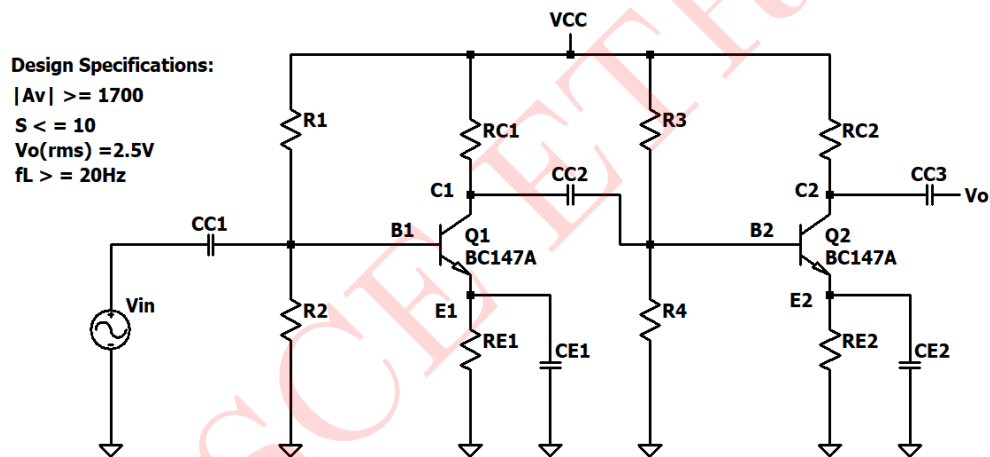


Figure 1: Circuit 1

3. Selection of Voltage gains:

$$A_{V_T} = A_{V_1} A_{V_2} = 1700$$

$$A_{V_1} = 0.5 A_{V_2} \implies A_{V_T} = 0.5 A_{V_2}^2$$

$$\text{i.e } 1700 = 0.5 A_{V_2}^2 \implies A_{V_2} = 58.30$$

$$A_{V_1} = \frac{A_{V_T}}{A_{V_2}} = \frac{1700}{58.3} = \mathbf{29.159}$$

$$\text{Let } A_{V_2} = 59 \text{ \& } A_{V_1} = 29$$

Design of 2nd stage:

4. Calculation of R_{C_2} :

$$|A_{V_2}| = \frac{h_{fe(typ)} \times R_{C_2}}{h_{ie}} = \frac{220 \times R_{C_2}}{2.7k\Omega}$$

$$59 = \frac{220 \times R_{C_2}}{2.7k\Omega}$$

$$R_{C_2} = \mathbf{724\Omega}$$

Select $R_{C_2} = 750\Omega, \frac{1}{4}W$

We select a higher standard value to increase the gain.

5. Selection of Q point (V_{CEQ_2} & I_{CQ_2})

$$V_{o_{peak}} = V_{o_{rms}} \times \sqrt{2} = 2.5 \times \sqrt{2} = \mathbf{3.5355V}$$

$$V_{CEQ_2} = 1.5 [V_{o_{peak}} + V_{CE(sat)}]$$

The value is multiplied by 1.5 to take care of saturation voltages, variation in resistance, variation in supply voltage & variation in device parameter variation.

$$V_{CEQ_2} = 1.5(3.5355 + 0.25) = \mathbf{5.68V}$$

$$I_{o_{peak}} = \frac{V_{o_{peak}}}{R_{C_2}} = \frac{3.5355V}{750\Omega} = \mathbf{4.714mA}$$

$$I_{CQ_2} \geq I_{o_{peak}} \quad [\text{For undistorted output signal}]$$

Select $I_{CQ_2} = \mathbf{4.8mA}$

6. Selection of DC power supply V_{CC} :

In order to achieve maximum symmetrical output swing, always select Q point at the center of DC load line.

$$\text{i.e } V_{CC} \geq 2V_{CEQ_2}$$

$$V_{CC} \geq 2 \times 5.68V$$

$$V_{CC} \geq 11.36$$

Select $V_{CC} = \mathbf{12V}$

7. Calculation of R_{E_2}

For proper operation,

$$V_{RE_2} = 10\% \text{ of } V_{CC}$$

$$V_{RE_2} = 0.1V_{CC} = 0.1 \times 12 = \mathbf{1.2V}$$

$$V_{RE_2} = R_{E_2} \times I_{EQ_2}$$

$$R_{E_2} = \frac{V_{RE_2}}{I_{EQ_2}} \approx \frac{V_{RE_2}}{I_{CQ_2}}$$

$$R_{E_2} = \frac{1.2V}{4.8mA} = \mathbf{250\Omega}$$

Selecting a lower standard value

$$\text{Select } R_{E_2} = \mathbf{220\Omega}, \frac{1}{4}\mathbf{W}$$

8. Calculation of Biasing Resistors R_3 & R_4

$$S = \frac{1 + h_{FE(typ)}}{1 + h_{FE(typ)} \left[\frac{R_{E_2}}{R_{E_2} + R_{B_2}} \right]}$$

$$R_{TH_2} = R_{B_2} = R_3 \parallel R_4$$

$$10 = \frac{1 + 180}{1 + 180 \left[\frac{220}{220 + R_{B_2}} \right]}$$

$$R_{TH_2} = R_{B_2} = 2.095k\Omega = \frac{R_3 R_4}{R_3 + R_4} \quad \dots(1)$$

$$V_{TH} = V_{B_2} = \frac{R_4 V_{CC}}{R_3 + R_4} \quad \dots(2)$$

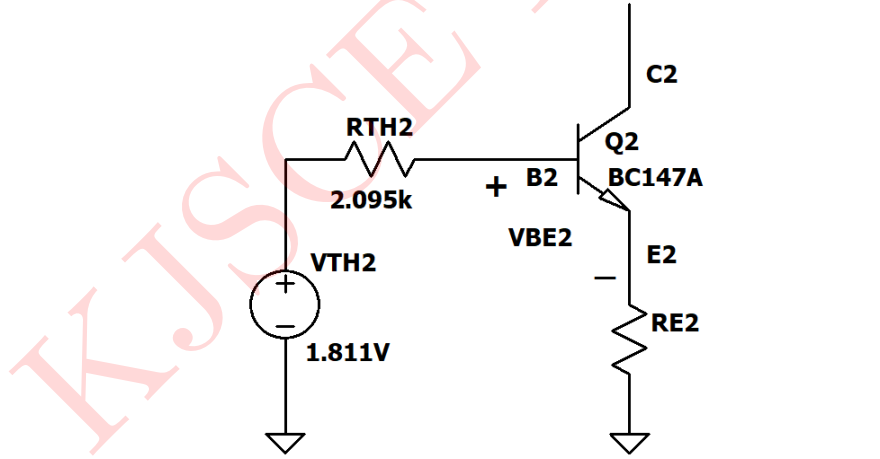


Figure 2: Thevenin's Equivalent Circuit for 2nd stage

Applying KVL at B-E loop of Q_2 ,

$$V_{TH_2} - I_{BQ_2} R_{TH_2} - V_{BE_2} - I_{EQ_2} R_{E_2} = 0$$

$$V_{TH_2} = I_{BQ_2} R_{B_2} + V_{BE_2} + I_{EQ_2} R_{E_2}$$

$$= V_{BE_2} + \frac{I_{CQ_2}}{\beta} R_{B_2} + I_{CQ_2} R_{E_2}$$

$$= 0.7 + \frac{4.8mA}{180} \times 2.095k\Omega + (4.8mA \times 220\Omega)$$

$$= \mathbf{1.811V}$$

From equation (2),

$$V_{TH_2} = V_{B_2} = 1.811V = \frac{R_4}{R_3 + R_4} \times 12V$$

$$\frac{R_4}{R_3 + R_4} = 0.1509 \quad \dots(3)$$

Substituting equation (3) in equation (1),

$$R_3 \times (0.1509) = 2.059k\Omega$$

$$R_3 = 13.6447k\Omega$$

Selecting a higher standard value so that circuit draws minimum current,

$$\text{Select } R_3 = 15k\Omega, \frac{1}{4}W$$

From equation (3),

$$\frac{R_4}{15k\Omega + R_4} = 0.1509$$

$$R_4 = 2.6657k\Omega$$

Selecting a lower standard value,

$$\text{Select } R_4 = 2.4k\Omega, \frac{1}{4}W$$

Design of 1st stage:

9. Selection of R_{C1}

$$\begin{aligned} |A_{V2}| &= \frac{h_{fe(typ)} \times R_{C2}}{h_{ie}} \\ &= \frac{220 \times 750}{2.7k\Omega} \\ &= 61.11 \end{aligned}$$

$$A_{V1} = \frac{A_{VT}}{A_{V2}} = \frac{1700}{61.11} = 27.818$$

Let $A_{V1} = 28$

$$|A_{V1}| = \frac{h_{fe(typ)} \times R_{L1}}{h_{ie}}$$

 


Figure 3: Small Signal Equivalent Circuit for selection of R_{C1}

$$\begin{aligned}
R_{L_1} &= R_{C_1} \parallel R_3 \parallel R_4 \parallel h_{ie} \\
&= R_{C_1} \parallel 15k\Omega \parallel 2.4k\Omega \parallel 2.7k\Omega \\
&= R_{C_1} \parallel 2.068k\Omega \parallel 2.7k\Omega \\
&= R_{C_1} \parallel 1.171k\Omega
\end{aligned}$$

$$\therefore 28 = \frac{220 \times R_{C_1} \times 1.171k\Omega}{2.7k\Omega(R_{C_1} + 1.171k\Omega)}$$

$$343.636 = \frac{R_{C_1} \times 1.171k\Omega}{R_{C_1} + 1.171k\Omega}$$

$$R_{C_1} = \mathbf{486.36\Omega}$$

Select a higher standard value,

$$\text{Select } R_{C_1} = \mathbf{510\Omega}, \frac{1}{4}\mathbf{W}$$

10. Calculation of R_{E_1} :

$$V_{CEQ_1} = V_{CEQ_2} = 5.68V$$

$$V_{RE_1} = V_{RE_2} = 1.2V$$

$$V_{RC_1} = V_{RC_2}$$

$$\therefore I_{CQ_1}R_{C_1} = I_{CQ_2}R_{C_2}$$

$$\begin{aligned}
I_{CQ_1} &= \frac{I_{CQ_2}R_{C_2}}{R_{C_1}} \\
&= \frac{4.8mA \times 750\Omega}{510\Omega} \\
&= \mathbf{7.058mA}
\end{aligned}$$

$$V_{RE_1} = I_{EQ_1}R_{E_1} = \mathbf{1.2V}$$

$$R_{E_1} = \frac{V_{RE_1}}{I_{EQ_1}} \approx \frac{V_{RE_1}}{I_{CQ_1}}$$

$$R_{E_1} = \frac{1.2V}{7.058mA} = \mathbf{170.019\Omega}$$

Select a lower standard value,

$$\text{Select } R_{E_1} = \mathbf{150\Omega}, \frac{1}{4}\mathbf{W}$$

11. Calculation of Biasing Resistors ($R_1 + R_2$):

$$S = \frac{1 + h_{FE(typ)}}{1 + h_{FE(typ)} \left[\frac{R_{E_1}}{R_{E_1} + R_{B_1}} \right]}$$

$$R_{B_1} = R_1 \parallel R_2$$

$$10 = \frac{1 + 180}{1 + 180 \left[\frac{150}{150 + R_{B_1}} \right]}$$

i.e $R_{TH1} = R_{B1} = 1428.947\Omega$

$$R_{TH1} = R_{B1} = \frac{R_1 R_2}{R_1 + R_2} = 1428.947\Omega \quad \dots(4)$$

$$V_{TH1} = V_{B1} = \frac{R_2}{R_1 + R_2} \times V_{CC} \quad \dots(5)$$

 


Figure 4: Thevenin's Equivalent Circuit for 1st stage

Applying KVL at B-E loop of Q_1 ,

$$V_{TH1} - V_{BE1} - I_{BQ1} R_{B1} - I_{EQ1} R_{E1} = 0$$

$$\begin{aligned} V_{TH1} &= V_{BE1} + \frac{I_{CQ1}}{\beta} R_{B1} + I_{CQ1} R_{E1} \\ &= 0.7 + \frac{7.058mA}{180} \times (1428.947\Omega) + (7.058mA \times 150\Omega) \\ &= \mathbf{1.8147V} \end{aligned}$$

From equation (5),

$$\begin{aligned} V_{TH1} = 1.8147V &= \frac{R_2}{R_1 + R_2} \times 12V \\ \frac{R_2}{R_1 + R_2} &= 0.1512 \quad \dots(6) \end{aligned}$$

Substituting equation (6) in equation (4),

$$\begin{aligned} R_1 \times (0.1512) &= 1428.947\Omega \\ R_1 &= 9.45k\Omega \end{aligned}$$

Select a higher standard value,

$$\text{Select } R_1 = \mathbf{10k\Omega}, \frac{1}{4}\mathbf{W}$$

From equation(6),

$$\frac{R_2}{R_1 + R_2} = 0.1512$$

$$\frac{R_2}{10k + R_2} = 0.1512$$

$$R_2 = 1.781k\Omega$$

Select a lower standard value,

$$\text{Select } R_2 = 1.5k\Omega, \frac{1}{4}W$$

12. Calculation of coupling capacitors:

a. Calculation of C_{C_1}

 


Figure 5: Small Signal Equivalent Circuit for C_{C_1}

$$C_{C_1} = \frac{1}{2\pi R_{eq} f_L}$$

$$\begin{aligned} R_{eq} &= R_1 \parallel R_2 \parallel h_{ie} \\ &= 10k\Omega \parallel 1.5k\Omega \parallel 2.7k\Omega \\ &= 1.304k\Omega \parallel 2.7k\Omega \\ &= 879.32\Omega \end{aligned}$$

$$C_{C_1} = \frac{1}{2\pi \times 879.32\Omega \times 20} = 9.049\mu F$$

Selecting a higher standard value

$$\text{Select } C_{C_1} = 10\mu F / 24V$$

b. Calculation of C_{C_2} :

$$C_{C_2} = \frac{1}{2\pi R_{eq} f_L}$$

$$\begin{aligned} R_{eq} &= R_{C_1} + R_3 \parallel R_4 \parallel h_{ie} \\ &= 510k\Omega + 15k\Omega \parallel 2.4k\Omega \parallel 2.7k\Omega \\ &= 510k\Omega + 2.068k\Omega \parallel 2.7k\Omega \\ &= 510k\Omega + 1.171k\Omega \\ &= 1.681k\Omega \end{aligned}$$

 


Figure 6: Small Signal Equivalent Circuit for C_{C2}

$$C_{C2} = \frac{1}{2\pi \times 1.681k\Omega \times 20Hz} = 4.733\mu F$$

Selecting a higher standard value,

Select $C_{C2} = 6.8\mu F/24V$

c. Calculation of C_{C3} :

 


Figure 7: Small Signal Equivalent Circuit for C_{C3}

$$C_{C3} = \frac{1}{2\pi \times R_{eq} \times f_L}$$

$$R_{eq} = R_{C2} = 750\Omega$$

$$C_{C3} = \frac{1}{2\pi \times 750 \times 20} = 10.61\mu F$$

Selecting a higher standard value,

Select $C_{C3} = 12\mu F/24V$

13. Calculation of Bypass Capacitors:

a. C_{E1} :

$$X_{CE1} = \frac{R_{E1}}{10}$$

[To ensure complete bypass of R_E , $X_{CE} < R_E$]

$$\text{i.e } \frac{1}{2\pi f_L C_{E1}} = 0.1R_{E1}$$

$$\begin{aligned}
C_{E_1} &= \frac{1}{2\pi \times f_L \times 0.1R_{E_1}} \\
&= \frac{1}{2\pi \times 20 \times 0.1 \times 150} \\
&= 530.516\mu F
\end{aligned}$$

Selecting a higher standard value

Select $C_{E_1} = 560\mu F/24V$

b. CE_2 :

$$X_{CE_2} = \frac{R_{E_2}}{10} \Rightarrow X_{CE_2} = 0.1R_{E_2}$$

$$\text{i.e. } \frac{1}{2\pi f_L C_{E_2}} = 0.1R_{E_2}$$

$$\begin{aligned}
C_{E_2} &= \frac{1}{2\pi f_L \times 0.1R_{E_2}} \\
&= \frac{1}{2\pi \times 20 \times 0.1 \times 220} \\
&= 361.715\mu F
\end{aligned}$$

Selecting a higher standard value

Select $C_{E_2} = 470\mu F/24V$

14. Complete Designed Circuit:

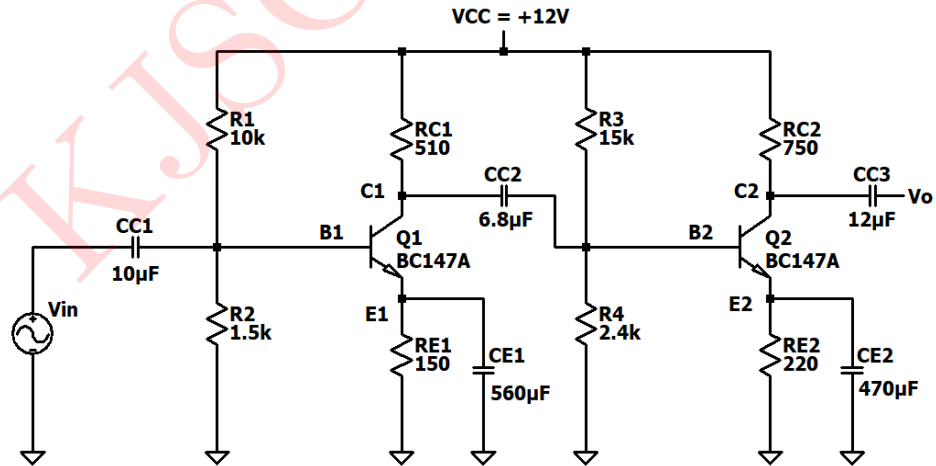


Figure 8: Designed Circuit

DC Analysis:

For 1st stage:

$$R_{TH_1} = 10k\Omega \parallel 1.5k\Omega = 1.304k\Omega$$

$$V_{TH_1} = \frac{R_2}{R_1 + R_2} \times V_{CC} = 1.565V$$

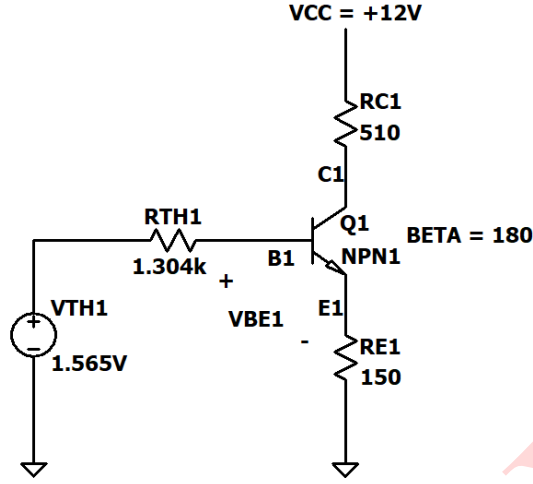


Figure 9: DC Equivalent Circuit for 1st stage

Applying KVL at B-E loop of Q_1 ,

$$V_{TH1} - I_{B1}R_{TH1} - V_{BE1} - I_{E1}R_{E1} = 0$$

$$V_{TH1} - I_{B1}R_{TH1} - V_{BE1} - (1 + \beta_1)I_{B1}R_{E1} = 0$$

$$\begin{aligned} I_{B1} &= \frac{V_{TH1} - V_{BE1}}{R_{TH1} + (1 + \beta_1)R_{E1}} \\ &= \frac{1.565 - 0.7}{1.304k\Omega + (181 \times 150)} \\ &= \mathbf{30.399\mu A} \end{aligned}$$

$$I_{C1} = \beta_1 I_{B1} = 180 \times 30.399\mu A = \mathbf{5.47mA}$$

$$I_{E1} = I_{C1} + I_{B1} = 5.47mA + 30.399\mu A = \mathbf{5.5mA}$$

$$V_{E1} = I_{E1}R_{E1} = 5.5mA \times 150 = \mathbf{0.825V}$$

$$V_{BE} = 0.7V = V_{B1} - V_{E1} = \mathbf{1.525V}$$

For 2nd stage:

Applying KVL at B-E loop of Q_2 ,

$$V_{TH2} - I_{B2}R_{TH2} - V_{BE2} - I_{E2}R_{E2} = 0$$

$$V_{TH2} - I_{B2}R_{TH2} - V_{BE2} - (1 + \beta_2)I_{B2}R_{E2} = 0$$

 


Figure 10: DC Equivalent Circuit for 2nd stage

$$I_{B_2} = \frac{V_{TH_2} - V_{BE_2}}{R_{TH_2} + (1 + \beta_2)R_{E_2}}$$

$$\begin{aligned} V_{TH_2} &= \frac{R_3}{R_3 + R_4} \times V_{CC} \\ &= \frac{2.4k\Omega}{15k\Omega + 2.4k\Omega} \times 12V \\ &= \mathbf{1.655V} \end{aligned}$$

$$R_{TH_2} = R_3 \parallel R_4 = 15k\Omega \parallel 2.4k\Omega = \mathbf{2.068k\Omega}$$

$$I_{B_2} = \frac{1.655 - 0.7}{2.068 + (181 \times 220)} = \mathbf{22.798\mu A}$$

$$I_{C_2} = \beta_2 I_{B_2} = 180 \times 22.798\mu A = \mathbf{4.1mA}$$

$$I_{E_2} = I_{C_2} + I_{B_2} = 4.1mA + 22.798\mu A = \mathbf{4.722mA}$$

$$V_{E_2} = I_{E_2} R_{E_2} = 4.722mA \times 220\Omega = \mathbf{1.0388V}$$

$$V_{BE_2} = 0.7V = V_{B_2} - V_{E_2} = \mathbf{1.7388V}$$

Small Signal Parameters:

$$g_{m_1} = \frac{I_{C_1}}{V_T} = \frac{5.47mA}{0.026V} = 210.384mA/V$$

$$r_{\pi_1} = \frac{\beta_1 V_T}{I_{C_1}} = \frac{180 \times 0.026V}{5.47mA} = 855.575\Omega$$

$$g_{m_2} = \frac{I_{C_2}}{V_T} = \frac{4.1mA}{0.026V} = 157.692mA/V$$

$$r_{\pi_2} = \frac{\beta_2 V_T}{I_{C_2}} = \frac{180 \times 26mV}{4.1mA} = 1.141k\Omega$$

Mid Frequency AC Equivalent Circuit:

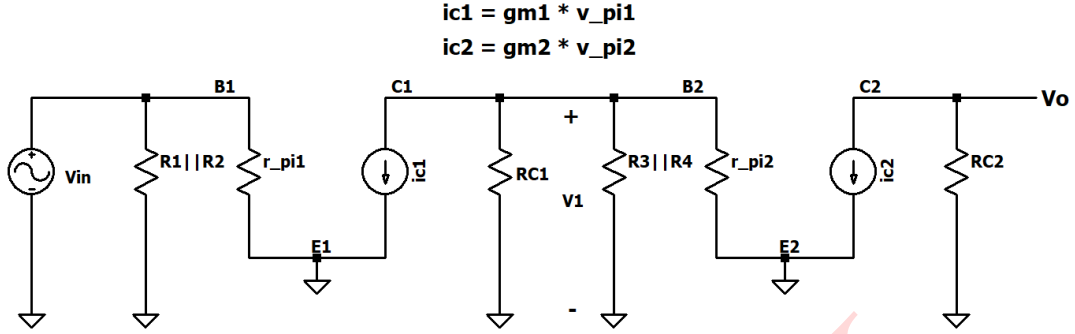


Figure 11: Small Signal Equivalent Circuit

Voltage gain of 1st stage: $Av_1 = \frac{V_1}{V_{in}}$

$$Av_1 = \frac{V_1}{V_{in}} = \frac{-g_{m1} V_{\pi_1} (R_{C1} \parallel R_3 \parallel R_4 \parallel r_{\pi_2})}{V_{\pi_1}}$$

$$Av_1 = -g_{m1} (R_{C1} \parallel R_3 \parallel R_4 \parallel r_{\pi_2})$$

$$= -(210.384 \text{ mA/V}) (510 \parallel 15 \parallel 2.4 \parallel 1.141 \text{ k}\Omega)$$

$$= -(210.384 \text{ mA/V}) (301.155 \Omega)$$

$$= \mathbf{-63.358}$$

Voltage gain of 2nd stage: $Av_2 = \frac{V_o}{V_1}$

$$Av_2 = \frac{-g_{m2} V_{\pi_2} R_{C2}}{V_{\pi_2}}$$

$$= -g_{m2} R_{C2}$$

$$= -(157.692 \text{ mA/V}) (750 \Omega)$$

$$= \mathbf{-118.269}$$

Overall Voltage Gain: $Av_T = \frac{V_o}{V_{in}}$

$$Av_T = Av_1 \times Av_2$$

$$= (-63.358) \times (-118.269)$$

$$= \mathbf{7493.287} \quad (\geq 1700)$$

$$Av_T \text{ in dB} = 20 \log_{10} (Av_T) = \mathbf{77.493 \text{ dB}}$$

Input Impedance of 1st stage: Z_i

$$Z_i = R_1 \parallel R_2 \parallel r_{\pi_1}$$

$$= 10 \text{ k}\Omega \parallel 1.5 \text{ k}\Omega \parallel 855.575 \Omega$$

$$= \mathbf{516.67 \Omega}$$

Output Impedance of 2nd stage: Z_o

$$Z_o = R_{C_2}$$

$$Z_o = 750\Omega$$

SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

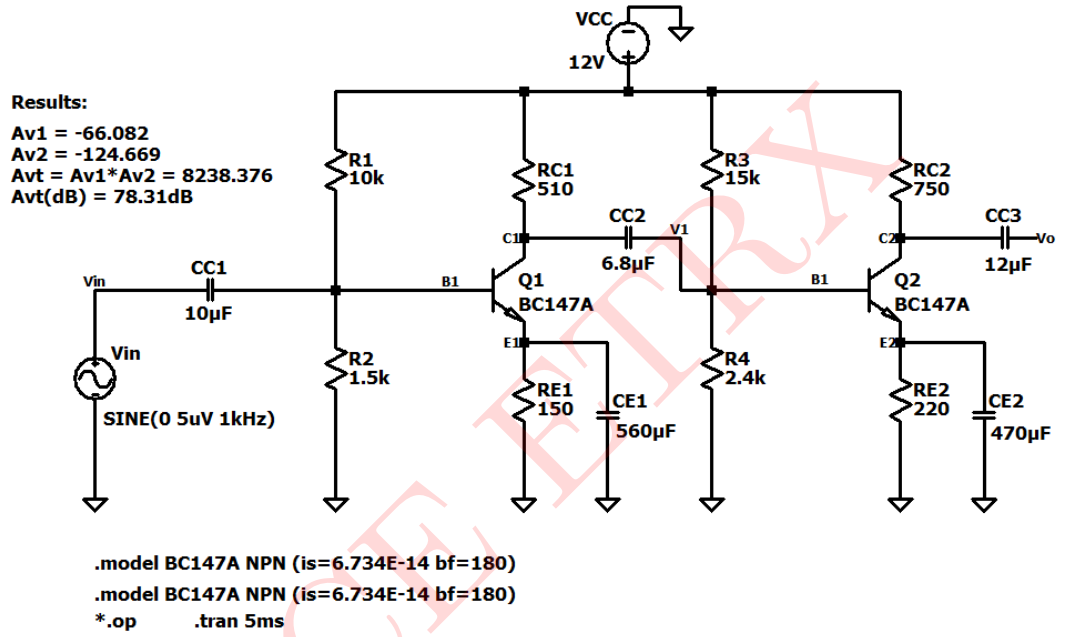


Figure 12: Circuit Schematic

 


Figure 13: Input Output waveform of 1st stage

 


Figure 14: Input Output waveform of 2nd stage

Comparison of Theoretical and Simulated results:

Parameters	Theoretical	Simulated
I_{B1}, I_{B2}	$30.399\mu A, 22.798\mu A$	$32.12\mu A, 24.14\mu A$
I_{C1}, I_{C2}	$5.47mA, 4.1mA$	$5.78mA, 4.34mA$
I_{E1}, I_{E2}	$5.5mA, 4.722mA$	$5.81mA, 4.37mA$
V_{E1}, V_{E2}	$0.825V, 1.0388V$	$0.872V, 0.9614V$
V_{B1}, V_{B2}	$1.525V, 1.7388V$	$1.5233V, 1.6052V$
Voltage gain of 1 st stage: Av_1	-63.358	-66.082
Voltage gain of 2 nd stage: Av_2	-118.269	-124.669
Overall Voltage gain: Av_T in dB	77.493dB	78.31dB
Input Impedance of 1 st stage: Z_i	516.67Ω	—
Output Impedance of 2 nd stage: Z_o	750Ω	—

Table 1: Numerical 1

Numerical 2:

Design a two stage RC coupled cascade amplifier for following specifications: $A_v \geq 480$, $V_{CC} = 20V$, $S \leq 10$, $R_i \geq 1M\Omega$. Select a suitable transistor from data sheet

Solution:

Above requirements can be fulfilled by CS-CE stage

We select CS as 1st stage since $R_i \geq 1M\Omega$

1. Circuit Diagram and Selection of Transistor:

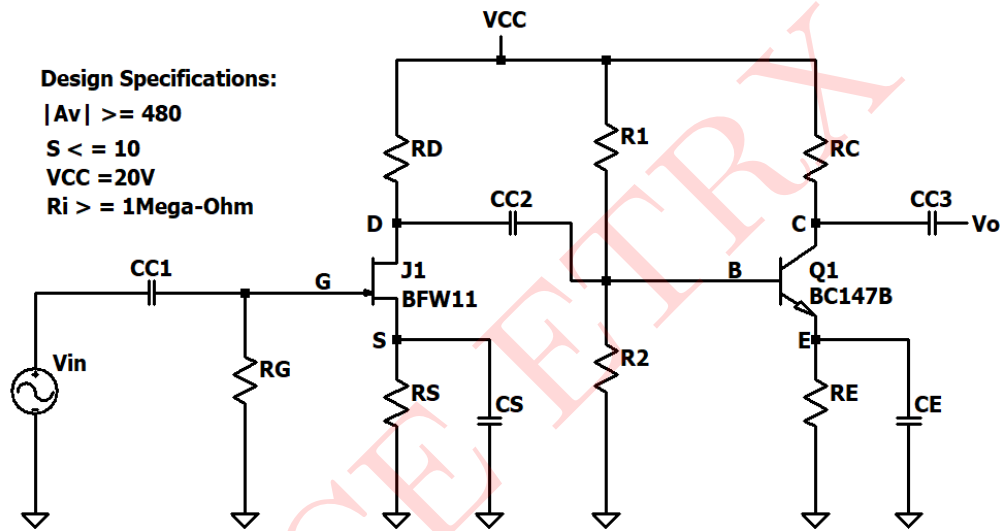


Figure 15: Circuit 1

Select BC147B since its $h_{fe(typ)}$ & h_{ie} is higher, its specifications are:

$$h_{fe(typ)} = 330, h_{FE(typ)} = 290 = \beta$$

$$h_{ie} = 4.5k\Omega, V_{CE(sat)} = 0.25V$$

Select BFW11, its specifications are:

$$I_{DSS} = 7mA, g_{mo} = 5600\mu S$$

$$V_p = -2.5V, r_d = 50k\Omega$$

3. Selection of gains:

$$A_v \geq 480$$

Let $A_{v1} = 4$ [Since JFET amplifier gain is less]

$$\text{i.e } A_{v2} = \frac{480}{4} = 120$$

$$\text{Let } A_{v2} = 125$$

Design of 2nd stage:

3. Selection of R_C :

$$|A_{V_2}| = \frac{h_{fe(typ)} \times R_C}{h_{ie}}$$

$$125 = \frac{330 \times R_C}{4.5k\Omega}$$

$$R_C = 1.704k\Omega$$

Selecting a higher standard value,

Select $R_C = 1.8k\Omega, \frac{1}{4}W$

4. Selection of Q point (V_{CEQ} & I_{CQ})

$$V_{CC} = 20V$$

$$\text{Let } V_{CEQ} = \frac{V_{CC}}{2} = 10V$$

$$V_{RE} = 0.1V_{CC} = 0.1 \times 20 = 2V$$

 


Figure 16: DC Equivalent Circuit for selection of Q point

Applying KVL to CE loop of BJT,

$$V_{CC} - V_{RC} - V_{CEQ} - V_{RE} = 0$$

$$V_{RC} = V_{CC} - V_{CEQ} - V_{RE}$$

$$= 20 - 10 - 2$$

$$= 8V$$

$$\text{i.e } V_{RC} = I_{CQ}R_C = 8$$

$$I_{CQ} = \frac{V_{RC}}{R_C} = \frac{8}{1.8k\Omega} = 4.44mA$$

5. Selection of R_E :

$$V_{RE} = 2V$$

$$I_{EQ}R_E = 2 \implies R_E = \frac{2}{I_{CQ}} \quad [\because I_{CQ} \approx I_{EQ}]$$

$$R_E = 450.45\Omega$$

Selecting a lower standard value,

$$\text{Select } R_E = 420\Omega, \frac{1}{4}\text{W}$$

6. Selection of Biasing Resistors R_1 & R_2

$$S \leq 10$$

$$\text{Let } S = 9, \beta = 290$$

$$S = \frac{1 + \beta}{1 + \beta \left[\frac{R_E}{R_E + R_B} \right]}$$

$$9 = \frac{1 + 290}{1 + 290 \left[\frac{420}{420 + R_B} \right]}$$

$$R_B = 3.467k\Omega$$

$$R_{TH} = R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = 3.467k\Omega \quad \dots(1)$$

$$V_{TH} = V_B = \frac{R_2 V_{CC}}{R_1 + R_2} \quad \dots(2)$$

 


Figure 17: Thevenin's Equivalent Circuit

Applying KVL at B-E loop of BJT,

$$V_{TH} - I_{BQ}R_{TH} - V_{BE} - I_{EQ}R_E = 0$$

$$\begin{aligned} V_{TH} &= \frac{I_{CQ}}{\beta} R_{TH} + V_{BE} + I_{CQ}R_E \\ &= \frac{4.44mA}{290} \times (3.467k\Omega) + 0.7V + (4.44mA \times 420) \\ &= \mathbf{2.617V} \end{aligned}$$

From equation (2),

$$V_{TH} = 2.617 = \frac{R_2}{R_1 + R_2} \times 20V$$

$$\frac{R_2}{R_1 + R_2} = 0.13 \quad \dots(3)$$

Substituting equation (3) in equation (1),

$$R_1 \times (0.13) = 3.467k\Omega$$

$$R_1 = 26.669k\Omega$$

$$\text{Select } R_1 = \mathbf{27k\Omega}, \frac{1}{4}\mathbf{W}$$

From equation (3),

$$\frac{R_2}{27k\Omega + R_2} = 0.13$$

$$R_2 = 4.034k\Omega$$

Selecting a higher standard value,

$$\text{Select } R_2 = \mathbf{4.2k\Omega}, \frac{1}{4}\mathbf{W}$$

Design of 1st stage:

7. Selection of Q point (I_{DQ} & V_{GSQ})

Using mid point biasing,

$$I_{DQ} = \frac{I_{DSS}}{2} = \frac{7mA}{2} = \mathbf{3.5mA}$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$\begin{aligned} V_{GSQ} &= V_p \left(1 - \sqrt{\frac{I_{DQ}}{I_{DSS}}}\right) \\ &= -2.5 \left(1 - \sqrt{\frac{3.5mA}{7mA}}\right) \\ &= \mathbf{-0.732V} \end{aligned}$$

$$\begin{aligned}
g_m &= g_{mo} \left(1 - \frac{V_{GSQ}}{V_p} \right) \\
&= (5600 \times 10^{-6}) \left(1 - \frac{(-0.732V)}{-2.5V} \right) \\
&= \mathbf{3.96mA/V}
\end{aligned}$$

8. Selection of R_D :

$$|A_{V_2}| = \frac{h_{fe(typ)} \times R_C}{h_{ie}} = \frac{330 \times 1.8k\Omega}{4.5k\Omega} = 132$$

$$|A_{V_1}| = \frac{A_V}{|A_{V_2}|} = \frac{480}{132} = 3.636$$

 


Figure 18: Small Signal Equivalent Circuit for selection of R_D

$$|A_{V_1}| = g_m [R_D \parallel R_1 \parallel R_2 \parallel r_d \parallel h_{ie}]$$

$$\begin{aligned}
R_{L_1} &= r_d \parallel R_1 \parallel R_2 \parallel h_{ie} \\
&= 50k\Omega \parallel 27k\Omega \parallel 4.2k\Omega \parallel 4.5k\Omega \\
&= 17.532k\Omega \parallel 2.172k\Omega \\
&= \mathbf{1.932k\Omega}
\end{aligned}$$

$$|A_{V_1}| = g_m [R_D \parallel 1.932k\Omega]$$

$$3.636 = (3.96mA/V) \left[\frac{R_D \times 1.932k\Omega}{R_D + 1.932k\Omega} \right]$$

$$918.181 = \frac{R_D \times 1.932k\Omega}{R_D + 1.932k\Omega}$$

$$R_D = \mathbf{1.749k\Omega}$$

Select a higher standard value,

Select $R_D = \mathbf{2.2k\Omega}$, $\frac{1}{4}\mathbf{W}$

9. Selection of R_S

$$V_{GSQ} = -I_{DQ}R_S$$

$$-0.732 = -3.5mA \times R_S$$

$$R_S = 209.14\Omega$$

Selecting a lower standard value,

$$\text{Select } R_S = 180\Omega, \frac{1}{4}W$$

10. Selection of R_G

$$\text{Let } R_G = 1.2M\Omega, \frac{1}{4}W \quad [\text{Since } R_i = 1M\Omega \text{ to prevent loading we take } R_G \geq 1M\Omega]$$

11. Selection of Coupling capacitors:

Since f_L is not given we consider audio frequency $f_L = 20Hz$

a. C_{C_1}

 


Figure 19: Small Signal Equivalent Circuit for C_{C_1}

$$\begin{aligned} C_{C_1} &= \frac{1}{2\pi R_G f_L} \\ &= \frac{1}{2\pi \times 1.2 \times 10^6 \times 20} \\ &= 6.63nF \end{aligned}$$

Selecting a higher standard value

$$\text{Select } C_{C_1} = 6.8nF/50V$$

b. C_{C_2}

$$\begin{aligned} C_{C_2} &= \frac{1}{2\pi \times R_{eq} \times f_L} \\ R_{eq} &= (r_d \parallel R_D) + R_1 \parallel R_2 \parallel h_{ie} \\ &= 50k\Omega \parallel 2.2k\Omega + 27k\Omega \parallel 4.2k\Omega \parallel 4.5k\Omega \\ &= 2.107k\Omega + 2.010k\Omega \\ &= 4.117k\Omega \end{aligned}$$

 


Figure 20: Small Signal Equivalent Circuit for C_{C_2}

$$C_{C_2} = \frac{1}{2\pi \times 4.117k\Omega \times 20Hz} = 1.932\mu F$$

Selecting a higher standard value,

Select $C_{C_2} = 2.2\mu F/50V$

c. C_{C_3}

 


Figure 21: Small Signal Equivalent Circuit for C_{C_3}

$$C_{C_3} = \frac{1}{2\pi \times R_{eq} \times f_L}$$

$$R_{eq} = R_C = 1.8k\Omega$$

$$C_{C_3} = \frac{1}{2\pi \times 1.8k\Omega \times 20} = 4.42\mu F$$

Selecting a higher standard value,

Select $C_{C_3} = 4.7\mu F/50V$

12. Selection of Bypass Capacitors:

a. C_S :

$$C_S = \frac{1}{2\pi \times R_{eq} \times f_L}$$

$$\begin{aligned}
R_{eq} &= \left(\frac{1}{g_m} \parallel R_S \right) \\
&= \left(\frac{1}{3.96 \times 10^{-3}} \parallel 180 \right) \\
&= 252.52 \parallel 180 \\
&= \mathbf{105.09\Omega}
\end{aligned}$$

$$C_S = \frac{1}{2\pi \times 105.09 \times 20} = 75.72\mu F$$

Selecting a higher standard value,

Select $C_S = \mathbf{82\mu F/50V}$

a. C_E :

$$X_{CE} = 0.1R_E$$

[Ensures complete bypass of R_E]

$$\text{i.e. } \frac{1}{2\pi f_L C_E} = 0.1R_E$$

$$C_E = \frac{1}{2\pi f_L 0.1R_E} = \frac{1}{2\pi \times 20 \times 0.1 \times 420}$$

Selecting a higher standard value

Select $C_E = \mathbf{220\mu F/50V}$

13. Complete Designed Circuit:

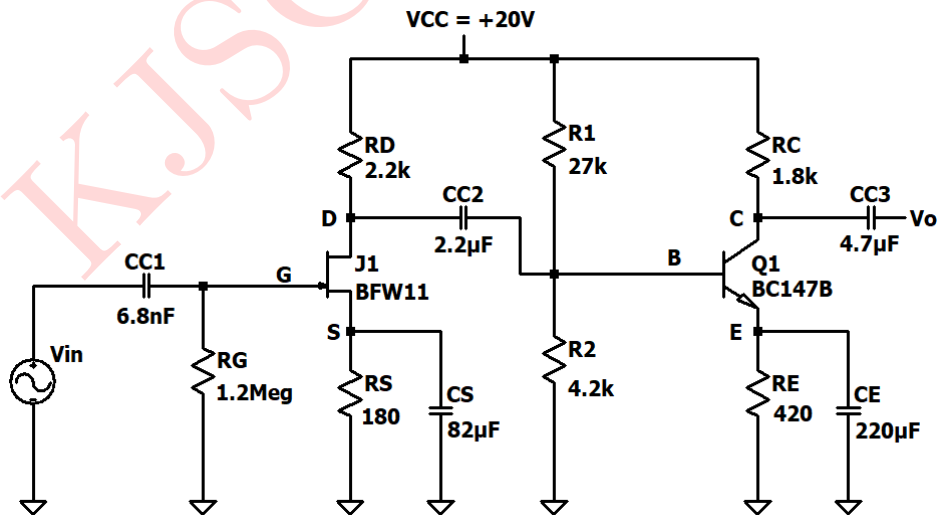


Figure 22: Designed Circuit

DC Analysis:

For 1st stage:

Applying KVL at G-S loop,

$$V_{GS} - I_D R_S = 0$$

$$V_{GS} = I_D R_S$$

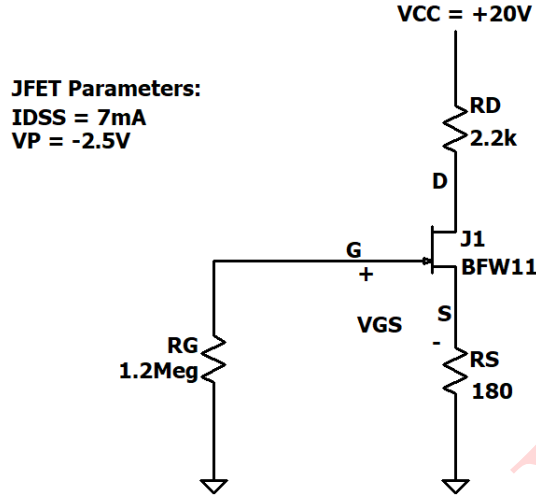


Figure 23: DC Equivalent Circuit for 1st stage

$$V_G - V_S = I_D R_S$$

$$V_G = 0, \text{ since } I_G = 0, \therefore V_{GS} = -V_S$$

$$V_{GS} = -I_D R_S$$

.....(1)

$$\text{Now, } I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = (7\text{mA}) \left(1 + \frac{V_{GS}}{2.5} \right)^2$$

.....(2)

Substituting equation(2) in equation(1),

$$\begin{aligned} I_{GS} &= -(7\text{mA} \times 180\Omega) \left(1 + \frac{V_{GS}}{2.5} \right)^2 \\ &= -1.26 \left(1 + \frac{V_{GS}}{2.5} \right)^2 \\ &= -1.26 \left(1 + \frac{V_{GS}^2}{6.25} + \frac{2V_{GS}}{2.5} \right) \\ &= -1.26 - 0.2016V_{GS}^2 - 1.008V_{GS} \end{aligned}$$

$$0.2016V_{GS}^2 + 2.008V_{GS} + 1.26 = 0$$

$$V_{GS} = -0.67\text{V} \quad \text{or} \quad V_{GS} = -9.28\text{V}$$

$$\therefore V_{GS} > V_P, \therefore V_{GSQ} = -0.67\text{V}$$

From equation (1),

$$V_{GS} = -I_D R_S$$

$$-0.67\text{V} = -I_D(180\Omega)$$

$$I_{DQ} = 3.722\text{mA}$$

For 2nd stage:

 


Figure 24: DC Equivalent Circuit for 2nd stage

$$R_{TH} = R_1 \parallel R_2 = 27k\Omega \parallel 4.2k\Omega = 3.634k\Omega$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{CC} = 2.692V$$

Applying KVL at B-E loop,

$$V_{TH} - I_B R_{TH} - V_{BE} - I_E R_E = 0$$

$$V_{TH} - I_B R_{TH} - V_{BE} - (1 + \beta) I_B R_E = 0$$

$$\begin{aligned} I_B &= \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E} \\ &= \frac{2.692 - 0.7}{3.634k\Omega + (291 \times 420)} \\ &= 15.827\mu A \end{aligned}$$

$$I_C = \beta I_B = 290 \times 15.827\mu A = 4.589mA$$

$$I_E = I_B + I_C = 4.589mA + 15.827\mu A = 4.6mA$$

$$V_E = I_E R_E = 4.6mA \times 420\Omega = 1.932V$$

$$V_{BE} = 0.7V = V_B - V_E$$

$$V_B = V_{BE} + V_E = 2.632V$$

Small Signal Parameters:

For 1st stage:

$$g_m = \frac{2I_{DSS}}{|V_p|} \left(1 - \frac{V_{GS}}{V_p} \right) = \frac{2 \times 7mA}{2.5V} \left(1 - \frac{0.67}{2.5} \right) = 4.09mA/V$$

$$r_d = 50k\Omega \quad [\text{Given}]$$

$$r_d = \frac{1}{\lambda I_{DQ}}$$

$$\lambda = \frac{1}{r_d \times I_{DQ}} = \frac{1}{50k\Omega \times 3.722mA} = 5.373mV^{-1}$$

For 2nd stage:

$$g_m = \frac{I_C}{V_T} = \frac{4.589mA}{0.026V} = 176.5mA/V$$

$$r_\pi = \frac{\beta V_T}{I_C} = \frac{290 \times 26mV}{4.589mA} = 1.643k\Omega$$

Mid Frequency AC Equivalent Circuit:

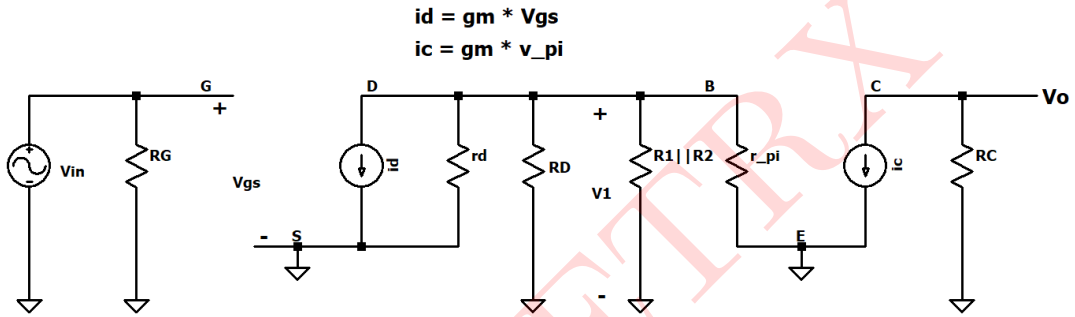


Figure 25: Small Signal Equivalent Circuit

Voltage gain of 1st stage: $Av_1 = \frac{V_1}{V_{in}}$

$$Av_1 = \frac{V_1}{V_{in}} = \frac{-g_m V_{gs} (r_d \parallel R_D \parallel R_1 \parallel R_2 \parallel r_\pi)}{V_{gs}}$$

$$Av_1 = -g_{m1} (r_d \parallel R_D \parallel R_1 \parallel R_2 \parallel r_\pi)$$

$$= -(4.09mA/V)(50k\Omega \parallel 2.2k\Omega \parallel 27k\Omega \parallel 4.2k\Omega \parallel 1.643k\Omega)$$

$$= -(4.09mA/V)(2.107k\Omega \parallel 3.634k\Omega \parallel 1.643k\Omega)$$

$$= -(4.09mA/V)(736.1439\Omega)$$

$$= -3.01$$

Voltage gain of 2nd stage: $Av_2 = \frac{V_o}{V_1}$

$$Av_2 = \frac{-g_m V_\pi R_C}{V_\pi}$$

$$= -g_m R_C$$

$$= -(176.5mA/V)(1.8k\Omega)$$

$$= -317.7$$

Overall Voltage Gain: $Av_T = \frac{V_o}{V_{in}}$

$$Av_T = Av_1 \times Av_2$$

$$= (-3.01) \times (-317.7)$$

$$= 956.277$$

$$Av_T \text{ in dB} = 20 \log_{10}(Av_T) = 20 \log_{10} 965.277 = 59.611 \text{ dB}$$

Input Impedance of 1st stage: Z_i

$$Z_i = R_G = 1.2 \text{ M}\Omega$$

Output Impedance of 2nd stage: Z_o

$$Z_o = R_C$$

$$Z_o = 1.8 \text{ k}\Omega$$

SIMULATED RESULTS

The above circuit is simulated in LTspice and results are presented below:

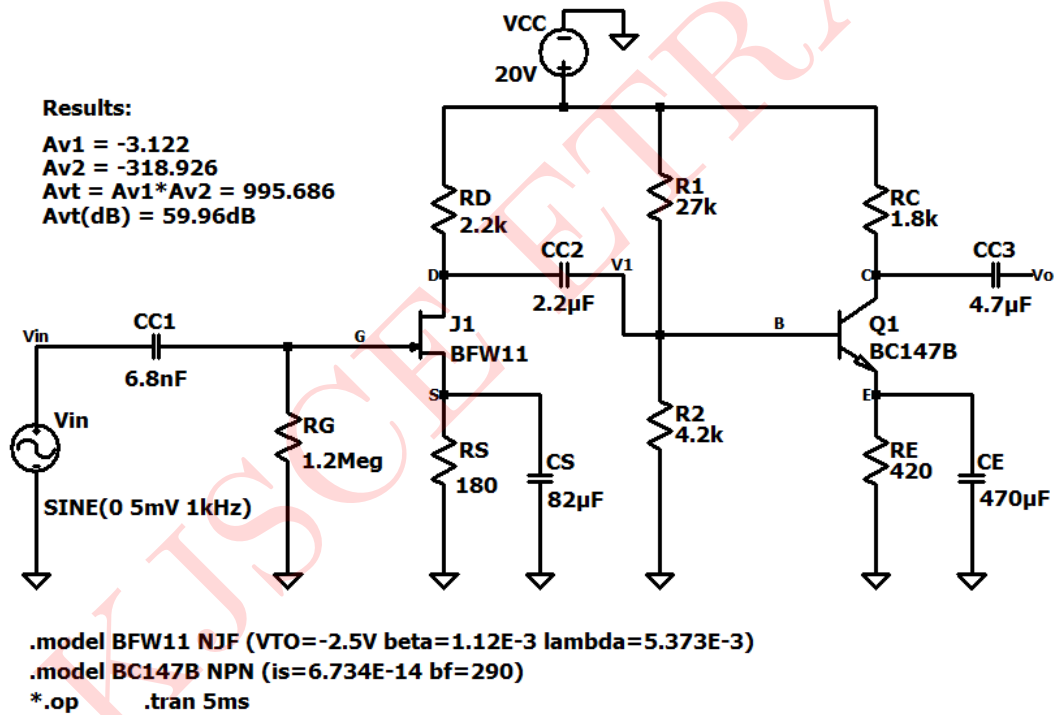


Figure 26: Circuit Schematic

 


Figure 27: Input Output waveform of 1st stage

 


Figure 28: Input Output waveform of 2nd stage

Comparison of Theoretical and Simulated results:

Parameters	Theoretical	Simulated
I_{DQ}, V_{GSQ}	$3.722mA, -0.67V$	$3.86mA, -0.694V$
I_B	$15.827\mu A$	$16.26\mu A$
I_C	$4.589mA$	$4.715mA$
V_E	$1.932V$	$1.987V$
V_B	$2.632V$	$2.633V$
Voltage gain of 1 st stage: Av_1	-3.01	-3.122
Voltage gain of 2 nd stage: Av_2	-317.7	-318.926
Overall Voltage gain: Av_T in dB	$59.611dB$	$59.96dB$
Input Impedance of 1 st stage: Z_i	$1.2M\Omega$	—
Output Impedance of 2 nd stage: Z_o	$1.8k\Omega$	—

Table 2: Numerical 2
