

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DIODE APPLICATIONS

Numerical 1: Simulate a half wave rectifier circuit with input amplitude = 100V, $f = 50\text{Hz}$, $R_L = 75\Omega$. Select diode as 1N4148. Use 10:1 step down transformer.

Plot the following:

- Primary peak Voltage
- Secondary peak Voltage
- Output voltage across Resistor
- Output voltage across Diode
- Current through the circuit

Also calculate the efficiency.

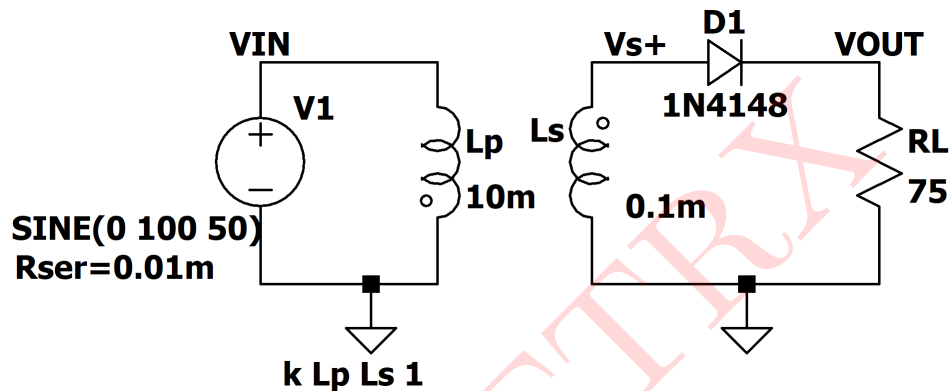


Figure 1: Circuit 1

Solution:

$$V_{m_{peak}} = 100V$$

For the secondary peak voltage, as the coils of the transformer are in ratio of 10:1

$$V_{m_{sec}} = \frac{V_m}{10} = 10V$$

$$\text{Peak inverse voltage} = -V_m = -10V$$

For the peak current,

$$I_m = \frac{V_m}{(R_S + R_L)}$$

$$I_m = \frac{10}{0.01m\Omega + 75\Omega}$$

$$I_m = 0.1333A$$

$$I_m = 133.33mA$$

$$\text{AC power} = \left(\frac{I_m}{2} \right)^2 \times (R_S + R_L)$$

$$\text{AC power} = 0.333W$$

$$\text{DC power} = \left(\frac{I_m}{\pi} \right)^2 \times R_L$$

$$\text{DC power} = 0.1358\text{W}$$

$$\% \eta = \frac{\text{DC power}}{\text{AC power}} \times 100$$

$$\% \eta = \frac{0.1358}{0.333} \times 100$$

$$\% \eta = 40.5280\%$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the result obtained are as follows:

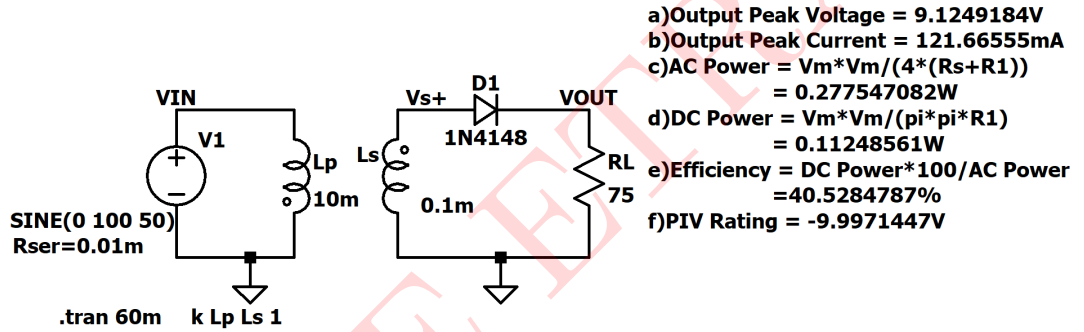


Figure 2: Circuit Schematic and Simulated Results

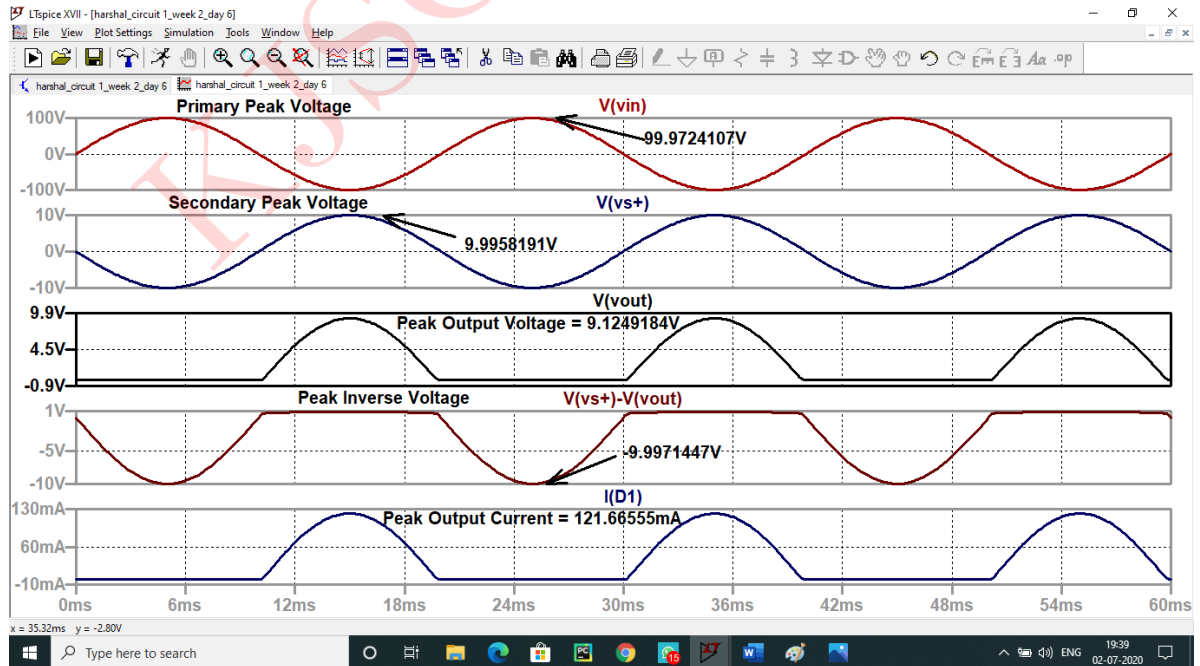


Figure 3: Plots in LTSpice

Comparison of Theoretical and Simulated values:

Parameters	Theoretical Values	Simulated Values
Output Peak Value(V_m)	10V	9.1247V
Output Peak Current (I_m)	133.33mA	121.665mA
AC Power	0.333W	0.27754W
DC Power	0.13508W	0.11248W
Efficiency	40.5280%	40.5284%
PIV Rating	-10V	-9.997144V

Table 1: Numerical 1

Numerical 2: Simulate a full wave rectifier circuit with input amplitude = 150V, frequency = 50Hz, $R_L = 150\Omega$.

Select the diode as 1N4148. Use 10:1 step down center tap transformer. Plot the following:

- Primary Peak Voltage
- Secondary Peak Voltage
- Output Voltage across the resistor
- Output Voltage across the diodes
- Current flowing through the diodes.

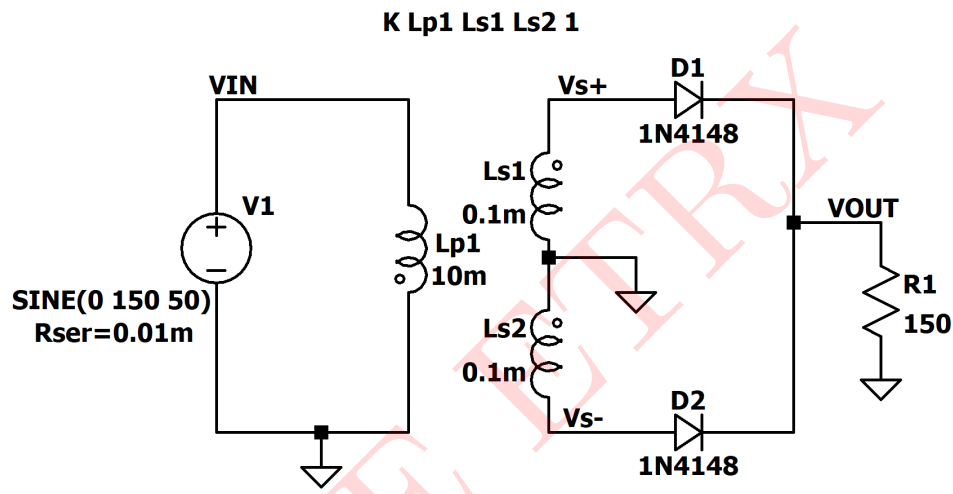


Figure 4: Circuit 1

Solution:

$V_{m_{peak}} = 150V$ (Primary Peak Voltage)

For the secondary peak voltage, as the coils of the transformer are in ratio of 10:1

$$V_{m_{sec}} = \frac{V_m}{10} = 15V$$

Peak inverse voltage = $2 \times -V_m = 2 \times -15 = -30V$

For the peak current,

$$I_m = \frac{V_m}{(R_S + R_L)}$$

$$I_m = 0.0999A$$

$$I_m = 99.99mA$$

$$AC \text{ power} = \left(\frac{I_m}{2} \right)^2 \times (R_S + R_L)$$

$$AC \text{ power} = 0.7499W$$

$$\text{DC power} = 4 \times \left(\frac{I_m}{\pi^2} \right)^2 \times R_1$$

$$\text{DC power} = 0.60791\text{W}$$

$$\% \eta = \frac{\text{DC power}}{\text{AC power}} \times 100$$

$$\% \eta = \frac{0.6079}{0.7499} \times 100$$

$$\% \eta = 81.0654\%$$

SIMULATED RESULTS:

The given circuit is simulated in LTSpice and the result obtained are as follows:

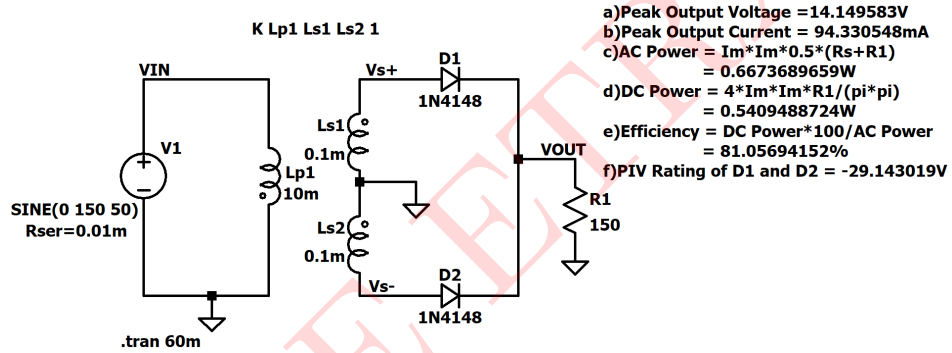


Figure 5: Circuit Schematic and Simulated Results

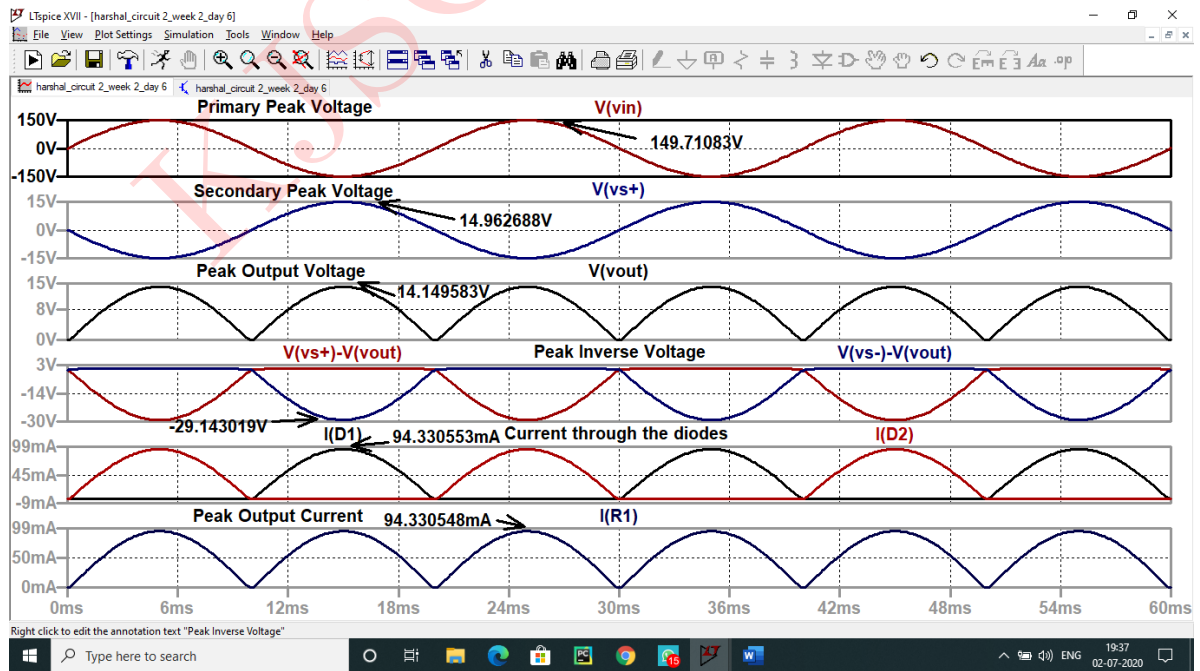


Figure 6: Plots in LTSpice

Comparison of Theoretical and Simulated values:

Parameters	Theoretical Values	Simulated Values
Output Peak Value(V_m)	15V	14.149V
Output Peak Current (I_m)	99.99mA	94.33054mA
AC Power	0.7499W	0.6673W
DC Power	0.6079W	0.54094W
Efficiency	81.0654%	81.0569%
PIV Rating	–30V	–29.143V

Table 2: Numerical 2
