

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
DC CIRCUITS

Numerical 1:

- Using the nodal analysis, determine the total circuit current I for the circuit shown in the Figure 1.
- Show the current directions for every resistance in the circuit.

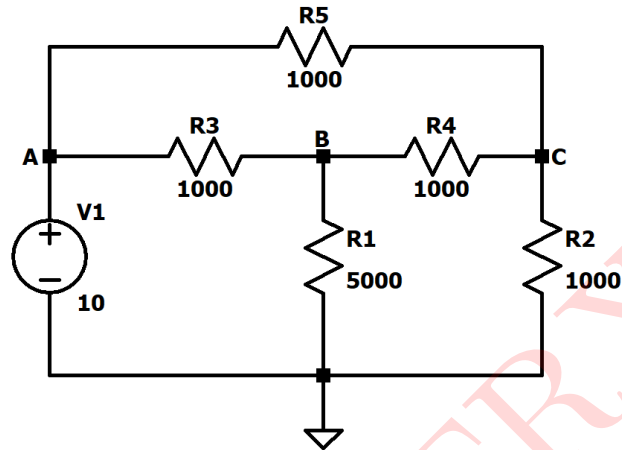


Figure 1: Circuit 1

Solution:

Using Nodal analysis:

Applying KCL at node A:

$$V_B = 10V$$

As voltage source is directly connected between node A and reference node (ref)

Applying KCL at node B:

$$\frac{V_B - V_A}{1000} + \frac{V_B - V_C}{1000} + \frac{V_B}{5000} = 0$$

$$\frac{V_B - 10}{1000} + \frac{V_B - V_C}{1000} + \frac{V_B}{5000} = 0$$

$$11V_B - 5V_C = 50 \quad \text{.....(i)}$$

Applying KCL at node C:

$$\frac{V_C - V_A}{1000} + \frac{V_C - V_B}{1000} + \frac{V_C}{1000} = 0$$

$$V_C - 10 + V_C - V_B + V_C = 0$$

$$3V_C - V_B = 10 \quad \text{.....(ii)}$$

Solving equation(i) and equation(ii), We have

$$V_B = 7.142857V$$

$$V_C = 5.71429V$$

Hence,

$$I(R_5) = \frac{V_C - V_A}{1000} = \frac{5.71429 - 10}{1000} = -0.00428571A$$

$$I(R_4) = \frac{V_C - V_B}{1000} = \frac{5.71429 - 7.142857}{1000} = -0.00142857A$$

$$I(R_3) = \frac{V_B - V_A}{1000} = \frac{7.142857 - 10}{1000} = -0.00285714A$$

$$I(R_2) = \frac{V_C}{1000} = \frac{5.71429}{1000} = -0.00571429A$$

$$I(R_1) = \frac{V_B}{5000} = \frac{7.1428571}{5000} = -0.00142857A$$

$$\begin{aligned} I(V_1) &= I(R_5) + I(R_3) \\ &= -0.00428571 - 0.0028571 \\ &= -0.00714286 \end{aligned}$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

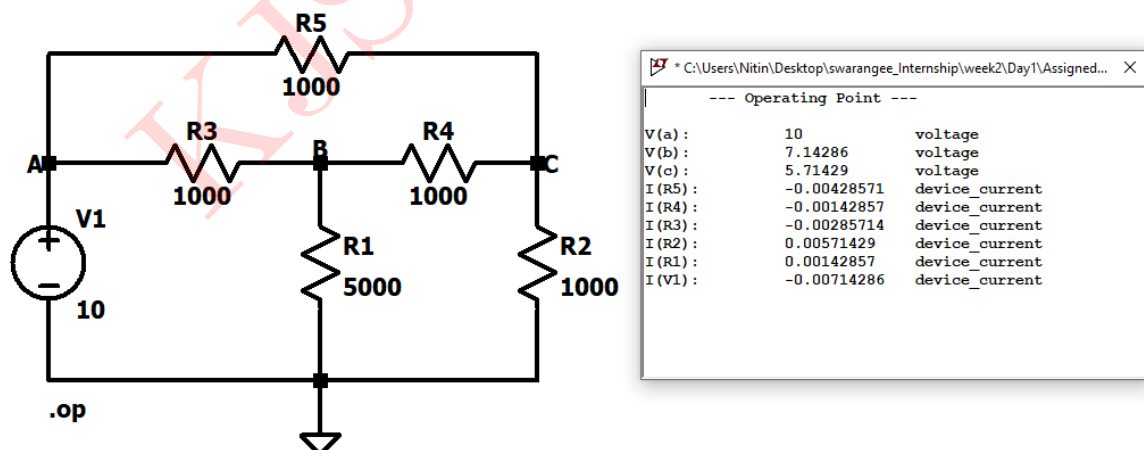


Figure 2: Circuit schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|--------------------|--------------------|------------------|
| V(A) | 10V | 10V |
| V(B) | 7.14286V | 7.1428V |
| V(C) | 5.71429V | 5.71429V |
| I(R ₅) | −0.00428571A | −0.00428571A |
| I(R ₄) | −0.00142857A | −0.00142557A |
| I(R ₃) | −0.00285714A | −0.00285714A |
| I(R ₂) | 0.00571429A | 0.00571429A |
| I(R ₁) | 0.00142857A | 0.00142857A |
| I(R _I) | −0.00714286A | −0.00741286A |

Table 1: Numerical 1

Numerical 2: Using Maxwell's loop current method, calculate the output V_o for the circuit shown in the Figure 3

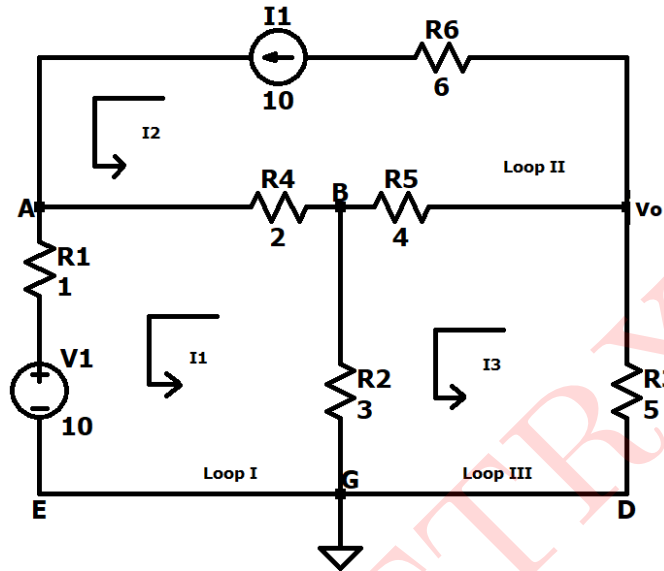


Figure 3: Circuit 2

Solution:

Using Maxwell's loop current method:

In loop II:

$$\mathbf{I_2 = 10A}$$

*Current source is present in a mesh not common to any other loop. Hence, KVL cannot be applied as voltage drop is unknown.

Applying KVL in loop I:

$$-10 - I_1 - 2(I_1 - I_2) - 3(I_1 - I_3) = 0$$

$$-10 - I_1 - 2(I_1 - 10) - 3(I_1 - I_2) = 0$$

$$6I_1 - 3I_3 = 10 \quad \dots(i)$$

Applying KVL in loop III,

$$-5I_3 - 4(I_3 - I_2) - 3(I_3 - I_1) = 0$$

$$-5I_3 - 4(I_3 - 10) - 3(I_3 - I_1) = 0$$

$$12I_3 - 3I_1 = 40 \quad \dots(ii)$$

On solving equation(i) and equation(ii), we get

$$\mathbf{I_1 = 3.80952A}$$

$$\mathbf{I_3 = 4.28571A}$$

Hence,

$$I(V_1) = I_1 = 3.80592A$$

$$I(R_1) = I_1 = 3.80592A$$

$$I(R_2) = I_3 - I_1 = 0.49619A$$

$$I(R_3) = -I_3 = -4.28571A$$

$$I(R_4) = I_1 - 10 = -6.19048A$$

$$I(R_5) = I_3 - 10 = -5.71429A$$

$$I(R_6) = I_2 = 10A$$

$$I(I_1) = I_2 = 10A$$


$$\begin{aligned} V_A &= V_B + (I(R_4) \times R_4) \\ &= 1.42857 + (-6.19048 \times 2) \\ &= 13.8095V \end{aligned}$$

$$\begin{aligned} V_B &= I(R_2) \times R_2 \\ &= 0.47619 \times 3 \\ &= 1.42857V \end{aligned}$$

$$\begin{aligned} V_o &= V_C = I(R_3) \times R_3 \\ &= -4.28571 \times 5 \\ &= -21.42855V \end{aligned}$$

SIMULATED RESULTS:

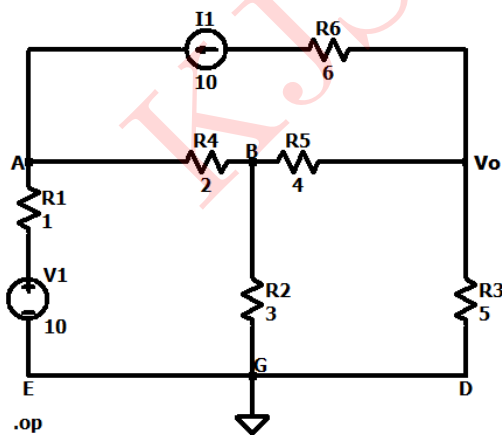Above circuit is simulated in LTspice. The results are presented below:



| --- Operating Point --- | | |
|-------------------------|----------|----------------|
| V(n002) : | 10 | voltage |
| V(a) : | 13.8095 | voltage |
| V(b) : | 1.42857 | voltage |
| V(vout) : | -21.4286 | voltage |
| V(n001) : | -81.4286 | voltage |
| I(I1) : | 10 | device_current |
| I(R6) : | 10 | device_current |
| I(R5) : | -5.71429 | device_current |
| I(R4) : | -6.19048 | device_current |
| I(R3) : | -4.28571 | device_current |
| I(R2) : | 0.47619 | device_current |
| I(R1) : | 3.80952 | device_current |
| I(V1) : | 3.80952 | device_current |

Figure 4: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $I(R_1)$ | 3.80952A | 3.80952A |
| $I(R_2)$ | 6.47619A | 6.47619A |
| $I(R_3)$ | -4.28571A | -4.28571A |
| $I(R_4)$ | -6.10948A | -6.10948A |
| $I(R_5)$ | -5.71429A | -5.71429A |
| V_o | -21.42855V | -21.42855V |

Table 2: Numerical 2

Numerical 3: Using Maxwell's loop current method, calculate the output V_o for the circuit shown in the Figure 5.

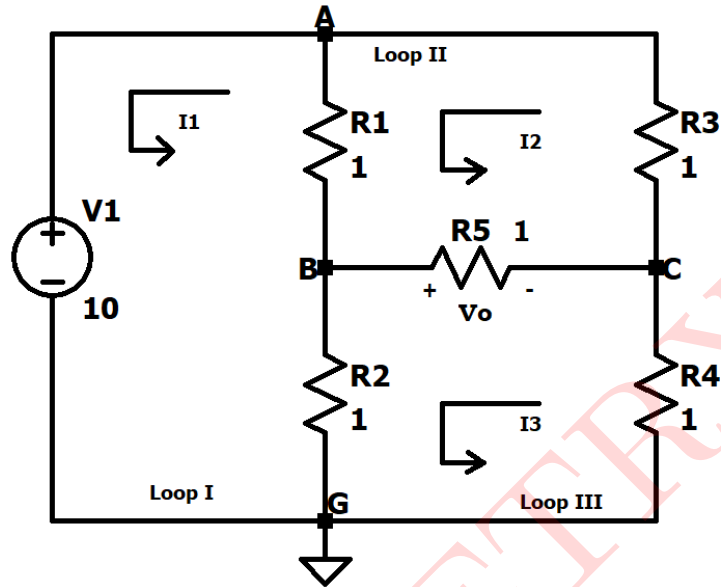


Figure 5: Circuit 3

Solution:

Using Maxwell's loop current method:

Let us assume in this case $V = 10V$

*Although the final value of V_o remains same irrespective of the value of the V assumed

Applying KVL in Loop I:

$$-10 - (I_1 - I_2) - (I_1 - I_3) = 0$$

$$-2I_1 + I_2 + I_3 = 10 \quad \dots(i)$$

Applying KVL in Loop II:

$$-I_2 - (I_2 - I_3) - (I_2 - I_1) = 0$$

$$I_1 - 3I_2 + I_3 = 0 \quad \dots(ii)$$

Applying KVL in Loop III:

$$-I_3 - (I_3 - I_2) - (I_3 - I_1) = 0$$

$$I_1 + I_2 - 3I_3 = 0 \quad \dots(iii)$$

On solving equation(i) , equation(ii) and equation(iii), we get

$$I_1 = 10A$$

$$I_2 = 5A$$

$$I_3 = 5A$$

Hence,

$$V_A = V_{assume} = 10V$$

$$V_B = I(R_1) \times R_1 = 1 \times 5 = 5V$$

$$V_C = I(R_3) \times R_3 = 1 \times 5 = 5V$$

$$I(R_5) = I_3 - I_2 = 5 - 5 = 0A$$

$$I(R_4) = I_3 = 5A$$

$$I(R_3) = I_2 = 5A$$

$$I(R_2) = I_1 - I_3 = 10 - 5 = 5A$$

$$I(R_1) = I_1 - I_2 = 10 - 5 = 5A$$

$$I(V_1) = -I_1 = -10A$$

$$V_o = I(R_5) \times R_5$$

$$= 0 \times 1$$

$$= 0V$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

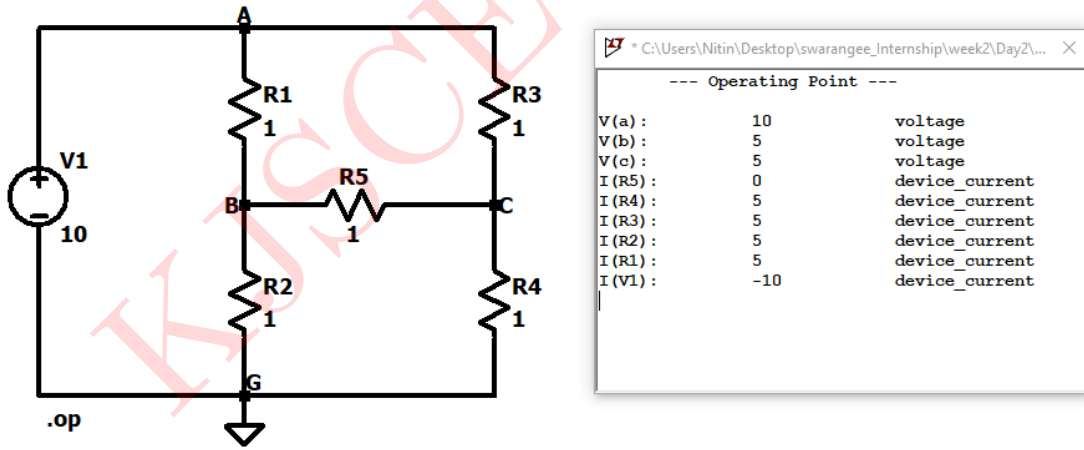


Figure 6: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| V_A | 10V | 10V |
| V_B | 5V | 5V |
| V_C | 5V | 5V |
| $I(R_5)$ | 0A | 0A |
| $I(R_4)$ | 5A | 5A |
| $I(R_3)$ | 5A | 5A |
| $I(R_2)$ | 5A | 5A |
| $I(R_1)$ | 5A | 5A |
| V_o | 0V | 0V |

Table 3: Numerical 3

Numerical 4: For the circuit shown in figure 7, find the equivalent resistance.

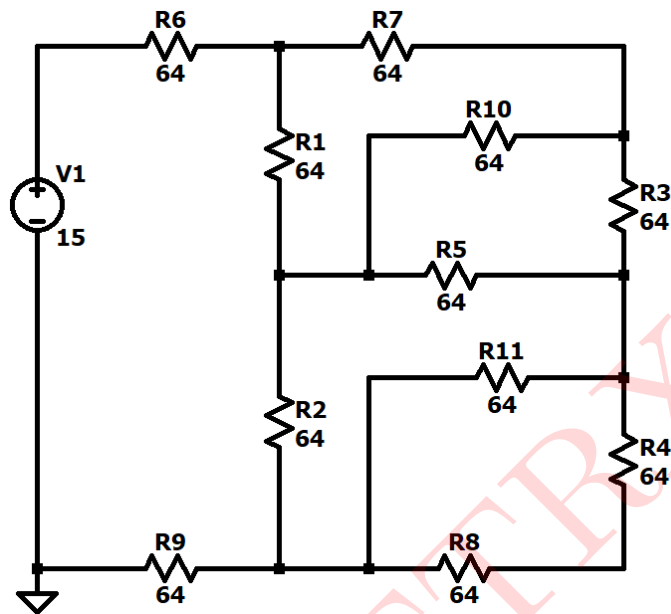


Figure 7: Circuit 4

Solution:

In Figure 8:

Converting the series circuit

$$R_S = 64 + 64 = 128\Omega$$

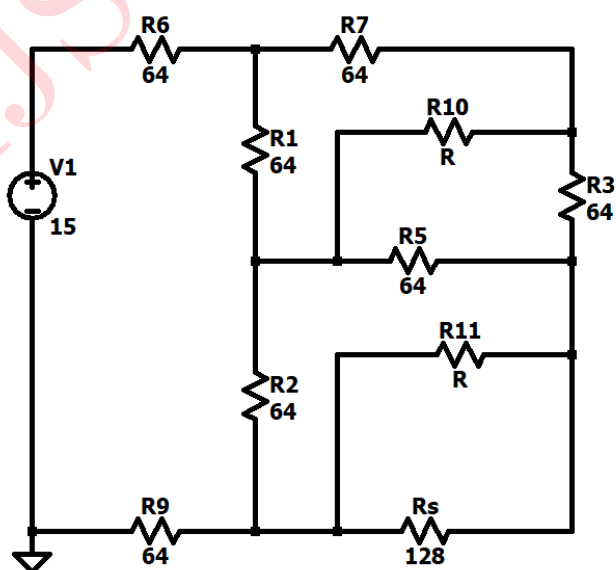


Figure 8: Modified Circuit after adding series resistances

In Figure 9:

Converting the parallel circuit

$$\frac{1}{R_P} = \frac{1}{128} + \frac{1}{64} = 42.67\Omega$$

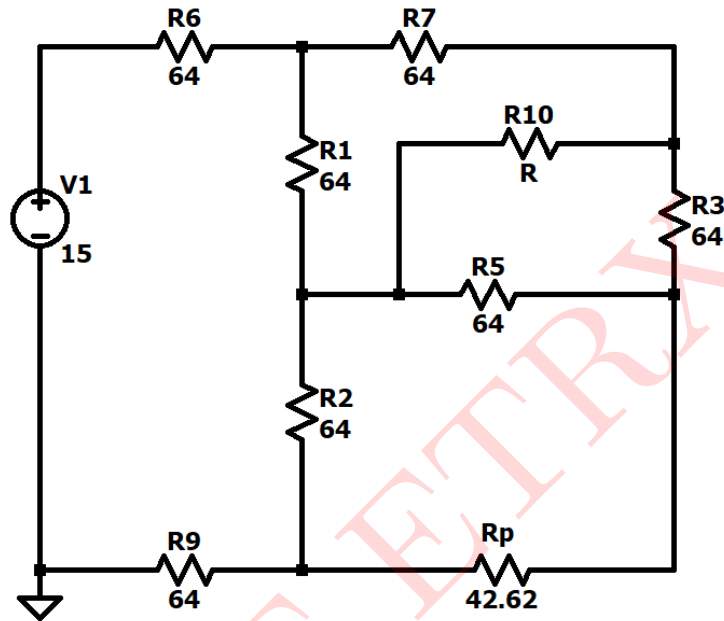


Figure 9: Modified Circuit after adding parellel resistance

In Figure 10:

Converting delta to star

$$R_1 = R_2 = R_3 = \frac{64 \times 64}{64 + 64 + 64} = 21.33\Omega$$

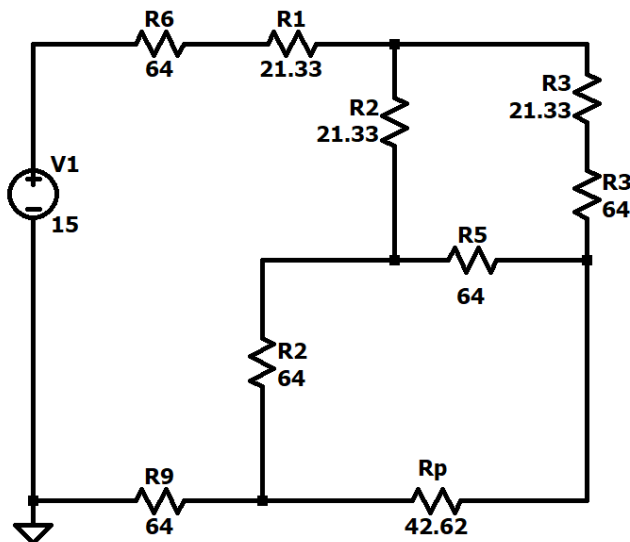


Figure 10: Modified Circuit after coversion of delta to star

In Figure 11:

Converting to delta to star

$$R_2 = R_3 = \frac{42.67 \times 64}{64 + 64 + 42.67} = 16.001\Omega$$

$$R_1 = \frac{64 \times 64}{64 + 64 + 42.67} = 23.995\Omega$$

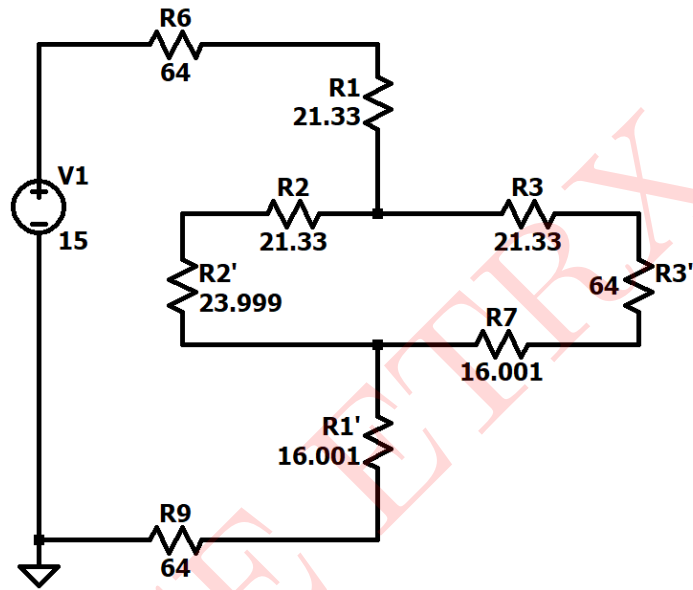


Figure 11: Modified Circuit after conversion of delta to star

In Figure 12:

Converting the series circuit

$$R_{S_1} = 64 + 21.33 + 16.001 = 101.331\Omega$$

$$R_{S_2} = 21.33 + 23.9995 = 45.3295\Omega$$

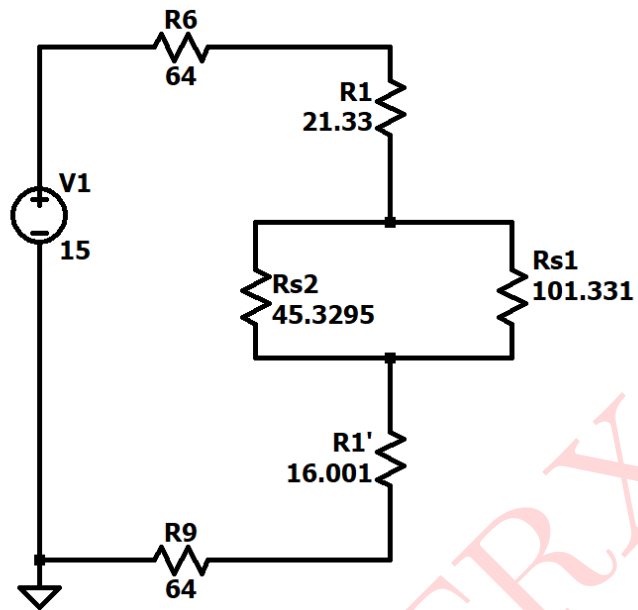


Figure 12: Modified Circuit after adding series resistances

In Figure 13:
Converting the parallel circuit

$$\frac{1}{R_P} = \frac{1}{101.331} + \frac{1}{45.3295} = 31.28\Omega$$

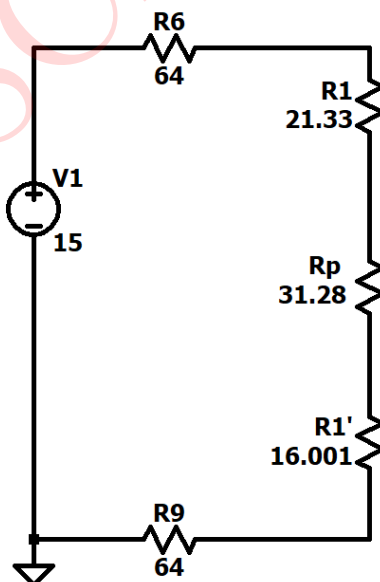


Figure 13: Modified Circuit after adding parallel resistances

$$R_{eq} = 64 + 21.33 + 31.28 + 16.001 + 64$$

$$= 196.611\Omega$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

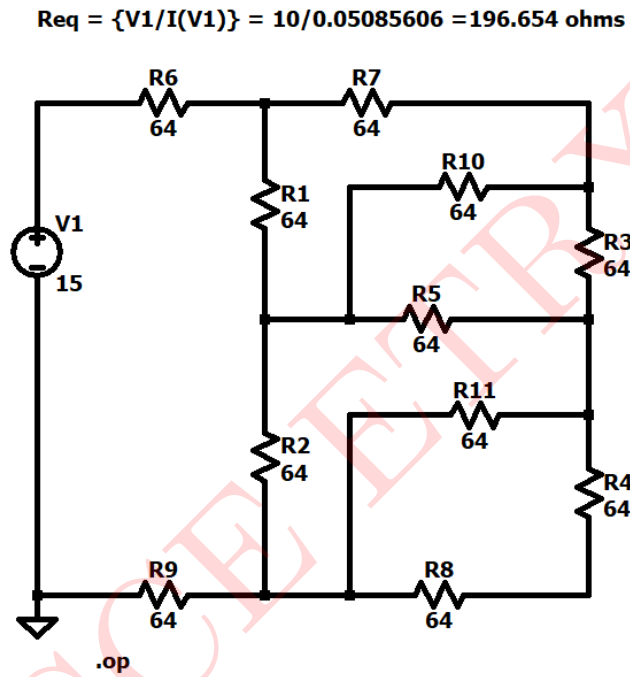


Figure 14: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| V_1 | 10V | 10V |
| $I(V_1)$ | 0.0508506A | 0.0508506A |
| R_{eq} | 196.661 Ω | 196.654 Ω |

Table 4: Numerical 4

Numerical 5: Obtain the Thevenin and Norton equivalent circuits for the circuit shown in Figure 15. All the resistance values are in ohms.

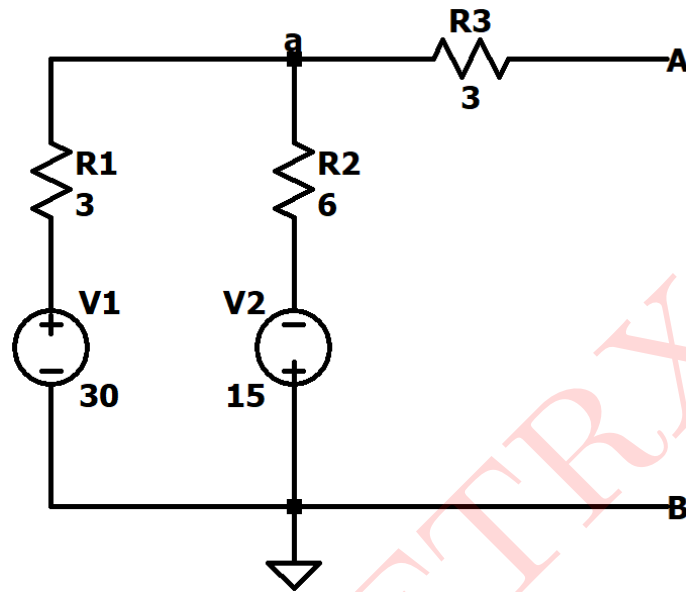


Figure 15: Circuit 5

Solution:

Solution for Thevenin's equivalent circuit:

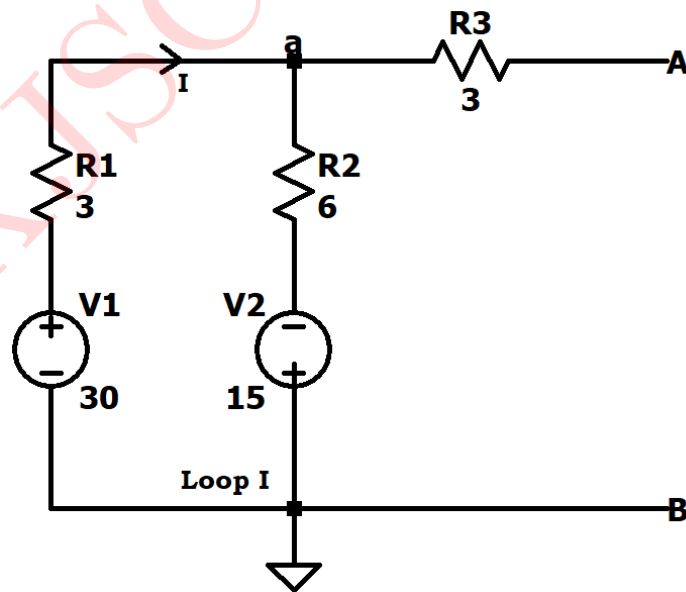


Figure 16: Circuit

Applying KVL to loop I:

$$-30 + 3I + 6I - 15 = 0$$

$$9I = 45$$

$$\therefore I = 5A$$

$$V_{Th} = I \times R_3$$

$$= 5 \times 3$$

$$\mathbf{V_{Th} = 15V}$$

To calculate R_{Th} , we replace voltage sources with a short circuit equivalent:

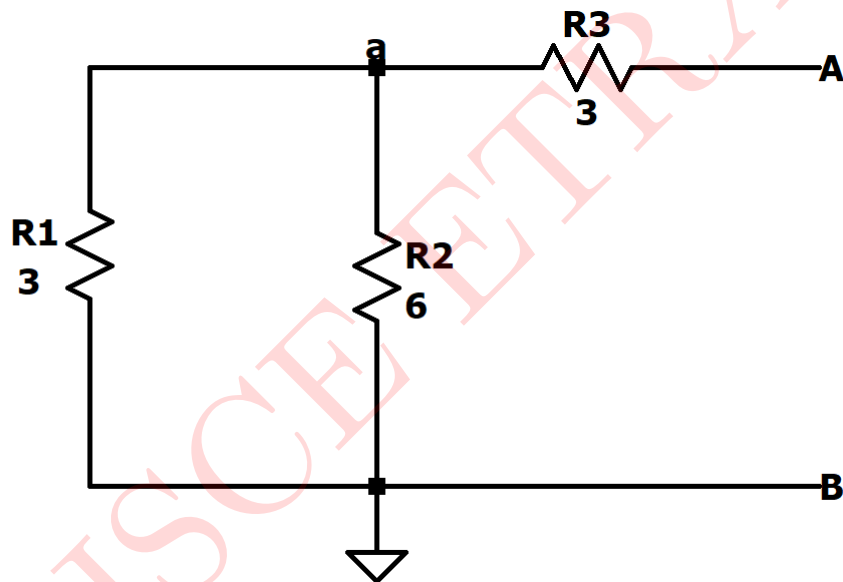


Figure 17: Modified circuit after short circuiting voltage sources

From Figure 18:

Parallel Circuit

$$\frac{1}{R_P} = \frac{1}{3} + \frac{1}{6}$$

$$R_P = 2\Omega$$

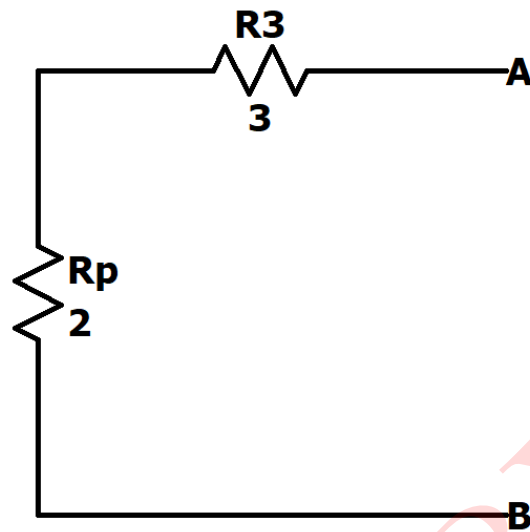


Figure 18: Modified circuit after calculating Parallel resitors

From Figure 19:

Series circuit

$$R_s = 3 + 2 = 5\Omega$$

$$R_s = 5\Omega$$

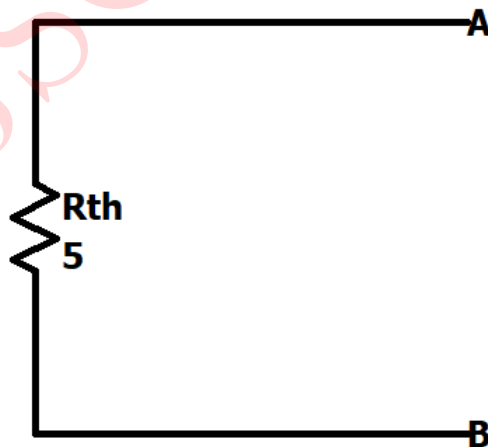


Figure 19: Modified circuit after calculating series resistances

$$R_{Th} = 5\Omega$$

Hence, the equivalent circuit for Thevenin's Theorem is

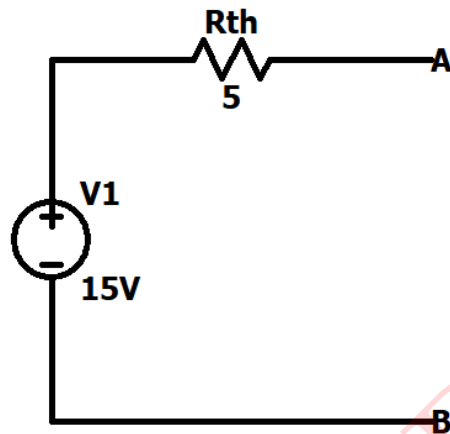


Figure 20: Thevenin's equivalent circuit

Solution for Norton's equivalent circuit:

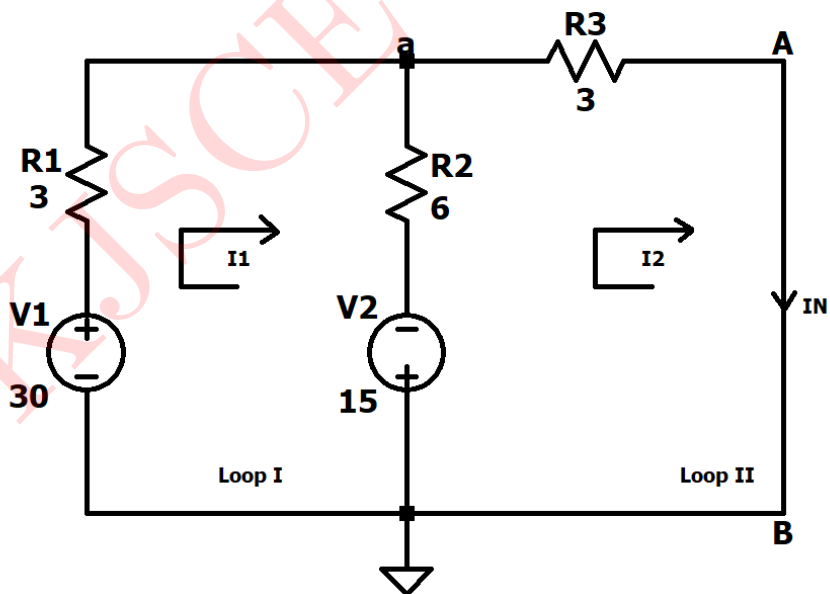


Figure 21: Circuit

Applying KVL to loop I:

$$\begin{aligned}
 30 + 3I_1 + 6(I_1 - I_2) - 15 &= 0 \\
 9I_1 + 6I_2 &= 45 \\
 3I_1 + 2I_2 &= 15
 \end{aligned}$$

Applying KVL to loop II:

$$-15 - 6(I_2 - I_1) - 3I_2 = 0$$

$$6I_1 - 9I_2 = 15$$

$$2I_1 - 3I_2 = 15$$

Solving equation(i) and equation(ii), we get

$$I_1 = 7\text{A}$$

$$I_2 = I_N = 3\text{A}$$

To calculate R_N :

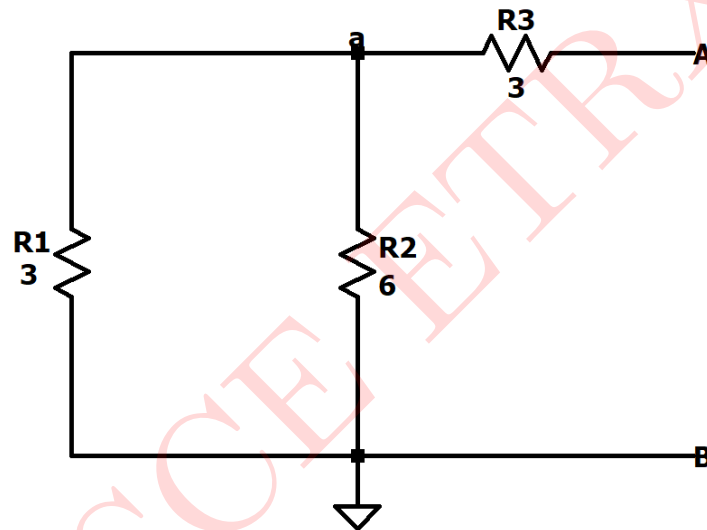


Figure 22: Circuit after short circuiting Voltage sources

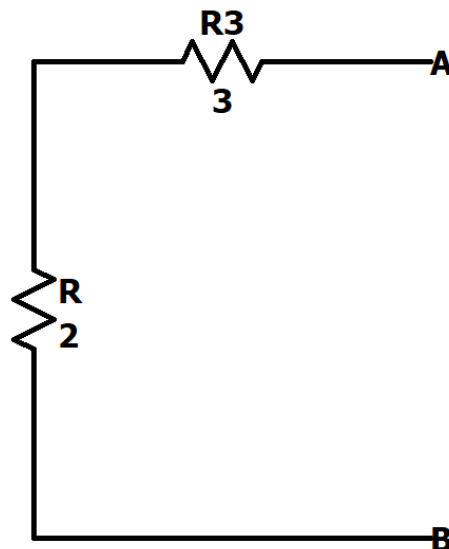


Figure 23: Modified Circuit after solving parallel circuits

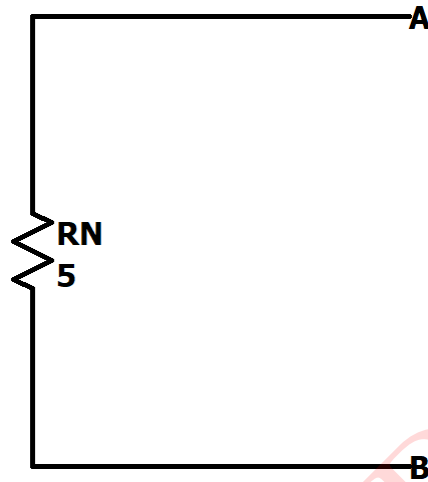


Figure 24: Modified circuit after adding series resistances

$$R_N = 5\Omega$$

Nortons equivalent circuit:

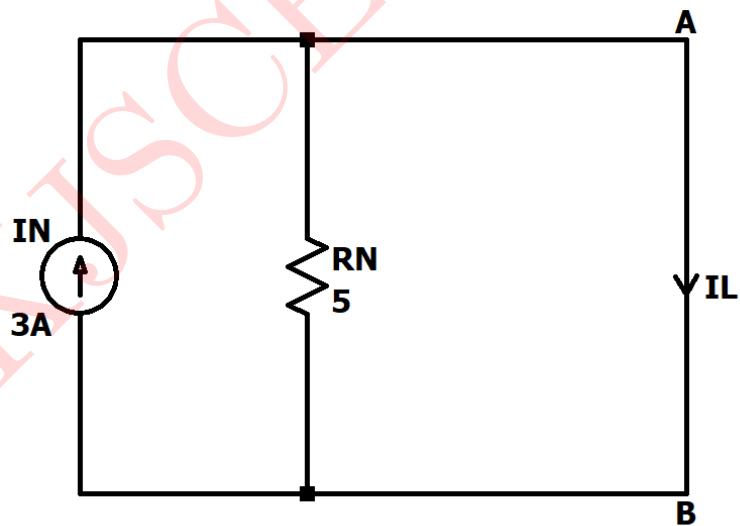


Figure 25: Norton's equivalent circuit

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

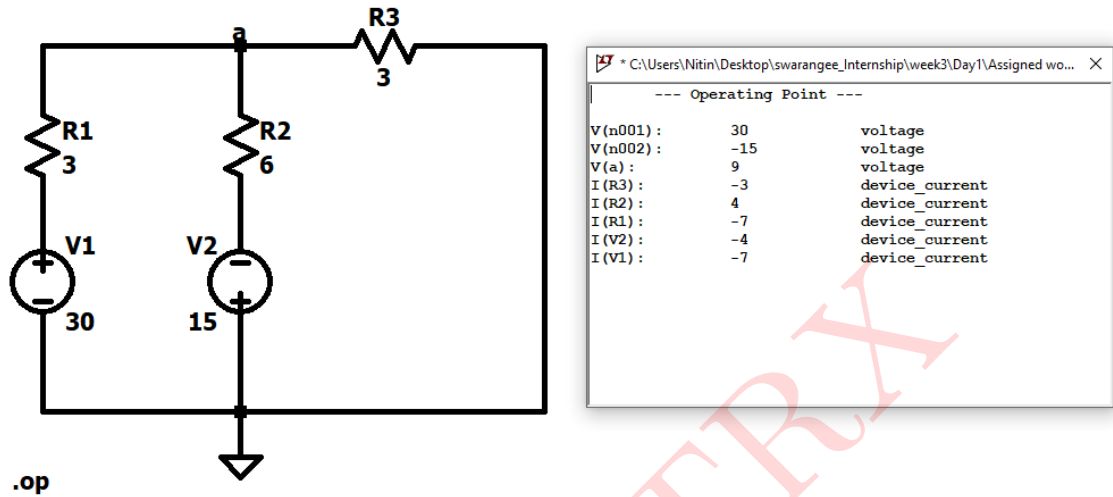


Figure 26: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| $I(R_1)$ | $-7A$ | $-7A$ |
| $I(R_2)$ | $4A$ | $4A$ |
| $I(R_3)$ | $-3A$ | $-3A$ |
| $I(V_2)$ | $-4A$ | $-4A$ |
| $I(V_1)$ | $-7A$ | $-7A$ |

Table 5: Numerical 5

Sample Calculations:

$$I(R_1) = I_1 = -7A$$

$$I(R_2) = (I_1 - I_2) = 4A$$

$$I(R_3) = -I_N = -3A$$

$$I(V_1) = -I_1 = -7A$$

$$I(V_2) = -(I_1 - I_2) = -4A$$

Numerical 6: Find the currents and voltages in the circuit shown in Figure 27.

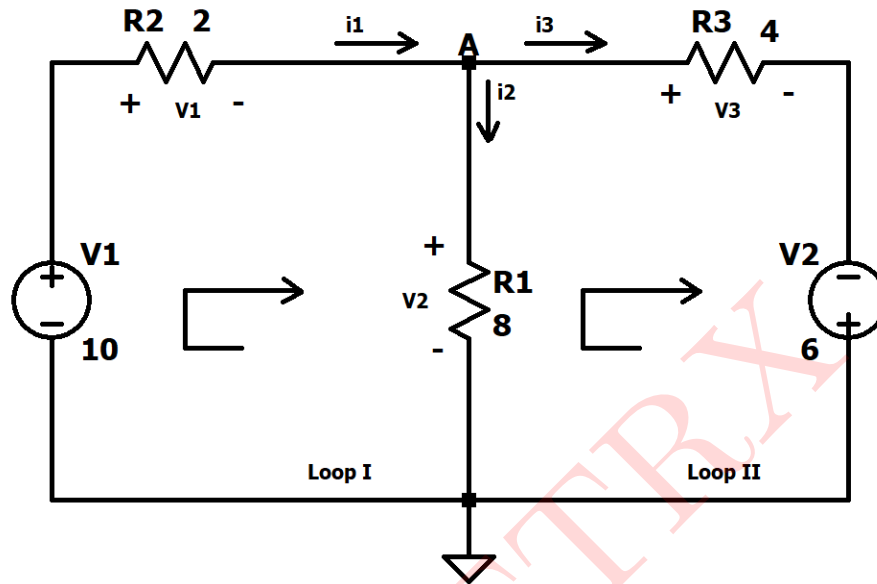


Figure 27: Circuit 6

Solution:

By Ohm's law:

$$V_1 = 2i_1; V_2 = 8i_2; V_3 = 4i_3$$

Now we apply KCL at Node A,

$$i_1 - i_1 - i_1 = 0 \quad \dots(i)$$

Applying KVL to loop I, we get

$$-10 + V_1 + V_2 = 0$$

Substituting values of V_1 and V_2 , we get

$$-10 + 2i_1 + 8i_2 = 0 = 0$$

$$i_1 = \frac{10 - 8i_2}{2} \quad \dots(a)$$

Applying KVL in Loop II, we get

$$-6 - V_2 + V_3 = 0 = 0$$

Substituting values of V_2 and V_3 , we get

$$-6 - 8i_2 + 4i_3 = 0 = 0$$

$$i_3 = \frac{4i_2 + 3}{2} \quad \dots(b)$$

Substituting (a) and (b) in (i)

$$\frac{10 - 8i_2}{2} - i_2 - \frac{4i_2 - 3}{2} = 0$$

$$i_2 = 0.5A \text{ OR } 500mA$$

$$i_1 = 3A; i_3 = 2.5A; V_1 = 6V; V_2 = 4V; V_3 = 10V$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

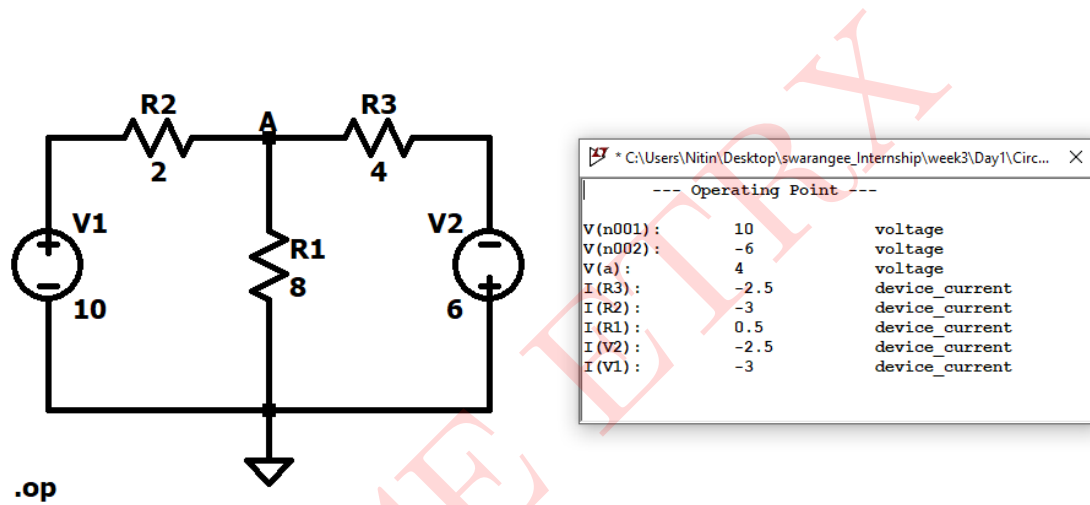


Figure 28: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| i_1 | 3A | 3A |
| i_2 | 500mA | 500mA |
| i_3 | 2.5A | 2.5A |
| V_1 | 6V | 6V |
| V_2 | 4V | 4V |
| V_3 | 10V | 10V |

Table 6: Numerical 6

Numerical 7: Find currents and voltages in the circuit shown in Figure 29.

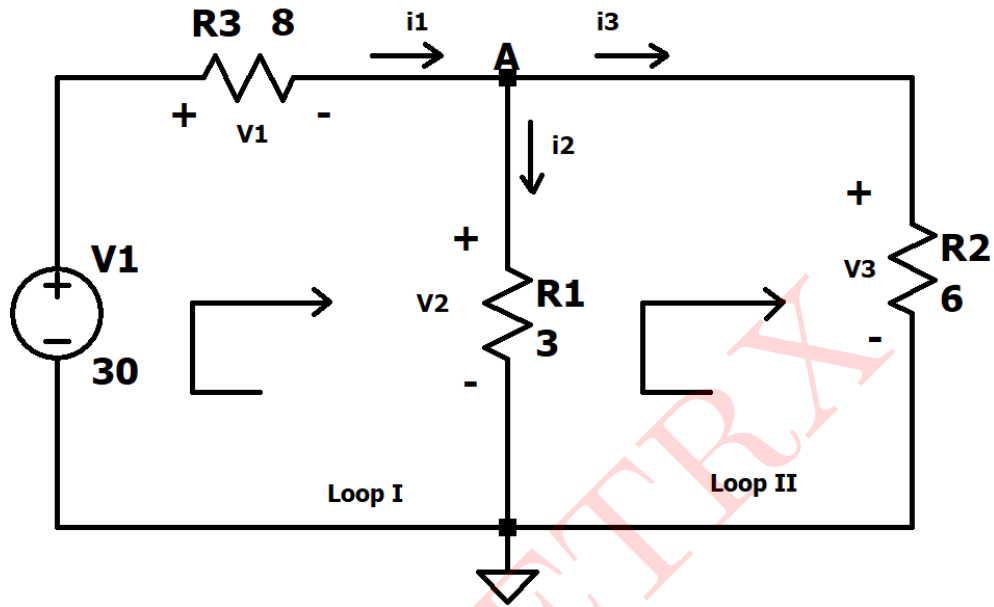


Figure 29: Circuit 7

Solution:

We apply Ohm's law and Kirchoff's law.

By Ohm's law,

$$V_1 = 8i_1 ; V_2 = 3i_2 ; V_3 = 6i_3$$

Since the voltage and current of each resistors are related by ohm's law as shown, we are really looking for three things: (V_1, V_2, V_3) OR (i_1, i_2, i_3)

At node A, KCL gives,

$$i_1 - i_2 - i_3 = 0 \quad \dots(i)$$

Applying KVL to loop I:

$$-30 + V_1 + V_2 = 0$$

expressing equation in terms of i we get

$$-30 + 8i_1 + 3i_2 = 0$$

$$i_1 = \frac{30 - 3i_2}{8}$$

Applying KVL to loop II:

$$-V_2 + V_3 = 0$$

As expected the two resistors are in parallel

$$V_3 = V_2$$

expressing V_3 and V_2 in terms of i_3 and i_2

$$6i_3 = 3i_2$$

$$i_3 = \frac{i_2}{2} \quad \dots(ii)$$

Substituting equation (ii) in equation (i)

$$\frac{30 - 3i_2}{8} - i_2 - \frac{i_2}{2} = 0$$

$$i_2 = 2A$$

$$i_1 = 3A; i_3 = 1A; V_1 = 24V; V_2 = 6V; V_3 = 6V$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

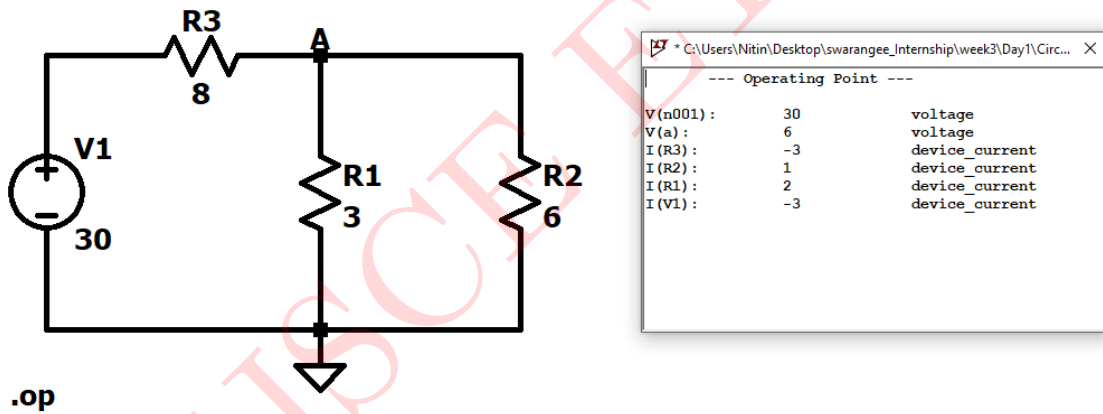


Figure 30: Circuit Schematic and simulated results

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| i_1 | 3A | 3A |
| i_2 | 2A | 2A |
| i_3 | 1A | 1A |
| V_1 | 24V | 24V |
| V_2 | 6V | 6V |
| V_3 | 6V | 6V |

Table 7: Numerical 7

Numerical 8: Find:

a) Thevenin (or equivalent) voltage:

b) Thevenin (or equivalent) resistance:

for the two-terminal networks shown in figure 31.

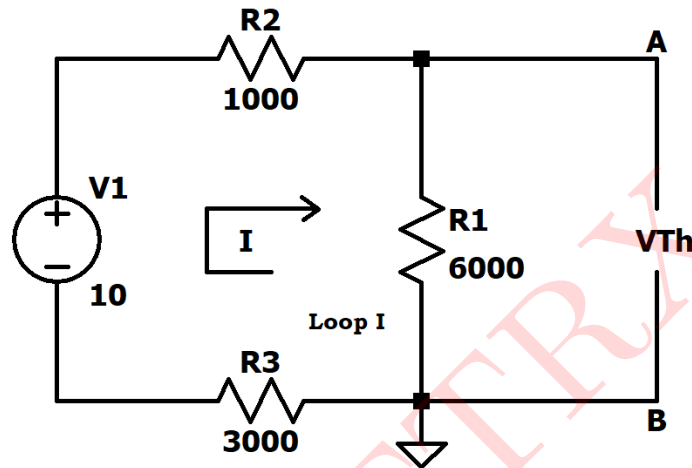


Figure 31: Circuit 8

Solution:

To calculate V_{Th} :

Applying KVL in loop I:

$$10 - 1000I - 6000I - 3000I = 0$$

$$I = \frac{10}{10000}$$

$$I = \frac{1}{1000}$$

$$I = 0.001A$$

$$\begin{aligned} V_{Th} &= I \times R_1 \\ &= 0.001 \times 6000 \end{aligned}$$

$$\mathbf{V_{Th} = 6V}$$

To calculate R_{Th} :

we replace voltage sources with a short circuit equivalent for finding R_{Th} .

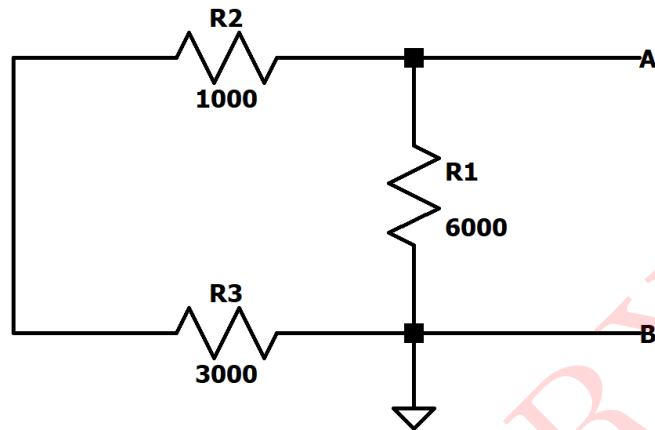


Figure 32: Modified circuit after shorting the voltage sources

From Figure 33:

For series Circuit

$$R_s = R_2 + R_3 = 4k\Omega$$

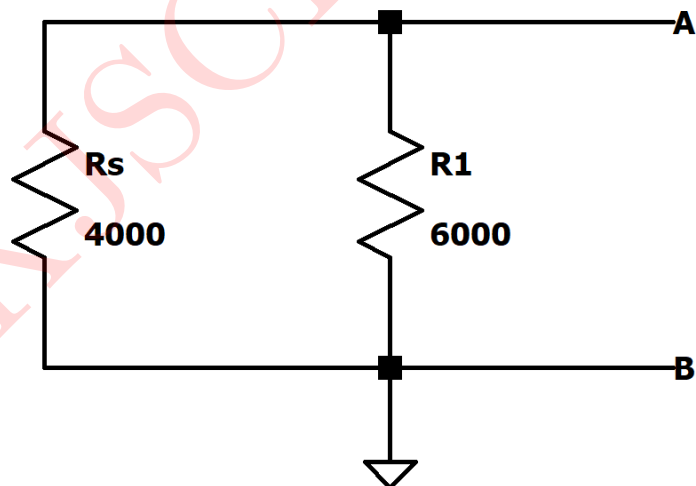


Figure 33: Modified circuit after adding series resistances

From Figure 34:

For parallel circuit

$$\frac{1}{R_P} = \frac{1}{64k} + \frac{1}{4k} = 2.4k\Omega$$

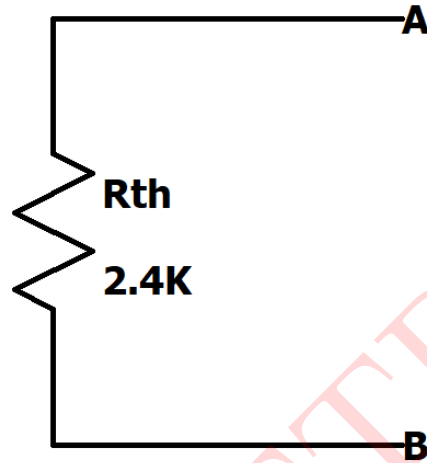


Figure 34: Modified circuit after solving parallel resistance

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

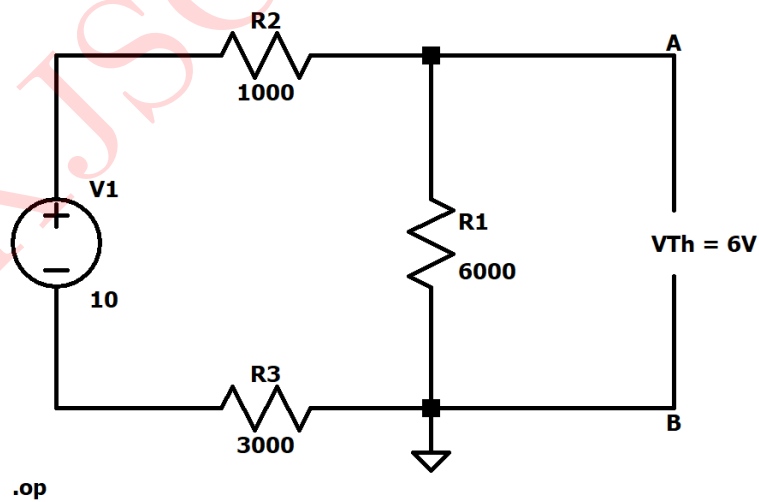


Figure 35: Circuit Schematic and simulated results for V_{Th}

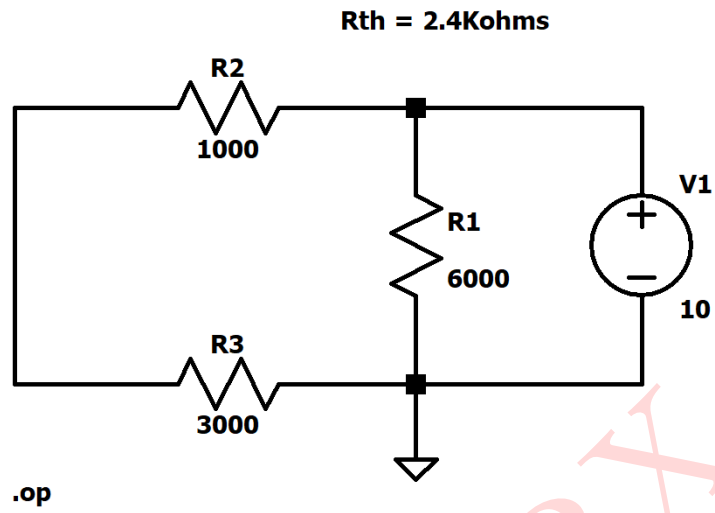


Figure 36: Circuit Schematic and simulated results for R_{Th}

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|--------------------------|--------------------|------------------|
| V_{Th} | 6V | 6V |
| R_{Th} | 2.4k Ω | 2.4k Ω |
| $I(R_1), I(R_2), I(R_3)$ | 0.001A | 0.001A |

Table 8: Numerical 8

Calculations from simulations:

$$I(R_{Th}) = \frac{V_1}{I(V_1)} = \frac{10}{0.00416667} = 2.4K\Omega$$

Numerical 9: Find:

a) Thevenin (or equivalent) voltage:

b) Thevenin (or equivalent) resistance:

for the two-terminal networks shown in Figure 37.

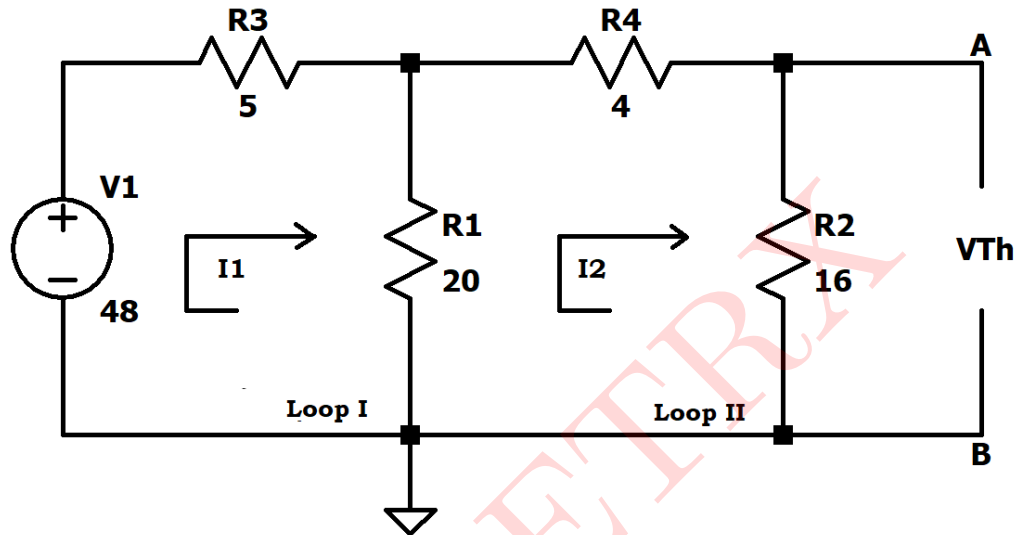


Figure 37: Circuit 9

Solution:

To calculate V_{Th} :

Applying KVL in loop I:

$$48 - 5I_1 - 20(I_1 - I_2) = 0$$

$$25I_1 - 20I_2 = 48$$

.....(i)

Applying KVL in loop II:

$$-20(I_2 - I_1) - 4I_2 - 16I_2 = 0$$

$$I_1 = 2I_2$$

.....(ii)

Solving equation(i) and equation(ii), we get

$$I_2 = \frac{8}{5} = 1.6A$$

$$I_1 = \frac{6}{5} = 1.2A$$

$$V_{Th} = I_2 \times R_2$$

$$= \frac{8}{5} \times 16$$

$$\mathbf{V_{Th} = 25.6V}$$

To calculate R_{Th} :

we replace voltage sources with a short circuit equivalent to find R_{Th} .

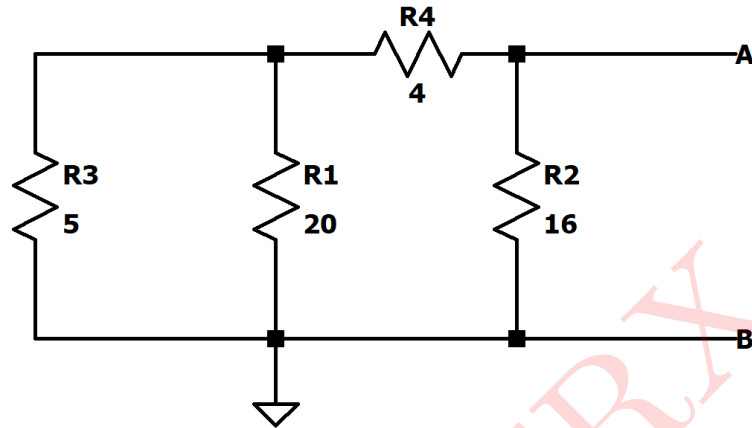


Figure 38: Modified circuit after shorting voltage sources

From Figure 39:

For parallel circuit

$$\frac{1}{R_P} = \frac{1}{5} + \frac{1}{20}$$

$$R_P = \frac{20}{5} = 4\Omega$$

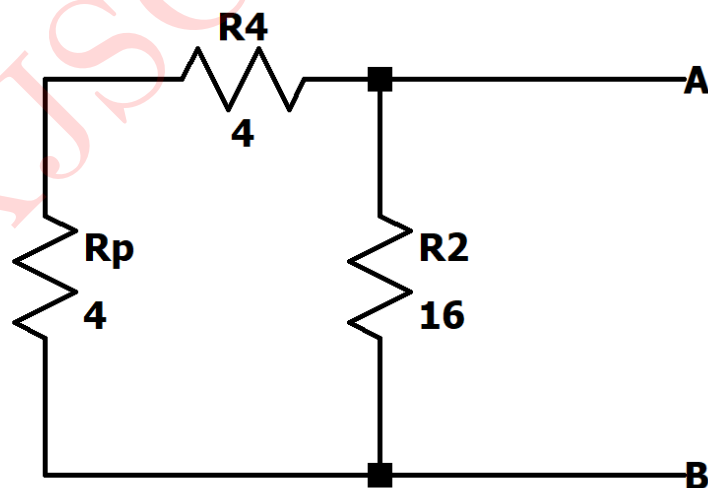


Figure 39: Modified circuit after solving parallel combination

From Figure 40:

For series Circuit

$$R_s = 4 + 4 = 8\Omega$$

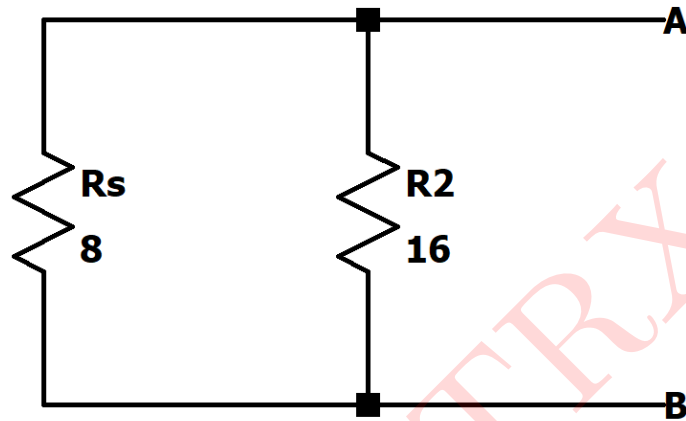


Figure 40: Modified circuit after adding series resistances

From Figure 41:

For parallel circuit

$$\frac{1}{R_P} = \frac{1}{16} + \frac{1}{8}$$

$$R_P = R_{Th} = \frac{16}{3} = 5.33\Omega$$

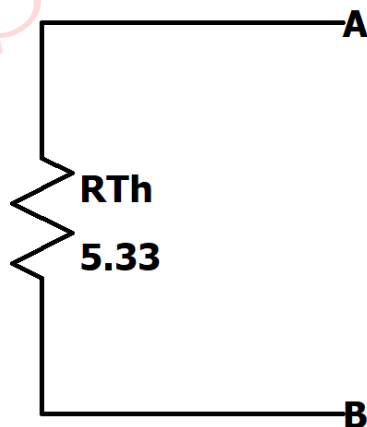


Figure 41: Modified circuit after solving parallel resistances

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

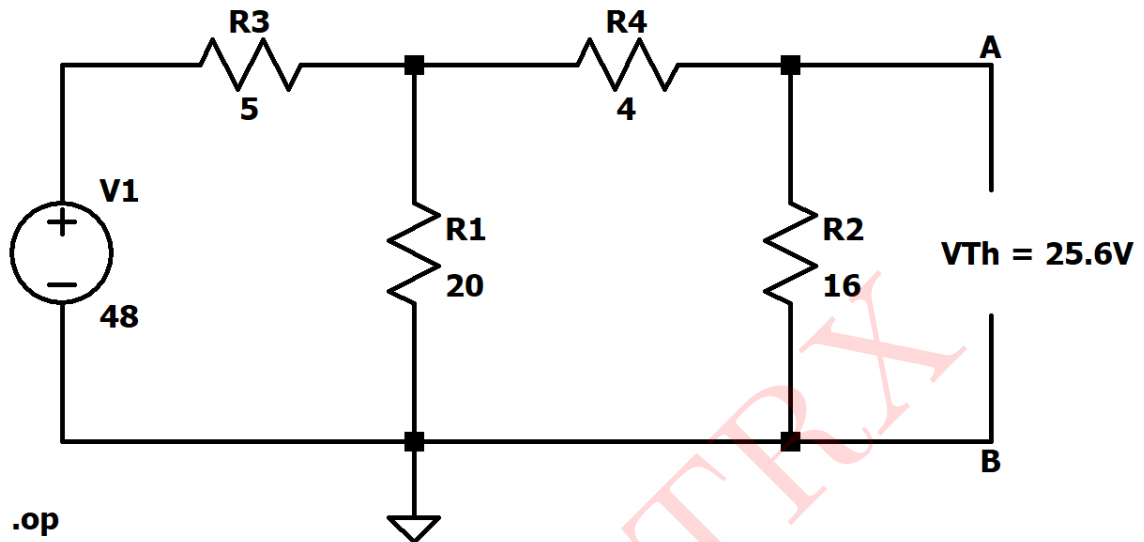


Figure 42: Circuit Schematic and simulated results for V_{Th}

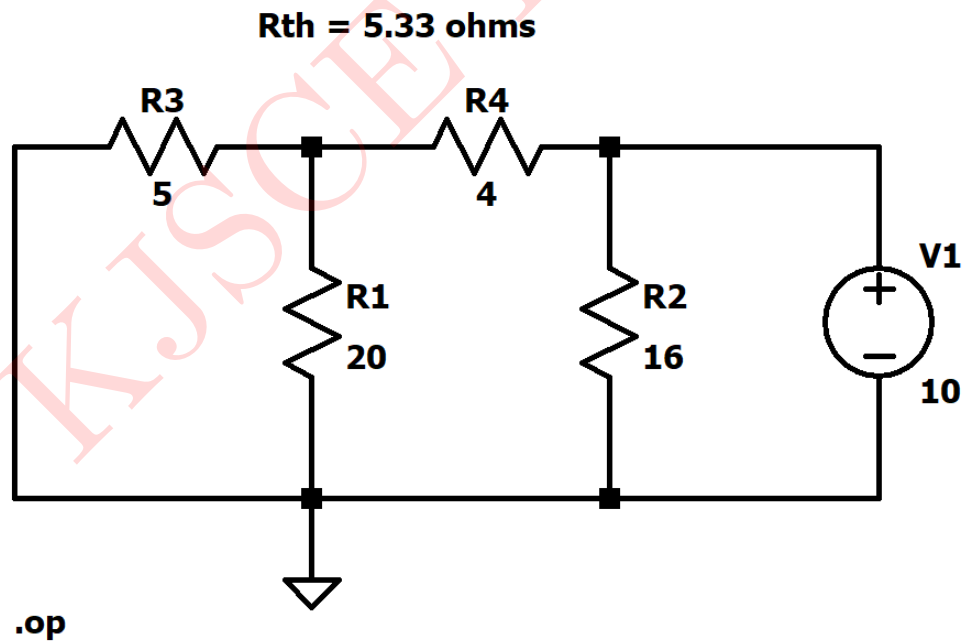


Figure 43: Circuit Schematic and simulated results for R_{Th}

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|--------------------------|--------------------|------------------|
| V_{Th} | 25.6V | 25.6V |
| R_{Th} | 5.33Ω | 5.33Ω |
| $I(R_1), I(R_2), I(R_4)$ | 1.6A | 1.6A |
| $I(R_3)$ | 3.2A | 3.2A |

Table 9: Numerical 9

Calculations from simulations:

$$I(R_{Th}) = \frac{V_1}{I(V_1)} = \frac{10}{1.875} = 5.33\Omega$$

Numerical 10: Obtain the Norton equivalent of the circuit 10 in Figure 44 to the left of terminals a-b. Use the result to find current i .

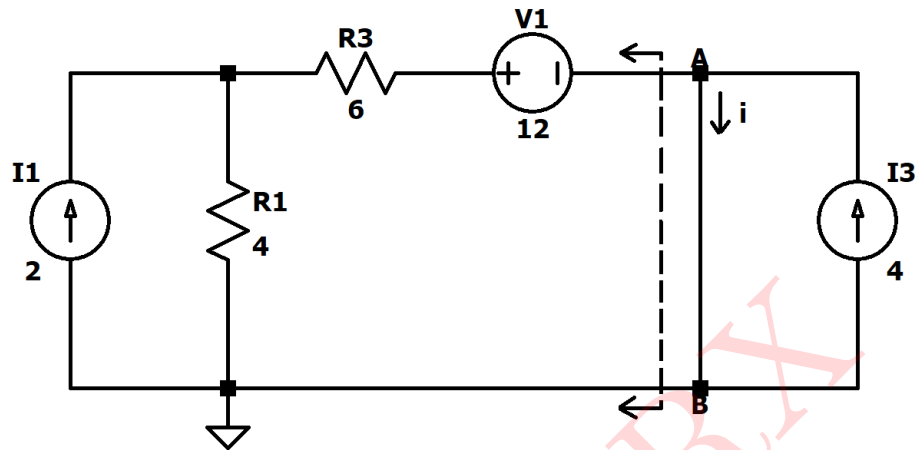


Figure 44: Circuit 10

Solution:

To calculate the Norton's equivalent to the left of terminals a and b

To calculate I_N :

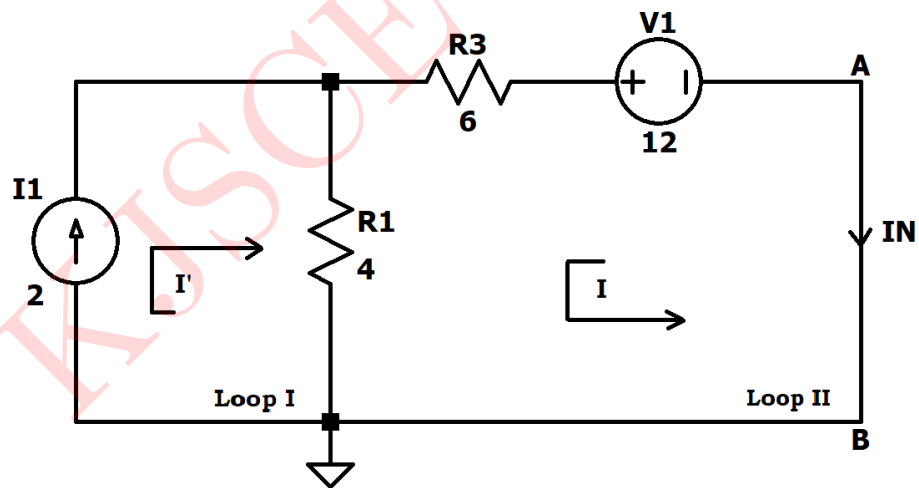


Figure 45: Circuit to the left of a-b terminals

In loop I:

$$I' = 2A$$

Applying KVL to loop II

$$12 - 6I - 4(I - (-I')) = 0$$

$$12 - 6I - 4(I + I') = 0$$

$$I = 0.4A$$

$$I_{4\Omega} = (I + I')$$

$$= 2 + 0.4$$

$$\mathbf{I_N = 2.4A}$$

To calculate R_N :

From Figure 46:

For series circuit

$$R_N = R_s = 6 + 4 = 10\Omega$$

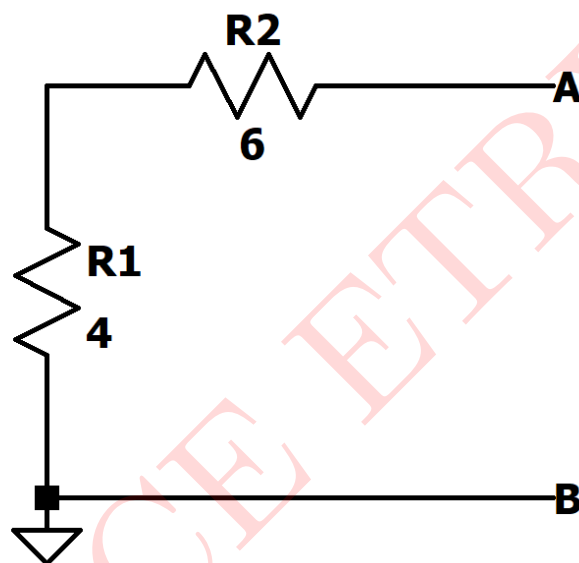


Figure 46: To calculate R_N

Norton's equivalent circuit and the remaining circuit

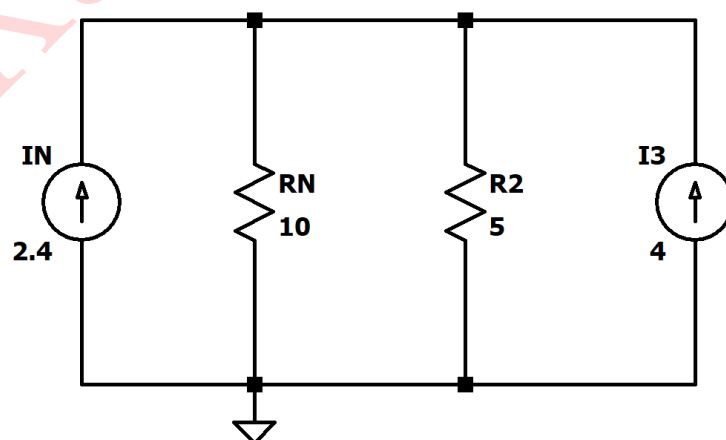


Figure 47: Norton's equivalent circuit

From Figure 48:

Adding parallel current sources

$$I_{5\Omega} = i = 6.4 \times \frac{10}{5 + 10} = 4.2667 A$$

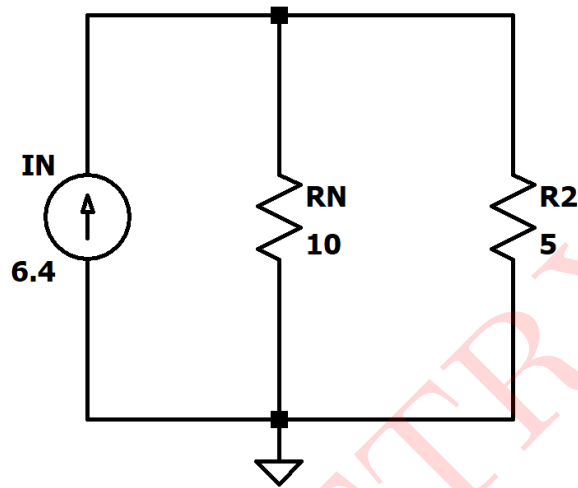


Figure 48: Modified circuit after solving parallel sources

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

$$\mathbf{I(AB) = I(N) = 2.4A}$$

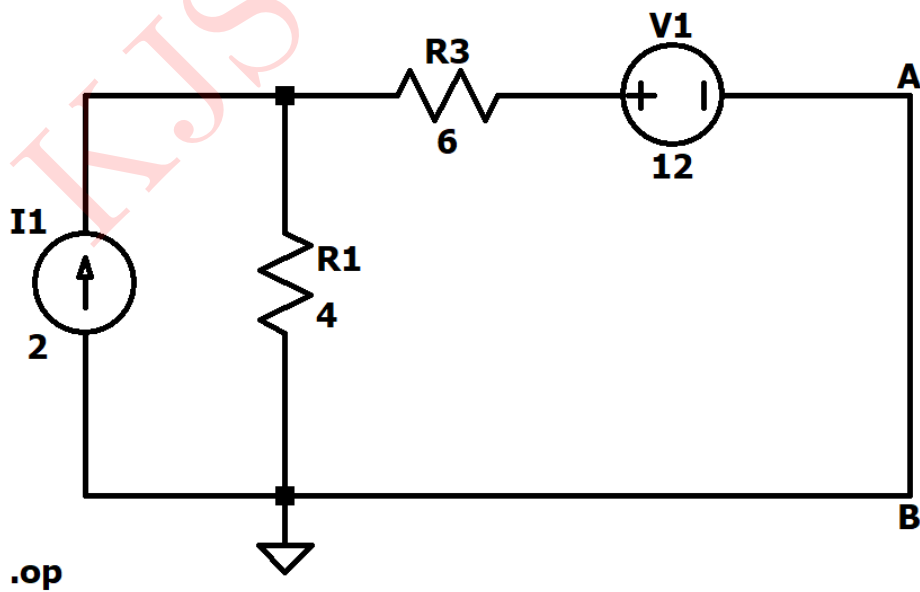


Figure 49: Circuit Schematic and simulated results for I_N

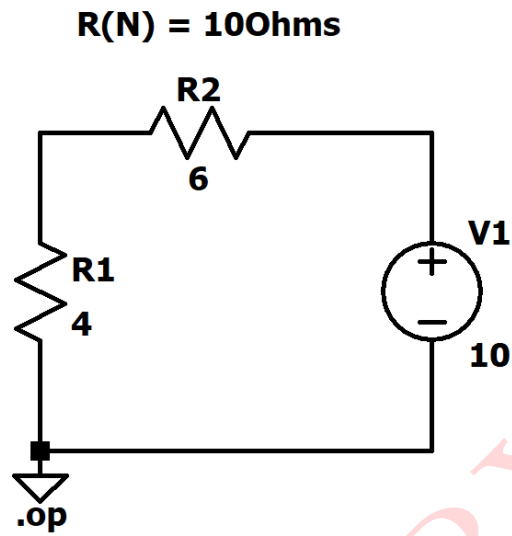


Figure 50: Circuit Schematic and simulated results for R_N

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|-------------------|--------------------|------------------|
| $I_N/I_{4\omega}$ | 2.4A | 2.4A |
| R_N | 10Ω | 10Ω |
| $I(R_{5\Omega})$ | 4.2667A | 4.2667A |

Table 10: Numerical 10

Calculations from simulations:

$$I(R_{Th}) = \frac{V_1}{I(V_1)} = \frac{10}{1} = 10\Omega$$

Numerical 11: Calculate the value of R_L for it to absorb the maximum power and find out the maximum power in the circuit of Figure 51.

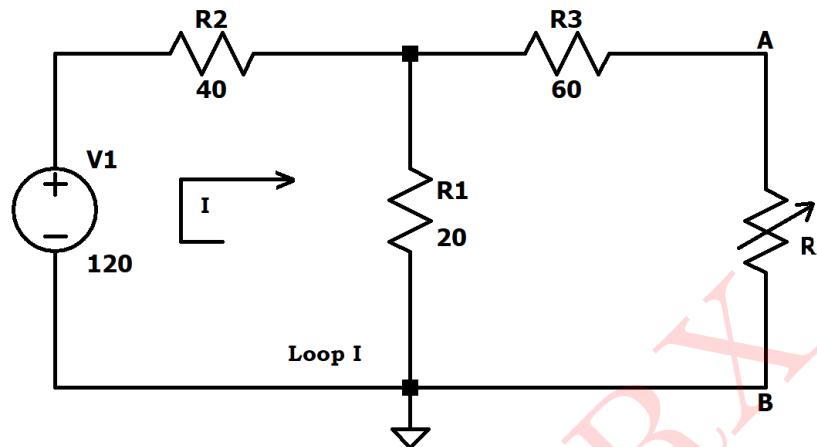


Figure 51: Circuit 11

Solution:

Applying Thevenin's theorem:

To calculate V_{Th} :

Applying KVL to loop:

$$120 - 40I - 20I = 0$$

$$\therefore I = 2A$$

$$V_{Th} = I \times R_1$$

$$= 2A \times 20\Omega$$

$$V_{Th} = 40V$$

To calculate R_{Th} :

We replace voltage sources with a short circuit equivalent

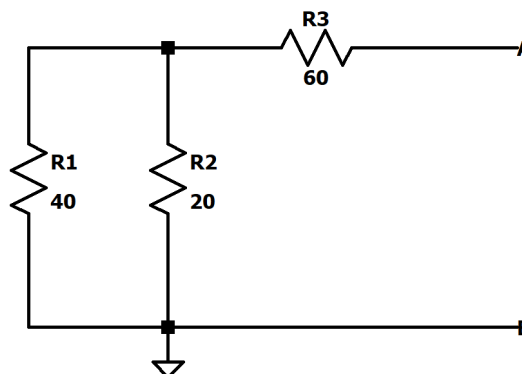


Figure 52: Modified circuit after short circuiting voltage source

From Figure 53:

For parallel circuit

$$\frac{1}{R_P} = \frac{1}{20} + \frac{1}{40}$$

$$R_P = \frac{40}{3} = 13.333\Omega$$

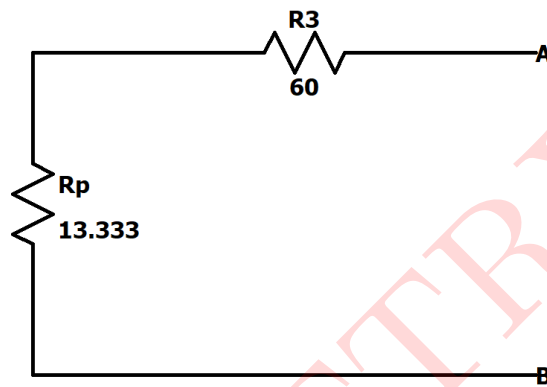


Figure 53: Modified circuit after calculating parallel resistances

From Figure 54:

$$R_{Th} = \frac{40}{3} + 60$$

$$R_{Th} = 73.33\Omega$$

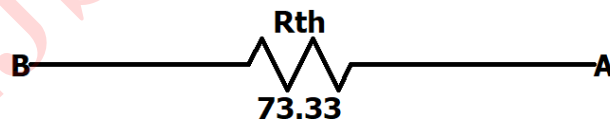


Figure 54: Modified circuit after calculating series resistances

Thevenin's equivalent circuit:

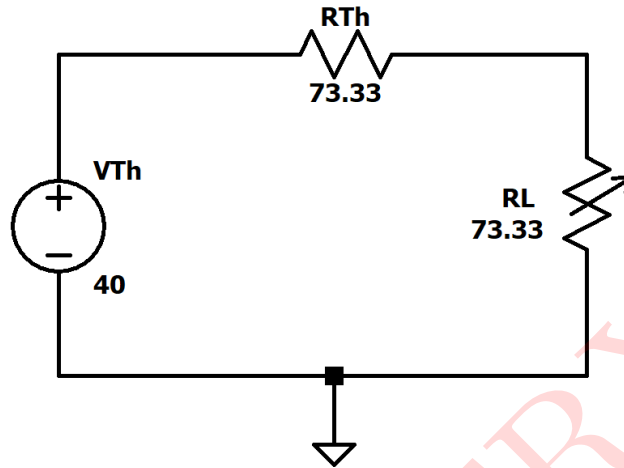


Figure 55: Thevenin's equivalent circuit

For maximum power

$$R_L = R_{Th} = 73.33\Omega$$

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = 5.4548W$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

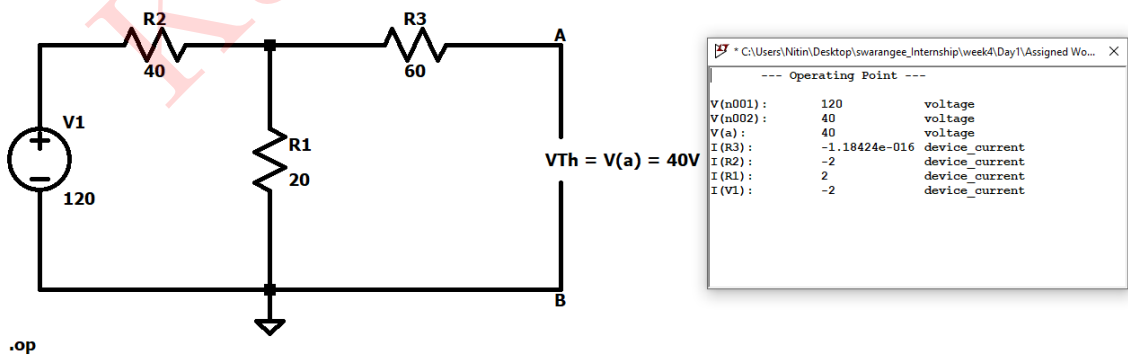


Figure 56: Circuit schematic and simulated results for V_{Th}

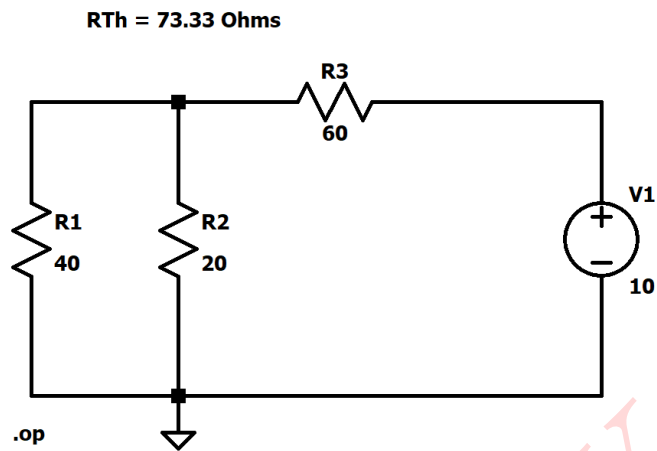


Figure 57: Circuit schematic and simulated results for R_{Th}

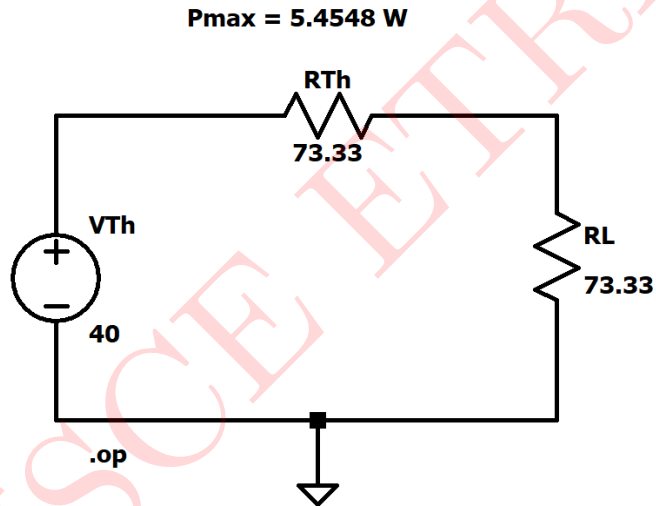


Figure 58: Circuit schematic and simulated results for P_{max}

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|------------|--------------------|------------------|
| V_{Th} | 40V | 40V |
| R_{Th} | 73.33Ω | 73.33Ω |
| P_{max} | 5.4548W | 5.4548W |

Table 11: Numerical 11

Numerical 12: For the circuit shown below, what will be the value of R_L to get the maximum power? What is the maximum power delivered to the load?

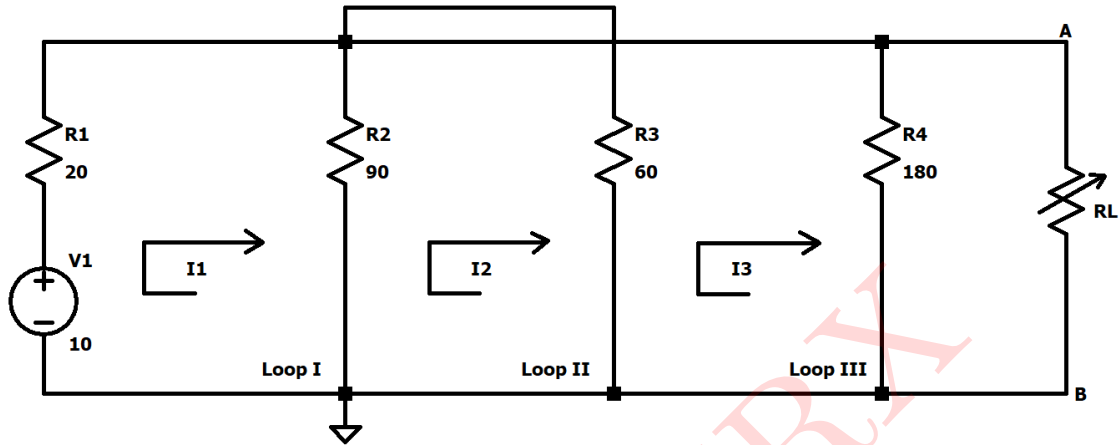


Figure 59: Circuit 12

Solution:

Applying Thevenin's theorem:

To calculate V_{Th} :

Applying KVL to loop I:

$$10 - 20I_1 - 90(I_1 - I_2) = 0$$

$$11I_1 - 9I_2 = 1 \quad \dots(i)$$

Applying KVL to loop II:

$$-90(I_2 - I_1) - 60(I_2 - I_3) = 0$$

$$3I_1 - 5I_2 + 2I_3 = 1 \quad \dots(ii)$$

Applying KVL to loop III:

$$-60(I_3 - I_2) - 180I_3 = 0$$

$$I_2 = 4I_3 \quad \dots(iii)$$

Solving equation(i), equation(ii) and equation(iii), we get

$$I_1 = 0.2A; I_2 = 0.133A; I_3 = 0.0333A$$

$$V_{Th} = I_3 \times R_4$$

$$= 180 \times 0.0333$$

$$V_{Th} = 5.999V$$

To calculate R_{Th} :

We short circuit voltage sources

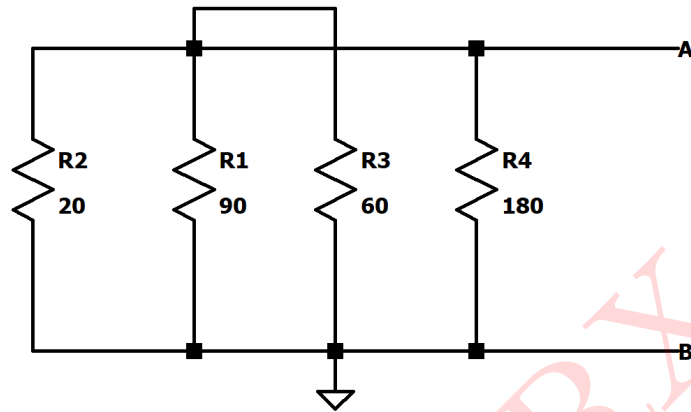


Figure 60: Circuit to calculate R_{Th}

From Figure 61:

For parallel circuit

$$\frac{1}{R_P} = \frac{1}{20} + \frac{1}{90}$$

$$R_P = \frac{180}{11} = 16.36\ \Omega$$

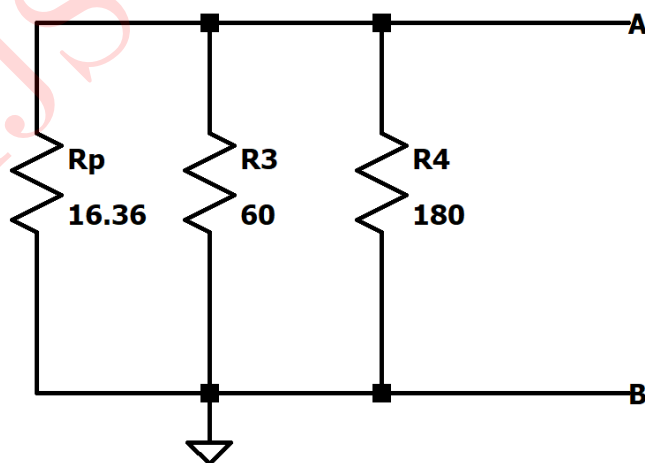


Figure 61: Modified Circuit for calculating parallel resistances

From Figure 62:

For parallel circuit

$$\frac{1}{R_{Th}} = \frac{1}{180} + \frac{1}{60} + \frac{1}{180}$$

$$R_{Th} = 12\Omega$$



Figure 62: Modified Circuit for calculating parallel resistances

Thevenin's equivalent circuit:

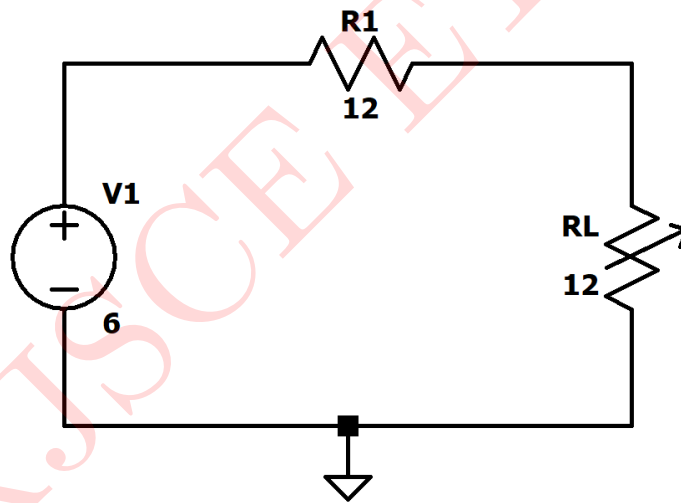


Figure 63: Thevenin's equivalent circuit

For maximum power

$$R_L = R_{Th} = 12\Omega$$



$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$= \frac{(5.9994)^2}{4 \times 12}$$

$$P_{max} = 0.74985W$$

SIMULATED RESULTS:

The given circuit is simulated in LTspice and the results obtained are as follows:

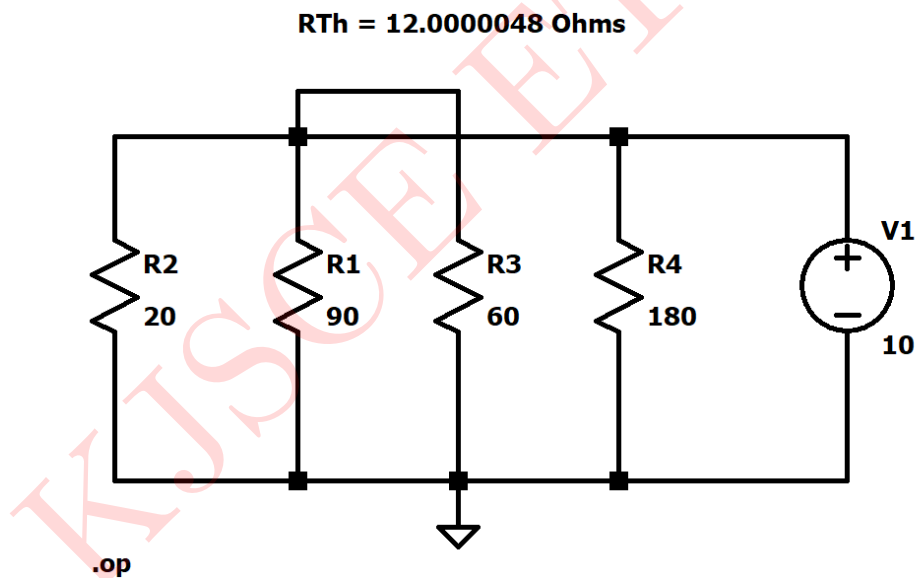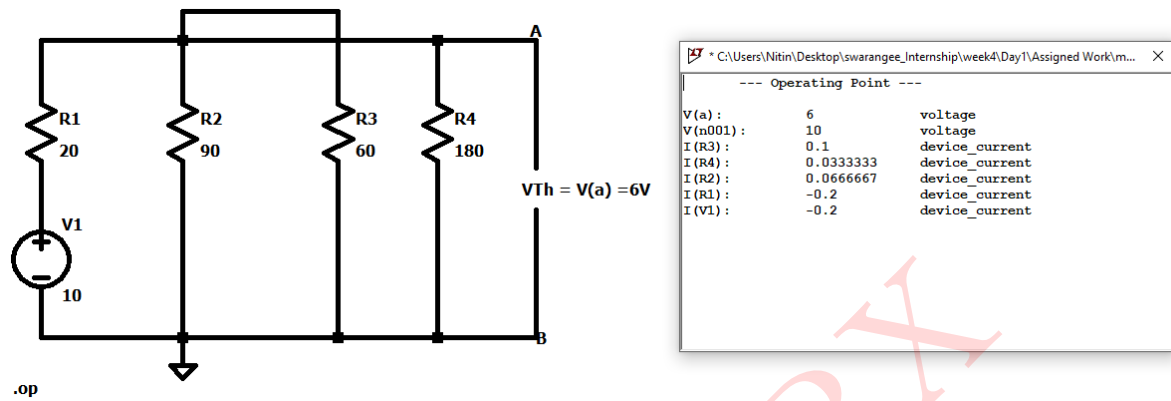

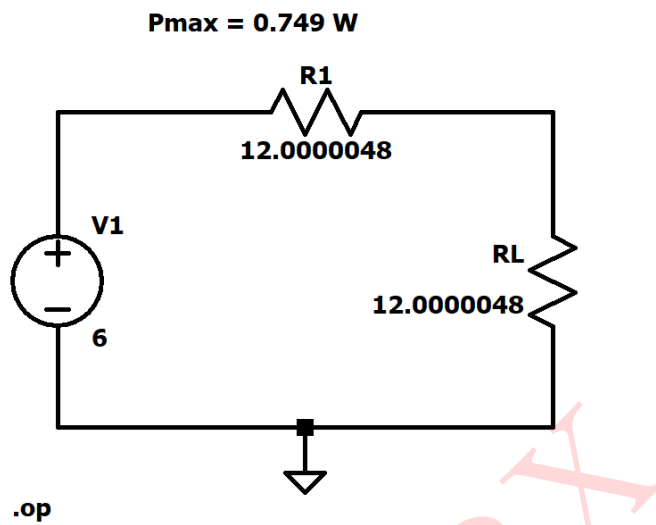


Figure 66: Circuit schematic and simulated results for P_{\max}

Comparison of theoretical and simulated values:

| Parameters | Theoretical Values | Simulated Values |
|----------------------|--------------------|------------------|
| $I(R_1) = I(N_1)$ | 0.2A | 0.2A |
| $I(R_2) = I_2 - I_1$ | 0.066667A | 0.066667A |
| $I(R_3) = I_3 - I_2$ | 0.1A | 0.1A |
| $I(R_4) = I_3$ | 0.03333A | 0.03333A |
| V_{Th} | 5.994V | 5.994V |
| R_{Th} | 12 Ω | 12 Ω |
| P_{max} | 0.74985W | 0.74985W |

Table 12: Numerical 12
