

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Cascade Amplifier Design**

16<sup>th</sup> July, 2020

**Design 1:** Design a two stage RC coupled cascade amplifier for following specifications  
 $A_V \geq 1750$ ,  $V_{ORMS} = 2V$ ,  $S \leq 10$ ,  $f_L \geq 30Hz$ . Use transistor BC 147A from the data sheet.

**Solution:**

**1) Circuit diagram selection and selection of transistor:**

Given:  $A_V \geq 1750$ ,  $V_{ORMS} = 2V$ ,  $S \leq 10$ ,  $f_L \geq 30Hz$

Transistor BC 147A specification:

$h_{fe(typ)} = 220$ ,  $h_{ie} = 2.7k\Omega$

$h_{FE(typ)} = 180$ ,  $V_{CE(sat)} = 0.25V$

We use voltage divider biasing because it provides stability of Q point against variations in  $\beta$  or stability of Q point against variations in temperature

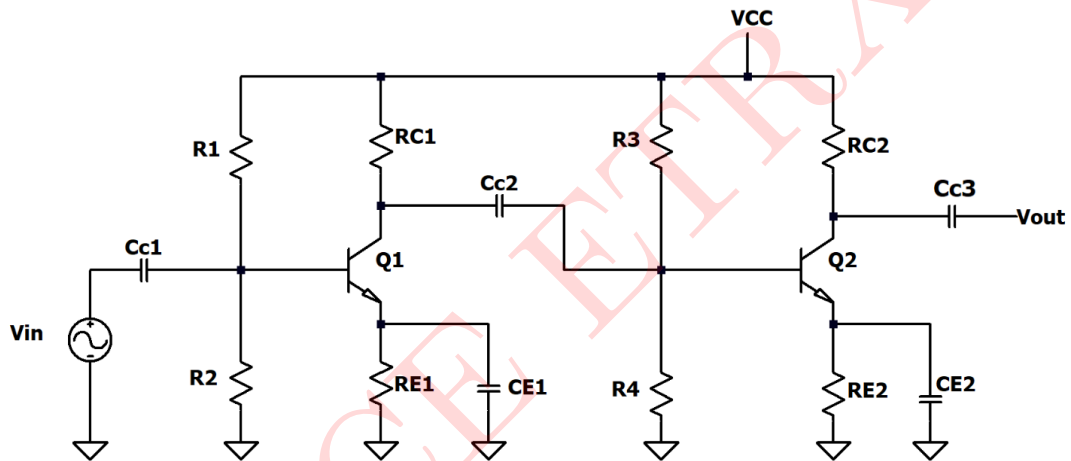


Figure 1: Circuit 1

**2. Selection of voltage gains:**

$$A_{VT} = A_{V1} \times A_{V2} = 1750$$

$$A_{V1} \approx 0.5A_{V2}$$

$$\therefore A_{VT} = 0.5A_{V2}^2$$

$$1750 = 0.5A_{V2}^2$$

$$A_{V2} = \sqrt{\frac{1750}{0.5}} = \mathbf{59.16}$$

$$A_{V1} = 0.5 \times 59.16 = \mathbf{29.58}$$

Let  $A_{V1} = 30$  and  $A_{V2} = 59$

**Design of second stage:**

**3. Calculations of  $R_{C2}$ :**

$$|A_{V2}| = \frac{h_{fe(typ)} R_{C2}}{h_{ie}} = \frac{220 \times R_{C2}}{2.7 \times 10^3} = \mathbf{59}$$

$$\therefore R_{C2} \frac{2.7 \times 10^3 \times 59}{220} = \mathbf{724\Omega}$$

Selecting HSV,  $R_{C2} = \mathbf{750\Omega, 1/4W}$

**4. Selection of Q point ( $V_{CEQ2}, I_{CQ2}$ )**

Since  $V_{CC}$  is not given to us, we take;

$$V_{CEQ2} \geq 1.5(V_{opeak} + V_{CE(sat)})$$

(The value is multiplies by 1.5 to take care of saturation voltages, variations in resistors, variation in supply voltage and decide parameter variations.)

$$V_{opeak} = V_{orms} \times \sqrt{2} = 2\sqrt{2} = \mathbf{2.828V}$$

$$V_{CEQ2} \geq 1.5(2.828 + 0.25)$$

$$V_{CEQ2} \geq \mathbf{4.6176}$$

$$V_{CEQ2} = \mathbf{4.7V}$$

$$I_{opeak} = \frac{V_{opeak}}{R_{C2}} = \frac{2.828}{750} = \mathbf{3.77mA}$$

$$I_{CQ2} \geq I_{opeak} \text{ (for undistorted output signal)}$$

$$I_{CQ2} \geq \mathbf{3.77mA}$$

$$I_{CQ2} = \mathbf{3.8mA}$$

**5. Selection of DC power supply ( $V_{CC}$ ):**

In order to achieve maximum symmetrical output swing, we always select Q point at center of DC load line

$$V_{CC} \geq 2V_{CEQ2} \geq 2 \times 4.7 \geq 9.4V \text{ (select HSV)}$$

$$\text{Select } V_{CC} = 10V$$

**6. Calculations of  $R_{E2}$ :**

For proper operation,

$$V_{RE2} = 10\% \text{ of } V_{CC} = 0.1 \times 10 = \mathbf{1V}$$

$$V_{RE2} = I_{EQ2} R_{E2}$$

$$R_{E2} = \frac{V_{RE2}}{I_{EQ2}}$$

$$I_{EQ2} = I_{CQ2}$$

$$R_{E2} = \frac{V_{RE2}}{I_{EQ2}} = \frac{1}{3.8 \times 10^{-3}} = 263.16V$$

$$R_{E2} = \mathbf{240\Omega, 1/4W} \text{ (selecting LSV)}$$

**7. Calculation of biasing resistors ( $R_3$  and  $R_4$ ):**

$$S \frac{1 + \beta}{1 + \beta \left( \frac{R_{E2}}{R_{E2} + R_{B2}} \right)}$$

$$\beta = h_{FE(typ)} = 180$$

$$10 = \frac{1 + 180}{1 + 180 \left( \frac{240}{240 + R_{B2}} \right)} = \mathbf{2286.315\Omega}$$

$$R_{B2} = \frac{R_3 R_4}{R_3 + R_4}$$

.....1

$$V_{TH2} = V_{B2} = \frac{R_4}{R_3 + R_4} \times V_{CC}$$

.....2

Applying KVL at loop of  $Q_2$

 


Figure 2: Thevenin Equivalent Circuit of  $Q_1$

Applying KVL at loop of  $Q_2$

$$V_{B2} - I_{BQ2}R_{B2} - V_{BE2} - I_{EQ2}R_{E2} = 0$$

$$V_{B2} = V_{BE2} + I_{BQ2}R_{B2} + I_{EQ2}R_{E2}$$

$$\text{But } I_{EQ2} = I_{CQ2} \text{ and } I_{BQ2} = \frac{I_{CQ2}}{\beta_2}$$

$$V_{B2} = 0.7 + \frac{I_{CQ2}}{\beta_2} R_{B2} + I_{CQ2} R_{E2} = 0.7 + \frac{3.8 \times 10^{-3}}{180} (2286.315) + (3.8 \times 10^{-3})(240)$$

$$= 0.7 + 0.04826 + 0.912 = \mathbf{1.66V}$$

$$\text{From 2, } V_{B2} = 1.66 = \frac{R_4}{R_3 + R_4} \times V_{CC}$$

$$\frac{R_4}{R_3 + R_3} = \frac{1.66}{10} = \mathbf{0.166} \quad \dots 3$$

$$\text{Putting 3 in 1, } 0.166 \times R_3 = \mathbf{2286.315}$$

$$R_3 = 13.772k\Omega$$

$$\text{Selecting HSV } R_3 = \mathbf{15k\Omega, 1/4W}$$

$$\text{From 3, } \frac{R_4}{R_3 + R_4} = 0.166$$

$$\frac{R_4}{15k + R_4} = 0.166$$

$$R_4 = 0.166 \times 15 \times 10^3 + 0.166 R_4$$

$$0.824 R_4 = 2490$$

$$R_4 = 2985.61$$

$$\text{Selecting LSV, } R_4 = \mathbf{2.7k\Omega, 1/4W}$$

**Design of first stage:**

#### 8. Selection of $R_{C1}$ :

$$|A_{V2}| = \frac{h_{fe(typ)} R_{C2}}{h_{ie}} = \frac{220 \times 750}{2.7 \times 10^3} = \mathbf{61.11}$$

$$A_{V1} = \frac{A_{VT}}{A_{V2}} = \frac{1750}{61.11} = \mathbf{28.636}$$

$$\text{Let } A_{V1} = 29$$

$$|A_{V1}| = \frac{h_{fe(typ)} R_{L1}}{h_{ie}}$$

$$\text{Where, } R_{L1} = R_{C1} \parallel R_3 \parallel R_4 \parallel h_{ie} = R_{C1} \parallel 15k \parallel 2.7k \parallel 2.7k = R_{C1} \parallel 15k \parallel 1.35k$$

$$= R_{C1} \parallel 1.2385k$$

$$\therefore 29 = \frac{220 \times (R_{C1} \parallel 1.2385k)}{2.7k} = \frac{220 \times R_{C1} \times 1.2385k}{2.7k(R_{C1} + 1.2385k)}$$

$$\frac{R_{C1}}{R_{C1} + 1.2385k} = 0.28737$$

$$R_{C1}(1 - 0.28737) = 0.38737 \times 1.2385 \times 10^3 = 499.43\Omega$$

$$\text{Selecting HSV, } R_{C1} = 510\Omega, 1/4W$$

### 9. Calculation of $R_{E1}$ :

$$V_{CEQ1} = V_{CEQ2} = 4.7V$$

$$V_{RE1} = V_{RE2} = 1V$$

$$V_{RC1} = V_{RC2}$$

$$\text{So, } I_{CQ1}R_{C1} = I_{CQ2}R_{C2}$$

$$\frac{I_{CQ2}R_{C2}}{R_{C1}} = \frac{3.8 \times 10^{-3} \times 750}{510} = \mathbf{5.588mA}$$

$$V_{RE1} = I_{EQ1}R_{E1} = 1V$$

$$R_{E1} = \frac{V_{RE1}}{I_{CQ1}} = \frac{1}{5.588 \times 10^{-3}} = \mathbf{178.95\Omega}$$

Selecting LSV,  $R_{E1} = 150\Omega, 1/4W$

### 10. Calculation of biasing resistors ( $R_1$ and $R_2$ ):

$$S = \frac{1 + \beta}{1 + \beta \left( \frac{R_{E1}}{R_{B1} + R_{E1}} \right)}$$

$$R_{B1} = R_1 \parallel R_2$$

$$h_{fe(typ)} = \beta = 180$$

$$10 = \frac{1 + 180}{1 + 180 \left( \frac{150}{R_{B1} + 150} \right)} = \mathbf{1428.94}$$

$$R_{B1} = \frac{R_1 R_2}{R_1 + R_2} = \mathbf{1428.94}$$

.....4

Applying KVL at Base - Emitter Loop of  $Q_1$ ;

$$V_{B1} - V_{BE1} - I_{BQ1}R_{B1} - I_{EQ1}R_{E1} = 0$$

$$I_{BQ1} = \frac{I_{CQ1}}{\beta_1} \text{ and } I_{EQ1} = I_{CQ1}$$

$$V_{B1} = V_{BE1} + \frac{I_{CQ1}}{\beta_1} R_{B1} + I_{CQ1} R_{E1} = 0.7 + \frac{5.588 \times 10^{-3}}{180} (1428.94) + (5.588 \times 10^{-3} \times 150)$$

$$V_{B1} = 0.7 + 0.044 + 0.8382 = 1.5822V$$

$$\text{Now, } V_{B1} = V_{TH1} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$1.5822 = \frac{R_2}{R_1 + R_2} \times 10$$

$$\frac{R_2}{R_1 + R_2} = 0.15822$$

.....5

 


Figure 3: Thevenin Equivalent Circuit of  $Q_1$

From 4 and 5, we get;

$$R_1(0.15822) = 1428.94 = \mathbf{9.0313k\Omega}$$

Select HSV,  $R_1 = 9.1K\Omega, 1/4W$

$$\frac{R_2}{9.1k + R_2} = 0.15822$$

$$R_2(1 - 0.15822) = 0.15822 \times 9.1 \times 10^3 = 17104\Omega$$

Select LSV,  $R_2 = 1.5k\Omega, 1/4W$

## 11. Calculations of Coupling capacitors ( $C_{C1}$ , $C_{C2}$ , $C_{C3}$ )

a.  $C_{C1} = \frac{1}{2\pi R_{eq} f_L}$

 


Figure 4: Small signal equivalent circuit of  $C_{C1}$

Where,  $R_{eq} = R_1 \parallel R_2 \parallel h_{ie} = 9.1k \parallel 1.5k \parallel 2.7k = 871.89\Omega$

$$C_{C1} = \frac{1}{2\pi \times 30 \times 871.89} = 6.0846\mu F$$

Select HSV,  $C_{C1} = 6.2\mu\text{F}/25\text{V}$

b.  $C_{C2} = \frac{1}{2\pi R_{eq2} f_L}$

 


Figure 5: Small signal equivalent circuit of  $C_{C2}$

Where,

$$R_{eq2} = R_{C1} + (R_3 \parallel R_4 \parallel h_{ie}) = 510 + (15k \parallel 2.7k \parallel 2.7k) = 510 + 1.2385k = 1748.53\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 30 \times 1748.53} = 3.034\mu\text{F}$$

Select HSV,  $C_{C2} = 3.3\mu\text{F}/25\text{V}$

c.  $C_{C3} = \frac{1}{2\pi R_{eq3} f_L}$

 


Figure 6: Small signal equivalent circuit of  $C_{C3}$

$$R_{eq3} = R_{C2} = 750\Omega$$

$$\therefore C_{C3} = \frac{1}{2\pi \times 30 \times 750} = 7.07\mu\text{F}$$

Select HSV,  $C_{C3} = 7.5\mu\text{F}/25\text{V}$

## 12. Calculations of bypass capacitors ( $C_{E1}$ , $C_{E2}$ )

a. For  $C_{E1}$ :

$$X_{CE1} = \frac{R_{E1}}{10}$$

$$\frac{1}{2\pi f_L C_{E1}} = \frac{R_{E1}}{10}$$

$$C_{E1} = \frac{10}{2\pi f_L R_{E1}} = \frac{10}{2\pi \times 30 \times 150} = 353.67 \mu F$$

Select HSV,  $C_{E1} = 390 \mu F / 25V$

b. For  $C_{E2}$ :

$$X_{CE2} = \frac{R_{E2}}{10} = \frac{240}{10} = 24$$

$$\frac{1}{2\pi C_{E2} f_L} = 24$$

$$C_{E2} = \frac{1}{2\pi \times 24 \times 30} = 221.04 \mu F$$

Select HSV,  $C_{E2} = 240 \mu F / 25V$

13. Complete designed circuit:

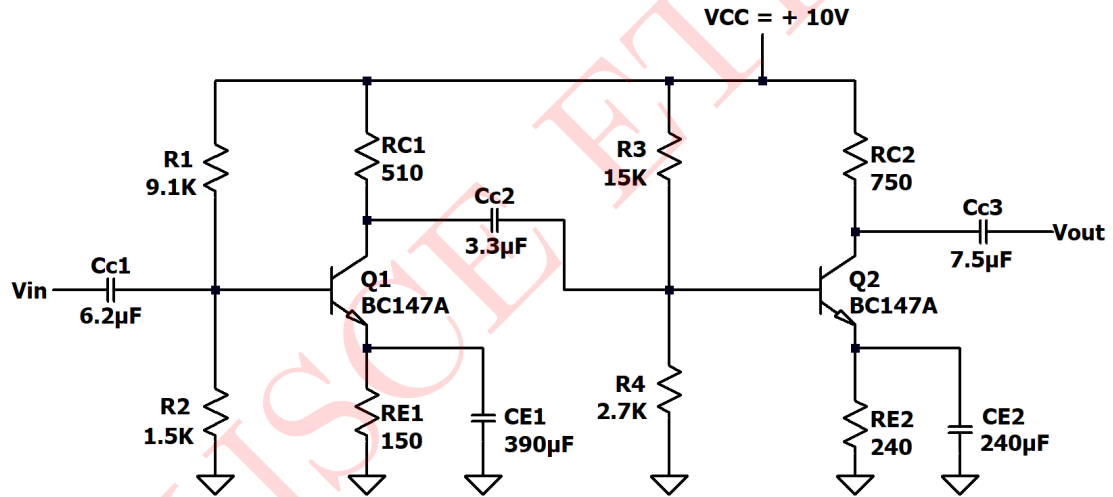


Figure 7: Designed circuit

Verification of Overall gain  $A_{VT}$ :

$$A_{V2} = \frac{h_{fe(typ)} R_{C2}}{h_{ie}} = \frac{220 \times 750}{2.7 \times 10^3} = 61.111$$

$$A_{V1} = \frac{h_{fe(typ)} (R_{C2} \parallel R_3 \parallel R_4 \parallel h_{ie})}{h_{ie}} = \frac{220 \times (510 \parallel 15k \parallel 2.7k \parallel 2.7k)}{2.7 \times 10^3}$$

$$= \frac{220 \times (493.23 \parallel 1350)}{2.7 \times 10^3} = 29.43$$

$$\text{Now, } A_{VT} = A_{V1} \times A_{V2} = 61.111 \times 29.43 = 1798.79$$

So,  $A_{VT} \geq 1750$



**DC Analysis:** For first stage:

 


Figure 8: Thevenin equivalent circuit for first stage

$$R_{TH1} = R_1 \parallel R_2 = 9.1k \parallel 1.5k = 1.2877k\Omega$$

$$V_{TH1} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{1.5k}{9.1k + 1.5k} \times 10 = 1.415V$$

Applying KVL to Base - Emitter loop;

$$V_{TH1} - I_{B1}R_{TH1} - V_{BE1} - I_{E1}R_{E1} = 0$$

$$\text{But } I_{E1} = (1 + \beta_1)I_{B1}$$

$$\therefore V_{TH1} - V_{BE1} = I_{B1}R_{TH1} + (1 + \beta_1)I_{B1}R_{E1}$$

$$I_{B1} = \frac{V_{TH1} - V_{BE1}}{R_{TH1} + (1 + \beta_1)R_{E1}} = \frac{1.415 - 0.7}{1.2877k + (181)(150)} = \frac{0.71509}{28437.7} = \mathbf{25.14\mu A}$$

$$\text{Now, } I_{C1} = \beta_1 I_{B1} = 4.5mA$$

$$I_{E1} = (\beta_1 + 1)I_{B1} = 181 \times 25.14 \times 10^{-6} = \mathbf{4.5mA}$$

$$V_{E1} = I_{E1}R_{E1} = 4.5 \times 10^{-3} \times 150 = \mathbf{0.675V}$$

$$V_{BE1} = 0.7 = V_{B1} - V_{E1}$$

$$V_{B1} = 0.7 + V_{E1} = 0.7 + 0.675 = 1.375V$$

$$\text{Here, } R_{TH2} = 15k \parallel 2.7k = 2.288k\Omega$$

$$V_{TH2} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{2.7k}{15k + 2.7k} \times 10 = \mathbf{1.5254V}$$

Applying KVL to Base - Emitter loop;

$$V_{TH2} - I_{B2}R_{TH2} - V_{BE2} - I_{E2}R_{E2} = 0$$

$$\text{But, } I_{E2} = (1 + \beta_2)I_{B2}$$

 


Figure 9: Thevenin equivalent circuit for second stage

$$I_{B2} = \frac{V_{TH} - V_{BE2}}{R_{TH2} + (1 + \beta_2)R_{E2}} = \frac{1.5254 - 0.7}{2.288k + (181)(240)} = \frac{0.8254}{45728} = \mathbf{18\mu A}$$

$$I_{C2} = \beta_2 I_{B2} = 180 \times 18 \times 10^{-6} = \mathbf{3.24mA}$$

$$I_{E2} = (\beta_2 + 1)I_{B2} = 181 \times 3.24mA = \mathbf{3.26mA}$$

$$V_{E2} = I_{E2}R_{E2} = 3.26 \times 10^{-3} \times 240 = \mathbf{0.78V}$$

$$V_{B2} = V_{BE2} + V_{E2} = 0.7 + 0.78 = \mathbf{1.48V}$$

**Small signal parameters:**

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{4.5 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{173.076mA/V}$$

$$r_{\pi1} = \frac{\beta_1 V_T}{I_{C1}} = \frac{180 \times 26 \times 10^{-3}}{4.5 \times 10^{-3}} = \mathbf{1040\Omega}$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{3.24 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{124.6mA/V}$$

$$r_{\pi2} = \frac{\beta_2 V_T}{I_{C2}} = \frac{18 \times 26 \times 10^{-3}}{3.24 \times 10^{-3}} = \mathbf{1444.44\Omega}$$

### Mid band frequency equivalent circuit

 


Figure 10: mid band frequency equivalent circuit

**Voltage gain of first stage:**

$$\begin{aligned}
 A_{V1} &= \frac{V_1}{V_{in}} = \frac{-g_m V_{\pi1} (R_{C1} \parallel R_3 \parallel R_4 \parallel r_{\pi2})}{V_{\pi}} = -g_m (R_{C1} \parallel R_3 \parallel R_4 \parallel r_{\pi2}) \\
 &= -173.076 \times 10^{-3} (15k \parallel 2.7k \parallel 510 \parallel 1444.44) \\
 &= -173.076 \times 10^{-3} (2288.135 \parallel 376.918) = \mathbf{-56}
 \end{aligned}$$

**Voltage gain of second stage:**

$$A_{V2} = \frac{V_{out}}{V_1} = \frac{-g_{m2} V_{\pi2} R_{C2}}{V_{\pi2}} = -g_{m2} R_{C2} = -124.6 \times 10^{-3} \times 750 = \mathbf{-93.45}$$

**Overall voltage gain:**

$$A_{VT} = A_{V1} \times A_{V2} = -56 \times -93.45 = \mathbf{5233.2}$$

$$A_{VT} \text{ in dB} = 20 \log_{10}(5233.2) = \mathbf{74.375dB}$$

Input impedance of first stage

$$Z_i = R_1 \parallel R_2 \parallel r_{\pi1} = 9.1k \parallel 1.5k \parallel 1040 = \mathbf{575.34\Omega}$$

**Output impedance of second stage:**

$$Z_o = R_C = \mathbf{750\Omega}$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

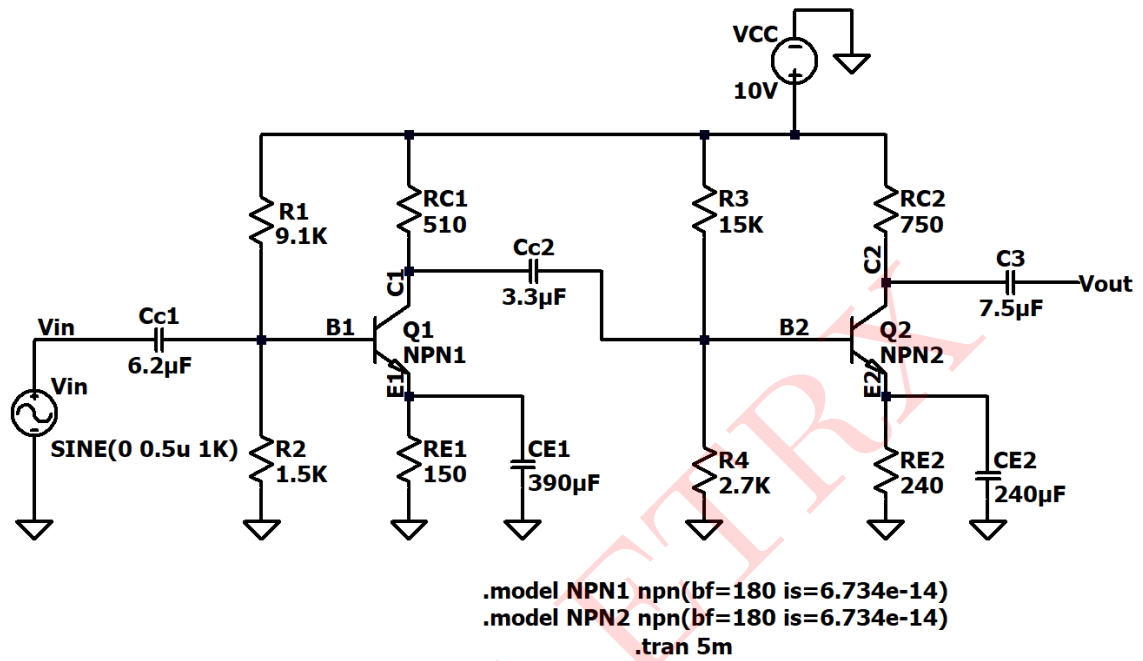


Figure 11: Circuit Schematic

 


Figure 12: Input output waveform stage 1

 


Figure 13: Input output waveform stage 2

**Comparison between Theoretical and Simulated values :-**

Parameters	Theoretical	Simulated
$I_{B1}$	$25\mu A$	$27\mu A$
$I_{C1}$	$4.5mA$	$4.8mA$
$I_{E1}$	$4.5mA$	$4.8mA$
$I_{B2}$	$18\mu A$	$19\mu A$
$I_{C2}$	$3.2mA$	$3.49mA$
$I_{E2}$	$3.2mA$	$3.5mA$
$V_{B1}$	$1.375V$	$1.38V$
$V_{E1}$	$0.67V$	$0.73V$
$V_{B2}$	$1.48V$	$1.48V$
$V_{E2}$	$0.88V$	$0.84V$
Voltage gain of first stage	$-30$	$-59.28$
Voltage gain of second stage	$-59$	$-100.3$
Overall voltage gain	$64.86dB$	$75.48dB$
input impedance	$575.34\Omega$	—
output impedance	$750\Omega$	—

Table 1: Numerical 1

**Design 2:** Design a two stage RC coupled cascade amplifier for following specifications  
 $A_V \geq 400$ ,  $V_{CC} = 20V$ ,  $S \leq 10$ ,  $R_i \geq 1M\Omega$ . Use transistor BC 147A from the data sheet.

**Solution:**

Above requirements can be fulfilled by CS - CS stage. (We select CS as the first stage since  $R_i \geq 1M\Omega$ )

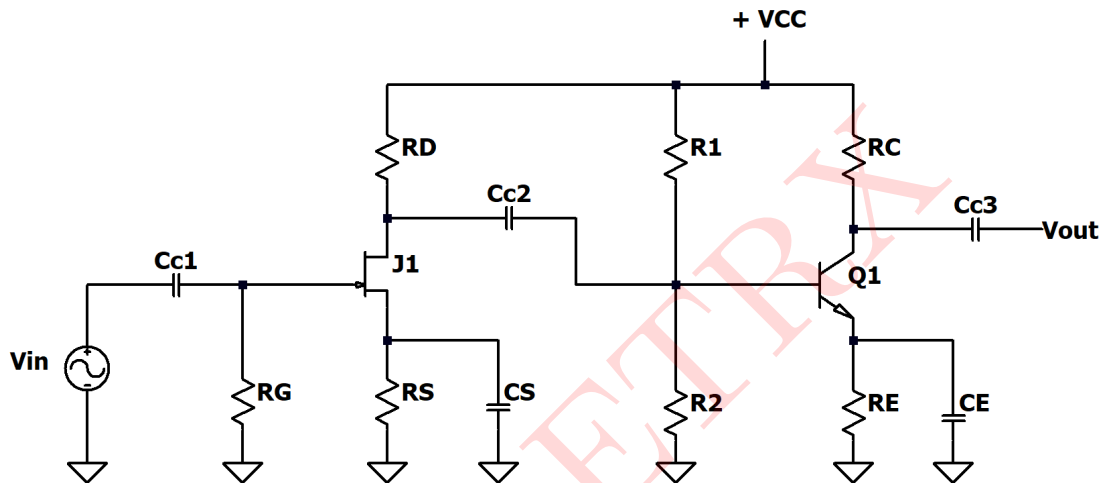


Figure 14: Circuit 2

### 1) Selection of transistor:

Selecting BC147B:

$$h_{fe(typ)} = 330, h_{FE(typ)} = 290 = \beta$$

$$h_{ie} = 4.5k\Omega, V_{CE(sat)} = 0.25V$$

Selecting BFW11:

$$I_{DSS} = 7mA, g_{mo} = 5600\mu S$$

$$V_P = -2.5V, r_d = 50k\Omega$$

### 2. Selection of voltage gains:

$$A_V \geq 400$$

Let  $A_{V1} = 4$  (Since JFET amplifier gain is less)

$$A_{V2} = \frac{400}{4} = 100$$

$$\text{Let } A_{V2} = 100$$

### Design of second stage:

### 3. Calculations of $R_C$ :

$$|A_{V2}| = \frac{h_{fe(typ)} R_C}{h_{ie}}$$

$$100 = \frac{330 \times R_C}{4.5 \times 10^3}$$

$$R_C = 1.3636k\Omega$$

Selecting HSV,  $R_{C2} = 1.5k\Omega, 1/4W$

#### 4. Selection of Q point ( $V_{CEQ2}, I_{CQ2}$ )

$$V_{CC} = 20V;$$

$$\text{Let } V_{CEQ2} = \frac{V_{CC}}{2} = 10V$$

$$V_{RE} = 0.1V_{CC} = 0.1 \times 20 = 2V$$

 


Figure 15: Thevenin Equivalent Circuit of BJT

Applying KVL to Common - emitter loop;

$$V_{CC} - V_{RC} - V_{CEQ} - V_{RE} = 0$$

$$V_{RC} = V_{CC} - V_{CEQ} - V_{RE} = 20 - 10 - 2 = 8V$$

$$V_{RC} = I_{CQ}R_C = 8$$

$$I_{CQ} = \frac{8}{1.5 \times 10^3} = 5.33mA$$

#### 5. Selection of $R_E$ :

$$V_{RE} = 2V$$

$$\therefore I_{EQ}R_E = 2$$

$$\therefore R_E = \frac{2}{5.33 \times 10^{-3}} = 375.23\Omega \text{ (since } I_{EQ} = I_{CQ}\text{)}$$

Selecting LSV,  $R_E = 390\Omega, 1/4W$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{5.33 \times 10^{-3}}{290} = 18.37\mu A$$

$$I_{EQ} = I_{CQ} + I_{BQ} = 5.34mA$$

**6. Selection of biasing resistors  $R_1$  and  $R_2$ :**

$$S \leq 10 \text{ and } \beta = 290$$

$$\text{Let } S = 10$$

$$S = \frac{1 + \beta}{1 + \beta \left( \frac{R_E}{R_B + R_E} \right)}$$

$$10 = \frac{1 + 290}{1 + 290 \left( \frac{390}{390 + R_B} \right)}$$

$$R_B = 3.6349k\Omega$$

$$R_B = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} = 3.6349k\Omega \quad \text{.....1}$$

$$V_B = V_{TH2} = \frac{R_2}{R_1 + R_2} \times V_{CC} \quad \text{.....2}$$

Applying KVL at base -emitter loop of BJT;

$$V_B - I_{BQ}R_B - V_{BE} - I_{EQ}R_E = 0$$

$$V_B = I_{BQ}R_B + V_{BE} + I_{EQ}R_E$$

$$I_{EQ} = I_{CQ} \text{ and } I_{BQ} = \frac{I_{CQ}}{\beta}$$

$$\therefore V_B = \frac{I_{CQ}}{\beta} R_B + V_{BE} + I_{CQ} R_E = \frac{5.33}{290} \times 10^{-3} \times 3.6349 \times 10^3 + 0.7 + 5.33 \times 10^{-3} \times 390 = \mathbf{2.8455V}$$

$$\text{From 2, } 2.8455 = \frac{R_2}{R_1 + R_2} \times 20$$

$$\frac{R_1}{R_1 + R_2} = 0.142275 \quad \text{.....3}$$

Putting 3 in 1;

$$R_1 \times 0.142275 = 3.6349 \times 10^3$$

$$R_1 = \mathbf{25548.40\Omega}$$

Selecting HSV,  $R_1 = \mathbf{27k\Omega, 1/4W}$

$$\text{From 3; } \frac{R_2}{R_2 + 27k} = 0.142275$$

$$R_2 = 0.142275 R_2 + 3841.425 = \mathbf{4.4786k\Omega}$$

Selecting HSV,  $R_2 = \mathbf{4.7k\Omega, 1/4W}$

$$V_E - I_{EQ}R_E = 5.34 \times 10^{-3} \times 390 = \mathbf{2.0826V}$$



**Design of first stage:**

**7. Selection of Q point  $I_{DQ}, V_{GSQ}$ :**

using Mid- point biasing

$$I_{DQ} = \frac{I_{DSS}}{2} = \frac{7mA}{2} = \mathbf{3.5mA}$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_{GS} = V_P \left(1 - \sqrt{\frac{I_{DQ}}{I_{DSS}}}\right) = -2.5 \left(1 - \sqrt{\frac{3.5}{7}}\right) = \mathbf{-0.732V}$$

$$g_{m1} = g_{mo} \left(1 - \frac{V_{GSQ}}{V_P}\right) = 5600 \times 10^{-6} \left(1 - \frac{(-0.732)}{-2.5}\right) = \mathbf{3.96mA/V}$$

**8. Calculation of  $R_D$ :**

$$|A_{V2}| = \frac{h_{fe(typ)} \times R_C}{h_{ie}} = \frac{330 \times 1.5 \times 10^3}{4.5 \times 10^3} = \mathbf{110}$$

$$A_{V1} = g_{m1}(R_D \parallel r_d \parallel R_1 \parallel R_2 \parallel h_{ie})$$

$$R_{L1} = r_d \parallel R_1 \parallel R_2 \parallel h_{ie} = 50k \parallel 27k \parallel 4.7k \parallel 4.5k = \mathbf{2032.426\Omega}$$

$$|A_{V1}| = g_m(R_D \parallel 2032.416)$$

$$\text{Now, } |A_{V1}| = \frac{A_{VT}}{A_{V2}} = \frac{400}{110} = \mathbf{3.636}$$

 


Figure 16: Small signal equivalent circuit for selection of  $R_D$

$$\therefore 3.636 = 3.96 \times 10^{-3}(R_D \parallel 2032.416)$$

$$\therefore 3.636 = 3.96 \times 10^{-3} \left( \frac{R_D \times 2032.416}{R_D + 2032.416} \right)$$

$$\therefore 918.27(R_D) = 1866314.05 = 2032.416(R_D)$$

$$R_D = 1.675k\Omega$$

Selecting HSV,  $R_D = 1.8k\Omega, 1/4W$

**9. Selection of  $R_S$ :**

$$V_{GSQ} = -I_{DQ}R_S$$

$$-0.732 = -3.5 \times 10^{-3} R_S$$

$$R_S = 209.14\Omega$$

Selecting LSV,  $R_S = 180\Omega, 1/4W$

#### 10. Calculations of $R_G$

Let  $R_G = 1.2M\Omega, 1/4W$  (since  $R_i \geq 1M\Omega$ , to prevent loading  $R_G \geq R_i$ )

#### 11. Calculations of Coupling capacitors ( $C_{C1}, C_{C2}, C_{C3}$ )

a.  $C_{C1} = \frac{1}{2\pi R_G f_L}$  (since  $f_L$  is not given we consider audio frequency  $f_L = 20Hz$ )

 


Figure 17: Low frequency equivalent circuit of  $C_{C1}$

$$C_{C1} = \frac{1}{2\pi \times 1.2 \times 10^6 \times 20} = 6.63nFF$$

Select HSV,  $C_{C1} = 6.63nF/50V$

b.  $C_{C2} = \frac{1}{2\pi R_{eq} f_L}$

 


Figure 18: Low frequency equivalent circuit of  $C_{C2}$

$$R_{eq} = r_d \parallel R_D + (R_1 \parallel R_2 \parallel h_{ie}) = (50k \parallel 1.8k) + (27k \parallel 4.7k \parallel 4.5k)$$

$$= 1737.45 + 2118.53 = 3855.98\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 3855.98 \times 20} = 32.06374\mu F$$

Select HSV,  $C_{C2} = 2.2\mu F/50V$

c.  $C_{C3} = \frac{1}{2\pi R_{eq2} f_L}$

 


Figure 19: Low frequency equivalent circuit of  $C_{C3}$

$$R_{eq3} = R_C = 1.5k\Omega$$

$$\therefore C_{C3} = \frac{1}{2\pi \times 1.5 \times 10^3 \times 20} = 5.305\mu F$$

Select HSV,  $C_{C3} = 5.6\mu F/50V$

## 12. Calculations of bypass capacitors:

a. For  $C_S$ :

$$R_{eq} = \left( \frac{1}{g_m} \parallel R_S \right) = \left( \frac{1}{3.96 \times 10^{-3}} \parallel 180 \right) = 105.09\Omega$$

$$C_S = \frac{1}{2\pi \times 105.09 \times 20} = 75.72\mu F$$

Selecting HSV,  $C_S = 82\mu F/50V$

b. For  $C_E$ :

$$X_{CE} = 0.1R_E$$

$$\frac{1}{2\pi C_E f_L} = 0.1R_E$$

$$C_E = \frac{1}{2\pi \times 20 \times 0.1 \times 390} = 204\mu F$$

Select HSV,  $C_E = 220\mu F/50V$

### 13. Complete designed circuit:

 


Figure 20: Designed circuit

### Mid band frequency equivalent circuit

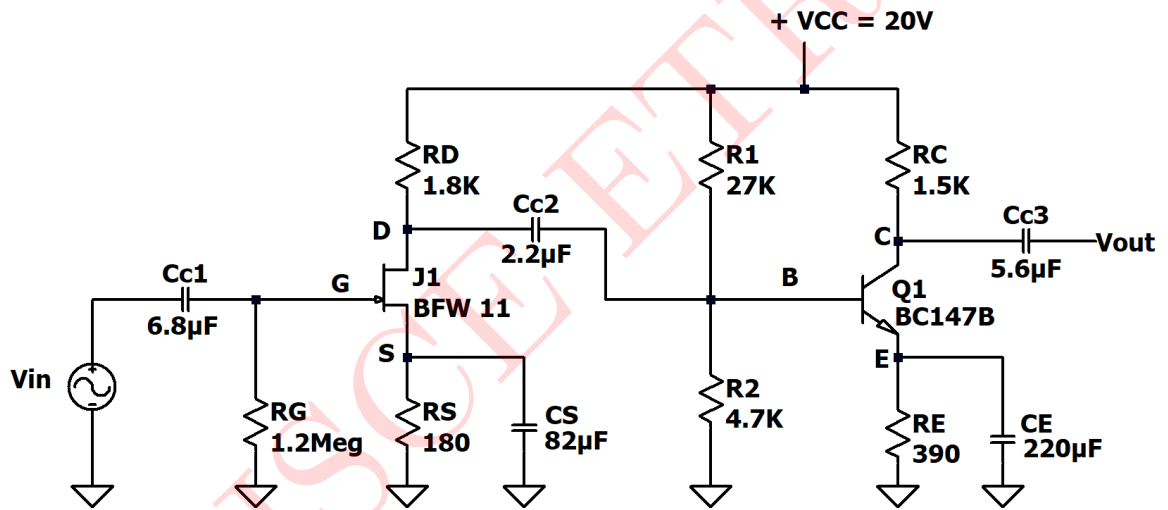


Figure 21: Mid band frequency equivalent circuit

**Input impedance:**

$$Z_i = R_G = 1.2\text{M}\Omega$$

**Output impedance :**

$$Z_o = R_C = 1.5\text{k}\Omega$$

$$g_{m1} = 3.96\text{mA/V}$$

$$g_{m2} = \frac{I_{CQ}}{V_T} = \frac{5.33 \times 10^{-3}}{26 \times 10^{-3}} = 205\text{mA/V}$$

$$A_{VT} = A_{V1} \times A_{V2}$$

$$\text{Here, } A_{V2} = \frac{V_{out}}{V_1} \text{ and } A_{V1} = \frac{V_1}{V_{in}}$$

$$A_{V2} = \frac{-g_{m2}V_{\pi}R_C}{V_{\pi}} = -g_{m2}R_C = -205 \times 10^{-3} \times 1.5 \times 10^3 = -307.5$$

$$A_{V1} = \frac{V_1}{V_{in}} = \frac{-g_{m1}V_{gs}(r_d \parallel R_D \parallel R_L \parallel R_2 \parallel r_\pi)}{V_{gs}} = -g_{m1}(r_d \parallel R_D \parallel R_1 \parallel R_2 \parallel r_\pi)$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{290 \times 26 \times 10^{-3}}{5.33 \times 10^{-3}} = 1.4146k\Omega$$

$$A_{V1} = -3.96 \times 10^{-3}(50k \parallel 1.8k \parallel 27k \parallel 4.7k \parallel 1.4146k) = -2.584$$

$$A_{VT} = -307.5 \times -2.584 = 794.58$$

$$A_{VT} \text{ in dB} = 20\log_{10}(794.58) = 58\text{dB}$$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and the result is as follows:

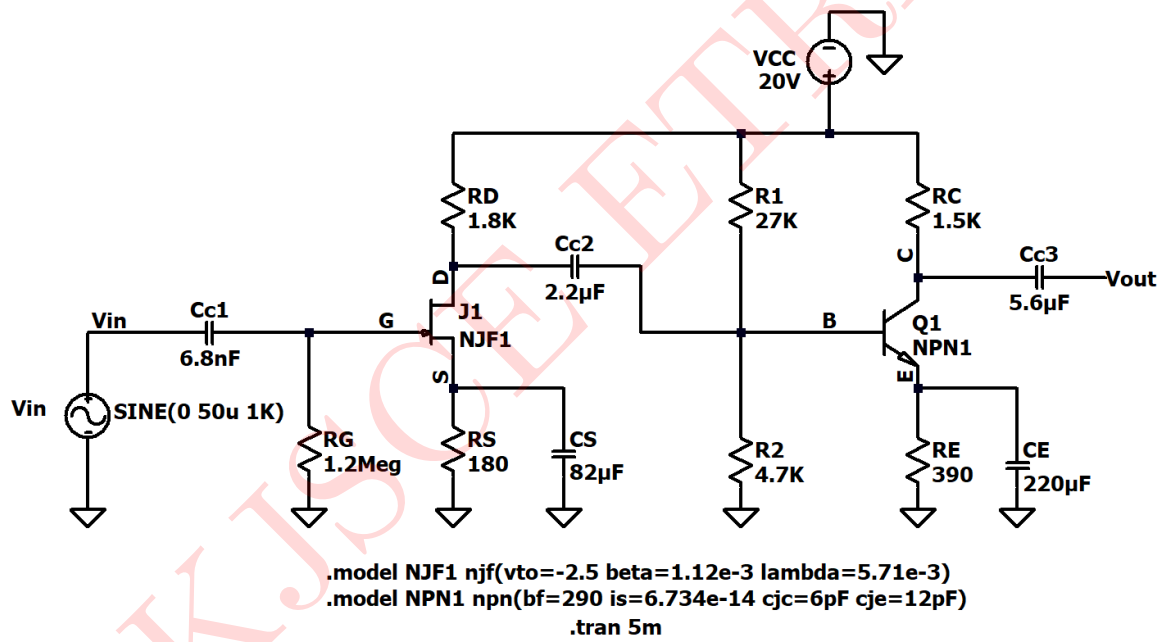


Figure 22: Circuit Schematic

 


Figure 23: Input output waveform of stage 1

 


Figure 24: Input output waveform of stage 2

**Comparison between Theoretical and Simulated values :-**

Parameters	Theoretical	Simulated
$I_{DQ}$	3.5mA	3.8mA
$V_{GSQ}$	-0.732V	-0.6885
$I_B$	18.37 $\mu$ A	19.67 $\mu$ A
$I_C$	5.33mA	5.7mA
$I_E$	5.34mA	5.7mA
$V_E$	2.0826V	2.23V
$V_B$	2.8455V	2.88V
Voltage gain of first stage	-2.584	-2.77
Voltage gain of second stage	-307.5	-320.08
Overall voltage gain	52.04dB	58.97dB
input impedance	1.2M $\Omega$	—
output impedance	1.5k $\Omega$	—

Table 2: Numerical 2

\*\*\*\*\*