

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Darlington Amplifier

12th July, 2020

Numerical 1:

For each of the transistor, $\beta = 100$ and $V_A = \infty$, determine:

1. Q-point for both transistors
2. Overall small signal voltage gain $A_V = V_o/V_i$
3. Input and output resistance R_i and R_o

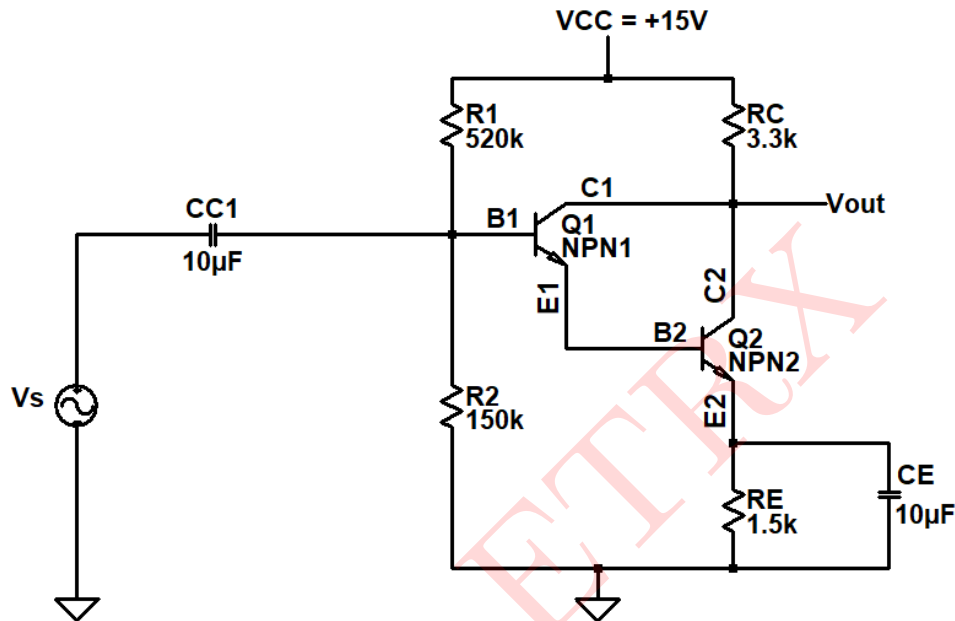


Figure 1: Circuit diagram

Solution: Circuit shown in figure 1 is a CE Darlington pair circuit.

DC equivalent circuit is shown in figure 2:

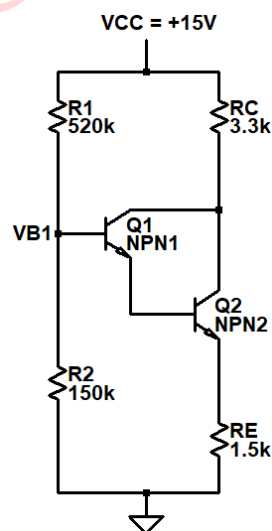


Figure 2: DC equivalent circuit

$$V_{TH} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{150k\Omega}{520k\Omega + 150k\Omega} \times 15$$

$$\therefore V_{TH} = 3.3582V$$

$$R_{TH} = 150k\Omega \parallel 520k\Omega$$

$$\therefore R_{TH} = 116.4179k\Omega$$

Applying KVL to B-E loop:

$$V_{TH} - I_{B1}R_B - V_{BE} - I_{E2}R_E = 0 \quad \dots(\text{here } R_B = R_{TH})$$

$$V_{BE} = V_{BE1} + V_{BE2} = 0.7 + 0.7$$

$$\therefore V_{BE} = 1.4V$$

$$I_{E2} = (1 + \beta_2)I_{B2}$$

$$\therefore I_{E2} = (1 + \beta_2)I_{E1} \quad \dots(\because I_{B2} = I_{E1})$$

$$\therefore I_{E2} = (1 + \beta_2)(1 + \beta_1)I_{B1}$$

$$\therefore V_{TH} - I_{B1}R_B - V_{BE} - (1 + \beta_1)(1 + \beta_2)I_{B1}R_E = 0$$

$$\therefore I_{B1} = \frac{V_{TH} - V_{BE}}{R_B + (1 + \beta_1)(1 + \beta_2)R_E} = \frac{3.3582 - 1.4}{116.4179k\Omega + (101)(101)(1.5k\Omega)}$$

$$\therefore I_{B1} = 0.12701\mu A$$

$$I_{C1} = \beta_1 I_{B1} = 100(0.12701\mu A)$$

$$\therefore I_{C1} = 0.0127mA$$

$$I_{E1} = I_{C1} + I_{B1} = 0.01283mA$$

$$\therefore I_{C2} = \beta_2 I_{B2} = (100)(0.01083mA) = 1.2827mA$$

$$I_{E2} = I_{C2} + I_{B2} = 1.2955mA$$

$$\therefore V_{E2} = I_{E2}R_E = (1.2955mA)(1.5k\Omega)$$

$$\therefore V_{E2} = 1.9433V$$

$$V_{C2} = V_{CC} - I_{C2}R_C$$

$$\therefore V_{C2} = 15 - (1.2827mA)(3.3k\Omega)$$

$$\therefore V_{C2} = 10.7671V$$

Small signal parameters:

$$r_{\pi 1} = \frac{\beta V_T}{I_{C1}} = \frac{100 \times 26mV}{0.0127mA}$$

$$\therefore r_{\pi 1} = 204.724k\Omega$$

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{0.0127mA}{26}$$

$$\therefore g_{m1} = 0.4885mA/V$$

$$r_{\pi 2} = \frac{\beta V_T}{I_{C2}} = \frac{(100)(26mV)}{1.2827mA}$$

$$\therefore r_{\pi 2} = 2.0269k\Omega$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{1.2827mA}{26mV}$$

$$\therefore g_{m2} = 49.335mA/V$$

Small signal equivalent circuit is shown in figure 3:

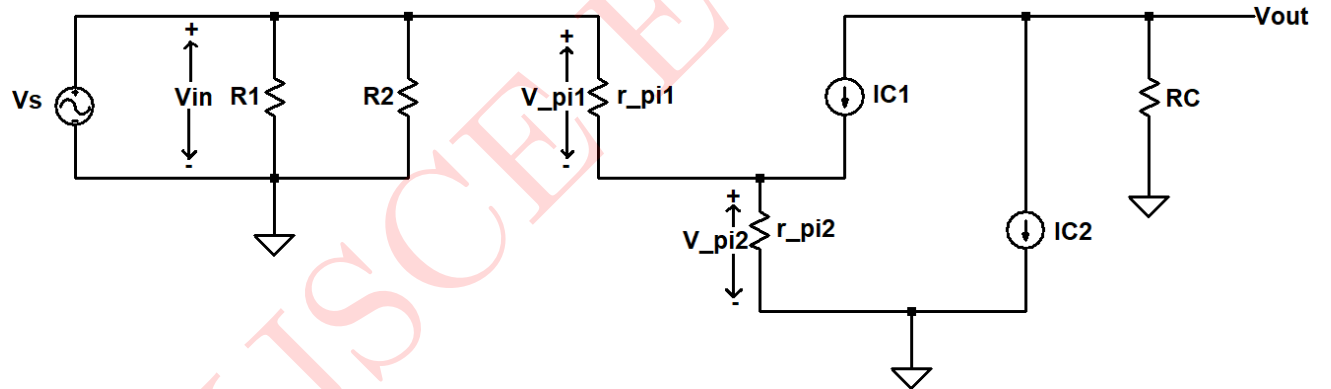


Figure 3: Small signal equivalent circuit

$$Z_{1i} = r_{\pi 1} + (1 + \beta_1)r_{\pi 2}$$

$$Z_{1i} = 204.724 + (101)(2.0269k\Omega)$$

$$\therefore Z_{1i} = 409.44k\Omega$$

$$\text{Input impedance: } Z_i = R_1 \parallel R_2 \parallel Z_{i1}$$

$$\therefore Z_i = 116.4179k\Omega \parallel 409.44k\Omega$$

$$\therefore Z_i = 90.645k\Omega$$

Output impedances: $Z_{o1} = \frac{R_1 \parallel R_2 + r_{\pi 1}}{1 + \beta_1} = \frac{116.4179k\Omega + 204.724k\Omega}{101}$

$$\therefore Z_{o1} = 3.1796k\Omega$$

$$Z_{o2} = \frac{Z_{o1} + r_{\pi 2}}{1 + \beta_2} = \frac{3.1796k\Omega + 2.0269k\Omega}{101}$$

$$\therefore Z_{o2} = 0.5155k\Omega$$

$$\therefore Z_o = Z_{o2} \parallel R_C = 0.5155k\Omega \parallel 3.3k\Omega$$

$$\therefore Z_o = 0.508k\Omega$$

Current gain of Stage 1: $A_{i1} = \frac{I_{C1}}{I_{B1}} = \frac{\beta_1 I_{B1}}{I_{B1}} = \beta_1$

$$\therefore A_{i1} = 100$$

Current gain of Stage 2: $A_{i2} = \frac{I_{C2}}{I_{B2}} = \frac{\beta_2 I_{B2}}{I_{B2}} = \beta_2$

$$\therefore A_{i2} = 100$$

$$A_{id} = A_{i1} \times A_{i2} = 10000$$

Overall current gain:

$$A_{is} = \frac{I_o}{I_i} = \frac{I_o}{I_{B2}} \times \frac{I_{B2}}{I_{B1}} \times \frac{I_{B1}}{I_i}$$

$$\therefore A_{is} = A_{i2} \times A_{i1} \times \frac{I_{B2}}{I_i}$$

$$\therefore I_{B2} = I_{E1} \text{ and } I_{E1} = I_{C1}$$

$$\therefore A_{is} = A_{i2} \times A_{i1} \times \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + Z_i}$$

$$\therefore A_{is} = 100 \times 100 \times \frac{116.4179k\Omega}{116.4179k\Omega + 409.44k\Omega}$$

$$\therefore A_{is} = 2213.866$$

Voltage gain for stage 1:

$$A_{V1} = \frac{V_1}{V_s} = \frac{I_{E1}}{I_{B1}} \times \frac{r_{\pi 2}}{Z_{i1}}$$

$$\therefore A_{V1} = \frac{I_{C1}}{I_{B1}} \times \frac{r_{\pi 2}}{Z_{i1}} = A_{i1} \times \frac{r_{\pi 2}}{Z_{i1}}$$

$$\therefore A_{V1} = 100 \times \frac{2.0269k\Omega}{409.44k\Omega}$$

$$\therefore A_{V1} = 0.4950$$

Voltage gain for stage 2:

$$A_{V2} = \frac{V_o}{V_1} = \frac{I_o}{I_{B2}} \times \frac{R_C}{r_{\pi2}}$$

$$\therefore A_{V2} = A_{i2} \times \frac{R_C}{r_{\pi2}} = 100 \times \frac{3.3k\Omega}{2.0269k\Omega}$$

$$\therefore A_{V2} = 162.81$$

$$\therefore A_{Vt} = A_{V1} \times A_{V2} = 80.591$$

$$A_V = \frac{V_{out}}{V_s}$$

$$\therefore V_{out} = A_{Vt} \times V_s$$

For $V_s = 20mV$,

$$\therefore V_{out} = 80.591(20mA) = -1.6118V$$

SIMULATED RESULTS:

Above circuit was simulated in LTspice and results obtained are as follows:

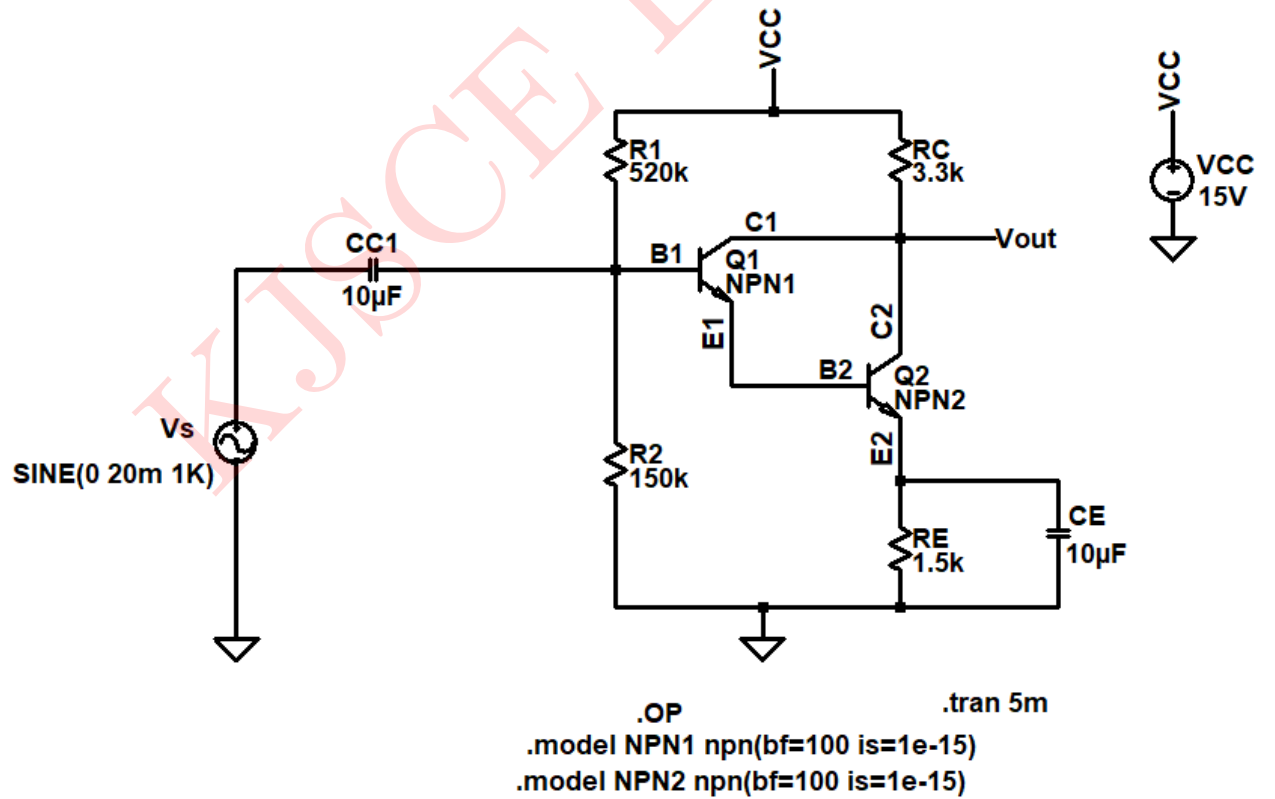


Figure 4: Circuit Schematic: Results

Input and output waveforms for each stage are shown below:

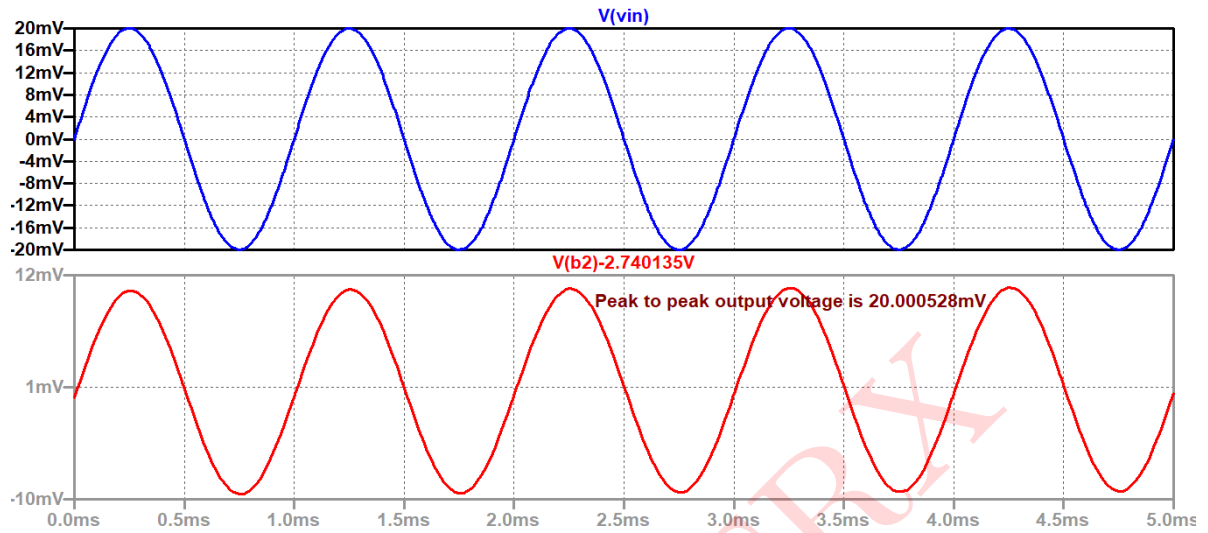


Figure 5: Input and output voltage waveform for Stage 1

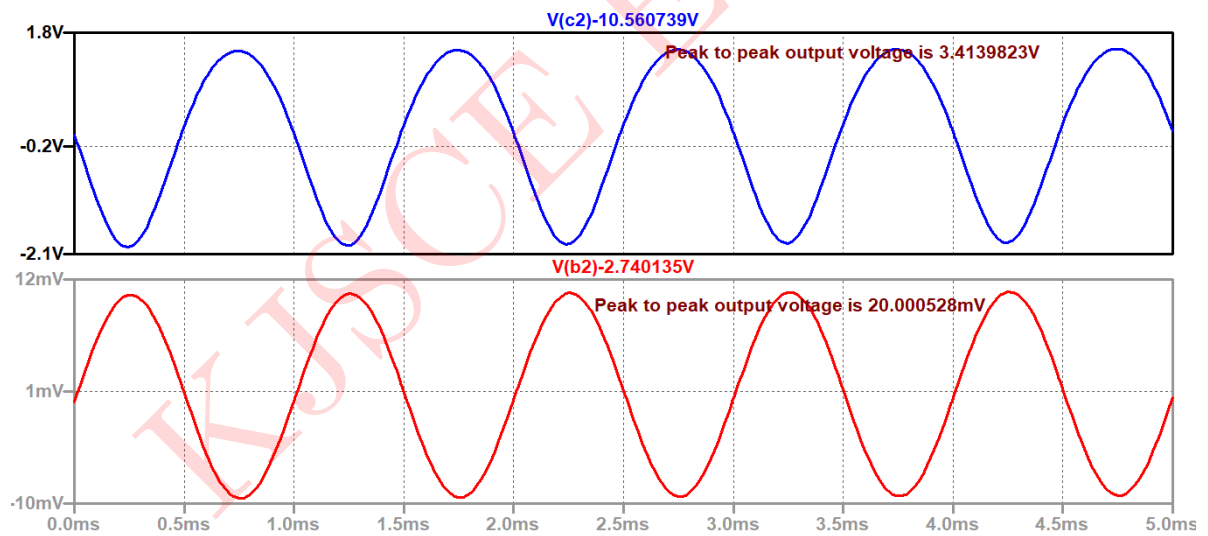


Figure 6: Input and output voltage waveform for Stage 2

Input and output waveforms for each stage are shown below:

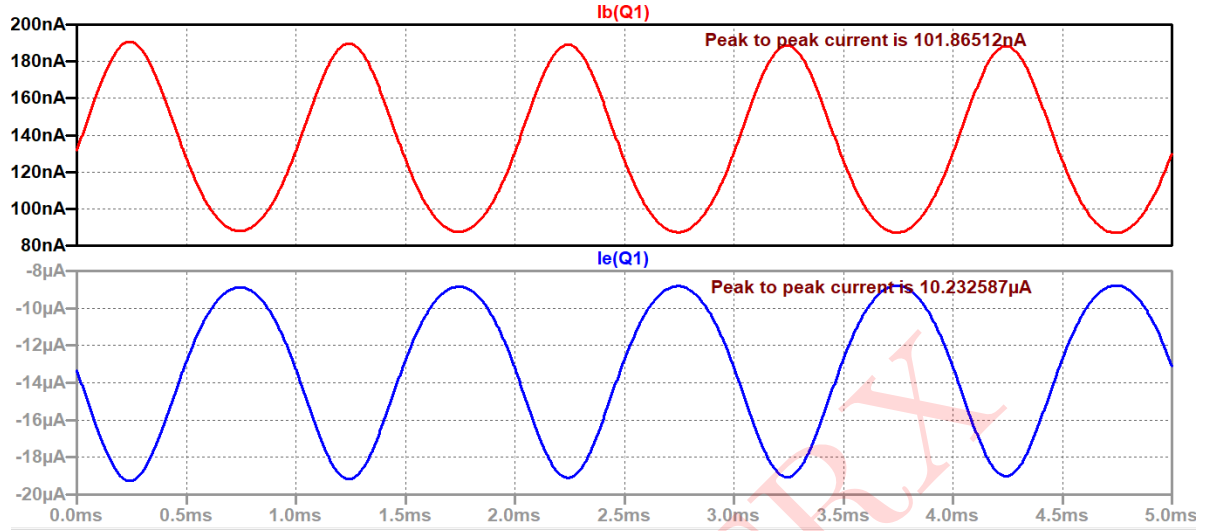


Figure 7: Input and output current waveform for Stage 1

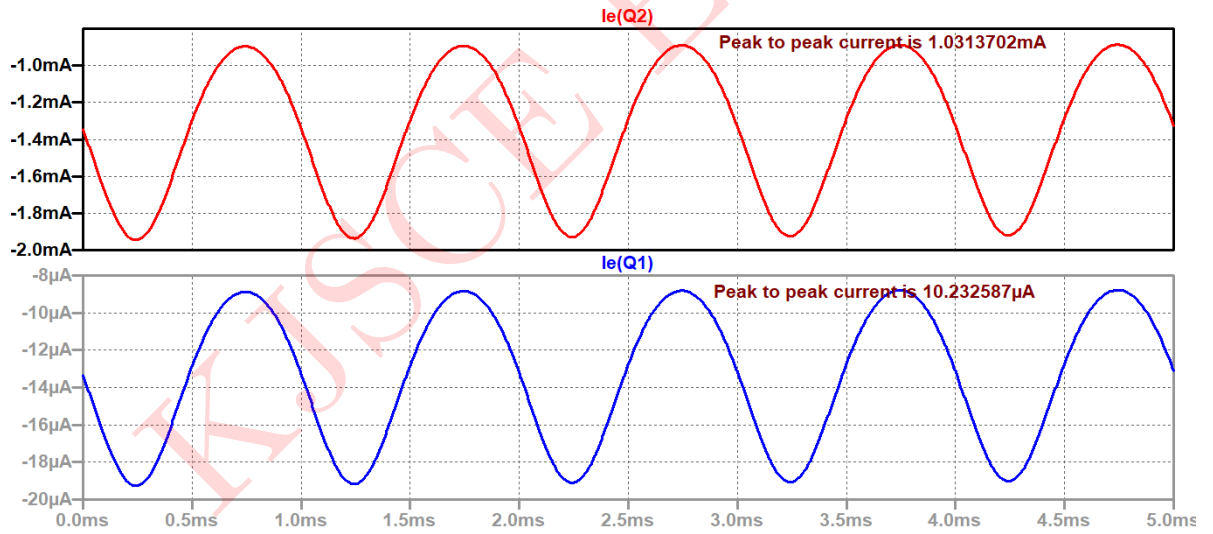


Figure 8: Input and output current waveform for Stage 2

Comparsion between theoretical and simulated values:

Parameter	Theoretical value	Simulated value
I_{B1}	$0.12701\mu A$	$0.13188\mu A$
I_{C1}	$0.0127mA$	$0.013189mA$
I_{E1}	$0.01283mA$	$0.01392mA$
I_{B2}	$0.01283mA$	$0.01332mA$
I_{E2}	$1.2955mA$	$1.3454mA$
V_{E2}	$1.9433V$	$2.0180V$
V_{C2}	$10.7671V$	$10.5607V$
Voltage gain of stage 1: A_{V1}	0.4950	0.5
Voltage gain of stage 2: A_{V2}	162.81	170.695
Overall gain: A_{Vt}	80.591	85.3475
Current gain of Stage 1: A_{i1}	100	100.8013
Current gain of Stage 2: A_{i2}	100	100.7926
Darlington pair gain: A_{id}	10000	10160.025
Input impedance of Stage 1	90.645 k Ω	–
Output impedance of Stage 2	0.0508 k Ω	–
Output voltage	$-1.6118V$	-1.7069

Table 1: Numerical 1