

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Design of single-stage Amplifier

Design 1: Design a single stage RC coupled BJT amplifier for following specifications: $V_o = 3\text{ V}$, $V_{CC} = 18\text{ V}$, $f_L \leq 20\text{ Hz}$, $S \leq 10$, $|A_V| \geq 180$
Calculate A_V , Z_i & Z_o of the amplifier designed.

Solution:

Step 1: Data

$V_o = 3\text{ V}$, $V_{CC} = 18\text{ V}$, $f_L \leq 20\text{ Hz}$, $S \leq 10$, $|A_V| \geq 180$

Step 2: Selection of transistor

Transistor selected is BC 147A with following specifications:

$h_{FE(max)} = 220$, $h_{ie} = 2.7\text{ k}\Omega$, $h_{fe(min)} = 125$

Step 3: Selection of biasing network

Voltage divider biasing network is selected to keep Q point independent of variation in β and temperature.

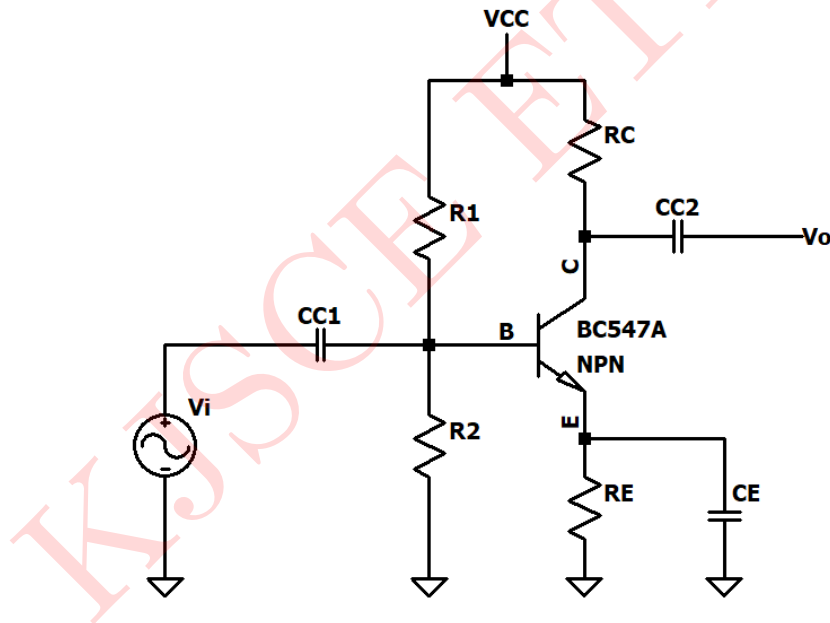


Figure 1: Circuit 1

Step 4: Selection of R_C

$$|A_V| = \frac{h_{fe(min)} R_C}{h_{ie}}$$

$$180 = \frac{125 \times R_C}{2.7 \times 10^3} = 3.888\text{ k}\Omega$$

Selecting higher standard value of R_C to increase the gain.

$R_C = 3.19\text{ k}\Omega$, $1/4\text{ W}$

Step 5: Selection of Q point (V_{CE} & I_C)

$$V_{o\ peak} = \sqrt{2}V_o$$

$$V_{o\ peak} = \sqrt{2} \times 3$$

$$V_{o\ peak} = \mathbf{4.24\ V}$$

$$V_{CE} = 1.5 (V_{o\ peak} + V_{CE\ sat})$$

The value is multiplied by 1.5 to take care of saturation voltages, variation in resistance variation is supply voltage and device parameter variation.

$$V_{CE} = 1.5(4.24 + 0.25) = \mathbf{6.735\ V}$$

$$\text{We know, } I_{o\ peak} = \frac{V_{o\ peak}}{R_C}$$

$$I_{o\ peak} = \frac{3 \times \sqrt{2}}{2.7 \times 10^3} = \mathbf{1.571\ mA}$$

$$I_C \geq I_{o\ peak} \text{ (for undistorted output signal)}$$

$$I_C \geq 1.571\ mA = \mathbf{1.6\ mA}$$

Step 6: Selection of R_E

V_{RE} should be 10% of V_{CC}

$$V_{RE} = \frac{V_{CC}}{10}$$

$$V_{RE} = \frac{18}{10} = \mathbf{1.8\ V}$$

$$\text{We know, } R_E = \frac{V_{RE}}{I_E}$$

$$R_E = \frac{1.8}{1.6 \times 10^{-3}} = 1.125\ k\Omega$$

$$\dots (\because I_C \simeq I_E)$$

Selection lower standard value of R_E to improve stability.

$$R_E = \mathbf{1.1\ k\Omega, 1/4\ W}$$

Step 7: Selection of R_1 & R_2

$$S = \frac{1 + h_{FE\ (typ)}}{1 + h_{FE\ (typ)} \left(\frac{R_E}{R_B + R_E} \right)}$$

$$10 = \frac{1 + 220}{1 + 220 \left(\frac{1.1 \times 10^3}{R_B + 1.1 \times 10^3} \right)}$$

$$R_B = \mathbf{10.478\ k\Omega}$$

$$R_B = \frac{R_1 \times R_2}{R_1 + R_2} \quad \dots(1)$$

$$V_B = \frac{V_{CC} \times R_2}{R_1 + R_2} \quad \dots(2)$$

Applying KVL to input B-E loop we get,

$$V_B - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_B = \frac{I_C}{\beta} R_B + V_{BE} + V_{RE}$$

$$V_B = \frac{1.6 \times 10^{-3}}{220} \times 10.478 \times 10^3 + 0.7 + 1.8 = \mathbf{2.576 \text{ V}}$$

$$\frac{V_B}{V_{CC}} = \frac{R_2}{R_1 + R_2} \quad \dots(\text{From 2})$$

$$\frac{R_2}{R_1 + R_2} = 0.1431 \quad \dots(3)$$

Substituting in equation 1,

$$R_3 = R_1 \left(\frac{R_2}{R_1 + R_2} \right)$$

$$10.478 \times 10^3 = R_1 \times 0.1431 = 73.22 \text{ k}\Omega$$

Selecting higher standard value for R_1 , so that the circuit draws minimum current.

$$R_1 = \mathbf{75 \text{ k}\Omega, 1/4 \text{ W}}$$

$$\frac{R_2}{R_1 + R_2} = 0.1431 \quad \dots(\text{From 3})$$

$$\frac{R_2}{75 \times 10^3 + R_2} = 0.1431$$

$$R_2 = 0.1431 R_2 + 10.7325 \times 10^3$$

$$0.8569 R_2 = 10.7325 \times 10^3$$

$$R_2 = \frac{10.7325 \times 10^3}{0.8569} = 12.52 \text{ k}\Omega$$

Selecting lower standard value for R_2 ,

$$R_2 = \mathbf{12 \text{ k}\Omega, 1/4 \text{ W}}$$

Step 8: Selection of coupling capacitors (C_{C1} & C_{C2})

a) C_{C1}

$$C_{C1} = \frac{1}{2\pi R_{eq} f_L}$$

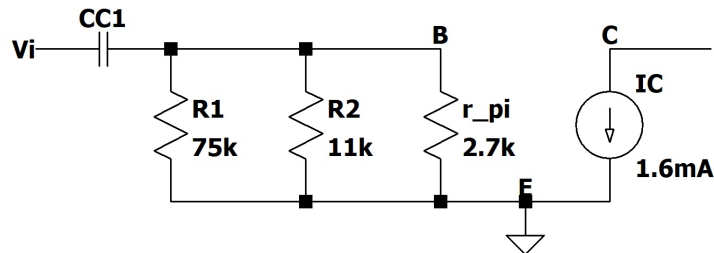


Figure 2: Small Signal Low Frequency Equivalent circuit for C_{C1}

$$R_{eq} = R_1 \parallel R_2 \parallel h_{ie}$$

$$R_{eq} = 75 \times 10^3 \parallel 12 \times 10^3 \parallel 2.7 \times 10^3 = \mathbf{2.14 \text{ k}\Omega}$$

$$C_{C1} = \frac{1}{2\pi \times 2.14 \times 10^3 \times 20} = 3.71 \text{ }\mu\text{F}$$

Selecting higher standard value for C_{C1} ,

$$C_{C1} = \mathbf{4.7 \text{ }\mu\text{F}, 25 \text{ V}}$$

b) C_{C2}

$$C_{C2} = \frac{1}{2\pi R_{eq} f_L}$$

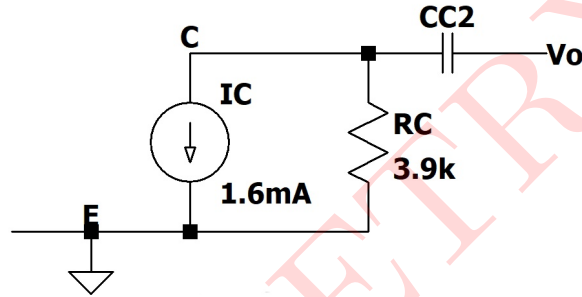


Figure 3: Small Signal Low Frequency Equivalent circuit for C_{C2}

$$R_{eq} = R_C = 3.9 \text{ k}\Omega$$

$$C_{C2} = \frac{1}{2\pi \times 3.9 \times 10^3 \times 20} = 2.04 \text{ }\mu\text{F}$$

Selecting higher standard value for C_{C2} ,

$$C_{C2} = \mathbf{2.2 \text{ }\mu\text{F}, 25 \text{ V}}$$

Step 9: Selection of bypass capacitor C_E

To ensure complete bypass of R_E ,

$$X_{CE} < R_E$$

$$X_{CE} = \frac{R_E}{10}$$

$$X_{CE} = 0.1 \times R_E$$

$$X_{CE} = 0.1 \times 1.1 \times 10^3 = \mathbf{110 \text{ }\Omega}$$

$$C_E = \frac{1}{2\pi f_L X_{CE}}$$

$$C_E = \frac{1}{2\pi f_L \times 0.1 \times R_E}$$

$$C_E = \frac{1}{2\pi \times 20 \times 110} = \mathbf{72.34 \text{ }\mu\text{F}}$$

Selecting higher standard value for C_E ,

$$C_E = \mathbf{75 \text{ }\mu\text{F}, 25 \text{ V}}$$

Step 10: Redraw designed circuit

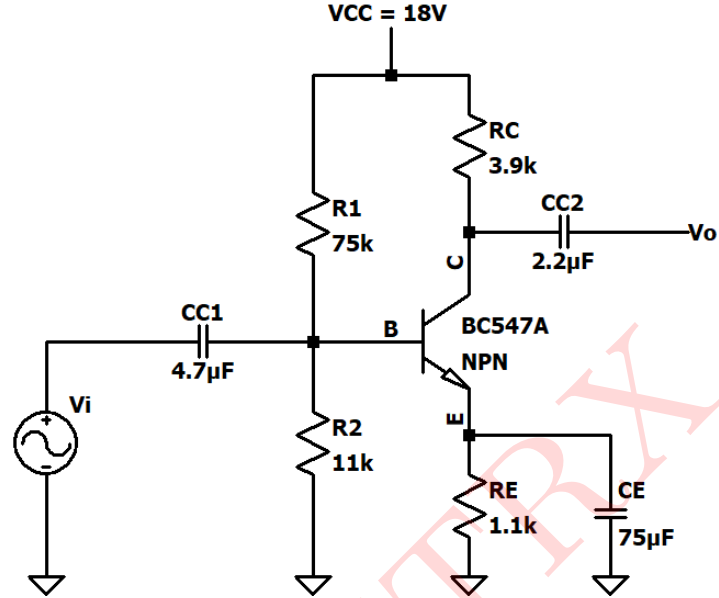


Figure 4: Designed Circuit

AC Analysis:

$$g_m = \frac{I_C}{V_T}$$

$$g_m = \frac{1.6 \times 10^{-3}}{26 \times 10^{-3}} = 61.538 \text{ mA/V}$$

$$r_\pi = h_{ie} = 2.7 \text{ k}\Omega$$

Small signal equivalent circuit:

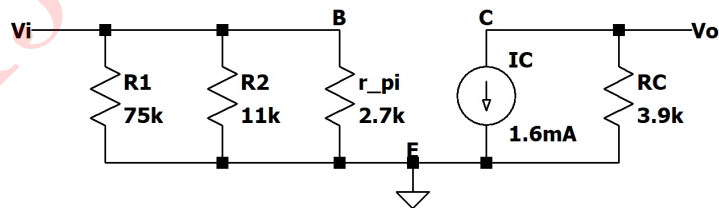


Figure 5: Small Signal Equivalent Circuit

$$A_V = \frac{V_o}{V_i} = \frac{-g_m V_\pi R_C}{V_\pi}$$

$$A_V = -g_m R_C$$

$$A_V = -61.538 \times 10^{-3} \times 3.9 \times 10^3 = -239.9$$

$$Z_i = (R_1 \parallel R_2 \parallel r_\pi)$$

$$Z_i = (75 \times 10^3 \parallel 11 \times 10^3 \parallel 2.7 \times 10^3)$$

$$Z_i = 2.14 \text{ k}\Omega$$

$$Z_o = R_C = 3.9 \text{ k}\Omega$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

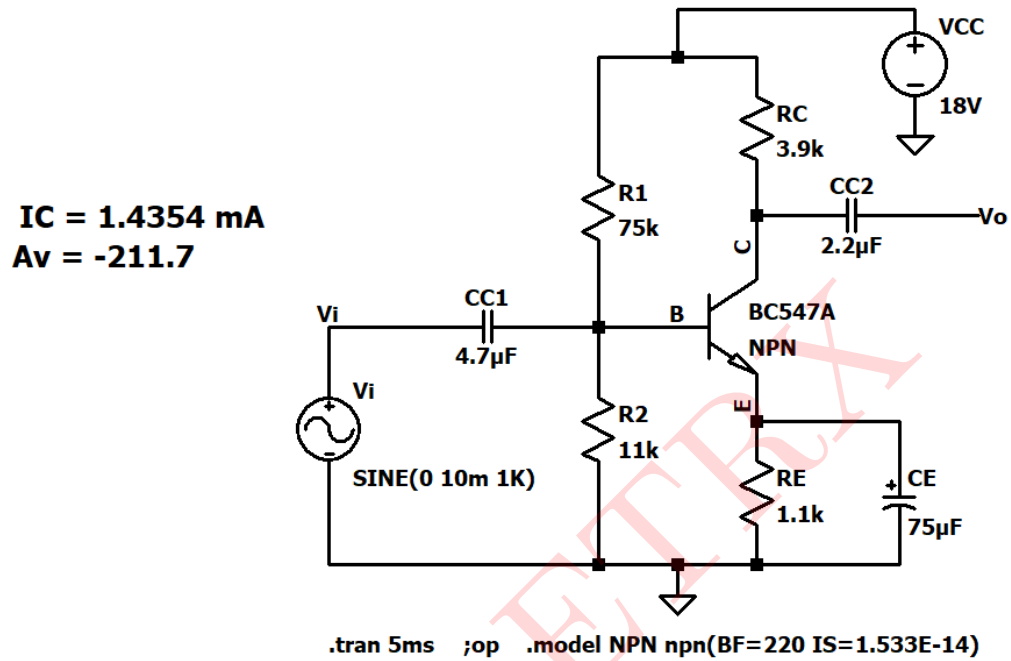


Figure 6: Circuit Schematic 1: Results

The input and output waveforms are shown in figure 7.

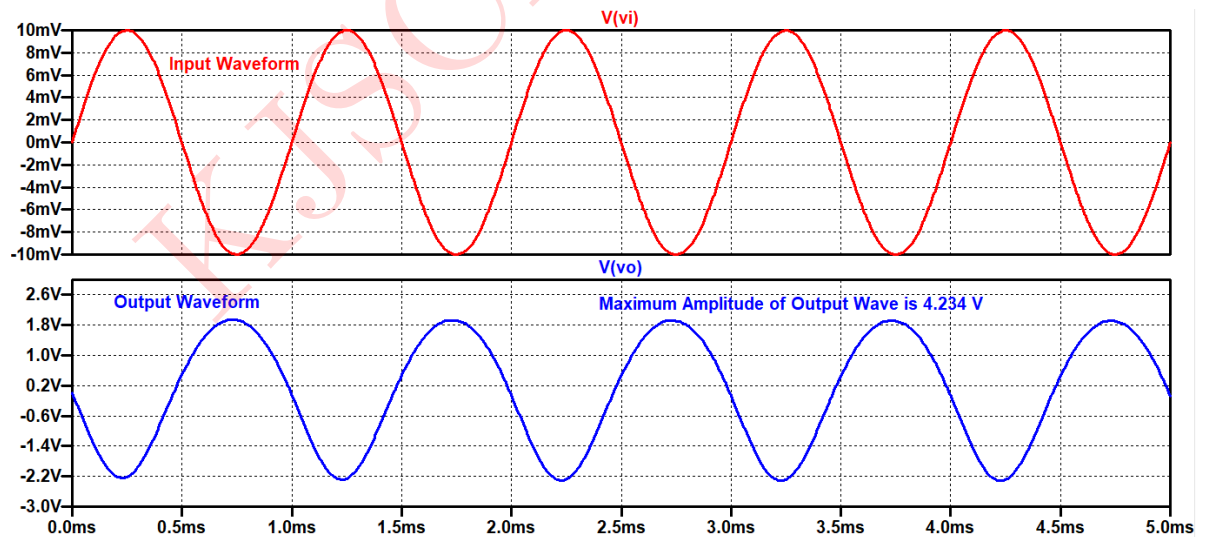


Figure 7: Input & Output waveforms

Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
Voltage gain A_V	-180	-211.7
I_C	1.6 mA	1.4354 mA

Table 1: Design 1

KJSCE ETRX