

K. J. SOMAIYA COLLEGE OF ENGINEERING
DEPARTMENT OF ELECTRONICS ENGINEERING
ELECTRONIC CIRCUITS
Power Amplifier Circuits

Numerical 1:

In a class AB push-pull amplifier, load $R_L = 10\Omega$, $R_1 = R_2 = 100\Omega$, supply voltage $V_{CC} = 20V$, $V_{EE} = -20V$, AC input voltage is 18V peak, frequency is 1000Hz. Calculate the efficiency of the circuit.

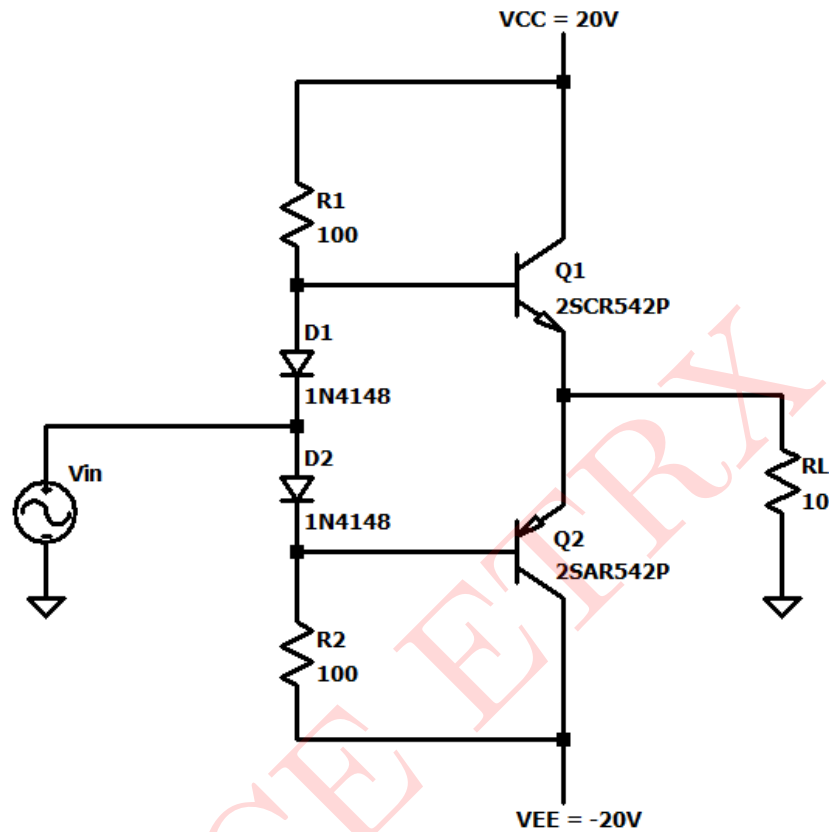


Figure 1: Circuit 1

Solution:

$$V_m = 18V$$

$$\therefore P_{out(ac)} = \frac{V_m^2}{2R_L}$$

$$\therefore P_{out(ac)} = \frac{18V^2}{2 \times 10\Omega} = \mathbf{16.2W}$$

$$I_m = \frac{V_m}{R_L}$$

$$I_m = \frac{18V}{10\Omega} = \mathbf{1.8A}$$

$$P_{in(dc)} = \frac{2(V_{CC})(I_m)}{\pi}$$

$$P_{in(dc)} = \frac{2 \times 20V \times 1.8A}{\pi} = \mathbf{22.929W}$$

$$\text{Efficiency } (\eta) = \frac{P(ac)}{P(dc)}$$

$$\therefore \eta = \frac{16.2W}{22.929W} = 0.7065$$

$$\therefore \text{Efficiency } (\% \eta) = 70.65\%$$

SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows:

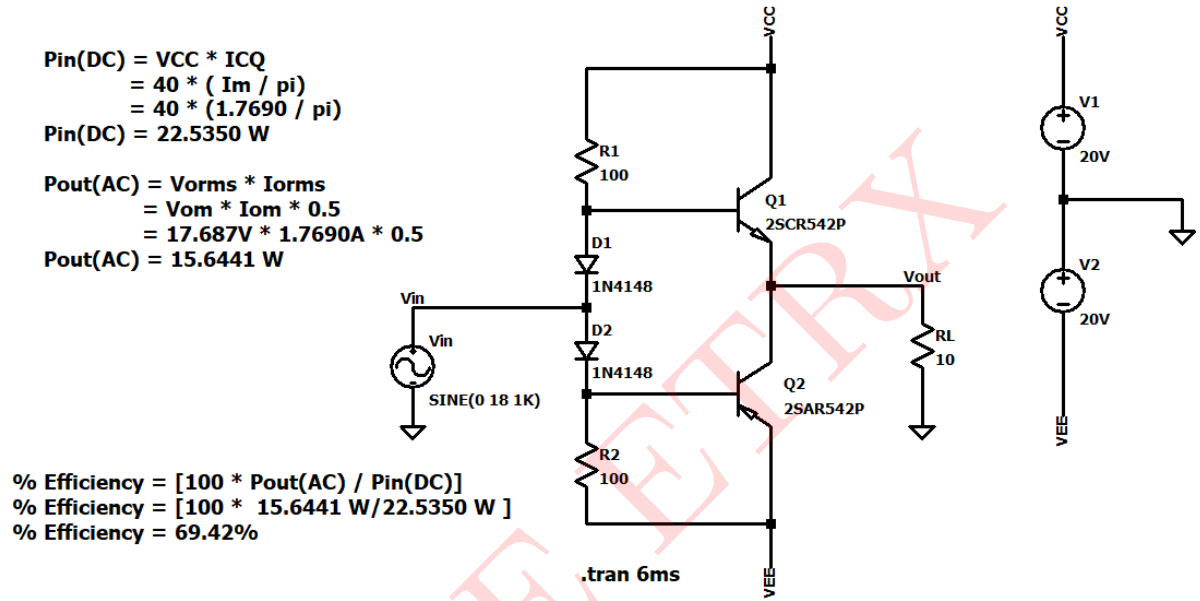


Figure 2: Circuit Schematic

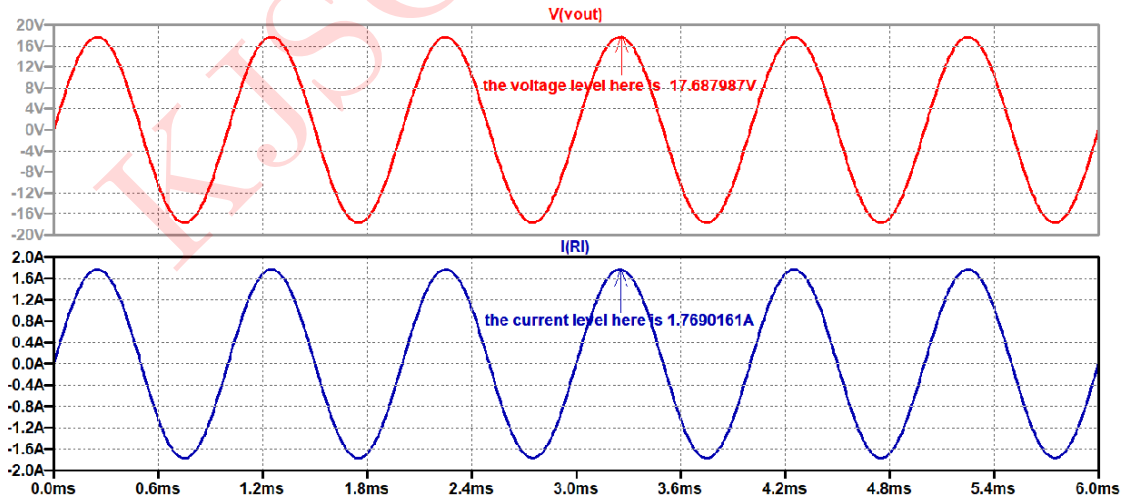


Figure 3: Output voltage and current waveform

Comparison between theoretical and simulated values:

Parameters	Theoretical values	Simulated values
Input DC power	22.929W	22.5350W
Output AC power	16.2W	15.6441W
Efficiency	70.65%	69.42%

Table 1: Numerical 1

KJSCE ETRX