

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Low & High Frequency Response of Single-Stage Amplifier**

**Numerical 1:**

For the circuit shown in figure 1, The transistor parameters are  $\beta = 100$ ,  $V_{BE_{ON}} = 0.7V$ .

a) Calculate Lower corner frequency b) Determine mid-band voltage gain.

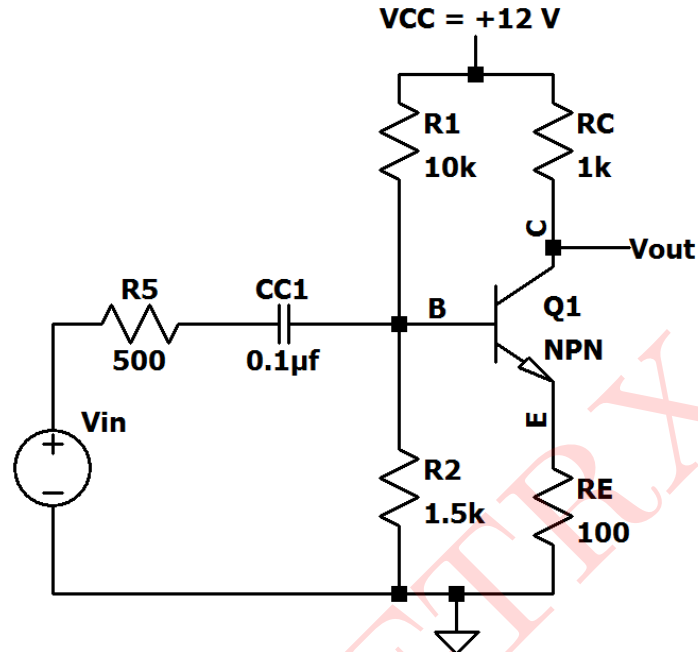


Figure 1: Circuit 1

**Solution:**

Above circuit 1 is a common-emitter BJT amplifier

DC Analysis:-

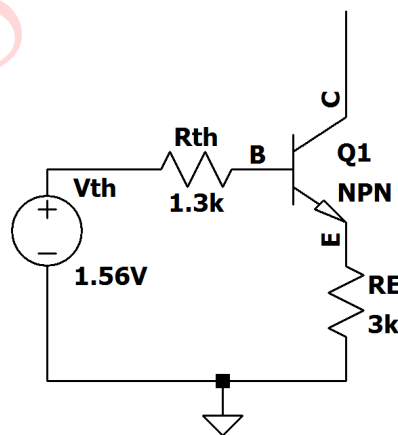


Figure 2: DC Equivalent circuit

$$V_B = V_{th} = \frac{R_2}{R_1 + R_2} \times V_{CC} = \frac{1.5k\Omega}{10k\Omega + 1.5k\Omega} \times 12 = 1.56V$$

$$V_{th} = 1.56V$$

$$R_{th} = R_1 \parallel R_2 = 1.30k\Omega$$

$$R_{th} = 1.30k\Omega$$

Applying KVL to the base-emitter loop:-

$$V_{th} - I_B R_{th} - V_{BE(ON)} - I_E R_E = 0$$

$$I_E = I_C + I_B = (\beta + 1)I_B$$

$$\text{Assume } V_{BE(ON)} = 0.7V$$

$$V_{th} - I_B R_{th} - 0.7V - (\beta + 1)I_B R_E = 0$$

$$I_B = \frac{V_{th} - 0.7V}{R_{th} + ((\beta + 1)R_E)} = \frac{1.56 - 0.7}{1.3k\Omega + (101 \times 0.1k\Omega)} = 75.43\mu A$$

$$I_B = 75.43\mu A$$

$$I_C = \beta I_B = 100 \times 75.43\mu A = 7.5mA$$

$$I_C = 7.5mA$$

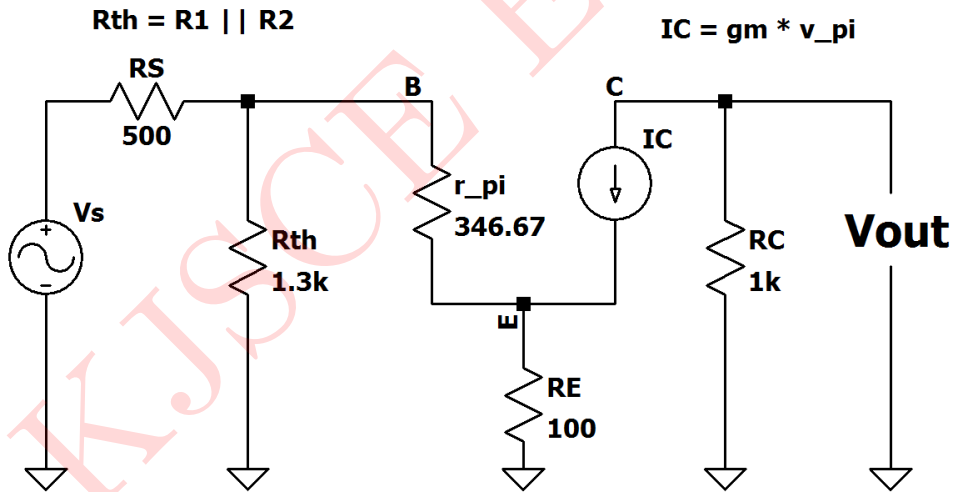


Figure 3: Small Signal Equivalent Circuit

Small-Signal parameters:-

$$g_m = \frac{I_C}{V_T} = \frac{7.5mA}{26mV} = 288.46 \frac{mA}{V}$$

$$g_m = 288.46 \frac{mA}{V}$$

$$r_\pi = \frac{V_T}{I_B} = \frac{26mV}{75.43\mu A} = 346.67\Omega$$

$$r_\pi = 346.67\Omega$$

Applying KCL at the collector terminal:-

$$g_m V_\pi + \frac{V_{out}}{R_C} = 0$$

$$V_\pi = -\frac{V_{out}}{g_m R_C} \quad \text{.....(1)}$$

Applying KCL at emitter node,

$$\left( \frac{V_\pi}{r_\pi} + g_m V_\pi \right) R_E = \text{Voltage drop on } R_E$$

$$\left[ \frac{-V_{out}}{g_m R_C} \times \frac{1}{r_\pi} + g_m \left( \frac{-V_{out}}{g_m R_C} \right) \right] R_E = \text{Voltage drop on } R_E \quad \text{.....(2)}$$

Applying KVL at the base-emitter loop:-

$$V_{in} = V_\pi + \text{Voltage drop on } R_E$$

From (1) & (2)

$$V_{in} = \frac{-V_{out}}{g_m R_C} - \frac{V_{out}}{g_m r_\pi R_C} R_E - \frac{V_{out}}{R_C} R_E$$

$$V_{in} = \frac{-V_{out}}{g_m R_C} - \frac{V_{out}}{\beta R_C} R_E - \frac{V_{out}}{R_C} R_E \quad [\because g_m R_\pi = \beta]$$

$$V_{in} = \frac{-V_{out}\beta + g_m R_E V_{out} + \beta g_m R_E V_{out}}{\beta(g_m R_C)}$$

$$\frac{V_{out}}{V_{in}} = \frac{-\beta g_m R_C}{\beta + (\beta + 1)g_m R_E}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{-R_C}{\frac{1}{g_m} + \left( \frac{\beta + 1}{\beta} \right) R_E}$$

$$A_V = \frac{V_{out}}{V_{in}} = \frac{-1k\Omega}{\frac{1}{0.28846} + \left( \frac{101}{100} \right) \times 100} = -9.57$$

$$\mathbf{A_V = -9.57}$$

$$A_{V_{mid}} \text{ with } R_S = \frac{V_{out}}{V_S} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_S}$$

Current through base =  $I_B$ , Current through emitter =  $I_E = (\beta + 1)I_B$

$$Z_i = R_{th} \parallel [r_\pi + (\beta + 1)R_E]$$

$$\frac{V_{in}}{V_S} = \frac{Z_i}{Z_i + R_S}$$

$$Z_i = 1300 \parallel [346.67 + (10100)] = 1300 \parallel 10446.67 = 1.16k\Omega$$

$$\mathbf{Z_i = 1.16k\Omega}$$

$$\frac{V_{in}}{V_S} = \frac{1160}{1160 + 500} = 0.6987$$

$$\frac{V_{in}}{V_S} = \mathbf{0.6987}$$

$$A_{V_{mid}} \text{ with } R_S = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_S} = -9.57 \times 0.6987 = -6.686$$

$$A_{V_{mid}} \text{ with } R_S = \mathbf{-6.686}$$

$$A_{V_{mid}} \text{ in dB} = 20 \log_{10}(6.686) = 16.5 \text{ dB}$$

$$A_{V_{mid}} \text{ in dB} = \mathbf{16.5 \text{ dB}}$$

**Lower cut-off frequency analysis:-**

Due to  $C_{C1}$  alone:-

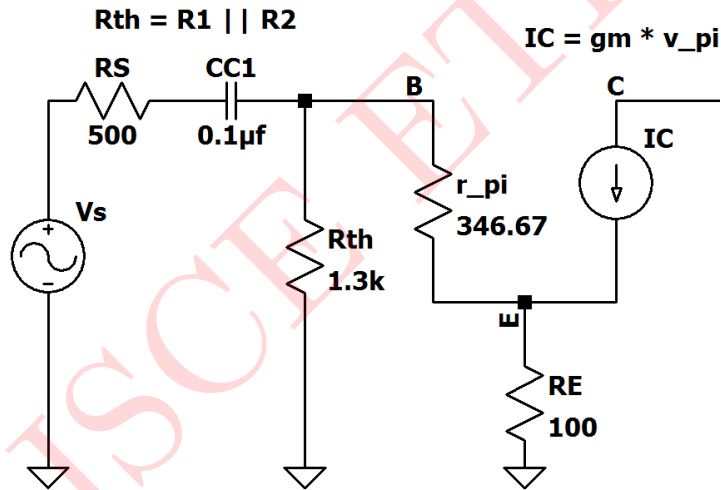


Figure 4: Small Signal low frequency equivalent circuit for  $C_{C1}$

To find  $R_{eq}$

$$R_{eq} = R_S + R_i$$

$$R_i = R_{th} || (r_{\pi} + (\beta + 1)R_E)$$

$$R_i = R_{eq} = 1.16 \text{ k}\Omega$$

$$f_{L_{CC1}} = \frac{1}{2\pi \times C_{C1} \times R_{eq}} = \frac{1}{2\pi \times 0.1 \times 10^{-6} \times 1.66 \times 10^3} = 958.76 \text{ Hz}$$

Since we have only one capacitor, Overall cut-off frequency  $f_L$  will be:-

$$\mathbf{f_L = f_{L_{CC1}} = 958.76 \text{ Hz}}$$

### SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

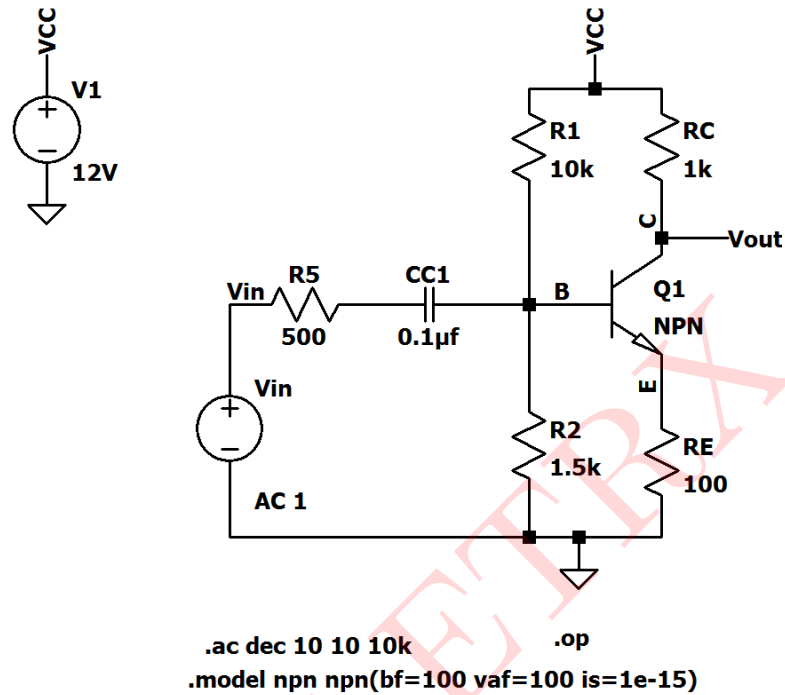


Figure 5: Circuit Schematic 1

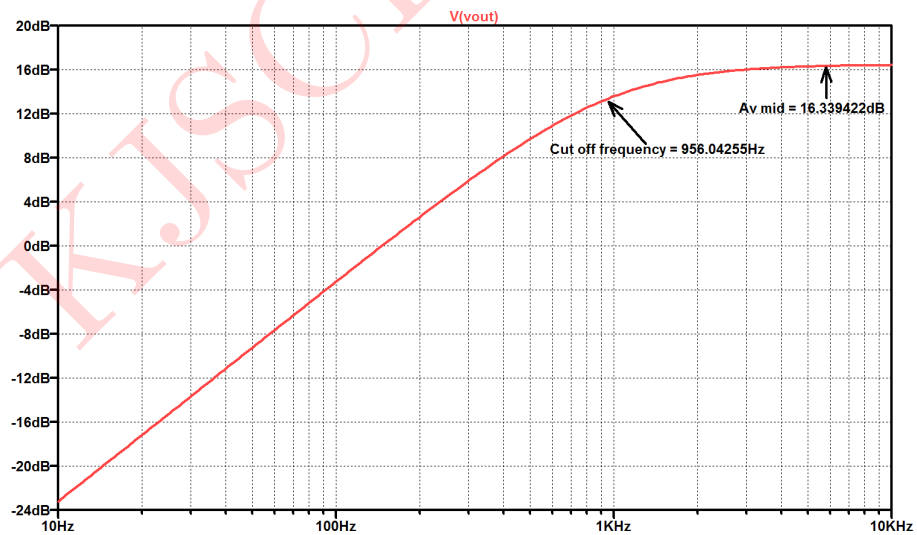


Figure 6: Low frequency response

**Comparison of Theoretical and Simulated Values:**

Parameters	Theoretical	Simulated
$I_C$	$7.5mA$	$7.1mA$
$A_{V_{mid}}(dB)$	16.5	16.34
Overall Cut-off frequency $f_L$	$958.76Hz$	$956.04Hz$

Table 1: Numerical 1

KJSCE ETRX

**Numerical 2:**

For the circuit shown in figure 7, a) Determine  $V_{GS}$ ,  $I_D$  b) Find  $g_{m_o}$ ,  $g_m$  c) Calculate mid-band gain( $A_V$ ) d) Determine  $Z_i$  e) Calculate  $A_{V_S}$  f) Determine  $f_{L_{CC1}}$ ,  $f_{L_{CC2}}$ ,  $f_{L_S}$  g) Determine cut-off frequency

Given:  $I_{DSS} = 6mA$ ,  $V_P = -6V$ ,  $r_d = 100k\Omega$

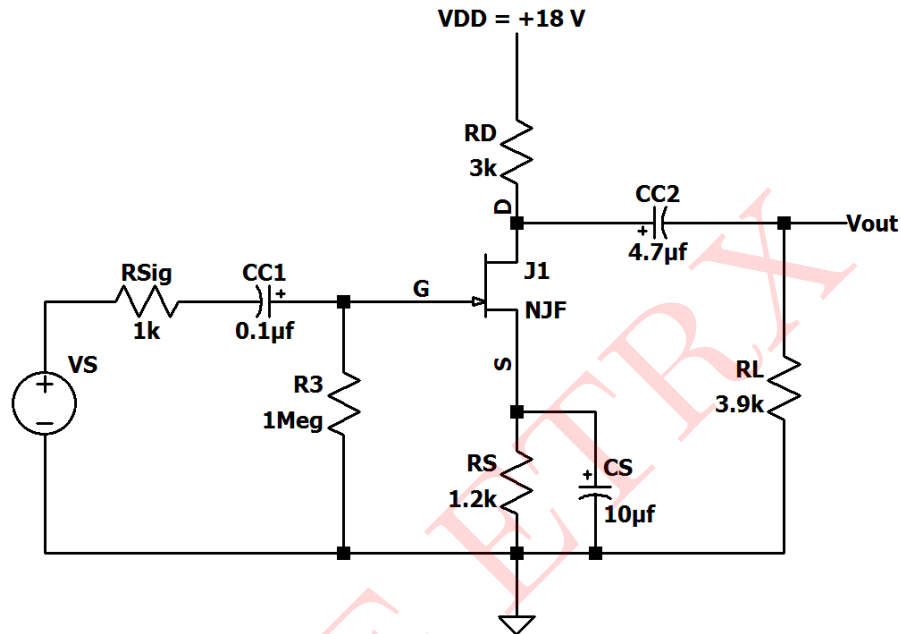


Figure 7: Circuit 2

**Solution:**

DC Analysis:-

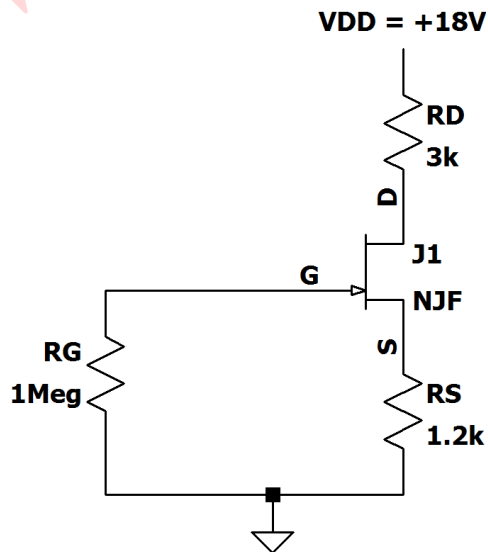


Figure 8: DC Equivalent circuit

Applying KVL to the Gate-Source loop:-

$$V_{GS} = -I_D R_S$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = -6mA \left( 1 + \frac{V_{GS}}{6} \right)^2 \times 1.2k\Omega$$

$$V_{GS} = -7.2 \left( 1 + \frac{V_{GS}}{3} + \frac{V_{GS}^2}{36} \right)^2$$

$$V_{GS} = -7.2 - 0.2V_{GS}^2 - 2.4V_{GS}$$

$$0.2V_{GS}^2 + 3.4V_{GS} + 7.2 = 0$$

Solving above quadratic equation, we get

$$V_{GS} = -2.479V$$

or

$$V_{GS} = -14.52V, \text{ We reject this value, as } (V_{GS} > V_P)$$

$$\therefore V_{GS} = -2.479V$$

$$I_D = -\frac{V_{GS}}{R_S} = \frac{2.479V}{1.2k\Omega} = 2.065mA$$

$$I_D = 2.065mA$$

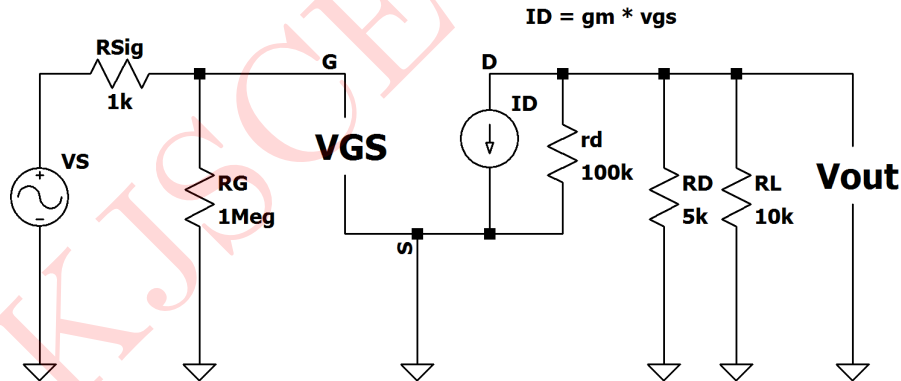


Figure 9: Small Signal Equivalent Circuit

Small-Signal parameters:-

$$g_{m_o} = \left| \frac{2I_{DSS}}{V_P} \right| = \frac{2 \times 6}{6} = 2mA/V$$

$$g_m = g_{m_o} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = 2 \times \left( 1 - \frac{2.479}{6} \right)^2 = 1.1736 \text{ mA/V}$$

$$g_m = 1.1736 \text{ mA/V}$$

$$r_d = 100k\Omega \quad (\text{Given})$$



Applying KCL at the drain terminal:-

$$g_m V_{GS} + \frac{V_{out}}{r_d} + \frac{V_{out}}{R_D} + \frac{V_{out}}{R_L} = 0$$

$$V_{GS} = -\frac{V_{out}}{g_m} \left( \frac{1}{r_d} + \frac{1}{R_D} + \frac{1}{R_L} \right)$$

$$V_{GS} = V_{in}$$

$$A_{V_{mid}} = \frac{V_{out}}{V_{in}} = -g_m(r_d \parallel R_D \parallel R_L)$$

$$A_{V_{mid}} = -1.1736 \text{ mA/V} (100k \parallel 3k \parallel 3.9k) = -1.956$$

$$\mathbf{A_{V_{mid}} = -1.956}$$

Input Impedance:-

$$Z_i = R_{sig} + R_G$$

$$Z_i = 1k\Omega + 1M\Omega = 1001k\Omega$$

$$\mathbf{Z_i = 1001k\Omega}$$

$$A_{V_{mid}} \text{ with } R_{sig} = \frac{V_{out}}{V_S} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_S}$$

$$\frac{V_{in}}{V_S} = \frac{R_G}{R_G + R_{sig}} = \frac{1M\Omega}{1001k\Omega} = 0.999$$

$$A_{V_{mid}} \text{ with } R_{sig} = 0.99 \times -1.956 = -1.954$$

$$\mathbf{A_{V_{mid}} \text{ with } R_{sig} = -1.954}$$

$$A_{V_{mid}} \text{ in dB} = 20 \log_{10}(1.954) = 5.818 \text{ dB}$$

$$\mathbf{A_{V_{mid}} \text{ in dB} = 5.818 \text{ dB}}$$

Due to  $C_{C1}$  alone:-

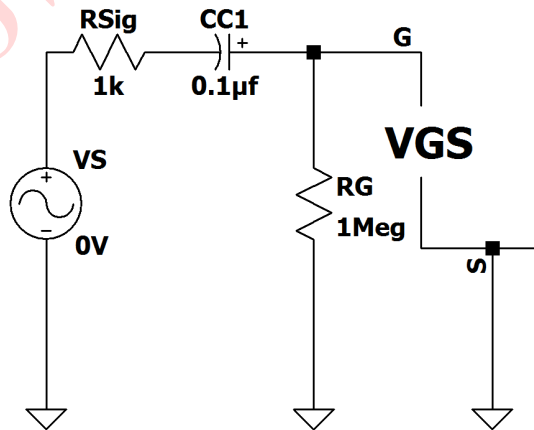


Figure 10: Small Signal low frequency equivalent circuit for  $C_{C1}$

$$R_{eq} = R_{sig} + R_G = 1k\Omega + 1M\Omega = 1001k\Omega$$

$$f_{L_{CC1}} = \frac{1}{2\pi \times C_{C1} \times R_{eq}} = \frac{1}{2\pi \times 1001 \times 1000 \times 0.1} = 1.589Hz$$

$$f_{L_{CC1}} = 1.589Hz$$

Due to  $C_{C2}$  alone:-

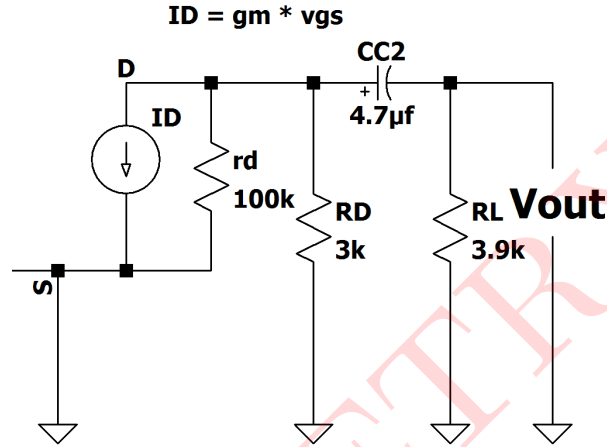


Figure 11: Small Signal low frequency equivalent circuit for  $C_{C2}$

$$R_{eq} = R_D + R_L = (r_d \parallel R_D) + R_L = (100k \parallel 3k) + 3.9k = 6.813k\Omega$$

$$f_{L_{CC2}} = \frac{1}{2\pi \times C_{C2} \times R_{eq}} = \frac{1}{2\pi \times 6.813k \times 4.7} = 4.97Hz$$

$$f_{L_{CC2}} = 4.97Hz$$

Due to  $C_S$  alone:-

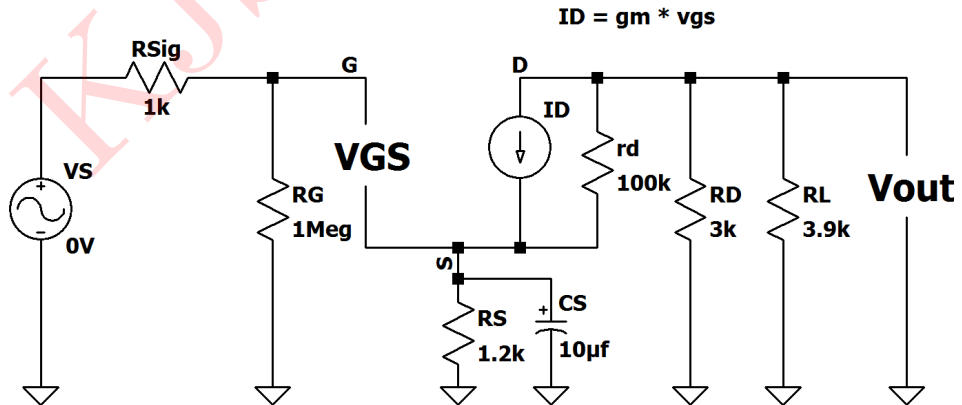


Figure 12: Small Signal low frequency equivalent circuit for  $C_S$

Since  $V_S = 0$ ; and also gate and source are open circuit  $\rightarrow \therefore R_{sig}$  &  $R_G$  are ignored

$$R_{eq} = R_S \parallel \left[ \frac{r_d + (R_D \parallel R_L)}{1 + g_m r_d} \right] = 1.2k \parallel \left[ \frac{100k + 1.695k}{1 + 117.36} \right] = 1.2k \parallel 0.8592k = 500.7\Omega$$

$$f_{L_{CS}} = \frac{1}{2\pi \times C_S \times R_{eq}} = \frac{1}{2\pi \times 10 \times 500.7} = 29.68Hz$$

$$f_{L_S} = 29.68Hz$$

Since,  $f_{L_{CS}} > f_{L_{CC2}} > f_{L_{CC1}}$

$\therefore$  Lower cut-off frequency =  $f_{L_{CS}} = 29.68Hz$

### SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

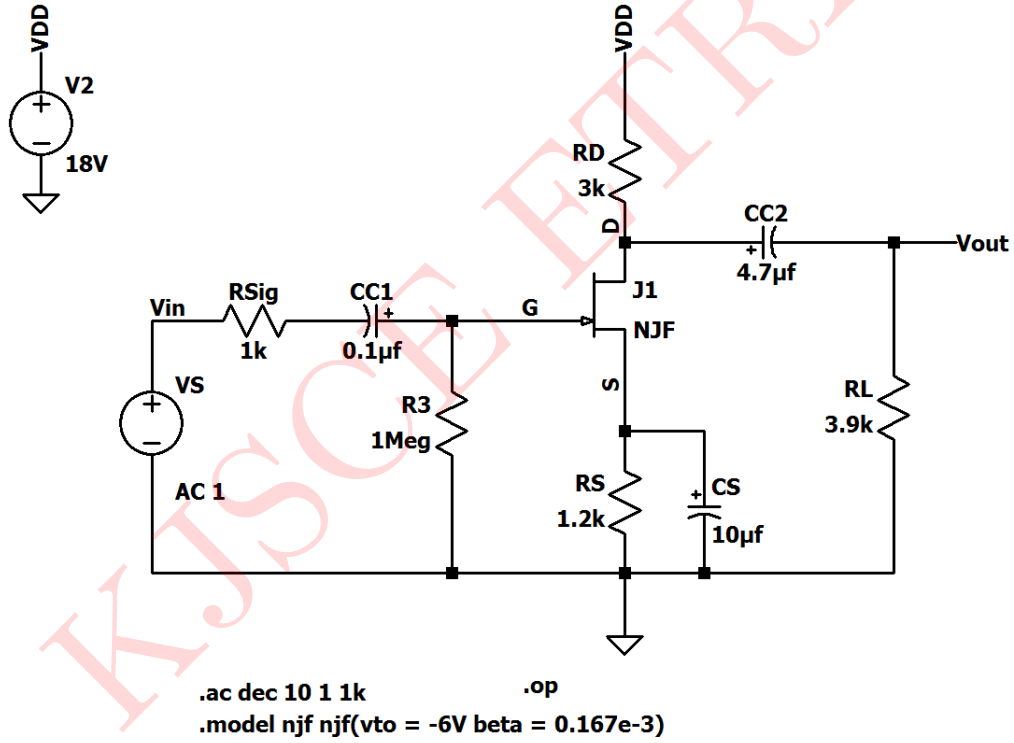


Figure 13: Circuit Schematic 2

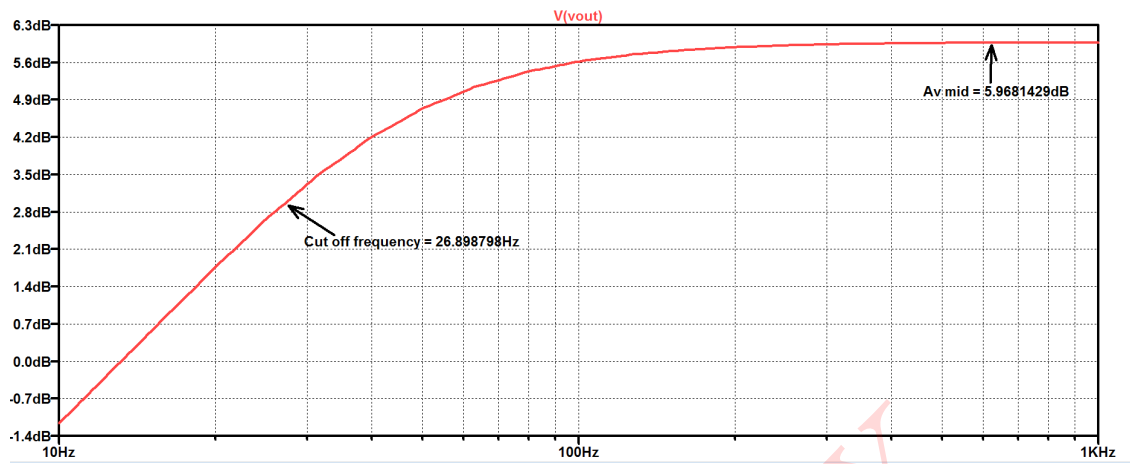


Figure 14: Low frequency response of the circuit

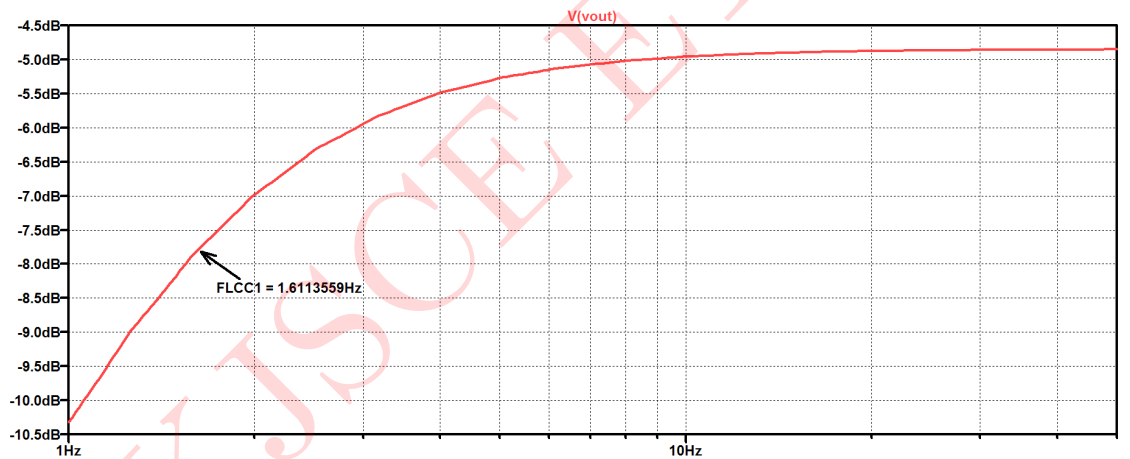


Figure 15: Low frequency response for  $C_1$

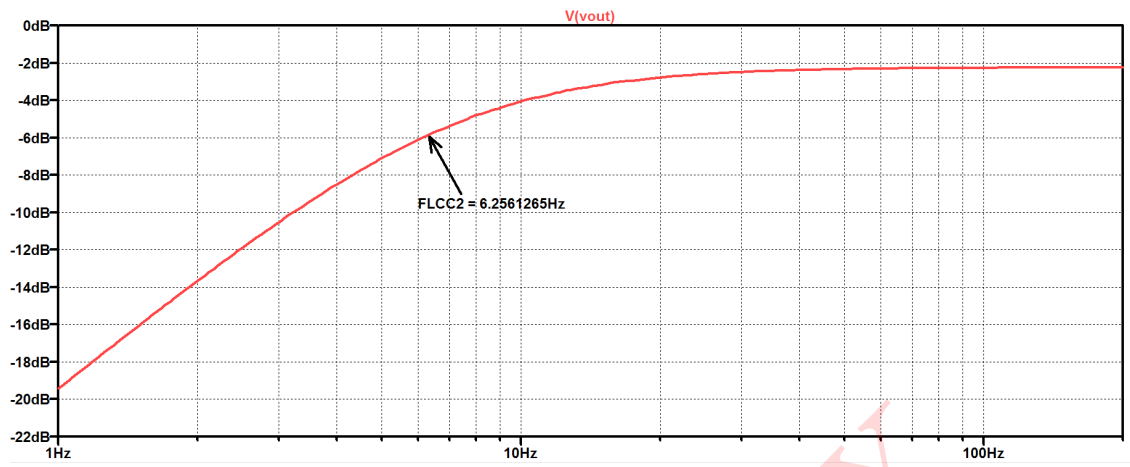


Figure 16: Low frequency response for  $C_{C2}$

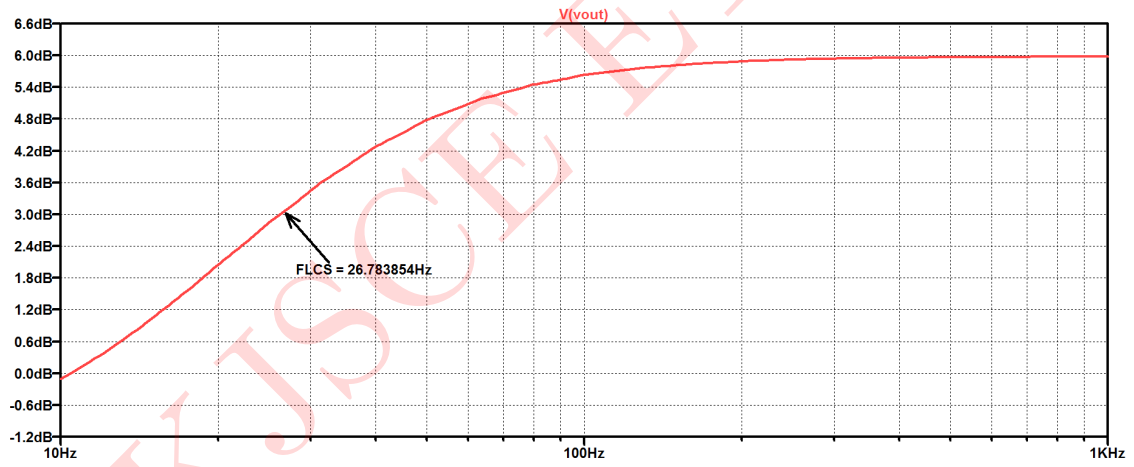


Figure 17: Low frequency response for  $C_S$

**Comparison of Theoretical and Simulated Values:**

Parameters	Theoretical	Simulated
$I_D, V_{GS}$	$2.065mA, -2.479V$	$2.067mA, -2.481V$
Lower cut-off frequency due to $C_{C_1}$	$1.589Hz$	$1.611Hz$
Lower cut-off frequency due to $C_{C_2}$	$4.97Hz$	$6.2Hz$
Lower cut-off frequency due to $C_S$	$29.68Hz$	$26.78Hz$
Overall cut-off frequency $f_L$	$29.68Hz$	$26.86Hz$
Mid-band Voltage gain $A_V$ in $dB$	$5.82dB$	$5.96dB$

Table 2: Numerical 2

### Numerical 3:

For the circuit shown in figure 18, a) Determine  $V_{GS}$ ,  $I_D$  b) Find  $g_{m_o}$ ,  $g_m$  c) Calculate mid-band gain( $A_V$ ) d) Determine  $Z_i$  e) Calculate  $A_{V_S}$  f) Determine  $f_{L_{CC1}}$ ,  $f_{L_{CC2}}$ ,  $f_{L_S}$  g) Determine low cut-off frequency h) Determine high cut-off frequency  
Given:  $I_{DSS} = 6mA$ ,  $V_P = -6V$ ,  $r_d = 100k\Omega$ ,  $C_{wi} = 3pF$ ,  $C_{wo} = 5pF$ ,  $C_{gd} = 4pF$ ,  $C_{gs} = 6pF$  and  $C_{ds} = 1pF$

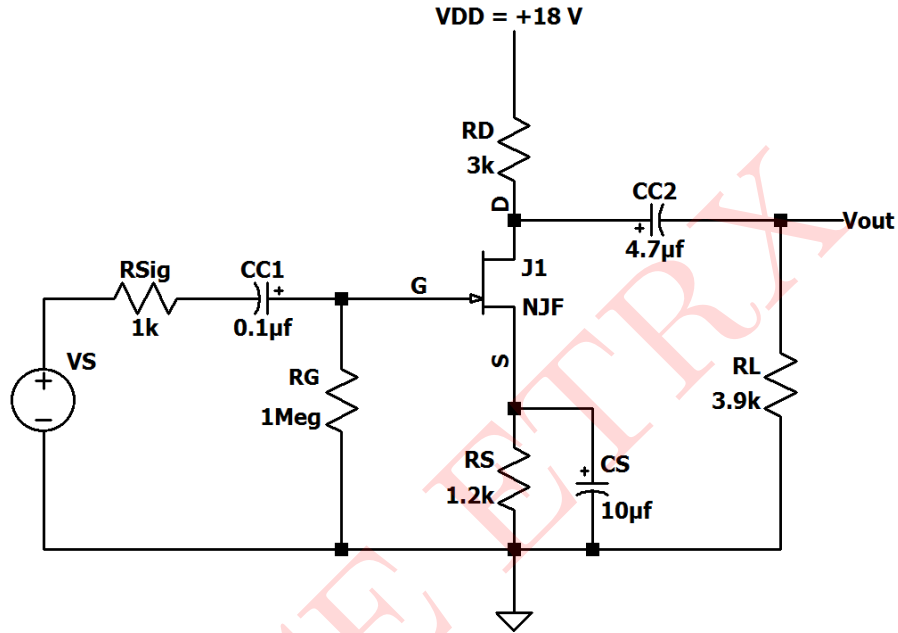


Figure 18: Circuit 3

### Solution:

DC Analysis:-

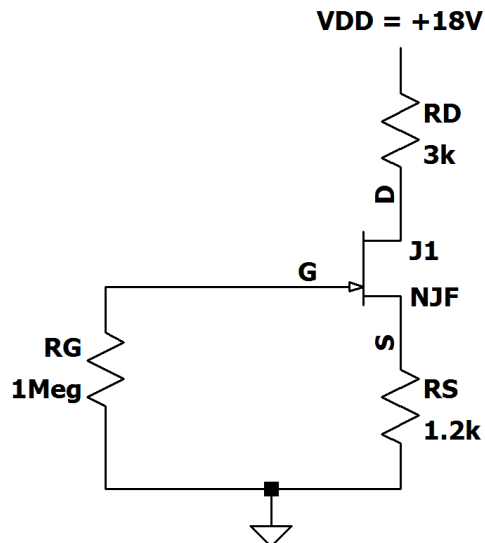


Figure 19: DC Equivalent circuit

Applying KVL to the Gate-Source loop:-

$$V_{GS} = -I_D R_S$$

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = -6mA \left( 1 + \frac{V_{GS}}{6} \right)^2 \times 1.2k\Omega$$

$$V_{GS} = -7.2 \left( 1 + \frac{V_{GS}}{3} + \frac{V_{GS}^2}{36} \right)^2$$

$$V_{GS} = -7.2 - 0.2V_{GS}^2 - 2.4V_{GS}$$

$$0.2V_{GS}^2 + 3.4V_{GS} + 7.2 = 0$$

Solving above quadratic equation, we get

$$V_{GS} = -2.479V$$

or

$$V_{GS} = -14.52V, \text{ We reject this value, as } (V_{GS} > V_P)$$

$$\therefore V_{GS} = -2.479V$$

$$I_D = -\frac{V_{GS}}{R_S} = \frac{2.479V}{1.2k\Omega} = 2.065mA$$

$$I_D = 2.065mA$$

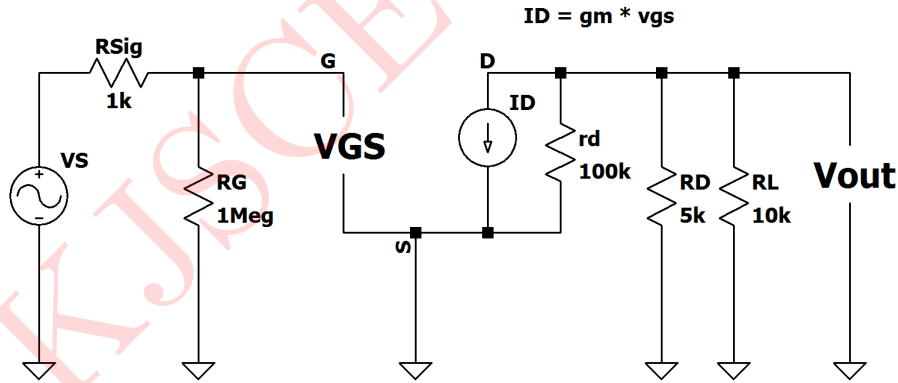


Figure 20: Small Signal Equivalent Circuit

Small-Signal parameters:-

$$g_{m_o} = \left| \frac{2I_{DSS}}{V_P} \right| = \frac{2 \times 6}{6} = 2mA/V$$

$$g_m = g_{m_o} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = 2 \times \left( 1 - \frac{2.479}{6} \right)^2 = 1.1736 mA/V$$

$$g_m = 1.1736 mA/V$$

$$r_d = 100k\Omega \quad (\text{Given})$$



Applying KCL at the drain terminal:-

$$g_m V_{GS} + \frac{V_{out}}{r_d} + \frac{V_{out}}{R_D} + \frac{V_{out}}{R_L} = 0$$

$$V_{GS} = -\frac{V_{out}}{g_m} \left( \frac{1}{r_d} + \frac{1}{R_D} + \frac{1}{R_L} \right)$$

$$V_{GS} = V_{in}$$

$$A_{V_{mid}} = \frac{V_{out}}{V_{in}} = -g_m (r_d \parallel R_D \parallel R_L)$$

$$A_{V_{mid}} = -1.1736 \text{ mA/V} (100k \parallel 3k \parallel 3.9k) = -1.956$$

$$\mathbf{A_{V_{mid}} = -1.956}$$

Input Impedance:-

$$Z_i = R_{sig} + R_G$$

$$Z_i = 1k\Omega + 1M\Omega = 1001k\Omega$$

$$\mathbf{Z_i = 1001k\Omega}$$

$$A_{V_{mid}} \text{ with } R_{sig} = \frac{V_{out}}{V_S} = \frac{V_{out}}{V_{in}} \times \frac{V_{in}}{V_S}$$

$$\frac{V_{in}}{V_S} = \frac{R_G}{R_G + R_{sig}} = \frac{1M\Omega}{1001k\Omega} = 0.999$$

$$A_{V_{mid}} \text{ with } R_{sig} = 0.99 \times -1.956 = -1.954$$

$$\mathbf{A_{V_{mid}} \text{ with } R_{sig} = -1.954}$$

$$A_{V_{mid}} \text{ in dB} = 20 \log_{10}(1.954) = 5.818 \text{ dB}$$

$$\mathbf{A_{V_{mid}} \text{ in dB} = 5.818 \text{ dB}}$$

Due to  $C_{C_1}$  alone:-

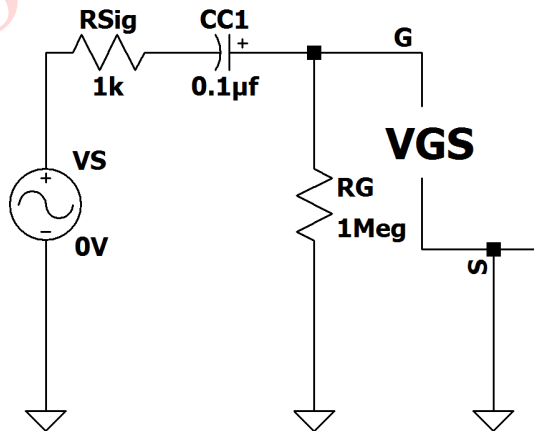


Figure 21: Small Signal low frequency equivalent circuit for  $C_{C_1}$

$$R_{eq} = R_{sig} + R_G = 1k\Omega + 1M\Omega = 1001k\Omega$$

$$f_{L_{CC1}} = \frac{1}{2\pi \times C_{C1} \times R_{eq}} = \frac{1}{2\pi \times 1001 \times 1000 \times 0.1} = 1.589Hz$$

$$f_{L_{CC1}} = 1.589Hz$$

Due to  $C_{C2}$  alone:-

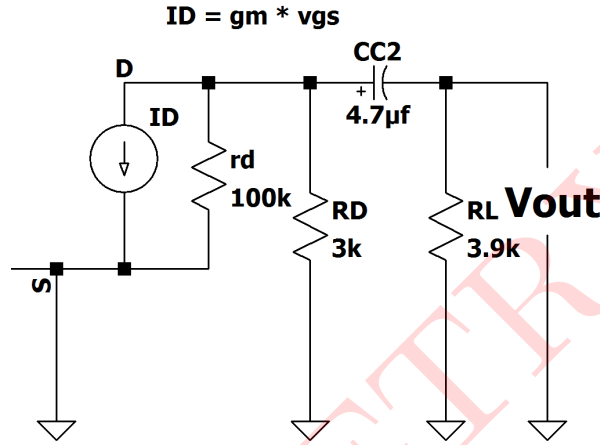


Figure 22: Small Signal low frequency equivalent circuit for  $C_{C2}$

$$R_{eq} = R_D + R_L = (r_d \parallel R_D) + R_L = (100k \parallel 3k) + 3.9k = 6.813k\Omega$$

$$f_{L_{CC2}} = \frac{1}{2\pi \times C_{C2} \times R_{eq}} = \frac{1}{2\pi \times 6.813k \times 4.7} = 4.97Hz$$

$$f_{L_{CC2}} = 4.97Hz$$

Due to  $C_S$  alone:-

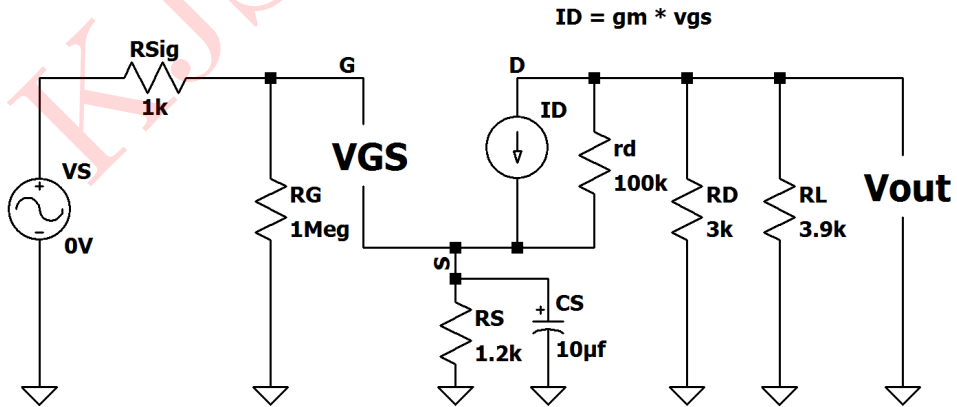


Figure 23: Small Signal low frequency equivalent circuit for  $C_S$

Since  $V_S = 0$ ; and also gate and source are open circuit  $\rightarrow \therefore R_{sig}$  &  $R_G$  are ignored

$$R_{eq} = R_S \parallel \left[ \frac{r_d + (R_D \parallel R_L)}{1 + g_m r_d} \right] = 1.2k \parallel \left[ \frac{100k + 1.695k}{1 + 117.36} \right] = 1.2k \parallel 0.8592k = 500.7\Omega$$

$$f_{L_{CS}} = \frac{1}{2\pi \times C_S \times R_{eq}} = \frac{1}{2\pi \times 10 \times 500.7} = 29.68Hz$$

$$f_{L_S} = 29.68Hz$$

Since,  $f_{L_{CS}} > f_{L_{CC2}} > f_{L_{CC1}}$

$\therefore$  Lower cut-off frequency =  $f_{L_{CS}} = 29.68Hz$

High frequency equivalent circuit:-

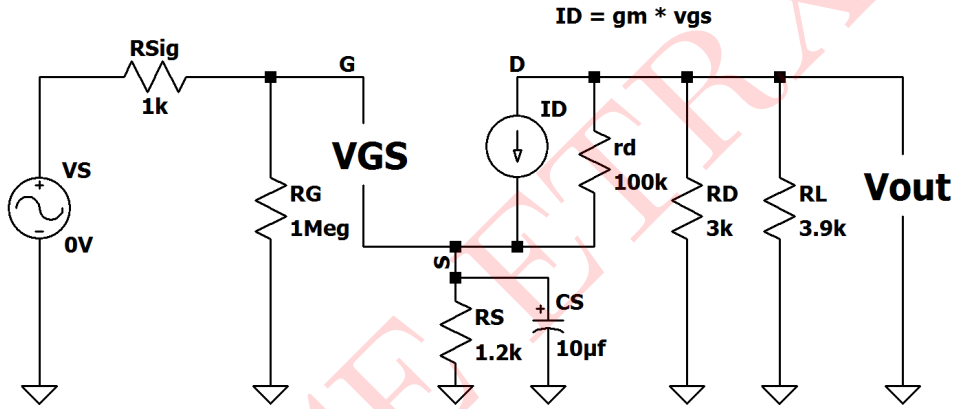


Figure 24: Small Signal high frequency equivalent circuit

$$C_i = C_{gs} + C_{mi} + C_{wi}$$

$$C_{mi} = C_{gd}(1 - A_{V_{mid}}) = 4(1 + 5.82) = 27.28pF$$

$$C_i = 6pF + 27.28pF + 3pF = 36.28pF$$

$$C_o = C_{wo} + C_{mo} + C_{ds}$$

$$C_{mo} = C_{gd} \left( 1 - \frac{1}{A_{V_{mid}}} \right) = 4 \left( 1 - \frac{1}{5.82} \right) = 4.687pF$$

$$C_o = 5pF + 4.687pF + 1pF = 10.687pF$$

For  $f_{H_i}$

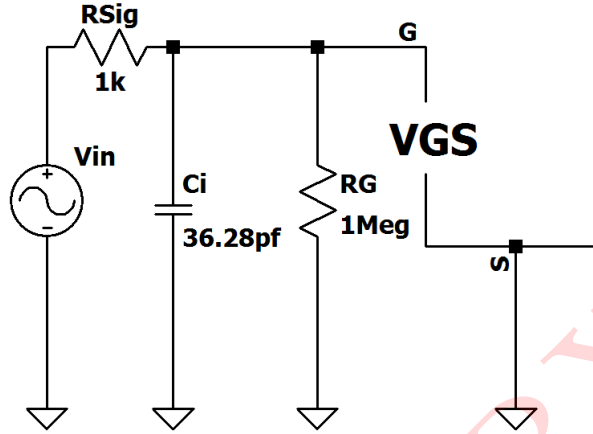


Figure 25: Small Signal equivalent circuit for  $f_{H_i}$

$$R_{eq} = R_{sig} \parallel R_G$$

$$R_{eq} = 1k\Omega \parallel 1M\Omega$$

$$R_{eq} = 999\Omega$$

$$f_{H_i} = \frac{1}{2\pi R_{eq} C_i} = \frac{10^{12}}{2\pi \times 999 \times 36.28} = 4.39MHz$$

$$f_{H_i} = 4.39MHz$$

For  $f_{H_o}$

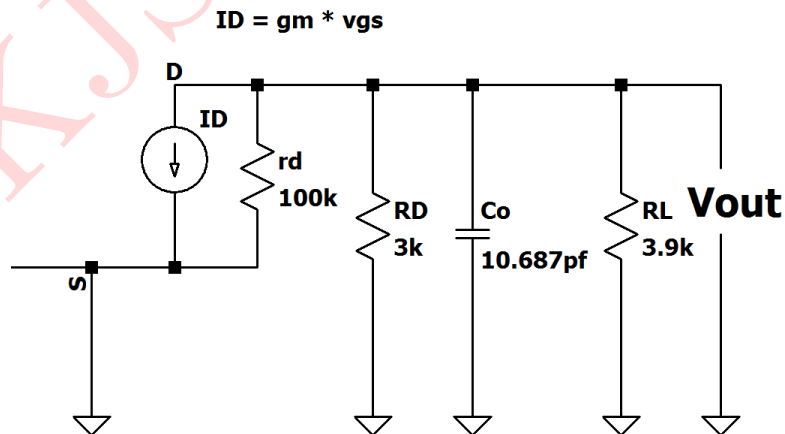


Figure 26: Small Signal equivalent circuit for  $f_{H_o}$

$$R_{eq} = r_d \parallel R_D \parallel R_L$$

$$R_{eq} = 100k\Omega \parallel 3k\Omega \parallel 3.9k\Omega$$

$$R_{eq} = 1.667k\Omega$$

$$f_{H_o} = \frac{1}{2\pi R_{eq} C_o} = \frac{10^{12}}{2\pi \times 1.667 \times 10^3 \times 10.687} = 8.93MHz$$

$$f_{H_o} = 8.93MHz$$

Since,  $f_{H_i} < f_{H_o}$

$\therefore$  Higher cut-off frequency  $f_H = f_{H_i} = 4.39MHz$

### SIMULATED RESULTS:

Above circuit was simulated in LTSpice and results are presented below:

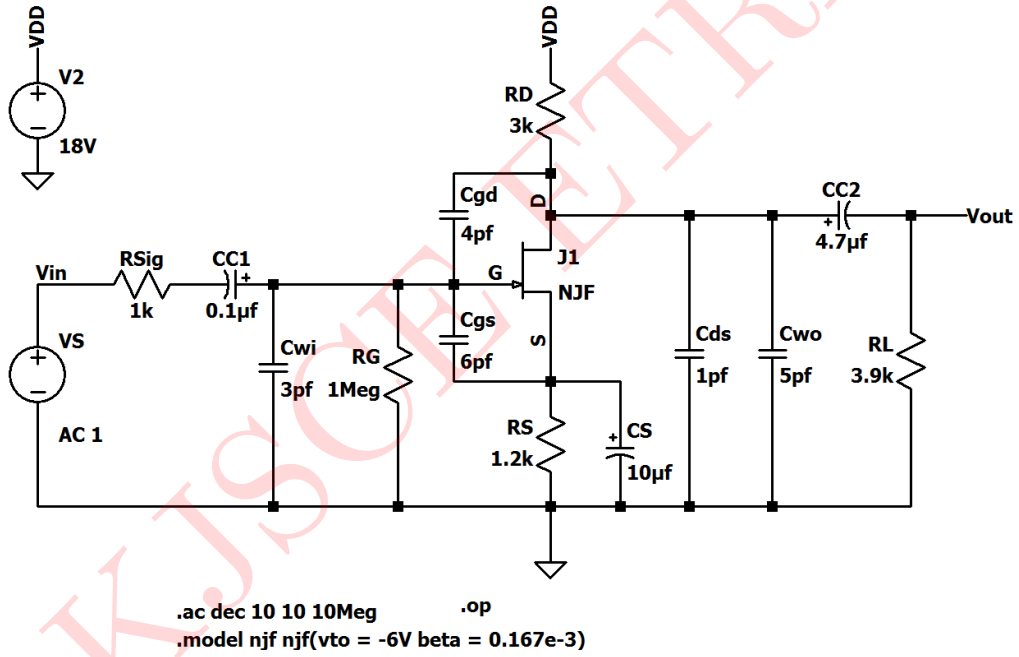


Figure 27: Circuit Schematic 3

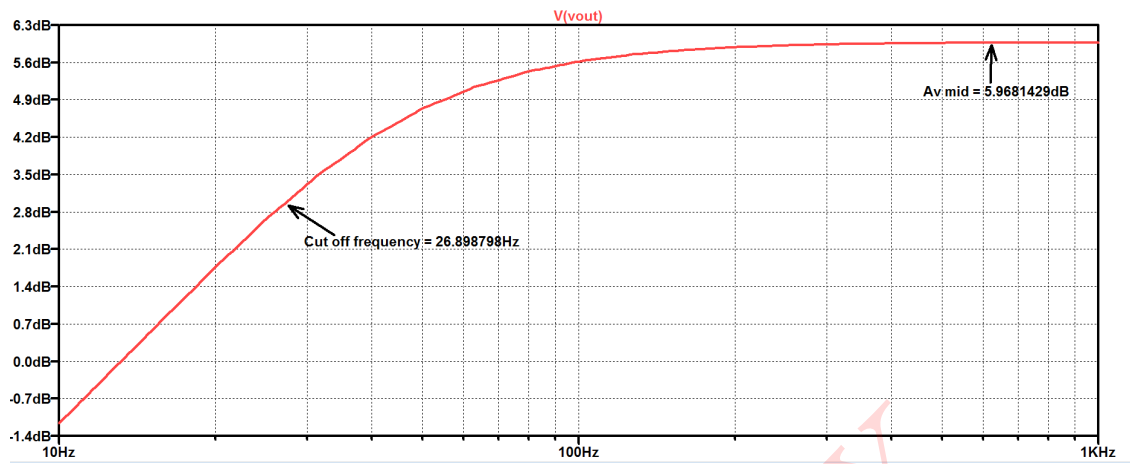


Figure 28: Low frequency response of the circuit

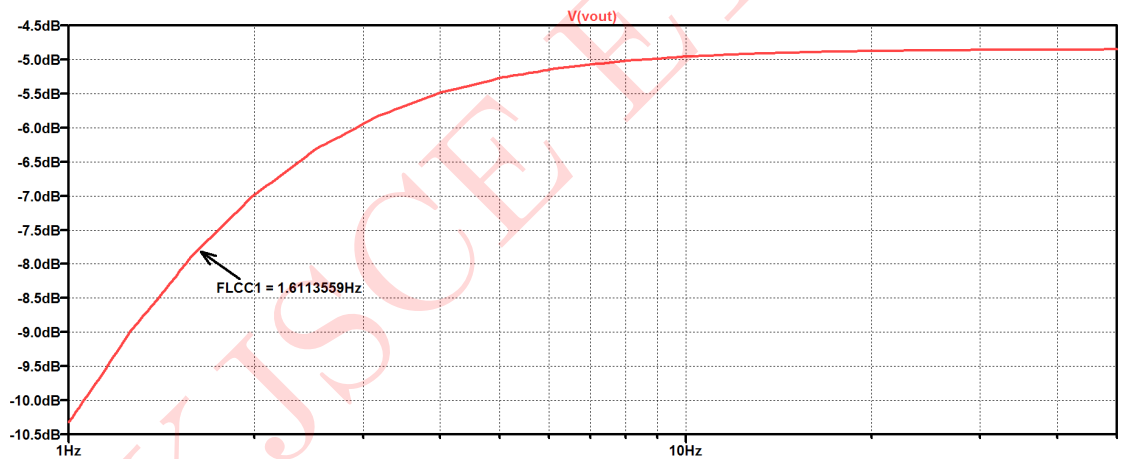


Figure 29: Low frequency response for  $C_{C1}$

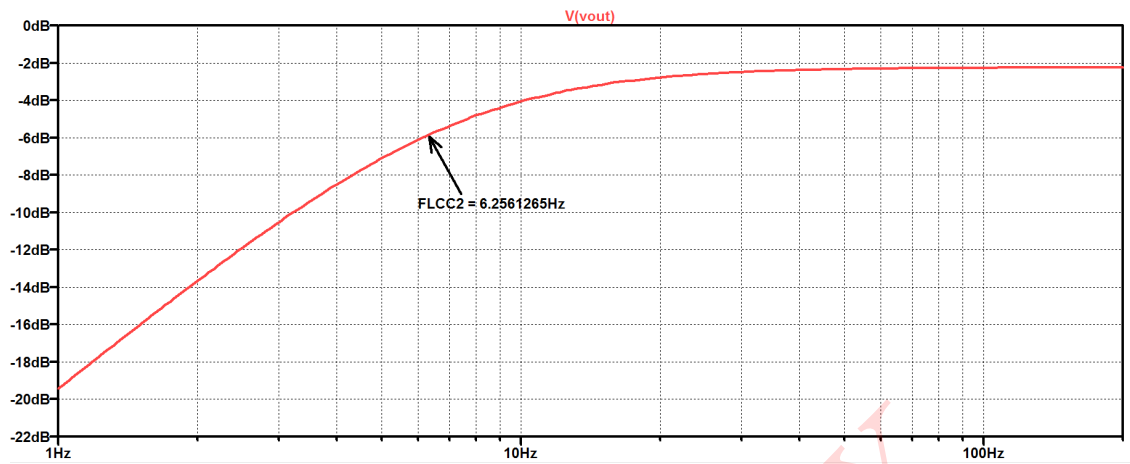


Figure 30: Low frequency response for  $C_{C2}$

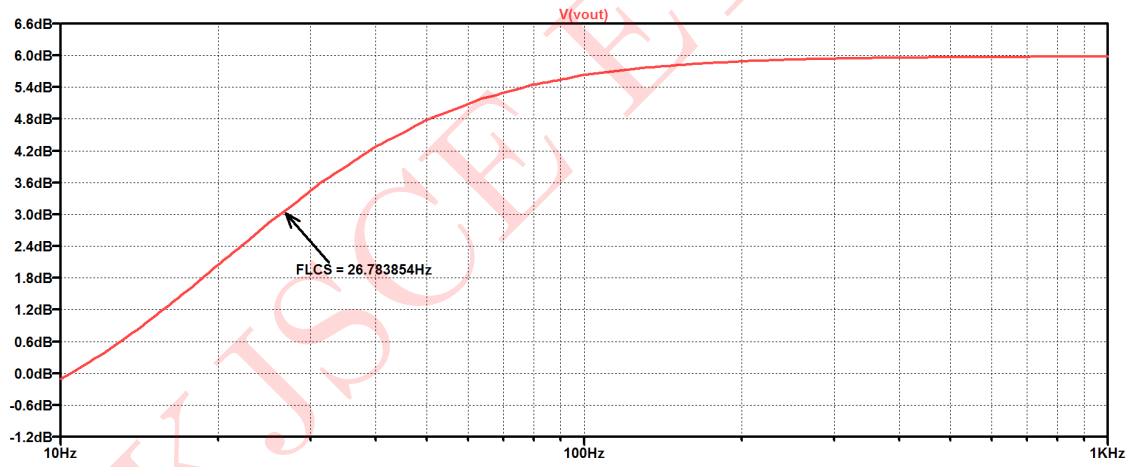


Figure 31: Low frequency response for  $C_S$

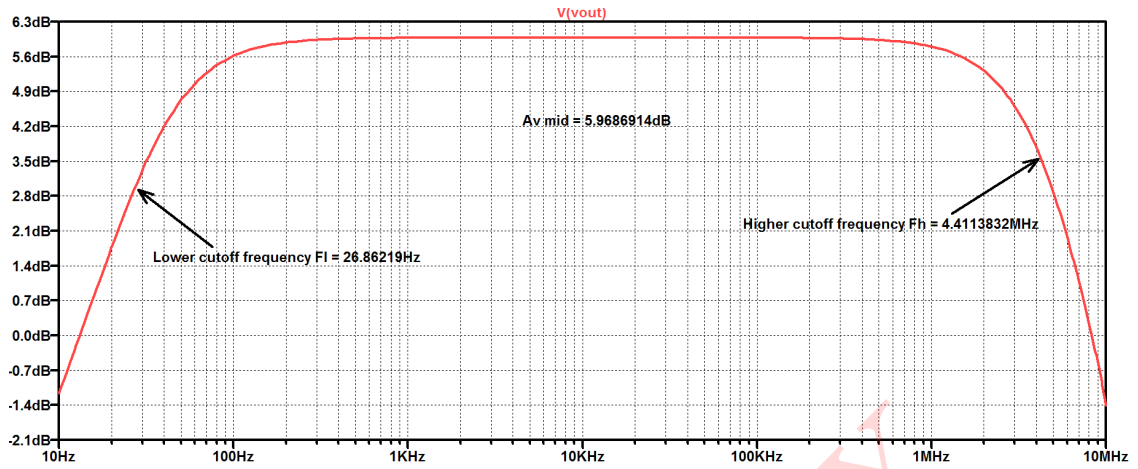


Figure 32: Complete frequency Response

#### Comparison of Theoretical and Simulated Values:

Parameters	Theoretical	Simulated
$I_D, V_{GS}$	$2.065mA, -2.479V$	$2.067mA, -2.481V$
Lower cut-off frequency due to $C_{C1}$	$1.589Hz$	$1.611Hz$
Lower cut-off frequency due to $C_{C2}$	$4.97Hz$	$6.2Hz$
Lower cut-off frequency due to $C_S$	$29.68Hz$	$26.78Hz$
Overall cut-off frequency $f_L$	$29.68Hz$	$26.86Hz$
Mid-band Voltage gain $A_V$ in $dB$	$5.82dB$	$5.96dB$
Overall cut-off frequency $f_H$	$4.39MHz$	$4.41MHz$

Table 3: Numerical 3

\*\*\*\*\*