

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**

**Clipper Circuits**

15<sup>th</sup> June, 2020

Numerical

1. For the circuit shown in circuit 1 Plot:  
Input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms, also VTC curves

**Given:**

$V_{in}(t) = 10V_{p-p}$ , sinusoidal signal with frequency 5000Hz use constant voltage model  
ie  $V_{D(ON)} = 0.7V$ ,  $V_B = 1V$ ,  $R_1 = 1k\Omega$

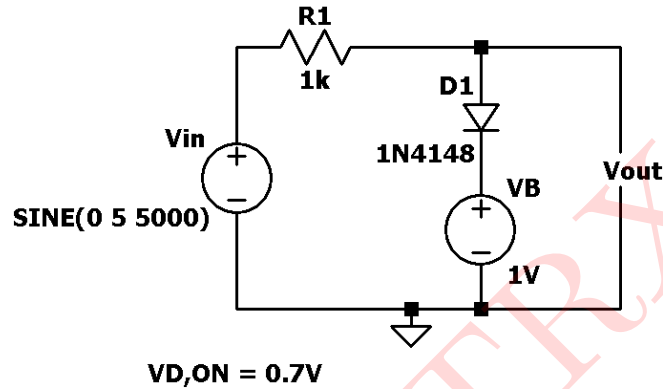


Figure 1: Circuit 1

$$V_{in} = V_m \sin \omega t = 10 \sin(2\pi \times 5000)t = 100 \sin 10000\pi$$

**Solution:**

Assuming a constant voltage model for diode,  $D_1$

**CASE 1:** If  $V_{in} < V_{D(on)} + V_B$  then  $D_1$  is OFF, Therefore Diode  $D_1$  behaves as open circuit as follows

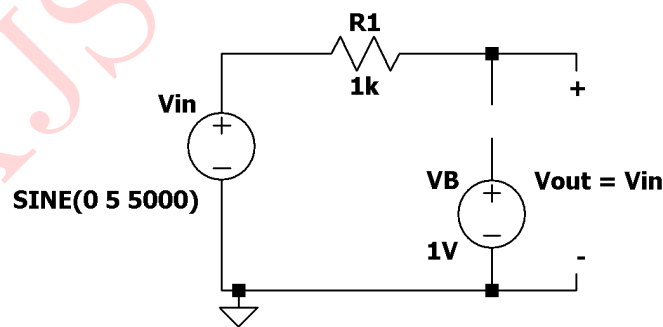


Figure 2: Circuit 1: When Diode 1 is OFF

$$V_{in} < 0.7 + 1$$

$$V_{in} < 1.7$$

$$V_{in} = V_{out} \quad (\text{For } V_{in} < 1.7)$$

**CASE 2:** If  $V_{in} > V_{D(on)} + V_B$  then  $D_1$  is ON, Therefore Diode  $D_1$  behaves shortcircuited as follows

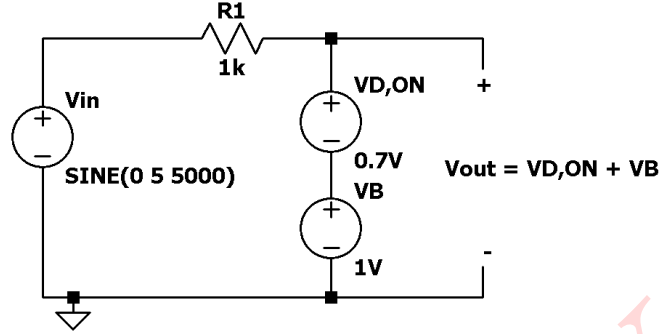


Figure 3: Circuit 1: When Diode 1 is ON

Applying KVL to the output of circuit 1

$$V_{out} = V_{D(on)} + V_B$$

$$V_{out} = 1 + 0.7$$

$$V_{out} = 1.7$$

For  $V_{in} > V_{D(on)} + V_B$

$$V_{in} > V_{D(on)} + V_B$$

$$V_{in} > 0.7 + 1 = 1.7$$

$$V_{out} = 1.7V$$

Thus when  $D_1$  is ON the positive part of the cycle is clipped

### SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

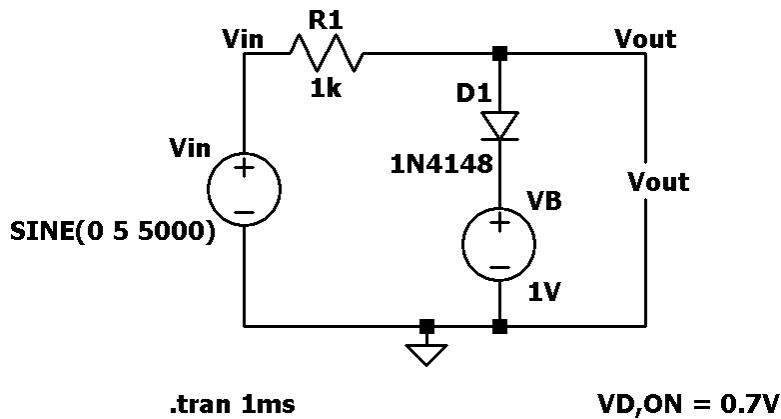


Figure 4: Circuit Schematic: Results

The input and output waveforms are shown in figure 5.

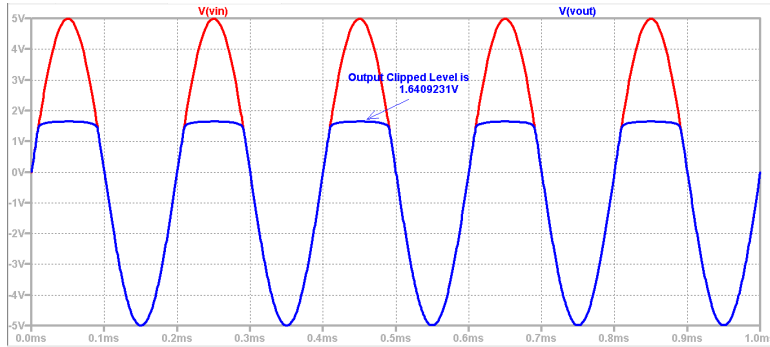


Figure 5: Input and Output Waveform

The VTC curve for the following circuit is given below in figure 6.

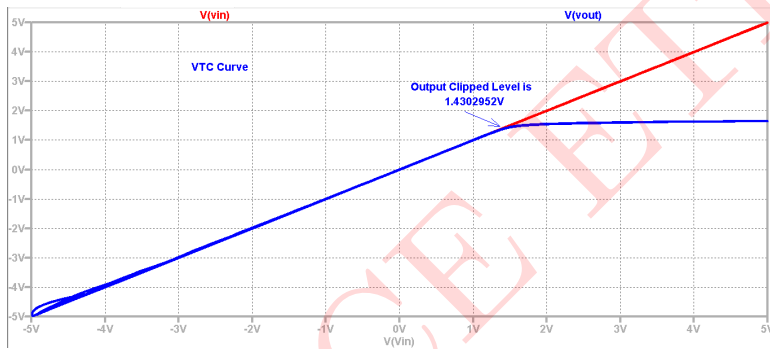


Figure 6: VTC Curve

**Comparison between observed and theoretical values :**

Parameter	Observed	Theoretical
Max value of clipped output voltage	1.64092V	1.7V

Table 1: Numerical 1

2. For the circuit shown in circuit 2 Plot:  
Input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms

**Given:**

$V_{in}(t) = 24V_{p-p}$ , triangular wave with frequency 1000Hz,  $R_1 = 10k\Omega$

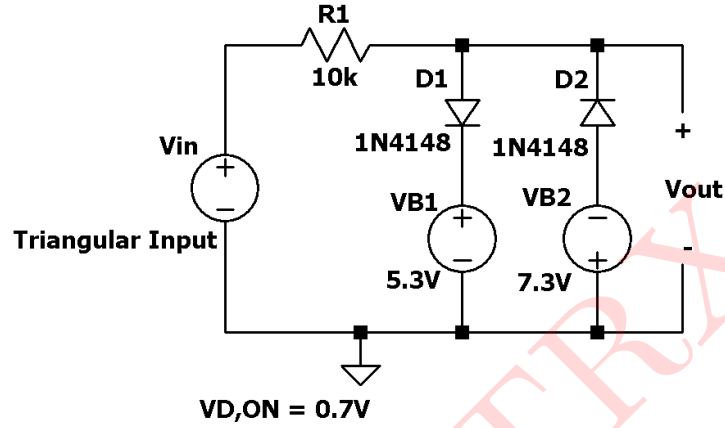


Figure 7: Circuit 2

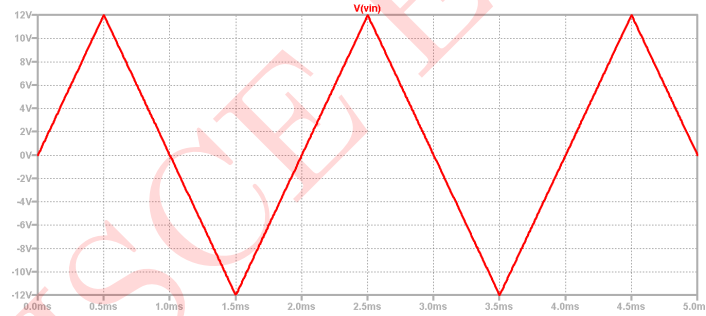


Figure 8: Circuit 2: Input waveform

**Solution:**

The given diodes  $D_1$  and  $D_2$  are silicon diodes and  $V_{D(on)} = 0.7V$ ,  $V_m = 12V$

**CASE 1:** When  $V_{in} > V_{D(on)} + V_B$ ,  $V_{in} > 6V$ , Diode  $D_1$  is forward biased and is ON also diode  $D_2$  is reversed biased and is OFF.

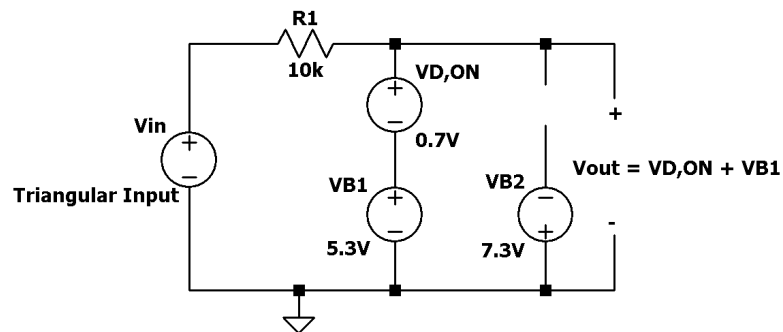


Figure 9: Circuit 2: When Diode 1 is ON and Diode 2 is OFF

The diode  $D_2$  behaves as open circuit while current passes through diode  $D_1$   
 Diode  $D_1$  is ON because the anode voltage is greater than cathode voltage by 0.7V

$$V_{out} = V_{D(on)} + V_{B1}$$

$$V_{out} = 0.7 + 5.3$$

$$V_{out} = 6V$$

$$V_{in} > 6V \quad (V_{in} > V_{D(on)} + V_{B1} = 6V)$$

**CASE 2:** When  $V_{in} < -V_{D(on)} - V_B$ ,  $V_{in} < -8$  V, Diode  $D_1$  is reversed biased and is OFF also diode  $D_2$  is forward biased and is ON.

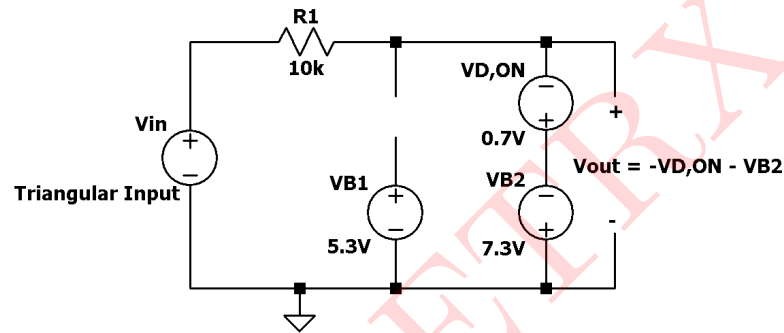


Figure 10: Circuit 2: When Diode 1 is OFF and Diode 2 is ON

The diode  $D_1$  behaves as open circuit while current passes through diode  $D_2$

$$V_{out} = -V_{D(on)} - V_{B2}$$

$$V_{out} = 8V$$

$$\therefore V_{out} \text{ is } -8V \text{ for } V_{in} < -8V$$

For  $V_{out} < 6V$  and  $V_{in} > -8$  both diodes are reversed bias and  $V_{out} = V_{in}$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

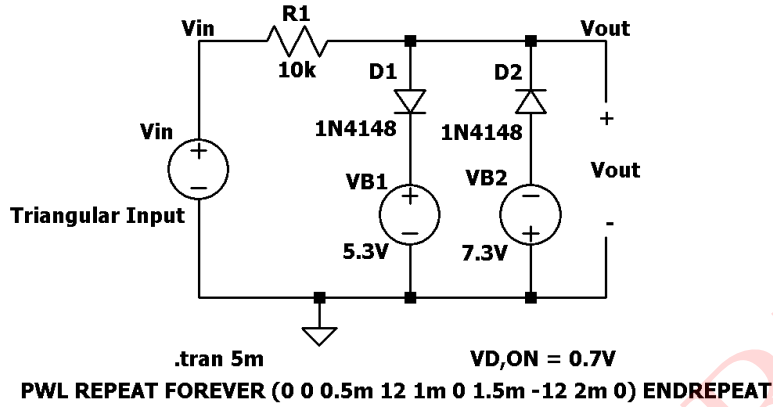


Figure 11: Circuit Schematic: Results

The input and output waveforms are shown in figure 12.

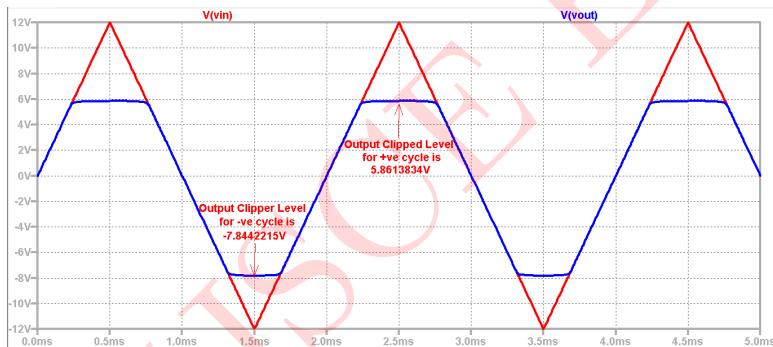


Figure 12: VTC Curve

Comparison between observed and theoretical values :

Parameters	cycles	Observed	Theoretical
Max value of clipped output voltage	positive(+)	5.8613	6V
	negative(-)	-7.8442V	-8V

Table 2: Numerical 2

3. For the circuit shown in circuit 3 Plot:  
Input  $V_{in}(t)$  and output  $V_{out}(t)$  waveforms

**Given:**

$V_{in}(t) = 10V_{p-p}$ , square wave with frequency 1000Hz,  $R = 10k\Omega$ ,  $C = 10\mu F$

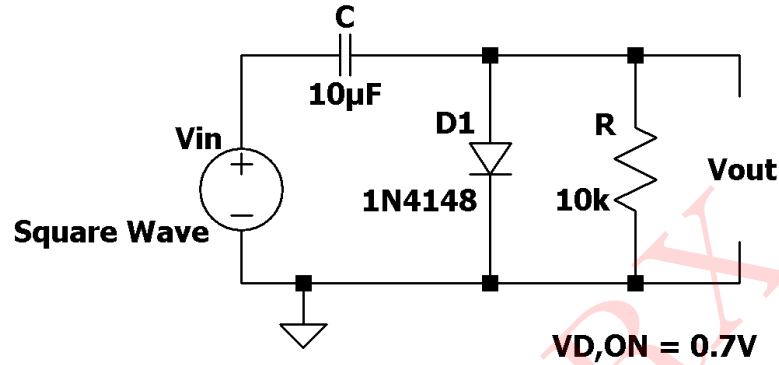


Figure 13: Circuit 3

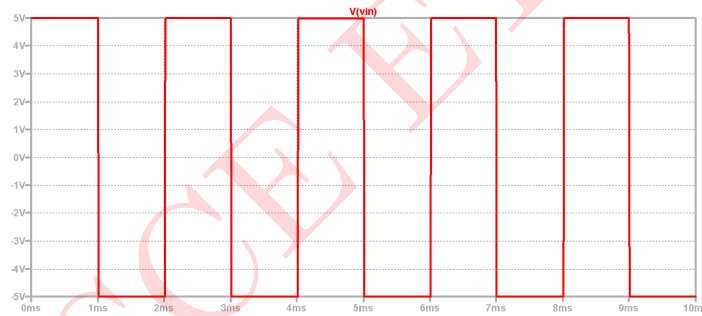


Figure 14: Circuit 3: Input waveform

**Solution:**

The given diode  $D_1$  is a silicon diode we will prefer constant voltage model  $V_{D(on)} = 0.7V$ ,  $V_m = 5V$

**Assumption:** RC time constant is large enough to ensure that voltage across capacitor does not discharge significantly during the period diode is OFF

**CASE 1:** During the positive half cycle Diode  $D_1$  is ON when  $V_{in} > V_{D(on)}$ , When diode  $D_1$  is ON the anode voltage is greater than cathode voltage by  $0.7V$

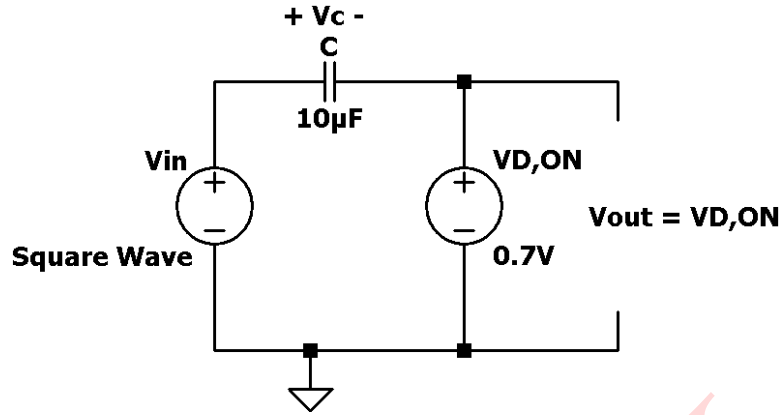


Figure 15: Circuit 3: When Diode D1 is ON

$$V_{out} = V_{D(on)} = 0.7V$$

At the same time Capacitor C charges and voltage across capacitor  $V_C$  reaches output to  $V_m$

Applying KVL on the circuit 1

$$V_{in} - V_{D(on)} - V_C = 0$$

$$V_C = V_{in} - V_{D(on)}$$

$$V_C = 5 - 0.7 = 4.3V$$

**CASE 2:** During negative half cycle diode  $D_1$  is OFF for entire negative cycle

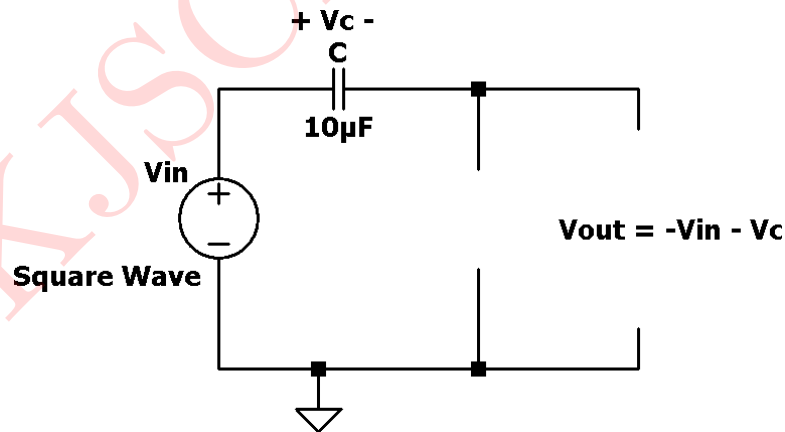


Figure 16: Circuit 3: When Diode D1 is OFF

During negative half cycle capacitor holds the charges  $V_C = 4.3 V$  and acts as a battery or a voltage source

Applying KVL on the given figure

$$V_{in} - V_{out} - V_C = 0$$

$$V_{out} = -V_{in} - V_C$$

$$V_{out} = -5 - 4.3$$

$$V_{out} = -9.3V$$



### SIMULATED RESULTS:

Above circuit is simulated in LTspice and results are as follows

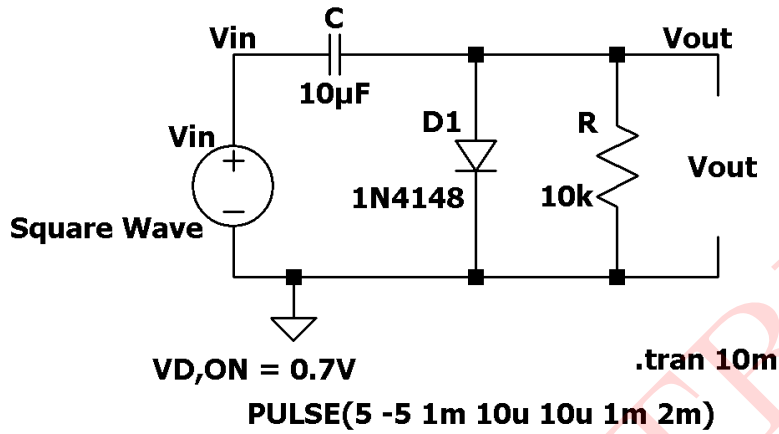


Figure 17: Circuit Schematic: Results

The input and output waveforms are shown in figure 18.

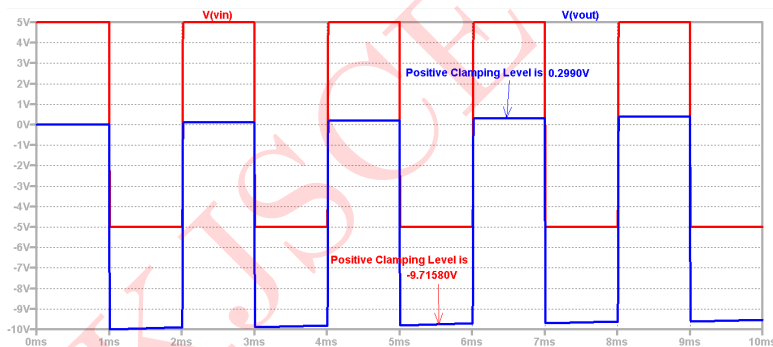


Figure 18: VTC Curve

### Comparison between observed and theoretical values :

Parameters	cycles	Observed	Theoretical
Max value of clipped output voltage	positive(+)	0.299V	0.7V
	negative(-)	-9.715V	-9.3V

Table 3: Numerical 3

\*\*\*\*\*